

This is a digital copy of a book that was preserved for generations on library shelves before it was carefully scanned by Google as part of a project to make the world's books discoverable online.

It has survived long enough for the copyright to expire and the book to enter the public domain. A public domain book is one that was never subject to copyright or whose legal copyright term has expired. Whether a book is in the public domain may vary country to country. Public domain books are our gateways to the past, representing a wealth of history, culture and knowledge that's often difficult to discover.

Marks, notations and other marginalia present in the original volume will appear in this file - a reminder of this book's long journey from the publisher to a library and finally to you.

### Usage guidelines

Google is proud to partner with libraries to digitize public domain materials and make them widely accessible. Public domain books belong to the public and we are merely their custodians. Nevertheless, this work is expensive, so in order to keep providing this resource, we have taken steps to prevent abuse by commercial parties, including placing technical restrictions on automated querying.

We also ask that you:

- + *Make non-commercial use of the files* We designed Google Book Search for use by individuals, and we request that you use these files for personal, non-commercial purposes.
- + Refrain from automated querying Do not send automated queries of any sort to Google's system: If you are conducting research on machine translation, optical character recognition or other areas where access to a large amount of text is helpful, please contact us. We encourage the use of public domain materials for these purposes and may be able to help.
- + *Maintain attribution* The Google "watermark" you see on each file is essential for informing people about this project and helping them find additional materials through Google Book Search. Please do not remove it.
- + *Keep it legal* Whatever your use, remember that you are responsible for ensuring that what you are doing is legal. Do not assume that just because we believe a book is in the public domain for users in the United States, that the work is also in the public domain for users in other countries. Whether a book is still in copyright varies from country to country, and we can't offer guidance on whether any specific use of any specific book is allowed. Please do not assume that a book's appearance in Google Book Search means it can be used in any manner anywhere in the world. Copyright infringement liability can be quite severe.

#### **About Google Book Search**

Google's mission is to organize the world's information and to make it universally accessible and useful. Google Book Search helps readers discover the world's books while helping authors and publishers reach new audiences. You can search through the full text of this book on the web at http://books.google.com/









Copyright, 1918, 1919, 1920, 1922 by AMERICAN TECHNICAL SOCIETY

> Copyrighted in Great Britain All Rights Reserved





.



## **CONTENTS**

Sources of current (continued)	1	PAGE
D:-:		
Sources of current (continued) Dixie magneto. Magnetos for eight- and twelve-cylinder	· · · · · · · · · · · · · · · · · · ·	IIZ
Magnetos for eight- and twelve-cylinde	er motors	115
ignition systems		117
Dual ignition system	· · · · · · · · · · · · · · · · · · ·	118
Duplex ignition system		123
Double-spark ignition		124
Ford magneto	· · · · · · · · · · · · · · · · · · ·	124
Spark timingAdvance and retard	· · · · · · · · · · · · · · · · · · ·	129
Advance and retard		129
Magneto speeds Ignition system fixed timing point		137
Ignition system fixed timing point	· · · · · · · · · · · · · · · · · · ·	138
Automatically timed systems		138
Firing Order Typical firing orders Firing orders and ignition advance for Wiring	• • • • • • • • • • • • • • • • • • • •	143
l ypical firing orders	1:a	143
riring orders and ignition advance for	different motors	14/
Wiring		102
Magneto mounting		170
Modern battery ignition systems.  Effect of starting and lighting development		1/2
Westinghouse ignition unit	nents on ignition	1/2
Atunton Vant ameters	• • • • • • • • • • • • • • • • • • • •	177
Atwater Kent system Connecticut battery system	• • • • • • • • • • • • • • • • • • • •	170
Dominion Dattery system		1/7
Remy system Delco system Testing, adjustment, and maintenan Testing		102
Testing adjustment and maintenant		107
Testing, adjustment, and maintenan	ice	107
Solving troubles		100
Solving troubles Ignition instructions		205
Electric Starting and	Lighting Systems	
C164		
C. J		275
Single wine and two wine eventure		275
		275 275 273
Constant surrent senerator		275 275 277 281
Constant-current generator		275 275 277 281
Constant-current generator Output of generator Automatic battery cut-out		275 275 277 277 281 282 288
General features Fundamental characteristics Single-wire and two-wire systems Constant-current generator Output of generator Automatic battery cut-out		275 275 277 281 282 288 289
Constant-current generator Output of generator Automatic battery cut-out Circuit-breaker Requirements in design		275 275 277 281 282 288 289 292
Requirements in design		<del>207</del> 292
Requirements in design Installation		292 296
Circuit-oreaker Requirements in design Installation Driving connections		292 296 296 299 300
Circuit-oreaker Requirements in design Installation Driving connections Automatic engagement		292 296 296 299 300
Circuit-preaker Requirements in design Installation Driving connections Automatic engagement Clutches Back-kick releases		292 296 296 299 300
Requirements in design Installation Driving connections Automatic engagement Clutches Back-kick releases		292 296 299 300 301 303
Requirements in design Installation Driving connections Automatic engagement Clutches Back-kick releases		292 296 299 300 301 303 304 310
Requirements in design Installation Driving connections Automatic engagement Clutches Back-kick releases		292 296 299 300 301 303 304 310
Requirements in design Installation Driving connections Automatic engagement Clutches Back-kick releases		292 296 299 300 301 303 304 310 312
Requirements in design Installation Driving connections Automatic engagement Clutches Back-kick releases		292 296 299 300 301 303 304 310 312 312
Requirements in design Installation Driving connections Automatic engagement Clutches Back-kick releases		299 296 299 300 301 303 304 310 312 313
Requirements in design Installation Driving connections Automatic engagement Clutches Back-kick releases		292 296 299 300 301 303 304 310 312 312 313
Circuit-preaser Requirements in design Installation Driving connections Automatic engagement Clutches Back-kick releases Switches Electric horns Lighting equipment Incandescent lamps Lamp voltages Reflectors Headlight glare Dimming devices		299 299 296 299 300 301 303 304 310 312 313 314 315 316
Circuit-preaser Requirements in design Installation Driving connections Automatic engagement Clutches Back-kick releases Switches Electric horns Lighting equipment Incandescent lamps Lamp voltages Reflectors Headlight glare Dimming devices		299 299 296 299 300 301 303 304 310 312 313 314 315 316 318
Requirements in design Installation Driving connections Automatic engagement Clutches Back-kick releases Switches Electric horns Lighting equipment Incandescent lamps Lamp voltages Headlight glare Dimming devices Practical analysis of starting and ligh	nting types	299 299 299 300 301 303 304 310 312 313 314 315 316 318
Requirements in design Installation Driving connections Automatic engagement Clutches Back-kick releases Switches Electric horns Lighting equipment Incandescent lamps Lamp voltages Headlight glare Dimming devices Practical analysis of starting and ligh	nting types	299 299 299 300 301 303 304 310 312 313 314 315 316 318 321
Requirements in design Installation Driving connections Automatic engagement Clutches Back-kick releases Switches Electric horns Lighting equipment Incandescent lamps Lamp voltages Headlight glare Dimming devices Practical analysis of starting and ligh	nting types	299 299 299 300 301 303 304 312 313 314 315 316 318 321
Requirements in design Installation Driving connections Automatic engagement Clutches Back-kick releases Switches Electric horns Lighting equipment Incandescent lamps Lamp voltages Headlight glare Dimming devices Practical analysis of starting and ligh	nting types	299 299 299 300 301 303 312 312 313 314 315 316 318 321 325 325
Requirements in design Installation Driving connections Automatic engagement Clutches Back-kick releases Switches Electric horns Lighting equipment Incandescent lamps Lamp voltages Reflectors Headlight glare Dimming devices Practical analysis of starting and ligh Buick-Delco type Auburn-Delco type Chevrolet-Auto-Lite type Jeffery-Bijur type Circuit-breaker	nting types	299 299 299 300 301 303 304 312 313 314 315 316 318 321





WEIDENHOFF ELECTRICAL TEST BENCH COMPLETE



to give more than the usual amount of attention and study to this branch of the subject.

# **ELEMENTARY ELECTRICAL PRINCIPLES**

Knowledge of Principles Necessary. To acquire a good practical working knowledge of electricity as applied to the automobile today, it is essential not merely to find out how things are done, either by watching the other fellow do them, or by studying "pictures in a book", but also to learn why certain things are done and why they are carried out in just such a way. In other words, the man whose knowledge is based upon theory and principles applies knowingly the cause to produce the effect and is certain that the desired effect will be produced. On the other hand, the man who works only with his hands aimlessly goes from one thing to another trusting chiefly to luck to accomplish two things. One of these is to strike upon the remedy for the trouble the cause of which is sought, and the other is to deceive the spectator—usually the owner of the car—into believing that the fumbler really knows what he is about.

There are accordingly two distinct classes of knowledge as regards the electrical equipment of an automobile—one which is picked up by rote, an isolated point at a time, and applied in the same manner, and the other which is based upon a clear insight into the underlying reasons for the various actions and reactions that make up the different electrical phenomena involved. If we want to know what is wrong with an electric motor, it is essential that we should know what makes an electric motor operate when everything is right. In the same way, it would be groping in the dark to attempt to investigate the reasons for the failure of a dynamo to generate current, or a storage battery to give up its charge, if we had no knowledge of why a dynamo, when run by an outside source of energy, normally produces a current, or why an accumulator literally "gives back" what has been put into it when its circuit is closed after charging.

It will accordingly be the function of this introductory chapter to give a brief résumé of the principles underlying the operation of what has come to be the most important auxiliary of the gasoline motor as applied to the automobile—its electrical equipment.



of a duct for the admission of more air under the impulse of a powerful compressor, in a very short time there will be a marked difference between the air in this room and the air in the other rooms. Instead of the normal atmospheric pressure of 15 pounds per square inch, there will be a pressure against all parts of the room—floor, walk, and ceiling—of 50, 60, or 100 pounds, according to the length of time the compressor has been working and the degree of tightness with which the various openings have been closed. Thus there will be a great deal more air in the one room than in its neighbors. If it were electricity instead of air, the room would be said to be highly charged.

The air in this room, on account of the pressure which it is under, is constantly seeking an outlet, and it will gradually leak out through various small openings, probably without its escape being noticed. The same conditions obtain when a body become electrified beyond its capacity to hold a charge—the charge of electricity will leak away without giving any indication of its passing. Turning again to the room containing the compressed air, if a door or window of that room is opened suddenly, the pressure is immediately released through that opening and anyone standing in front of it would say that a strong current of air blew out. In the case of electricity, if any easy path of escape is provided, the entire charge will rush away from the body, and there is then said to be a current of electricity "flowing" from this point of escape to whatever other object equalizes the pressure by becoming charged. An electric current is accordingly electricity in motion; it is simply said to flow. But to cause it to do so there must be pressure. electrical term for this pressure is potential or voltage.

Electrical Pressure. Every day in the year the earth transmits a greater or less proportion of its electrical charge to the atmosphere, or receives a charge from the latter, but unless the conditions are favorable there is no visible indication of this difference of potential as it is termed. It must be borne in mind that this difference of potential, or difference in electrical pressure, between two points is what causes a current to flow. Given a hot day in summer, however, when the air is heavily charged with moisture and low cumuli, or rain-charged clouds form in great masses, then the electrical charges from the earth and the air accumulate in these



As a practical application of the preceding formula, take the case of a small conductor connecting the battery and starting motor of the electrical starting system on an automobile. The diameter of the wire is such that the length required to connect the two points has a resistance of 10 ohms. One ampere is that amount of current which will pass through a conductor having a resistance of one ohm under a pressure of one volt. The starting system in question operates at 6 volts. Hence,  $I = \frac{1}{10} = .6$ , that is, the battery would be able to force only .6 ampere through that small wire, and the starting motor would not operate.

It is apparent from the foregoing that the formula for Ohm's law may be transposed to find any one of the three factors that may be unknown. For example, given the conditions just mertioned, we may determine how much resistance the wire in question has. The resistance equals the voltage divided by the current: that is,  $R = \frac{E}{I}$ , or resistance equals  $\frac{6}{.6} = 10$  ohms. Or again, if it is desired to learn what voltage is necessary to send a current of f ampere through a resistance of 10 ohms, the solution calls for an equally simple transposition of the formula. Given any two factors, then the third may be readily determined.

Ohm's law is absolutely fundamental in all things pertaining to electrical operation, and the man who wants to make his knowledge of the greatest practical use will do well to familiarize himself with it. Naturally it does not enter into repair work to more than a small fraction of the extent that it enters into the design of motors, generators, and other electrical devices, but a knowledge of it is of distinct value.

Power Unit. To go back to the simile of air under pressure, it is apparent that the energy released by the lowering of this pressure may be made to perform useful work, such as driving a compressed-air drill, running a small air motor, or the like. So with the electric circuit, the drop from a higher to a lower potential, which causes a current to flow, is a source of power. Electrical power is the product of the amperage or current multiplied by the voltage at which it is applied. The power unit is the watt and it is equivalent to one ampere of current flowing under a pressure, or potential, of one volt. There are 746 watts in a horsepower.

Electrical computations, however, are based on the metric system to a large extent, so that instead of being figured in horsepower, electrical energy is figured by the kilowatt, or a unit containing one thousand watts, and the charge therefor is based upon the length of time for which this amount of energy is employed. From this comes the now familiar expression "kilowatt-hour".

The power equivalent is expressed as  $P = I \times E$ , current multiplied by electromotive force (potential), and, as in the case of Ohm's law, with any two of the factors given, the third may be readily determined. For example: How much power is developed by a 6-volt starting motor if 125 amperes of current are necessary to turn the automobile engine over fast enough to start it? The amount of current given is an arbitrary average taken simply for the purpose of illustration, for in overcoming the inertia of an automobile engine a great deal of current is required at first, the drain on the battery often exceeding 250 amperes for a few seconds, then dropping as the engine turns over to about 50 or 60 amperes. Taking 125 as the average, we have  $125 \times 6 = 750$  watts = .75 kilowatt, or slightly over one horsepower.

Granting that one horsepower is necessary to turn over a 3½ by 4-inch six-cylinder motor at 75 r.p.m.—a speed that has been predetermined as necessary to cause it to take up its own cycle under the most adverse starting conditions—and given a 6-cell storage battery capable of developing a potential of 12 volts, then

we have:  $I = \frac{P}{E}$ , or current =  $\frac{746}{12} = 62.1 + \text{ amperes, which represent}$ 

the average demand upon the storage battery to start that engine under normal conditions. This illustration and the previous one show the working of Ohm's law; doubling the voltage halves the amount of current necessary. As the life of a storage battery is largely determined by the rapidity as well as by the number of its discharges, and as the storage battery is the weakest element in any electric lighting-and-starting system, it may well be asked why the 12-volt standard is not universally adopted, or why, as is done in some cases, a 24-volt battery is not employed and the current consumption again reduced by half. Just why this is not done is explained in detail in the section on the voltages employed in electric starters generally.

Conductors. To lead steam or air under pressure from boiler or compressed-air reservoir to the point at which it is to utilized as energy, it is desirable to use a conductor that will waste too much of this energy in useless friction. That is, conductor must be of ample size in proportion to the volume be conveyed, smooth in bore, and free from sharp turns or ber The transmission of electrical energy involves some of the structures. While neither the smoothness of the bore nor the press of bends and turns has any effect, they have their counterprine in the conductivity of the material of which the wire is made, size of the wire in proportion to the amount of current to be car being also a matter of prime importance.

Resistance of Materials. Materials differ greatly in t ability to conduct an electric current, or, to put it the other around, they differ in the amount of resistance that they offer the passage of the current. Silver in its pure state heads the in the table of relative conductivities, and it is accordingly to possess a relative resistance of one, or unity; the resistance every other material may be expressed by a number which resents the resistance of that particular substance as compared v pure silver. Naturally silver does not represent a great possibi for commercial use, and so copper, which is second on the list almost universally employed. Pure copper is very soft and lacking in tensile strength; it is therefore alloyed, and it is a hardened in the drawing process; both of these processes incre its resistance slightly over the factor usually accorded it in standard table of specific conductivities of materials. table, German silver (which is an alloy containing no silver whate and having but a few of its properties), cast iron, steel, carb and similar substances will be found well down toward the e They are known as "high-resistance" conductors and are usus used where a certain amount of resistance to the current is desiral

It must be borne in mind that ability to conduct a given amout of current without undue loss through resistance depends up the size and the length of the conductor quite as much as up the material. In other words, if a steel rail is only one-thirtical good a conductor as a copper cable, it will require a cross-section of steel thirty times as great as that of a copper cable in order

conduct the current with the same ease—that is, to make a conductor of equal resistance. An illustration of this may be seen in the overhead copper wire of the usual trolley system. This wire of about one-half inch diameter forms one of the conductors, while the two steel rails form the "return". A similar example may be found in what is known as the single-wire system of installation for an electric starter in automobiles. A single copper cable conducts the current from the battery to the starting motor, while the steel frame of the automobile is the return side of the circuit, or vice versa.

Voltage Drop. It is evident that the resistance of a circuit varies inversely as the size of the conductor—the larger the cross-section of a conductor, the less its resistance—and increases directly as its length, besides depending upon the specific resistance of the material. The specific resistance of the metals constituting electrical circuits on the automobile are (silver being 1.0); copper 1.13, varying more or less with its hardness; aluminum 2.0; soft iron 7.40; and hard steel 21.0. Thus, 9.35 feet of No. 30 copper wire are required for a resistance of one ohm, while only 5.9 inches of hard steel wire of the same gage are required to present the same amount of resistance to the current. If the length of the conductor is doubled, its resistance is doubled, which accounts for the placing of the storage battery as close as possible to the starting motor. Furthermore, the heavy starting currents which are required by the motor demand the use of heavy copper cable for this circuit.

We true wises are of the control but the hut to be a second in

have a negative temperature coefficient, that is, they decrease in resistance with an increase in temperature.

It is consequently necessary to employ wires of proper size to carry the amount of current required by the apparatus in circuit -such as lamps-without undue heating, which would cut down the amount of current flowing. For the same reason it is also desirable to make the circuits as short as practicable, since in addition to cutting down the current, the resistance also cuts down the effective voltage. That is, there is a fall of potential, or drop in voltage, between the source of current supply and the apparatus utilizing it, due to the resistance of the conductors between them. This voltage drop is further increased by joints in the wiring and by switches. It is apparent that the lower the voltage of the source of supply, the more important it becomes to minimize the loss. or voltage drop, in the various circuits. For this reason lighting or other circuits on the automobile should never be lengthened where avoidable. When necessary to extend a circuit for any reason, wire of the same diameter and character of insulation as that forming the original circuit must be employed, and the joints should be as few as possible, all mechanically tight, and well soldered. The voltages employed in the electrical systems of automobiles are so low--varying from 6 to 24 volts, with a strong\_tendency to standardize the 6-volt system—that any increased resistance is likely to cause unsatisfactory operation.

Non-Conductors. In going down through a table of specific conductivities of various materials, the vanishing point is reached with those that cease to be conductors at all. Such materials are known as nonconductors or insulators, and some substances vary in the degree of insulation they afford quite as much as other materials do in their ability to conduct a current. Glass, rubber, shellac, oil, paraffin wax, wood, and fabrics are all good insulators when perfectly dry. Distilled water has such a high resistance as to be almost an insulator, but in its natural state water contains alkaline salts or other impurities that make it a conductor. Consequently, when any otherwise good insulating substance is wet, the current is likely to leak across the wet surface of the insulator. This is particularly the case with a current of high potential, or high tension, and explains why it is of the greatest importance

to keep all parts of the secondary side of the ignition system perfectly dry. The potential which causes the current to arc across the gap of the spark plug is so high that it will leak across even slightly damp surfaces, such as the porcelains of the plugs. This leakage is often visible, especially in the dark, and it may also be detected by placing the bare hand on the porcelain.

Just as the amount of current to be carried determines the size of the conductor to be employed, so the potential or pressure under which this current is transmitted determines the amount of insulation that will be necessary. The latter is also affected, however, by mechanical reasons, for example, by the liability of the conductor to chafing or abrasion. The best grades of copper cable employed for both ignition and starting-lighting systems on automobiles today are stranded, that is, composed of a number of fine wires, to make them flexible. The stranded cable is then tinned to prevent corrosion due to the sulphur in the insulation, after which it is covered with a soft-rubber compound of a thickness dependent upon the purpose for which the wire is intended. For hightension ignition wire this rubber covering is about three-sixteenth inch thick. This covering is vulcanized and is then further protected by braided linen, or silk-cotton thread which is made waterproof by being impregnated with shellac or some other insulating compound.

Circuits. When air under high pressure escapes from its container, it simply mingles with the atmosphere, and as soon as the difference in pressure is equalized there is no distinction between it and air in general. But to equalize a difference in potential of an electric current there must be a conducting path between the points of high and low potential. This is termed a circuit. Current to operate trolley cars is fed to the motors of the car from the overhead wire and returns through the tracks to the generators at the power house. This is known as a ground-return circuit. In the single-wire electric starting system of an automobile, current from the storage battery reaches the starting motor through the starting switch and a single heavy cable, and returns through the frame and other metal parts of the car itself, or vice versa. This is another instance of a ground-return circuit.

Both the primary and secondary sides of the ignition system of an automobile are also grounded circuits. In contrast with

this, the circuit may be composed of copper cables directly connecting both poles of the battery and switch with the starting motor. The highly insulated cable employed for both ignition and starting systems is expensive and the use of a single wire greatly simplifies the connections, considerations which account for the general use of this type of circuit. A circuit is said to be open when there is a break in it which prevents the current from flowing, as

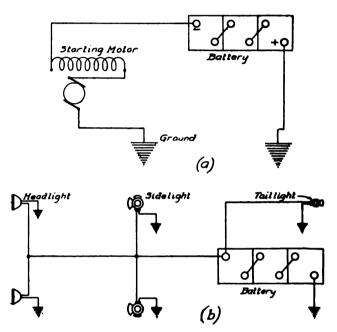


Fig. 1. Typical Starting-Lighting Wiring Diagrams. (a) Series Circuit of Starting Motor; (b) Multiple Circuit of Lamps

when the switch is opened, or when a connection or the wire itself is broken.

Series Circuit. The connections between a storage battery, switch, and starting motor, comprise the simplest form of circuit, in which the motor is said to be in series with the battery, and the cells of the battery are in series with one another. This is termed a series circuit and a break in it at any point opens the entire circuit. The starting motor, Fig. 1 (a), requires the entire output of the storage battery for its operation.

ne circuit and to return on the negative side. In the case of a s circuit as described, the current flows through each piece pparatus in turn; each receives all the current in the circuit potential proportioned to the resistance of the apparatus in tion. For example, in the simple starter circuit referred to be the starting motor receives the entire output of the 3-cell age battery at its full voltage of 6 volts, less the drop in voltage to the resistance of the circuit. If there were two starting pers instead of one in the circuit, both in series, both would ive all the current but at only half the voltage.

Multiple or Shunt Circuit. As opposed to this, in a multiple sit, Fig. 1 (b), in which every piece of apparatus is connected to sides of the circuit "in parallel", each piece of apparatus in circuit receives current at the same voltage but draws from circuit the current determined by its resistance. The failure or drawal of any one or more instruments in a multiple or parallel sit has no effect on those remaining. The lighting circuits n automobile equipped with a 6-volt starting system are an apple of this. Each lamp is designed to burn to its maximum sination at 6 volts, but the 25-candle-power headlights take current than the 5-candle-power side lights or the 2-candle-r taillight, owing to the difference in the size and resistance of

tiple circuit of its own, and these two groups are connected in series so that the lamps in each circuit receive 6 volts, but the circuit as a whole takes the battery current at 12 volts. Such a combination

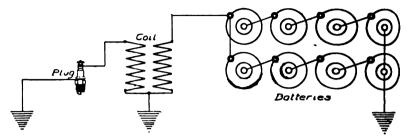


Fig. 2. Dry Cells in Series-Multiple for Ignition Circuit

is known as a series-parallel or series-multiple circuit and is more or less commonly used for connecting dry cells for ignition use, Fig. 2.

Circuits may also be in parallel, that is, practically a circuit on a circuit. The method of connecting up the voltmeter that is mounted on the dash of the car is an instance of this, a wire being led from each side of the main circuit to the instrument. The instrument is then said to be in shunt, Fig. 3, and the amount of current that is diverted to it is entirely dependent on the resistance. As a voltmeter is wound to a high resistance, Fig. 4, it is designed to take very little current for its operation. The

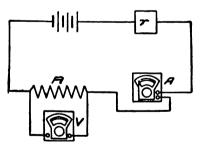


Fig. 3. Diagram Showing How Voltmeter Is Shunted in the Circuit

ammeter, Fig. 5, on the other hand, is intended to indicate the entire current output of the generator on charge or discharge, and is accordingly connected in series so that all the current passes through

it. (Owing to the heavy rush of current taken by a starting motor in overcoming the inertia of the gasoline engine, the ammeter is

not included in this circuit.)

Short-Circuits and Grounds. The previous paragraphs have made clear the necessity for having a complete path or circuit for the current in order that its power may be utilized. There must be a connecting cable on one side and there must be a return on the other (grounded circuit). If instead of passing through the apparatus. such as the starting motor. the current finds an easier path through an abrasion in the insulation of the cable and some metal part against which that touches, it is said to be short-circuited. where a stripped cable


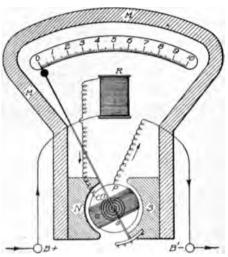


Fig. 4. Diagram of Voltmeter Principle

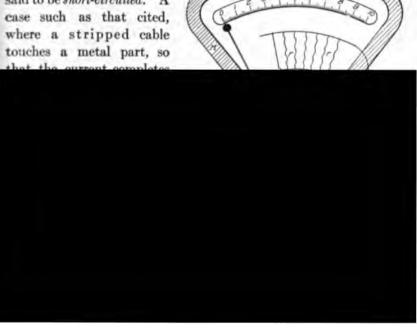

all short circuits are grounds, as short circuits may occur from many other causes—for instance, where two wires touch at uninsulated points or where stray metal makes contact with connections, etc.

Size of Conductors. The influence of the factor of resistance makes plain the reason for using wires of different sizes for the various circuits of the ignition starting and lighting systems of the automobile. If an ample flow of compressed air is desired for power purposes, a liberal outlet must be provided, while if only a small spray is required, as for cleaning purposes, a small-bore tube will suffice. If we try to employ the small-tube line for power purposes, we shall not gain the desired result because its resistance is so great that it will not permit a sufficient flow of air. For the same reason a conductor of much larger diameter and, therefore, of correspondingly low resistance must be employed to handle the heavy current necessary to operate the electric starting motor, that is needed for the comparatively small current which is demanded by the ignition system.

Whether it is mechanical or electrical in its nature, the power necessary to overcome resistance is liberated in the form of heat Mechanical resistance is friction and its presence between moving bodies always generates heat. Electrical resistance may, for the purpose of illustration, be termed internal or molecular friction. and it also results in heat. The extent of the rise in temperature of a conductor or wire, depends entirely upon the proportion that its size and, consequently, its current-carrying ability bear to the amount of current that is sent through it. Roughly speaking. a wire is three-fourths the size it should be to carry the starting current, it will become uncomfortably warm to the hand after the motor has been operated several times in succession. If it is only one-half the size it should be, continuous operation of the starting motor for a few minutes will doubtless burn off most of the insulation. Further reducing its size would cause the wire to become so hot as to set fire to the insulation the moment the current was turned on, and any great decrease in diameter would result in the immediate fusing of the wire itself. The wire would literally "burn up" and in a flash.

It would not be practical to attempt to conduct live steam

TABLE I
American Wire Gage (B. & S.)

No.	DIAMETER IN		Circular	Ohms	N	DIAMETER IN		Circular	Ohms
	Mils	Mm.	Mila	1000 Ft.	No.	Mils	Mm.	Mila	per 1000 Ft.
0000	460.00	11.684	211600.0	.051	19	35.89	.912	1288.0	8.617
000	409.64	10.405	167805.0	.064	20	31.96	.812	1021.5	10.566
00	364.80	9.266	133079.4	.081	21	28.46	.723	810.1	13.323
0	324.95	8.254	105592.5	.102	22	25.35	.644	642.7	16.799
1	289.30	7.348	83694.2	.129	23	22.57	.573	509.5	21.185
2	257.63	6.544	66373.0	.163	24	20.10	.511	404.0	26.713
3	229.42	5.827	52634.0	.205	25	17.90	.455	320.4	33.684
4	204.31	5.189	41742.0	.259	26	15.94	.405	254.0	42.477
5	181.94	4.621	33102.0	.326	27	14.19	.361	201.5	53.563
6	162.02	4.115	26250.5	.411	28	12.64	.321	159.8	67.542
7	144.28	3.665	20816.0	.519	29	11.26	.286	126.7	85.170
8	128.49	3.264	16509.0	.654	30	10.03	.255	100.5	107.391
9	114.43	2.907	13094.0	.824	31	8.93	.277	79.7	135.402
10	101.89	2.588	10381.0	1.040	<b>32</b>	7.95	.202	63.2	170.765
11	90.74	2.305	8234.0	1.311	33	7.08	.108	50.1	215.312
12	80.81	2.053	6529.9	1.653	34	6.30	.160	39.7	271.583
13	71.96	1.828	5178.4	2.084	35	5.61	.143	31.5	342.433
14	64.08	1.628	4106.8	2.628	36	5.00	.127	25.0	431.712
15	57.07	1.450	3256.7	3.314	37	4.45	.113	19.8	544.287
16	50.82	1.291	2582.9	4.179	38	3.96	.101	15.7	686.511
17	45.26	1.150	2048.2	5.269	39	3.53	.090	12.5	865.046
18	40.30	1.024	1624.1	6.645	40	3.14	.080	9.9	1091.865

t high pressure through a cardboard tube. Nor is it any more o to attempt to send a heavy current through "any old piece of rire". Electric lighting and starting systems as they exist on cars oday are of all degrees of merit. The cars themselves have reached stage of reliability where their useful life is now on the average

com five to ten years or more. Consequently there are a great

Heating Effect of Current. The amount of heat that a given current will produce in passing through a conductor of a certain size is expressed by Joule's law: The number of heat units developed in a conductor is proportionate to its resistance, to the square of the current, and to the time that the current lasts.

The heat generated, therefore, increases in direct proportion to the resistance. For example, if the cable between the starting motor and the battery be replaced by one-half its size, the resistant will be doubled and the heat generated will increase in the same no portion, the current remaining the same in both instances. the current, however, adds to the amount of heat generated, as the square of the increase. Thus, if with the original starting cable show mentioned, the amount of current necessary to start the motor has to be doubled, owing to gummed lubricating oil or stiff bearings, the volume of heat generated will increase fourfold. The amount of heat generated also increases in direct proportion to the time that the current lasts. It will be easy to realize from this why abnormal conditions may quickly bring the heating effect of the current to a point where the insulation of the wires, or even the wires themselves. may be endangered. For instance, in the case of a motor that is very hard to start, the discharge from the battery is greatly increased in turning it over, and the starting motor must be operated for a ver much longer period to get the engine under way, causing a direct increase in the heating effect, due to the longer time that the current is passing through the cable, and a fourfold increase for the additional current necessary.

Heat Generated in Starting Motor. Take the case of a motor that requires 150 amperes for the first few seconds and 50 amperes once the engine is turning over freely. If stiff bearings or gummed oil cause the initial current to rise to 200 amperes and the running current to 80 amperes for a period three times as long as would ordinarily be required to start, there will be a very considerable increase in the number of heat units generated. This is one of the reasons why it is good practice to use the starting motor intermittently when the engine does not at once fire and take up its own cycle, instead of running the starting motor continuously until the engine begins to fire and generate its own power. A much more important reason, however, is the fact that the intermittent use of the starting motor

is not nearly so hard on the battery, as the storage battery recuperates very quickly when given short periods of rest between the demands for its power. Running the starting motor for ten periods of 30 seconds each, with a like interval between the attempts to start, will not discharge the battery anything like as much as will operating the starting motor continuously for five minutes. A longer rest between trials will be of greater benefit to the battery.

Heating Effect on Lamps and Fuses. It must not be concluded from the above that the heating effect of the current is always detrimental, as it is taken advantage of in many ways. Two of the commonest of these are the incandescent lamp and the fuse. In the case of the former, the increase in heat with an increase in resistance is mainly depended upon, the filament being made of such a size that a given amount of current at a certain voltage will just bring it to incandescence. For this reason an increase in the current, or voltage. will burn the filament and destroy the lamp. The fact that the heating effect increases as the square of the current is taken advantage of in the design of fuses which are made of soft alloys that will melt at comparatively low temperatures. Resistance is also a factor in the fuse, as in cutting down the cross-section of the fusible wire the resistance is increased, while the current-carrying capacity of the wire is The cross-section, or diameter, of the fuse is gaged to carry the amount of current that is a safe load for the circuit and the apparatus in it plus a reasonable factor of safety to prevent the fuse from burning out, with a small percentage of increase that would do no damage. For example, a 10-ampere fuse, such as is used in connection with many automobile-lighting generators, would seldom burn out with an increase in the current to 12 amperes or even to 15 amperes for short periods, as the time element is also important. Some other applications of the heating effect are electric welding, blasting fuses, soldering coppers, cooking utensils, and the like.

Chemical Effect of Current. The passage of an electric current likewise has a chemical effect depending upon the nature of the conductor. This may take various forms, such as the conversion of one chemical compound into another, as in the case of the storage battery; the decomposition of water into hydrogen and oxygen; the deposition of metals, as in electroplating; or the decomposition of metals, as in electrolysis.

### ELECTRICAL EQUIPMENT

TABLE II
Carrying Capacity of Wires

E & S Cold	Justinak Mina	RUBBER INSULATION	OTHER INSULATION	
_		Ampères	Amperes	
•	:.624	3	5	
* /	2.583	3 6 12 17	5 8 16 23 32 46 65	
-	4.207	12	16	
<u>:</u>	6.530	17	23	
:	1.7 380	24	32	
•	16 510	33	46	
;	26 250	<b>46</b> ;	65	
7	N 100	46 54 65	77	
•	4.4.	65	92	
		76	110	
<del>.</del>	187 S. (1	90 107	131	
		127	156	
•	11 1	150	185 220	
	- 50	177	262	
111		210	312	

#### MAGNETISM

Natural and Artificial Magnets. It has been known for ma centuries that some specimens of the ore known as magnetite (Fed

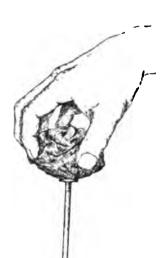


Fig. 6. Natural Magnet or Lodestone

have the property of attracting small be of iron and steel, Fig. 6. This ore probably received its name from the fact that is abundant in the province of Magne in Thessaly, although the Latin with Pliny says that the word magnet is divided from the name of the Greek she herd Magnes, who, on the top of Moulda, observed the attraction of a lar stone for his iron crook. Pieces of a which exhibit this attractive proper for iron or steel are known as natural magnets.

It was also known to the ancier that artificial magnets could be made stroking pieces of steel with natural manets, but it was not until the twelf

century that the discovery was made that a suspended magnet would assume a north-and-south position. Because of this property, natural magnets came to be known as lodestones (leading

stones); and magnets, either artificial or natural, began to be sused for determining directions.

The first mention of the use of a compass in Europe was in 1190. introduced from China.



Fig. 7. Bar Magnet

It is thought to have been

Artificial magnets are now made either by repeatedly stroking a bar of steel, first from the middle to one extremity with one of the ends, or poles, of a magnet, and then from the mid-



Fig. 8. Horseshoe Magnet

dle to the other extremity with the other pole; or else by passing electric currents about the bar in a manner to be described later.

The form shown in Fig. 7 is called a bar magnet, that shown in Fig. 8 is a horseshoe magnet.

Poles of a Magnet. If a magnet is dipped into iron filings, the filings are observed to cling in tufts near the ends, but scarcely at all near the middle, Fig. 9. These places near the ends of the magnet, in which its strength seems to be concentrated, are called the poles of the magnet. It has been decided to call the end of a freely suspended magnet which points to the north, the north-seeking, or north pole, and it is commonly designated by the letter N. The other end is called the south-seeking, or



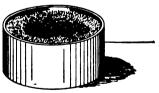


Fig. 9. Location of Poles of a Magnet

south pole, and is designated by the letter S. The direction in which the compass needle points is called the magnetic meridian.

Laws of Magnetic Attraction and Repulsion. In the experiment with the iron filings no particular difference was observed between

the action of the two poles. That there is a difference, however, may be shown by experimenting with two magnets, either of which may be suspended. Fig. 10. If two N poles are brought near each other, each is found to repel the other. The S poles likewise are found to act in the same way. But the N pole of one magnet is found to be attracted by the S pole of the other. The results of these experiments may be summarized in the general law: Magnetic set like kind repel each other, while poles of unlike kind attracted.

This force of attraction or repulsion between poles is found like gravitation, to vary inversely as the square of the distant between the poles; that is, separating two poles to twice their original distance reduces the force acting between them to one-fourth is

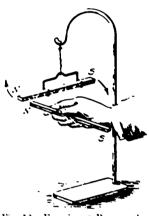


Fig. 10. Experiment Proving the Law of Magnetic Attraction and Repulsion

original value, and separating them thee times their original distance reduces the force to one-ninth its original value, etc.

Magnetic Substances. Iron and steel are the only common substance which exhibit magnetic properties to a marked degree. Nickel and cobalt, however, are also attracted appreciably by strong magnets. Bismuth, antimony, and a number of other substances are actually repelled instead of attracted, but the repulsion is very small. Until quite recently, iron and steel were the only substances whose magnetic properties were sufficiently strong to make

them of any value as magnets. Recently, however, it has been discovered that it is possible to make rather strongly magnetic alloys out of non-magnetic materials. For example, a mixture d 65 per cent copper, 27 per cent manganese, and 8 per cent aluminum is rather strongly magnetic. These are known as the *Heussler alloys*.


Electromagnets. The identity of magnetism with electricity is readily established by some very simple experiments that have been repeated so often as to become classics. By taking a bar of iron and winding some insulated wire around it in the form of a coil and then connecting the terminals of this coil with a battery or other source of current, the bar becomes magnetic. One end

of it is the positive, plus, or north pole of the magnet, and the other the negative, minus, or south pole. Break the connections or otherwise "open the circuit" and the magnetism instantly dis-Reverse the connections to the battery by attaching the wire previously at the positive pole to the negative, and vice versa, complete the circuit again, and the bar is once more magnetic. but now the pole that was previously north or positive is south. The bar is once more a magnet, but its polarity has been reversed by reversing the direction of flow of the magnetizing current. bar of iron with a coil of wire wound around it is known as an electromagnet because it becomes magnetic only when a current is passing through the coil. If a rod of hard steel is substituted for the bar of soft iron and the current passed through it, the bar will be found to be strongly magnetic after the current has been shut off. is, the bar of steel has, through the action of the current, become a permanent magnet like that shown in Fig. 7. This method is often used for making permanent magnets from hardened steel.

To determine the polarity of a magnet it is only necessary to hold a small pocket compass near it; let the compass needle come to rest normally and then bring the compass near to one end of the magnet. If the needle continues to point in the same direction and gives evidences of being strongly attracted to the magnet, the end to which it is being held is the south pole. Bring the compass near to the other end of the magnet, and the needle will turn away sharply, showing that like poles repel each other.

Magnetic Field. If a bar magnet is placed on a sheet of glass and a handful of fine iron filings thrown around it, they will automatically assume the position shown by Fig. 11. As originally dropped on the glass some of the filings may not be within reach of the influence of the magnet, but if the glass be gently tapped and tilted slightly, first one way and then another, they will arrange themselves in the symmetrical pattern shown. This gives a graphic illustration of the field of influence of the magnet, usually termed the magnetic field. This field is most powerful at the poles, as will be noted by the attraction of the filings at the N and S points, representing the north and south poles of the magnet. At intermediate points along the length of the magnet the filings will be seen to have placed themselves as if to indicate a circular movement

of the lines of force. This is the magnetic circuit and these concentric circles represent the magnetic flux, or flow. If the magnet is the removed from the glass and the north pole extension of it places

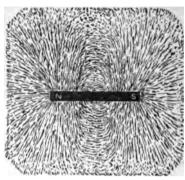

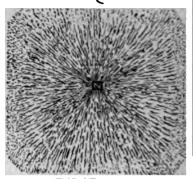


Fig. 11. Field of Force about a Bar Magnet

Fig. 12. Field of Force about a fingle

centrally under the glass, a striking illustration is given of the magnetic field around the pole, Fig. 12. A bar magnet has been shown here for purposes of simplicity, but a common horsesher magnet such as can be had for a few cents will serve equally well for the experiments.

By carrying the experiments a little further, the identity of magnetism and electricity is strikingly shown. Take a piece of

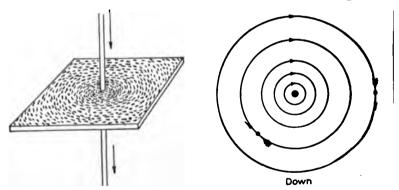


Fig. 13. Field about a Conductor Carrying a Current

cardboard or heavy paper, punch a hole through its center and pass through this hole a wire connected to two or three dry cells. Scatter on the paper the filings used in the previous experiments,

then complete the circuit by touching the end of the wire to the other terminal of the battery. The filings will immediately arrange themselves as shown in Fig. 13, illustrating the magnetic field which is always present around any current-carrying conductor.

Lines of Magnetic Force. Punch another hole through the cardboard and rearrange the circuit of the dry cells so that the wire passes from the positive battery terminal up through one hole of the cardboard and down through the other hole to the zinc or negative. Scatter the filings as before and touch the loose end of the wire to the negative terminal. The arrangement of the filings will then be that shown in Fig. 14, the positive field being at the left and the negative at the right. The fact that the mag-

netic fields overlap in the curious alignment indicated is simply due to the proximity of the conductors carrying the current.

Another simple method of demonstrating the identity of electricity and magnetism is to place an ordinary pocket compass above or below a wire which is running north and south and is carrying a current. If this is a direct current the needle of the

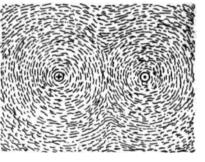


Fig. 14. Field about a Coil

compass will tend to set its axis at right angles to the wire, that is parallel to the lines of force; the direction of the deflection will depend upon the direction of the current. This test, therefore, not only indicates the magnetic field about the wire bearing a current, but shows its direction.

All of the arrangements which the filings assume under the influence of either a magnet or a current, as shown by the various llustrations, indicate that the stresses in the medium surrounding a magnet or current-carrying conductor follow certain definite lines, the lines showing the direction of stress at any point. These are termed lines of force.

Solenoids. It has been determined that the direction of the current and that of the resulting magnetic force are related to one another as the rotation and travel of an ordinary, or right-hand,

screw thread. Consequently, if the conductor be looped install of straight, the lines of magnetic force will surround it as shown in Fig. 15. The field of such a loop, if outlined with the aid of filings or explored with a compass needle, will be seen to retain



Fig. 15. Direction of Magnetic Lines about a Conductor

the general character of the field surrounding a straight conductor, so that all the lines will leave by one face and return by the other, the entire number passing

through the loop. Hence one face of the loop will be equivalent to the north pole of a magnet and the other face to the south pole. In fact, the loop will act exactly as if it were a thin disk magnetized perpendicularly to the plane. By winding a number of these loops to make a hollow coil, there is formed a solenoid, Fig. 16. Exploring its field shows that the lines of force past directly through the center or opening of the hollow coil, leaving by one end and returning by the opposite end, as indicated.

If such a solenoid is held vertically and a bar of soft iron placed so that it extends for an inch or so into the lower end of the solenoid, a current passed through the latter will cause the iron to be violently drawn up into the coil and held there. As long as the current flows, this rod is strongly magnetic and has all the properties already

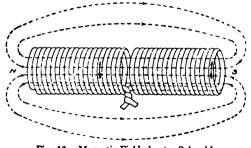


Fig. 16. Magnetic Field about a Solenoid

described. But the moment the current is shut off, the magnetism practically disappears and the rod immediately drops out of the coil by its own weight. Reversing the direction of the current reverses the polarity of the solenoid

but makes the effect the same; increasing or decreasing the amount of current sent through it increases or decreases correspondingly the strength of its magnetic field. The principle of the solenoid is used in starting systems to operate electromagnetic starting switches.

Effect of Iron Core on Strength of Solenoid. The magnetic flux or flow of lines of force through a solenoid is much greater when an iron core is present than when the coil is empty or a core of wood is inserted. The magnetism flows through the iron as a current would. Soft iron is said to have a high magnetic permeability. The magnetic permeability of air (or a vacuum) is taken as unity and other substances rated accordingly: for very soft iron it may be as high as 2500, while for substances such as silk, cotton, wood, glass, brass, copper, and lead, it is unity, the same as for air. Such metals are said to be non-magnetic. All insulators are likewise non-magnetic.

## INDUCTION PRINCIPLES IN GENERATORS AND MOTORS

Induction. When a current suddenly flows in a wire placed close to another wire, a delicate measuring instrument such as a galvanometer will indicate a momentary current in the second wire. When the current in the first wire ceases, that in the second will likewise cease immediately. This phenomenon is known as induction, and a current is said to have been induced in the second wire.

Winding the first wire in the form of a coil and bringing this coil close to the second wire, will give the induced current considerably greater strength. The induced effect is still further increased in three other ways: first, by inserting an iron core in the coil; second, by winding the second wire in the form of a coil; and, third, by bringing these coils as close together as possible by winding one directly over the other.

Transformer Principle. The arrangement just discussed is termed an induction coil or transformer (step-up) and is universally employed in connection with ignition systems. The character of the induced current depends upon the relation that the first coil, termed the primary, bears to the second coil, known as the secondary. In the usual ignition coil the primary consists of a few turns of comparatively heavy wire, and a current of about 2 amperes (4 to 5 on starting) is sent through it at a low voltage, one seldom exceeding 6 volts. The secondary coil, however, consists of a great number of turns of exceedingly fine wire, and the current induced in this is proportional to the relative number of turns between the two and the value of the current in the primary. The

secondary current is accordingly of extremely high potential later flow current value.

In the commercial step-down t above are reversed, the primary bei wire, while the secondary is a com.

In this case, the current is receive voltage and correspondingly red voltage down to the standard go ally employed, 110 or 220 volt, and increases the amount of current oportionately.

Self-Induction. It has already pointed out that electricity may be put under pressure or potential, and that the greater the pressure, the greater the amount of work a certain amperage of current will perform, thus affording direct analogy with stars, water, or air under pressure. An electric current also possess other characteristics corresponding to mechanical equivalent. Chief among these is inertia and it is the latter that is responsible for what is known as self-induction.

When a current is passed through a coil of wire, a strong magnetic field is set up in the coil owing to the concentration of a great many turns of wire in a small compass. By inserting a core of soft ires wires into this coil, the magnetic field is greatly strengthened, since the permeability of the iron affords a path of slight resistance for the magnetic circuit. There is, of course, a magnetic field surrounding every conductor in a circuit when the current is passing but the iron core of the solenoid converts a certain part of this current into magnetism. An appreciable time is necessary after the circuit is closed for such a coil "to build up". This "building up" consists of saturating the core with magnetism.

When the circuit is suddenly opened, the current that has been stored in this core in the form of magnetism is as quickly retransformed and its value is impressed upon the circuit, causing a flash at the break. The flash is also aggravated by a certain amount of inertia which the current possesses. We may illustrate this by a stream of water flowing in a pipe. If the water is suddenly shut off by the closing of a valve, it tends to keep on flowing and momentarily causes a great increase in the pressure against the face of the valve, resulting in the familiar "water hammer". The same thing happens when a circuit is suddenly broken, and the

higher the potential the more marked this effect will be. The current tends to keep on flowing, and the extra potential which this self-induction gives it will cause it to arc, or bridge, the gap at the break, unless a condenser is provided to take care of this. Every circuit possesses self-induction, but it is only marked in circuits having considerable inductance, that is, in coils, and especially those with iron cores, such as induction coils, circuit breakers, etc.

Canacity of Condensers. Every conductor of electricity has capacity to hold a charge just as a vessel holds water. But the capacity of a conductor is dependent upon its surface area rather than its cross-section, or cubic volume, and is also influenced by surrounding conditions. Where it is desired to accumulate a considerable charge, as for an ignition spark, a special form of capacity is utilized. This is known as a condenser (a detailed description of which is given later in connection with ignition coils). The ability of a condenser to absorb the rise in potential that occurs through selfinduction whenever a circuit containing inductance is opened is also utilized to prevent sparking at contact points. Comparatively small condensers are necessary for this purpose, and they are shunted around the contact points, that is, connected in parallel with the latter. When the circuit is opened the excess energy of the circuit passes into the condenser instead of forming a hot spark at the The occurrence of any undue amount of sparking at contacts should accordingly be made the subject of an investigation of the condenser connections, or of the condenser itself.

Comparison of Generator Current to Water Flow. The comparison of air in a room has been made to illustrate the presence of electricity and its characteristics, since it may be made to partake of all the latter by being put under pressure, allowed to escape through various sized outlets, and made to perform work of differing nature by being utilized at varying pressures and volumes, exactly as electricity is. Where an electric current is produced by a generator, however, the older simile of water flowing under pressure due to the impulse of a pump may serve to make it much clearer. This comparison of a water pump and its piping with an electric generator and its circuits is known as a hydraulic analogue, and, it may be added, there is scarcely any characteristic or function of the electrical current that cannot be similarly compared.

Take, for example, a waterworks system of the type in which a large pump at the power house draws water from a reservoir and forces it into a closed system of pipping. Located on this piping system are all the house outlets, street hydrants, and the like. The speed of the pump is regulated so as to keep a certain amount of pressure on the water in the pipes, based upon the average demand at different periods of the day. The pressure is reduced at night and is increased at any time, day or night, in case of fire.

Pressure and Voltage. This constant pressure in pounds per square inch that the pumps maintain on the supply of water in the entire piping system is the exact counterpart of the voltage, or electromotive force, produced by a dynamo, or generator, when running. Just as the pressure exerted on the water by the pumps depends upon the speed of the latter, so the voltage produced by the dynamo is proportional to its speed. In the case of the pump, the pressure depends upon the number of times that the pistons of the pump reciprocate; in the dynamo, upon the number of times that the coils, or windings, of the armature cut the lines of force of the magnetic field in which it revolves. This is explained in detail later in connection with generator principles.

When the pump moves very slowly, there is very little pressure produced in the pipes, and this is the case with the dynamo to as even greater extent, since dynamos are usually designed to run at very much higher speeds, and consequently their voltage, or pressure, drops off very sharply at low speeds. This will explain why the majority of lighting generators on automobiles do not begin to charge the battery until the motor of the car is running at a speed equivalent to ten to fifteen miles per hour, as explained later. At low speeds they do not generate sufficient voltage to overcome that of the battery.

Fall in Pressure. When either a pump or a dynamo is running at a constant speed, the pressure, or voltage, produced at the machine is practically constant. But in the case of the water system, the pressure is not the same at the outlet of a branch line a mile away from the power house as it is at the delivery end of the pump, nor is the voltage on a branch circuit at a great distance from the dynamo the same as it is at the terminals of the latter, consequently, the fall in pressure in the water piping is the exact counterpart of



## ELECTRICAL EQUIPMENT

31

the drop in voltage on the electric circuit due to the resistance of the wires. In the case of the water supply, the friction encountered by the water in passing through the pipes is analogous to the resistance which the electric current must overcome, except that bends in a wire do not impose any greater resistance to the current than the same length of wire when straight, whereas bends in piping greatly add to the friction with a correspondingly greater drop in pressure.

Friction and Resistance. There is, in consequence, almost an exact parallel between the mechanical friction of water passing through a pipe and that of the electric current passing through a wire, as it is commonly said to do. Friction in water piping is inversely proportional to the size of the pipe in proportion to the pressure to which the water is subjected, and is directly proportional to the length of the pipe in exactly the same way that a wire opposes more resistance to the electric current the smaller the wire is, and the amount of resistance also increases with the length of the wire itself. In both cases, the product of this friction, or resistance, is heat; and it results in a drop in pressure, whether mechanical or electrical.

Current and Volume. So far the comparison has been limited entirely to the pressure exerted by the pump on the supply line as compared with the voltage of the generator imposed on the circuit. In a similar way the flow of water from the pipe line may be compared with that of the current in an electrical circuit. Assume, for example, that, in the case of the water-supply system, the pumps generate a pressure of 100 pounds to the square inch. Eliminating from consideration any drop in pressure between the pump and outlet as only tending to confuse the comparison, suppose a half-inch faucet to be opened at a distant part of the system. Then there will flow from the pipe an amount of water proportioned to the size of the outlet times the pressure, or head, back of it. Let us assume that this will be one cubic foot per minute, or, roughly, eight gallons.

In the same way, assume that the generator imposes a pressure of 100 volts on the line and, for purposes of comparison, there is no drop between the generator and the end of the line. So long as there is no outlet open there is pressure on the water in the supply system, but no flow. This is likewise the case with the electric circuit. The voltage is present as long as the armature of the dynamo

Fig. 17. Elementary Principle of Generator

11

GENERALUK PKIN

Classification.

namo-electric machi commercial applicat Faraday's discovery

duced currents in 1831. They are all designed to transfer mechanical energy of a steam engine, a waterfall, a gasoline etc., into the energy of an electric current. Whenever larger are required—for example, in running street cars; in systighting and heating; in the smelting, welding, and refining of the charging of storage batteries, etc.—they are always p by dynamo-electric machines.

There are two kinds of generators (1) d.c., or those procunidirectional (direct) current, that is, one which always the same direction in the external circuit, and (2) a.c., or producing an alternating current, that is, one which revidirection continuously throughout the entire circuit.

Elementary Dynamo. Whenever lines of magnetic flux ar a conductor, for example, by a wire passing through them, a (electromotive force) is produced in the conductor, and the s of this e.m.f. is entirely dependent upon the speed at wh conductor passes through the magnetic field. If, at the tir this is done, the ends of the wire are brought together to circuit, a current will be induced in the conductor. The s

ting the magnetic flux at right angles and are consequently cutting more lines of force per second than in any other part of the revolution. Note that as CD moves up, AB moves down (and vice versa) across the magnetic flux so that the induced currents in all

parts of the loop at any instant are flowing in one direction. The value of this e.m.f. depends upon the speed, and as the loop approaches the 90-degree, or vertical, position, the e.m.f. decreases because the rate of cutting is diminishing, until when the loop is vertical both the cutting

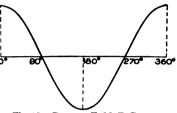


Fig. 18. Dynamo E. M. F. Curve

of the magnetic flux and the generated e.m.f. are at zero. If the rotation is continued, the rate again gradually increases, until at 180 degrees it is once more a maximum. The cutting, however, in the two quadrants following the 90-degree position has been in the opposite direction to that occurring in the first quadrant, so that the direction

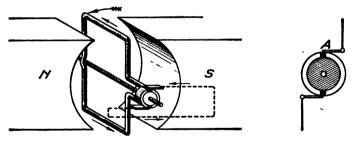


Fig. 19. Simple Form of Generator Showing Arrangement of Brushes in Contact with Commutator

of the e.m.f. generated is reversed. Plotting this through an entire rotation gives the curve shown in Fig. 18. Such an e.m.f. is termed alternating because of its reversal from positive to negative values, first in one direction and then in the other, through the circuit. It cannot be utilized for charging a storage battery, and hence it is not employed in connection with starting and lighting dynamos and motors. To convert an alternating current into a direct or continuous current, a commutator must be added.

Commutators. Fig. 19 illustrates a commutator in its simplest torm. It may be imagined as consisting of a small brass tube which has been sawed in two longitudinally, the halves being mounted

on a wooden rod. The wood and the two cuts in the tube insula the halves from each other. Each one of these halves is connect to one terminal of the loop, as shown in the illustration, Fig. 2

Against this commutator. Fig. 19, two brushes bear at opposite points and lead the current due to the generated e.m.f. to the external circuit. If these brushes are so set that each half of the split tube moves out of contact with one brush and into contact with another at the instant when the loop is passing through the


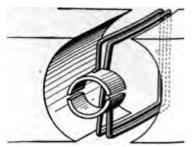


Fig. 20. Commutator with Double Tu

positions where the rate of cutting is minimum (as indicated the enlarged end view of the commutator shown at A), a unic rectional current will be produced, but it will be of the pulsati character as indicated by the curve for one cycle shown in Fig. ?

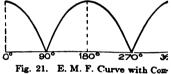This would also be the case, if instead of the single loop, a coil wound on an iron ring be substituted, as in Fig. 22, the only effect of this being to increase the e.m.f. by increasing the number of times



the electrical circuit cuts the magnetic flux. Now assume that to coils are connected to the commutator bars, instead of the sine loop, shown in Fig. 22. This arrangement will give the simt device shown in Fig. 23, called an armature. The two coils a

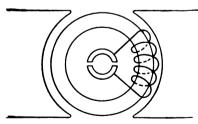


Fig. 22. Armature with Single Coil

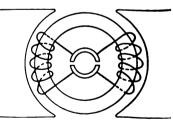


Fig. 23. Two-Coil Armature

in parallel and while the voltage generated by revolving this windi with two coils is no greater than with one coil, the current-carryi capacity of the winding is doubled. The current generated

this form of armature would still have the disadvantage, however, of being pulsating. As in the case of the automobile motor, the number of cylinders must be increased to make the power output

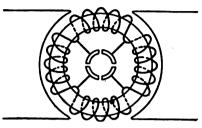


Fig. 24. Four-Coil Armsture

a continuous unbroken line, so armature coils and their corresponding commutator brushes must be added that one set may come into action before the other "goes dead". By placing an extra pair of coils on the armature, at right angles to the first, as shown in Fig. 24, one set will

be in the position of maximum activity when the other is at the point of least action. While this armature would produce a continuous current, it would not be steady, having four pulsations per revolution, and it is consequently necessary to increase the number of coils and commutator segments still further to generate a steady, continuous current. This is what is done in practice.

A commutator consists of a number of copper bars or segments, equal to the number of sections in the armature. These bars are separated by sheets of insulating material, usually mica, and are

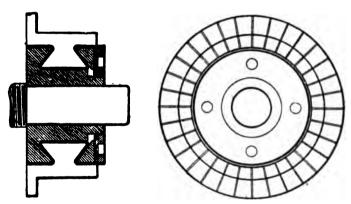


Fig. 25. Sectional and End Views of a Commutator Courtesy of Horseless Age

firmly held together by a clamping device consisting of a metal neeve with a head having its inner side undercut at an angle, a the similar in shape to the head of the sleeve, and a nut that

screws over the end of the sleeve, as shown in the left-hand or sectional view of Fig. 25. The sleeve is surrounded by a bushise of insulating material, and washers of the same material are placed between the assembly of commutator bars and the two clamping heads Each bar is then completely insulated from every other bar and from the clamping sleeve. Commutators are also made by pressing the entire assembly of copper segments together, or molding then in insulating material (Bakelite), which thus forms the hub or mounting of the commutator as well as the insulating material between the segments. After assembling, the commutator is turned down in a lathe to a true-running cylinder and then sand papered on its outer cylindrical surface to present a smooth bearist surface for the brushes. At the inner end of the commutate which is closest to the armature windings, the commutator has are provided with lugs as shown in the sectional view; these lug are slotted and the armature leads are soldered to them. At the right. Fig. 25, is shown an end view of the same commutator.

From the repair man's point of view, the commutator is the most important part of the generator or the motor, since it is an of the first with whose shortcomings he makes acquaintance. Pretically all lighting and starting motors now have their armster shafts mounted on annular ball bearings, so that the commutator and the brushes are the only parts that are subject to wear. I the time devoted in the garage to the maintenance of automobile electric systems were to be divided according to the units demandia attention, the battery would naturally come first, brushes and commutators next, then switches, regulating instruments. nections, and wiring, about in the order named. After all of the come, of course, burnt-out armatures or other internal derangement which necessitate returning the units to the manufacturer: but troubles of this nature are quite rare. While this list gives the order of precedence, it has no bearing on the relative importance of the troubles; with respect to the total time taken by each, the battery is responsible for not far from 90 per cent, the commutator for about 5 per cent, all other causes comprising the remaining 5 per cent.

Armature Windings. In the simple illustrations given to show the method of generating e.m.f. in the armature and leading

in insulating material (Bakelite), which thus forms the mounting of the commutator as well as the insulating between the segments. After assembling, the commuturned down in a lathe to a true-running cylinder and the papered on its outer cylindrical surface to present a smooth surface for the brushes. At the inner end of the commutator are provided with lugs as shown in the sectional view; the are slotted and the armature leads are soldered to them. right, Fig. 25, is shown an end view of the same commutative.

1

į

From the repair man's point of view, the commutat most important part of the generator or the motor, since of the first with whose shortcomings he makes acquaintance tically all lighting and starting motors now have their a shafts mounted on annular ball bearings, so that the con and the brushes are the only parts that are subject to a the time devoted in the garage to the maintenance of au electric systems were to be divided according to the units de attention, the battery would naturally come first, brus commutators next, then switches, regulating instrumen nections, and wiring, about in the order named. After all come, of course, burnt-out armatures or other internal deran which necessitate returning the units to the manufactur troubles of this nature are quite rare. While this list g

the current to the external circuit, what is known as the ring type of winding is shown. This is inefficient because half the length of the conductor—the portion inside the ring—does not cut any lines of force and hence does not aid in generating the current. The design, moreover, does not lend itself to compactness, so that it would not be adapted to automobile work even if there were no objection to it on the score of inefficiency. A slotted type of armature core is very generally employed for the small generators and starting motors used on automobiles and the wire is either wound directly in the slots, or is "form wound", that is, the wire is placed on a wooden form shaped to correspond to the position the coil will take when in place on the armature. After winding the necessary length of conductor on this foundation, the wire is taped together, and varnished or impregnated with an insulating compound, and baked.

Owing to its high magnetic permeability, iron is universally employed for the core of the armature, since the function of the core is to carry the magnetic flux across from pole to pole of the field magnets, as well as to form a foundation for the coils. However. when a mass of iron is rotated in the field of a magnet what are known as "eddy currents" are set up in the metal itself, and these prevent the inner parts of the mass from becoming magnetized as rapidly as the outer and also cause the interior to retain its magnetism longer. As the efficiency of the generator depends upon the rapidity with which the sections of the armature become magnetized and demagnetized as they revolve, the lag due to these eddy currents is a detriment. To reduce this effect to the minimum. the armature cores are always laminated, that is, built up of thin disks of very soft iron or mild steel, these disks having the necessary slots punched in them to accommodate the windings when assembled on the shaft. The disks are insulated from one another either by varnishing them or by inserting paper disks between them. are assembled on the shaft and are put together under considerable pressure, various means being employed to hold them in place. These disks are so thin that hundreds of them are required to make an armature core only a few inches long, and when pressed together in place they are to all intents and purposes a solid mass.

Armature winding, however, is something that is entirely beyond the province of either the car owner or the repair man, no

matter how well equipped a shop he has. It is a job for the experiment in that particular line, and on the rare occasions when an armsum does go wrong, it should always be returned to the manufacture.

if possible, if not, to a shop making a speciality of such work.

Field Magnets. In the foregoing explanation of the generation of an e.m.f. in a conductor when rotated in a magnetic field and the leading out of the current through a commutator, the presence of the field has been assumed and nothing has been said regarding the method of providing it. The term field is applied interchangeably to the magnetic flux between the pole faces of the field magnets and to the magnets themselves, but it is more generally understood to refer to the latter directly and to the former by inference. There are various methods of maintaining

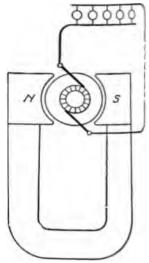


Fig. 26. Diagram of Magnets

the flux, usually described as "field magnet excitation", but only two of them are applicable to the electric generators employed at the automobile.

Permanent Field Used in Magneto. The simplest of these and the first to be designed, employed permanent magnets, from

which such a generator takes its name, magneto. Fig. 26 is a diagrammatic representation of an early form of the magneto-generator. Since magnetism cannot be maintained permanently at the high flux-density or strength which can be produced by an exciting coil fed by a current, this method is only employed in very small generators, as its bulk for large powers would be excessive. Its

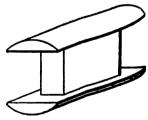


Fig. 27. Sketch Showing Shape of Armature Core

Courtesy of Horseless Age

great advantage is its simplicity and constancy. The magneto-gene ator shown in Fig. 26, however, is designed to produce a continuou current, and is not the type in general use on the automobile today

The type usually installed is made with a two-pole armature, as shown by Fig. 27. This figure illustrates the core known as a "shuttle" type because the wire is wound around the center of the core in much the same manner as thread is put on a shuttle. These cores are laminated as already described, in all well-built magnetos. The space on the core is filled with a single coil of comparatively coarse wire on the majority of magnetos, which generate a low voltage current that is subsequently stepped up through an outside transformer. In some instances, in what may be termed the true high-tension type of magneto, there is a second winding of fine wire on the core so that the magneto generates a current

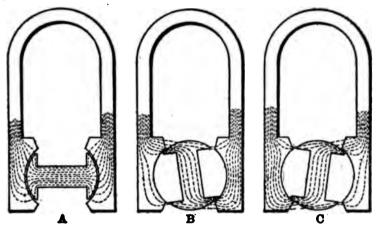


Fig. 28. Diagrams Showing Distribution of Magnetic Flux for Various Positions

Courtest of Herneless Age

and steps it up without the aid of any outside devices. In either case, one end of the winding is "grounded on the core", that is, connected to it electrically, so that the core and other metal parts of the machine form one side of the circuit, while the other end is connected to a stud against which a spring-controlled carbon brush bears, to collect the current. Detailed descriptions of various types of magnetos are given later so that nothing further concerning the construction need be added here.

Principle of Operation of Magneto. Under "Generator Principles", the principle of the operation of the magneto has already been explained, the method by which the rotation of the conductors in the magnetic field generates an e.m.f. and a current is induced

in them. But as the actual operation of the magneto as des for ignition purposes is radically different from any other for generator, it is given here. If unrestricted, the armature o magneto will always assume the position shown at A, Fig. 28 considerable effort will be required to turn it from this posas the magnetic flux through the armature is then a maxim When the armature is rotated a little over 90 degrees from horizontal position so that the armature poles leave the field 1 as at B in the same figure, the flux decreases, and when in a ve position no lines of force pass through it. At this point, the dire

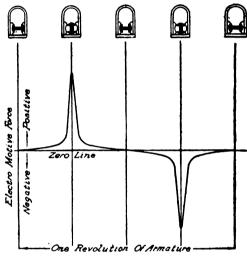


Fig. 29. Curve of Primary E. M. F. in Magneto on Open Circuit Courtesy of Horseless Age

of the magnetic flux through the armature core reverses. Has a two-pole armature, the magneto produces an alternating cut of one complete cycle per revolution, as shown by the curve, 29, which illustrates the electromotive force generated at the ferent positions in the rotation of the armature. The similar between this curve and the one generated by the elementary dyns. Fig. 17, will be noted. With the armature in the horizontal posithere is a dead point, the e.m.f. curve only starting as the pieces of the armature begin to cut the edges of the field mappoles. It then rises very sharply to a peak, and as sharply d

away to zero again, thus forming one-half cycle, which is then repeated in the opposite direction. As the present discussion comprises

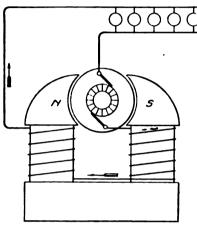


Fig. 30. Diagram Showing Series Generator

only an introduction to elementary principles and theories, further details of construction and operation of the magneto are given later in the section on "Ignition".

Self-Excited Fields. In a machine of the magneto type, the only method of varying the current output is to vary the speed of the armature, and it is therefore not well adapted to the . majority of uses for which a generator is employed. Consequently, other methods of excit-

into two classes: first, those separately excited, in which current from an independent source is supplied to the field windings. This is now practically restricted to large alternating-current generators and so need not be considered further here. Second. self-excited fields, which are now characteristic of all continuous current generators. In this method all or a part of the current induced in the armature windings is passed through the field coils, the amount depend-

ing the fields have been developed, which may be roughly divided

Series Generator. Where the entire current output is utilized for this purpose, the dynamo is of the series type, and a reference to the section on "Cir-

ing on the type of generator.

Diagram Showing Shunt-Wound

cuits", in connection with the illustration, Fig. 30, will make this plain. There is but a single circuit on such a dynamo and while it has the advantage of simplicity, it does not generate a current until a fairly high speed is reached, or unless the resistance in the external circuit is below a certain limit. It is also likely to have its polarity reversed so that it is not fitted for charging storage batteries. As the only series generators put into commercial use have been for supplying arc lamps in series for street lighting they need not be considered further.

Shunt-Wound Generator. By winding the generator with two circuits instead of one and giving that of the fields a relatively high resistance as compared with the outside circuit on which the generator is to work, a machine that is self-regulating within certain limits

is produced. As shown by Fig. 31, the main circuit of the generator is that through the armature with which the field winding is in shunt. The current accordingly divides inversely as the resistance and only a small part of it flows through the field coils, while the main output of the generator flows through the external circuit to light the lamps. to charge a battery, or the like, the resistance of this external circuit being much less than that of the fields. But in this type,

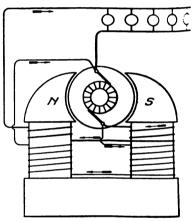


Fig. 32. Diagram Showing Compound-Wound Generator

as well as in the simple series form, the e.m.f. generated varies more or less with the load, and as the latter is constantly changing, it is necessary to provide some means of varying the e.m.f. generated to suit the load, in other words, to make the generator self-regulating. Of the several available methods of doing this the only one applicable to the small direct-current generators used in automobile lighting and starting systems, is that of varying the magnetic flux through the armature.

Compound-Wound Generator. There are also several method of effecting this variation of the magnetic flux, but the most advantageous and consequently the most generally used, is to vary the amount of current in the energizing coils on the field magnets

By adding to the shunt winding a few turns of heavy wire in series with the armature so that all the current passes through them, the magnetic flux may be made to increase with the load as it is directly affected by the current demanded by the latter. This combination of the shunt and series is termed a compound winding, and the usual method of affecting it is shown by Fig. 32. Such a machine

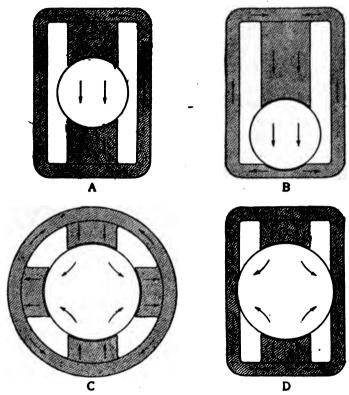


Fig. 33. Forms of Field Frames

is called a compound generator, and is sometimes used for lighting and for charging the storage batteries of automobiles.

In view of the great range of speed variation required of the automobile motor, the series wiring is sometimes reversed so as to act against the shunt instead of with it, in order to prevent an excessive amount of flux and a current that would be dangerous to the windings themselves due to a very high speed. The compound

winding then opposes the shunt-winding and is termed a bucking-coil or winding. This is referred to later in connection with the discussion of methods of regulating the generator on the automobile.

Forms of Field Magnets. For greater simplicity, all of the illustrations shown in connection with the explanation of the various types of generators are of the old bipolar type in a form long since obsolete. The field frame, as it is designated may, however, take a number of different forms depending entirely upon the designer's conception of what best meets the requirements of ample power in the minimum of space and with the minimum weight. 33 shows some typical forms of field frames in general use on automobile generators, and it will be noted that in addition to providing a magnetic circuit the field frame also serves to enclose the windings. These are known as "ironclad" types from the fact that all parts are thoroughly enclosed and protected. The arrows in each case indicate the paths of the magnetic circuits, the number of the circuits varying with the number of pole pieces. The form at A has two opposed poles, each of which is designed to carry an exciting coil or winding. This is a bipolar machine. Field frame B is also of the bipolar type but only one pole carries an exciting winding. the other being known as a consequent pole. In both of these field frames, it will be noted that the magnetic circuits are long. which adds to the magnetic reluctance and tends to decrease the efficiency. To overcome this, multipolar types of field frames are very generally employed. One of these, with two wound or salient poles and two consequent poles, is shown at D, the extra poles making four short instead of two long magnetic circuits. C is a multipolar type with four salient poles.

Brushes. Brushes serve to conduct the current generated by the armature to the outer circuit and to the field coils in order that the excitation of the latter may correspond with the demand upon the generator. The brushes originally employed were strips of copper which bore on the commutator; as generators increased in size these brushes were built up of thin laminations of copper. Plain copper brushes in any form, however, cause an excessive amount of sparking which is ruinous to the smooth surface and true running of a commutator. Built-up copper gauze brushes were then adopted, and they were fitted to bear against the com-

mutator. Though an improvement, these did not meet all the requirements and were in turn superseded by carbon brushes, which are now practically universal. The carbon brushes usually bear directly against the face of the commutator, either through a blunt, squared end, or one that is slightly beveled. The brush holders are generally attached to rocker rings, which allow adjustments to prevent sparking; in these holders are small helical springs under compression, which serve to press the brush against the commutator. Ordinarily, the brushes are composed of a uniformly smooth and homogeneous compound of carbon that soon acquires a glazed surface at its bearing end and wears indefinitely without requiring any attention, but at times a gritty brush will be found. Such a brush scratches the commutator surface, wears unevenly, and is generally a source of trouble.

Badly worn commutators frequently result from the use of improper brushes, or too heavy a spring pressure—also from too light a spring pressure. The manufacturer has found out by experiment and study just what character of brush is best adapted to his particular generator or starting motor and also the exact amount of spring pressure that is necessary to insure the best results. Consequently, much trouble will be avoided if brushes are replaced only with those supplied by the manufacturer of that particular machine, in connection with the brush springs that were designed for it. There are electrical as well as mechanical reasons for this, since both the resistance and current-carrying capacity of carbon brushes vary. This has been taken into consideration by the manufacturer who has provided a brush especially adapted to his machine.

### **ELECTRIC MOTOR PRINCIPLES**

Theory of Operation. A machine that is designed to convert mechanical into electrical energy or the reverse, is known as a dynamo-electric machine. When its armature is rotated by an external source of power, such as a steam engine, hydraulic turbine, or gasoline engine, it is a generator. By sending a current through it from another generator or a battery it converts electrical into mechanical energy and is a motor. It is evident, then, that a generator and a motor are fundamentally one and the same thing, and that by a reversal of the conditions one unit may be made to

Counter E.M.F. Though being rotated by means of current obtained from an external source of power, it is apparent that the motor armature in revolving its coils in the magnetic field is fulfilling the conditions previously mentioned as necessary for the generation of an e.m.f. Experiment shows that the voltage and current this generated are in an opposite direction to that which is operating the motor. It is accordingly termed a counter e.m.f. as it opposes the operating current. This, together with the fact that the resistance of copper increases with its temperature and that the armsture becomes warmer as it runs, explains why the resistance of a motor is apparently so much greater when running than when standing idle. The counter e.m.f. approaches in value that of the line e.m.f. or voltage at which current is being supplied to the motor. of course, never quite equal the latter for in that case no current would flow. The two opposing e.m.f.'s would equalize each other: there would be no difference of potential.

Types of Motors. Being the counterparts of electric generators, electric motors differ in type according to their windings in the same manner as already explained for generators. The plain series wound motor is nothing more or less than the simple series-wound generator to which reference has already been made; the shunt and compound motors likewise correspond to the shunt and compound generators But while the series-wound generator was of extremely limited application and has long since become obsolete, the series-wound motor possesses certain characteristics which make it very generally used. It is practically the only type employed for starting service on the automobile, and it is also in almost universal use for railway service. The reasons for this are its very heavy starting torus which increases as the speed of the motor decreases, the quick dro in the current required as the motor attains speed, and its liberal overload capacity. It is essentially a variable speed motor, and just as the plain series-wound generator delivers a current varying with the speed at which it is driven, so the speed of the motor changes in proportion to the load. These are characteristics which make it valuable for use both as a starting motor for the gasoline engine. and for a driving motor on the electric automobile, though in the latter case it is seldom a simple series-wound type. As its speed is inversely proportional to the load, however, it tends to race when

the load is light; in other words, it will "run away" if the load is suddenly removed, as in declutching from the automobile engine after starting the latter, unless the current is instantly shut off or very much reduced. This is provided for, as will be explained in detail later in connection with the various systems.

Shunt motors and compound-wound motors are the same as their counterparts, the generators of the same types, but as they are not used in this connection, no further reference need be made to them here.

Dynamotors. As the term suggests, this is a combination of the generator or dynamo and the electric motor, and it is a hybrid


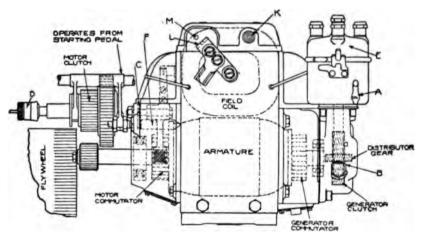


Fig. 34. Dynamotor (Single Unit) of the Delco System

for which the automobile starting system has been responsible. It is frequently mistermed a "motor-generator" and while its assumption of the two rôles may justify the name, the use of the term is misleading as it becomes confused with the motor-generators employed for converting alternating into direct current. The latter consist of an a-c. motor on one end of a shaft and a d-c. generator on the other end of the same shaft. The two units are distinct except for their connection, whereas a dynamotor is a single unit comprising both generator and motor, and it can perform only one of these functions at one time. A motor-generator, such as is used in garages for transforming alternating into direct current for charging storage batteries, must carry on both functions at

## ELECTRICAL EQUIPMENT

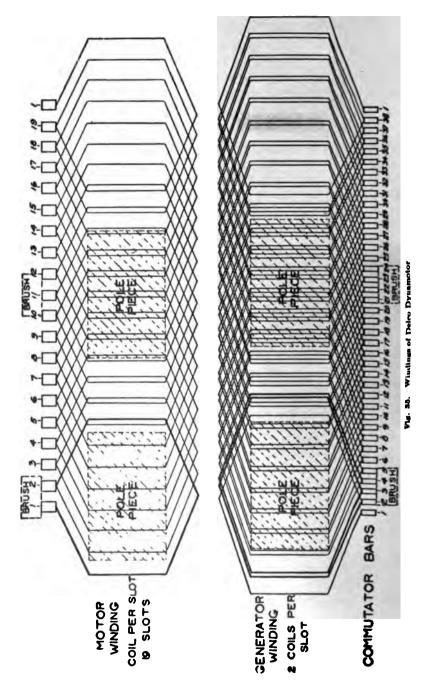


same time in order to operate. That is, the a-c. motor must as a motor in order to drive the d-c. generator and cause it enerate a direct current. Hence, the term motor-generator pplied to the single-unit type of electric starting system for an mobile is not in accordance with the accepted meaning of the Is and is likely to be confusing.

A typical example of the dynamotor is to be found in the Delco e-unit system, illustrated in Fig. 34. This is really the windings vo radically different machines, a shunt-wound generator and ries-wound motor, placed on the same armature core and field As will be noted, the terminals of the two sets of windings he armature are brought out in different directions and two



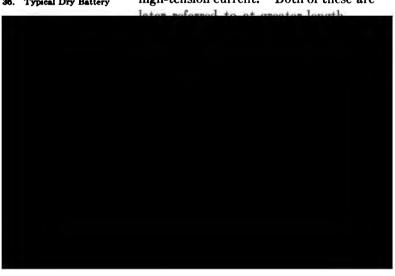36. Typical Dry Battery

commutators are employed, that at the right-hand end being for the generator windings, and that at the left for the The method of winding the armature is illustrated by Fig. 35, which shows the generator and motor windings projected on a plane. In the preceding illustration the detail at the left shows the gearing and starting connection for coupling the starting motor with the flywheel of the engine, the one at the right an ignition distributor for the high-tension current. Both of these are



of the battery. The cell is sealed at the top to prevent evaporation, since, when the cell does actually become as dry inside as it is outside it is no longer of any use. Some of its other characteristics are mentioned under "Ignition", Part II.

The storage battery or accumulator does not generate a current in any sense of the word. By means of a much more complicated chemical reaction than that of the primary cell it absorbs a charge of electricity. Upon the completion of the circuit of a storage cell with a suitable load or resistance, such as driving a motor or lighting a lamp, a reversal of this chemical process takes place and the battery redelivers a part of the current which it has previously absorbed. Full details of the characteristics, construction, and working of the storage battery are given in the article on "Electric Automobiles". The storage battery and the dry cell are the only two forms of battery employed on the automobile so that no mention of the other types is necessary, particularly as all but very few of them are practically obsolete.

# SUMMARY OF ELECTRICAL PRINCIPLES GENERAL PRINCIPLES

The importance of a knowledge of the fundamental principles of electricity and of its characteristics to the man who wishes to familiarize himself with the electrical apparatus on the automobile to the point where he can readily diagnose and remedy its ills has already been dwelt upon. To bring these out more clearly and make them easier to memorize, they are repeated here in the form of a brief résumé in questions and answers.

- Q. What is electrical pressure, and to what may it be compared?
- A. Electrical pressure is electromotive force, usually termed e.m.f., or voltage, also potential, and may be likened to water under pressure in a pipe or to compressed air in a container.
- Q. Of what does this electrical pressure consist, and how is it measured?
- A. It is represented by the difference of potential between two points in a circuit, and it is measured in volts.
  - Q. What does the unit volt represent?

- A. The volt is the amount of e.m.f. required to force a current of one ampere through a resistance of one ohm.
  - Q. What is the ampere?
  - A. It is the unit of current flow.
  - O. What is the ohm?
- A. The unit of resistance represented by a length of wire that will pass one ampere under a pressure of one volt.
  - Q. In what unit is the volume of current flow measured?
- A. In the coulomb, which is the equivalent of one ampere per second.
- Q. Are the factors of electrical quantity, flow, and pressure related, and how?
- A. They are all closely related, and their relation is governed by the factor of resistance.
  - Q. What is resistance, and of what may it consist?
- A. Any element which tends to retard the flow of the current is resistance. It may consist of the wire of the circuit itself; the windings of different apparatus in the circuit, such as an induction coil or a motor; the filament of a lamp; a switch; or the like.
  - Q. Are these the only forms that resistance takes?
- A. No. Poor joints in wires, dirty and loose connections, dirty switch blades, all produce increased resistance in the circuit. These are undesirable increases in the resistance. In addition to these, there are special resistances intentionally inserted in the circuit to serve a definite purpose. These are known as rheostats, resistance coils, windings, or grids, according to the form they take.
- Q. Why is it desirable to keep the resistance of the circuit, outside of that produced by the apparatus itself, at a minimum?
- A. Because any resistance other than that interposed by the windings of the motor, the filaments of the lamps, or other useful apparatus in the circuit, not only means waste current, but also prevents the full amount of current required from reaching the desired points.
  - O. How does this waste occur?
- A. In a poor joint, a loose connection, or a dirty switch blade, the current is dissipated as heat and accordingly represents that much energy passing off into the air.

- Q. Can undesirable resistance be interposed in a circuit in any ways other than those already mentioned?
- A. Yes, by the use of wire too small to carry the amount of current required by the apparatus.
  - Q. What is the effect of using wires too small for the current?
- A. The wires waste a great deal of the current in heat and, if much too small for the purpose, are likely to become overheated to a point at which they will burn the insulation off or to actually become fused by the current.
  - Q. What determines the voltage in an electrical circuit?
- A. The potential, or voltage, of the source of supply, such as a storage battery, in which case the voltage will be constant less the drop caused by the resistance of the circuit; or, in the case of a lighting generator, it will depend upon the design of the latter (winding, etc.) and the speed at which it is running.
  - Q. How may the voltage be varied?
- A. In the case of a battery, by varying the number of cells, each cell of a storage battery giving approximately 2 volts. In a generator, by varying the windings of the field and the armature and by increasing or decreasing the speed at which it runs. On a circuit having a higher voltage than desired, by the insertion of an amount of resistance calculated to give the drop required.
- Q. Can lamps of a certain voltage be burned on a circuit having a higher voltage?
- A. Not if inserted directly in such a circuit. For example, the standard 6-volt lamp cannot be used directly on a 6- or a 12-cell storage-battery circuit as employed for the lighting and starting systems of many cars. The filament would immediately burn out, as its thickness is calculated to a nicety to become incandescent when current of the voltage for which it is designed is passed through it, and anything in excess of this voltage will fuse the wire.
- Q. How can lamps of lower voltage be used on such circuits without the employment of a wasteful resistance to cut the voltage down?
- A. By cutting down the number of cells employed for the lighting, as, for example, where 12 cells are used to operate the starting motor, the battery is divided into four groups of 3 cells each for the lighting, these groups delivering current at 6 volts, while

the complete battery has a potential of 24 volts. This is termed putting the battery into *series-multiple* connection, which is explained further under the head of "Circuits".

- Q. When the voltage is lower than that required by the lamp, what happens?
- A. The lamp filament will give only a dull red glow with a voltage drop of but 20 per cent or less of the total, since there is insufficient potential to cause the current to bring the filament wire to incandescence.
- Q. Is the insertion of any apparatus, such as lamps, a motor, etc., in a circuit having a voltage higher than that for which they are designed likely to damage them?
- A. Yes, it will burn them out if, for instance, 110-volt lamps or motors are connected to 220-volt current, or 6-volt lamps put on a 12-volt circuit.
  - Q. Does the opposite also hold true?
- A. No. The apparatus will merely fail to function properly if put on a circuit of a voltage lower than that for which it is designed.

### OHM'S LAW

## Q. What is Ohm's law?

- A. It is the basis of all computations concerning the flow of an electric current. It is stated as current equals voltage divided by resistance and may be transposed to find any of the three factors, as, resistance equals voltage divided by current, so that, given any two of the factors, the third may be readily determined.
- Q. How is the power equivalent of an electric current expressed?
- A. Power equals current times voltage, the product being watts, as one volt times one ampere equals one watt.
  - Q. How many watts are there in a horsepower?
- A. 746. Electrical horsepower, however, is usually figured in kilowatts, or units of one thousand watts, generally abbreviated to KW.
- Q. Given a 6-volt storage battery fully charged and a circuit including a starting motor, the total resistance of which (idle) is .1 ohm, how much current will pass through the motor?
- A. As current equals voltage divided by resistance, we have  $6 \div .1 = 60$  amperes.

- Q. If, instead of a heavy stranded cable between the battery and motor, we substitute a fine wire having a resistance of 10 ohms, how much current will pass?
  - A. Only .6 ampere.
- Q. What would happen if a very small wire were employed to connect the starting motor with the battery?
- A. Not sufficient current would reach the motor to operate it, and the wire would probably be fused by the heating effect of the heavy current.
- Q. If one horsepower be required to turn the engine over at 100 r.p.m., and the car is equipped with a 6-volt battery, how many amperes will be necessary to start?
- A. As power divided by voltage equals current,  $746 \div 6 = 124\frac{1}{3}$  amperes.
  - Q. How is the power equivalent usually expressed?
  - A. Power equals current times voltage.
- Q. As the voltage is one of the chief determining factors, what effect does doubling it have?
- A. Reduces by one-half the amount of current required, exactly the same as doubling the pressure of a steam boiler reduces correspondingly the volume of steam necessary to perform the same amount of work.
- Q. If the voltage be cut in half, what will be necessary to perform the same amount of work?
- A. The number of amperes, or amount of current, must be doubled.

### **MAGNETISM**

- Q. What is magnetism?
- A. It actually is electricity in another form and is evidenced by the attraction or repulsion that one magnet exerts on another, or that any piece of magnetized metal has for objects of steel or iron.
- Q. How is this relation between magnetism and electricity shown?
- A. By the fact that they are interchangeable. By passing a current of electricity through a coil surrounding an iron or steel bar, it becomes magnetic; upon moving a magnetized piece of metal close to a coil of wire, a current of electricity is induced in the wire.
  - Q. What is meant by the polarity of a magnet?

- A. Upon being magnetized, a bar of steel will attract other pieces of metal (iron or steel) indiscriminately, but upon being brought close to another magnet, it will display an attraction at one end and a repulsion at the other for the second magnet. In other words, the magnetic attraction at both ends is not the same. These ends are termed the poles, one north and the other south, by analogy with the compass which is merely a magnetized needle having a natural tendency to point north and south.
  - Q. What other characteristics do the poles of a magnet display?
- A. They show that the force of the magnet is practically concentrated at these poles, as the magnetic attraction is very much less at any other part of the bar.
  - Q. What is the law of magnetic attraction and repulsion?
- A. Like poles repel one another and unlike poles attract. In other words, if a bar magnet be suspended, and the north pole of a second magnet be held close to the north pole of the suspended magnet, the latter will swing away; if the south pole of the second magnet be approached to the north pole of the suspended magnet, the latter will swing toward the former until they touch.
  - Q. How does the force of this attraction or repulsion vary?
- A. Inversely as the square of the distance, i.e., separating the poles by twice the distance reduces the force acting between them to one-fourth its value. For example, if two magnets exhibit a strong attraction for each other at a distance of one-half inch, the attraction will be four times stronger when they are separated by only one-fourth inch.
  - Q. What are the chief magnetic substances?
  - A. Iron and steel.
  - Q. What is meant by the magnetic field?
- A. The space immediately surrounding the poles and at which the magnetic force is most plainly apparent, as shown by the experiments with filings which graphically illustrate the field of influence of the magnet, and from which the term in question originates.
  - Q. What is a magnetic circuit?
- A. The path followed by the magnetic flux, or flow, from one pole to the other.
- Q. What analogy is there between the poles of a magnet and the flow of a current in an electric circuit?

- A. The current is said to flow from the positive, or north, pole of a battery or generator, to the negative, or south, pole to complete the circuit, exactly as the lines of force in a magnet flow to complete the magnetic circuit.
- Q. How can the polarity of a current flowing in a wire be determined by a simple experiment?
- A. Hold a small pocket compass close to the wire. If the needs of the compass is attracted at its north pole to the wire, the current flowing in the latter is negative (south pole), as unlike poles attract and vice versa. This will be true only when a direct current is flowing in the wire, since an alternating current, as the term indicates, alternates in polarity with every cycle.
  - O. What are lines of force?
- A. The invisible flow of magnetic influence from the north to the south pole of a magnet or about any conductor carrying at electric current.
  - O. What is a solenoid?
- A. A hollow coil of wire through which a current may be passel to produce a magnetic field.
- Q. What is the difference between a permanent magnet and at electromagnet?
- A. When a piece of hard steel has been magnetized, either by being rubbed on another magnet or by being placed in a solenoid through which a current is passed, the steel retains a large percentage of its magnetism when removed from this magnetic field and is said to be a permanent magnet. An electro magnet consists of a soft iron or steel core on which a coil of wire is wound. When a current passes through the wire, the coil becomes strongly magnetic, but when the current ceases, the magnetism does likewise.
- Q. When a bar of iron is placed partly in the coil of a solenoid through the winding of which a current is passed, what takes place?
- A. The bar is strongly attracted to the center of the coil and held there.
- Q. How is this principle taken advantage of in electric starting and lighting systems on the automobile?
- A. It is employed for the operation of electromagnetic switches for the starting motor, and it is also the principle upon which the electromagnetic gear shift depends for its operation.

- O. What effect has the insertion of an iron core in a solenoid?
- A. It greatly increases the flow of magnetism through the soleid, with the same amount of current passing through the winding the latter.
- Q. What effect has reversing the direction in which the current passed through the winding of a solenoid?
- A. It reverses the polarity of the latter so that if the core were a ir of hard steel, it would be drawn into the opening of the solenoid ith the current in one direction, and expelled from it when the current was reversed.
- Q. What bearing have the principles of magnetic attraction and pulsion and of magnetic polarity on electric generator and motor peration?
- A. They are the fundamental principles upon which the operaon of all electric generators and motors are based.

#### INDUCTION

- Q. What is the principle of electric induction?
- A. If a circuit carrying an electric current be opened and closed nickly in the case of direct current, and a coil of wire be held close this circuit, a current will be induced in the coil. If the latter be ound on an iron core, the induced current will be very much stronger, and if both the active circuit and the coil are on the same magnetic ore, the maximum inductive effect will be produced. The latter is, effect, a transformer, and if an alternating current be sent through



ingly magnetized to full strength with a certain polarity, is the demagnetized and again remagnetized with the opposite polarity, and it is this rise and fall in the strength of the magnetic field from zero to maximum, first in one direction and then in the other, that causes the inductive effect.

### Q. What is a cycle?

A. It consists of one alternation from zero to maximum in our direction, back to zero and then to the maximum in the opposite direction, and back again to zero. The ordinary house-lighting supply current is 60 cycles, i.e., it alternates 60 times per second, or 36000 times per minute. It is owing to this extreme rapidity in alternation that no flickering is apparent in an incandescent lamp fed by alternating current.

# Q. Where alternating current is not available, how can a transformer be operated?

- A. By making and breaking the circuit at a high rate of spect as with a vibrator used on automobile induction coils.
- Q. In general, why is no vibrator necessary on a coil where fed with current from the magneto?
  - A. Because the magneto supplies an alternating current.
- Q. On the so-called dual system of ignition, the same coil with out any vibrator is used with both the battery and magneto as a source of current. How is this effected?
- A. The circuit breaker, or interruptor, of the magneto takes the place of the vibrator when the battery is used. The current from the magneto alternates twice per revolution and the circuit is broken at the breaker points the same number of times.

# Q. What relation does the induced current bear to the current from the source of supply?

A. This depends upon the transformer and the purpose for which it is intended. On the automobile where it is desired to raise the current to a high voltage to enable it to bridge the gap of the spark plugs, the transformer is known as a step-up type, i.e., it takes current at a low voltage and transforms it to one of high voltage, or tension. The original, or primary, current passes through a winding of a comparatively small number of turns of coarse wire on a core of soft iron wires. Directly over this winding is a second one consisting of a great number of turns of very fine wire. This is known as the secondary

winding, and the current induced in it is termed a secondary current. The voltage of this secondary current depends upon the voltage of the source of supply and the proportion that the number of turns in the secondary winding bears to that of the primary winding.

- Q. Is the transformer used in any other form or type on the automobile?
- A. In the so-called true high-tension type of magneto, the transformer is made integral with the armature, the fine wire, or secondary winding, being placed directly over the coarser winding that serves to generate the current. The step-up is the only type of transformer used on the automobile.

#### CONDUCTORS

- Q. Do materials differ greatly in their ability to conduct electricity, and which are the most efficient in this respect?
- A. They vary all the way from absolute insulators to those metals which will pass the electric current with the minimum resistance, such as silver, copper, and aluminum.
- Q. Do the characteristics of a material affect its current-conducting ability?
- A. Very greatly. The harder copper is, the poorer its conductivity, and this is likewise the case with steel.
- Q. Name the different materials in the order of their current-conducting ability.
- A. Silver in pure state, soft copper, brass, aluminum, iron, steel, carbon, German silver, etc.; also water, depending upon how alkaline or acid it is.
  - Q. Is German silver a good conductor?
- A. No. It is known as high-resistance conductor and is accordingly used chiefly for winding resistances and not for the wires of a circuit.
  - Q. What are some good insulators?
- A. Wood, glass, resin, paraffin wax, silk, cotton, asbestos, rubber, and similar mineral or vegetable substances.
- Q. Are they always equally good insulators, regardless of their condition?
- A. They are efficient as insulators only when dry. The presence of moisture on any of them affords a path for the current to cross them.

- Q. What effect on the ability of the conductor to carry a current has the amount of material used?
- A. The resistance is increased with a decrease in size and is also increased directly as the length of the conductor.
- Q. Where, for mechanical or other reasons, it is not practical to use copper or aluminum, how can an equally efficient conductor of some other material be provided?
- A. By increasing the amount of material employed in the same proportion that its conductivity bears to that of copper. For example, assuming that steel is only one-thirtieth as good a conductor as copper, thirty times as much of it must be employed to give the same conductivity.
  - Q. Give an example of this?
- A. The single-wire system of connecting the starting and lighting outfit on an automobile. A small copper cable forms one side of the circuit, while the entire chassis forms the other. The ordinary trolley-road circuit is another, the small overhead wire forming one side of the circuit, and the rails on which the car runs, the other.
- Q. Name some of the materials which are employed for their high resistance to the current.
- A. German silver, iron wire, cast iron in the form of grids of small cross-section, and carbon. Very fine copper wire is also employed where the resistance desired is not very great, and space considerations permit its employment.
  - Q. What is meant by the "specific conductivity" of a material?
- A. Its ability to conduct the current as compared with that of pure silver which has a specific conductivity of one.
- Q. Does this ability of a conductor to convey the current vary particularly with a great increase in voltage?
- A. Yes. The so-called high-tension current which has been stepped-up in a transformer from the 6-volt potential of the 3-cell storage battery to many thousand volts for ignition purposes will cross surfaces and penetrate materials that are perfect insulators to the low-tension current. For example, the high-tension current will leak across a moist wooden surface or it will sometimes puncture the one-fourth inch of rubber and cotton insulation of the secondary cable.
- Q. What is one of the chief effects of transforming a current at a low voltage to one of high notential?

A. It enables the current to leap an air gap, the width of which is proportioned to the voltage itself. The greater the voltage the greater the width of the gap it will jump. This is the principle on which the spark plug is based.

#### **HIGH-TENSION CURRENTS**

- Q. When a current of 2 amperes at 6 volts, such as would be consumed by the ordinary ignition coil from a storage battery, is transformed to a high potential, is the amount of current still the same? In other words, can 2 amperes at 6 volts be transformed or stepped-up to 2 amperes at 10,000 volts?
- A. No. The current decreases as the voltage increases. For example, to make the comparison more clear, consider a current of 10 amperes at 100 volts. This is passed through a step-up transformer, of which the ignition coil is a type, and is given a potential of 1000 volts. The current, however, would then be 1 ampere, that is, the current decreases in the same proportion that the voltage is increased. The opposite is also true. By passing this current of 1 ampere at 1000 volts through a step-down transformer, it may be converted into a current of 100 amperes at 10 volts. It will be noted that the product of volts times amperes in any of the above instances cited, or of any possible combinations that can be made, is always the same. In other words, a certain amount of energy is sent through the transformer, and the same amount, barring losses due to the transformation process itself, is taken out.
- Q. Is there any mechanical analogue of this process of transforming a current up or down to impress upon it a greater or lesser potential?
- A. There is nothing in mechanics that corresponds exactly to this peculiar property of electricity. The resulting change in the form in which the energy is applicable as a result, however, may readily be compared with mechanical standards. For example, we may have in a very small boiler, a pressure of 1000 pounds to the square inch, but a volume of only one cubic foot of steam. This small amount at its high pressure represents the equivalent in energy of 10 cubic feet of steam at a pressure of 100 pounds.
- Q. What is the object of stepping the current up to such high voltages?

A. On the automobile, simply to enable it to jump the gap of the spark plug and fire the charge. In ordinary commercial service, to permit of sending it long distances with a minimum expenditure for copper wire and a minimum loss in the amount of energy transmitted.

### **CIRCUITS**

- Q. What is meant by an electric circuit?
- A. The path by which the electrical energy, or current, is said to flow from and return to its source.
- Q. Is a circuit absolutely necessary in order to permit of utilizing electricity?
- A. Unless there is a circuit or complete path for the current, it does not flow.
- Q. Must a circuit be comprised completely of wires leading from, and returning to, the source, such as the battery or generator?
- A. No, it is not necessary that wire be used for both sides of the circuit. One side or the other may be composed of a ground, such as the tracks of a trolley system, the overhead wire constituting the other side of the circuit, or in the case of a single-wire lighting and starting system in which one cable is employed to conduct the current from the battery to the starting motor and lights. and the chassis itself forms the ground return for both.
  - Q. How many forms of circuits are there in general use?
- A. Three: the series, the multiple, and the series-multiple. In the first, all apparatus in the circuit is in series. That is, all the current from the source must pass through each instrument or light in turn to complete the circuit. In the multiple type of circuit, every instrument or light on it is independent of all the others. Lights may be turned on or off, motors started or stopped, without interfering in any way with any of the others. As its name indicates, the series-multiple is a combination of the two forms of circuits. For example, in using incandescent lamps to cut down the current for charging a storage battery from the lighting mains, the lamps themselves are in multiple, but the whole bank of lamps is in series with the storage battery. See illustration on charging storage battery direct from lighting mains.

# Q. Which of these forms of circuit is in most general use on the automobile?

A. All three will be found on practically every car equipped with a starting and a lighting system. For instance, the starting motor is operated in series with the battery, while the lamps are wired in multiple for the side and head lights, and the speedometer and tail light are wired in series as a branch of the multiple-lighting circuit, thus giving a series-multiple circuit. The ignition distributor, coil, and battery are in series.

### Q. What is meant by a grounded circuit?

A. This is ordinarily used to indicate that through lack of insulation at some part of the wire, or similar injury, the circuit has been shortened, owing to this bare wire touching a ground, thus permitting the current to return to its source without passing through whatever instruments there may be on the circuit. A grounded circuit, however, is also one in which one side consists of a ground return instead of having two wires. This is frequently distinguished by being termed a ground-return circuit.


### O. What is a short-circuit?

A. As the term indicates, a completion of the circuit short of the point or apparatus which the current is intended to reach. The example just cited is a short circuit as well as a ground, sometimes termed a grounded short-circuit. In other words, the abrasion of the insulation of one of the conductors has permitted the current to
 
#### HYDRAULIC ANALOGUE

- Q. What is a hydraulic analogue, and what bearing has it on an electrical system?
- A. It is a comparison of the electrical system with a hydraulic or water-pressure system and serves to make clear the resemblance or analogy that exists between the principles upon which both operate.
- Q. What type of hydraulic system is similar to an electrical system consisting of a generator, external circuits, and lamps, motors, or the like, as a load?
- A. A constant-pressure system in which the pumps keep the water in the pipes under a certain amount of pressure corresponding to the demand. When the demand increases, the supply does likewise and *vice versa*. (In the case of the pumping system, this is not automatic, but is controlled by the attendant.)
- Q. To what does the pressure of such a pumping system correspond in the electrical system?
  - A. To the voltage, or electromotive, force.
- Q. Can there be voltage, or potential, in an electrical system without a flow of current?
- A. Yes, exactly as in the pumping system in which there is always a constant pressure on the water in the pipes whether the water is escaping through any of the outlets or not. In other words, there may be pressure but no flow. The same thing is true of the generator. If it be turning at its normal speed and is wound to produce current at 100 volts, there will be a potential of 100 volts across its terminals, even though there are no lamps or motors switched on in the external circuit.
- Q. How does the resistance of the pipe lines in the water system compare with the resistance of the wires in a circuit to the electric current?
- A. It is nearly the same. It varies inversely as the size of the pipe and directly as its length. The smaller the pipe the greater the resistance per foot; the longer the pipe the greater the total resistance. In the same way, the resistance to the electric current increases with the decrease in the size of the wire and increases with the length of the wire, the chief difference being that bends or turns in the wire do not add to the electrical resistance, whereas bends in the pipe impose greatly added resistance to the flow of water.

- Q. What comparison may be made between the speed at which the generator and the pumps run?
- A. The greater the speed, the greater the pressure in the case of the pumps, and of the voltage in the case of the generator. Below a certain speed, usually termed the normal speed, there is a sharp falling off in the pressure in both. Neither can be operated safely at an excessive speed.
- Q. What is the cause of the increase in voltage with increasing speed in the case of the generator?
- A. Voltage, or electromotive force, is generated by the coils, or windings, of the armature cutting the magnetic lines of force of the field of the generator. The greater the number of times that these coils pass through the lines of force per minute, the greater the voltage will be.
  - Q. How does fall in pressure correspond to voltage drop?
- A. To reach the end of the piping system, the water must overcome the resistance of the latter to its passage, and the friction involved robs it of some of its pressure in overcoming this resistance. Consequently, there is less pressure at the outlet a mile away from the pumps than there is at the pumps themselves. The same thing is true of the electric circuit. The current must force its way through the wires by reason of its voltage or pressure and, in so doing, some of the voltage is lost in overcoming the resistance of the wires, joints, switches, and the like. In both cases allowance for this loss is made



connections, dirty switch contacts, dirty commutator, and worn brushes are apt to increase the resistance to a point where the voltage drop is in excess of this, the importance of properly maintaining these parts of the system may be appreciated.

- Q. How does the flow of water correspond to the flow of current?
- A. In both cases, the amount is proportionate to the resistance of the outlet and to the pressure back of the current, whether water or electricity. In other words, the volume of water that will flow depends upon the size of the outlet (the smaller the outlet the greater the resistance to the flow) times the pressure back of it. In the same way the number of amperes that will flow when the circuit is closed depends upon the voltage of the circuit divided by the resistance (Ohm's law). For example, the ordinary 16 c.p. carbon-filament lamp for a 110-volt circuit has a resistance of 220 ohms, which, divided by 110, gives  $\frac{1}{2}$  ampere as the current that will flow when the lamp is switched into the circuit.
- Q. Can the piping system properly be compared with an electric circuit?
- A. In practically every way except that of the return required for the latter. For example, the opening of a series of outlets in the piping system reduces the pressure in proportion to the number opened; so in connecting a number of different pieces of apparatus in series in an electric circuit, the voltage through each will decrease as another is added. It may also be compared with a parallel or multiple circuit in that the opening of one outlet does not prevent drawing water from another. A break in a main corresponds to a short-circuit or a ground in that no water can then be drawn from any outlet beyond the break. The comparisons between the piping system and the circuit are not exact, owing to the lack of any necessity for a return in the case of the water piping, but they serve to make clearer some of the fundamentals of the electric circuit.

### **GENERATOR PRINCIPLES**

- Q. What makes it possible to generate a current of electricity by mechanical means?
- A. The fact that electricity and magnetism are different manifestations of the same force and that, given one, the other may be

produced. Also the fact that they are readily interchangeable, i.e., one may be readily converted into the other.

- Q. On what fundamental principle does the generation of electricity in this manner depend?
  - A. That of induction.
  - O. How is it utilized?
  - A. By revolving a coil of wire in the field of a magnet.
  - O. What occurs when this is done?
  - A. An e.m.f. is generated in the coil.
  - Q. Describe the simplest form of generator.
- A. Such a generator consists of a horseshoe magnet between the poles of which a coil of wire is revolved.
- Q. What governs the strength of the e.m.f. or potential, thus generated?
- A. The speed with which the conductor or wire revolves, or is said to "cut the lines of force" of the magnetic field.
  - Q. How can this potential be further increased?
- A. By winding the coil of wire on an iron core, as the iron becomes strongly magnetic and greatly increases the inductive effect.
- Q. What is this simplest form of generator consisting of horseshoe magnets for the field and of a single winding on an iron core termed, and for what is it employed on the automobile?
- A. It is known as a magneto and is generally employed for producing the current needed for ignition purposes.
- Q. Can such a generator be directly employed for charging a storage battery or for lighting lamps?
- A. No, it cannot be used for charging purposes, since it generates an alternating current. Moreover, owing to the small number of poles (two), its single winding, and the high speed at which it is driven, it produces very little current but a high e.m.f., as this is desirable for ignition. It cannot be used for lighting purposes for the same reason, i.e., the simple winding produces an alternating current with a very perceptible interval between the alternations, or cycles, so that a lamp would flicker very badly. As its e.m.f., or voltage, is proportionate to its speed and as there is no method of controlling it, the lamp would be burned out as soon as the magneto was speeded up.
  - Q. What are the essentials of this simple form of generator?

- A. The field consisting of the horseshoe magnets, and the armature consisting of a soft iron or steel core, usually in the form of an H, in the slots of which, the single winding of comparatively coarse wire is wound.
- Q. Why is the field of a magneto usually referred to as a "permanent field?"
- A. Because it consists of so-called permanent magnets. Naturally, they are not permanent in the real sense of the word, but their magnetism is constant while it lasts and it decreases only very gradually under the influence of heat and vibration.
- Q. Why does heat affect the magnetism of the field of a generator of this type?
- A. Because a piece of hard steel that is strongly magnetic when cold loses its magnetism altogether when raised to a sufficiently high temperature. In other words, if heated to a bright red and then cooled, it is no longer a magnet, and the steel must be remagnetized. Constant vibration has the same effect, but it is much slower.
- Q. Is there any other way of increasing the voltage of such a generator besides running its armature at a higher speed?
- A. Yes, by increasing the number of turns of wire in the winding, which has the same effect as revolving a single coil at a higher speed.
- Q. How is the current produced by a simple form of generator, such as the magneto, conducted to an outside circuit?
- A. Ordinarily, this would be done by means of slip rings, i.e., plain bands of copper mounted on the armature shaft with narrow copper brushes bearing on these rings, as is the case with large alternating-current generators. But as the ignition system of the automobile is a grounded circuit, one end of the armature winding of the magneto is connected directly to the core of the armature, and the other is led to a small V-shaped ring or to an insulated stud on the end of the shaft against which either a copper or a carbon brush is held by a small spring.
- Q. What is the cause of the alternating cycle of the magneto, and at what points in the revolution of the armature does it occur?
- A. In revolving in the field of the magnets, the armature passes successively from the field of influence of a north pole to one of opposite polarity, so that the direction of the e.m.f. is reversed.

When the armature is in a horizontal position in the field, the e.m.f. curve is at zero; as it turns, the edges of the armature core pass the ends of the pole pieces of the field, and the e.m.f. rises sharply to a maximum as the central line of the core passes the ends of the poles, when it is said to be cutting the maximum number of lines of force. It drops off again quickly from this point and again reaches zero, when the armature is in a vertical position. As its ends come under the influence of opposite poles, the curve again rises, but is now in the opposite direction, or of opposite polarity. In other words, it passes from zero to maximum and back again in every half revolution, or 180 degrees.

- Q. How can a generator be made to produce a direct, instead of an alternating current?
- A. The current is always alternating as generated in the armature, but it may be conducted to the outside circuit as a unidirectional, or so-called direct, current by the addition of a commutator.
- Q. Can such a current be produced by the addition of a commutator to the simple single-coil winding already mentioned in connection with the magneto?
- A. Yes, but as the commutator would have but two parts, the e.m.f., while passing in one direction, would be strongly pulsating.
- Q. What is a commutator and how does it convert the alternating current produced in the armature to a direct current in the outside circuit?



# Q. How is the pulsating nature of the direct current thus generated overcome?

A. By adding coils and commutator bars to the armature so that new coils come into action before the e.m.f. produced in those just preceding them under the brushes has an opportunity to drop much below the peak or maximum. Thus, only the peak of the wave is utilized, and the e.m.f. of a direct current consists of a series of these wave peaks overlapping one another.

### Q. Are permanent magnets used for the fields of all generators?

A. No, only for those of magnetos. In other types, an electromagnetic field is used.

# Q. What are the advantages of the permanent field for use in connection with the magneto?

A. It is always at its maximum strength, so that the magneto generates a powerful e.m.f., even though turned over very slowly. Regardless of the speed of the armature, the strength of the field remains the same, so that no controlling devices are necessary to prevent the armature from burning out, owing to excessive speed.

## Q. What is an electromagnetic field and how is it produced?

A. It is based on the fact that when a current of electricity is sent through a winding surrounding an iron core, the core becomes strongly magnetic. It accordingly consists of windings on the fields of the generator, in addition to those on the armature. Depending upon the particular type of generator in question, either all or only part of the current produced in the armature is sent through the windings of the field. The latter is then said to be self-excited in that it depends upon no outside source.

# Q. Is the self-excited field characteristic of all generators except the magneto?

A. Yes, of all direct-current generators. Large alternating-current generators are said to be separately excited, a smaller direct-current generator being employed solely for the purpose of rendering the fields of the larger machine magnetic.

# Q. What is a series-wound generator, and why is this type not used on the automobile?

A. It is one in which the entire current generated in the armsture is passed through the field windings. It does not generate until a high speed is reached. Its voltage varies sharply as its speed, and


it may have its polarity reversed by the battery if its speed drops below a certain point, consequently, it is not fitted for charging storage batteries. (In fact, the series-wound generator is practically obsolete, except for some special uses.)

### Q. What are shunt- and compound-wound generators?

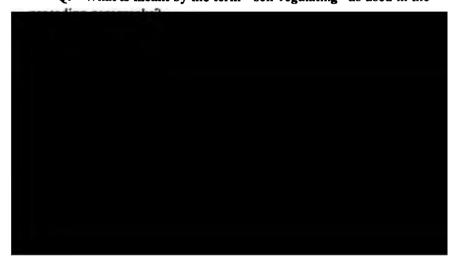A. In the former, the windings of the armature and of the fields are in multiple, or shunt, so that only a certain amount of current, depending upon the difference in the resistance of the outside circuit and that of the fields, passes through the windings of the latter. As the load and consequently the resistance of the outside circuit increases, more current passes through the shunt, and the fields become more strongly magnetic, thus increasing the output so that the generator is, to a certain extent, self-regulating.

In the compound type, there is, in addition to the main shunt winding on the fields, an auxiliary winding of heavier wire (lower resistance) which is connected in series with the armature. As in a series-wound generator, the amount of current exciting the fields is directly proportional to the speed, more current in proportion passes through the compound winding than through the shunt winding as the load is increased, and the generator is self-regulating to a much greater degree. The compound-wound type of generator is in practically universal use on the automobile as well as for general power purposes. See Figs. 31 and 32.

Q. What is meant by the term "self-regulating" as used in the



- Q. What is meant by the "load" on a generator?
- A. The lamps, motors, storage battery, or similar apparatus to which it is supplying current.
- Q. As the speed of the generator itself does not increase, how does it provide for an increase in the load?
- A. By absorbing more power from its driving unit. For example, if a generator be operating with only ten 100-watt lamps in the circuit, it is requiring approximately one and one-half horsepower to drive it. Now, if another group of ten lamps of the same size be switched on, the amount of power demanded by the generator of its engine will be doubled. This may be very readily demonstrated in a rough way by fitting a handcrank to any small automobile generator and turning the machine over with one lamp in the outside circuit. It will be found very easy to spin the generator very rapidly by hand, as practically no resistance is felt. Now connect in the circuit a discharged storage battery, and the additional power required to turn the machine will at once be very perceptible.
  - O. What are the brushes and what purpose do they serve?
- A. They are strips of copper or carbon (the latter is now almost universally used), which serve to conduct the current generated in the armature to the outside circuit and to the field windings by bearing on the revolving commutator. Except where an additional brush is employed for regulating purposes, there is usually one brush for each pole of the field, i.e., a bipolar generator is fitted with two brushes, a four-pole with four brushes. The brushes are held against the commutator by springs. Soft copper embedded in carbon is also employed, especially for low-voltage generators, such as the lighting generator on the automobile.

#### **ELECTRIC MOTORS**

- Q. Is there any difference in principle between the electric generator and the electric motor?
- A. Fundamentally, they are the same, as is evidenced by the fact that either is reversible, that is, an electric generator, when supplied with current from an outside source (of the proper voltage, of course), will operate as a motor, and a motor, when driven by an outside source of power, will generate an electric current. They are naturally not interchangeable in practice, owing to differences in

design and winding. The generator is wound to produce the maximum amount of current at a certain voltage with a given horsepower, while the motor is designed to produce the maximum amount of power with the minimum current.

- Q. What is the operative principle of the electric motor?
- A. That of magnetic attraction and repulsion.
- Q. How is it applied?

As in the generator, both the fields and the armature of the motor consist of electromagnets. The brushes and the commutator serve the same purpose of reversing the direction of the current through the armature coils every time a different pair of commutator segments passes under the former. As has already been explained, reversing the direction of current flow through the winding of an electromagnet reverses the polarity of the magnet itself. To simplify the illustration, take a bipolar motor with a two-pole armature having but a single winding. When the current is switched on, the armature is at a 45-degree angle, so that its poles are just under the poles of the field. As the commutator causes the current to flow through the armature winding in a reverse direction to that of the fields. unlike poles will be created. They will attract each other, and the armature will revolve a small part of a revolution, until it is directly in the strongest part of the field of the influence of the field magnets. Just as this point is reached, however, the brushes pass on to new segments of the commutator, and the direction of the current in the


operation, thus reducing the amount of current necessary to drive it. For example, when the motor is standing idle, the resistance of its windings is low. It is for this reason that large direct-current motors (one h.p. or over) cannot be started without the aid of an outside resistance to cut down the starting current, otherwise the armature would be burned out. As the armature speeds up, the counter e.m.f. generated opposes that of the driving current and accordingly increases the resistance. The heating of the windings in operation further serves to increase the resistance, as the resistance of most metals increases with a rise in their temperature.

- Q. How many types of motors are there, and what type is most generally used for automobile starting?
- A. As they correspond exactly to generators, there are the same number of types, i.e., series, shunt, and compound wound. The series type is almost universally employed on the automobile and is also very largely used on trolley cars.
- Q. If the series-wound generator is of so little practical application, how is it that the series-wound motor is found so advantageous?
- A. The same characteristics that are a disadvantage in the generator are correspondingly valuable in a motor, which explains why generators and motors are not interchangeable in practice, as already mentioned. A series-wound machine is essentially a variable-speed machine, and this is not desirable in a generator, while it is in a motor. The series type of motor has a very heavy starting torque, or pull, which increases as the speed of the motor decreases. This is exactly what is wanted to overcome the inertia of the gasoline engine. Its current consumption falls off very quickly as its speed increases, and it has a very liberal overload capacity, being capable of carrying loads up to five times the normal, for short periods.
- Q. As the speed of the series motor decreases in proportion to the load, what happens when the load is suddenly relieved as in the starting of the gasoline motor?
  - A. The electric motor tends to race, or run away.
  - Q. How is this prevented on the automobile?
- A. The method employed differs in different systems, but, as a rule, the starting of the gasoline engine automatically opens the starting motor circuit, or means are provided for greatly reducing the amount of current it receives the moment the load is removed.

- Q. Are either shunt- or compound-wound motors used on automobiles?
- A. They are employed on electric vehicles, but not often in connection with the starting systems used on gasoline cars.
  - Q. What is a motor-generator, and what is it employed for?
- A. As its name indicates, it consists of two units, a motor and a generator, the former having an alternating current, and the latter a direct current. It is employed for converting an alternating current into a direct current, so that it may be utilized for charging storage batteries. The alternating-current supply is used simply for running a motor of that type to which is directly coupled a direct-current generator. There is no electrical connection between the two machines.
  - Q. Are motor-generators ever used on automobiles?
- A. No, but the combination of a direct-current generator and a starting motor in one machine, as in the single-unit systems, is frequently so-called through error. This single unit is variously termed a dynamotor and a genemotor to distinguish it from a motor-generator.
- Q. How are the two radically different purposes for which the generator and the motor must be designed combined in one machine?
- A. By putting independent windings on the fields and the armature, and, in some instances, by employing two commutators at different ends of the armature shaft.

#### BATTERIES



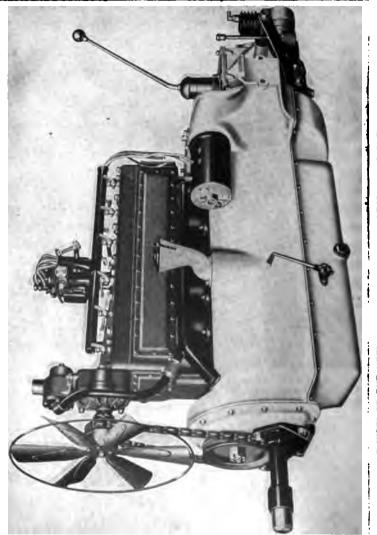

SIDE VIEW OF THE NEW PACKARD SINGLE-SIX MOTOR, 1920 MODEL. SHOWING THE STARTING AND IGNITION MOUNTING

# LECTRICAL EQUIPMENT FOR GASOLINE CARS


### PART II

### IGNITION
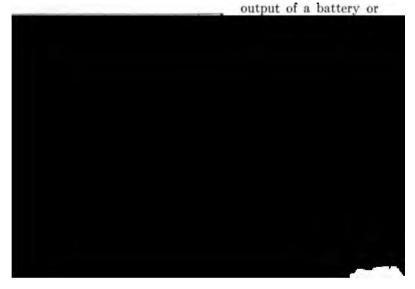
### **FUNDAMENTAL IGNITION PRINCIPLES**

aulty Ignition Cause of Much Early Trouble. More than of the troubles encountered by the designers and the drivers early automobiles were the direct results of the extremely ignition systems at first adopted. With knowledge of gasonotor operation generally scant at that time, much of this le was attributed to causes entirely foreign to its real source general principles, the motor was roundly "cussed" as a and unfathomable mystery. Subsequently it became plain much of this inexplicable tendency to balk was due to the eness of the electric current. Crude insulation and contacts, ently defective spark plugs, and extremely wasteful currenting devices, fed from a weak source, were the causes.

Distinctions between Low Tension and High Tension. A ension ignition system uses a low-tension current—i.e., the



to as a secondary current It is the result of induction and is commonly termed a high-tension current owing to its great voltage or potential. The battery produced current of high amperage value at 6 to 8 volts, which after being passed through the coil became a current of microscopic amperage value at anywhere from 10,000 to 25,000 volts, according to what the designer of the coil thought was sufficient potential to produce a good spark, that is, to enable it to readily jump the gap in the points of the plug. The curve, Fig. 37, shows the voltage necessary to force a spark across a given distance in air under various pressures.

As the low-tension current will not jump an air gap, a further distinction between the two systems is the employment of totally


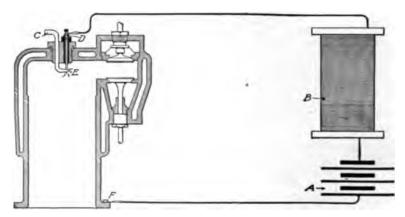


Fig. 38. Diagram of Low-Tension Ignition System

different types of spark plugs. In the former, a mechanically operated plug, i.e., one that is held closed until the maximum current is passing through it and is then suddenly opened by being mechanically tripped by a cam or rod operated by the engine, is essential. Such a plug produces a spark that is immensely superior in heating value and, consequently, in igniting ability, to the usual thin spark that bridges the gap of a high-tension spark plug. But this most desirable quality is likewise quickly destructive of the contact points, necessitating frequent readjustment of the mechanically operated plugs. Moreover, the mechanical lag or time element of operation, due to the inertia of the numerous moving parts, rendered it difficult to make a low-tension spark plug suitable for a high-

speed engine without resorting to the most expensive machine work, and much greater skill was necessary for their proper adjustment.

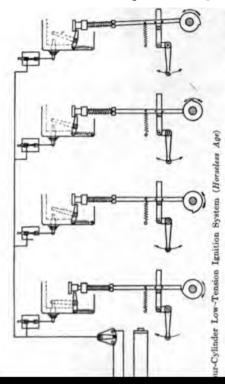The shortcomings of the original high-tension systems were so



glaring, however, that some of the most successful automobiles of earlier days were fitted with low-tension ignition.

Low-Tension System. Fig. 38 shows diagrammatically the essentials of a low-tension system for a single-cylinder motor, while Fig. 39 shows a complete low-tension system for a four-cylinder motor. The details of the operating mechanism and the plug are shown in Figs. 40 and 41. Referring to Fig. 38, A is the battery, B is a spark coil (a single coil which by its self-induction develops a high-voltage spark), and C, D, and E are the elements of a makeand-break device that is mechanically actuated at regular

slight rocking movement. For the best results this rocking movement must be very sharp and rapid, in the nature of a snap, and it must, of course, be correctly timed to occur in proper relation to the moment when the spark is required. (See also Fig. 41.)

The chief advantage of lowtension ignition is its immunity from troubles caused by short-circuiting by leakage of the current through poor insulation or across moistened termi-This led to its almost universal employment on motor boats for a number of years, but it has since been generally abandoned even for marine use so that it is now only to be found on stationary engines, the low rotative speeds of which make it practical. So far as the automobile is concerned, the low-tension system is only of historical interest as it is already several years since it was wholly discarded.

High-Tension System. High-tension ignition systems are based on the fact that when a sufficiently high potential is impressed upon a current of electricity, it will leap an air gap or other break in the circuit of a width dependent upon the potential or voltage itself. In bridging such a gap, the current becomes visible in the form of an arc, flash, or spark, depending upon its duration and intensity, and it will readily ignite a gasoline or other gaseous fuel mixture. Its

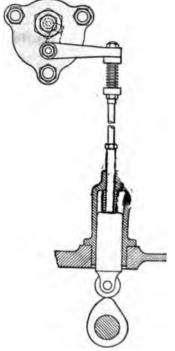


Fig. 40. Make-and-Break Mechanism.

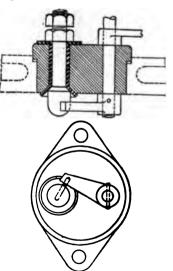


Fig. 41. Low-Tension Spark Plus (Horseless Age)

very ability to do so, however, was one of the most prolific sources of trouble in the early days, as the designer's conception of the insulation required to conduct such a current without grounding or short-circuiting was far from approaching the reality.

The essentials of a high-tension system are shown diagrammatically in Fig. 42. A is the source of current, usually a battery in earlier days, as indicated by the conventional sign, placed in a primary circuit that also includes the contact maker C, the primary winding of the coil B, and the vibrator G. The contact maker C is positively driven by a connection with some revolving part of the motor, so that it makes contact at the exact time ignition is required in each cylinder.

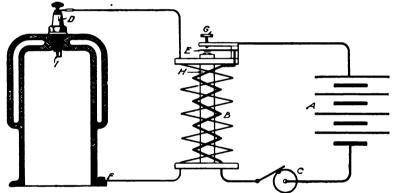


Fig. 42. Diagram of High-Tension Ignition System



This briefly describes what may be termed the rudiments of a high-tension ignition system and the diagram shows their relation to one another. Of course, this simply has reference to a single-cylinder motor. For each extra cylinder in an ignition system of the type illustrated, there is another contact point on the timer and another coil. The timer or contact maker is sometimes referred to as an interrupter, though this is not technically correct as its function is first to close the circuit.

### SOURCES OF CURRENT

Up to about 1905, batteries were universally relied upon in this country for ignition work, the only exceptions to this being a few high-priced imported cars, some of which had magnetos operating low-tension systems with the so-called make-and-break spark plugs, while one or two, notably the Panhard, was equipped with the Eisemann magneto, designed to operate a non-vibrator coil. The writer imported the second of these magnetos to be brought into this country in the latter part of 1902, but the principles of its operation were so little understood, despite the fact that the magneto had been used in hand-ringing telephones for a generation, that automobile designers were frankly skeptical regarding it, and only the few electrical men then in the industry had the slightest conception of its possibilities. In fact, Mr. J. M. Packard, then head of the Packard Company, was the first man out of dozens to whom it was shown to realize what the magneto meant to automobile ignition.

### CHEMICAL SOURCES OF CURRENT

Primary Batteries. In the face of the advent of the magneto (1902), the majority of American designers preferred to stick to the battery, usually the dry cell. The term dry cell is really a misnomer, since a cell of this type consists simply of a zinc element constituting the case of the cell, a carbon element centered within this, and an electrolyte composed of a moist paste of suitable chemicals. The top of the cell is commonly sealed with pitch or wax compound to prevent the moisture from evaporating, and if by any chance the cell does become really "dry", its usefulness is then at an end.

Defects of Dry Cells. The chief defect of the dry cell is that it is an "open-circuit" battery, that is, the circuit is normally open and when closed for a brief period the cell will produce a heavy cur-

rent, at a low voltage, i.e., 1½ volts on the average. But to enable it to do so, the time of contact must be brief and the periods of rest frequent. Otherwise, the cell becomes "polarized". The hydrogen generated as the zinc element passes to the carbon element in such volume as to completely cover and insulate it from the active material of the cell, consisting of a solution of sal-ammoniac and water. use of a depolarizer, usually manganese dioxide, prevents this to a certain extent, but not sufficiently to avoid having the current output of the cell fall off very rapidly if the contact exceeds a few seconds. But as soon as the circuit is broken again, the hydrogen is rapidly dissipated and the cell is said to recuperate. It was the marvelous ability of the dry cell to recuperate rapidly after having been run down to a point where it no longer produced sufficient current to pass a spark at the plug, that led to so much dissatisfaction and to such a misunderstanding of the gasoline engine in the earlier days. With the extremely wasteful contact makers then used, a set of cells would run an engine satisfactorily for an hour or so, then it would begin to miss firing badly and soon stop. Inspection would reveal no sign of current. If a new battery were installed, the • engine would again run satisfactorily, and the motorist usually decided that the old cells were "dead". If, however, the inspection consumed ten or fifteen minutes, the battery recuperated and upon being cranked the engine again ran, only to repeat the performance a short time later.

Liquid Batteries. The dry cell is, of course, one form of primary battery, this term being used to distinguish it from other forms in which the exciting chemicals are in liquid solution. Few attempts have been made to employ the latter type of battery for automobile ignition, due to the violent agitation of the liquid which would necessarily ensue from the vibration and jolting. The Edison-Lalande cell and a few others of similar character, in which the charging chemicals were supplied in convenient units ready for quick replenishing when the battery "died", were tried in isolated instances but never met with general application, except on the motor boat, where the Edison-Lalande cells have been widely used.

Storage Cells. The construction and advantages of the storage cell as well as its operation and handling are detailed at length in "Electrical Equipment," Part VII. Due to its ability to provide a

very much greater supply of current, it soon displaced the dry cell on all except the then lower-priced cars. While it represented a great improvement, the wastefulness of the contact maker and of the coil vibrators proved too much of a drain on even the storage battery, and it was accordingly displaced by the magneto. All modern cars are equipped with an electric starting and lighting system; this necessitates the use of a storage battery. A generator is used to charge the battery, and as it is both expensive and unnecessary to provide two charging instruments—magneto and generator—the magneto has been practically discarded on the pleasure cars.

### **VOLTAGE AND SPARK CONTROL DEVICES**

Changes in Ignition Methods. Up to a few years ago, it was generally considered that the magneto practically represented the

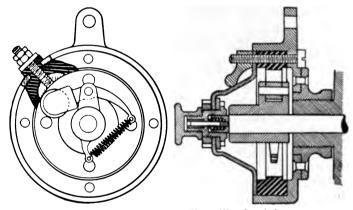


Fig. 43. Roller Contact Timer (Horseless Age)

ultimate type of ignition current generator and that batteries would never play anything but a secondary rôle. Small direct-current dynamos had been tried in a number of instances, chiefly prior to the advent of the magneto, but they were not then sufficiently developed for this form of service and proved quite as unreliable as the dry cell. The magneto was entirely dependable, made possible much greater speeds, and had few shortcomings, none of which were of a serious nature, so that its position was deemed impregnable. This was prior to the successful development of electric-lighting dynamos on the automobile, and more particularly the combined lighting and starting systems which are now in such general use.

The latter, in conjunction with improved forms of contact makers, has been responsible for bringing about a reversion to former practice with improved equipment.

Contact Makers or Timers. Roller Contact Timer. It was largely due to the crudity of the timing device that so much difficulty was experienced with early ignition systems. As the term indicates, the timer closed the circuit through the coil at exactly the moment necessary to produce the spark in the cylinder ready to fire. But the long wiping or rolling contact usually employed was so

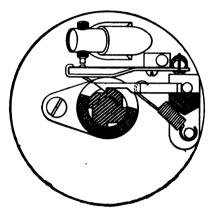


Fig. 44. Atwater-Kent Interrupter Atwater-Kent Manufacturing Works, Philadelphia, Pennsylvania

wasteful of current that it quickly exhausted even a storage battery. Fig. 43 shows a roller contact timer. The coil vibrators were another serious source of loss.

Atwater - Kent Interrupter. The difficulties with roller contact led to the adoption of a totally different principle embodied in the Atwater-Kent interrupter, Fig. 44. This affords an exceedingly brief contact with an abruptness of the making and breaking of the circuit that is not secured with any other device.

The effect is to produce a strong current surge and a heavy spark, but of the briefest possible duration.

The advantage of the brief duration is that great current economy is realized. The fact that only one spark is required for each ignition is an important contributing element to this economy.

With the Atwater-Kent interrupter, embodied in a distributor termed the "Unisparker", it is possible to run a car much further on a set of dry cells than could formerly be done with a storage battery, two to three thousand miles on four or five dry cells being nothing uncommon. This has led to the development of other devices along similar lines, and, with the unfailing source of current now provided by the lighting dynamo and the storage battery which forms part of the system, battery ignition has been raised to a level where it is now almost the equal of the magneto. But before

making further mention of that phase of the subject, it is necessary to refer to the coil in order to give a clear understanding of the matter.

Coils and Vibrators. Function of the Coil. Mention has already been made of the function of the induction coil or transformer in stepping up the voltage of the current in order that it may bridge the gap in the spark plug. A coil is also employed in connection with a low-tension system, but it is simply a single winding on an iron core which intensifies the current by what is known as self-induction. Though it raises the voltage by what may be termed the accumulation and sudden release of electrical energy acting in conjunction with a magnetized core, due to the sudden making and breaking of the circuit, it is not an induction coil as that term is ordinarily employed.

As shown by Fig. 42, the latter has two distinct windings, one of a few turns of comparatively coarse wire and the other of many thousand feet of exceedingly fine wire, with high-grade silk insulation. After completing the coil, consisting of two superimposed windings and an iron-wire core passing through their center, it is placed in a wood box which is filled with melted paraffine wax which, upon solidifying, greatly enhances the resisting power of the insulation to breakdown, due to the great difference in potential between various parts of the secondary winding. To set up an induced current in the secondary winding, the primary circuit must be quickly opened and closed.

Necessity for Vibrator. The breaking of the primary circuit is accomplished by the use of a vibrator, a typical form of which is illustrated at E, G, and H, Fig. 42. This consists simply of the thin blade of spring steel at E, provided with an armature at the free end to intensify the attraction of the coil H, and adjacent to the adjusting screw at G, by which the distances between the contact points can be accurately set. In addition to these elements it is usual to provide a screw adjustment for increasing or reducing the tension of the vibrator blades.

Contacts in the best vibrators are made of platinum, or, better still, of platinum-iridium alloys, which are very hard as well as extremely resistant to the very high, though brief and localized, temperatures of the small arcs that form across the terminals each time the contacts are separated. In cheaper coils, German silver, silver, and other metals often are much used for contact points, but the only advantage of these over platinum or platinum alloys is their lower price.

Complication of Multi-Vibrator. A vibrator coil is necessary for each cylinder, each coil being energized as the timer passes over the contact corresponding to it, thus putting it in connection with the battery at the moment that particular cylinder is to fire. Fig. 45 shows a four-unit coil, i.e., for a four-cylinder motor. However, the coil cannot act before its core becomes "saturated", that is, thoroughly magnetized, and it must then pull its armature down against the tension of its spring, so that there is both an electrical and a mechanical lag, or, in other words, an appreciable amount of time elapses between the moment the circuit is closed by the timer



Fig. 45. Pittsfield Multi-Vibrator Coil Courtesy of Pittsfield Spark Coil Company, Dallon, Massachusetts

and that at which it is again broken by the vibrator to cause the spark in the cylinder. A delicate adjustment is most sensitive and minimizes the lag besides economizing on current, but it is difficult to maintain. A stiff adjustment, on the other hand, will remain operative for a longer time, but its greater



takes the place of the four vibrators on the original coils, so that the extra coil is termed a master vibrator. In operation, all four of the original vibrators are screwed down hard so as to make a permanent connection, and the fifth coil is connected in the primary circuit so that the action of its vibrator breaks the circuit in the

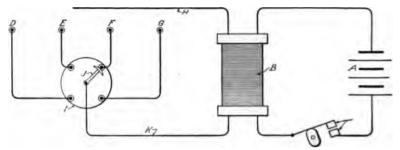


Fig. 43. Wiring Diagram of Non-Vibrator High-Tension System

primary of each one of the coils in turn. It is accordingly only necessary to adjust a single vibrator, and regardless of whether this adjustment be good or bad, it is uniform for all four cylinders so that they fire with the same timing. But at the best, the arrangement is

only a makeshift as the vibrator coil long ago ceased to have any legitimate excuse of existence on the automobile.

Non-Vibrator Coil. As the term indicates, this is simply an induction coil minus the vibrator. But instead of using four coils, as with the vibrator type, a single coil is employed, and a distributor is inserted in the secondary or high-tension circuit. The essentials of such a system are shown by Fig. 46, a battery being indicated as the source of current. The timer C is driven by the camshaft of the motor so that the battery circuit is suc-



Fig. 47. Atwater-Kens Distributor

cessively closed and opened in the usual firing order of the cylinders, four contacts being made for each two revolutions of a four-cylinder four-cycle motor. The contact is of sufficient duration to permit the coil to "build up", i.e., to have its soft iron core become thoroughly magnetized, and is then quickly broken. At the instant that the latter occurs, the finger J of the distributor is passing the contact of the

cylinder F to be fired. The timer and distributor must accordingly be driven synchronously, so that the contacts in both occur simultaneously. This is accomplished by combining them in a single unit, as shown in Fig. 47, illustrating the Atwater-Kent "Unisparker", or as in the various types of magnetos illustrated further along.

Limitations of current supply having been overcome by the adoption of the magneto or the storage battery kept charged by the lighting dynamo, non-vibrator coils are usually wound to a higher resistance than the old vibrator coils, so as to produce a current of higher tension in the secondary. As this type of coil requires no adjustment, it is generally installed horizontally with its face flush

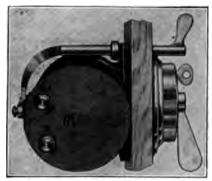


Fig. 48. Remy Single Non-Vibrator Coil Showing Method of Installation

with the dash, and on this face is mounted the switch giving three control points, i.e., neutral, battery (for starting), and magneto. The Remy dash coil, Fig. 48, is a typical example.

Distributor. This is simply a modification of the timer, designed to handle the high-tension current, or to distribute it to the different plugs. It takes the place of the multi-unit coil in which an

independent coil is employed for each cylinder. Owing to the high voltage of the secondary current, actual contact is not necessary in a distributor, a small gap or clearance presenting no obstruction to the passage of the high-tension current, so that wear at this point is avoided. In the earlier types, a brass arm passing close to contact points, or sectors embedded in hard rubber, was usual. Carbon brushes making contact against the disk by means of light springs, were subsequently adopted and are now commonly used. As the carbon is very hard and its contact surface becomes glazed by the friction, the wear is practically negligible. The complete wiring of a distributor system is shown in Fig. 46. H is the ground or commonreturn connection of the secondary circuit and K is the connection to the distributor I, from which the high-tension current is distributed by the arm J to the spark plug leads D, E, F, and G.

Condenser. The condenser is technically known as an electrical "capacity" in that it has the ability to absorb a quantity of electricity proportioned to the area of its conducting surfaces and to the nature of the dielectric employed. This property is utilized to absorb the excess current passing at the moment the primary circuit of the ignition system is opened by a vibrator, thus bringing about a quick cessation of the current flow and preventing the destructive arcing or burning that would otherwise occur at the contact points. The charge thus absorbed is immediately returned to the circuit in the form of a discharge, when the points come together again and a higher potential value is impressed upon the current. A condenser consists of conducting surfaces placed between insulating surfaces, known as the dielectric. For ignition work, the conducting surfaces

are sheets of thin tinfoil cut with conducting tabs which project beyond the ends of sheets of paraffined paper on which the tinfoil is placed. Between each two sheets of paraffined paper is placed a sheet of tinfoil, the latter being arranged so that the tabs project at alternate ends, Fig. 49. The paraffined paper


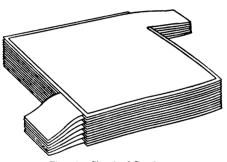


Fig. 49. Sketch of Condenser

overlaps the tinfoil all around to the extent of an inch or more to prevent a discharge over the edges of the sheets. The capacity of the condenser depends upon the number and the size of the sheets of tinfoil and the thinness and the character of the dielectric separating them; and, when a sufficient number have been assembled, the projecting tabs at each end are riveted or clamped together and a flexible wire lead connected to each. It is then connected in multiple with the vibrator, and, in the case of a coil is inserted in the containing case of the latter and further insulated as well as held in place by having molten paraffine poured around it so as to fill the space. A condenser practically eliminates sparking at the contact points and is also used with the contact breaker of a magneto.

Spark Plugs. No small part of the trouble experienced with early ignition systems was due to the defective design of the spark

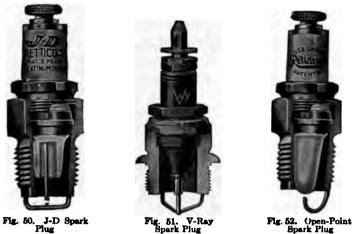plugs employed. Where an over-rich mixture is delivered by the carbureter, i.e., one containing too much gasoline in proportion to the air, a certain amount of the carbon is unburned and remains in the



cylinder in the form of soot. This is greatly increased by an excess of lubricating oil finding its way into the combustion chamber. The heavier carbons of this burn to the same consistency and are also



deposited on the piston head, cylinder walls, valves, and other exposed surfaces in the form of a flint-hard coating. The end of the spark plug receives its share and, as the carbon is an excellent conductor, the plug is accordingly short-circuited, so that the current, instead of jumping the gap between the points, takes a path of lower resistance across the carbon-coated insulating surfaces.

Fundamental Requisite. The spark plug is the "business end" of the ignition system and no matter how elaborate or efficient the essen-

tials of the latter may be, its successful operation is governed entirely by that of the plug. As originally designed, the insulating material filled the shell at the sparking end, affording a direct path for the current as soon as this small surface became covered with carbon. Failure was accordingly frequent, it being nothing unusual to have to clean such a plug in less than fifty miles of running. To overcome this, a recess was allowed between the insulation of the central electrode and the outer shell. This simple expedient constitutes a basic patent (Canfield) under which all spark plugs are manufactured. Porcelain, mica, or artificial stone is used as the insulating material, the first-named being most generally employed. This is made in various forms, as shown by the sections, Figs. 50 and 51, and it will be noted that the smaller diameter of the insulated



Fig. 55. Bosch High-Tension Spark Plug

electrode in the center greatly increases the area of the surface of both shell and porcelain that must be coated with carbon before a path is formed for the current.

Electrode Arrangement. Practice also varies considerably in the arrangement of the electrodes, taking the form of open points as in Fig. 52, a bridge as in Fig. 50, or a number of points as shown in Figs. 51 and 53. In some instances, the central electrode is enclosed in a chamber, the gas entering through a small hole in the shell, as shown in Fig. 54. Considerable advantage is claimed for the type of plug having a plurality of gaps, the number usually being three, as shown in Fig. 55, or four as in Fig. 53. It is more theoretical than actual, however, as the current always takes the shortest path and the

### ELECTRICAL EQUIPMEN'S

bridging of any one of the gaps by a particle of conducting material, such as carbon, short-circuits all of them.

Series Plugs. As shown in the various wiring diagrams, the



Fig. 56. Series-Type Spark Plug

shell of the plug is one of the electrodes and forms a part of the circuit by being screwed into the cylinder, the latter constituting part of the common ground return for both the primary and the secondary circuits of all ignition sys-Experiment has shown a slightly increased power resulting from the simultaneous occurrence of two sparks in different parts of the combustion chamber of the cylinder, especially with the T-head type of cylinder in which the two plugs can be located in the oppositely placed valve ports. This is termed doublespark ignition and the type of magneto designed for this purpose is described in the section on "Magnetos". To obtain the same result with the standard ignition circuit designed to produce but one spark in each cylinder, what

is known as a "series" type of plug has been developed. One of these is shown in Fig. 56. In this the spark occurs between two central



Fig. 57. Method of Converting Series Plug

electrodes, as shown, the shell not forming a connection with the cylinder. The lead from the distributor is attached to one of the binding posts of this plug and a second wire connected to the other binding post is led to a standard type of plug, thus completing the circuit and placing both plugs in series so that a spark occurs simultaneously in both. By means of an attachment as shown in Fig. 57, this type of plug can be used with a grounded return, the arm shown connecting the shell in the circuit. As the majority of motors now in use have L-head cylinders, and even at the best the advantage gained is very slight, the use of series plugs has not a great deal to recommend it.

Magnetic Plugs. With a view to overcoming the defects of the mechanically operated make-and-break plug as used on low-

tension ignition systems, an automatic plug was developed. As shown by the section, Fig. 58, this is simply a solenoid A and plunger C, the latter being held in contact at D by a spring B. The current passing through the winding A lifts the plunger and the spark occurs at D. The remainder of the system consists of a low-tension magneto or other source of current supply and a timer. Such plugs have been used to some extent on stationary engines, but have not proved practical on the automobile motor, as the high temperatures drew the temper of the plunger spring and often burned out the insulation of the winding.

Priming Plugs. For low-priced motors, such as the Ford, which have no pet cocks or compression-release cocks on the cylinders, a spark plug combined with a pet cock,

such as that shown in

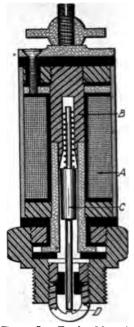


Fig. 58. Low-Tension Magnetic Spark Plug

Fig. 59, can be had. These are usually known as "priming" plugs in that they permit of priming the cylinder with gasoline to render starting easy in cold weather.

Waterproof Plugs. Ignition systems, or motor-boat engines in particular, are apt to suffer short-circuiting from spray or dampness, though this often happens on the automobile as well in heavy rainstorms. To guard against this a so-called waterproof type of plug is provided. The precaution usually takes the form of a hood of hard rubber or other insulating material placed over the connection, as shown in Fig. 60.

Plug Threads. European practice has standardized a straight-threaded plug, the thread itself usually being of fine pitch. A plug of this kind is screwed home on a gasket



Fig. 59. Priming Type Spark Plug

of copper and asbestos or of the latter material alone, which is relied upon to prevent leakage. Foreign types are usually referred to as "metric" plugs, as the thread dimensions are based on the metric standard. As developed at first in this country, all spark plugs were made with an "iron-pipe" thread. This has a taper of three-

fourths inch to the foot and the plug is screwed into the cylinder as far as the taper will permit, no other provision being made to hold the compression. As this is a crude expedient, adopted chiefly because of its cheapness, and the metric standard is not employed here, an S.A.E. standard plug has been developed along the same lines, both the plug diameter and the thread itself being made somewhat larger than those used abroad.

Hydraulic Analogy in an Ignition System. A comparison of the workings of an ignition system with the action of an hydraulic system having similarly related parts will serve to make clear the operation of the former. It



Fig. 60. Spark Plug, with Waterproof Connections

must first be borne in mind that a high-tension ignition system consists of a source of current; an interrupter, or method of automatically breaking the circuit of this current supply, timed with relation to the revolution of the engine crankshaft; a condenser to suppress the arc at the interrupter contacts; a transforming device, or induction coil, to transform a current of comparatively high amperage at a low potential to one of high voltage; a device for distributing this high-tension current to the spark plugs, also timed with relation to the crankshaft; and the spark plugs themselves.

Current. The electric current in the ignition system may be represented by water flowing in a pipe from a source of supply which puts it under pressure, corresponding to the storage battery. A certain amount of frictional resistance must be overcome by the water in flowing through the pipe and this is equivalent to the electrical resistance of the wiring in the ignition circuit. The rate of water flow in the pipe corresponds to the current in the coil, and the inertia of the water to the inductance of the primary winding of

the induction coil. Now, if the flow of water be suddenly stopped, there will be an enormous increase in the pressure, due to the inertia of the water. This effect, known as water hammer, is commonly noticed in the larger sizes of pipes carrying water under considerable pressure. It corresponds to the great increase in the pressure, or voltage, which takes place when the flow of current in the primary of the ignition circuit is opened suddenly by the interrupter. This is due to the inductance in the coil. A quick-closing valve in the water system would accordingly correspond to the timer contacts which interrupt the current in the primary of the induction coil.

Office of Condenser. There is one peculiar tendency of timer contacts which must be mentioned here to make the analogy more complete. Unless protected by a condenser, they are apt to burn away very rapidly, due to the arc produced by the current at the moment of separation. (This is also true of the contacts of the battery cut-out and of the regulator employed in connection with starting and lighting systems; the condenser does not eliminate this tendency to burn away but reduces it to a minimum.) This failing on the part of the timer contacts would correspond in the hydraulic system to a valve with a very thin edge which would be liable to bend under the sudden rise in pressure before it is fully closed. In the case of both systems, therefore, it is necessary to arrange for some protection, and a condenser is supplied for this purpose in the ignition system.

In the hydraulic system, it takes the form of a surge chamber, as shown in Fig. 61. This chamber has an elastic diaphragm centrally placed in it, and the chamber itself is shunted, or connected, around the valve in the same manner as the condenser is connected to the contact points. When the valve begins to close, this surge chamber relieves the pressure to some extent during the operation of closing the valve and so protects the thin edge of the valve from bending. After the valve is fully closed, there is, of course, no further danger of its being bent over. In the electrical system, the condenser supplies similar protection, reducing the voltage at the timer contacts at the moment of separation and keeping this voltage reduced until they are fully open, thus preventing the current from bridging the gap, or arcing. Once the contacts are fully separated, the low-tension current cannot jump the air gap, so that there is no further danger of their burning.

Transformer. In order to utilize the pressure produced by the sudden closing of the valve, it is necessary to provide some transforming device, such as a pressure chamber. This is illustrated in Fig. 61, and it will be noted that it is of a much larger diameter than the pipe. As the pressure in the chamber and the pressure in the pipe will both have some unit value (measured in pounds per square inch), the total pressure on the piston will be to the pressure in the pipe as the area of the piston is to the area of the pipe. By the use of a pressure chamber of large diameter, compared to that of the pipe, a very considerable force is applied to the piston, but the

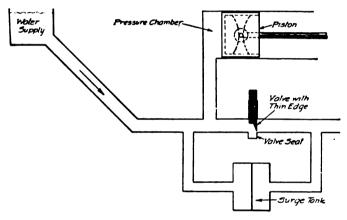


Fig. 61. Diagram Showing Hydraulic Analogy of Ignition System



This high voltage is accompanied by a very small amount of current, just as in the hydraulic system the greatly increased pressure on the piston produces but a very slight movement of the latter. This rise in the voltage and decrease in the current can be made clear by a brief explanation. By the principles of induction, a current flowing in the primary coil will induce a current in the secondary coil. The energy of these currents in watts is equal to the electromotive force in volts times the current in amperes. Now, as the transformer cannot create electrical energy, the energy of the transformed current must equal the energy of the current before it is transformed, barring a small loss within the transformer. This means that if the voltage of the current is raised from 6 volts, say, in the primary to 6000 volts in the secondary (that is, made one thousand times greater), the amperage of the primary current must be correspondingly reduced from 2 amperes, say, to .002. In other words, the product of the current and electromotive force must be always the same before and after transformation.

## INDUCTION SOURCES OF IGNITION CURRENT-MAGNETOS

Owing to the failure of either dry cells or storage batteries to supply sufficient current to operate the wasteful contact devices at first employed, mechanically driven current generators were adopted. American practice at first favored the small, high-speed direct-current dynamo, but as proper regulating devices had not then been developed, it was not successful, chiefly because its speed range was so limited. Few of these little dynamos generated sufficient current at less than 1200 r.p.m. to ignite the charge in the cylinder, so that at slow speeds they would not run the motor. If run much faster, they burned out and were accordingly abandoned.

Working Principle. The magneto is simply a small dynamo in which the fields consist of permanent magnets, instead of electromagnets, the cores of which only become magnetic when a current is passed through their windings. Hard steel, particularly when alloyed with tungsten, retains a very substantial percentage of its magnetism, after having been once magnetized by contact with a powerful electromagnet. Its retaining power is further increased by placing a "keeper", or armature, across the poles, or ends. The advantage of a permanent field for magneto use is that it is at its

maximum intensity regardless of how slowly the armature is revolving so that a good spark is produced at very low speeds; while its initial value cannot be exceeded no matter how fast the machine is run, so that the armature winding cannot be burned out. All

magnetos generate an alternating current so that when used with a coil there is no necessity of frequently making and breaking the circuit, as is done by the vibrator of a coil handling direct current, the alternate surges of current from zero to maximum of opposite polarity producing the same effect more efficiently.



Fig. 62. Remy Magneto Contact Breaker

Low-Tension Magneto. A low-tension magneto is nothing more or less than the simple instrument which formed part of the thousands of telephones

of the hand-ringing type still to be found in rural districts. Built with more powerful magnets and wound to give a greater current output at a lower voltage, it was employed in connection with low-tension ignition systems.



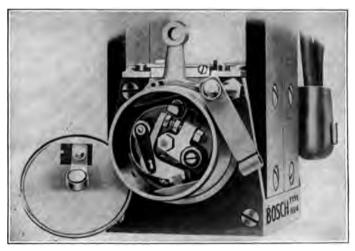


Fig. 63. Contact Breaker of High-Tension Magneto (Bosch)

As the mechanically operated make-and-break plug circuits are timed, the magneto is simply revolved continuously without reference to the motor timing, the current being constantly delivered to the circuit through the usual collector ring and brushes. Magnetos

# ELECTRICAL EQUIPMENT

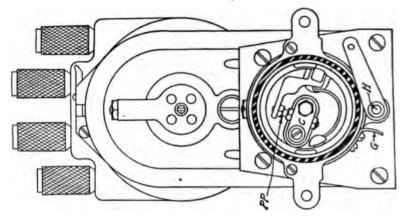

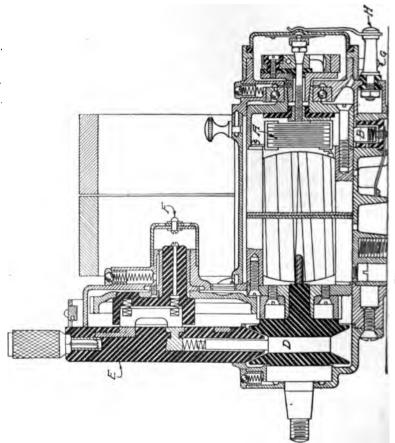

101

of this type are still used to a greater or less extent on large, slowspeed stationary engines.

High-Tension Magneto. Essentially all magnetos are the same: that is, they have a permanent magnet field and a two-pole armature. In what may be best identified by terming it the true high-tension type, there are two windings on this armature, a primary winding of comparatively coarse wire in which the current is generated, and a secondary winding of fine wire, the same as an induction coil. A magneto of this type is timed with the motor according to the number of cylinders, being driven at crankshaft speed in the case of a four-cylinder motor and at one and a half times crankshaft speed in the case of a six. In addition to the usual current-collecting device, it is equipped with a contact breaker or interrupter, such as that shown in Fig. 62, which is part of a Remy magneto. Fig. 63 shows the same essential of a Bosch light-car type magneto. Except at the point in the revolution at which the spark is to occur in the cylinder, the armature circuit is normally short-circuited upon itself. This permits it to "build up", so to speak; that is, as the armature poles come within the most intense part of the field, the current in the armature winding reaches its maximum value and. at this moment, the contact points of the breaker are opened and a strong current is induced in the secondary winding. As the distributor runs synchronously with the contact breaker, the circuit to one of the plugs is closed at the same time the spark occurs at it.

Description of True High-Tension Type. A sectional view of a true high-tension magneto is shown in Fig. 64. In this the primary and the secondary windings on the shuttle armature are entirely separate to insure better insulation. These windings are not shown in section in the illustration, the usual insulating tape winding being indicated on the armature. Twice during every revolution of the armature, the primary circuit is opened at the platinum points PP of the circuit breaker, the interruption occurring substantially at the moment when the primary current is at its maximum. From the primary winding, the current is conducted to the stationary member of the contact breaker C through the terminal B. A is the condenser. One terminal of the secondary winding is connected to the end of the primary winding, as in a coil, and the other connects with the high-tension collector ring D, from which it is conducted through a carbon

brush to the brush of the distributor above it for distribution to the four brass segments in the distributor plate E. These segments are connected to the four terminals shown extending above the magneto in the end view at the right and from them the usual high-tension cables are led to the plugs. The distributor is driven from the armature shaft of the magneto through 2 to 1 gearing so that it only makes one revolution for two turns of the crankshaft in the case of four-cylinder four-cycle motor, as in the latter but two explosions occur per revolution. To vary the time of occurrence of the spark in



Fig. 65. Eisemann Magneto Generator for Four-Cylinder Cars

the cylinders, the contact breaker may be turned through part of a revolution by means of a rod and linkage fastened to one of the extensions of the contact breaker box, as shown in the end view. This connects with the spark timing lever on the steering wheel and, to stop the action of the magneto, it is only necessary to move this lever to the extreme retard position, which brings the spring G in contact with the bolt H and short-circuits the primary winding.

This instrument, Fig. 65, differs from Fig. 63, as it is a magneto and a generator combined. Ignition and battery charging are accomplished by this unit.

Typical High-Tension Magneto Circuit. Fig. 66 is the wiring diagram for a high-tension system, using a true high-tension type magneto. B is a wire of the primary circuit. A primary generating coil is in this circuit, being wound on the shuttle type armature; there is also a contact breaker, E, which is carried on the same revolving spindle that bears the armature. C is a high tension coil wound on the armature, being located in the circuit. The dotted lines indicate the return ground.

High-Tension Type with Coil. This is not actually a high-tension magneto, properly so-called, as it only generates a low-tension current, which is subsequently stepped up through a transformer or non-vibrator coil, but it is commonly so termed as it is always used in connection with a high-tension ignition system. In this case there is only a single winding on the armature and the current is led from the latter through the usual contact breaker and then to an independent coil, generally located on the dash. The condenser is combined with the coil, and from the latter the high-tension current is led back to the magneto to be distributed. Owing to its lower cost, this type of

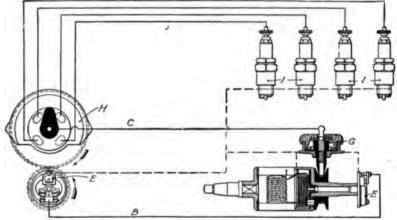


Fig. 66. Wiring Diagram of High-Tension Magneto System

magneto is probably more generally employed, especially on mediumpriced American cars, than any other.

Safety Gap. If the current induced in the secondary winding of an induction coil meet with a resistance in the outer circuit in which the coil is connected, greater than the resistance presented by the insulation of its own windings, it will puncture this insulation and the expensive coil will be ruined. The placing of such a resistance in the high-tension circuit occurs when the connection of a spark plug is removed from the plug terminal and is allowed to dangle in the air beside the motor and, unless this were guarded against, it would result in the breakdown of the ignition system. The precaution takes the form of a safety gap. This is an opening inserted in the circuit, and its length is based on the safe maximum distance that the coil


can bridge in normally dry air. A safety gap of this kind is shown at F in Fig. 64. In the type of magneto just described above it is embodied in the coil. When an opening at any point in the high-tension circuit exceeds the length of this gap, the current takes the path thus provided, thus preventing the imposition of an excessive strain upon the insulation of the secondary windings.

Wiring Connections. For the actual operation of an induction coil, there is no necessity for any electrical connection between the primary and the secondary windings, the electrical energy being transferred from one to the other entirely by induction, i.e., through the intermediary of the magnetic lines of force which interlink both. However, for the sake of simplicity of external connections, the beginning of the secondary winding is usually connected to the end of the primary. Both the primary and the secondary circuits have a "ground return", which necessitates that one end of both the primary and the secondary winding of the coil be placed in positive metallic connection with the engine or car frame. By connecting the twe windings, as mentioned, a single wire serves to ground both. The average coil, therefore, has only three terminals, i.e., one primary, one secondary, and one common ground connection.

On cars that are provided with magneto ignition alone, as is the case with French taxicabs and many other French light cars, there would be only two connections between the magneto and the coil. one primary and one secondary; one connection from the coil to a ground, as the motor or frame; and four connections direct from the magneto distributor to the spark plugs. This represents an ignition system reduced to its lowest terms of simplicity. As a matter of f. ct. it is even more simple in reality, as most French cars use the true high-tension type of magneto so that the four leads from the magnete to the plugs are the only external wires in evidence. Unless a magneto is in excellent condition, however—and the magnets lose their strength more or less rapidly under the influence of the heat and vibration—too much effort is required to start the motor. American manufacturers accordingly supply a battery for starting purposes. and on some of the high-priced cars this takes the form of an entirely independent battery ignition system, i.e., having a battery, coil timer, distributor, and a separate set of spark plugs. It also constitutes an emergency system that may be resorted to in case of

breakdown of the magneto, but the latter is so rare and the cost and complication of the extra system are such that the latter is not generally used. Instead, the magneto coil, contact breaker, and distributor are utilized with the battery as the source of current

Inductor-Type Magneto. Mention has been made in the introductory of the fact that if a coil of wire be moved so as to cut the lines of force of a magnetic field, an e.m.f. will be induced in the wire. If, instead of moving the wire, a magnetic flux be made to pass through it first in one direction and then in the other, the same result will be obtained, i.e., an alternating e.m.f. will be produced,

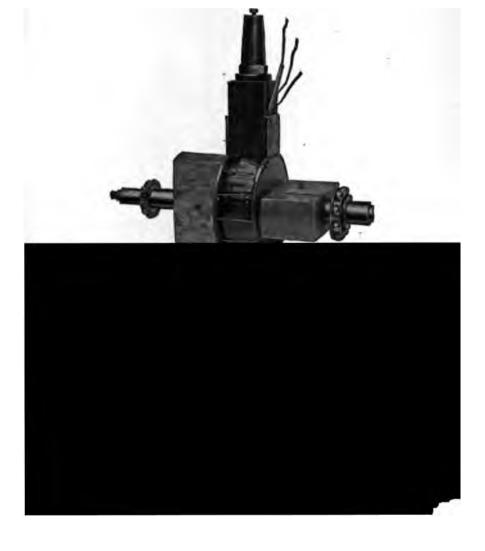

winding in the center is mounted on the shaft of the rotor and consists of a primary and secondary coil.

There is no mechanical or electrical connection between the windings and the rotor shaft, nor between the laminated blocks of the rotor and the windings. As shown in the illustration these are placed at right angles to one another and are riveted to the shaft. It will be evident that in the position shown in the illustration the right-hand member of the rotor will be bridging the pole pieces of

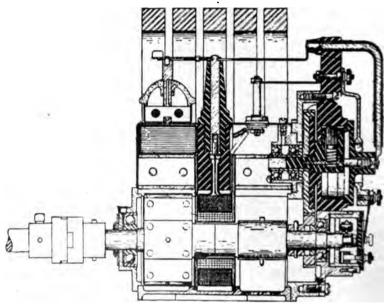


Fig. 68. Section through K-W Inductor Magneto Courtesy of K. W. Ignition Company, Clereland, Ohio

the magnetic field; by giving the shaft a quarter turn the two rotor members will have their ends facing opposite poles of the magnetic field, thus completing the magnetic circuit through the center of the windings. Consequently, a current wave will be produced each time the rotor revolves through a quarter-turn, or 90 degrees, so that this inductor magneto produces four impulses per revolution instead of two as in the ordinary type having a wound bipolar armature of H form. Apart from the method of producing the current, the remaining essentials of the magneto are the same.

except that no collector brush is necessary as is the case where the current is generated in a revolving winding on an armature.

The details of construction of the K-W high-tension magneto are shown in Fig. 68. While, from an external view of the rotor, it apparently consists of two independent parts, it will be seen in the section that it is practically one piece, the connecting part passing through the center of the winding so that the magnetic circuit is completed through the latter. The primary winding, consisting of four layers of comparatively coarse wire, will be noted close to the rotor; just outside of this is the secondary winding of many layers of fine wire and from the latter the connection is carried upward to a horizontal strip of copper termed a bus bar. At the right, this bar connects with the distributor for the high-tension

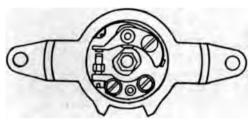


Fig. 69. K-W Interrupter

current; at the left it connects with the safety gap, directly beneath which is the condenser.

Timing. The magneto is timed by an interrupter operated by a cam on the rotor shaft in the usual manner; the

details of this interrupter are shown in Fig. 69. As is the case with all ignition magnetos, these points remain closed, thus short-circuiting the primary winding, until the current reaches its maximum, and then are opened suddenly, thereby inducing a current in the secondary winding. The firing point of the magneto is just as the contact points begin to separate, as shown in Fig. 69, which is exaggerated to make this clear. At the same moment, the distributor arm is passing one of the segments connected to a spark plug, as shown in Fig. 70, the firing order of the motor in this case being 1, 2, 4, 3. While the magneto produces four waves per revolution, these are not necessarily all utilized; the cam (c in Fig. 70) opens the interrupter twice per revolution, giving two sparks for each turn of the crankshaft, as required by a four-cylinder four-cycle motor. In a four-cylinder two-cycle motor, a four-sided cam would be employed thus producing four sparks per revolution.

The letters on the Mastration are: A contact breaker box; c cam;

P contact points of interrupter; R cam roller to lessen friction at that point; B distributor arm; S distributor segments; R H and L H referring to the direction of rotation, as either right hand—also termed "clockwise" or from left to right—and left hand, anti-clockwise.

Dixie Magneto. Essential Elements; Circuits. While based on the inductor principle, this differs from an inductor type of magneto in that the pole pieces themselves are revolved and they do not reverse their polarity as in the case of an inductor or an armature.

The rotating element of the Dixie is shown in Fig. 71; B is a brass block which prevents any magnetic flux flowing directly from

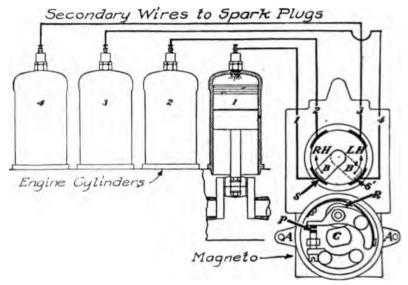


Fig. 70. Wiring Diagram for K-W Magneto Circuits

N to S, which are the rotating pole pieces. The coil with its primary and secondary windings is placed directly above this rotating element, in the hollow of the magnets, as shown in Fig. 72. At the right in the same figure is shown the relation between the rotor, the magnets, and the coil. It will be noted that the core of the coil C bridges the stationary pole pieces F and G and that the shaft of the rotor passes through the magnets in a plane at right angles to that of the usual magneto. The reversal of the magnetic flux, with varying positions of the rotor, is shown in the right-hand sketch of Fig. 72, and in Fig. 73.

The primary circuit of the Dixie is shown in Fig. 74; A being the core of the coil, P the primary winding, R the condenser, X and


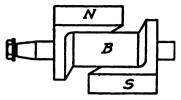


Fig. 71. Rotating Element of Dixie Magneto

Y the points of the interrupter or contact breaker. The terminal D is a screw on the head of the coil, and the wire Z connects directly with the contact Y of the interrupter. Fig. 75 shows the details of this interrupter, the housing of which is attached to the mounting of the wind-

ings, while the details of the secondary circuit are shown in Fig. 76. C is the end of the high-tension, or secondary winding of

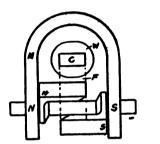


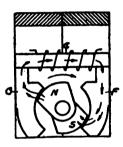


Fig. 72. Details of Dixie Magneto Courtesy of Splitdorf Electrical Company, Newart, N. J.

the coil, which is connected to a metal plate D embedded in the hard-rubber end piece of the coil A. A small coil spring holds the

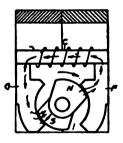

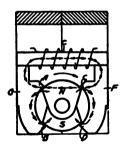


Fig. 73. Diagram Showing Reversal of Magnetic Flux in Dixie Magneto

connection F in contact with D and at its outer end F connects with J which is the distributor brush. The latter revolves, successively passing over the segments leading to the corresponding spark plugs.

But one of these segments is indicated by L, the dotted lines indicating the completion of the circuit through the ground connections.

Timing. As the contact-breaker box is attached to the mounting of the coil, the latter moves with it when the former is partly

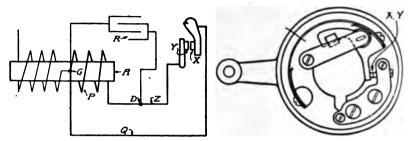


Fig. 74. Primary Circuit of Dixie Magneto

Fig. 75. Dixie Interrupter

rotated to advance or retard the occurrence of the spark in the cylinders, so that the opening of the contact points always takes place at the point of maximum current. This is shown diagram-

matically in Fig. 77. As the contact points are opened by the revolution of the cam, it will be apparent that a movement of the mounting of these points with relation to the cam will alter the time at which they will operate. For example, assuming that the

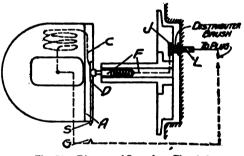


Fig. 76. Diagram of Secondary Circuit in Dixie Magneto

magneto is designed to run clockwise, moving the interrupter in the same direction as the rotation will cause the spark to occur later, as shown by the retarded position in the sketch. Moving the interrupter against the direction of rotation of the cam accordingly would cause the spark to occur earlier. The range of movement is approximately 15 degrees each side of the neutral point indicated by the horizontal position of the lever on the breaker box; the dotted lines show how the firing point may be advanced 15 degrees or retarded an equal amount. The lever in question is connected by means of linked rods to the spark lever on the steering wheel.

Magnetos for Eight-Cylinder and Twelve-Cylinder Motors. It will be evident that, regardless of the number of cylinders to be fired, the principles of current generation, transformation (to high tension), and distribution remain the same, so that a reference to

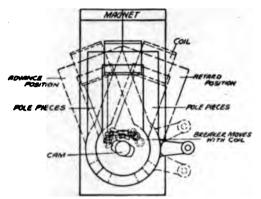


Fig. 77. Diagram Showing Method of Timing Dixic Magneto Courtesy of Splitdorf Electrical Company, Newark, N. J.


the models of the Dixie for eight-cylinder and twelve-cylinder motors will suffice to cover the modifications required by the increased number of cylinders. To keep the speed of the magneto down, the rotor is provided with four poles instead of two, so that four impulses are generated in the windings per revolution. This permits of



lifting faces being provided for this purpose—and the distributor is provided with twice as many segments and spark-plug leads as a magneto designed for four-cylinder or six-cylinder motors. But as the contact segments of the distributor must be sufficiently long to permit of the distributor brush being in contact with them, regardless of the point to which the ignition timing is advanced or retarded. it is impossible to place more than six contact segments in a circle without reducing the insulation between them to a point where there would be danger of the high-tension current jumping the gap and thus deranging the ignition. To avoid this a compound distributor is employed, i.e., two distributors are combined, but instead of being placed on a flat surface as in the magnetos for a smaller number of cylinders, the segments are spaced around the inner periphery of a hollow cylinder. Two radial contact brushes are carried by the revolving member of the distributor, each of which makes contact with one of the sets of segments. Fig. 78 illustrates the distributor itself, while Fig. 79 is the revolving member. radial brushes A2 and B2 of Fig. 79 are electrically connected to contact brushes extending laterally (A1 and B1) from the revolving member. These brushes make contact alternately with the arms of a metal spider sunk flush in the end wall of the distributor. S in Fig. 78, with which the central pin of the distributor rotor D, Fig. 79, also connects. The high-tension current from the windings is fed to this distributor rotor through the spring brush contact C.

Path of Current. The path followed by the current is accordingly as follows: from the high-tension winding of the coil (not shown here) to the distributor rotor through the brush C; from brush D to the spider S; from S alternately through brushes A1 and B1 to the distributor segments representing the inner and outer row of spark-plug leads, through the brushes A2 and B2. Brushes A1 and B1 are so spaced that, when one is centrally in contact with an arm of the spider S, the other is midway between the second and third arms from the one with which contact is being made.

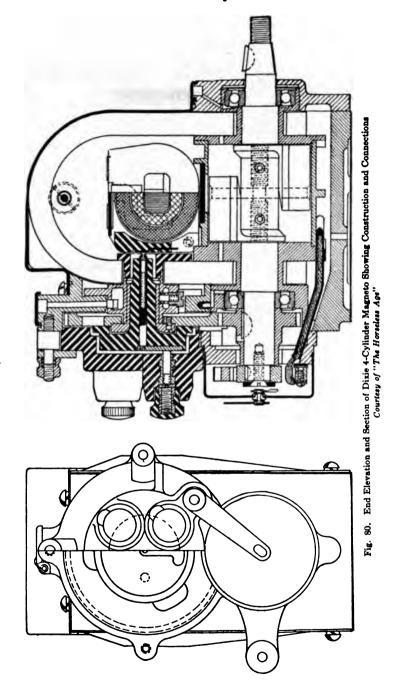The relation of the various members of the Dixie magneto will be clear upon reference to the sectional view, Fig. 80, showing one of the four-cylinder models. The contact breaker or interrupter is at the left-hand end of the rotor shaft; just above the rotor itself is the coil, while to the left of this is the distributor.



## ELECTRICAL EQUIPMENT

## **IGNITION SYSTEMS**

### STANDARD TYPES

Dual Ignition System. Bosch Type. The dual type of ignition system uses one coil and one set of plugs with either the battery or the magneto as the source of current supply, the magneto contact breaker and distributor being common to both. Fig. 81 illustrates the connections of a dual system. Wire Number 1 is in the low-tension circuit and conducts the battery current from the primary winding of the coil to the contact breaker of the magneto. Low-tension wire Number 2 is the grounding wire by which the primary


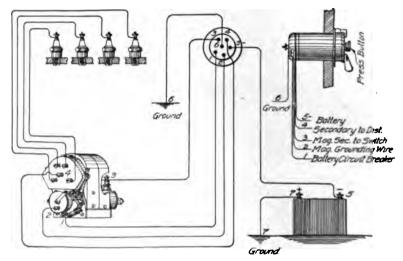


Fig. 81. Wiring Diagram Dual Ignition System

circuit of the magneto is grounded when the switch is thrown to the "off" or "battery" position. Wire Number 3 leads the high-tension current from the magneto to the switch contact, and wire Number 4 is the wire that carries the high-tension current from the coil to the distributor. Number 5 leads from the negative terminal of the battery to the coil, and the positive terminal of the battery is grounded by Number 7; a second ground wire, Number 6, is connected to the coil terminal. The press button on the switch cuts in the battery circuit which includes a special vibrator on the coil which is employed simply for "starting on the spark"; i.e., when a charge of gas is left in the cylinders and the crankshaft has stopped with

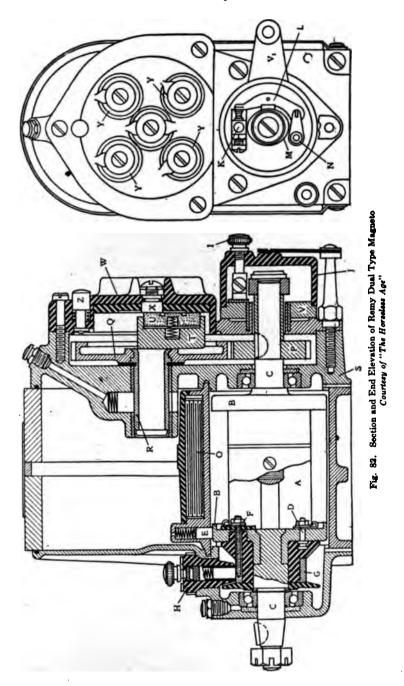

·119

the pistons in the proper position for firing the next one in order, a spark in that cylinder will frequently start the motor.

Remy Type. Prior to the general adoption of electric lighting and starting systems, the dual type of ignition system was almost universally employed on the lower and medium priced cars, a number of which are still in service. The Remy magneto, a section and end elevation of which are shown in Fig. 82, is typical of the class used for this service. The armature A is of the H or shuttle type, of laminated construction fitted with cast bronze heads B. It carries a single winding, one end of which is grounded by connecting it to the rear bronze head at D, the ground connection being further insured by the carbon brush E, pressed against the head by a spring. The other end of the armature winding is connected through an insulated stud F to the collector ring G from which the current is taken by a carbon brush in the holder H. From this brush a low-tension cable runs to the induction coil mounted on the dash.

The other primary terminal of the coil is connected to the terminal I on the breaker box at the right-hand end of the magneto. This terminal, which extends through the breaker-box cover J of insulating material, forms an integral part of the contact screw K which carries one of the contact points of the interrupter. The other contact point is mounted on the free end of the lever L, pivoted at its lower end and provided with a fiber contact block bearing against the cam M carried on the armature shaft. The contact screw K, interrupter lever L, and its stud N are all supported on the metal plate V forming the interrupter base. This plate is supported on a lateral projection from a disc secured to the forward end plate S of the magneto and is provided with the radial arm V. which is connected by jointed rods to the spark timing lever on the steering wheel. This permits of moving the breaker box through part of a revolution with relation to the cam on the armature shaft to advance or retard the time of ignition, as explained later under Spark Timing. The interrupter lever L is grounded to the frame of the magneto through the stud N. The condenser O is placed in the armature cover plate and has one terminal connected to the stationary contact screw K and the other terminal grounded, so that it is shunted or "bridged" directly across the interrupter and

serves to minimize the spark or arc caused by the opening of the contacts. The condenser is sometimes combined with the coil.

Details of Typical Distributor. Apart from slight variations in detail, the following description of the distributor is typical of all magneto distributors. At its right-hand end, the armature shaft, Fig. 81, carries the steel pinion P, which meshes with the bronze gear Q having twice the number of teeth. Rigidly mounted in the bronze distributor gear Q is a carbon brush U carried in the holder T. This brush is pressed by its spring against the inner surface of the insulating cover of the distributor W, in which are embedded a central contact block X and four or six (according to the number of cylinders) contact blocks YY, equally spaced about a circle. At their outer ends these contact blocks carry terminals for the attachment of the high-tension cables. As the distributor revolves it makes contact with the central block X and all of the blocks YY in succession.

Since the distributor gear Q has twice as many teeth as the armature pinion, it makes but one revolution for every two turns of the crankshaft (four-cylinder motor) and of the armature, the latter being driven at crankshaft speed. As the four-cylinder motor fires only twice per revolution, it is only necessary for the distributor to make one complete turn for every two revolutions of the crankshaft. The distributor is so geared to the armature shaft that it operates synchronously with the interrupter, i.e., whenever the contacts of the latter separate to open the magneto armature circuit and permit the current to flow through the primary of the coil, the brush U is on one of the contact blocks Y. The exact moment of opening is governed by the setting of the timing lever, but the distributor brush U is made of sufficient width to cover the contact block throughout the whole timing range. A feature of this model of the Remy magneto is the timing button Z fitted into the distributor cover, to facilitate the adjustment of the timing of the magneto to the motor. Most magnetos have to be disconnected from the driving shaft to accomplish this. This button is normally held out by its coil spring. If the button is pressed in and the armature shaft is then turned, the plunger of the button will drop into a recess in the distributor gear. Then the engine must be turned over by hand until the piston of cylinder No. 1 is exactly

at the upper dead-center position at the beginning of the powe stroke, and while the crankshaft of the engine and the armatur shaft of the magneto are in these relative positions, the magnet driving gears must be meshed and the magneto gear secured on th tapered end of the armature shaft by means of a Woodruff ke which is held in place by a bushing and nut, as shown in the setional view, Fig. 82.

Typical Wiring Diagram. Fig. 83 is a wiring diagram of typical dual-ignition system that illustrates the connections i greater detail than in the case of the Bosch system. The switch

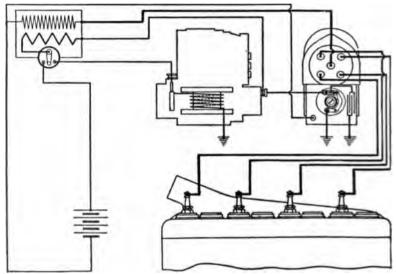


Fig. 83. Wiring Diagram of Magneto and Coil in the Remy Dual System

Courtesy of "The Horseless Age"

shown just below the induction coil has three positions: "OFF (central); "BATTERY" (left); and "MAGNETO" (right). Whe the switch is on the BATTERY contact, the current flows from the battery through the switch and the primary winding of the coil the interrupter, and completes the circuit by means of the groun connection of the latter and the coil. The secondary current i distributed in exactly the same manner as when the armature of the magneto is supplying the low-tension current. As the interrupter has its contacts closed, except for the momentary break when the spark occurs, its demand upon the battery is large, so that the

switch should immediately be shifted to MAGNETO as soon as the engine starts. Otherwise a dry-cell battery will be exhausted in a comparatively short time, or an unnecessary drain will be made from the storage battery where the latter is employed for starting.

Duplex Ignition System. This is designed to facilitate the starting of the motor by utilizing the current from a battery as well as that from the magneto when cranking to start. To throw the battery current in phase with that of the magneto, it having previously been stepped up to high tension through a coil on the dash, a commutator is fitted to the magneto shaft. The magneto is of the

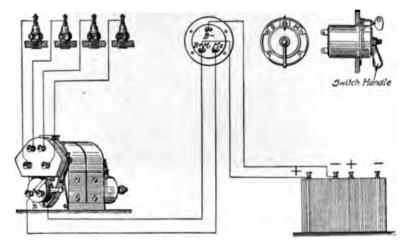


Fig. 84. Wiring Diagram of Bosch Duplex Ignition System

true high-tension or independent type, and by means of this commutator the flow of battery current is in the same direction as the flow of magneto current, a change in the direction of one (alternating current as generated by the magneto) is accompanied by a change in the direction of the other, and they are said to be "in phase," i.e., the cycles of alternation correspond in both. To accomplish this the battery current's polarity must be the same as that of the magneto and the battery must not be grounded, as shown by the wiring diagram, Fig. 84. The necessity for using the battery current to supplement that of the magneto exists only at very low cranking speeds, and the assistance of the battery is no longer needed once the engine starts. This type is not in general use.

Double-Spark Ignition. Mention has already been made the employment of two sparks occurring simultaneously the cylinders under the head of "Series Plugs". It will

evident that simply by adding another distributor to a magneto and taking leads from it to a second set of plugs placed at another point in the cylinders, preferably as far away from the first as possible, the same result is accomplished. Fig. 85 shows a Remy two-spark magneto, the distributors being mounted at opposite ends of the field.



Fig. 85. Remy Two-Spark Magneto

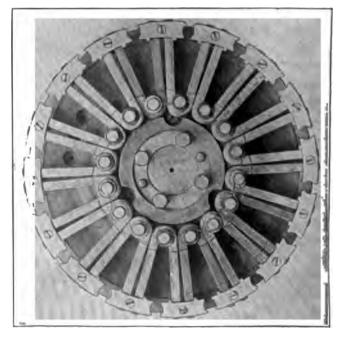


Fig. 86. Magnets of Ford Magneto

Ford Magneto. The Ford magneto is sui generis. What t patent lawyers term the "prior art" shows nothing even vague resembling it and no ignition current generator used on eith

American or foreign cars, past or present, can lay claim to any family ties. Not that its principles differ in any way, but their application is very unusual, and as this magneto is now employed on more

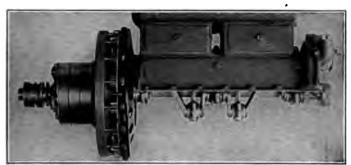


Fig. 87. Ford Magneto as Installed

than a million cars, it is of particular interest. Instead of the two or three horseshoe permanent magnets employed on the ordinary magneto, the Ford has sixteen magnets arranged radially with their poles outward, and all are bolted directly to the flywheel, as shown in Fig. 86. Directly in front of them and separated by a very small

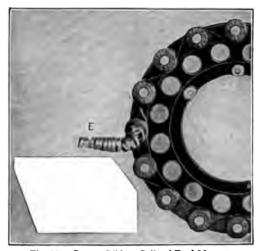


Fig. 88. Copper Ribbon Coils of Ford Magneto

clearance are sixteen coils, wound of copper strip or ribbon and attached to a spider which is bolted to the crankcase of the motor just forward of the flywheel, as shown by Fig. 87. The spider itself

and the coils are illustrated by Fig. 88, which shows one of the coils partly unwound at E. The spider and its coils remain stationary while the magnets are rotated in close proximity to them at high speed by the flywheel, thus inducing a current in the coil windings. The current is taken from the collector ring B, through the single brush C, the other side of the magneto circuit being grounded. Fig. 89 shows the complete ignition system as installed on the motor. The magneto coils are shown marked "generator"; at its upper center is the collecting brush mentioned, connected to the four-unit coil, which in practice is mounted on the dash. From the coil, four

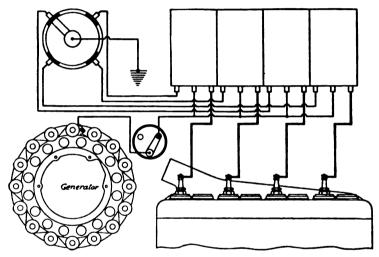


Fig. 89. Wiring Diagram for Ford Ignition System
Courtesy of "The Horseless Age"

primary connections are made to the low-tension timer mounted at the forward end of the motor and driven from the camshaft, and the four high-tension cables for the spark plugs will be noted just below the primary connections. The other two binding posts on the back of the coil are for the current from the magneto and the ground connection. While a battery is ordinarily fitted in addition to facilitate starting, this can be accomplished on the magneto alone, as the latter is very powerful. Complete details of this system are taken up in the article on Ford Cars, Part II.

Testing Spark by Means of Neon Gas. The spark "C" tester consists of a hard rubber case about 7 inches long and  $\frac{3}{4}$  inch in

diameter, pointed at one end like a pencil. In the side of the case is a small slot or window through which can be seen the small glass indicator tube, which contains neon gas. A wire is sealed in one end of this tube and is soldered to the brass nose-piece at the pointed end of the case. A second wire, sealed in the other end of the tube, is connected to a piece of copper foil, rolled up and placed in the other end of the case. Ordinary air is composed of approximately 79 per cent nitrogen, 20 per cent oxygen, and 1 per cent of rare gases such as argon, xenon, krypton, helium, and neon gas. Neon gas is one of the rare gases of the air which offers little resistance to the passage of an electric current, provided it is pure.

This gas has a peculiar property of glowing bright orange red when a very small amount of electricity passes through it. There is 1 cubic foot of neon gas in about 80,000 cubic feet of air. This rare gas is extracted from the air during the process of making liquid air. As neon and helium do not readily liquefy they are left in the gaseous state after which they are separated. The neon gas is then purified to be used in the spark testers.

The neon tube is especially useful in testing high tension circuits of the automobile. If the point of the instrument is placed on the terminal of the spark plug and no light appears in the window, it indicates that the line is open or the plug is shorted. This means that there is no voltage available to force the current through the neon gas into the condenser in the tube. This may be due either to a broken wire or connection somewhere or to a short circuit in the plug, the latter allowing the current to pass so readily that it has no tendency to take the more difficult course through the neon gas.

If there is a dim light in the window it indicates a faulty plug or wiring, meaning that the current is finding too easy a path to the ground and is not giving a hot spark in the cylinder. It may be due to the points of the spark plug being too close together, to poor compression, or to poor insulation on the cables.

When a medium light shows in the window it indicates that the spark plug is working properly. If the light is very bright, it indicates that the spark-plug gap is too wide, causing greater resistance in the secondary circuit than is necessary.

The Westinghouse uses the above construction in their spark

and the coils are illustrated by Fig. 88, which shows one of the coipartly unwound at E. The spider and its coils remain stational while the magnets are rotated in close proximity to them at his speed by the flywheel, thus inducing a current in the coil winding The current is taken from the collector ring B, through the sing brush C, the other side of the magneto circuit being grounde Fig. 89 shows the complete ignition system as installed on the moto The magneto coils are shown marked "generator"; at its upp center is the collecting brush mentioned, connected to the four-un coil, which in practice is mounted on the dash. From the coil, for

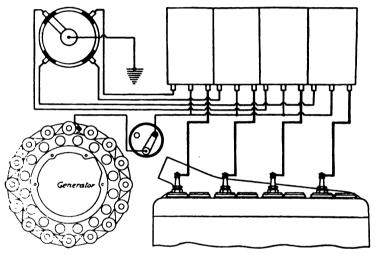


Fig. 89. Wiring Diagram for Ford Ignition System

Courtesy of "The Horseless Age"

primary connections are made to the low-tension timer mounted at the forward end of the motor and driven from the camshaft, and the four high-tension cables for the spark plugs will be noted just below the primary connections. The other two binding posts on the bacoff the coil are for the current from the magneto and the ground connection. While a battery is ordinarily fitted in addition to facilital starting, this can be accomplished on the magneto alone, as the latt is very powerful. Complete details of this system are taken up the article on Ford Cars, Part II.

Testing Spark by Means of Neon Gas. The spark "C" test consists of a hard rubber case about 7 inches long and 3 inch i

diameter, pointed at one end like a pencil. In the side of the case is a small slot or window through which can be seen the small glass indicator tube, which contains neon gas. A wire is sealed in one end of this tube and is soldered to the brass nose-piece at the pointed end of the case. A second wire, sealed in the other end of the tube, is connected to a piece of copper foil, rolled up and placed in the other end of the case. Ordinary air is composed of approximately 79 per cent nitrogen, 20 per cent oxygen, and 1 per cent of rare gases such as argon, xenon, krypton, helium, and neon gas. Neon gas is one of the rare gases of the air which offers little resistance to the passage of an electric current, provided it is pure.

This gas has a peculiar property of glowing bright orange red when a very small amount of electricity passes through it. There is 1 cubic foot of neon gas in about 80,000 cubic feet of air. This rare gas is extracted from the air during the process of making liquid air. As neon and helium do not readily liquefy they are left in the gaseous state after which they are separated. The neon gas is then purified to be used in the spark testers.

The neon tube is especially useful in testing high tension circuits of the automobile. If the point of the instrument is placed on the terminal of the spark plug and no light appears in the window, it indicates that the line is open or the plug is shorted. This means that there is no voltage available to force the current through the neon gas into the condenser in the tube. This may be due either

"C" tester, Fig. 90, and it is fast becoming a modern way of testing ignition systems quickly.

The spark "C" tester cannot be used for tracing out or testing ordinary lighting circuits because the voltages are not high enough to cause the tube to glow. In its present form it should never be used for testing high voltage power circuits.

Misfiring. Irregular firing can be traced most frequently to the timer and will be caused either by a lack of oil or an accumulation of dirt; with the timer in good condition, misfiring will most after be due to a lack of uniformity in the adjustment of the vibrates or to worn and pitted vibrator contacts. With the motor running the vibrator adjustment screws should be turned up or down very



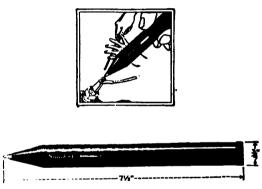


Fig. 90. This shows Spark "C" in Use, also Size of the Tester

slowly until all four cylinders fire uniformly. Instructions taking care of the vibrator points are given in detail in connection with the description of battery cut-outs and circuit breaks. Part III, Starting and Lighting Systems. Failure to fire is undue to lack of contact at the collector brush on the magneto, timer is so located that the primary cables get the full benefit oil and dirt, while its movement to advance or retard the ignitialso apt to abrade the insulation from these wires close to the take so that irregular firing may also be due to this cause. Committing replacements may be had at such low cost that when cables become oil soaked and their insulation worn, the easiest way correct troubles from this source is to install a new set of connections

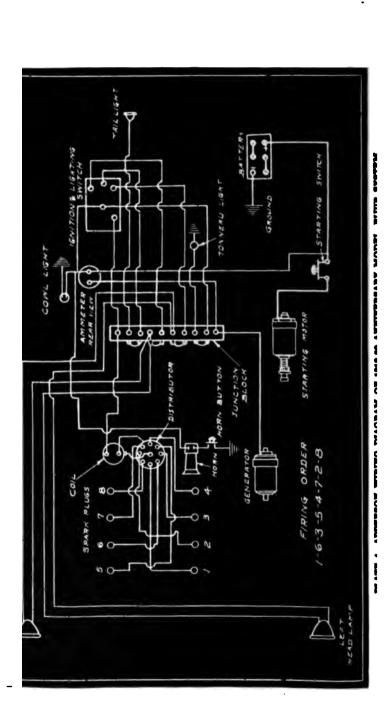


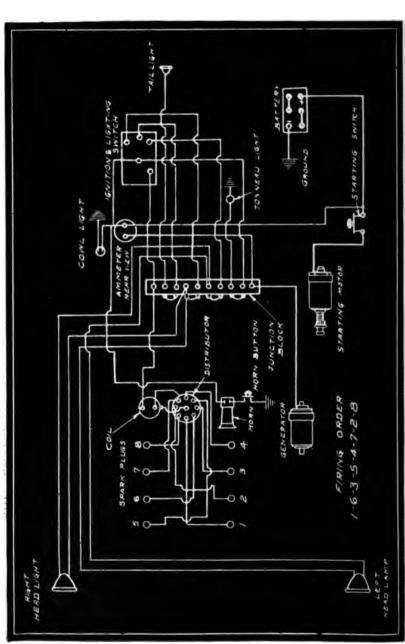


1


PLATE 4-APPERSON WIRING DIAGRAM OF 1919-20 ANNIVERSARY MODEL, BIJUR STSTEM


PLATE & APPERSON WIRING DIAGRAM OF SALL

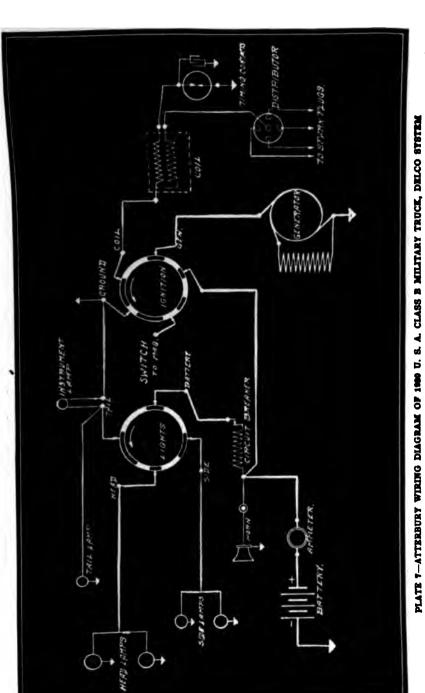



STRRTING & LIGHTING DYNAMO STORMSE BATTERY JUNCTION BLOCK THIL LIGHT MELHY SWITCH ruse BUTTON SIDE LIGHT SIDE LIGHT HEND LIGHT HEHD LIGHT

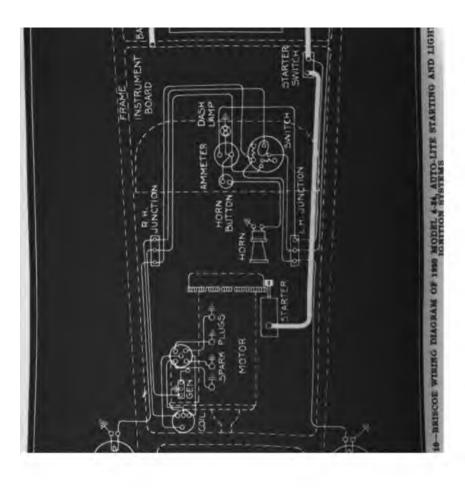

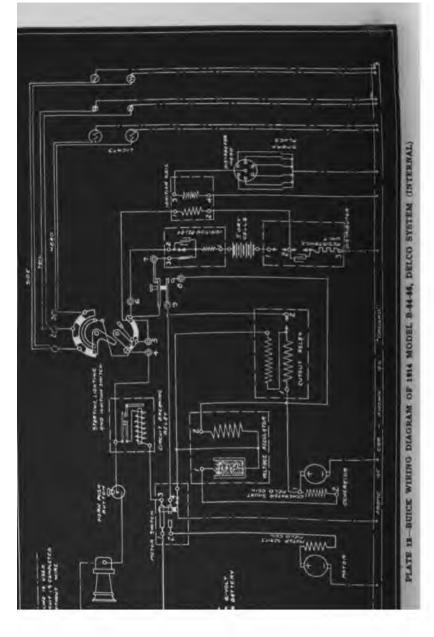

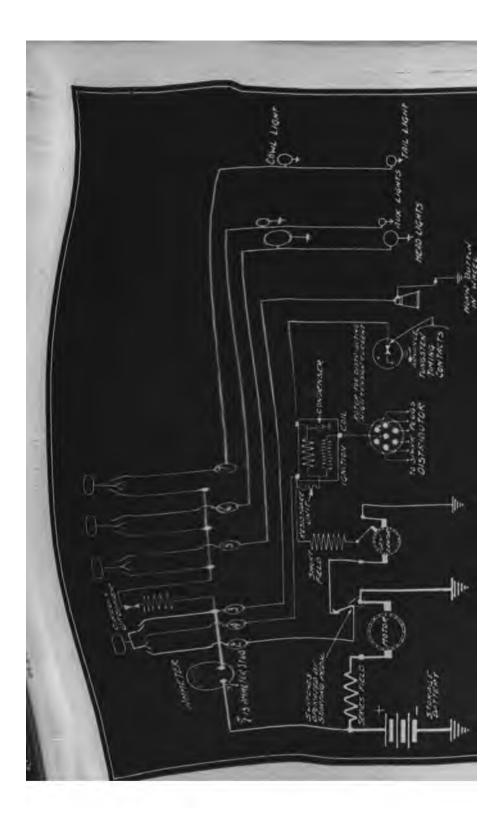

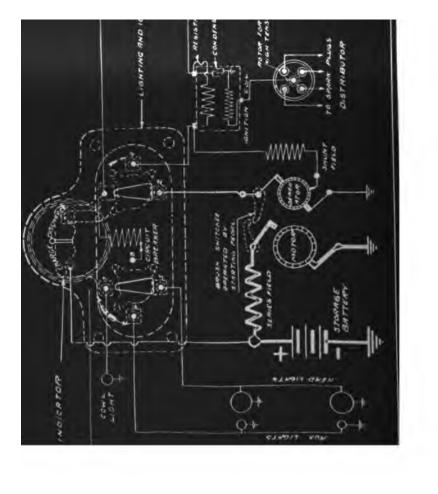

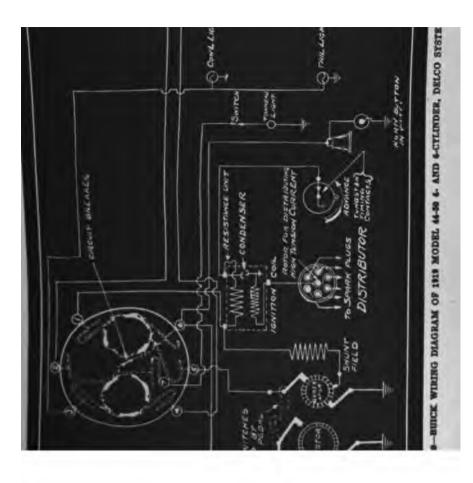

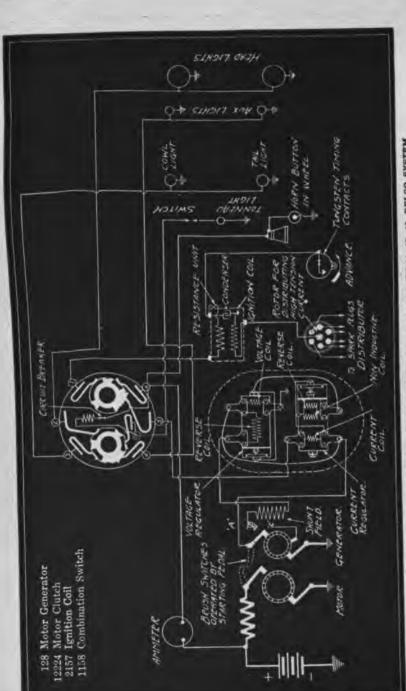


PLATE 16-BUICK WIRING DIAGRAM OF 1920 EXPORT MODEL KX-44, 45, 49, DELCO SYSTEM

## SPARK TIMING

Effect of Irregular Sparking. Like a steam engine, an internal combustion motor depends for its power output on the mean effective pressure developed in the cylinder, usually referred to as its m.e.p. This is affected directly by three factors: first, the initial compression of the charge, that is, the pressure to which the piston compresses the gaseous mixture on its upward or compression stroke just before firing; second, the time at which the charge is ignited; and third, the length of the stroke. It is with the second factor alone that this phase of the ignition problem is concerned. In contrast with the steam engine in which the steam as admitted is at a comparatively low pressure and expands gradually throughout the stroke. the pressure developed in the internal combustion motor at the moment of ignition is tremendous, but it falls off very rapidly. The impulse given the piston is more in the form of a sharp blow than a steady push, as with steam. The mean effective pressure developed depends very largely upon the pressure reached at the moment of explosion and this in turn depends upon the time ignition occurs with relation to the stroke. As the speed of an automobile motor varies over a wide range, it will be apparent that means must be employed for varying the time of explosion. To be most efficient it must occur at the point of maximum compression, i.e., when the piston is exactly at the upper dead center on the compression stroke. As both a mechanical and an electrical lag, or delay, must be com-

for the necessity of this will make plain the car maker's often repeated injunction to the novice—never to drive with the spark retarded. Another and equally important reason is that when operated this way, the combustion is incomplete, the gas continues to burn throughout the stroke, and a greatly increased percentage of its heat has to be absorbed by the water jackets, causing the motor to overheat badly.

Adjusting for Time Factor of Coil. Every induction coil has a certain time constant, which represents the period necessary to completely charge the coil, that is, the time required for the current in the primary winding to attain its maximum value. This time constant depends very largely upon the amount of magnetic energy which can be stored up in the coil. There must be added to this the time required to overcome the inertia of moving parts, such as the timer and the vibrators of a high-tension battery system, or the contact breaker and the distributor in a magneto high-tension system. As these parts are very small and light this would be practically negligible for any other purpose, but when figuring in hundredths of a second, as in the case of the ignition timing of highspeed multi-cylinder motors, it becomes of importance. The object sought, as already mentioned, is to have the spark always occur at the point of maximum compression. To accomplish this with the motor running at high speed, the ignition devices must act while the piston is still an appreciable distance below upper dead center. The timer in the case of a battery system, or the contact breaker of a magneto, is accordingly mounted so that it can be turned through part of a revolution with relation to its driving shaft, or more particularly the cam carried by the latter. For starting the motor by hand, the spark must occur either at or after upper dead center is reached, never before. In the latter case, the piston would be driven backward and the familiar "back kick" result. Hence the manufacturer's admonition—always retard the spark fully before attempting to crank the motor.

Calculation of Small Time Allowance. The relation of spark advance in degrees to piston travel in inches with motors having strokes running from 3 to 8 inches is shown by the accompanying chart, Fig. 91. In this the ratio between the crank and the connecting rod length is 1 to 4.5. The lettering shown indicates the method

of using the chart, the problem being to find the piston travel for an advance of 30 degrees in a motor of 6-inch stroke. The vertical line a, corresponding to this stroke, is traced upward until it intersects the 30-degree line at c; following the latter to the left brings it out at a

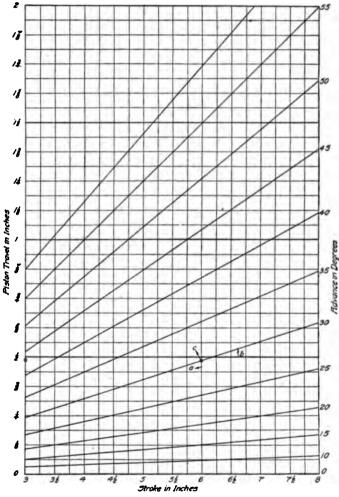


Fig. 91. Relation of Spark Advance to Piston Travel (Bosch)

point just below the ½-inch division, or approximately .46 inch. Assuming that the 6-inch stroke motor were running at 1800 r.p.m., its pistons would be traveling 1800 feet per minute (i.e., stroke doubled or 1 foot per revolution), 30 feet, or 360 inches per second,

so that each inch of the stroke would be covered at an averag speed of 1 inch in  $\frac{1}{380}$  of a second, and the  $\frac{1}{2}$  inch in  $\frac{1}{720}$  of a second from which the necessity for a timing allowance will be apparent

Magneto Timing. Timing is usually 30 to 40 degrees, whice means that the spark occurrence can be advanced or retarded half that distance from a neutral line representing the upper dead center position of the piston. As shown by Fig. 92, the allowance is 34 degree in the Splitdorf magneto, "left" and "right" in this connection having

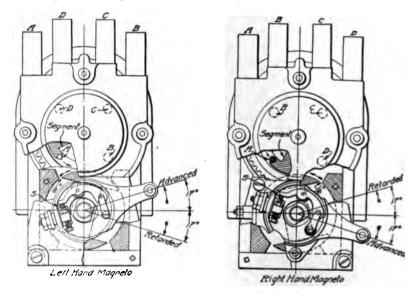


Fig. 92. Method of Advancing and Retarding Spark, Splitdorf Magneto

reference to the direction in which the magneto armature is driver. The necessity of providing this allowance, however, introduces complicating factor in magneto design.

As the timing of the spark is accomplished by opening the contact points of the interrupter earlier or later, it will be apparent that as the magnetic field remains stationary in the ordinary magnetic the relative positions of the armature and field vary. This is illustrated by the sketch, Fig. 93, the left-hand member of which show the position of the armature with advanced spark. This is the point at which the current and voltage are at their maximum, so that the most efficient spark is produced at the plugs. With the sparl retarded, the armature has already had time to turn practically one

eighth of a revolution and the point of maximum intensity has been passed. While this is a factor of which much is usually made in sales literature, it is not so important as the theory of the matter would make it appear, since the spark is seldom retarded except for starting. With the modern high-speed engine there is rarely sufficient


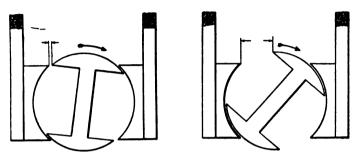


Fig. 93. Position of Magneto Armature for "Advanced" and "Retarded" Ignition

slowing down in hill-climbing to make it necessary to retard the spark, while gear-changing at the proper time further makes this unnecessary, so that practically all the time it is in service, the magneto is operating under the most efficient conditions. The great difference in the positions of the magneto armature between the advanced

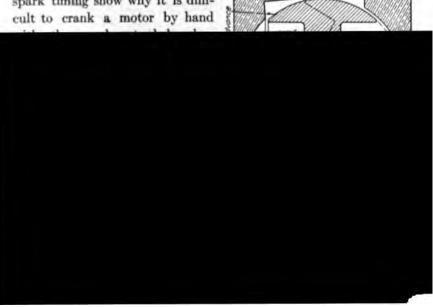and the retarded points of the spark timing show why it is difficult to crank a motor by hand



leeway for variation one way or the other, if the greatest current value is to be utilized.

Analysis of Oscillograph Diagrams. In the oscillograph, the dotted vertical line at the left represents the moment of closing the primary circuit, the current then beginning to increase gradually in value. The resistance of this circuit is such that the current would attain a value of 5 amperes, if the circuit remained closed long enough. However, when the current has attained a value of 4 amperes, the circuit is broken by the vibrator (battery and coil system) and the current then falls off very rapidly. It will be noted that there is no current in the secondary circuit while the primary is attaining its full value, which is due to the fact that the e.m.f.

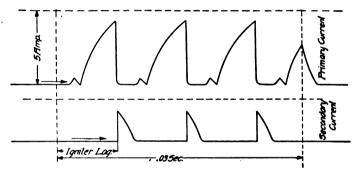


Fig. 95. Oscillograph Diagram of Primary and Secondary Currents (Horseless Age)

induced in the secondary during this period is not sufficient to break down the resistance of the air gap in the spark plug. The spark occurs when the primary circuit is broken, and it is interesting to note that it attains its maximum value instantly, this having been confirmed by numerous oscillograph tests. The right-hand dotted line represents the moment the primary circuit is broken by the timer. With a vibrator coil a series of sparks is produced, as compared with the single spark of the magneto, but these are of no advantage except at low speeds, as when running at full speed, if the first spark fails to ignite the charge, it is already too late by the time the second occurs.

Oscillograph diagrams taken of the current and voltage of a magneto show that both rise to a sharp peak, first in one direction and then in the reverse, as the current is alternating. As the oscillograph illus-

trated shows that only the peak, or maximum, value of the current in the primary of the coil can be utilized for producing a strong induced current in the secondary, so the peak of the magneto current must be taken advantage of to produce the most efficient spark. This point of maximum current value in the revolution of the armature occurs when it is cutting the greatest number of magnetic lines of force of the permanent magnetic field, which is when it is just about to pass from the influence of one set of poles into that of the other, as shown

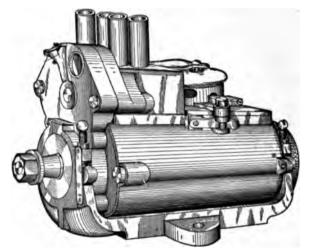


Fig. 96. Mea Magneto in Trunnion Mounting

in the section, Fig. 94. This also shows the relative positions of full advance and full retard and is designed to illustrate the advantages obtained with the patent extended pole pieces of the Simms magneto, most magnetos having the upper and lower faces of both poles in the same plane.

Mea Method of Advancing Spark. Doubtless the most ingenious method of taking care of the necessity for advancing the spark has been developed in the Mea magneto, shown in Fig. 96. Instead of being of horseshoe form, as in the Bosch and Nilmelior magnetos, shown in Figs. 97 and 98, it is bell-shaped, as shown in Fig. 99. The entire magneto is carried in a trunnion mounting so that the field magnets may be turned to the same extent that the contact breaker is moved to give the necessary advance, thus insuring that the circuit will be broken with the armature in the same relative

position to the field poles, which is naturally that of maximum current value.

The method of accomplishing this is shown in Fig. 100, which illustrates the relative positions of the armature and field magnet at the advanced and retarded sparking points to be the same, since the entire magnetic field is partly revolved about the armature



Fig. 97. Bosch Enclosed Type Magneto



Fig. 98. Front View Nilmelior Magneto

This movement is against the direction of rotation of the armature when advancing the spark, and with it when retarding the timing of the ignition, the illustration showing a magneto arranged to be driven clockwise. Fig. 101 illustrates the position of the fields when looking at the driven end of the magneto for advanced and retarded spark in both the clockwise and anti-clockwise types. The range of timing varies from 55 degrees to 70 degrees in the various models: and a specially long range totaling 90 degrees to 100 degrees can be provided, if necessary, by increasing the overall height of the magneto, as the shaft must be supported higher in the trunnions to permit of this. Among the advantages of this method of ignition timing are ease of starting without a battery, quick acceleration, and a uniformly efficient spark at all positions of the spark ing lever.

Magneto Speeds. As the revolution of the armature of the igneto always bears a definitely fixed relation to that of the crank-

aft of the engine, it will be parent that the speed at ich the magneto is driven ll depend upon the number cylinders to be fired, as ill as upon the relation of e cylinders to one another, ., firing 180 degrees or 360 grees a part, as measured the crankshaft. The fol-

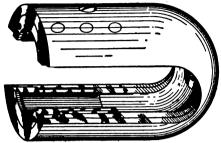


Fig. 99. Bell-Shaped Magnets of Mea Magneto

ving are the various magneto speeds required for engines of the ir-cycle type having from one to twelve cylinders:

cylinder: Either crankshaft or camshaft speed

cylinder: (Impulses 360° apart, as in 2-cylinder opposed motor) camshaft

speed

cylinder: (Impulses alternately at 180°, with 540° intervals, as in the

2-cylinder V-type motor) camshaft speed

cylinder: Three-fourths crankshaft speed


cylinder: Crankshaft speed

cylinder: One and one-half times crankshaft speed

cylinder: Twice crankshaft speed

cylinder: Three times crankshaft speed

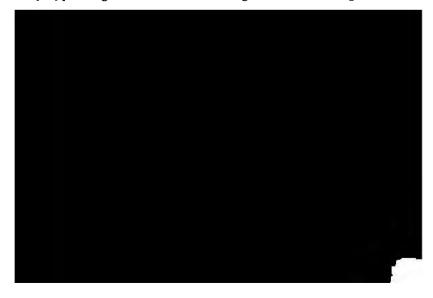Owing to the extremely high speeds necessary, the modern ttery type of ignition is favored to a great extent on eight- and



The magneto speeds necessary on two-cycle motors are twice those given above for the corresponding four-cycle types, with the exception that, on the 2-cylinder 180-degree or V-type motor, crankshaft speed would be correct.

Ignition-System Fixed Timing Point. It has become more or less general practice with French builders to provide an ignition system having a fixed timing point, i.e., one that cannot be controlled by the driver through the usual spark-advance lever as found on practically all American pleasure cars. This is particularly the

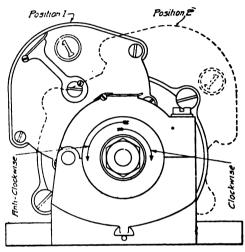


Fig. 101. Spark Advance with Meo Magneto, With Clockwise Instruments, Position 1 Supplies Advanced Spark, Position 2 Retarded Spark

case with taxicabs. While "fixed" in the sense that they are not variable while running, such systems have two firing points, one of maximum advance, which is always employed when the motor is in operation, and the other of maximum retard to enable the driver to crank the motor without danger of injury. So-called fixed-spark ignition systems have come into very general use abroad, more especially on the Continent, but have found very little favor here.

Automatically Timed Systems. The stress laid by automobile manufacturers on their instructions, "always retard the spark before cranking the motor" and "always run with the spark advanced as far as possible, except when necessary to retard it owing to the motor slowing down on hills and causing a hammering noise in the cylinders",

make it evident that there is a considerable amount of discretion left in the driver's hands where this important point is concerned. It is

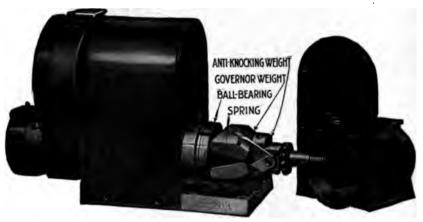


Fig. 102. Eisemann G-A 4 High-Tension Magneto Showing Spark Advance Governor

not desirable that this should be exercised by unskilled drivers, particularly those in charge of large and costly commercial vehicles, and automatically timed systems have accordingly been developed.



Fig. 103. Eisemann G-A 4 Automatic Spark Advance Magneto

Eisemann Centrifugal-Governor Type. To advance the spark timing automatically, a centrifugal governor has been mounted on

the armature shaft in the Eisemann magneto of this type, as shown in Fig. 102. Normally, the weights are contracted by the spring and the contact breaker is held at the fully retarded position, so that it is always safe to crank the motor without the necessity of taking any precautions. With an increase in speed, these weights tend to fly apart and in doing so they draw a sleeve and with it the armature along the shaft with them toward the left-hand end. As there are two helicoidal ridges on the shaft, however, and splines on the inner



Fig. 104. Herz Automatic Spark Advance Coupling




Fig. 105. Herz Automatic Coupling (Side View)

diameter of the sleeve engaging them, the sleeve is forced to make a partial revolution as it moves along the shaft, thus automatically advancing the ignition timing in accordance with the speed. The contact breaker is in fixed relation to the armature. An Eisemann magneto fitted with the automatic timing device is shown in Fig. 103. The manufacturers of the Eisemann magnetos make the claim that their late-model magnetos are constructed with water-tight dust-proof joints, so that rain, water leaks, etc., will not interfere with their operation.

Herz Ball-Governor Type. Another method of accomplishing the same end is the Herz automatic coupling, shown in Figs. 104 and 105. This consists of two juxtaposed disks, each of which is provided with five grooves running in a direction opposite to those of the other disk. Five steel balls are held in these grooves and

act like the weights of a governor, being forced outward in direct proportion to the speed of the motor, thus imparting a twisting movement to the magneto armature with relation to its shaft. The device is supplied either as an integral part of the magneto or as an independent coupling. The range of movement is 40 degrees, the adjustment being varied by altering the curve of the grooves. Fig. 106 shows the Herz magneto. In the Eisemann, spindles having grooved slots of several different pitches are supplied, giving from 19 to 60 degrees of advance. The Atwater Kent, Connecticut, and Westinghouse ignition systems may also be had with automatic advance operated by a centrifugal governor.

Ignition Setting Point. It will be apparent that as provision is made for advancing the time of ignition beyond a certain point as well as retarding it so as to occur before that point, there must be what may be termed a neutral position. This is usually referred to as the ignition setting point. In the majority of instances, this is the upper dead center, particularly where a magneto is employed. For the reason that it is possible to start the motor by handcranking on the magneto with the time of ignition advanced very much farther than would be safe with a battery, as explained in another

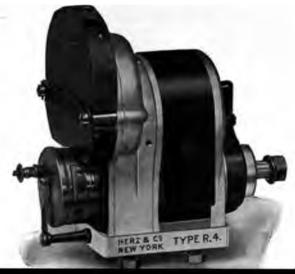



Where a battery is employed, however, it is customary to allow a greater range of timing in both directions with a *late* spark to insure safety in starting, particularly by handcranking. The relation of the ignition distributor of a battery system to the crankshaft is shown in Fig. 107, which illustrates the ignition diagram of the four-cylinder Regal Motor. The firing order in this case is 1-2-4-3, and it will be noted that the ignition setting point is upper dead center.

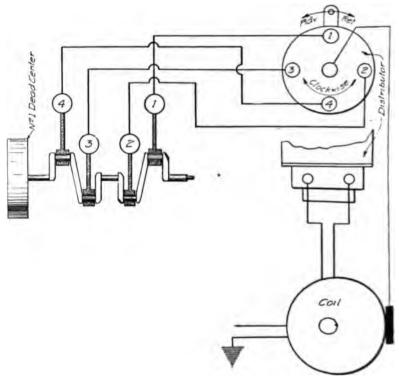


Fig. 107. Relation of Ignition Distributor to Engine Crankshaft.

Courtesy of Regal Motor Car Company, Detroit, Michigan

Both the ignition and the valve timing of practically all motors built in recent years may be checked by marks on the flywheel. A corresponding mark or pointer on the crankcase is used as a checking point.

Fig. 107 shows that when piston No. 1 is exactly at upper dead center, contact No. 1 of the distributor is under the brush leading to the spark plug of that cylinder, and, as shown by the center line this is the ignition setting point for that motor. As the distributor

turns in a clockwise direction, rotating it toward the right, as shown in the diagram, retards the time of ignition, while turning it to the left advances it. The interrupter is just below the distributor and while its battery, ground, and distributor cables are shown, the contacts themselves are not illustrated.

Upper Dead Center. In many cases it is no longer possible to check the ignition timing or the position of the pistons by the flywheel, as the latter is entirely enclosed. To find the upper dead center of the piston of the first cylinder it is accordingly customary to take out a spark plug and use a long knitting needle or similar piece of straight wire. While an assistant turns the motor over slowly by hand, watch the valves of cylinder No. 1. When the inlet valve of this cylinder has closed, the piston is traveling upward on the compression stroke and the needle will rise. It must be borne in mind, however, that the piston is not actually at upper dead center for ignition purposes when the needle ceases rising. In other words, a certain part of the revolution of the crank is not represented by a corresponding movement of the piston, and the proportion that this bears to the whole revolution naturally increases with the length of the stroke.

The starting crank should accordingly be turned until the needle actually starts downward again on the firing stroke, and then the motor turned backward again slightly until it ceases to rise. This may be done by putting the gear lever in high, engaging the clutch,


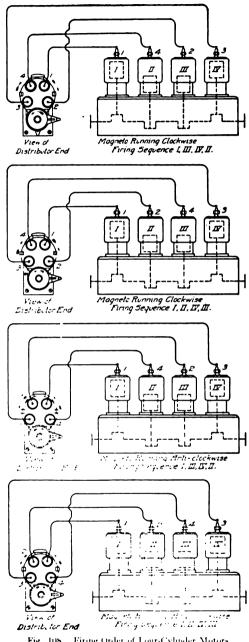



Fig. 108 Firing Order of Lour-Cylinder Motors (Bosch Magneto Company)

at just the right momen Regardless of the numb of cylinders, the cran shaft throws are alwa in pairs. Hence, the p tons rise and fall in pai and the cylinders of the pairs (which have no re tion whatever to the met od of casting the cyl ders themselves) natura cannot follow each oth in firing, the firing ord alternating from one pa to the other. For example to the other. ple, 1-3-4-2- as in t upper diagram of Fig. 10 or 1-2-4-3- as in the d gram just below it, t motors in both instances running "clos wise", i.e., with the crar shaft turning from left right. A similar variati is possible with the mot turning "anti-clockwis or from right to left. shown in the two lowerd grams, which show firi orders of 1-3-4-2- and 2-4-3- the changes bei made by shifting the d tributor connections to t spark plugs of the vario cylinders. In the case a high-tension batte system using unit coi the timer connections a

varied in the same manner. In six-cylinder motors the crank throws are 120 degrees apart, but as the pistons are attached in pairs to cranks in the same plane, the method of distributing the firing order among them is similar to that already given. The Bosch dual ignition system, as installed on the six-cylinder Winton, is a typical firing order for a six. As shown by Fig. 109, this runs 1-5-3-6-2-4.

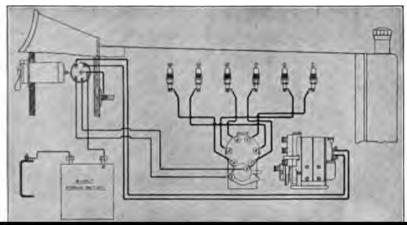Possible Combinations. There are so many possible firing orders in the six-cylinder motor and likewise in the more recent eight-cylinder and twelve-cylinder motors that one of the most puzzling questions arising in the repair shop frequently has been to determine just which one has been adopted by the manufac-



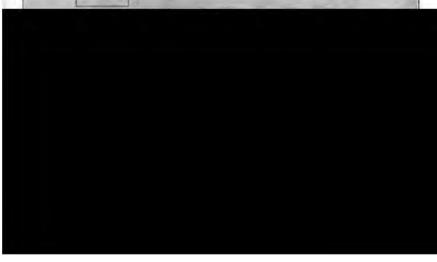

For the V-type eight-cylinder motor, the possible firing orders are as follows:

- (i) 1R 1L 2R 2L 4R 4L 3R 3L (m) 1R 1L 3R 2L 4R 4L 2R 3L
- (j) 1R 1L 3R 3L 4R 4L 2R 2L (n) 1R 1L 2R 3L 4R 4L 3R 2L
- (k) 1R 4L 2R 3L 4R 1L 3R 2L (o) 1R 4L 2R 3L 4R 1L 3R 3L
- (i) 1R 4L 2R 3L 4R 1L 3R 2L (o) 1R 4L 2R 3L 4R 1L 3R 3L (l) 1R 4L 3R 3L 4R 1L 2R 3L 4R 1L 3R 3L 3R 3L

As the last four mentioned involve different firing orders in each set of four cylinders, they need not be considered. With the

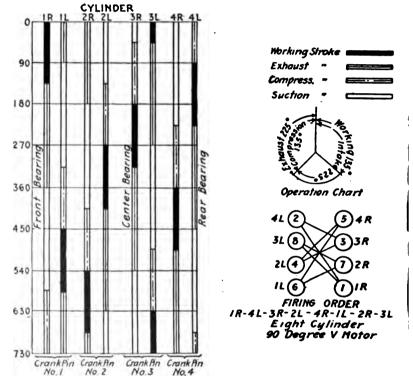


Fig. 110. Firing Order of Eight-Cylinder, V-Type Motor Courtesy of "Automobile Topics", New York City

rocker-arm type of valve lifters using only eight cams, as in the De Dion (French, and the first to use an eight-cylinder motor). Cadillac, and King engines, it is only possible to use the orders k and I, while, as a matter of fact, all three employ the order given in I, which is shown diagrammatically in Fig. 110. The other possible order for an eight (k) may be read from the same diagram by turning it around and changing the numbers from 4L to 1R, 3L to 2R,

and so on. A curious fact is that in each of these orders the sum of the numbers of two cylinders which fire in succession is always 5. By starting always with a right-hand cylinder, the firing order can readily be determined by noting whether the firing order in one of the groups of four cylinders is 1-3-4-2 or 1-2-4-3,

Just as the eight-cylinder V-type motor is simply a combination of two groups of four cylinders, each of which considered alone would have the standard firing order of a four, so the twelve-cylinder V-motor is simply the bringing together on one crankshaft of two six-cylinder motors. The firing order adopted is accordingly one of the two preferred for the six-cylinder motor (g and h), alternating from the right-hand to the left-hand group in the same manner as shown for the eight-cylinder motor.

Firing Orders and Ignition Advance. Repairs and adjustments to the ignition system of a motor are always much easier to carry out when the characteristics of the system in question are known. For this reason the firing orders of the various models of different makes, together with the setting point and the amount of advance and retard, are given here for practically all makes of cars. Wherever it could be obtained, this information is given for all models of every make for several years past, but in some instances it was not available. The information is given in the alphabetical order of the makers' names to make reference easy.

Allen. 1916 Model 37; F. O. 1-2-4-3; contacts open .006 to 008 inch 1917 Classic Model: F. O. 1-2-4-3; contacts open .006

open when mark on flywheel is ½ inch past indicator. Spark fully retarded.

Auburn. 1916 Model 6-40A; F. O. 1-5-3-6-2-4; contacts open .018 to .020 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1917-18 Model 6-39; F. O. 1-5-3-6-2-4; contacts open .025 inch. 1918 Model 6-44; F. O. 1-5-3-6-2-4; contacts open .018 to .020 inch. 1919 Models 6-29, 6-39H and 6-39K; F. O. 1-5-3-6-2-4; contacts open .020 to .025 inch. 1920 Model 6-39A; F. O. 1-5-3-6-2-4; contacts open .022 inch. 1921 Model 6-39; F. O. 1-5-3-6-2-4; contacts open .020 to .025 inch. Contacts open when piston is at upper dead center. Spark fully retarded.

Briscoe. 1917-18 Model 4-24; F. O. 1-3-4-2; contacts open .014 to .015 inch. Model B4-24; F. O. 1-3-4-2; contacts open .023 inch. 1919 Model B4-24; F. O. 1-3-4-2; contacts open .023 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1920-21 Model 4-34; F. O. 1-3-4-2; contacts open .020 inch. Contacts open when mark on flywheel is 1½ inches past indicator. Spark fully retarded.

1916 Models D44, D45, D46, D47, D54, and D55; F. O. Buick. 1-4-2-6-3-5; contacts open .018 inch. Contacts open when mark on flywheel is about 1 inch past upper dead center. Spark fully retarded. 1917 Models D34 and D35; F. O. 1-3-4-2; contacts open .018 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1918 Models E4-34 and E4-35; F. O. 1-3-4-2; contacts open .018 inch. 1916-17 Models D6-44, D6-45, D6-46, and D6-47; F.O. 1-4-2-6-3-5; contacts open .018 inch. 1918 Model E6, 1919 Model H6; F.O. 1-4-2-6-3-5; contacts open .018 inch. 1921 Model 21-Six; F. O. 1-4-2-6-3-5; contacts open .020 inch. Contacts open when DC mark is approximately 1 inch past indicator. Spark fully retarded. 1922 Model 22-Six; F. O. 1-4-2-6-3-5; contacts open .020 inch. Contacts open when 7-degree mark on flywheel is at indicator. Spark fully retarded. Model 22-Four; F. O. 1-3-4-2; contacts open .025 inch. Contacts open when 7-degree mark on flywheel is at indicator. Spark fully retarded.

Cadillac. 1916 Model 53, 1917-18 Model 55, 1918 Model 57, 1919 Model 57, 1920 Model 59; F. O. 1L, 2R, 3L, 1R, 4L, 3R, 2L, 4R; contacts open .018 inch. Contacts open when flywheel mark

"1-GA" registers with indicator with No. 1 piston on left-hand block starting on power stroke. Spark fully retarded. 1921 Model 59; F. O. 1L, 2R, 3L, 1R, 4L, 3R, 2L, 4R; contacts open .020 inch. Contacts open when piston is on compression stroke 121 inches before top dead center. Spark fully advanced.

Case. 1916 Model T; F. O. 1-3-4-2; contacts open .006 to .008 inch. 1917 Model MT; F. O. 1-3-4-2; contacts open .023 inch. 1918-19 Model U; F. O. 1-5-3-6-2-4; contacts open .006 to .008 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1920-21 Model V; F. O. 1-5-3-6-2-4; contacts open .018 inch. Contacts open when flywheel mark "1-6" registers with indicator. Spark one-third advanced.

Chalmers. 1915-16 Models 32 and 32B; F. O. 1-4-2-6-3-5; contacts open .010 to .012 inch. Contacts open when DC mark on flywheel is 1½ inches past indicator. Spark fully retarded. 1916-17 Models 35A, 35B, 35C; F. O. 1-4-2-6-3-5; contacts open .015 to .020 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1916-1917 Model 35B, Series No. 82001-90000, 1918-19 Models 35C, 35D, Series No. 94000-001 to 111000-025; F. O. 1-4-2-6-3-5; contacts open .015 to .018 inch. 1920 Model 35C; F. O. 1-4-2-6-3-5; contacts open .015 to .018 inch. Contacts open when DC mark on flywheel is ½ inch past indicator. Spark fully retarded. 1921 Model 35C; F. O. 1-4-2-6-3-5; contacts open .016 inch. Contacts open when top DC mark on flywheel is 1½ inches past indicator. Spark fully retarded.

Chandler. 1915-16; F. O. 1-5-3-6-2-4; contacts open .015 to .017 inch. 1917-18 Light Six; F. O. 1-5-3-6-2-4; contacts open .014 to .016 inch. 1919 New Series; F. O. 1-5-3-6-2-4; contacts open .014 to .016 inch. 1920-1921 New Series; F. O. 1-5-3-6-2-4; contacts open .015 inch. Contacts open when piston is at upper dead center. Spark fully retarded.

Chevrolet. 1916-17-18 Model 490; F. O. 1-2-4-3; contacts open .023 inch. 1918-19 Model D; F. O. 1R, 4L, 2R, 3L, 4R, 1L, 3R, 2L; contacts open .020 to .025 inch. 1920 Model 490; F. O. 1-2-4-3; contacts open .030 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1921 Model FB; F. O. 1-2-4-3; contacts open .022 inch. Contacts open when piston is at top dead center. Spark fully retarded.

1

Cole. 1915 Model 4-40, 1916 Model 6-66; F. O. Sixes 1-5-3-6-2-4, Fours 1-3-4-2; contacts open .010 to .012 inch. 1916 Model 850; F. O. 1R, 4L, 2R, 3L, 4R, 1L, 3R, 2L; contacts open .018 inch. 1917 Model 860; F. O. 1R, 4L, 2R, 3L, 4R, 1L, 3R, 2L; contacts open .018 inch. 1917 Model 880, 1918 Models 860, 870; F. O. 1R, 4L, 3R, 2L, 4R, 1L, 2R, 3L; contacts open .018 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1919-20-21 Model 870; F. O. 1R, 4L, 3R, 2L, 4R, 1L, 2R, 3L; contacts open .018 inch. Contacts open when piston is 1½ inches from top dead center. Spark fully advanced.

Columbia. 1917-18-19-20 Models C and D; F. O. 1-5-3-6-2-4; contacts open .005 to .008 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1921 Series 7-R; F. O. 1-5-3-6-2-4; contacts open .006 inch. Contacts open when piston is at upper dead center. Spark fully retarded.

Crow-Elkhart. 1916 Models CE-30 and 33; F.O. 1-3-4-2; contacts open .023 to .027 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1917 Models CE-33 and 35, 1918 Models K34, K36; F.O. 1-3-4-2. Contacts open when piston is at upper dead center. Spark 1 inch from fully retarded 1919 Models 32, 34, 36, 42, 44, 46, Series H and K, and 1920 Models 53, 54, 55, 56; F.O. 1-5-3-6-2-4; contacts open .025 to .027 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1921 Models 53, 54, 55 and 56, Series H and L; F.O. Lycoming Four 1-3-4-2, Valve-in-head Four 1-2-4-3, Sixes 1-5-3-6-2-4; contacts open .026 inch. Contacts open when piston is at top dead center. Spark fully retarded.

Cunningham. 1916 Model D, Series 1; F. O. 1R, 4L, 3R, 2L, 4R, 1L, 2R, 3L; contacts open .008 inch. 1917 Model V, Series 2; F. O. 1R, 4L, 3R, 2L, 4R, 1L, 2R, 3L; contacts open .006 inch. 1918-19-20 Model V, Series 3; F. O. 1R, 4L, 3R, 2L, 4R, 1L, 2R, 3L; contacts open .018 inch. Contacts open when piston is at upper dead center. Spark 2 inches from fully retarded position. 1921 Model V, Series 5; F. O. 1R, 4L, 3R, 2L, 4R, 1L, 2R, 3L; contacts open .018 inch. Contacts open when piston is at top dead center. Spark lever 2 inches from lowest position on sector.


**Dodge.** 1915-16; F. O. 1-3-4-2; contacts open .015 to .020 inch. 1917-18; F. O. 1-3-4-2; contacts open .018 to .020 inch. 1919-20-21;

F. O. 1-3-4-2; contacts open .020 inch. Contacts open when piston is at upper dead center. Spark fully retarded.

Dorris. 1916-17 Model IA-6; F. O. 1-5-3-6-2-4; contacts open .014 to .016 inch. 1918 Model IC-C; F. O. 1-5-3-6-2-4; contacts open .014 to .016 inch. 1919 Model 6-8; F. O. 1-5-3-6-2-4; contacts open .014 to .016 inch. 1920 Model 6-8; F. O. 1-5-3-6-2-4; contacts open .014 to .016 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1921-22; F. O. 1-5-3-6-2-4; contacts open .015 inch. Contacts open when piston is at upper dead center. Spark fully retarded.

Dort. 1916 Models 5 and 5A, and 1917 Models 6, 9, 9S, and 9T, using 400R generator; F. O. 1-3-4-2; contacts open .023 inch. 1917 Models 6 and 9, using 400 Generator; F. O. 1-3-4-2; contacts open .025 to .027 inch. 1918 Model 11; F. O. 1-3-4-2; contacts open .023 inch. 1919-20 Model 11; F. O. 1-3-4-2; contacts open .025 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1921 Models 12, 12C, 17, and 17S; F. O. 1-3-4-2; contacts open .025 inch. Contacts open when DC mark on flywheel is 1 inch past indicator. Spark fully retarded.

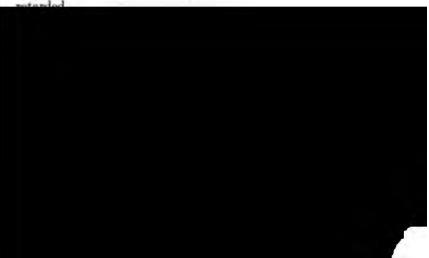Elgin. 1917-18 Model 6-E, Series 1700 to 177760; F. O. 1-4-2-6-3-5; contacts open .020 inch. Contacts separate when DC1-6 mark on flywheel is at center of the opening. Spark fully retarded. 1919 Model H; F. O. 1-4-2-6-3-5; contacts open .022 inch. 1920 Model K; F. O. 1-4-2-6-3-5; contacts open .027 inch. Contacts separate when piston is at top dead center. Spark fully



13 inches past indicator. Spark fully retarded. 1919 Series 9-B; F. O. 1-4-2-6-3-5; contacts open .010 to .012 inch. 1921 Series 9-B; F. O. 1-4-2-6-3-5; contacts open .010 to .012 inch. Contacts open when center line 1-6 on flywheel is 11 inches before the indicator. Spark fully retarded. This control is automatic.

Grant. 1917-18 Model K; F.O. 1-4-2-6-3-5; contacts open .020 to .025 inch. Contacts open when 1-6TC mark on flywheel is  $\frac{3}{4}$  inch past indicator. Spark button pulled out one-half its stroke. 1920 Model H; F.O. 1-5-3-6-2-4; contacts open .006 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1921; F.O. 1-5-3-6-2-4; contacts open .006 inch. Contacts open when piston is at top dead center. Spark fully retarded.

Havnes. 1915-16 Models 30, 33, 34 and 35; F. O. 1-4-2-6-3-5; contacts open .018 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1918 Models 38, 39, 39R, and 39L; F. O. 1-4-2-6-3-5; contacts open .018 to .020 inch. Contacts open when center mark on flywheel is 1 inch past indicator. fully retarded. 1917-18 Models 40, 40R, 41 and 44; F. O. 1R, 6L, 4R, 3L, 2R, 5L, 6R, 1L, 3R, 4L, 5R, 2L. Contacts open when DC mark is \frac{1}{2} inch past indicator. Spark fully retarded. 1919 Model 45-Six; F. O. 1-4-2-6-3-5; contacts open .018 to .020 inch. Contacts open when mark on flywheel is 1 inch past indicator. Spark fully 1920 Model 45; F. O. 1-4-2-6-3-5; contacts open .020 inch. Contacts open when mark on flywheel is ? inch past indicator. Spark fully retarded. 1920 Model 47; F. O. 1-4-2-6-3-5; contacts open .018 inch. Contacts open when DC mark is 25 inch past indicator. Spark fully retarded. 1920 Model 46; F. O. 1R, 6L, 4R, 3L, 2R, 5L, 6R, 1L, 3R, 4L, 5R, 2L; contacts open .018 inch. Contacts open when piston is at upper dead center. Spark one-third advanced. 1921 Model 45; F. O. 1-4-2-6-3-5; contacts open .020 inch. Contacts open when mark on flywheel is # inch past indicator. Spark fully retarded. 1921 Model 47; F.O. 1-4-2-6-3-5; contacts open .018 inch. Contacts open when DC mark is # inch past indicator. Spark fully retarded. 1921 Model 46; F.O. 1R, 6L, 4R, 3L, 2R, 5L, 6R, 1L, 3R, 4L, 5R, 2L; contacts open .018 inch. Contacts open when piston is at upper dead center. Spark one-third advanced.

Holmes. 1918-19-20 Model 1; F. O. 1-4-2-6-3-5; contacts open .012 to .014 inch. Contacts open when mark on flywheel is 1½ inches before indicator. Spark fully retarded.

Hudson. 1916 Model 6-4; F. O. 1-5-3-6-2-4; contacts open .010 inch. 1917-18 Model Super Six; F. O. 1-5-3-6-2-4; contacts open .018 inch. 1919-20 Model O; F. O. 1-5-3-6-2-4; contacts open .018 inch. Contacts open when A mark on flywheel is at indicator. Spark fully retarded. 1921 Model O Super Six; F. O. 1-5-3-6-2-4; contacts open .018 inch. Contacts open when A mark on flywheel is at indicator. Spark fully advanced.

Hupmobile. 1916-17 Series N; F. O. 1-2-4-3; contacts open .010 to .012 inch. 1917-18-19 Model R; F. O. 1-2-4-3; contacts open .006 inch. 1919 Model R; F. O. 1-2-4-3; contacts open .005 to .008 inch. 1920 Models R-3 and R-4; F. O. 1-2-4-3; contacts open .006 inch. 1921 Series R-5; F. O. 1-2-4-3; contacts open .006 inch. Contacts open when DC mark on flywheel is 2 inches past indicator. Spark half-way advanced.

Jordan. 1917 Model 60; F. O. 1-5-3-6-2-4; contacts open .014 to .016 inch. Contacts open when mark on flywheel is \( \frac{1}{6} \) to \( \frac{1}{6} \) inch before indicator. Spark fully retarded. 1918-1919 Model C; F. O. 1-5-3-6-2-4; contacts open .020 inch. Contacts open when mark on flywheel is 1 inch past indicator. Spark fully retarded. 1920 Series M; F. O. 1-5-3-6-2-4; contacts open .020 inch. 1921 Series F and Series M. Contacts open when mark on flywheel is 2\( \frac{1}{2} \) inches past indicator. Spark fully retarded.

King. 1916 Model E; F. O. 1R, 4L, 3R, 2L, 4R, 1L, 2R, 3L; contacts open .010 to .012 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1917 Model EE; F. O. 1R, 4L, 3R, 2L, 4R, 1L, 2R, 3L; contacts open .005 to .008 inch. Contacts open when piston is at upper dead center. Spark ½ inch advanced. 1919 Model G; F. O. 1R, 4L, 3R, 2L, 4R, 1L, 2R, 3L; contacts open .006 inch. 1920 Model H; F. O. 1R, 4L, 3R, 2L, 4R, 1L, 2R, 3L; contacts open .006 inch. Contacts open when piston is at upper dead center. Spark fully retarded.

Kissel-Car. 1917; F. O. 1R, 1L, 4R, 4L, 2R, 2L, 6R, 6L, 3R, 3L, 5R, 5L; contacts open .018 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1917-1918; F. O. 1-5-3-6-2-4; contacts open .020 to .025 inch. Contacts open

k

ľ

when DC mark on flywheel is 11 inches past indicator. Spark full retarded. 1919-1920; F. O. 1-5-3-6-2-4; contacts open .020 to .02 inch. Contacts open when piston is at upper dead center. Spar fully retarded.

Lexington. 1916-17 Model O; F. O. 1-5-3-6-2-4; contacts ope .023 inch. 1917 Models 6-0 and 6-00; F. O. 1-5-3-6-2-4; contact open. 023 inch. 1918-19 Model R; F. O. 1-5-3-6-2-4; contacts ope .017 to .024 inch. Contacts open when piston is at upper dea center. Spark fully retarded. 1921; F. O. 1-5-3-6-2-4; contact open .020 inch. Contacts open when piston is at top dead cente Spark fully retarded.

Liberty. 1916-17-18-19 Models 10, 10A and 10B; F. O. 1-5-3 6-2-4; Delco contacts open .018 inch, Atwater-Kent contacts open .005 to .008 inch. 1920; F. O. 1-5-3-6-2-4; contacts open .024 t .029 inch. Contacts open when piston is at upper dead cente Spark fully retarded. 1921 Model 10C; F. O. 1-4-2-6-3-5; contact open .006 inch. Contacts open when piston is at top dead cente Spark 1 inch from fully retarded position.

Locomobile. 1915-16 Model 38, Type R6, and Model 48 Type M6; F. O. 1-5-3-6-2-4; Bosch contacts open .014 to .016 incl Eisemann contacts open .015 inch. 1917 Models 38 and 48; contact open when piston is  $\frac{5}{16}$  inch from top dead center on Model 3 and  $\frac{7}{16}$  inch from top dead center on Model 48. Spark full retarded. 1919-20 Series VI and VII; F. O. 1-5-3-6-2-4; Berlir contacts open .016 to .020 inch. Magneto contacts separate whe piston is  $\frac{3}{16}$  inch from top dead center. Spark fully retarded Battery contacts separate when piston is  $\frac{3}{16}$  inch from top dead center. Spark fully retarded.

Marmon. 1916-17-18-19 Model 34; F. O. 1-5-3-6-2-4; contact open .014 to .016 inch. 1920 Model 34B; F. O. 1-5-3-6-2-4; contact open .020 to .025 inch. Contacts open when DC mark on flywher is 1 inch past indicator. Spark fully retarded. 1921 Model 341 F. O. 1-5-3-6-2-4; contacts open .022 inch. Contacts open when 1-6 TC mark on flywheel is 1 inch past indicator. Spark full retarded.

Maxwell. 1916-17; F. O. 1-3-4-2; contacts Contacts open when DC mark on flywheel is 1<sup>r</sup> cator. Spark fully re 18 Model 25; F. en .015 incl hes past ind contact open .005 to .008 inch. Contacts open when DC mark on flywheel is 1½ inches past indicator. Spark fully retarded. Early 1919 Model; F. O. 1-3-4-2; contacts open .005 inch. Contacts open when DC mark on flywheel is 1½ inches past indicator. Spark fully retarded. 1920 Model 25, Series 266801-294601; F. O. 1-3-4-2; contacts open .006 inch. 1920 Model 25, Series 294601 up; F. O. 1-3-4-2, contacts open .006 inch. Contacts separate when mark on flywheel is 1½ inches past indicator. Spark fully retarded.

McFarlan. 1916; F. O. 1-5-3-6-2-4; contacts open .006 to .008 inch. Contacts open when piston is at upper dead center. Spark 1 inch from fully retarded position. 1917 Model 127; F. O. 1-5-3-6-2-4; contacts open .014 to .016 inch. Contacts open when piston is at upper dead center. Spark 1 inch from fully retarded position. 1919-20 Model 12, Series X; F. O. 1-5-3-6-2-4; contacts open .014 to .016 inch. Battery contacts separate when DC mark on flywheel is ½ inch before indicator. Magneto contacts separate when DC mark is at indicator. Spark fully retarded in both cases. 1921 Twin Valve Six; F. O. 1-5-3-6-2-4; contacts open .012 to .016 inch. Battery contacts open when DC mark on flywheel is ½ inch before indicator. Magneto contacts open when piston is at upper dead center. Spark fully retarded in both cases.

Mercer. 1916 Series 22-72; F. O. 1-3-4-2; contacts open .014 to .016 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1917 Series 22-73; F. O. 1-3-4-2; contacts open .014 to .016 inch. Set magneto shaft bumper on contact arm. Will be at highest point of breaker cam when piston is on upper dead center. 1918-19-20 Series 4-5; F. O. 1-3-4-2; contacts open .016 to .018 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1921 Series 5; F. O. 1-3-4-2; contacts open .011 inch. Contacts open when piston is at top dead center. Spark fully retarded.

Metz. 1916-17-18 Model 25; F. O. 1-2-4-3; Bosch contacts open .014 inch, Dixie contacts open .018 to .020 inch. 1917-18 Model G; F. O. 1-2-4-3; Atwater-Kent contacts open .006 inch. Contacts open when piston is at top dead center. Spark 1 inch from fully retarded position. 1919-20 Master Six; F. O. 1-5-3-6-2-4; contacts open .018 to .024 inch. Contacts open when piston is at upper dead center. Spark fully retarded.

Mitchell. 1916-17-18; F. O. 1-5-3-6-2-4; contacts open .01 to .020 inch. Contacts open when piston is at upper dead center Spark fully retarded. 1917-18 Model D40; F. O. 1-5-3-6-2-4 contacts open .020 inch. Contacts open when piston is at top dea center. Spark 1 inch from fully retarded position. 1919-20 Mode E40 and E42; F. O. 1-5-3-6-2-4; contacts open .020 to .025 incl Contacts open when piston is at top dead center. Spark full retarded. 1921 Model F40; F. O. 1-5-3-6-2-4; contacts open .02 inch. Contacts open when piston is at top dead center. Spark full retarded. Spar fully retarded.

Moline-Knight, 1914-15 Model MK-30, 1916-17-18 Model MK-40, 1917-18 Models C and G; F. O. 1-3-4-2; contacts open .01 to .020 inch. 1919 Model G; F. O. 1-3-4-2; contacts open .025 incl Contacts open when piston is at upper dead center. Spark full retarded. 1916 Models 6-30 and 6-40; F. O. 1-5-3-6-2-4; contact open .018 inch. Contacts open when piston is at upper dead center Spark half-way advanced. 1917 Models 6-43, 6-66, and 6-45; F. C 1-5-3-6-2-4; contacts open .018 inch. 1918-19 Model 6-66; F. C 1-5-3-6-2-4; contacts open .020 inch. 1920 Victory; F. O. 1-5-3-6 2-4; contacts open .024 to .027 inch. 1920 Model 6-48; F. C 1-5-3-6-2-4; contacts open .018 inch. Contacts open when piston i at upper dead center; spark fully retarded. 1921 Model 6-68; F. C 1-5-3-6-2-4; contacts open .020 inch. Contacts open when top Dt mark on flywheel is  $2\frac{1}{4}$  inches past indicator. Spark fully retarded

Nash. 1917 Model 671; F. O. 1-5-3-6-2-4; contacts open .01 to .020 inch. Contacts open when DC mark on flywheel is \( \frac{1}{2} \) inc past indicator. Spark fully retarded. 1918-19 Models 681, 68 and 687; F. O. 1-5-3-6-2-4; contacts open .015 inch. Contacts ope when DC mark on flywheel is at indicator. Spark fully retarded 1920 Models 681 and 684; F. O. 1-5-3-6-2-4; contacts open .024 t .029 inch. Contacts open when piston is at upper dead center Spark fully retarded. 1921; F. O. 1-5-3-6-2-4; contacts open .02 inch. Contacts open when piston is at top dead center. Spar fully retarded.

National. 1917 Series A and F; F. O. 1-5-3-6-2-4; contacts open .018 to .020 inch. Contacts open when DC mark on flywheel i 1½ inches before indicator. Spark fully advanced. 1917 Serie A and K; F. O. 1R, 6L, 5R, 2L, 3R, 4L, 6R, 1L, 2R, 5L, 4R, 3L

contacts open .018 inch. Contacts open when piston is at upper dead center. Spark one-third advanced. 1919-20-21 Series A1 and BB; F.O. 1-5-3-6-2-4; contacts open .018 inch. Contacts open when DC mark on flywheel is  $\frac{3}{4}$  inch past indicator.

Oakland. 1916 Model 32; F. O. 1-5-3-6-2-4; contacts open .020 to .025 inch. 1916-17 Model 50; F. O. 1-7-2-5-4-6-3-8; contacts open .018 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1917 Models 32B and 34; F. O. 1-5-3-6-2-4; contacts open .018 inch. 1918 Model 34B; F. O. 1-5-3-6-2-4; contacts open .020 to .025 inch. 1920 Model 34B; F. O. 1-5-3-6-2-4; contacts open .022 inch. Contacts open when DC mark on flywheel is ½ inch before indicator. Spark fully retarded. 1921 Model 34C; F. O. 1-5-3-6-2-4; contacts open .022 inch. Contacts open when top DC mark on flywheel is ½ inch past indicator. Spark fully retarded.

Oldsmobile. 1916-17 Models 44, 37 and 45; F. O. 1R, 4L, 3R, 2L, 4R, 1L, 2R, 3L; contacts open .018 inch. Contacts open when DC mark is ½ inch before indicator. Spark fully retarded. 1918 Models 45A and 37; F. O. 1R, 4L, 3R, 2L, 4R, 1L, 2R, 3L; contacts open .020 inch. 1919 Model 45A; F. O. 1R, 4L, 3R, 2L, 4R, 1L, 2R, 3L; contacts open .018 inch. Contacts open when piston is at upper dead center 2 inches from top of sector. 1919 Models 37 and 37A; F. O. 1-5-3-6-2-4; contacts open .020 to .025 inch. Contacts open when piston is at top dead center. Spark fully retarded. 1919-20 Model 45D; F. O. 1R, 4L, 3R, 2L, 4R, 1L, 2R, 3L; contacts open .020 inch. 1920 Model 37A; F. O. 1-5-3-6-2-4; contacts open when piston is at upper dead center. Spark fully retarded. 1921 Models 37 and 37A; F. O. 1-5-3-6-2-4; contacts open .020 inch. Contacts open when piston is at top dead center. Spark fully retarded.

Overland. 1916 Model 75; F. O. 1-3-4-2; contacts open .018 to .020 inch. Contacts open when DC mark on flywheel is 1½ inches past indicator. Spark fully retarded. 1916 Model 83; F. O. 1-3-4-2; contacts open .018 to .020 inch. Contacts open when DC mark on flywheel is 1½ inches past indicator. Spark fully retarded. 1916 Model 86; F. O. 1-5-3-6-2-4; contacts open .020 inch. Contacts open when DC mark on flywheel is 1½ inches past indicator. Spark fully retarded. 1917 Model 85-6; F. O. 1-5-3-6-2-4;

١,

contacts open .018 inch to .020 inch. Contacts open when D mark on flywheel is 11 inches past indicator. Spark fully retarde 1917-18 Models 85-4 and 90; F. O. 1-3-4-2; contacts open .016 .018 inch. Light Four and Country Club; F. O. 1-3-4-2, contac open .016 to .020 inch. Contacts open when mark on flywheel Spark fully retarded. 11 inches past indicator. 1920 Model F. O. 1-3-4-2; contacts open .016 to .018 inch. Contacts open who piston is at upper dead center. Spark fully retarded. 1919-: Models 3-25, 3-35; F. O. 1R, 6L, 4R, 3L, 2R, 5L, 6R, 1L, 3R, 4 5R. 2L; contacts open .015 to .020 inch. Right-hand contacts open when flywheel mark SR is at indicator. Spark fully advance This is firing position for No. 1 right-hand cylinder. contacts open when SL mark on flywheel is at indicator. fully advanced. This is the firing position for No. 1 left-hai cylinder. 1921 Models 3-25 and 3-35; F. O. 1R, 6L, 4R, 3L, 2l 5L, 6R, 1L, 3R, 4L, 5R, 2L; contacts open .015 inch. Contacts open on right-hand side when SR mark on flywheel is at indicator. fully advanced. Piston No. 1 on right-hand block is ready to fir 1921 Single Six; F. O. 1-5-3-6-2-4; contacts open .018 inch. Co tacts open when mark on flywheel is 11 inches before center lin of motor. Spark fully advanced.

Paige. 1916-17-18 Models 6-38 and 6-39; F. O. 1-5-3-6-2-contacts open .020 to .025 inch. Contacts open when DC mark of flywheel is 1 inch before indicator. Spark fully retarded. 19 Model 6-51; F. O. 1-5-3-6-2-4; contacts open .020 to .025 inc Contacts open when DC mark is 1½ inches past indicator. Spar fully retarded. 1919; F. O. 1-5-3-6-2-4; contacts open .020 to .025 inch. Contacts open when piston is at upper dead center. Spar fully retarded. 1920 Models 16-19 and 15-19; F. O. 1-5-3-6-2-contacts open .006 inch. Contacts open when DC mark on flywhee is 1½ inches past indicator. Spark fully retarded. 1921 Models 15-19 and 17-20; F. O. 1-5-3-6-2-4; contacts open .006 inch. Contacts open when TC 1-6 mark on flywheel is 1½ inches past indicator. Spark fully retarded.

Peerless. 1917 Model 56; F. O. 1R, 4L, 3R, 2L, 4R, 1L, 2. 3L; contacts open .010 to .012 inch. Contacts open when piste is at top dead center. Spark half-way advanced. 1919-20 Mode 66 and 56, Series 6; F. O. 1R, 4L, 3R, 2L, 4R, 1L, 2R, 3L; contact

open .005 to .008 inch. Contacts open when piston is at top dead center. Spark fully retarded. 1921 Model 56, Series 7; F. O. 1R, 4L, 3R, 2L, 4R, 1L, 2R, 3L; contacts open .006 inch. Contacts open when piston is at top dead center. Spark one-half advanced.

Pierce-Arrow. 1916-17-18, Series 4, 1918 Series 5; F. O. 1-5-3-6-2-4; contacts open .010 to .012 inch. Contacts open when magneto mark on flywheel is at indicator. Spark fully retarded. Battery contacts open when ignition mark on flywheel is at indicator. Spark fully retarded. 1919-20 Models 38 and 48; F. O. 1-5-3-6-2-4; contacts open .015 inch. Contacts open when ignition mark on flywheel is at indicator. Spark fully retarded. Both contacts must open at the same time.

Premier. 1916-17 Models 6B and 6C; F. O. 1-5-3-6-2-4; contacts open .020 inch. 1919 Model 6C; F. O. 1-5-3-6-2-4; contacts open .018 inch. Contacts open when piston is at top dead center. Spark fully retarded. 1920 Model 6D; F. O. 1-5-3-6-2-4; contacts open .018 to .020 inch. Contacts open when DC mark on flywheel is 1½ inches past indicator. Spark fully retarded. 1921 Model 6D; F. O. 1-5-3-6-2-4; contacts open .018 inch. Contacts open when piston is at top dead center. Spark fully retarded.

Reo. 1916 Models R. S. M and N: F. O. 1-4-2-6-3-5; contacts open .015 to .020 inch. 1917 Models R, S, M and N; F. O. 1-4-2-6-3-5; contacts open .020 to .025 inch. Contacts open when DC mark on flywheel is 11 inches past indicator. Spark fully retarded. 1918 Models M, T and U; F. O. 1-3-4-2, Sixes 1-4-2-6-3-5; contacts open .018 to .023 inch. Contacts open when DC mark on four-cylinder cars is 1 inch before indicator and 1 inch before indicator on six-cylinder cars. Spark fully retarded. 1919 Models T and U: F.O. 1-3-4-2; contacts open .020 to .025 inch. Contacts open when mark on flywheel is 13 inches past indicator. fully retarded. 1921 Early Models T6 and U6; F.O. 1-4-2-6-3-5; contacts open .020 inch. Contacts open when "spark 1 & 6" mark on flywheel is in line with upper edge of right-hand engine support. Spark fully retarded. 1921 Late Models T6 and U6; F.O. 1-4-2-6-3-5; contacts open .020 inch. Contacts open when "spark 1 & 6" mark on flywheel is in line with upper edge of right-hand engine support. Spark fully retarded. 1916-17 Models S2, B5-R and B6-R; F. O. 1-5-3-6-2-4; contacts open .012 inch. 1917-18 Models S2-T, S4-T, S4-R, S4-S and Y-18; F. O. 1-5-3-6-2-4; contacts open .020 to .025 inch. 1919 Model Y-18; F. O. 1-5-3-6-2-4; contacts open .020 to .025 inch. Contacts open when DC mark on flywheel is 1 inch past indicator. Spark fully retarded.


Saxon. 1920 Model Y18-T; F. O. 1-4-2-6-3-5; contacts open .020 to .025 inch. Contacts open when piston is at top dead center. Spark fully retarded.


Scripps-Booth. 1916-17 Models C, D and G; F.O. 1R, 1L, 3R, 3L, 4R, 4L, 2R, 2L; contacts open .020 to .025 inch. Contacts open when piston is at top dead center. Spark fully retarded. 1917 Model G; F.O. 1-3-4-2; contacts open .020 to .025 inch. Contacts open when piston is \( \frac{3}{6} \) inch past DC mark on flywheel. Spark fully retarded. 1918-19 Models 6-39, 6-40; F.O. 1-5-3-6-2-4; contacts open .020 to .025 inch. Contacts open when piston is at upper dead center. Spark fully retarded. 1920 Series B; F.O. 1-5-3-6-2-4; contacts open .022 inch. Contacts open when DC mark on flywheel is 1 inch past indicator. Spark fully retarded.


Stearns-Knight. 1916-17-18 Models SKL4 and SK8, Series 30, 31 and 32; F. O. 1-2-4-3; Eights 1R, 4L, 2R, 3L, 4R, 1L, 3R, 2L; contacts open .020 to .025 inch. Contacts open when DC mark on flywheel is 1½ inches past indicator. Spark fully retarded. 1919 Model SKL4; F. O. 1-3-4-2; contacts open .020 to .022 inch. Contacts open when DC mark on flywheel is 1½ inches past indicator. Spark fully retarded. 1920 Model KL4; F. O. 1-3-4-2; contacts open .006 inch. Contacts open when DC mark on flywheel is 2¼ inches past indicator. Spark fully retarded.

Stephens. 1917-18-19 Models 65, 70, 74, 75 and 78; F.O. 1-4-2-6-3-5; contacts open .018 inch. Contacts open when piston is at top dead center. Spark one-third advanced. 1919-20, Salient Six, Series 2; F.O. 1-4-2-6-3-5; contacts open .025 inch. Contacts open when piston is at top dead center. Spark fully retarded.

Studebaker. 1916-17-18, Series 16, 17 and 18; F.O. Fours 1-3-4-2, Sixes 1-5-3-6-2-4; contacts open .015 inch. Contacts open when DC mark on flywheel is 4 inches before indicator on Fours, and on Sixes 5<sup>1</sup>/<sub>8</sub> inches before indicator. Spark fully advanced. 1918-19 Series 19; F.O. Fours 1-3-4-2, Sixes 1-5-3-6-2-4; contacts open .020 inch. 1920 Models EH and EG, Series 20; F.O. 1-5-3-

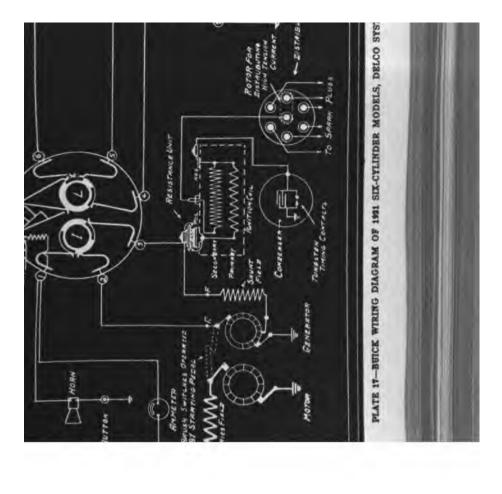

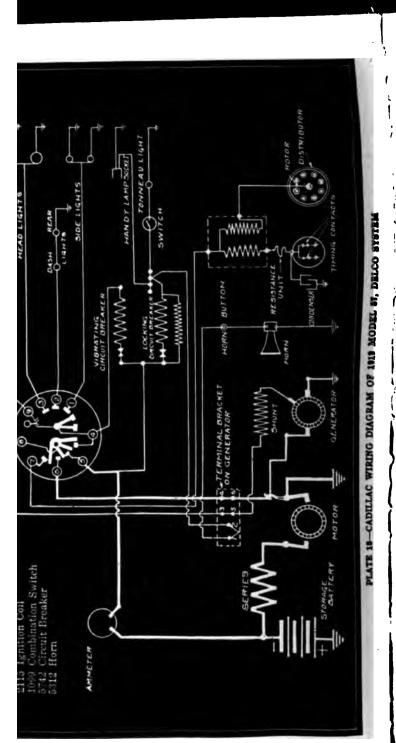

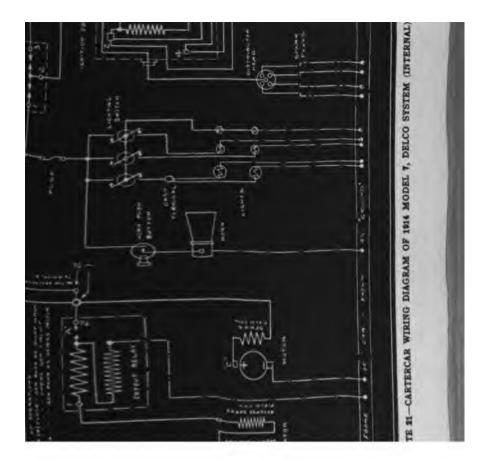



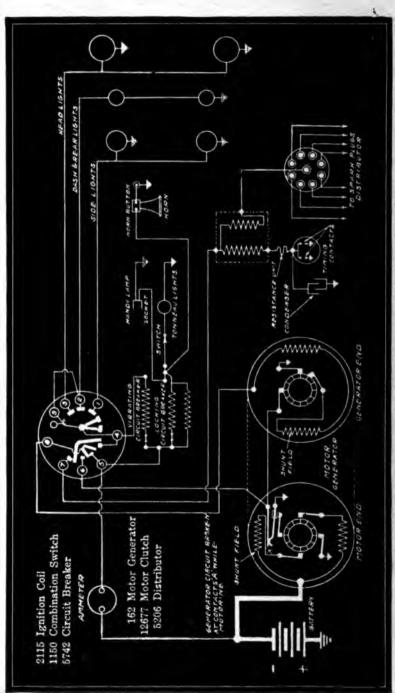


PLATE 20-CADILLAC WIRING DIAGRAM OF 1886 MODEL 89, DELCO SYSTEM

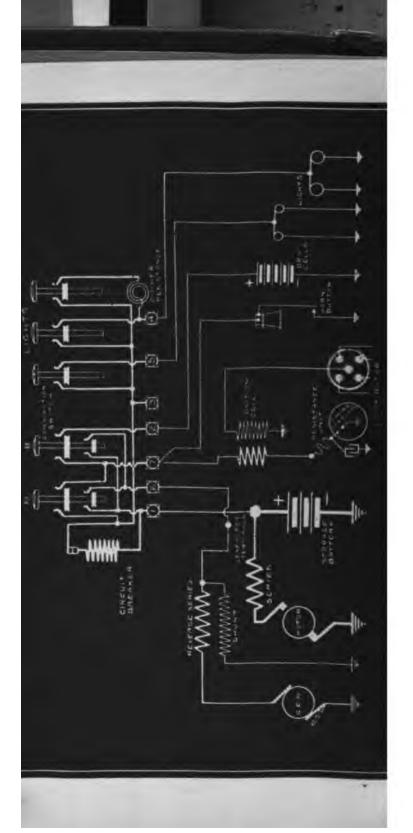

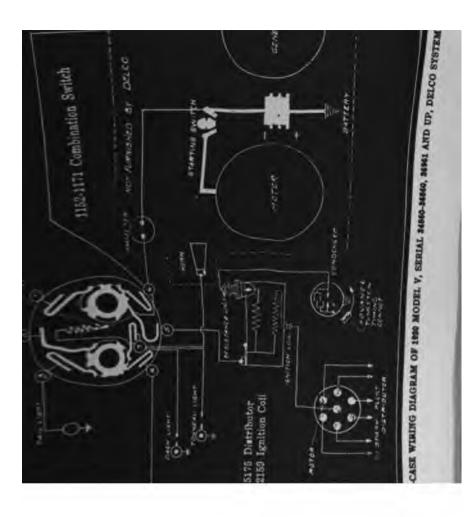



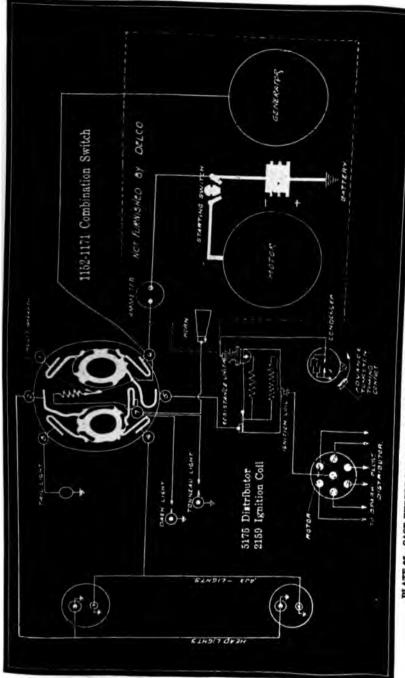


PLATE 26—CASE WIRING DIAGRAM OF 1920 MODEL V, SERIAL 34860-36640, 26961 AND UP, DELCO SYSTEM

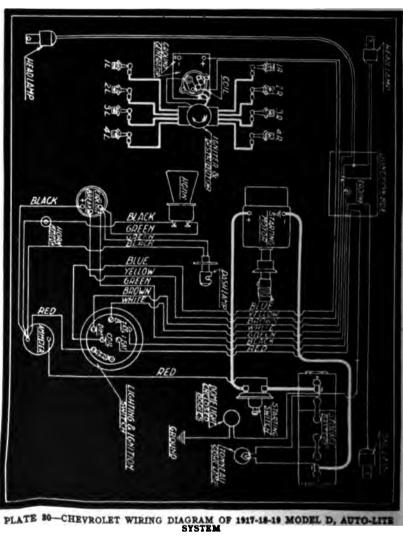

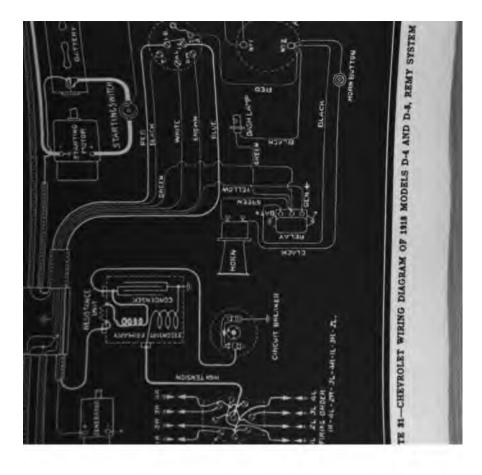

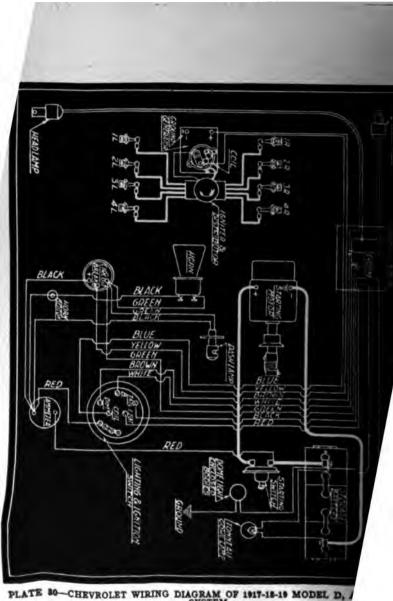


PLATE 30—CHEVROLET WIRING DIAGRAM OF 1917-18-19 MODEL D. SYSTEM

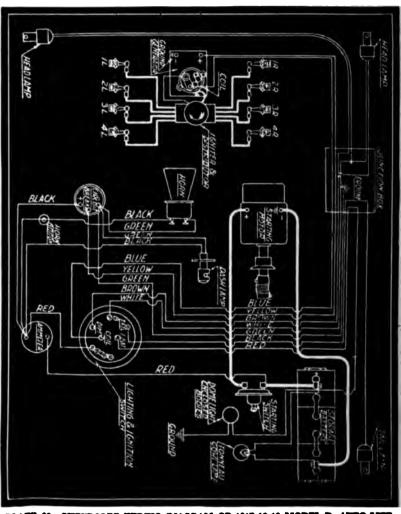


PLATE 80—CHEVROLET WIRING DIAGRAM OF 1917-18-19 MODEL D, AUTO-LITE SYSTEM

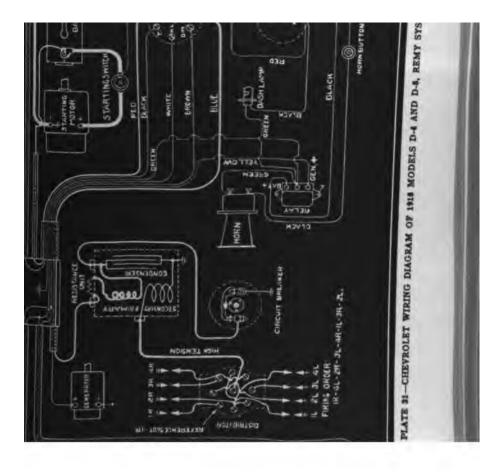


PLATE 39-CHEVROLET WIDING DIAGRAM OF THE TANDER WAS AUTO-LOTE SVETEW

6-2-4; contacts open .024 to .029 inch. Contacts open when AD-SP mark on flywheel is at indicator. Spark fully advanced.

Stutz. 1916-17-18; F.O. 1-3-4-2; contacts open .018 inch. Magneto contacts open when piston is at top dead center. Spark 1½ inches from the fully retarded position. 1919-20 Model II; F.O. 1-3-4-2; contacts open .018 inch. Contacts open when piston is at top dead center. Spark 1½ inches from fully retarded position. 1921 Series K; F.O. 1-3-4-2; contacts open .018 inch. Contacts open when piston is at top dead center. Spark lever 1½ inches from fully retarded position.

Templar. 1918 Model 445; F.O. 1-3-4-2; Battery contacts open .020 to .023 inch. Magneto contacts open .014 to .016 inch. 1920 Model A445; F.O. 1-3-4-2; contacts open .015 inch. Contacts open when piston is at top dead center. Spark fully retarded. 1921 Model 4-45; F.O. 1-3-4-2; contacts open .015 inch. Contacts open when piston is at top dead center. Spark fully retarded.

Velic. 1917 Model 28; F. O. 1-5-3-6-2-4; contacts open .025 inch. Contacts open when DC mark on flywheel is  $\frac{3}{8}$  inch past indicator. Spark fully retarded. 1918-1919 Models 38, 39, 39-7 and 39 Sport; F. O. 1-5-3-6-2-4; contacts open .015 to .018. Contacts open when DC mark on flywheel is  $\frac{1}{2}$  inch past indicator. Spark fully retarded. 1920 Model 48; F. O. 1-5-3-6-2-4; contacts open .006 inch. Contacts open when piston is at top dead center. Spark fully retarded. 1921 Model 48; F. O. 1-5-3-6-2-4; contacts open .006 inch. Contacts open when piston is at top dead center. Spark fully retarded.

Westcott. 1916 Models 45 and 51; F. O. 1-5-3-6-2-4; contacts open .018 inch. Contacts open when mark on flywheel is 1½ inches past indicator. Spark fully retarded. 1917-18 Series 17 and 18; F. O. 1-5-3-6-2-4; contacts open .018 inch. Contacts open when DC mark on flywheel is 2 inches past indicator. Spark fully retarded. 1919-20 Models A48 and A38; F. O. 1-5-3-6-2-4; contacts open .020 inch. Contacts open when piston is at top dead center. Spark one-third advanced. 1920 Models C48, A38 and C38; F. O. 1-5-3-6-2-4; contacts open .018 inch. Contacts open when DC mark on flywheel is 1¾ inches past indicator. Spark fully retarded. 1921 Model C48; F. O. 1-5-3-6-2-4; contacts open .018 inch. Contacts open .018 inch. Contacts open .018 inch.

tacts open when DC mark on flywheel is 13 inches past indicator. Spark fully retarded.


Willys-Knight. 1916 Model 48, F. O. 1-3-4-2; contacts open .020 inch. Contacts open when top DC mark on flywheel is 2½ inches past indicator. Spark fully retarded. 1916-17 Model 88-4; F. O. 1-3-4-2; contacts open .016 to .018 inch. Contacts open when DC mark on flywheel is 2½ inches past indicator. Spark fully retarded. 1916-17-18 Model 88-8; F. O. 1R, 1L, 3R, 3L, 4R, 4L, 2R, 2L; contacts open .020 to .025 inch. Contacts open when DC mark on flywheel is 1½ inches past indicator. Spark fully retarded. 1920 Model 20; F. O. 1-3-4-2; contacts open .018 inch. Contacts open when piston is at top dead center. Spark fully retarded. 1921 Model 20; F. O. 1-3-4-2; contacts open .018 inch. Contacts open when piston is at top dead center. Spark lever fully retarded.


Winton. 1915 Model 21A, 1916-17 Models 22 and 22A; F. O. 1-5-3-6-2-4; contacts open .014 to .016 inch. Contacts open when piston is at top dead center. Spark ½ inch from fully retarded position. 1920 Model 25; F. O. 1-5-3-6-2-4; contacts open .014 to .016 inch. Contacts open when piston is at top dead center. Spark fully retarded. 1921 Model 25; F. O. 1-5-3-6-2-4; contacts open .015 inch. Contacts open when piston is at top dead center. Spark fully retarded.

Wiring. Necessity for High-Tension Cables. Mention has been made of the fact that in early days much trouble was experienced with poorly insulated and poorly mounted wires. This was particularly the case with the secondary circuits, the insulation of which was frequently inadequate to carry currents at the high potentials employed, so that there was more or less leakage. This was further aggravated by the chafing, or rubbing, of these wires against moving parts. The former trouble was eliminated by the adoption of specially constructed cables which are tested to carry 30,000 volts. Cables of this type are illustrated in Fig. 111, which also shows the cables employed for electric lighting and starting installations, where the chief difficulty has usually been the selection of a cable of too small a carrying capacity for the current used.

The importance of using heavily insulated cables for both the primary and secondary cables of the ignition, and, more particularly

the latter, has come to be generally understood, and cables especially designed for this service have now been in use for a number of years; but the importance of using wiring of ample capacity, in the lighting and starting circuits, is not so well appreciated. In the former instance, the problem was one of insulation only, the amount necessary to prevent leakage of the secondary current not being fully realized in the early days; nor was the necessity for thoroughly protecting the primary cables from the effects of oil and water taken into account. Trouble from these sources, however, have long since been a matter of the past; even the well-insulated cables now in general

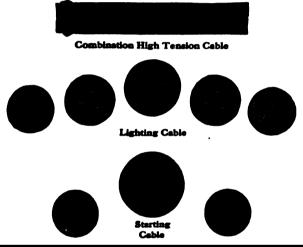

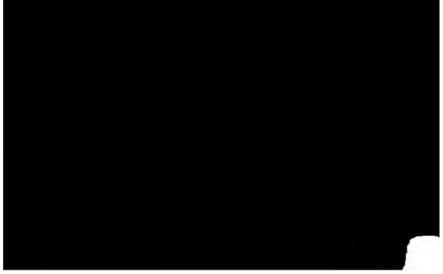

where the available potential is only 6 volts, are two very different things. A voltage drop of one to 5 volts in an incandescent lighting system is negligible. A drop of 5 volts below the 110-volt standard will cause a perceptible dimming of the lamps, but the life of the lamp filaments themselves will be greatly increased, other factors remaining the same, so that the loss in efficiency is not of such great moment.

Importance of Voltage Drop. But, in an electric starting and lighting system, the loss of even a fraction of a volt due to the wiring represents a substantial falling off in the power. As mentioned in the introductory, the unit of potential, or voltage, times the unit of current flow, or ampere, equals the watt or power unit, and there are 746 watts in an electrical horsepower. Take the case of an electric-starting motor with an unusually long connection between the battery and the electric motor. Assuming that the length and diameter of this wire is such that there is a loss of 1 volt between the battery and the motor and that, at the moment of starting, 300 amperes are required to break away the engine, i.e., free the pistons and bearings when the lubricating oil has thickened from the cold so as to bind them. In the actual power consumed, this voltage drop represents  $300 \times 1$ , or 300 watts, equivalent to more than  $\frac{3}{7}$  horsepower.

The loss of but ½ volt, other factors remaining the same, is equivalent to almost \(\frac{1}{6}\) horsepower, or about what a strong man can exert for a limited time. This appears to be getting things down pretty fine, but in the case of the Dyneto system, the manufacturers specify that the cable between the starting motor and the storage battery must be large enough to transmit 400 amperes with a total loss not to exceed \(\frac{1}{4}\) volt. With this amount of current, the voltage drop in question represents 100 watts, or nearly † horsepower. Of course. this loss only takes place at the instant of starting, but that is just the time when the highest efficiency and the full power of the battery is required. Moreover, the starting motor frequently has to be operated a number of times, especially in cold weather when the battery efficiency is at its lowest, before the engine will start. lower-current values necessary for turning the engine over after it has been broken away, a drop of one volt represents an appreciable power loss, as the current consumed is anywhere from 50 to 100 amperes. It will be apparent from this why the manufacturers lay such emphasis on their instructions not to lengthen connections, if avoidable.

and then only to use wire of the same size and kind. This, of course, does not apply to the starting motor connection, as that should never be lengthened without increasing the diameter of the wire to compensate for the increase in length.

Calculating Size of Cable. It is not advisable to do so where it can possibly be avoided, but, when made necessary by the fitting of an enclosed body, the following formula should be used for calculating the size of cable that should be employed:

$$\frac{\text{Maximum current} \times 10.7 \times \text{number of feet of wire}}{25} = \text{diameter or cross-}$$

section of wire in circular mils

For example, in the case cited above, where the maximum current at the instant of starting is 300 amperes and the distance between the battery and the starting motor is four feet (measured from battery to switch and from the latter to the starting-motor terminal), the size of wire necessary would be:

$$\frac{300\times10.7\times4}{.25} = 51,360 \text{ circular mils}$$

As shown in the table on page 27, which gives the corresponding sizes of the B & S gage, the nearest to this is No. 3 wire of 52,634 circular mils cross-section, but, to allow for a factor of safety, either a No. 2 or a No. 1 wire would be used for such an installation. Now, in case it becomes necessary to take the battery from the running board close to the engine and place it under the floor of an enclosed body, increasing the length of wire needed to 8 feet, the cross-section of the wire required would be 102,720 circular mils, the closest gage number to this being the No. 0 cable. In other words, doubling the length of the cable would make it necessary to double its cross-section in order to prevent exceeding the minimum permissible drop in the voltage. This will make plain why some of the amateur experiments in re-locating the essentials of an electric starting system have had such disastrous effects on its efficiency.

Effect on Lights. In the case of the lamps, the effect of an increased drop in the voltage is not so serious; though, because of the very low-battery voltage available, what would otherwise be a

negligible loss assumes important proportions. On the 3-cell 6-volt battery now so generally used, the lamp filaments are designed to burn to full brightness on a potential of 6 to 8 volts, this variation being provided to compensate for the difference in the battery voltage when fully charged and when partly discharged, as the voltage of the battery decreases as it discharges, dropping to but 1.50 volts per cell when practically exhausted, or a total of 4½ volts. Even if receiving this full voltage, the 6-volt bulbs would burn very dimly, but there must be deducted from it the voltage drop due to the wiring and the switches. This is the reason why the brightness of the lamps (with the generator idle) affords such an excellent indication of the state of charge of the battery.

It will be apparent from the above that a drop in potential of but one volt in the lighting circuit would cause a serious loss of efficiency at the bulbs. Assuming that the headlights consume 4 to 5 amperes, and applying the above formula on the basis of a maximum distance of 10 feet from the battery, it is found that a No. 16 wire is necessary; but, in order to provide a large factor of safety, nothing smaller than No. 14 wire is ordinarily employed for the lighting circuits, and, in some cases, it is No. 12.

Importance of Good Connections. Under the head of "Resistance", however, attention has been called to the fact that not alone the length and size of the connecting wires, but also all switches and joints are factors in calculating the total resistance of a circuit. Consequently, it is poor practice ever to make a joint in a wire where a single length may be employed. Whenever a wire is broken by accident, the trouble should always be remedied by replacing it with an entirely new piece rather than by making a joint in the old wire. Loose connections also add greatly to the total resistance in a circuit, as well as connections in which the contact faces of the terminals are dirty or corroded. In replacing or tightening connections, care should be taken to see that the parts in contact are scraped or filed bright and that both the terminal nut and its lock nut are screwed down firmly. The switches are also an important factor where voltage drop is concerned and switch blades or contacts that are dirty or corroded, or that are not held firmly in contact when closed, will be responsible for an appreciable drop in the voltage that will become increasingly perceptible as the battery becomes discharged.

Some Ignition Cable Pointers. At the beginning of the automotive industry, but little attention was paid to high-tension spark-plug wires. Today, however, automotive engineers are giving this subject more serious consideration, realizing the importance of this unit in the proper operation of the internal-combustion motor. As these wires are required to carry a voltage ranging from 6000 to 18,000 volts, it will be necessary to insulate them thoroughly. The material to be used should be a compound which has high dielectric characteristics. The reason for this is that continual satisfactory operation of the ignition depends upon the quality of this material.

Installations Used. Three general installations are used in automobile work: (1) open wiring between distributor and spark plugs, the wires being supported by brackets or running free; (2) wiring in fiber or other insulating conduits; and (3) wiring in grounded metal conduit.

Installation No. 1 can be successfully used on those motors where the distance between the distributor and the spark plugs is short and thus the wires will be prevented from striking the motor or other metal and injuring their insulation.

The disadvantages of this installation, however, are lack of mechanical protection and a development of electrostatic surface capacity when insulated brackets are used. If the wires are run through holes in brackets larger than the wires, the insulation will be chafed and weakened. On the other hand, if the wires are clamped in position, the thickness of the insulation will be lessened because of compression.

Installation No. 2 offers mechanical protection, but it has the great disadvantage of allowing the electrostatic charge to attain a high pressure before discharging to the ground.

Installation No. 3 can be used advantageously on the majority of four- and six-cylinder motors. This method also offers mechanical protection of the wires and greatly reduces the strength of the electrostatic charge, but this type of assembly is likely to cause more trouble because of the poor insulation of the porous cables. Invisible pores may be present in the insulation and allow the current to discharge through these pores into the conduit or ground, thereby weakening the current at the plug if a spark occurs in that unit. This installation also offers another advantage as cross fire

is practically eliminated. The current lost through poor instition will go to the ground and not take a path through anot porous lead into the wrong combustion chamber.

High-tension wire failures are generally due to one of the folling causes: mechanical stress, heat, chemical action, dielectric str

Mechanical Stress. A conductor of sufficient strength to w stand ordinary handling and vibration and possessing sufficiflexibility is secured by using copper stranded wire with an insuing material whose base is rubber. Of course, injuries result from handling high-tension wires should be taken into considerat Wires should be guarded to secure proper protection. Faults be avoided in eliminating unnecessary mechanical stresses are unported wires, tight wires, sharp bends, sharp edges, tightly clam brackets, or brackets with holes too large.

Heat. There is a wide variation of heat under the automo hood, and while these temperatures are seldom high enough endanger the rubber insulation, they are well above those c ducive to its normal life. When the motor is in operation, temperature seldom exceeds 175° F., but this temperature may to about 200° F. for a short period after the motor is stopped. C dation is also greatly increased by the additional heat.

Chemical Action. Gasoline is a very destructive agent wl in contact with rubber, although this action is not long, as vaporization is so rapid. Oil, however, does not evaporate so read and when once in contact, continues to act on the rubber, great weakening its insulating strength.

Dielectric Stress. The voltage of the high-tension curr passing through these leads has a wide range, depending upon width of the spark gap and the pressure in the cylinder at the ti the spark occurs. Various tests indicate the voltage to be betw 6000 and 18,000. The dielectric stress is generally sufficient cause a brush discharge on the surface of the insulating wall of high-tension lead at points where this lead comes in close proxin to grounded metal parts. This is especially true when wires contained in a grounded metal conduit. This brush discharge corona produces ozone and oxide of nitrogen, and these gases very detrimental to the insulation. For instance, the gases v start cracks on the surface, generally near the bend in the cal

Exhaustive investigations have shown that this cracking in the insulation is a phenomenon requiring the combination of several factors, namely, mechanical stress, electrification, and the presence of air. It is well known that ozone actively attacks rubber, and when the rubber is under mechanical stress, the products of reaction are pulled apart, forming small cracks which, when started, rapidly increase in size until the insulation is open to the cable.

Plain and Braided Cables. Braided covers over the insulation simply conceal this cracking; they do not prevent it. Braided covering also absorbs oil, thus producing an undesirable action as previously stated. The proper conductor must be of sufficient strength to prevent its breaking under ordinary conditions, and the insulation must be sufficiently durable to withstand mechanical, thermal, dielectric, and chemical conditions. Insulation will gradually fail as the porosity of the wall increases. This porosity may increase to a point where it will interfere with proper spark-plug functioning and even then the defect will not be visible.

Plain and braided cables formerly were extensively used, but a larger per cent of assemblies are now being equipped with plain cables. Braided cables are generally used where it is necessary to provide additional protection against mechanical injury; also in a few cases when the temperature is somewhat above 225° F., in which case the insulation softens and the cable is in danger of being seriously damaged at its pointed support. With the foregoing excep-

Magneto Mounting. As the magneto is timed exactly with the motor, it must be positively driven synchronously with it at a speed depending upon the number of cylinders. This is crankshaft speed on a four-cylinder and one and one-half times crankshaft speed on a six. It has become standard practice to a very large extent both here and abroad to mount the magneto on a "pad" or shelf attached to the crankcase and drive it from a special auxiliary shaft, usually also utilized for driving the water pump or other motor auxiliary. Variations from this are to be found in the Renault and a few other European as well as American cars, in which the magneto is mounted


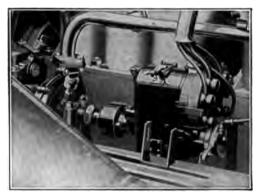


Fig. 112. Mounting of Magneto

at the forward end of the motor and driven by a cross-shaft and helical gears directly from the crankshaft of the motor. The only advantage of this is slightly greater accessibility. In any case, the magneto is not permanently fastened but is simply held on its support, against movement, by dowel pins in the base and a strap clamp tightened with a thumb nut, as shown in Fig. 112, which may be regarded as typical of American practice. As the efficiency of the magneto depends to a considerable extent on the very limited clearance between its armature and the pole pieces of the field, usually termed the armature tunnel, precautions are taken to avoid placing any stress on it that could tend to disturb this accurate alignment. The driving shaft is accordingly provided with a universal joint, the long familiar Oldham coupling being much used in this country for the purpose. On the Pierce-Arrow a leather disc universal drives the magneto and also cushions the armature.

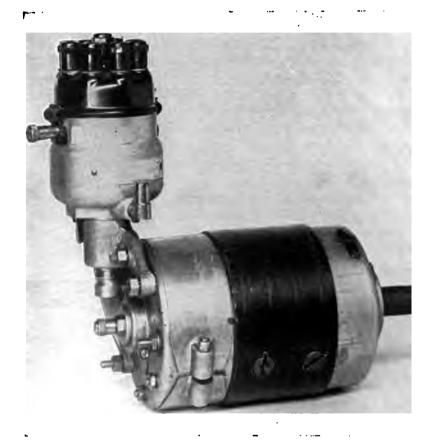



DELCO IGNITION GENERATOR USED ON COLE AND OLDSMOBILE EIGHT-CYLINDER CAR

Courtes, of Da Joe Engineering Laboratories Company, Daylon, Ohio

# ELECTRICAL EQUIPMENT FOR GASOLINE CARS

### PART III

# IGNITION—(Continued)

## MODERN BATTERY IGNITION SYSTEMS

Effect of Starting and Lighting Developments on Ignition. Prior to the advent of the electrical starting and lighting systems, the magneto had reached a degree of development that appeared to leave not the slightest doubt as to its representing the ultimate type of ignition current generator. With the installation of a direct-

current generator capable of supplying more than enough current for lighting and starting the car and charging a storage battery of high capacity. however, it appeared that there was a duplication of electrical apparatus for which there was no good economic reason. In other words, with such an ample and reliable source of current on the car as that presented by the charging generator



Fig. 113. Westinghouse Generator with Ignition Distributor

and storage battery, why continue the magneto? There is no sound reason why one electrical system should not combine all three functions of ignition, lighting, and starting, and this has been successfully carried out on the Cadillac for several years past, while the Reo and other makes have more recently followed suit.

Generator Design Follows Magneto Precedent. Several generator designs have been developed which resemble that of a magneto. In the Westinghouse generator, Fig. 113, and the Remy,

Fig. 114, their contact breakers are of the magneto type, as will plain from the Remy, Fig. 62, and the Westinghouse, Fig. 115 cite but two examples of a number. In the case of the Westinghouse the objection previously held against battery ignition—tha



Fig. 114. Remy Combination Lighting and Ignition Generator

required much more manipulation of the spark advance leve obtain efficient motor running—has been overcome by the provi of a centrifugally operated automatic advance device, Fig. 115, s lar in principle and results to the Eisemann and Herz devices, I

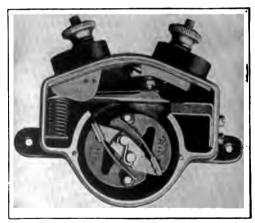


Fig. 115 Westinghouse Contact Breaker with Automatic Spark Advance

102 and 105, though differing from them in construction. distributors employed are practically identical with those used magnetos, but all resemblance disappears when the machine dismantled, Fig. 116, revealing a compact direct-current general



Fig. 116. Details Westinghouse Lighting and Ignition Generator

# TYPICAL ARRANGEMENTS

Westinghouse Ignition Unit. This is a combination of all the sentials of magnetic ignition, i.e., the interrupter, distributor, duction coil, and condenser, brought together in a compact unit lapted for mounting either on the lighting generator itself or rectly on the engine. It supersedes the type of ignition and shting generator previously described and which now will be found ily on cars of earlier models. As will be noted in Fig. 117, its imponents are the counterparts of the same essentials on the agneto, except that the interrupter cam has four lobes, so that no rether description is necessary.

Fig. 118 is a wiring diagram of the connections. The interrupter id condenser are located at the bottom of the housing with the



Fig. 117. Details of Westinghouse Ignition Unit Courtesy of Westinghouse Electric and Manufacturing Company, East Pittsburgh, Pennsylvania

duction coil above and the distributor at the top. To prevent an cessive amount of current passing through the ignition unit, a

"ballast resistor" is connected in series with it. This is a resistance unit which, in the various models, is combined either with the switch or with the fuse box, or may be mounted independently. In case this resistance unit should become inoperative for any reason, the car may be run by replacing it with a standard 5-ampere fuse cartridge. A fuse of larger capacity than this should not be used and the car should not be run any longer than absolutely necessary with

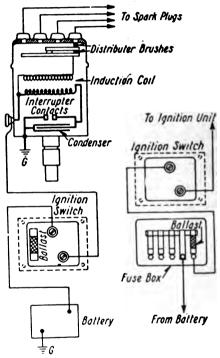


Fig. 118. Wiring Diagram for Vertical Ignition Unit. Left—with Ballast on Rear of Ignition Switch; Right—with Ballast in Fuse Box

the fuse in place, as the interrupter contacts would be badly burned. The working of the interrupter contacts may be inspected by loosening the set screw at the bottom of the housing and lifting the distributor an inch or so, Fig. 119.

**Atwater-Kent** System. The Atwater-Kent system is based on a "single spark" interrupter and was pioneer in making battery ignition successful on modern automobile before the advent of the perfected lighting generator, the current source usually being a dry-cell battery. It was considered an advantage in earlier years to produce a series of hightension sparks in the cylinder on the theory that, if the

first failed to explode the charge, it would be fired by the subsequent sparks. The fallacy of this long since became apparent and the reason therefor has been dwelt upon already. The Atwater-Kent interrupter is typical of devices of this class which have been developed since and as it is fitted on thousands of cars which come to the repair man's attention at one time or another, a detailed description of its working is given here.

Operation of "Unisparker". The ratchet A, Fig. 120, has as many notches as there are cylinders to be fired. It is mounted on the central vertical shaft of the device which also carries a distributor, and in this combined form is known as a "Unisparker". On four-cycle engines it is driven at half crankshaft speed, and at crankshaft speed on two-cycle engines (motor boats). The ratchet A engages the lifter B, and, as A rotates, its teeth or notches successively tend to draw B with them, against the tension of the spring C. In doing



Fig. 119. Westinghouse Ignition Unit with Interrupter Cover Raised Showing Interrupter Contacts Courtesy of Westinghouse Electric and Manufacturing Company, East Pittsburgh, Pennsylvania

so, the head of B strikes the swinging lever or "hammer" D, whose motion in both directions is limited as shown, and the hammer communicates the blow to the contact spring E, bringing the contact points together momentarily. E is a compound spring, the straight member of which carries the movable contact, while the stationary contact F is mounted opposite it. The second member of this compound spring is curved at its end to engage the straight member. Ordinarily the straight spring blade is held under the tension of the curved blade and the contact points are held apart.

When the curved blade is struck by the hammer D the points contact. The curved blade, however, is thrown over farther by the impact and its hook leaves the straight blade. Upon reaching the

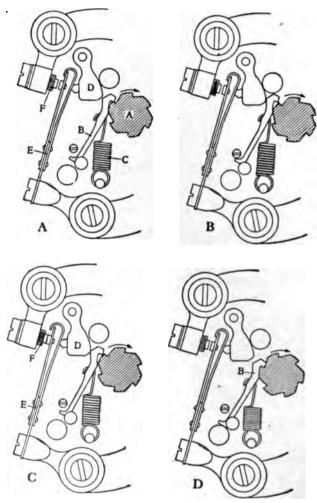


Fig. 120. Diagram Showing Operation of Atwater-Kent Interrupter

Courtesy of "The Horseless Age"

limit of its movement it flies back and strikes the end of the straight blade a blow causing a very sharp break of the circuit. This movement is so extremely rapid that it cannot be detected by the unaided eye, so that its working cannot be tested simply by watching the ion of the contacts as in the case of a magneto interrupter. and D, of Fig. 120, show the successive movements of the parts; a single phase. In A, a notch of the ratchet has engaged B drawing it against the tension of the spring C. In the second B, the hook is released. In C, the lifter is riding back over sunded portion of the ratchet and striking the hammer D, in turn pushes E for a brief instant against F. The return of the position shown in sketch D is so rapid that the eye carnot the movement of the parts D and E, which to all appearances a stationary.

djustment of the contact points is made by removing one of in washers from under the head of the contact screw F, and up should be .010 to .012 inch, never exceeding the latter.

e more accurate means of nining this distance are not ble, it may be gaged with a of manila wrapping paper should be perfectly smooth. the aid of a "mike" (micromsheet of paper of the proper ess can be selected. The conare of tungsten and as the g parts are all of glass-hard very accurately machined,



Fig. 121. Connecticut Interrupter



rs (

right. The primary of the coil is not grounded, insulated le being connected to the two binding posts of the interrupter, shown. The grounding of the secondary winding of the coil effected through the metal holding band and the bolts fastened the bed plate. A glass tube is employed to house the safety which is mounted under the cover of the coil.

Automatic Switch. The purpose of the automatic switch, 1 123, is to open the circuit in case the switch button has been left with the car stopped. The current passing with the contacts clos when the engine is idle, is much greater than when it is constar being interrupted by the rapid-fire action of the cam, but, unlik circuit-breaker, the device is not designed to act instantly upon passing of an overload current as this would prevent cranking motor. The device consists of a thermostatic arm regulated the adjustment screw at the top of the figure, an electromagne vibrator the armature of which carries a hammer, and the necess connections. Current enters at either the right- or left-hand sc at the bottom, according to whether the switch is closed at the end the sectors at the right or left of the figure (M or B on the swi cover plate), and flows through the heater tape on the arm of thermostat to the screw at the upper right in the figure. heater tape is a resistance that becomes warm upon the passage a certain amount of current for a short time and, with an incre in temperature, causes the arm of the thermostat to bend u it makes contact with the upper thermostatic arm. This p the windings of the magnet in circuit through the post just be the magnet coils and sets the vibrator in motion, causing hammer on the armature to strike the switch button and open Fig. 124 is a typical wiring diagram in connection with the light system, the automatic switch being combined with the light switch.

Remy System. The relation that the various essentials c battery-ignition system of the types here described bear to e other is made clear by glancing at the graphic wiring diagram the Remy system, Fig. 125. The starting switch shown at the has, of course, no connection with the ignition system but is inclu in the illustration because the current-supply wire for the latte connected to one terminal of the starting switch instead of be

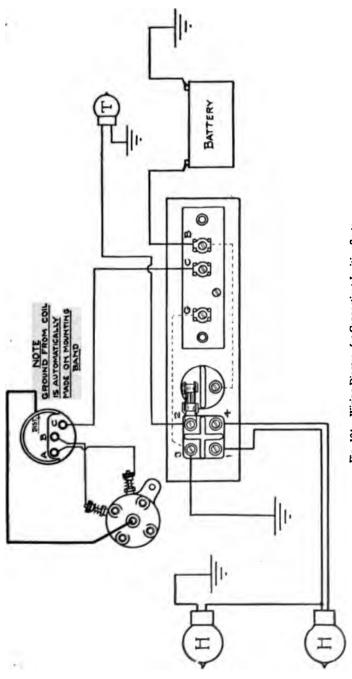


Fig. 124. Wiring Diagram for Connecticut Ignition System

right. The primary of the coil is not grounded, insulated lea being connected to the two binding posts of the interrupter, shown. The grounding of the secondary winding of the coil effected through the metal holding band and the bolts fastened the bed plate. A glass tube is employed to house the safety g which is mounted under the cover of the coil.

Automatic Switch. The purpose of the automatic switch, F. 123, is to open the circuit in case the switch button has been left with the car stopped. The current passing with the contacts close when the engine is idle, is much greater than when it is constant being interrupted by the rapid-fire action of the cam, but, unlike circuit-breaker, the device is not designed to act instantly upon t passing of an overload current as this would prevent cranking t motor. The device consists of a thermostatic arm regulated the adjustment screw at the top of the figure, an electromagne vibrator the armature of which carries a hammer, and the necessa connections. Current enters at either the right- or left-hand screen at the bottom, according to whether the switch is closed at the end the sectors at the right or left of the figure (M or B on the swit cover plate), and flows through the heater tape on the arm of t thermostat to the screw at the upper right in the figure. heater tape is a resistance that becomes warm upon the passage a certain amount of current for a short time and, with an increa in temperature, causes the arm of the thermostat to bend un it makes contact with the upper thermostatic arm. the windings of the magnet in circuit through the post just belo the magnet coils and sets the vibrator in motion, causing t hammer on the armature to strike the switch button and open Fig. 124 is a typical wiring diagram in connection with the lighti system, the automatic switch being combined with the lighti switch.

Remy System. The relation that the various essentials of battery-ignition system of the types here described bear to ea other is made clear by glancing at the graphic wiring diagram the Remy system, Fig. 125. The starting switch shown at the has, of course, no connection with the ignition system but is includ in the illustration because the current-supply wire for the latter connected to one terminal of the starting switch instead of bei

taken directly to the battery. This is done simply to save wire. The source of current supply is the storage, and, as is the case with all one-wire systems, one side of the battery is grounded, as shown. Similar ground connections, necessary to complete the circuit, will be noted at the various units of the system. The colors mentioned in connection with the various wires are those of their insulation, which serves to identify them.

Detecting Grounds. All current used by the ignition system passes through the ammeter, which thus serves as a method of detecting grounds. For example, if, with the engine idle and all lamps

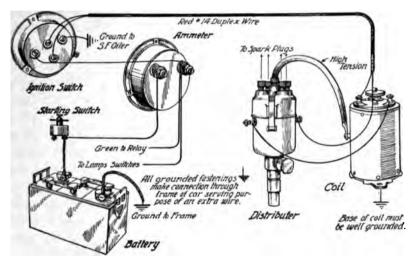


Fig. 125. Essentials of Battery Ignition System

turned off, the ammeter registers a discharge, it indicates a leak in the system. By disconnecting the wires leading to the lamps, relay, and ignition switch in turn, the particular part of the system in which the fault lies may be detected. If, for instance, the ammeter needle immediately drops back to zero upon disconnecting the lead to the ignition switch, it indicates that the leak is in some part of the ignition system; if it still indicates a discharge after disconnecting this lead, it shows that the leak is in one or the other of the two remaining parts of the system to which the wires in question lead, and it may be found by continuing the process of elimination further. Should the ammeter still show a discharge reading after disconnecting

L

all three of these wires, the trouble would lie either in the starting switch or in the cable connecting it with the battery. This could be proved by disconnecting the switch from the battery and running an independent lead from the battery to the ammeter, temporarily. There is always a possibility, of course, that the fault may lie in the ammeter itself. A current-measuring instrument is necessarily of delicate construction and is apt to suffer from the vibration and jolting. Before carrying out all the above tests, make certain that the ammeter needle has not become stuck.

Ignition Switch. From the ammeter, Fig. 125, the current passes to the ignition switch of the reversing type, that is, it serves to change the direction in which the current flows every time it is turned For the purposes of either ignition or lighting, it is immaterial in which direction the current flows, but the latter has an important bearing on the life of the expensive contact points in the interrupter. As has been explained previously, the passage of a current through contact points or across a gap tends to transfer the material of the positive electrode to the negative, resulting in the formation of a cone at the positive and a crater, or hollow, at the negative. the points have worn to this condition through long service, the contact is poor and uncertain, while the points are apt to stick, and to put them in good working order means filing away some of the platinum which is more costly than gold. The use of a reversing switch, which alternately makes the same point positive and negative. keeps both contacts in better condition for a greater length of time.

One side of the ignition switch is grounded on the oiler, through which the current passes to the frame to which the oiler or its support is attached. This particular connection is merely a matter of convenience and is only another instance of saving wire. The wiring diagram in question shows the installation of the Remy system on the Scripps-Booth four-cylinder chassis; on other machines, the ground connection will usually be found in some equally convenient point close to the switch. The two remaining connections from the ignition switch run to the coil and the interrupter, or contact breaker, respectively, and complete the primary circuit.

Interrupter and Distributor. The interrupter is enclosed in the same housing as the distributor, Fig. 125, and is directly below it. As with a magneto, the coil is grounded by attaching it to its pedestal

on the car, the plate shown serving as a ground connection for one side of both the condenser and the secondary windings of the coil. Consequently, but one connection for the primary circuit and one for the secondary circuit need be made from the coil to the interrupter.

By tracing the connections just described, it will be plain that when the contacts of the interrupter are closed, current flows from the battery through the primary of the coil. The revolving members of both the interrupter and the distributor are mounted on a vertical shaft driven by helical gearing from one of the half-time shafts of the engine. When the cam on this shaft opens the contact points

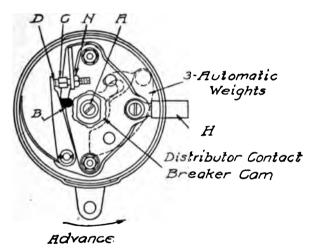


Fig. 126. Delco Magneto Type Interrupter

of the interrupter, the primary circuit is suddenly broken, and a high-tension current is induced in the secondary winding of the coil. As the revolving member of the distributor is timed to make contact with one of its stationary segments every time the contacts of the interrupter open, the secondary current is led to one of the spark plugs. The occurrence of the spark at the plug is practically simultaneous with the opening of the interrupter contacts.

Deko System. A magneto-type interrupter, substantially similar to that of the Connecticut system except that it is provided with an automatic-spark advance, is used, as shown in Fig. 126. The arm B carries the movable contact D and a fiber-striking lug which bears against the four-part cam and is lifted by its revo-

lution against the tension of the leaf spring held against the inner wall of the housing. The stationary contact is at C and is adjusted

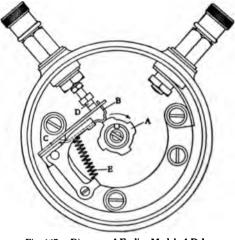


Fig. 127. Diagram of Earlier Model of Delco Interrupter

by means of the screw and locked in place by the nut N. These contacts should be so adjusted that when the fiber block on B is on top of one of the lobes of the cam, the contacts should open sufficiently to allow the gage on the distributor wrench, provided with the system, to close the gap. As in the Connecticut interrupter, the contacts normally remain closed, being opened mo-

mentarily by the cam, which has as many projections as there are cylinders to be fired. This is the later model of Delco interrupter (1916).

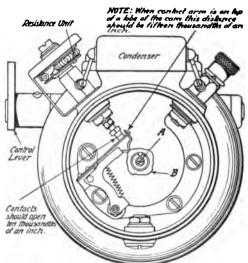


Fig. 128. Delco Timer with Resistance Unit

Earlier Model Interrupter. In an earlier model which will be found on a great many cars, the contacts are normally held open, Fig. 127. The movable contact is carried on a straight spring blade to which is attached a bent spring blade B held against the cam by the spring E. The latter also places the spring C under slight tension and holds the movable contact away from the stationary contact D. When the projection of the

cam strikes the raised portion of B, it deflects the latter and allows the contact points to come together. As it passes the bump on B, E

draws B back sharply, its end strikes C, and the contacts are suddenly opened, the duration of the contact varying with the speed of the engine.

Timer with Resistance Unit. Mention has been made of the fact that the contacts of the interrupter in the battery system of ignition are normally closed, just as they are in the magneto interrupter, only the circuit being opened at this point at the time of ignition. Owing to the rapidity of their action and the extremely short interval



Fig. 129. Four-Cylinder Battery Ignition Unit on Dodge Car (1917)—Coil at Left Courtesy of Dayton Engineering Laboratories Company, Dayton, Ohio

between contacts in the interrupter of a high-speed engine, this calls for a very small current consumption. Should the ignition switch be left closed when leaving the car, however, the timer cam is just as likely to stop in the closed position as in the open, and this small steady discharge will result in exhausting the storage battery. To prevent this waste of current and possible damage to the contacts and coil, a later type of timer has been provided with a resistance unit. This is shown on the left-hand terminal of the timer, Fig. 128, which illustrates the type used on the Cole, among others. The unit

consists of a small open coil of high-resistance wire wound upon a porcelain spool mounted on the head of the terminal.

All the current passing through the timer must first pass through this resistance winding, but, owing to the extremely short period it continues between interruptions due to the opening of the contact points, the resistance wire remains cool. When the switch has been left on with the engine idle, however, the current is then

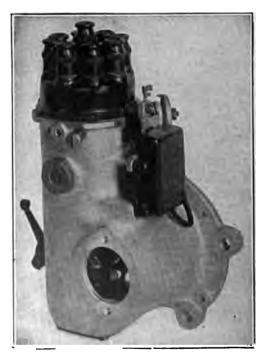


Fig. 130. Eight-Cylinder Distributor and Drive (Delco) as Used on 1917 Cadillac Courtery of Daylon Empiricaries Laboratories Company, Daylon, Ohio

continuous and of greater value, and it brings the resistance wire to a red heat in a comparatively short time. At this temperature, its resistance increases so greatly that it permits very little current to pass. It will also be noted that the condenser is mounted on the timer in this case.

As the spark occurs at the instant the timer contacts are opened, the ignition timing may be altered by moving cam B with relation to its shaft, which is done by loosening screw A. Turning the cam in a clockwise direction, or to the right, advances the time of ignition, and to the left, or

counter-clockwise, retards it. The distributor used in connection with this timer is provided with automatic spark advance, as well as with the usual manual control on the steering wheel. Typical distributors for five-, eight-, and twelve-cylinder installations are shown in Figs. 129, 130, and 131, respectively, the first being found in the 1917 Dodge, the second in the 1917 Cadillac, and the third in the 1917 Haynes. In Fig. 132 is illustrated a dual-type timer

having independent interrupter contacts for both the battery and the magneto. Apart from this feature, its construction is the same. This type is employed on the Oakland.

New Bosch Battery Magneto System. The American Bosch Magneto Company, Springfield, Massachusetts, has recently announced a new addition to the Bosch family, it being in the form of a battery ignition system built along the same standard of quality



Fig. 131. Twelve-Cylinder Delco Distributor on Haynes (1917)
Courtesy of Dayton Engineering Laboratories Company, Dayton, Ohio

and design that has been prevalent in this organization from its very beginning. This instrument has been in the course of development for the past four years and it is now placed on the market to fulfill the demand of manufacturers in the automotive industries that wish a fine-appearing and excellently formed apparatus.

General Description. The battery system as manufactured by the Bosch Company consists of a timer-distributor and B coil. The timer-distributor can be furnished in two types, "T" and "T M." Type "T" system, Fig. 133, is known as the Bosch Compensating Battery Ignition System and includes a governor that operates a cam so that in accordance with the characteristics and the speed of the engine the exact corresponding "advance" is given the ignition spark. thus making it possible to secure the very best performance from an ignition system that is not controlled by manual means. The type "T M" system is identical in general with the type "T," but differs

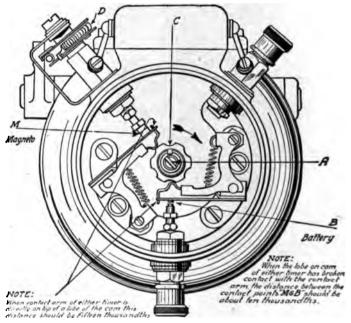


Fig. 132. Delco Dual Type Timer with Two Sets of Contacts

in that the compensating feature is omitted, the spark timing being controlled manually.

Details of Construction. Each one of these battery ignition systems consists of main housing, interrupter cup, compensating feature, distributor, and ignition coil. The main housing or shell of the timer-distributor unit is made of gray iron and is constructed of sufficient depth to accommodate the governor of the compensating mechanism. The shell for the type "T M" system naturally does not need to be as deep. Ventilation is taken care of in these breaker chambers so that the formation of nitric acid gas which is always present when

sparks occur in air-tight chambers will not cause any damage. This ventilation is accomplished through the spring clip rivets which are tubular. The advance lever is a one-piece forging so constructed



Fig. 133. Type "T" Breaker-Distributor Unit

that it can be clamped in any position on the unit. The timing of the engine can thereby be very easily changed by loosening the screw on this arm and turning the ignition unit in the desired direction. This naturally changes the relation of the breaker to the cam. Both

the manual and the compensating form of regulation can be used if This combination is sometimes advantageous when it is so desired. conditions such as a hot engine are encountered. The lubrication of the bearing in the compensating system is accomplished by means of the splash system. An oil cup is in the base of the main housing and permits the lubrication to be fed through the proper level into a sump within the shell. When the timer shaft with the governor mounted thereon starts to rotate, the governor ring dips into the oil and thoroughly sprays all the parts. The shaft bearings are lubricated by capillary action through a felt wick leading from the sump to the shaft. The manual system is lubricated in the original method which is generally the wick system. Although the lubrication of these parts is more or less automatic, it is well to frequently examine and lubricate them, for lack of oil will cause the compensating mechanism to stick with the consequent sluggish automatic advance

Interrupter. The interrupter, or breaker point, is assembled in a cup which also accommodates the condenser, Fig. 134. The entire

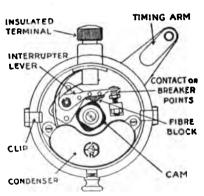


Fig. 134. Breaker and Condenser Unit

unit can easily be removed for inspection without disturbing any of the component parts of the electrical connection. low tension terminal that connects the primary is also carried by the cup itself. The interrupter cup is seated on a ledge so as to secure and maintain the interrupter lever in proper vertical relation to the cam. A thumb nut secures the cup in position and provides handles for lifting the

cup out for inspection. When this unit is assembled, the cup slightly projects above the main housing and thus secures the proper location of the distributor cap which fits over it. The interrupter lever is made from one-piece steel casting, copper and nickel-plated. Its construction is such that it provides a very light but strong lever and the spring tension required for its operation need be very slight. This combination provides not only an exceedingly fast lever but one that causes little wear on the fiber block upon the contact points.

The condenser is of the dry-wound type, it being totally enclosed and sealed in a moisture-proof metal housing. Before being shipped each condenser is tested for breakdown voltage at 1,000 volts for a period of one minute. Owing to the large capacity of this condenser, oxidation, pitting, and burning of the contact points is reduced to a minimum and the voltage of the secondary winding is greatly increased. It is an advantage in having the condenser enclosed completely to keep out moisture as previously stated, for that is the cause of most breakdowns in condensers. If the condenser is removed for any purpose, be sure when putting it back, it has good connection.

Compensating Feature. The governor or compensator is of the "tilting ring" type and is carried on the timer shaft just below the interrupter cam. The range of the ignition advance is determined by an advance control stud integral with the governor. As the timer shaft rotates, the resultant tilting movement of the governor ring, due to centrifugal force, advances the interrupter cam, which is assembled to the timer shaft in the form of a sleeve, by direct engage-

ment of a stud that projects into a slot provided by this sleeve. The total throw of the governor ring, Fig. 135, is readily adjustable by means of stop pins. To provide for the proper movement of the cam at different engine speeds, the tilting of the ring is opposed by an adjustable, spirally wound spring that is located in a recess in the bearing hub of the ring. This spring is not only adjustable in relation to the ring for varying the initial tension of the spring, thereby controlling the speed by which the advance mechanism is operated, but various springs of different tension may be provided so



Fig. 135. Bosch Compensating Governor

that the most suitable advance may be selected and assembled to the unit according to the characteristics of the engine. For the same general shape of characteristic curve or the same percentage of movement at advance speeds a total advance from zero to 60 degrees, and even more when measured on the flywheel, may be secured. In order to demonstrate the possibility of adjusting the automatic advance on the compensating "T" type to suit various engines, typical actual test curves are reproduced with the total advance expressed in percentage. These curves show clearly the advance may be according to the straight line or it may be curving considerably. In other words, the advance may be proportional to the increase in engine speed, or it may be variable for change in engine speed in the range of a certain desired movement. If desired, the governor may be adjusted so that the advance will start at a speed as low as 300 r.p.m. of the engine. Or it may be set at any other desired speed. This feature is quite an improvement in ignition systems in that the early type automatic advance systems simply advanced the ignition according to the speed of the engine. This was rather unsatisfactory because the proper advance ignition is not always dependent upon engine speed.

Distributor. The distributor rotor is mounted on a projection of the cam proper and rotates with it. A skirt is provided on the bottom of the rotor to protect the breaker mechanism. The rotor electrode is fastened by a screw that is recessed in the top of the rotor. The distributor cap is mounted on the main housing and is held in alignment by the projection of the interrupter cup. A moulded tongue fits in a slight recess of the housing so it cannot be incorrectly assembled. The high tension towers are of sufficient height to prevent short circuits due to water and foreign substances collecting on the distributor. A distinctive feature of the high-tension lead carbon brush is that it can neither stick nor drop out of the distributor when the distributor is removed.

The high tension cable connections are unusually simple and can easily be attached to the towers. It is only necessary to cut the cable off flush and push it into the towers of the distributor cap. This simple method is possible on account of the small patented clip that was previously snapped into a circular groove turned into the lower end of the distributor insert. A sharply pointed ear in the bottom of this clip makes electrical connections with the strands of the cable as it is pushed home in the tower. The small prongs projecting from the side of the clip hold these parts together firmly so that when the cable is removed the clip remains affixed to the end of the wire.

on Coil. The ignition coil is also of the dry assembly type, uction permits the easy accessibility and simplifies the of the entire unit, Fig. 136. It can be mounted at the rear trument board or on the engine side of the dash. It is niver the low voltage current taken from the storage bathigh voltage current of sufficient strength so it will jump plug gap. The coil can also be mounted on a bracket on distributor unit or upon the engine. The spark coil is , and is constructed so that the center bolt that holds the ; together can be passed through its center without in any rbing the core. This construction of the coil makes it



Fig. 136. Coil Assembly

for inspection at any time, and for the renewal of the l or resistance units should they suffer from damage or come broken.

nagnetic circuit is of a little different design in that the ad plates establish a shield for the magnetic circuit against ning effect of neighboring iron or steel. It is claimed that ial increases the spark energy. The ballast coil or resistis connected in a series with the primary winding. It is for the purpose of protecting the coil from burning out in nition switch is accidentally left on while the engine is not ad the contact points closed. It also assists in the producniform spark at various engine speeds.



ELECTRICAL EQUIPMENT

194

### TESTING, ADJUSTMENT, AND MAINTENANCE

Trouble Nearly Eliminated by Efficient Devices. With modern equipment, trouble from electrical sources has been decreased to an almost irreducible minimum and with a knowledge of the rudiments plus consistent observance of a few simple rules, these troubles can usually be remedied without calling in outside assistance. Causes of failure are the most important thing to remember as, with these in mind, it is far easier to trace the trouble logically than where the usual aimless hunt is undertaken on the chance of striking the cause. It must also be borne in mind that all causes of motor stoppage are not electrical. A dry gasoline tank, a plugged-up gasoline feed line or a choked carbureter, failure of a gasoline pressure-feed system, or a stopped-up air vent in a gravity-feed gasoline tank will have the same effect, though one or all of them have not infrequently been attributed to the ignition system.

Causes of Failure. Failures may be generally classed under three heads: short circuits or grounds; failure of current supply; and failure of ignition devices, such as contact breakers, distributors, vibrators, coils, spark plugs, wiring, connections, condensers, etc.

Short-Circuits. When a motor that has previously been running normally suddenly stops dead, the indication is almost invariably that of a short-circuit or ground. The difference between the two is that a short circuit takes place between two wires or other parts of the system, while a ground is the contact of a chafed wire or other exposed part with some portion of the metal foundation of the car. such as the frame or motor. The effect is the same in either case in that the current takes a shorter path and does not reach the spark plugs. Either may occur in the low- or high-tension wiring, i.e., between the contact breaker and the coil or the battery and the coil; or between the secondary side of the coil and distributor. Owing to the high voltage of the latter, grounding is more apt to result there either from a chafed wire or from a frayed end coming in contact with the motor or other metal. Failure from this cause can frequently be detected by sparking at the point of breakdown. An "open circuit" in one of the main feed cables, such as that connecting the magneto to the primary of the coil in a dual system, or the secondary of the coil to the distributor, or the battery cable in a battery system will naturally have the same effect. The cause

is usually a loose connection; sometimes, though rarely, a broken wire. If the connection has not parted entirely, irregular firing will result.

Failure of Current Supply. Failure of current supply will usually result in erratic running as the current weakens until it reaches a point where it is no longer adequate and the motor stops. But the symptoms in this case are the same as in gradual failure of the fuel supply, either through a choked carbureter nozzle, partially obstructed feed line, stopped air vent, lack of pressure, or the emptying of the tank. The motor will run by fits and starts with irregular missing at different cylinders. Defection of the contact breaker or distributor may also manifest itself either by similar erratic operation or by sudden stopping.

Weak Magnets. When the engine fires regularly on the battery but will not do so on the magneto except above a certain speed, it indicates that the magnets are weak and need remagnetizing. Heat and vibration weaken the magnets, so that on some cars it is necessary to overhaul the magneto every five or six thousand miles, whereas, on others, the magnetism shows no appreciable falling off after two or three seasons' use. With a new or recently overhauled magneto it should be easy to start on the magneto by spinning (by hand), but this is not conclusive as some engines will never start on the magneto.

Testing. Inspection of Wiring. Examination of the wiring and other parts of the system will usually suffice to reveal short circuits or grounds, or by making emergency connection with extra wire, proper operation through the latter indicating a failure of the parts of the wiring system thus replaced. Extra wire should always be carried on the car for this purpose. With the dual type of ignition system so generally employed, see that the zinc-containing case or the protruding terminals of dry cells are not allowed to come into contact with the metal battery box as this will cause a ground that is difficult to locate. The best preventive is a small wood container to insulate these cells from contact with any metal. Water falling on the high-tension cables will cause serious leaks that will not show in the form of sparks. Above all, every part of the system must be kept dry; sufficient precautions are frequently omitted when washing the car.

### TESTING, ADJUSTMENT, AND MAINTENANCE

Trouble Nearly Eliminated by Efficient Devices. With modern equipment, trouble from electrical sources has been decreased to an almost irreducible minimum and with a knowledge of the rudiments plus consistent observance of a few simple rules, these troubles can usually be remedied without calling in outside assistance. Causes of failure are the most important thing to remember as, with these in mind, it is far easier to trace the trouble logically than where the usual aimless hunt is undertaken on the chance of striking the cause. It must also be borne in mind that all causes of motor stoppage are not electrical. A dry gasoline tank, a plugged-up gasoline feed line or a choked carbureter, failure of a gasoline pressure-feed system, or a stopped-up air vent in a gravity-feed gasoline tank will have the same effect, though one or all of them have not infrequently been attributed to the ignition system.

Causes of Failure. Failures may be generally classed under three heads: short circuits or grounds; failure of current supply; and failure of ignition devices, such as contact breakers, distributors, vibrators, coils, spark plugs, wiring, connections, condensers, etc.

Short-Circuits. When a motor that has previously been running normally suddenly stops dead, the indication is almost invariably that of a short-circuit or ground. The difference between the two is that a short circuit takes place between two wires or other parts of the system, while a ground is the contact of a chafed wire or other exposed part with some portion of the metal foundation of the car, such as the frame or motor. The effect is the same in either case in that the current takes a shorter path and does not reach the spark plugs. Either may occur in the low- or high-tension wiring, i.e., between the contact breaker and the coil or the battery and the coil; or between the secondary side of the coil and distributor. Owing to the high voltage of the latter, grounding is more apt to result there either from a chafed wire or from a frayed end coming in contact with the motor or other metal. Failure from this cause can frequently be detected by sparking at the point of breakdown. An "open circuit" in one of the main feed cables, such as that connecting the magneto to the primary of the coil in a dual system, or the secondary of the coil to the distributor, or the battery cable in a battery system will naturally have the same effect. The cause

as every other part of the system will respond to the usual tests.

Remember Effect of Compression on Spark. The effect of compression on the spark must also be borne in mind, as an apparently efficient spark with the plug out of the cylinder is not equally effective when subjected to the compression. Partial failure of the current supply is the cause in this case, due to weak dry cells or an almost wholly discharged storage battery causing a drop in the voltage. Or it may result from spark plug points that have been burned away until the gap is too great,  $\frac{1}{32}$  inch being the maximum distance recommended.

Leakage at Distributor. Leakage may occasionally occur at the distributor due to the use of an excessive amount of lubricating oil which picks up carbon dust, the latter being carried around by the revolving arm until it forms a path for the high-tension current.

Spark Plugs. A broken spark plug porcelain or an internal short circuit of the plug, neither of which may be evidenced externally, will cause missing at that cylinder.

Erratic firing and a very perceptible loss of power will result from the gaps of the spark plugs being too large. With the powerful current supplied by a storage battery or by the modern magneto this takes place by the burning away of the points of the electrodes in a comparatively short time, it being nothing unusual for the \(\frac{1}{32}\)-inch gap to increase to almost \(\frac{1}{3}\) inch in a few weeks' running. This is particularly the case with the cheaper plugs which have iron-wire electrodes; they may be adjusted with the pliers, however, until there is no longer sufficient electrode left to adjust.

Loss of power will also be occasioned by a plug that is not tight in the cylinder or where the plug itself is not tight internally. Squirt a few drops of oil around the base of the plug on the cylinder and also on the porcelain of the plug. When the engine is running bubbles will form at these points: if the plug itself is at fault, a quarter-turn of the nut holding the porcelain in place will usually seat it on the gasket and overcome any leakage at that point; in case of leakage around the thread of the plug, a new asbestos gasket under it or a slight tightening of the plug itself where of the iron-pipe thread class will remedy the trouble. Cleaning at intervals with a

stiff brush and gasoline will prevent short-circuiting through an accumulation of carbon on the porcelain and walls of the shell.

Sparking at Safety Gap. In all magnetos of the true hightension type, the safety gap is incorporated in the magneto itself: in dual-ignition systems it is in the coil, as the latter must be protected from the battery current as well as from that of the magneto. Sparking at the safety gap is an indication that there is an opening in the circuit greater than the resistance of the secondary winding of the coil, and unless the spark bridged the safety gap, the insulation of the high-tension winding would be punctured. opening may be a spark plug whose points are too far apart or a connection that has dropped off either at the plug or at the coil. Owing to its high voltage the current will jump any gap smaller than that of the safety gap with no perceptible difference in the firing, so that loose connections on the high-tension side seldom cause trouble until they actually separate. A piece of metal accidentally falling on it or an accumulation of any conducting material such as dirt or moisture will short-circuit the secondary of the coil through the safety gap and no current will reach the plugs. terminals in which one or more of the strands of the flexible wire protrude and touch adjacent objects are sometimes responsible for a similar result; the remedy is to wind with friction tape.

Breakdown of Magneto. On cars employing a true high-tension type of magneto, the battery system is entirely independent, as a rule, so that a fault in one never involves the other. Where failure of the magneto is not due to faulty operation of the interrupter, it may be inspected with the aid of the test lamp described in connection with starting and lighting systems. Trace the various circuits of the magneto in question; apply the points to the opposite sides of the condenser. The lamp should not light; if it does, the condenser has broken down and must be replaced. Test the primary and secondary windings of the magneto in the same way; the lamp should light in each case; if it does not, there is a break in that particular winding and a new armature will be required. In the case of the dual-type magneto there is only one winding on the armature, and many of the older makes (1910 or earlier) have no conden-Many of these older magnetos in the cheaper grades are fitted with plain bearings and the wear of the latter may allow the armsture to bind against the pole pieces, or lack of oil may cause the shaft to bind in its bearings.

When a magneto is taken apart for any reason it must always be assembled with the magnets in the same relative position as formerly, otherwise their polarity will be reversed and the magneto will be inoperative. The magnets must never be left off the machine, even temporarily, without placing a bar of iron or steel across their poles to serve as an armature or "keeper"; unless this is done, they will lose their magnetism rapidly. Remagnetizing the magnets of a machine that has become weakened through long use is a simple

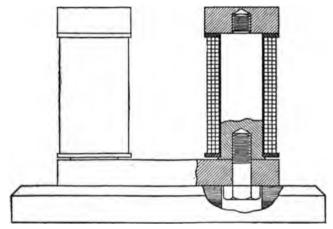


Fig. 140. Design for Magnet Recharger Courtesy of "The Horseless Age"

process and small electromagnets for this purpose are now to be had for garage use. They will operate, of course, only on direct current.

Remagnetizing. As misfiring at low speeds may be due to causes other than weak magnets on the magneto, the strength of the latter should be tested before deciding that it is necessary to remagnetize them. With the engine running, unclip one of the spark plug leads and hold it close to the terminal. If the magneto is developing a powerful current, it will jump a gap of  $\frac{1}{2}$  inch or more; should it not produce a spark at least  $\frac{1}{4}$  inch long it needs remagnetizing. In recharging the magnets their original polarity must be preserved, as otherwise it will be necessary to shift their locations

in reassembling them. Accordingly, it is important that unlike poles of the permanent magnets and of the electromagnet be brought together; i.e., the north pole of the permanent magnet to the south pole of the recharging magnet and vice versa. To insure this, the current should be turned into the recharging magnet and the other magnet held freely a short distance from its poles. As unlike poles attract and like poles repel, the magnet will find its own proper position, if allowed to do so. If forcibly held against the poles of the recharging magnet regardless of polarity, the strength of the electromagnet is so much greater than that of the weakened permanent magnets that it will reverse their polarity.

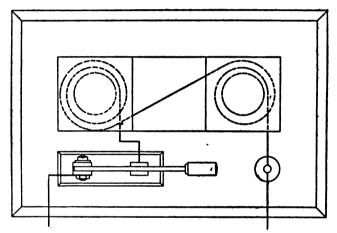


Fig. 141. Diagram of Connections of Magnet Recharger Courtesy of "The Horseless Age"

In recharging, set the magnet on top of the charger after its polarity has been determined and rock the magnet back and forth on its pole edges a number of times; then lay it on its side with its poles away from you and, extending just beyond the far edges of the recharging magnet poles, apply a keeper to the magnet poles, switch off the current and withdraw the magnet sideways from the recharger. The keeper should remain in place until the magnets are reassembled on the magneto.

Magnet Recharger. Electromagnets designed for this purpose and built specially for garage use are now on the market, or one may be made with little trouble. The following design, Fig. 140,

is from The Horseless Age. The cores of the magnet are made of soft bar steel 1 inch in diameter and 3 inches long. They are secured to a base measuring  $5\frac{1}{4}$  by  $1\frac{1}{2}$  by  $\frac{5}{8}$  inches and are provided with pole pieces measuring  $1\frac{3}{4}$  by  $1\frac{3}{4}$  by  $\frac{5}{8}$  inches. All contacting surfaces should be absolutely flat and square so that there will be good metallic contact over the entire surfaces. Before the wire is wound on them, the magnets must be insulated. A spool may be formed by placing a fiber ring at each end of the magnet cores, and a better job may be made by turning down a  $1\frac{1}{8}$ -inch bar, leaving a thin collar of the original diameter at one end. This will support the fiber ring at that end while the other rests against the pole piece. The core between the fiber rings is then insulated by wrapping with several layers of muslin which is given a coat of shellac in alcohol and allowed to dry.

The winding to be applied depends on the voltage to be used. For a 6-volt battery, wind on three layers of No. 12 double cottoncovered magnet wire; for a 110-volt circuit, eight layers of No. 22 double cotton-covered magnet wire. The ends or leads of the wire are then taped and the outer layers of the coils shellaced to make the exposed cotton insulation more enduring. Connect the coils together so that if the current flows through one right-handed, it flows through the other left-handed, when looked at from above. Fig. 141. Mount the completed magnet on a wooden base large enough to carry a single-pole switch and a binding post. battery or lighting mains are connected to the binding post and the free terminal of the switch; the other terminal of the switch being connected to one end of the magnet coil and the other terminal of the latter to the binding post. Where designed for 110-volt current, it will be preferable to use a double-pole switch mounted on a porcelain base with two screw-plug fuses; 10-ampere fuse plugs being screwed into the sockets. The free ends of the coil are then connected directly to the terminals of the switch at the plugs and the source of current is connected to the other end of the switch. windings specified will heat up quickly, when connected to current sources of the voltages given, so that the switch should never be left closed more than a few minutes at a time.

When a charger is not available, the magnets may be recharged by wrapping wire around each end of the magnet. Being flexible and well insulated, lamp cord may be used and must be wound directly on the magnets. The bared ends of the cord should be twisted together so that the two wires form a single conductor. Wrap on about fifty turns and connect this winding to the main switch through a 10-ampere fuse. Particular care must be exercised to make the connections so that the magnets will not have their polarity reversed. A current of high value will flow through the winding during the brief time that it will take to blow the fuse. This method is rather crude, but it will be found satisfactory when a recharger is not available. However, the magnet recharger usually will be found preferable, particularly where there is any doubt as to the polarity.

Care of Ford Magneto. Dirt will sometimes accumulate under the collector brush or on the collector ring and reduce the current



Fig. 142. Hoyt Magnetometer for Ford Cars

output. As a guide to the operation of the Ford magneto, the Hoyt magnetometer, Fig. 142, has been devised. The calibration of this is purely arbitrary, the letters representing Poor, Medium, Good, and Excellent. Probably end play in the bearings is the most frequent cause of poor operation of the Ford magneto. This is due to wear of the main crankshaft bearings which permits the magnets to rotate at a greater distance from the coils than originally intended.

Taking up this play or replacing the bearings is naturally the remedy. Small particles of metal may sometimes lodge beneath the ribbon terminals of the coils, or the latter may become so thoroughly impregnated with metallic dust as to ground them, making them inoperative. Cleaning and renewal of the oil in the magneto housing will remedy this. To test the coils, four or six dry cells connected in series should be used. Attach one terminal of the battery to the collector brush or insulated plug at the top of the magneto and the other terminal to the connection where the last coil is grounded to the supporting plate. Then with a piece of soft iron touch the iron core of each coil to see it if is strongly magnetized. It should take some effort to pull the iron away. A coil that does not respond properly is probably grounded. Weak magnets are occasionally

found to be the trouble, but this is comparatively rare, as well-made permanent magnets are usually good for years of service. When they are found, the best remedy is to replace the entire set, particularly as the cost is low.

#### SUMMARY OF IGNITION INSTRUCTIONS

- Q. How many different systems of ignition are in use on the automobile today?
- A. Generally speaking, only one, known as the high-tension system. The low-tension system used in earlier days has been obsolete for a number of years. The single classification, however, may be subdivided into several others which are known by their distinguishing features, the first being determined by the source of current supply, as magneto- and battery-ignition systems. These two classes may be divided further according to the type of magneto employed, such as the duplex, the dual, and the double-spark types. All battery systems are fundamentally the same, only differing in the type of circuit breaker and distributor employed, the mounting of the latter, i.e., whether direct driven from the engine or combined with the lighting generator, and in the type of controlling switches and auxiliary devices.

#### DIFFERENT SYSTEMS

- Q. Why is the system generally used termed "high-tension" system?
- A. Because the current must be passed through a step-up transformer or coil to impress upon it a sufficiently high voltage to cause it to jump the air gap in the spark plug.

#### Low-Tension System

- Q. · Is the old low-tension make-and-break system entirely obsolete?
- A. Since about 1909, it has not been used on the automobile but is still generally employed on small two-cycle marine engines and on stationary engines.
  - Q. Why is it not suitable for automobile engines?
- A. It will not work satisfactorily at high speeds since its time factor is limited by mechanical reasons, i.e., the inertia of the movable electrodes of the low-tension spark plugs, whereas, in the high-

tension system, only electrical lag has to be compensated for. It requires a skilled mechanic to time the spark plugs properly and they will not stay in adjustment for very long.

- Q. What is the chief attention it needs as employed on marine and stationary engines today?
- A. Keeping the electrodes clean; the current burns a film of oxide on the contacts and this insulates them to an extent where the low-voltage current will not pass. The timing of the plugs also needs regular attention as the hammering action of their operation tends to throw them out of adjustment. Considerable current is required for the efficient operation of the low-tension plugs, so that where used with batteries as on the motor boat, the cells frequently become exhausted in a comparatively short time.
- Q. How can the low-tension plugs be adjusted to give them the proper timing?
- A. Turn the engine over slowly by hand and watch the action of the plug. Its contacts should come together when the piston is three-fourths of the way up on the compression stroke; they should snap apart to cause the spark, the advance lever being in the retarded position, when the piston is at upper dead center. Provision is usually made for increasing or decreasing the length of the rod that operates the plug. If the spark is occurring too late, causing a falling off in the power, shorten the rod sufficiently by the adjustment to give the timing suggested above and lock tightly; if too early, lengthen it just enough to overcome any hammering that this would cause.
- Q. Why should the plug close the circuit so long before the piston reaches upper center?
- A. To give the coil sufficient time to "build up", i.e., for its core to become "saturated", or thoroughly magnetized; as the efficiency of the spark produced depends upon this.
  - Q. How does the coil of a low-tension system act?
- A. It is a single winding of coarse wire on a very heavy core of fine iron wires, i.e., a coil having a high self-inductance. When the circuit has been closed a sufficient length of time to permit this core to become saturated and is then suddenly broken, the current utilized to magnetize the core is redelivered to the coil and causes an rc at the plug as its contacts separate. The current producing this

arc is of much greater volume and at considerably higher voltage than could be obtained by making and breaking the battery circuit without a coil in it.

#### O. Does the coil ever need attention?

A. Only to see that its connections are clean and tight and that it is kept dry; owing to the solidity of its construction, failure of the coil itself is almost unknown. Test by holding one terminal of a three-cell or four-cell dry battery on one binding post and wiping the other with the wire from the other side of the battery circuit; a bright flash should result. If it does not, see if the wire has broken near one of the binding posts as this may result from vibration.

## Q. Is this the only low-tension system used?

A. No. Several makes of magnetic plugs have been used in connection with low-tension systems. Each plug is a solenoid the plunger of which makes and breaks the contact electrically. No mechanism is necessary to operate the plug but a timer must be used in the circuit to close the latter slightly in advance of the time for the spark to occur. This timer is the same as that used in the primary circuit of high-tension systems employing vibrator coils, as on the Ford.

### Q. What difficulty is usually encountered with magnetic plugs?

A. They seldom withstand the heat of the engine for any great length of time, so that the insulation fails. Apart from this the troubles encountered are the same as with any other system using movable contacts, i.e., dirt on the contact points, failure to make contact, broken connections, weak battery, etc.

#### **High-Tension** System

### Q. Of what does a high-tension system consist?

A. The essential parts of a high-tension ignition system are: (1) a source of current, such as a dry battery, the storage battery of the lighting and starting system, the direct-current generator of the latter, or a magneto; (2) a step-up transformer or induction coil, the primary winding of which is in circuit with the source of current supply; (3) a contact breaker or interrupter to open this circuit periodically, i.e., once every other revolution for each cylinder of a four-cycle engine; (4) a distributor in circuit with the secondary winding of the coil and provided with as many contacts as there are

۱

cylinders; (5) a spark plug for each cylinder; (6) primary and se ondary cables for the respective connections, and a controlling switch to open and close the supply circuit or to change from or supply circuit to another, where both a battery and a magneto at employed.

### Q. How do these essentials vary in different systems?

A. Where a battery is depended upon for the current supply the interrupter and the distributor are usually combined in a independent device which is driven from the camshaft of the engine

In the case of a magneto, both the interrupter and the ditributor are integral with it. This does not apply to the Formagneto which has a separate low-tension timer and uses no ditributor, as there is a vibrating coil for each cylinder.

In what are commonly known as modern battery systems, the timer and distributer may be either mounted separately, as first mentioned, or combined with the lighting generator.

#### CURRENT SUPPLY AND APPLICATION

#### Magnetos

### Q. How many types of magnetos are there in general use?

A. Two general classes, the low-tension and the high-tension and various special types, such as the dual, the double-spark, the duplex, and the inductor magnetos.

# Q. What is the difference between low-tension and the high tension magnetos?


A. The low-tension magneto has only a single winding on it armature the current being generated at low voltage and tranformed by passing through an independent coil, whereas the high tension magneto generates the current in one winding and steps in up through another, both on the same armature.


## Q. What is a dual magneto and why is it so called?

A. It is a low-tension type, the interrupter and distributor which are also employed in connection with a battery for starting It is so called because these essentials are common to both the magneto and the battery sides of the system.

## Q. What is a double-spark magneto?

 A. One provided with two distributors designed to product two sparks simultaneously at two different plugs in the same cylinder.

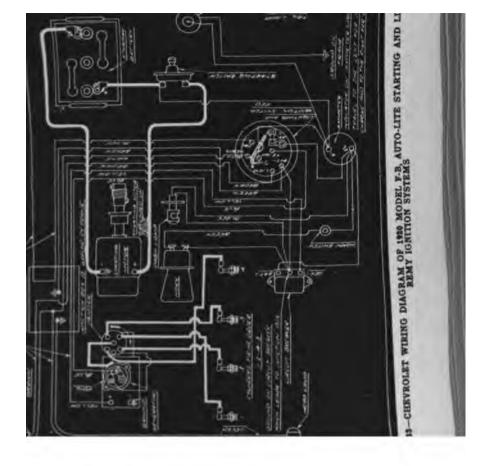

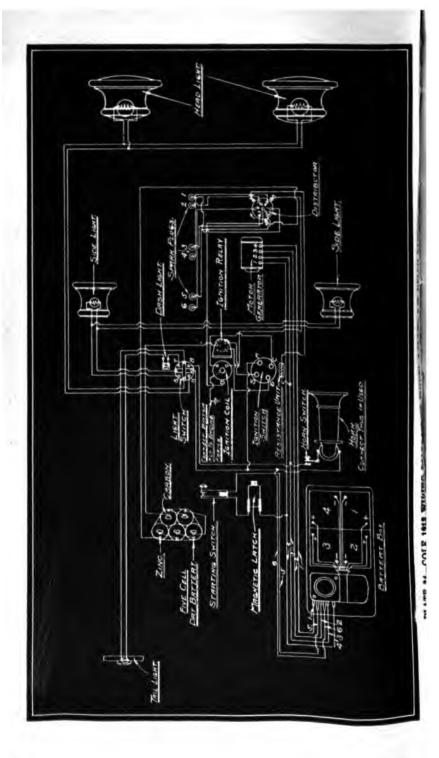

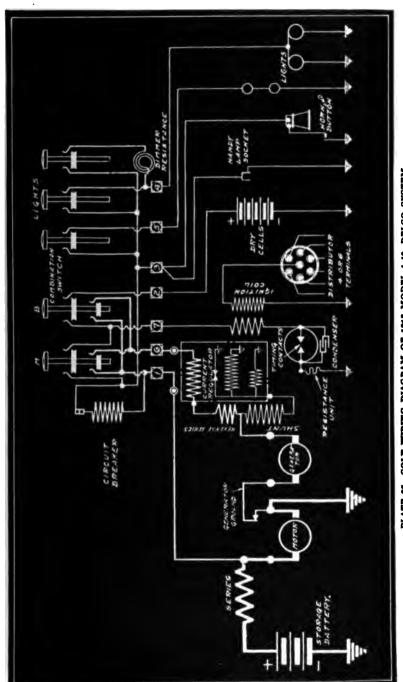


PLATE 36—COLE WIRING DIAGRAM OF 1918 MODEL 4-46, DELCO SYSTEM

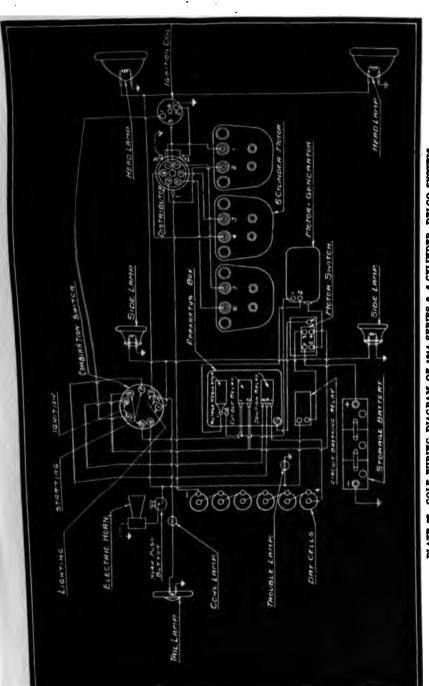


PLATE 57-COLE WIRING DIAGRAM OF 1914 SERIES 9, 6-CYLINDER, DELCO SYSTEM



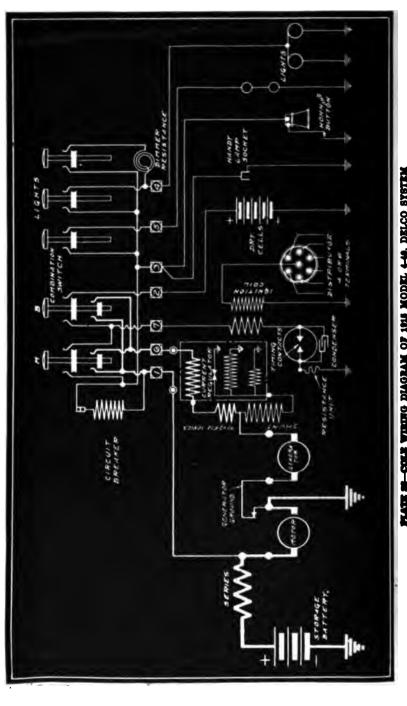


PLATE SP-COLE WINING DIAGRAM OF 1915 MODEL 4-49, DELCO SYSTEM

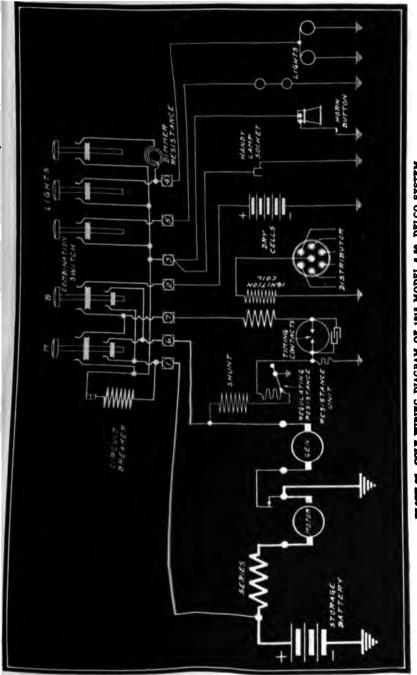

FILTE SE-COLE WIRING DIAGRAM OF 1918 MODEL 6-16, DELCO SYSTEM

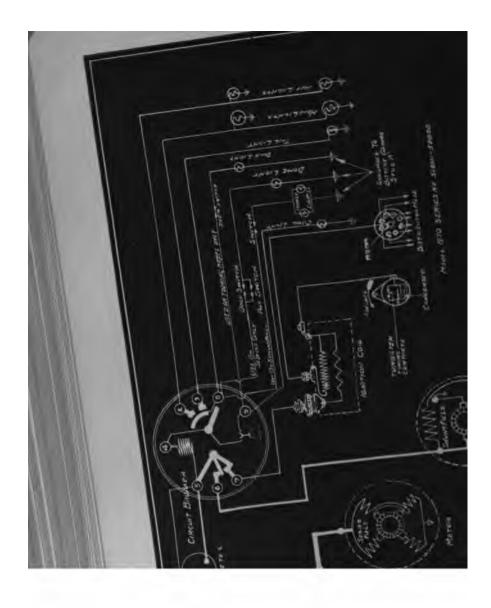





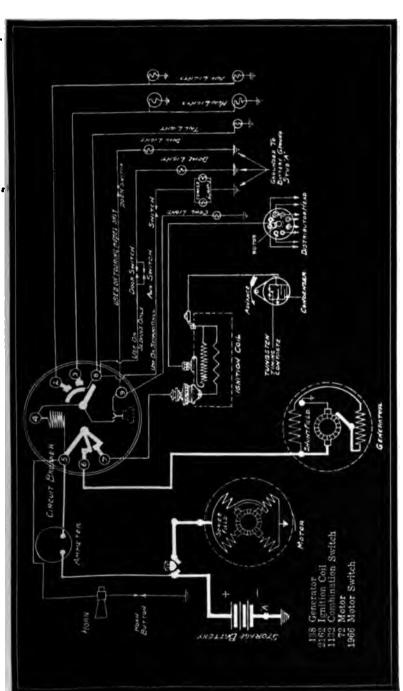


PLATE 41-COLE WIRING DIAGRAM OF 1919 MODEL 8-79, SERIAL 81001-34000, DELCO STSTEM

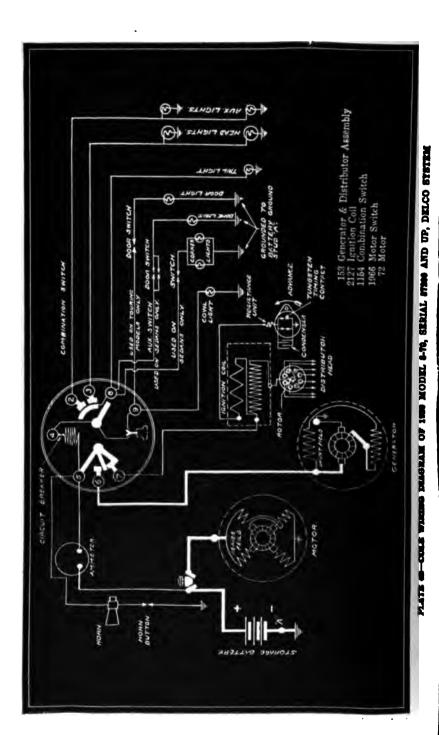

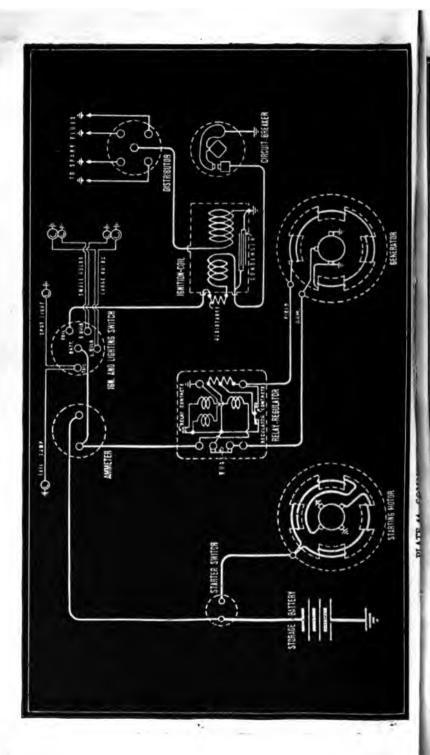

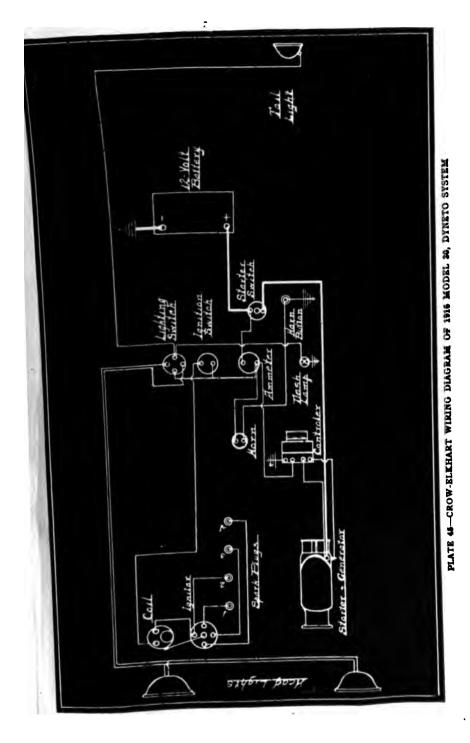

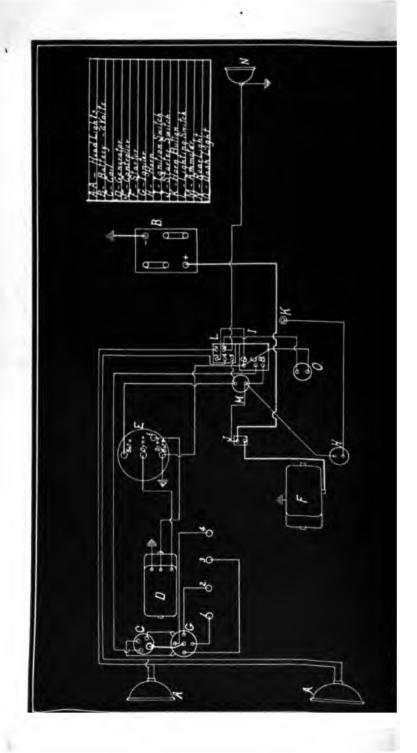

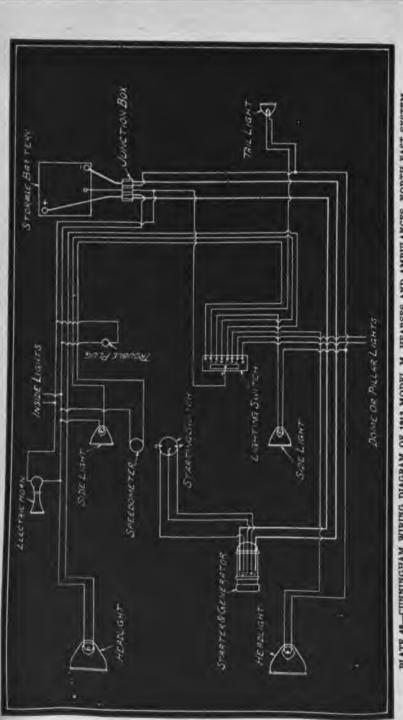


PLATE 48-CUNNINGHAM WIRING DIAGRAM OF 1913 MODEL M, HEARSES AND AMBULANCES, NORTH EAST SYSTEM

#### Q. What is a duplex magneto?

A. One designed to permit of passing the battery current through the armature of the magneto to facilitate starting, the magneto and battery both acting together to produce the spark at low speeds. To accomplish this a commutator is mounted on the armature shaft and the battery connected to it, the magneto being of the high-tension type. This commutator causes the battery current to alternate in direction with that produced by the magneto so that it is said to be "in phase" with the latter.

#### Q. What is an inductor magneto and how does it differ?

A. An inductor is employed instead of an armature, the windings being stationary. The inductor is simply a revolving piece of metal which alternately opens and closes the magnetic circuit. In the K-W inductor magneto this winding is of copper ribbon and is placed between the poles of the inductor; in the Dixie magneto it is a conventional induction coil placed in the hollow of the magnets above the inductor.

## Q. Why can a magneto not be run in either direction equally well?

A. Owing to the contour of the cam which serves to open the contacts of the interrupter. This must be designed to operate the magneto either as a "right-hand" or a "left-hand" machine.

#### Q. How is a magneto timed?

A. Disconnect its drive from the engine. Turn engine over by hand until the piston of cylinder No. 1 is exactly at the upper dead center on the firing stroke. Turn the armature shaft of the magneto to a point where the contacts of the interrupter are just beginning to open; the brush of the distributor which is then making contact with the distributor segment should be connected to the spark plug of cylinder No. 1. The next brush should be connected to cylinder No. 2 or No. 3, according to whether the firing order is 1-2-4-3 or 1-3-4-2. The armature of the magneto should be coupled to its driving shaft in the position as determined for the first cylinder.

#### Q. If after timing a magneto in this manner, it is found that the spark-timing lever does not give sufficient advance or retard, what should be done?

A. Remove the cover from the distributor housing of the

magneto, the piston of cylinder No. 1 being at upper dead center of firing stroke and the interrupter contacts just about to open as directed for timing. Note the relative position of the segment and the distributor brush which should be making contact with it. If the segment has already passed the brush, the spark-timing lever being at the maximum advance position, remove the distributor gear from its shaft and from engagement with the pinion on the armature shaft. Move it back one tooth (against the direction of its rotation which is the opposite of that of the armature pinion) and remesh with pinion. If this does not bring it into contact with the brush, move back another tooth. Should the distributor segment not have reached the brush when in the position as given above, move the distributor gear forward, or in the direction of its rotation, one or two teeth, and remesh.

## Q. How can the various types of magnetos be identified, as installed on car?

A. The two types in most general use may be distinguished at once by their external connections. The so-called dual type can be identified by its separate coil, or transformer, mounted on the face, or the front, of the dash, under the hood, and the connecting cables from the magneto to this coil. One of these connections is for the primary of the coil, and the other is for the secondary; the other ends of both coils are joined together and connected to a common ground wire, so that the coil has only three connections. The true high-tension type can at once be recognized by the fact that its only external wires are those connecting the distributor plate of the magneto directly with the spark plugs.

### Q. Of these various types, which are most commonly used?

A. The dual type will be found on most low-priced cars (except the Ford), and the straight high-tension type on higher priced cars not using battery ignition.

# Q. In searching for faults, is it easier to locate trouble in one type than in the other, and is the procedure different in each case?

A. Owing to its having but a single winding on its armature, and to the fact that all of its connections are external, the dual low-tension magneto is the simpler of the two; but the exposed location of its connections makes them more subject to default than those of the high-tension magneto. The procedure differs in that failure

o operate, in the case of a dual magneto, may be caused by injury o, or the breaking of, some of these external connections; whereas, with the high-tension type, the cables are so short and so direct that he fault is likely to lie in the magneto itself.

## Q. Where would be the most likely places to look for the ause of failure of a dual magneto to operate?

A. In about the order of their liability to occur, these would be as follows: broken or faulty connection at one of the coil terminals; brimary or secondary cable, connecting magneto with coil, grounded through chafing or from being soaked with oil and water; ground between the dry cells and the metal battery box (this last is a not infrequent ground and is very annoying to locate, as it will occur one moment and disappear the next, owing to the vibration breaking the contact); dirt, oil, or excessive wear at the primary collector brush, and similar conditions at the brush which conveys the highension current from the coil to the distributor; failure of the coil through breakdown; failure of the condenser, causing the interrupter soints to burn away rapidly; a break in the armature winding. All of these last are rare causes of trouble

#### Q. How are these faults best remedied?

A. Poor connections at the coil terminals can be overcome by paring about an inch and a half of the cable of insulation, twisting 1 1-inch loop in the end, and, after cleaning and wetting the oraided end with soldering flux, dipping the loop into molten solder. The terminal nuts can be screwed down hard on these loops without pening or injuring the stranded wires, and they will make solid and permanent terminals. Where cables have become so oil soaked hat the integrity of their insulation is suspected, they should be eplaced, and the new wires properly supported. If either of the orushes is at fault, due to excess of oil and dirt, clean with gasoline, and true up the ends square with a fine file. Should the brushes nave worn unevenly, or, in the case of the primary brush, taken on hard, glazed surface, treatment with the fine file will remedy the rouble. When they have worn down to a point where the spring to longer holds them in good contact, new brushes and springs attached) should be inserted.

Q. When examination shows no fault at any of these points, now can the coil be tested?

Disconnect the coil from the magneto, and connect to the battery terminal one wire from a spare battery of four dry cells or, if more convenient, to an ignition storage battery. Fasten the ground connection from the coil to some handy metal part of the chassis; lay the secondary cable from the coil on the chassis so that its bared end is not more than 1 inch from the metal of the motor. Then connect another length of wire to the opposite terminal of the testing battery. (The dry cells should be in series.) Scrape the end of this wire clean, and touch it rapidly to some part of the motor. A spark should occur every time it is touched, showing that the primary winding of the coil is uninjured, and, if the secondary is likewise uninjured, a spark should jump between the bared end of the secondary cable and the adjacent metal, every time the circuit is closed with the testing wire. The occurrence of these two sparks show the coil to be in proper working condition. If the spark occurs at the testing wire, but no high-tension spark takes place at the end of the secondary cable, it indicates that the secondary winding of the coil has broken down. Should the spark, taking place every time the testing wire is touched to a part of the motor, be very bright and hot, it is quite likely that the condenser has become punctured. Unless the failure of the secondary is due to a broken connection between the fine wire of the winding and the terminal, it must be sent to the maker for repairs. This is the case also when the condenser has been punctured. The magneto will continue to work with the condenser short-circuited, but this will cause a rapid burning away of the expensive platinum contact points of the interrupter.

### Q. How is the magneto armature winding tested for a break?

A. Employ the test battery already mentioned. Touch one wire to the armature shaft, and the other to the collector end which is insulated from the shaft. A spark should result if the winding is intact. Failure to obtain a spark would indicate a break in the winding, and the armature should be returned to the maker for repairs. In making tests with a battery in this manner, always make sure that the connections from the battery have not pulled loose nor become broken, before finally accepting the lack of a spark, at the point where it should occur as conclusive evidence of a fault in the part being tested. Otherwise, a failure of the testing apparatus itself may be put down as a fault in the part being tested.

- Q. Is a spark the best indication obtainable in making such tests?
- A. With a fresh battery of dry cells, the self-induction of the coils tested, such as the winding of the armature or the primary of the coil, will give a bright spark that cannot be mistaken; but, if an audible indication be desired, the battery may be placed in a box and a common electric door bell, or buzzer, mounted on the box. bell, or buzzer, must be connected in series with the testing wires. so that, when the circuit is completed, the current passes through it. Then the success of the test will be evidenced by the sounding of the bell, or buzzer, as long as the circuit is closed. In the case of the secondary winding of the coil, the spark is all that is necessary. Should a more visible signal be desired, the lamp-testing set, described in connection with trouble hunting on the starting and lighting system, may be employed. In this case, the test battery is dispensed with and the 110-volt lighting circuit used, but a 10-ampere fuseblock and fuses should be inserted in the testing circuit to guard against accidental short-circuits in handling the testing apparatus.
- Q. As secondary cable is expensive, and the owner does not usually want it replaced unless absolutely necessary, how can it be tested for faults?
- A. Connect the test battery to the coil, as previously described, but, instead of relying upon breaking the circuit by hand, insert a buzzer, or bell, in series, between the battery and the primary of the coil. This will give a vibrating contact, and will keep the coil working continuously. Connect the piece of cable to be tested to the secondary of the coil and support it well, clear of the ground, such as the motor or chassis. Take another piece of secondary cable and connect one end of it to the ground. Bare the other end, and pass this along the entire length of the cable being tested, very close to, or actually touching, the insulation of the cable under test. If there are any weak spots in the insulation, a spark will jump through it to the testing wire. In case a vibrating coil is at hand for making this test, it will not be necessary to insert the buzzer as mentioned.
- Q. What is likely to result when there are weak spots in the insulation of the secondary cables?
- A. The high-tension current will escape through them to the ground, because of the nearness or actual contact of the secondary

cable with the motor cylinders or other metal parts. This leakage will be neither visible nor audible, unless the insulation is very bad, and the failure to fire will usually be attributed to the spark plug instead.

- Q. Should primary cables be tested in the same manner.
- A. It is not necessary; as, unless the insulation is actually worn off, there will be no escape of current, owing to its low voltage. Where solid instead of flexible primary wire is employed, as on some old cars, or where the owner has made replacements, a test for a break in the wire itself under the insulation may be made with the aid of the battery and buzzer alone.
- Q. Are the causes of failure similar in a true high-tension magneto?
- A. No. As the primary-generating winding and the secondary, or high-tension winding, are both on the armature of the magneto itself, and all connections, except the high-tension leads from the distributor to the spark plugs, are made internally, there are no outside cables, terminals, or coils to default. Unless the repair man has become proficient in testing electrical apparatus and has familiarized himself with the construction of the high-tension type, he will find it preferable to refer to the manufacturer any cases of trouble in this class of apparatus. In fact, the maker usually absolves himself from any responsibility in case a magneto of this type has been taken apart. Even where the repair man is capable of dismantling and testing this type of magneto, its repair would ordinarily be beyond his facilities, so that it is better to refer it to the maker at once.
- Q. Are there any faults, peculiar to the "duplex" or to the "double-spark" types of magnetos, which are not encountered in the others?
- A. In the case of the duplex type, there may be a failure to work of the battery connections or of the battery commutator on the armature shaft, i.e., the commutator which throws the battery current into phase with the armature current of the magneto when starting. Since the advent of the self-starter, this type of magneto has had no particular advantage to recommend it, and will be found only on older cars. As the only difference between the double-spark and the usual magneto is a duplication of the distributor to give two sparks in the cylinder instead of one, its treatment is the same.

There are simply two distributors to maintain instead of one. This type is also of limited application and will be found only on comparatively few cars of several years back.

- Q. Why is it important that the magneto be accurately timed?
- A. Unless the spark occurs at exactly the right moment, the motor will not operate efficiently. If it occurs too soon, the explosion will tend to retard the piston; if too late most of the power that would have been derived from the compression will be lost. As the lag, i.e., the time intervening between the moment the contact points are opened at the interrupter and the occurrence of the spark at the plug, is negligible in the magneto, it must be more accurately timed than the old battery and vibrator-coil system.
- Q. Does the magneto ever fail to operate through lack of oil, and what attention should be given to its lubrication?
- A. Prior to 1910, when some of the lower-priced magnetos were made with plain bearings, this naturally occurred, but, with the adoption of high-grade annular ball bearings for the magneto shaft, it is practically unknown. However, even the high-grade ball bearing will not operate without lubrication. If it runs dry, the balls are apt to rust and ruin the bearing. Most of these bearings are packed with vaseline, or similar light grease, when the machine is assembled and require no attention during the life of the average car. Where this has not been done, as on some of the older machines, a few drops of fine sewing-machine oil once a year will suffice. The pivot and roller of the contact-breaker arm also should be oiled once or twice a year with one drop of oil to each, using a toothpick.
- Q. When taking a magneto apart, as where it is necessary to remagnetize the fields, why is it of the greatest importance to reassemble them in the same way?
- A. Unless this is done, the polarity of the fields will be reversed and the machine will not generate properly. The maker usually identifies the polarity of the fields by marking the magnets so that it is easy to reassemble them in the proper manner. See the illustration of the Eisemann magneto, Fig 103.
- Q. When remagnetizing the field magnets of a magneto, why is it important that their polarity should not be changed in the process?
  - A. The effect would be exactly the same as if the remagnetizing

were carried out properly, so far as their polarity were concerned, and then the magnets were put back the wrong way. The machine would not generate. For example, the marking on the side of the Eisemann magneto indicates the north pole of its fields. If in remagnetizing, this side of the field is made the south pole, and it is then correctly assembled, it will be evident that the polarity of the entire field has been reversed.

- Q. In the case of the dual magneto, how can trouble, caused by the grounding of the dry cells against the metal battery box, be overcome?
- A. By making a tight-fitting wooden box to hold the battery, this wooden box fitting inside the metal one.
- Q. Does the care required by an inductor type of magneto vary from that necessary for other types?
- A. No. So far as its outside connections go, it is the same. That is, in a dual type installation, using an external coil, or transformer, the causes of trouble and their remedies will be the same as in any dual system, as already given; and this also applies to the high-tension dual type.
- Q. In the order of their occurrence, what are the commoner causes of failure of the magneto, due to wear of its parts?
- A. In practically every case of failure of the magneto that is not otherwise apparent at a glance, an inspection should always be made of the contact points in the breaker box. Unless they open properly when the cam strikes the lifter, no current reaches the outside circuit and the coil is not energized. Next, inspect the contact of the collector brush; see that it is clean; that it is making good contact over its entire surface; and that its spring is holding it firmly in place. After this, inspect the distributor.
- Q. How often should the contact points in the breaker box require attention?
- A. This will depend upon the type of magneto, and when it was made. On some of the earlier types, prior to 1909, no condensers were used on many of the lower-priced magnetos, and the points required attention every 3,000 or 4,000 miles. Others will run two or three times this distance without requiring attention. If, when the points have been found in poor condition, they have not been properly trued up and adjusted, they are apt to require attention

ain much sooner, as any irregularities in their contact faces will use them to burn away much more rapidly.

- Q. As the platinum contacts of the magneto breaker box are pensive, how far down can they be allowed to wear before it is cessary to replace them?
- A. This will depend upon the amount of adjustment provided. long as there is sufficient platinum left to provide a true surface each contact point, it will not be necessary to replace them if ey can be adjusted so that the cam opens and closes them properly.
- Q. Since the magneto-armature circuit is normally closed on itself and only opens when a spark is required at one of the 1gs, how is the magneto ignition shut off?
- A. By short-circuiting the armature around the contact points stead of opening the entire ignition circuit, as in the case of a battery nere it is necessary to save current, the generating part of the cuit is closed. This is true of all high-tension magnetos.
- Q. When the contact points of the interrupter of the magneto il to separate, what is the result?
- A. The armature remains short-circuited upon itself throught the revolution, and no current reaches the outer circuit, so that e engine will not fire on the magneto at all.
- Q. What is the result when the contacts open but the gap is t wide enough?
- A. Erratic missing, probably at all speeds, but more prounced when the engine is running slowly. The increased kick ven the movable contact arm by the cam, when the engine is runng at a higher speed will cause it to fire more regularly.
  - Q. What happens when contact points are separated too far?
- A. The missing is likely to be more noticeable at high speeds an at low speeds; as, when turning very fast, the looseness of the ovable contact arm may prevent it from closing the circuit again time for the next cylinder to fire.
- Q. What is the proper distance for the setting of the contact ints of the magneto interrupter, or breaker box?
- A. Approximately strinch, or the equivalent of an ordinary eet of paper. When the points are properly adjusted, it should possible to insert the paper between them and move it around thout binding.

#### Q. How are the contact points usually adjusted?

A. Practically every magneto manufacturer now supplies an adjustment gage, which serves also as a screwdriver or small spanner, according to the construction of the interrupter. The thickness of the metal represents the distance that the contacts should open. In all except the old types produced several years ago, the interrupter may be removed without the use of any tools, and the adjustment



Fig. 143. Method of Adjusting Magneto Contact Points

made without the necessity of removing the magneto from its bedplate. The following instructions cover the Eisemann dual type in this respect, and are typical: "Insert from behind through the hole in the plate carrying the make-and-break mechanism, the metal adjuster which we supply with every magneto: by means of a flat wrench hold the nut on platinum screw (contact) and turn the platinum screw upward or downward until there is a gap of of the inch between the contacts,

i.e., a piece of paper must pass between them without getting jammed", Fig. 143.

# Q. How often should the magnets of a magneto need remagnetizing?

A. No definite time nor average can be given for this. In some cases, the makers state specifically that the magnets will never need remagnetizing during the entire life of the machine, unless they are taken off and allowed to stand without a "keeper", i.e., a piece of soft iron placed across the pole pieces, the magnets themselves being placed in their usual relation as when on the machine. In others, it has been nothing unusual to require this once a year, or after 6,000 to 10,000 miles running.

# Q. How can it be determined definitely whether the magnets actually need remagnetizing or not?

A. Many cases of weak or faulty ignition are attributed to loss of strength in the magnets, when they are actually due to some-

thing else. Before deciding that the magnets themselves are at fault. every part of the system should be gone over thoroughly. See that the contact points are clean and true, and that they are properly adjusted; that the low-tension collecting brush, or contact, is clean and is making good contact; also, that the distributor is clean. Inspect all terminals and connections. Test the condenser. Disconnect one of the spark-plug leads, keep it away from any metal part of the chassis and, with the engine running, note whether a spark occurs at the safety gap. In a high-tension magneto, this gap is ually located in the hollow of the magnets back of the distributor: in a low-tension type, having a separate coil, it is usually on the coil. Take the spark-plug lead which has been detached (engine running) and approach its metal terminal gradually to the spark-plug end, or to some metal part of the engine, noting the maximum distance that the spark will bridge. If this is one-quarter inch or more, the magnets are not at fault.

- Q. When there is no question but that the magnets are the cause of faulty ignition, how can the magnets be remagnetized?
- A. With the aid of a small electromagnet, as described in the chapter on this subject. Care must be taken to see that the polarity of the magnets is not reversed in the process, as this will render the magneto altogether inoperative.
  - Q. How is the ground connection made in a magneto?
- A. One side of the winding of the armature in a low-tension type, and of both windings, i.e., the primary and secondary are grounded by being electrically connected directly to the core of the armature itself, in the high-tension type. The fastening of the magneto in its bedplate on the engine, completes this ground connection.
- Q. Is it ever advisable to insert paper liners, or liners of any material, between the magneto and its bedplate?
- A. If on an old car, it is necessary to resort to liners or shims to correct the alignment of the magneto with its driving shaft, nothing but thin sheets of brass or iron should ever be employed, as the use of any insulating material for this purpose would break the ground connection and prevent the magneto from functioning properly. But even on old cars, where the lack of alignment of the magneto with its shaft is such as to be plainly perceptible to the

unaided eye, the Oldham coupling usually employed on the driving shaft, allows sufficient play to compensate for this. Any lack of alignment is more likely to be due to carelessness in replacing the magneto after it has been removed from the engine for attention, than to any fault in the placing of the bedplate and driving shaft.

- Q. What will be the result of the magneto being lined up incorrectly?
- A. The universal coupling is apt to wear badly, and the side pressure, which the lack of alignment causes, may not be taken care of entirely by the coupling, so that the pressure has to be taken in part by the magneto shaft and its bearing. This will result in undue wear of the bearing and, in time, may permit the armature core of the magneto to strike the pole pieces, or sides of the tunnel, so that it will jam. On many of the higher-priced cars, a flexible coupling, consisting of leather discs, is employed for the magneto drive.
- Q. Which is more likely to occur, separation of the points by too great a distance or their coming together so that they do not open?
- A. The result of wear will usually be to increase the distance between the points, but the writer has experienced the opposite on an old car where the cam apparently wore down faster than the points and prevented their opening. This was probably due to improper hardening of the cam itself or to the fact that the roller was harder than the cam. Many of the later models do not employ a roller in the movable contact arm, the cam striking directly against a projection on the arm itself (see Eisemann interrupter, Fig. 143). An example of the roller type, is the K-W interrupter, Fig 69.
- Q. Is it possible for the adjustment of the contact points to wear to such a degree that the magneto will fire the engine at high speeds, but not at all at low speeds?
- A. Instances of this nature on old magnetos have proved a puzzling cause of ignition failure. The extra kick of the cam at high speeds would separate the points, whereas at low speeds they remained together.
- Q. Inspection having shown other parts of the ignition system to be in good order, how can it be determined whether the magneto itself is at fault?
- A. Run the engine on the battery, and switch from battery to magneto while the engine is running at a good speed. If the magneto

is not operating properly, the difference in running will be perceptible immediately; in case the contact points are not opening, the explosions will cease at once upon throwing the switch to "magneto".

### Q. What is meant by "ignition timing"?

A. A four-cycle motor is so-called because there are four parts to each cycle: viz, suction, compression, firing, exhaust. It is evident that ignition is necessary only at one part of the cycle and that the spark must occur at a certain time with relation to the carrying out of that part of the cycle. Determining the point at which the spark is to occur in that part of the cycle is usually referred to as the "timing of the spark", or as the "ignition timing".

#### Q. Is it necessary that this be carried out with precision?

A. In the high-speed automobile motors of the present day, it must be extremely accurate with relation to the movement of the piston and must be exceedingly rapid in action; otherwise, the efficiency of the motor would suffer greatly. In the slower-running motors with fewer cylinders, of several years ago, neither of these factors was of such great importance; but the present-day high-speed multi-cylinder motors could never be operated satisfactorily on ignition apparatus of the type familiar on 1910 models, for example.

# Q. Why would a variation or a lack of precision affect the running of the motor?

A. Speeds are now so high that the time factor is reduced to exceedingly small fractions of seconds. For example, take a high-speed four. It turns at 2500 r.p.m.: as there are two explosions per revolution in a four-cylinder motor, this would mean 5000 sparks per minute, or one spark every .012 second. This is cutting time pretty fine, but in a modern twelve-cylinder motor, it is finer still. Say the twelve runs at 3000 r.p.m.: in a twelve there would be six explosions per revolution, requiring 18,000 sparks per minute, or one for every .0033 second—thirty-three ten-thousandths of a second—an incredibly brief space of time in which to carry out a combined mechanical and electrical function.

### Q. How is this extreme accuracy obtained?

A. By the use of precision machine work in the distributor, approaching that of a fine watch, and a great amount of "advance" to compensate for any lag in either the mechanical or electrical functioning of the apparatus.

## Q. What is meant by "lag", and what is the difference between mechanical and electrical "lag"?

As the term implies, lag is delay: in other words, it is the time elapsing between the moment a part begins to move and the actual moment at which it moves and makes contact or carries out the function for which it is designed. Mechanical lag is due entirely to the time necessary to overcome the inertia either of a part that is stationary or of one that is moving in another direction and whose direction must be reversed. Electrical lag, on the other hand, is the time elapsing between the moment that current is switched into a piece of electrical apparatus and the moment that the apparatus actually operates. This will appear strange at first sight in view of the universal belief that anything electrical operates so swiftly that it is next to impossible to measure the time required. when nothing more than the passing of a current of electricity from one point to another is concerned, but when actual work must be performed by the current, the time required is not only measurable but it may be so perceptible as to have a decided effect upon such extremely rapid functioning as that mentioned. For example. when the work to be performed by the current consists of magnetizing the core of a coil, as is necessary in automobile ignition, the time element is quite perceptible, as may be noted by referring to the oscillograph of the spark produced by an induction coil, Fig. 95. coil having the characteristics shown by this oscillograph would be worthless on a modern high-speed motor.

### Q. How is this lag compensated for?

A. By advancing the moment that contact is made outside of the cylinder to an extent that will insure the occurrence of the spark in the cylinder at the proper moment. In other words, the current is started on its way sooner with relation to the movement of the piston. This is generally referred to as "advancing the spark".

# Q. What is the proper point, in the travel of the piston on the compression stroke, for the ignition spark to occur?

A. Exactly at the upper dead center just before the piston starts downward again. The compression is then at its maximum, and firing the charge exactly at that moment results in the production of the greatest amount of power. The compression falls off very rapidly the moment the piston starts down on the power stroke, so

that in a high-speed motor, the loss of even a very minute fraction of a second causes a considerable loss of energy.

#### Q. What will happen if it occurs too soon?

This will depend largely upon the type of motor and upon how much in advance of the proper time it actually occurs. slow-speed type running well below its normal r.p.m. rate, as where a motor with a normal speed of 1000 r.p.m. is slowed down to 600 r.p.m., owing to climbing a hill, advancing the spark to its maximum will cause hammering or pounding in the cylinders, indicating that the explosion is taking place before the piston reaches upper dead center and, consequently, that most of its energy is being expended against the rising piston, instead of helping thrust it downward as it should. When running at its normal rate, the piston speed of such a motor would be sufficient for the piston to have reached upper dead center before the burning gases had time to expand, so that their entire output of energy would be expended in producing power. high-speed multi-cylinder motors with their diminutive cylinders and light moving parts, the piston speed is so great that even the maximum advance in the ignition timing would have no effect, even as the lowest speed of which the motor is capable.

### Q. What is the result when the spark occurs too late?

A. The piston has already started on its downward stroke; the point of maximum compression has been passed, so that the full benefit of the compression is lost, and with it, a large part of the energy that would otherwise have been utilized.

## Q. Has running with a late spark any other effect on the motor?

A. Yes. The gas in the combustion chamber is ignited so late that it continues to burn after the exhaust valve is opened. As the heat units it contains are not utilized as power, they are retained longer in the cylinder in the form of heat; the water jackets are compelled to absorb 50 per cent more of the heat than they should; and the whole motor is said to "run hot" or to "overheat". The late combustion of the gases does not permit of sufficient time for the normal amount of heat to escape by way of the exhaust, so that there is still burning gas in the combustion chamber when the exhaust valve closes.

#### O. What other term is used in referring to a late spark?

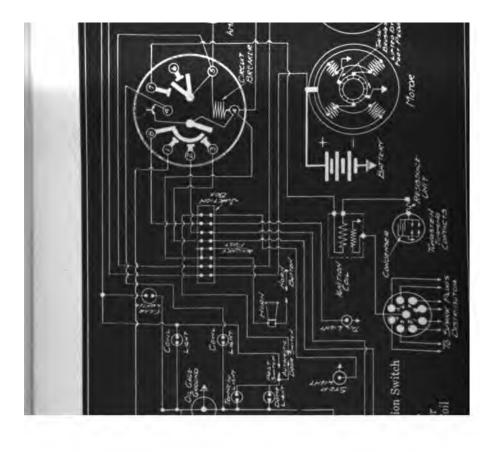


PLATE-49-CUNNINGHAM WINING DIAGRAM OF 1916-19 MODEL V-4, DELCO SYSTEM

A. Retarded ignition, or a retarded spark, meaning one that, occurs later in the firing part of the cycle, i.e., later with relation to the travel of the piston itself. An early spark, or advanced spark, is set to occur or rather start to take place well before the piston has reached upper dead center on the compression stroke. The time of ignition is always based on its relation to the position of the piston, though frequently referred to in terms of degrees on the periphery of the flywheel. This is done for greater convenience in setting the ignition, as the timing of the valves is always marked on the rim of the flywheel.

## Q. Why is it necessary to have the ignition occur later at one time than at another?


A. To permit of starting the motor, especially by hand. The time of ignition is advanced to compensate for the extremely rapic travel of the piston, and is designed to cause the spark to take place just as the piston reaches upper dead center on the compression stroke. In high-speed motors this advance amounts to as much at 1 inch of the stroke. It will, accordingly, be evident that if an attempt be made to start the motor with the spark advanced, ignition will take place before the piston reaches upper dead center and the motor will kick back.

# Q. How much allowance is usually made for retarding the time of ignition?

A. In the ordinary type of motor in which the speed does not exceed 1500 to 1800 r.p.m., it is customary to have the latest timing allowed coincide with the upper dead center position of the piston. In some cases, the spark may be retarded to take place after the piston has traveled a short distance down on the firing stroke, or about 5 degrees to 7 degrees on the rim of the flywheel. In the majority of cases, however, "extreme retard" is at the upper dead center of the piston.

## Q. How is the time of ignition, or "spark", advanced and retarded?

A. The timer, in the case of a system using vibrator coils, and the distributor, in all systems using one vibratorless coil, consists of two parts. In the case of the timer, the four contacts for a four-cylinder motor are set into the inner periphery of a circular casing and a single revolving contact, mounted on the camshaft, passes

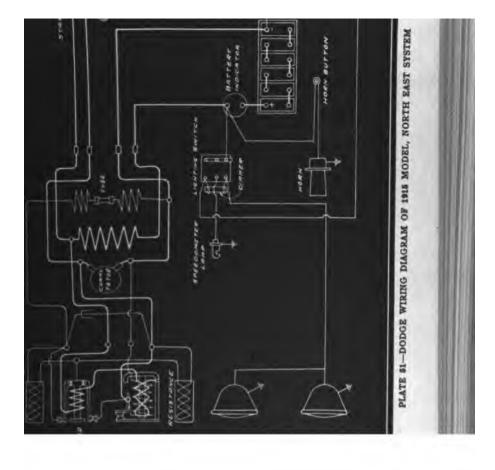



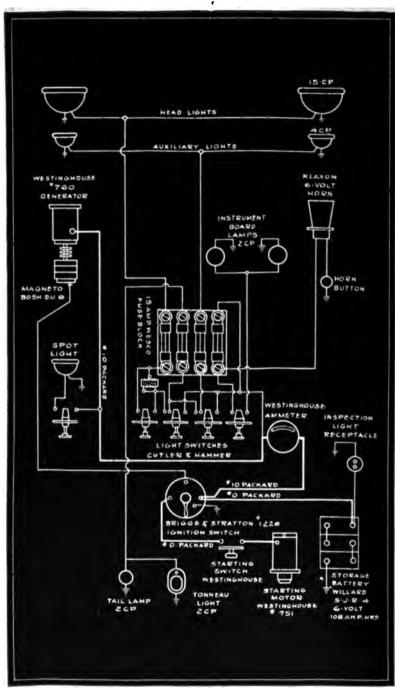


PLATE 52-DORRIS WIRING DIAGRAM OF 1920 MODEL 5-80, WESTINGHOUSE SYSTEM

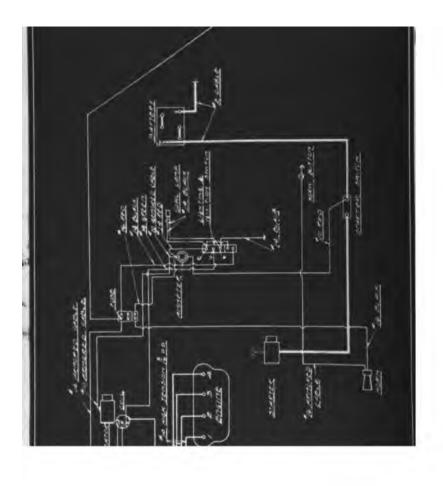

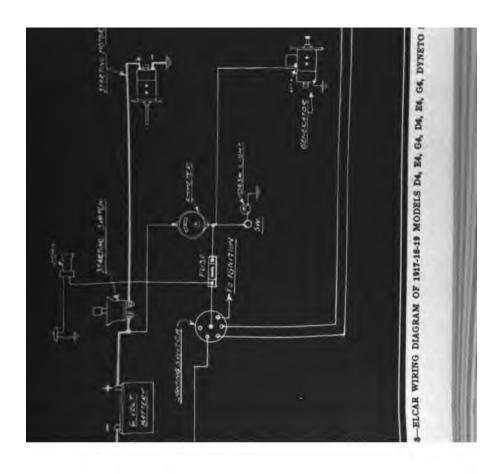



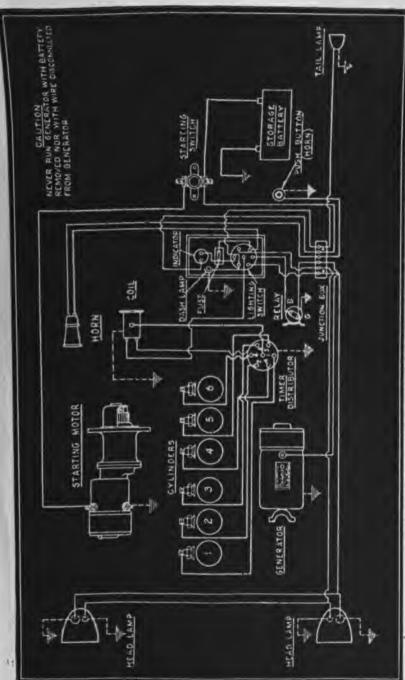


PLATE ST-ELGIN WIRING DIAGRAM OF 1917 MODEL 17, WAGNER SYSTEM

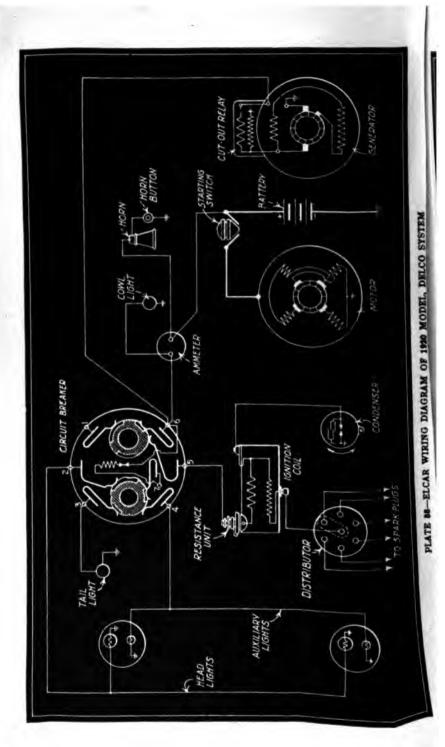


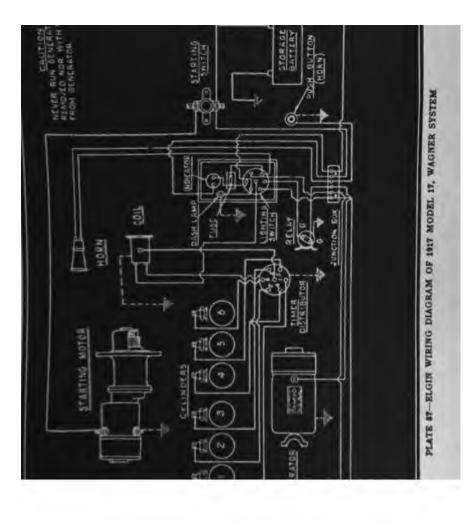



STARTING BLIGHTING DYNAMO STARTING SWITCH STORNGE BATTERY TRIL LIGHT RELAY 00000 PESISTANCE BUTTON FUSE PILOT LIGHT HEAD LIGHT HERD LIGHT

1

PLATE 60-EMPIRE WIRING DIACERA-

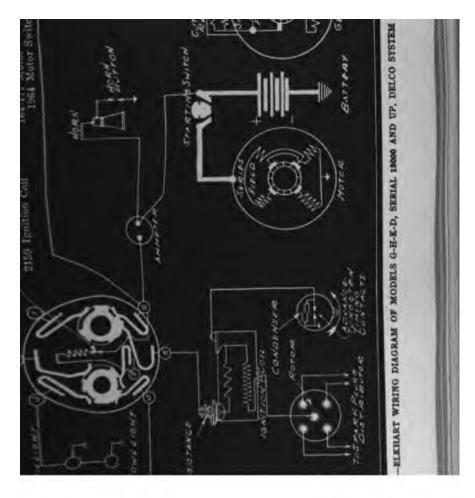

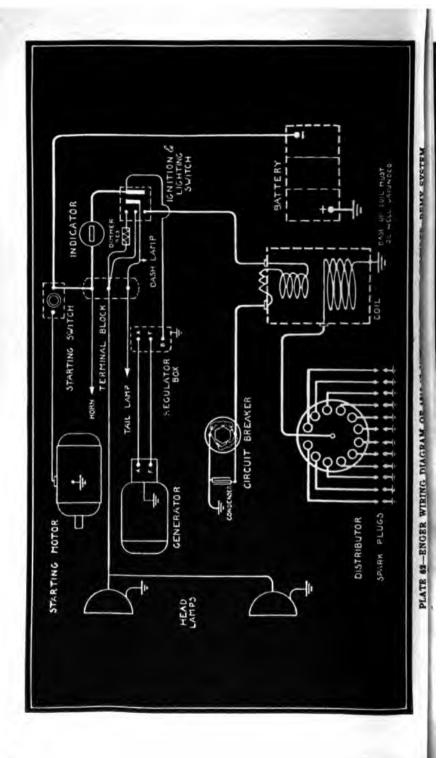

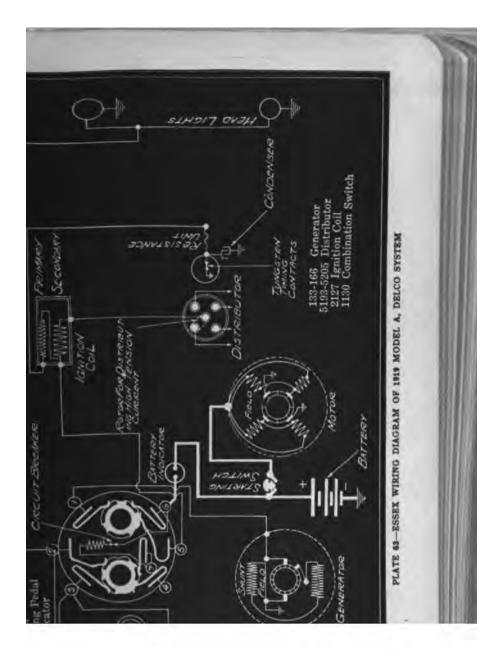

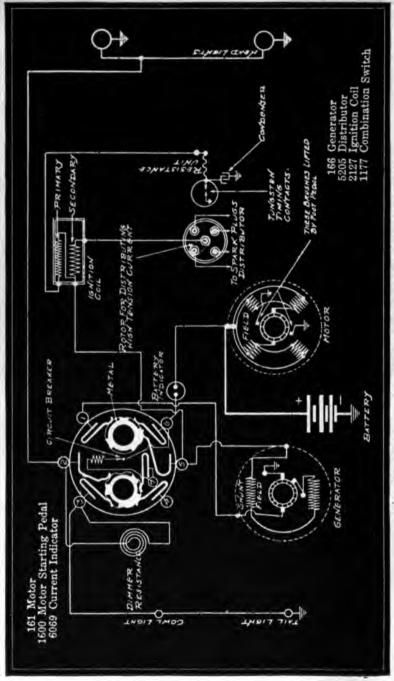


PLATE 64-ESSEX WIRING DIAGRAM OF 1880 MODEL & DELCO SYSTEM

over them consecutively, sending the current through the primary winding of each of the induction coils in rotation. These coils are connected to the spark plugs of the different cylinders in the proper firing order. While this outer casing of the timer is normally stationary, it may be moved part of a revolution with relation to the position of the revolving contact. For example, if the moving member in its revolution were within 20 degrees of touching the contact corresponding to coil and cylinder No. 1, and then the casing were revolved 20 degrees in the same direction as that in which the contact is moving, it will be evident that the meeting, or contact, of the two will take place that much later, and the occurrence of the spark in the cylinder will be correspondingly delayed. If, instead of being moved away from the revolving contact, the housing is revolved against the direction of rotation of the contact, the two will come together that much sooner and the spark will be advanced, or occur earlier. This housing of the timer is connected by means of linkage with the spark lever under the steering wheel.

In the case of the distributor, the principle is exactly the same, except that the current is sent in turn by each one of the contacts, through the same induction coil, instead of having a coil for each cylinder. The method of accomplishing this result is also varied: in many magnetos the distributor consists of a revolving block carrying a single contact, while a carbon brush for each cylinder bears against it. In most of the battery-system distributors, the arrangement is very similar to a timer, but the construction and insulation are naturally carried out in very much better fashion.

- Q. What is meant by an advance of 30 degrees for the ignition?
- A. That the difference between the point of extreme retard, usually upper dead center of the piston, and that of maximum advance or earliest ignition for high speed, represents 30 degrees on the flywheel. Just what this corresponds to in inches on the flywheel naturally depends entirely upon the diameter of the flywheel.
  - Q. What is meant by the magneto setting point?
- A. This is a line inscribed on the flywheel in the same manner as the usual marks for the valve timing of the motor. There is a corresponding dead line, or pointer, on the crankcase, with which these lines on the flywheel are registered to check the valve timing

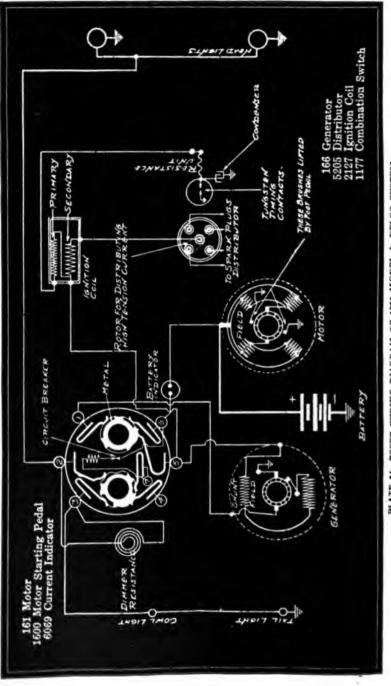


PLATE 64 -ESSEX WIRING DIAGRAM OF 1886 MODEL A DELCO SYSTEM

ture coils that it carries. With a battery, however, the occurrence of the spark is just as rapid at low speeds as at high, so that attempting to start on the battery with the lever fully advanced will invariably result in a vicious back kick; the whole force of the explosion is exerted against the rising piston. As there is a greater amount of lag in the ordinary battery system than there is with the magneto the movement of the spark lever represents more actual advance, as this is necessary to provide for the time lost in the operation of the system. This, however, applies only to old battery systems, such as the dry cells used in connection with the magneto in a dual systems and not so much so to the so-called modern battery-ignition systems which are practically as rapid as the magneto.

### Q. What is meant by fixed ignition?

A. The time of ignition is not variable by means of a sparkadvance lever. Only a magneto is employed (true high-tension type) for ignition and it is set to fire at the maximum advance at all times when running. Provision is usually made for retarding the time of ignition to allow for hand starting, though this is not always the case, as it is not absolutely necessary (see answer to previous question). Otherwise, the ignition is always advanced to the maximum and there is no lever on the steering wheel for varying it. This type of ignition system has been very generally employed abroad and, more particularly in France, on commercial vehicles, such as cabs, but has never found any favor here. It has not been used in this country, except on a very few makes of cars, and then only for the models of one or two seasons, the latest being about 1912.

## Q. What is meant by automatically advanced ignition, and how is this accomplished?

A. Instead of relying upon a manually operated spark lever under the steering wheel, a centrifugally operated device is incorporated with the timer or distributor. As this depends upon the speed of the motor for its operation, the ignition timing is always at the point of extreme retard when the motor is stopped, so that it may be cranked by hand without taking any precautions to retard the spark. The device is practically a small centrifugal governor the weights of which expand against the action of a spring under the influence of increasing speed. These weights are connected by a lever to the timer, or distributor housing, so that, as they expand

and the setting of the magneto. When the magneto-setting lines on the flywheel is directly opposite the dead line, or pointer, on the crankcase, the piston of cylinder No. 1 should be at upper dead center exactly on the compression stroke, i.e., on the previous down stroke, it has drawn in a fresh charge, and when the piston again reaches upper dead center it has completed compressing this charge, so that the cylinder is then ready to fire. With the piston of this cylinder at the position in question, the contact points in the breaker box of the magneto should be just opening.

- Q. How is the ignition timing advanced or retarded on a magneto?
- A. The magneto breaker box may be moved part of a revolution, with relation to the contact points, in exactly the same manner as previously described for a timer or distributor. This alters the relation of the cam which opens the contact points to the latter so that their separation takes place earlier or later, in accordance with the direction the breaker box is rotated.
- Q. Why is it that a motor may be cranked by hand with the spark lever in the fully advanced position when starting on the magneto, and why can this not be done safely with a battery?
- There is less actual advance in the time of ignition, as supplied by the magneto, represented by the movement of the That is, moving the spark-advance lever to its maximum does not cause so much advance in the actual timing of the ignition when connected to the magneto for starting, as it does when connected to the battery. The speed of the magneto itself is responsible for a considerable advance in firing time when the motor is running, whereas the battery ignition has a fixed speed of operation. regardless of whether the motor is being turned over by hand or is being run full speed. Moreover, as the usual magneto setting point is upper dead center, the spark does not actually occur until slightly later, when the motor is being cranked slowly, so that, while the spark lever may be in the advanced position, the actual occurrence of the spark is not perceptibly earlier than it would be with the lever fully retarded. This makes it possible to crank the motor with the lever fully advanced on the magneto, without any danger of a backfire. This is not true to the same extent with the Ford magneto as with other types, owing to the great number of pole pieces and arma-

- A. There is an actual break between the lever on the steering wheel and the timer, or distributor, or the breaker box of the magneto. This is apt to leave the ignition timing fully advanced, making it dangerous to attempt to start the motor by cranking it on the battery.
- Q. Why do some motors require a greater amount of ignition advance than others?
- A. Because of their greater speed or the increased amount of lag in the ignition system which must be compensated for by the timing.
- Q. What system of ignition has the greatest amount of lag, and which the least?
- A. The old battery system, using a roller-contact timer and vibration coils, has the maximum amount of lag, as there is both a mechanical and an electrical lag. The high-tension magneto and the modern battery system are great improvements in this respect, and there is not much choice between them on this point. As an illustration of the effect of the motor speed on the amount of advance required, the Packard "twin-six", using a modern battery system, requires as much advance as the old Packard "four", on which a low-tension magneto was employed; while the Packard six-cylinder motor, which was fitted with a high-tension magneto, required considerably less than either of these.
- Q. Why is it necessary in some ignition systems to set the spark "late", or after the piston has actually started downward on the firing stroke, when the spark lever is at the point of maximum retard, while in others it is only necessary to set it at upper dead center?
- A. This is due to the difference in the amount of lag, and also to whether a battery or a magneto is employed. It is necessary to insure safety in hand cranking, as, where the lag is reduced to the minimum, the explosion would take place before the piston had reached a point where it could start downward on the firing stroke, and a back kick would result.
- Q. Is the piston actually at upper dead center for ignitionsetting purposes when it has ceased to rise?
- A. No. There is an interval in the revolution of the crank during which the piston does not move, i.e., while the crank is moving

in practically a horizontal plane, and it should complete this part of the revolution, so that the piston is just on the point of starting downward again before it reaches the proper point for ignition setting at maximum retard.

### Q. To what systems does fixed ignition occur?

A. This refers to those systems in which there is no provision made for altering the time of ignition, either by a manually operated lever on the steering wheel, or by an automatic device for advancing and retarding it. In other words, the time of ignition is fixed and is always the same, regardless of the speed of the motor. It can be used only in connection with a magneto.

### Q. What is the ignition-setting point for "fixed" spark?

A. This represents a mean between what would be the points of maximum retard and maximum advance in a variable system. The spark must not occur too late as the motor will develop only a percentage of its power and will overheat; nor must it be too early, as the motor is then apt to fire against the rising pistons when slowed down, as in climbing a hill or when heavily loaded. The magneto must be set, therefore, so that the spark occurs before the piston reaches upper dead center. Just how much in advance of that point the setting should be, will depend upon the motor itself. As will be noted in the table of firing orders, a much greater range of timing is allowed for on some motors than on others, so that there is no rule which will apply to all. The ignition-setting point as given by the manufacturer should be learned and the magneto set in accordance.

### Q. Is fixed spark ignition in common use on American cars?

- A. Although very largely used abroad, particularly in France, on commercial vehicles such as taxicabs, it has never found favor here and will be found on very few cars.
- Q. Is there any other method of checking the ignition-setting point besides the marks on the flywheel or the position of the piston of one cylinder in its relation to the contacts of the interrupter?
- A. In some magnetos, such as the Eisemann, there is a setting mark on the distributor of the magneto. When the piston is in the proper position for firing, it is only necessary to bring this setting mark in line with a setting screw on the stationary part of the distributor.

- Q. Why do the cylinders of an automobile engine not fire consecutively?
- A. Because the pistons are attached to the crankshaft in pairs in the same plane, so that when one piston of a pair is firing the other one is going down on the suction stroke.
  - Q. How can the firing order of a motor be determined?
- A. Take out all the plugs and lay them on the cylinders so that the threaded part of the plug makes contact with the cylinder but the terminal does not. Switch battery on and turn engine over slowly, noting the order in which the sparks occur at the plugs. Watch the valve stems; after the inlet valve of cylinder No. 1 has opened and closed, it is ready to fire. The plug at which the spark then occurs is the proper plug for the first cylinder. The next plug to spark belongs to the cylinder whose inlet valve has just closed.
- Q. When a motor will not start, but fires once or twice and then stops, the flywheel rocking back and forth, what is the cause?
- A. Some of the spark-plug leads have been misplaced, so that after one or two explosions, the next one takes place out of sequence.
  - Q. How many different firing orders are possible in a motor?
- A. This depends upon the number of pairs of cylinders in a motor, as the two cylinders of a pair cannot fire consecutively, so that the ignition alternates from one pair to another. For example, in a four-cylinder motor, cylinders No. 1 and No. 4 constitute one pair, in that they are attached to crankpins in the same plane, i.e., they rise and fall together; cylinders No. 2 and No. 3 constitute the other pair. Consequently, starting with cylinder No. 1, there are only two firing orders possible in a four-cylinder motor, as follows: 1-2-4-3, or 1-3-4-2. By starting with cylinder No. 2, as the first to fire, two more orders may be used, as 2-1-3-4 or 2-4-3-1. It will be apparent, of course, that the last-named combination is merely the reverse of the second one given above, i.e., 1-3-4-2. In this way, the total number possible with a motor of this type is eight firing orders.
- Q. Do motors differ much in this respect, or are firing orders pretty well standardized?
- A. Of the eight possible firing orders that may be used in a four-cylinder motor, only two are in common use, viz: 1-2-4-3, and 1-3-4-2. This is because the selection of cylinder No. 1 as

- Take the instance cited above. Cable No. 1 has been connected to cylinder No. 2; cable No. 2 has been connected to cylinder No. 1. The firing order is 1-2-4-3, which means that when the piston of cylinder No. 1 is going down on the power stroke, the piston of cylinder No. 2 is drawing in a fresh charge of fuel mixture through the open inlet valve. But, as cable No. 2 is connected to cylinder No. 1, no spark takes place when the piston finishes its upward travel on the compression stroke, and no explosion results. The spark instead of occurring in cylinder No. 1, takes place in cylinder No. 2, and may ignite the incoming gas, resulting in a weak explosion or a back-fire through the inlet valve. If the placing of the inlet valve be such that the incoming charge is not fired by the spark of cylinder No. 1, but takes place in cylinder No. 2, on the suction stroke, nothing will occur in cylinder No. 2, either. its piston comes up on the compression stroke ready for firing, the spark occurs in cylinder No. 1, and the fresh charge passes out of the exhaust valve of cylinder No. 2 without being fired. In other words. both cylinders No. 1 and No. 2 miss. Cylinders Nos. 3 and 4 being connected up in the proper order, however, they will fire as they should, but in a four-cylinder motor they are not sufficient to keep the motor turning over steadily. It will give two jerky explosions and stop. After cranking several times, cylinder No. 2 will become more or less filled with fresh gas, and a back-fire will result at every other revolution, or every time it is the turn of cylinder No. 2 to fire. Cylinder No. 1 is not likely to back-fire, since the spark is occurring in its combustion chamber on the exhaust stroke.
- Q. What would be the effect if, instead of connecting to cylinder No. 1, the lead of cylinder No. 2 misconnected to No. 3?
- A. As the firing order of the motor is 1-2-4-3, it will be evident (the other cables being correctly connected) that cylinder No. 1 will fire properly; No. 2 will miss; No. 4 will fire properly; and No. 3 will either miss or back-fire; so that the motor as a whole will run very jerkily; although it will continue to run on this combination, i.e., one operating cylinder in each alternate pair firing a revolution apart. In this case, when the piston of cylinder No. 2 has just finished compressing its charge and should fire it, its spark takes place in the combustion chamber of cylinder No. 3, which is then exhausting, so that it is also much more likely to miss than to back-

#### SPARK PLUGS

- Q. What are the usual causes of failure of the spark plug?
- A. An accumulation of carbon on the inner end of the porcelain id the shell, causing a short-circuit; broken porcelain; points irned too far apart to permit spark to pass.
- Q. When there is a hissing noise at the plug, or when oil uirted on it bubbles violently with the motor running, what does indicate?
- A. Either that the porcelain of the plug is not screwed down shtly on its gasket on the shell, the porcelain is broken, or the plug self is not tight in the cylinder.
- Q. What is the cause of a discharge across the porcelain of the ug?
- A. The points are too far apart, or the porcelain is broken; ually the former. This usually will be noted only on plugs having ry short porcelains as where the latter are long, the distance is uch greater than the maximum to which the points can be sepated and any spark that would occur owing to the latter cause ould take place at the safety gap.
- Q. Why is it that when a good spark will occur between the ints of a plug in the open air, an equally good spark cannot be tained in the cylinder with the same distance between the points the plug?
  - A. Compressing air increases its resistance to the electric



## Q. How rapidly do the electrodes of the spark plugs away, and what effect does this have?

A. This will depend upon the plugs themselves and the char of the current supply. The cheaper plugs with ordinary iror electrodes will burn away very rapidly, becoming much too w separated in a few weeks' use. With better grade plugs, using a alloy for the electrodes, the time will depend more or less o magneto, or where a storage battery is employed, on the coil. produce a very much hotter spark than others and, conseque burn the plugs away that much sooner; but a good plug ough to need adjustment under two or three months of ordinary run. The fact that the plug points have burned too far apart w evidenced by a very perceptible falling off in the power; by m spasmodically in different cylinders at low speeds; and by an sional discharge across the porcelain on the outside of the pluthe latter is of the short type.

# Q. What can be done when there is an escape of compre around the porcelain of the plug?

A. If the porcelain is not broken, this can be remedic turning down the gland or packing nut which holds the porcela the metal shell. There is an asbestos washer under this panut, and tightening the latter causes it to fill completely any between the porcelain and the shell. The nut should be given a fraction of a turn, and the tightening should be done when plug is cold; if it is tightened when very hot, the contraction d the cold is liable to crack the porcelain.

# Q. What is one of the commonest ways of breaking s plug porcelains?

A. The use of a big wrench in putting the plugs interplaced cylinders. Only a spark-plug wrench or a small wrench having a 3-inch or a 4-inch handle should be employed. The level available with the big wrench is so great that the porcelain is crufted frequently without the knowledge of the man using it.

### Q. How can a broken porcelain be detected?

A. Usually by grasping the plug between the fingers and ing to turn the porcelain sideways or to revolve it. Any pl generally an indication that the porcelain is broken, though s times they will loosen up so much under the influence of vibr

that they may be turned easily with the fingers. Tightening the packing nut will overcome this. Where this treatment does not locate a break, squirting a little oil on the porcelain while the motor is running will do so.

### Q. How long should a good plug stay in service?

A. This is hard to average, but with occasional adjustment of the points, a good plug will frequently continue to give satisfactory service for several thousand miles; some have been known to run for well over 10,000 miles, and still continue to operate satisfactorily. When the motor does not run properly and the plugs are suspected, it is better to try the effect of a new set and note the running of the motor carefully, before discarding the old ones, as the fault will frequently be found elsewhere. The first thing that many repair men do with a motor that is a bit off is to throw away a perfectly good set of spark plugs.

### Q. What is a "series"-type plug, and what advantages has it?

A. This is a type of plug fitted with two insulated terminals, instead of one, as in the ordinary type, as it does not make a ground connection on the motor by being screwed into the cylinder. It is intended to be used in series with an ordinary plug, hence the name. The current passes through the series plug first, and then, through the second plug of the ordinary type, to the ground, thus producing two sparks instead of one. The advantages claimed for its use are a more rapid and thorough combustion of the mixture, due to the spark occuring at two widely separated places in the combustion chamber; but, in actual practice, the gain is not sufficient to warrant the extra complication, so that this type of plug is seldom used.

# Q. What is the object of fitting a plug with several sparking terminals, or electrodes?

A. The current will always follow the path of least resistance and will accordingly bridge the smallest gap. The sparking will start at this gap and, when that particular electrode burns away, will shift to one of the others until that has also burned too far open, i.e., until its resistance becomes greater than that of the next one, and so on. Such a plug should stay in service longer without the necessity of adjusting the gap, but, apart from this, it has no particular advantage, as the short-circuiting of one of the gaps renders all of them useless.

- Q. What threads are generally used on spark plugs, and which thread is to be preferred, from the repair man's point of view?
- A. Half-inch iron pipe, metric and S.A.E. standard. Plugs with iron-pipe threads are employed only on the cheaper cars; metric-threaded plugs will be found on foreign cars only, and S.A.E. standard plugs ( $\frac{7}{8}$  inch-18) on most, if not all, of the better American cars dating from about 1913 on. All work equally well so far as holding compression is concerned. The iron-pipe plug is likely to cause trouble in this way sooner than the others, as they do not depend upon the thread itself to prevent leakage. The S.A.E. standard plug is preferable, being a better mechanical product than the iron-pipe plug as the threads of the latter are not so accurate, and the plug itself is usually not so well made.
- Q. When a spark plug leaks at the base, i.e., at the point where it is screwed into the cylinder, what is the cause?
- A. If of the iron-pipe type which depends entirely upon its tapered thread to hold the compression, a section of the thread may have been damaged in handling. With either of the other types, the plug may not be seated snugly enough on its gasket, in which case a quarter-turn in will usually remedy the leak. If it does not, the gasket should be replaced with a new one.
- Q. Is there any danger of turning an iron-pipe plug in too tightly?
- A. If screwed home too tightly while the motor is hot, the plug may bind and become very difficult to remove, sometimes necessitating drilling it out and re-tapping the hole.
  - Q. Is the priming type of plug of any particular advantage?
- A. On low-priced cars not fitted with pet cocks in the cylinders, it is an aid to starting in cold weather; though, as a matter of fact, the priming inlet of the plug is likely to become clogged with soot, so that it cannot be used for injecting gasoline into the cylinders.
- Q. Why has the magnetic type of spark plug not come into general use?
- A. It is an expensive type of plug to make and is more subject to derangement than the ordinary kind. It is only intended to be used with a low-tension magneto and plain-spark coil (single winding on an iron core), and this type of magneto has long since become obsolete on the automobile.

### Q. Is porcelain or mica preferable, as the insulator of the plug?

A. While mica is practically unbreakable, it is liable to become saturated with oil and dirt, causing leaks that are hard to trace; so that the use of porcelain is preferable, despite its liability to breakage.

# Q. Is changing from one make of plug to another likely to cause any difference in the running of a motor?

A. As the power of the motor is dependent, to a very large extent, upon the proper ignition of the charge, a change from one make of plug to another will sometimes make a very marked difference. Because of the great amount of variation in the width of the cooling jacket and the thickness of the cylinder walls, certain types of plugs are particularly adapted to certain makes of motors. In fact, the plugs have been designed especially for service on those motors. For example, some motors require an unusually long plug to permit of the sparking points extending well into the combustion chamber. In others, a plug of this type might interfere with the piston when at upper dead center. Always use the type of plug recommended by the manufacturer of the car.

## Q. What is the cause of the spark plugs in a motor becoming fouled very rapidly?

A. An excess of lubricating oil is finding its way into the combustion chamber, and its burning there deposits a heavy layer of carbon on the ends of the plugs. This may be due to leaky piston rings; the use of improper oil for the motor, as where a very light oil, instead of a heavy bodied lubricant is used in a motor intended for the latter; or, in old cars, the lack of baffle plates between the crankcase and cylinders. Running the motor with an over-rich fuel mixture will also cause sooting of the plugs. The use of a heavier oil and with it a certain proportion of flake graphite, or "Gredag", will often greatly improve the compression of an old motor and effectively remedy this trouble.

### Q. Is it advisable to use lubricating oil mixed with graphite in all old cars?

A. It is usually good practice, except on the Ford, as the magneto of the latter runs in oil splashed back from the crankcase, and the presence of graphite in this oil would short-circuit the magneto. In case this has been done on a Ford, it would be necessary to wash

the magneto out very thoroughly with gasoline to remove all of the graphite, and even that might not remedy the short-circ

- Q. When the plug in only one cylinder of a motor conti soots up very rapidly, what is the cause?
- A. That particular cylinder is being flooded with oil, a excess amount of it is reaching the combustion chamber. A ring may have broken in that cylinder, the rings may have v around until their openings are in line with one another, or the system may have become deranged, causing an excess of oil to the section of the crankcase directly under that cylinder.
- Q. Is there any way of knowing to a certainty before und ing an inspection, whether missing is due to a faulty plug or to derangement of the carburetor?
- A. If the miss continually occurs in the same cylinder, i be put down as due to the plug or wiring of that particular cy even though the plug, when tested from the outside (i.e., w removing it from the cylinder), is apparently working prowing the missing is spasmodic, occurring first at one cylinder an at another, it is more likely to be due to faulty carburetor adjus or a partially clogged carburetor nozzle. A weak dry be however, will produce similar symptoms; failing fuel supply als though, in this case, the whole motor will run jerkily one mospeed up the next, and then almost stop, only to repeat th formance.
- Q. Is the usual test, made by unclipping the secondary from the plug and holding it near the terminal with the moto ning, always conclusive as to the proper working of the plug, w spark occurs between the two?
- A. No. Since a short-circuited plug will not prevent a sparl passing between its outer terminal and the end of the cable helit. The gap made by disconnecting the secondary cable and h it a short distance away has simply taken the place of the gap should exist between the plug points. This test is conclusive as to the proper functioning of the distributor and the integrate wiring connecting that particular plug.
- Q. When the motor misses spasmodically, and there are mittent discharges of high-tension current at different points cylinders, while it is running, what is the cause?

- A. Moisture. The secondary cables have become wet enough to cause leakage of the high-tension current; usually the result of the careless use of the hose in washing. The only remedy is to run the motor continuously until the heat dries things out thoroughly.
- Q. When no spark plug is obtainable at any of the plugs, so that the motor cannot be started, in what order should the cause of the trouble be run down?
- If a dry battery is used as the source of current, first see that it is not exhausted by testing with a small ammeter. Each cell should show 10 amperes or more. If one is considerably below the others, it reduces them to its level. Where a storage battery is used. switch on the lights as a test. They should burn brightly. Provided there is no failure of the current, inspect the interrupter, or contact breaker; see that its points separate when the high part of the cam strikes the arm carrying the movable point. If they do not separate. no current is induced in the secondary winding, and an adjustment of the points, to open about the space represented by an ordinary visiting card, will remedy the trouble. If the points open properly, inspect the wiring and connections between the interrupter and the battery. Should both the interrupter and its wiring be O. K., note whether the ground connection from the coil is fast. Failing all of these, inspect the high-tension distributor. This is about the order in which the trouble would be likely to occur.
- Q. When the motor continues to run after the current has been turned off, what is the cause?
- A. The cylinders have become so hot, due either to lack of oil or or low water in the cooling system, failure of circulation, etc., that either the spark-plug electrodes have become red hot, or particles of carbon, deposited in the combustion chamber, have become incandescent, thus firing the charge. The fuel supply must be shut off and the motor allowed to cool.
- Q. Should the motor back-fire when attempting to start, even though the spark-advance lever has been pulled back as far as it will go, what is causing the trouble?
- A. The linkage connecting the spark-advance lever with the breaker box of the magneto or of the interrupter (battery system) has parted at some point, so that it no longer moves the breaker box to retard the time of ignition.

### REGULATION DEVICES Interrupters and Timers

### Q. How does an interrupter operate?

A. It is normally closed, short-circuiting the battery on the primary winding of the coil until just before it is necessary for the spark to occur in the cylinder; a cam then separates the contact points, and the high-tension current induced in the secondary winding of the coil jumps the gap of the plug. In the case of a magneto, the winding of the armature is short-circuited on itself to permit it to "build up", so that when the interrupter contacts are opened by the cam, the peak or highest value of the current wave generated is utilized. The opening of the circuit in either case occurs at the same time the distributor arm is passing one of its contacts.

### Q. How does a timer operate?

A. Contacts, insulated from each other, their number corresponding to the number of cylinders, are located at equidistant points on the inner circumference of the timer housing, while the shaft carries a single contact which in its revolution successively touches each one of the stationary contacts. Where separate vibrator coils are used, as on the Ford, each stationary contact corresponds to one of the coils.

# Q. Do interrupters and timers fail from the same causes, and what are they?

A. No. The cause of failure in one case is the reverse of that in the other. An interrupter fails when it does not open the circuit. and a timer when it does not close it. Dirt and wear are the usual causes of failure in both cases; moisture is also responsible at times. Test by having an assistant turn the engine over slowly by hand and watch the operation of the interrupter; if the cam fails to separate the contact points, true up their faces with fine sandpaper and test again. (This does not apply to Atwater Kent interrupters. See description.) Stop with the cam in the opening position and see if a sheet of ordinary paper can be slipped between the contacts. See that there is not an excess of oil in the housing, as oil on the contact point insulates them. In the case of a timer, see that the spring of the movable contact has sufficient tension to keep it pressed firmly against the stationary contacts as it revolves; note whether sufficient wear has occurred to cause poor contact even with sufficient spring pressure.

### Q. How far should the contacts of an interrupter separate?

A. This differs somewhat with different systems, but in the case of the interrupters used on battery systems, it is very small, seldom exceeding a few thousandths of an inch. In the case of the Atwater Kent interrupter, this is .010 to .012 inch. (Coated catalogue paper is .005 to .007 inch thick; a thin visiting card is .010 to .015 inch thick.)

# Q. How does the Atwater Kent interrupter differ from other battery interrupters?

A. The circuit is normally open and only remains closed momentarily before being opened by the dropping of the lifter into its notch on the shaft.

### Q. Can this interrupter be tested in the same way as that just described?

A. No. The movement of the lifter in striking the latch to close the circuit is so rapid that it cannot be detected with the unaided eye, even though the engine be turned over very slowly by hand.

### Q. What will cause this interrupter to fail?

A. Wear of the lifter to an extent where it will not engage the notches of the shaft properly, usually caused by lack of oil. Other causes of failure are the same as for other types, generally worn or burned contact points.

# Q. When the contact points of an interrupter of any type burn away very rapidly, what is the cause?

A. The condenser has broken down so that it is no longer protecting the points from the full heating effect of the arc formed at the time of breaking the circuit. Use the testing-lamp outfit described in connection with lighting and starting systems. Apply one point to each of the condenser terminals; if the lamp lights, the condenser is short-circuited. The only practical remedy is replacement by the manufacturer, as even the best equipped garage is seldom fitted to take care of such work.

# Q. Does discoloration always indicate burned contact points, and how often should these points require cleaning and adjustment?

A. No. According to the particular alloy used in the contacts they will assume a bright purple, an orange, or a gray tinge. The squareness of their surfaces and the contact they make when together are the best indications of whether attention is needed; if pitted or

high on one side, truing up will be necessary. Unless the condenser has failed, they should not require attention oftener than once a season, or say 6000 to 8000 thousand miles' running.

#### **Distributors**


- Q. What is the function of the distributor and how does it differ from that of the interrupter and timer?
- A. At the same moment that the interrupter opens the primary circuit of the coil, or the timer makes it in the case of a vibrating coil, the distributor makes contact with a stationary segment representing a spark-plug terminal. The distributor accordingly is said to run synchronously with the interrupter or timer. It is practically a duplicate of the timer designed to handle a high-tension current, in that it has one revolving contact and a stationary contact for each cylinder.
- Q. Does the moving member of a distributor actually make contact with the stationary contacts, as in the timer?
- A. No. This is not necessary owing to the high voltage of the current. The moving member passes very close to the face of the stationary contact but does not actually touch it, thus avoiding wear. This applies, however, only to those early-type magnetos or to separate distributors employing a metal moving contact. Where carbon brushes are employed, they are pressed against a fiber disc with a metal segment countersunk flush with its face and this segment passes under each carbon brush in rotation.
  - O. What are the usual causes of failure in a distributor?
- A. Short-circuits, due to moisture, dirt, or carbon dust. Owing to the high voltage of the current it will leak across barely perceptible paths caused by dampness or carbon dust.
- Q. What is the so-called ignition unit of the modern battery system?
- A. This is a combined contact breaker and distributor similar to the contact breaker and distributor of a magneto—in other words, a magneto minus the current-generating end. It is mounted on a vertical shaft and is driven through bevel, or helical gearing, from either the camshaft or one of the auxiliary shafts of the engine (i.e., water pump or magneto-drive shaft). The contact breaker is placed directly below the distributor, the secondary cables coming out of the upper face of the latter. (See description of Westinghouse and Connecticut units.)

### Q. What is the "unisparker"?

A. This is the Atwater Kent ignition unit and is similar in genal design to those referred to above but it is an "open-circuit" type, nile they are "closed-circuit". The term is a trade name derived om the fact that the contact breaker makes but a single spark, as mpared with the vibrator coil which produces a series of sparks by one of which, however, is available for ignition. All contact eakers on magnetos and, as now used, on modern battery systems, oduce but a single spark. The time of ignition is so limited on a gh-speed engine, that, if this single spark fails to ignite the charge in e cylinder, subsequent sparks are of little value, as the piston is ready well down on the firing stroke by the time a later spark occurs, d much of the force of the explosion is lost.

### Q. How is the time of ignition advanced and retarded on the nition unit?

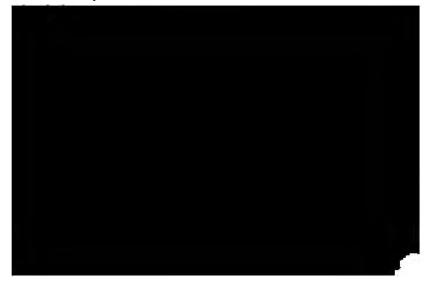A. Usually by altering the relation of the moving contact of the stributor to the stationary contacts. The distributor plate, i.e., e insulating disc carrying the stationary contacts is connected to e spark-advance lever on the steering column, and it may be moved rt of a revolution backward or forward to advance or retard the ne of ignition. To alter the timing, the position of the moving ntact on its driving shaft may be shifted. For example, in the elco distributor a central screw in this member is loosened, and e contact may then be moved in either direction with relation



- A. Poor contact due to wear or weakening of the spring; broken or frayed connections causing a ground or short-circuit.
  - O. What is an automatic switch?
- A. This term is frequently applied to the battery cut-out of the lighting and starting system. On the Connecticut ignition system, it is a thermally operated switch, designed to open the circuit when the switch has inadvertently been left on after the engine has stopped.
  - Q. Are there any troubles peculiar to automatic type of switch?
- A. None that is not equally so of any similar device such as the battery cut-out or the circuit breaker.

#### Coils

# Q. How many different types of coils are employed in connection with ignition systems?

A. Three. The first and simplest of these is usually termed a spark coil, and consists of a single winding of coarse wire on a heavy iron wire core. It acts by self-induction, the circuit remaining closed long enough to permit the core to become thoroughly magnetized; the energy thus stored in the core being released when the circuit is broken again. This gives increased voltage at the spark plug and causes an "arc" rather than a spark at the latter when the terminals of the plug are separated. This type of coil is only employed in connection with low-tension or mechanically operated spark plugs, and this system is now used on stationary engines and motor boats exclusively, having long since become obsolete on the auotomobile.

The other two types are known as induction coils, and differ merely in one being fitted with a vibrator while the other does not require this attachment to operate it. The induction coil is a miniature step-up transformer. It consists of a core of iron wires on which the primary of two or three layers of No. 16 or No. 18 wire is wound almost the full length of the core, and a secondary of many thousand turns of very fine wire, such as No. 36 or 38 B. & S. gage, or even No. 40, which is almost as fine as a hair. In coils of the best construction, this fine wire is wound in pancakes, or narrow sections, several of which are necessary to complete the secondary. Their terminals are connected in series thus making practically a single winding. Heavy insulation is placed between the primary and secondary windings, and the containing case is usually filled with an insulating compound melted into it and becoming solid when cold.

- Q. Why is an induction coil termed a "step-up" transformer?
- A. It literally steps up or raises the voltage of the current sent rough it. The primary winding is connected to the source of curnt and the secondary to the spark plugs through the distributor.
- Q. Is the action of the coil based on the same principle as that ilized in generators and motors?
- A. The principle of induction, as explained in Part I, is e same in all three, though it is utilized in a different manner in e induction coil. Instead of a moving coil of wire cutting the lines force of a magnet, impulses are produced either by sending a pulting current through the primary winding or by using an alternating rrent.
  - Q. How is this pulsating current produced in the primary?
  - A. By placing a vibrator in series with the primary winding.
  - Q. Of what does the vibrator consist, and how does it act?
- A. It consists of a spring-hinged armature and a pair of adjustole contact points, exactly as in an ordinary electric bell or buzzer, his armature is located directly over the end of the core of the coil and close to it. When a current passes through the primary winding, makes the core strongly magnetic and attracts the armature. This alls the latter away from the stationary contact point and breaks be circuit, so that the core is no longer magnetic. The spring mediately pulls the armature back and recloses the circuit, this tion taking place at high speed as long as the current is on.



vibrator coil very much slower in action than the other type, and this is greatly accentuated by a stiff adjustment of the vibrator spring.

- Q. Why is a vibrator necessary with one type of battery ignition and not with another, i.e., the so-called modern battery ignition?
- A. Owing to the type of timer or interrupter, frequently erroneously termed the "commutator", employed on the two systems.
- Q. What is the difference between the old-style timer and the modern interrupter?
- In the former, a long contact is provided for each cylinder and the revolving contact member is in touch with this for quite an appreciable period of time, during all of which the vibrator of a coil of that type is in action. If the contact member of the timer were depended upon to make and break the circuit through the coil to obtain the spark in the cylinder, the stationary contacts in the housing would have to be very much shorter, and no provision for advancing and retarding the time of ignition would be available. Furthermore, the wiping contact of the ordinary style of timer is not adaptable to the extremely rapid make-and-break that is necessary for this purpose. The interrupter of the modern battery system is designed along practically the same lines as the contact breaker used in the primary circuit of a high-tension magneto or the only circuit used on a lowtension magneto. Its parts are made very small and light and with great accuracy, so that its inertia is reduced to the minimum and it will act with extreme rapidity. The gap is so small and the rapidity of action so great that the movement is often not visible to the unaided It is practically a mechanical vibrator designed to give a single make-and-break at exactly the right moment as compared with the electrical vibrator, which must be started well in advance of the moment ignition is required, and which continues in action after the spark has occurred in the cylinder. Consequently, both the mechanical and the electrical lag, which make the vibrator coil comparatively slow in action, are reduced to a minimum, and the amount of current necessary is cut to a fraction of that required by the latter.
  - Q. How can the speed of operation of a vibrator be judged?
- A. By the note it produces in action. A low note well down the scale denotes slow action; the higher the note, or buzzing, the more rapid the vibrator is acting.

that they may be turned easily with the fingers. Tightening the packing nut will overcome this. Where this treatment does not locate a break, squirting a little oil on the porcelain while the motor is running will do so.

### Q. How long should a good plug stay in service?

A. This is hard to average, but with occasional adjustment of the points, a good plug will frequently continue to give satisfactory service for several thousand miles; some have been known to run for well over 10,000 miles, and still continue to operate satisfactorily. When the motor does not run properly and the plugs are suspected, it is better to try the effect of a new set and note the running of the motor carefully, before discarding the old ones, as the fault will frequently be found elsewhere. The first thing that many repair men do with a motor that is a bit off is to throw away a perfectly good set of spark plugs.

### Q. What is a "series"-type plug, and what advantages has it?

A. This is a type of plug fitted with two insulated terminals, instead of one, as in the ordinary type, as it does not make a ground connection on the motor by being screwed into the cylinder. It is intended to be used in series with an ordinary plug, hence the name. The current passes through the series plug first, and then, through the second plug of the ordinary type, to the ground, thus producing two sparks instead of one. The advantages claimed for its use are a more rapid and thorough combustion of the mixture, due to the spark occuring at two widely separated places in the combustion chamber; but, in actual practice, the gain is not sufficient to warrant the extra complication, so that this type of plug is seldom used.

# Q. What is the object of fitting a plug with several sparking terminals, or electrodes?

A. The current will always follow the path of least resistance and will accordingly bridge the smallest gap. The sparking will start at this gap and, when that particular electrode burns away, will shift to one of the others until that has also burned too far open, i.e., until its resistance becomes greater than that of the next one, and so on. Such a plug should stay in service longer without the necessity of adjusting the gap, but, apart from this, it has no particular advantage, as the short-circuiting of one of the gaps renders all of them useless.

pair noted. When the cylinder, or cylinders, at fault have been determined, adjust one at a time by releasing the lock nut of the adjusting screw of the vibrator and turning it up or down, according to whether improvement in running is noted, or not. Usually only a small fraction of a turn one way or the other will be necessary. Turn the screw very slowly and very little at a time and, when the proper adjustment of the screw has been secured, lock in place again securely. Ordinarily, the proper adjustment may be secured simply by noting the running of the motor. When all the cylinders fire regularly and without any apparent lag, the adjustment is considered correct. secure a finer adjustment, a small portable ammeter, reading by tenths to three or five amperes, may be used. Connect this in series with each one of the coils in turn, and note the reading at which the coil acts most rapidly. The other vibrators may then be adjusted to give the same reading. When dry batteries were relied upon for ignition, this test was employed to reduce the current consumption to the minimum but with the excess supply of current from the Ford magneto, this is not necessary, and the vibrators may be adjusted to the reading giving the most rapid action, regardless of the current consumption. This test may be employed also to check the operation of the magneto, as its current output may have fallen off to a point where it is no longer sufficient to operate the coils satisfactorily.

## Q. Why is a vibrator not necessary on the alternating current generated by the ordinary type of magneto?

A. The latter has but two field poles and a single coil on a two-pole armature, so that its cycles are very much fewer in number, and there is definite drop in the current, from the maximum to an absolute zero, twice in every revolution. Assuming a speed of 1200 r.p.m., the ordinary magneto would be running 600 r.p.m., as it is driven by a half-time shaft of the motor. This is 10 revolutions per second times 2 cycles per revolution which gives an alternating current of but 20 cycles, or one which would cause an incandescent lamp to flicker very badly. The Ford magneto, on the other hand, is directly on the crankshaft. Consequently, it is turning 20 revolutions per second, and its coils produce 16 cycles per revolution, or 320 cycles per second, equivalent to 19,200 cycles per minute. For ordinary commercial lighting, only 60 cycles per second are necessary to produce a steady light. The drop to zero in the current curve of the ordinary

agneto permits the core of the coil to become demagnetized, and it then remagnetized by the subsequent rise to the maximum value the other direction, so that no vibrator is necessary to accomplish is alternate magnetizing and demagnetizing of the core which is eded to produce the inductive effect in the coil or transformer.

### Q. How many connections are there on a coil?

A. Three; one to the primary, from the battery or magneto; ie from the secondary, to the distributor, in the case of a single coil, to the spark plug in the case of a multiple coil; and one to the ound. The last named is referred to as a common-ground connection, as it grounds one side of both the primary and secondary windges of the coil.

#### Q. How are these connections made?

A. On the single non-vibrator coil, as used with an ordinary agneto, by means of wire cables from the magneto to the primary the coil, from the secondary of the latter to the high-tension distibutor. In the case of the Ford multiple-vibrator coils, each coil an independent unit, having brass strap connections attached to the ottom of the coil-unit case. These straps are of spring brass and ey bear against corresponding plates of brass in the bottom of the bil box fastened to the dash. Simply lifting the coil unit out of the box breaks the connection and automatically remakes it when the bil is replaced. Due to this type of connection, irregular firing of the Ford motor will frequently be found to result from the cover of



Should it fail to do so, the covers of the coil may be removed to note if a wire has broken just beneath it. This is most likely to be the case with the secondary, owing to the very fine wire used. If there is no break, either at this point or where the primary lead is connected to its winding, it will be necessary to return the coil to the manufacturer as there is an internal short-circuit, which cannot be repaired in the garage. The only difference between the method above outlined for a single coil and that of a unit-vibrator coil as used on the Ford, is to touch the test points to the brass strap connections representing the different windings.

- Q. Why is but one coil used in connection with an ordinary magneto, while four are employed on the Ford?
- A. Where a single coil is used, the secondary current is led to a distributor from which it is again led to the various spark plugs in the proper order of firing. No distributor is employed on the Ford, so that a vibrator coil is necessary for each cylinder. The connections from the coils to the plugs are made in the same order as they would be to a distributor.
- Q. When a vibrator coil cannot be made to function properly by adjusting the contact screw, what should be done?
- A. The contacts should be trued up with a very fine file, as failure to function will usually be caused by their having become badly burned away or pitted, thus making poor electrical contact. Where the above is the case and the contact points are square and true, it is only necessary to clean them by drawing a worn piece of fine sandpaper between them several times, first on one side and then on the other. See that none of the holding screws of the vibrator frame have become loosened, and that the lock nut of the movable contact holds the latter firmly in place when tightened up.

#### **IGNITION BATTERIES**

- Q. What types of batteries or cells are used for ignition?
- A. Dry cells and storage cells, or accumulators. (For queries on the latter see under "Battery" in Lighting and Starting Section.)
  - Q. What type of cell is the so-called dry cell?
- A. It is a primary cell, i.e., one in which a current of electricity is generated by chemical reaction, and is technically known as an "open-circuit" battery.


# Q. Of what does the dry cell consist, and how much current es it generate?

A. The elements are the zinc container and a carbon plate cenally placed in the container and insulated from it at the bottom. ound this carbon plate, which constitutes the negative element ne negative element in a primary battery carries the positive termil and vice versa), is packed a depolarizing agent, usually dioxide of anganese. The active solution is sal ammoniac in water which is ured in after the cell is assembled and filled with the depolarizer, d then the cell is sealed at the top with pitch, so that it is dry in me only. No chemical action can take place without the presence moisture.

A dry cell of the ignition type generates a current of 20 to 25 peres (when new) at a potential of 1½ volts.

### Q. Why is a depolarizing agent necessary?

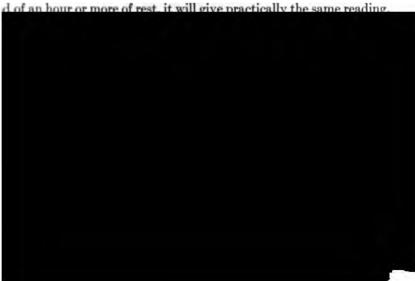A. The action of the cell generates hydrogen gas, which quickly vers the carbon plate in the form of globules, rendering it inactive. he cell is then said to be polarized, and the current generated drops is very rapidly. This may be illustrated by placing an ammeter ross the terminals of a new cell. The ammeter reading will remain 20 amperes for a short time and then will quickly drop until, at the d of five minutes, the instrument will show scarcely any reading at l. If the connection is broken and the cell allowed to stand for ten inutes, it will again show almost as high a reading as before; at the dof an hour or more of rest, it will give practically the same reading.



may be used as the main source of ignition current; as this intermakes instantaneous contact only at the moment the sp required in the cylinder, the battery otherwise being on open a

- Q. How can the life of such a battery be prolonged?
- A. By connecting two or more sets of four cells each in multiple, i.e., each group of four is connected in series to gi required voltage, and the positive and negative terminals of group are connected together. The amount of current then from each cell is only one-half what it would be if a single set were employed, or one-third what it would be where sets series-multiple, and so on.
- Q. When a set of four dry cells will last a certain length o why is it that adding extra cells in series, for example, a stattery, will not last longer?
- A. The amount of current drawn from the cells when t cuit is closed depends upon the voltage of the entire series, as greater the total voltage the larger the volume of current, in a ance with Ohm's law. Consequently, the six-cell battery w last so long as the four on the same service.
- Q. Why is it not good practice to connect an old set (cells in series-multiple with a new four-cell battery, or grouneven numbers in the same manner, as for instance, three and four in another?
- A. The new cells will have an output of twice that of t ones, so that when the circuit is closed they will discharge the latter until the amperage of all is equalized. Where the numbers are used in groups in series-multiple connection, the age of the larger will be superior to that of the smaller, and a action will take place on open circuit so that in a short time maximum potential of the battery will be that of the weakest
- Q. Why should one cell much lower than the others be included in a dry-cell battery?
- A. For the reason just given above, as well as the fact t exhausted cell increases the resistance of the battery as a and decreases the current.
- Q. Why will the dry-cell battery used on a dual i system not run the engine satisfactorily for any length of time the magneto is not in proper working order?


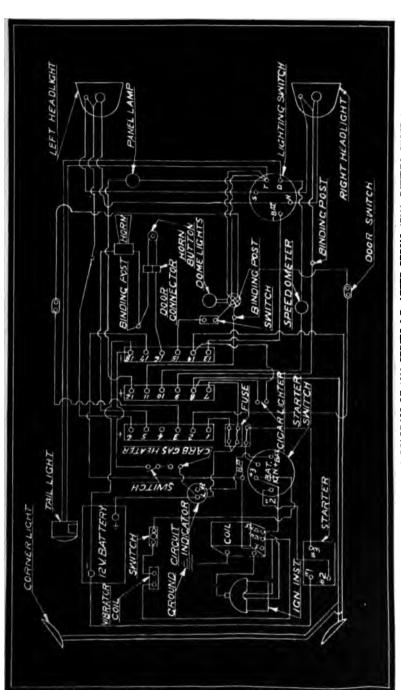


PLATE 65-PRANKLIN WIRING DIAGRAM OF 1990 SERIES 9-B, AFTER SERIAL 17900, DYNETO SYSTEM

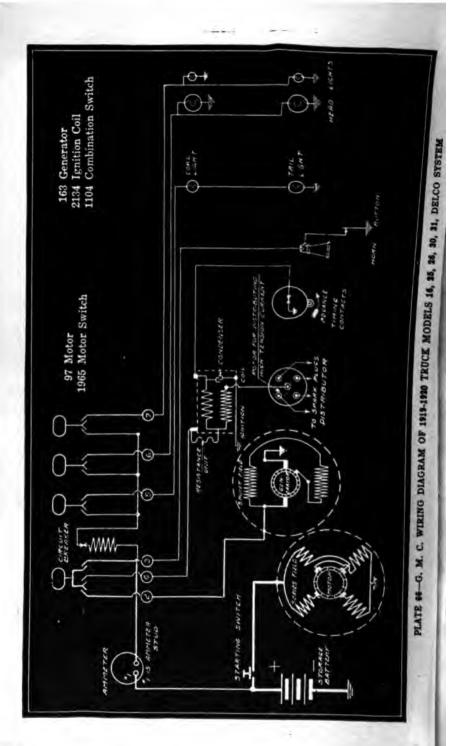



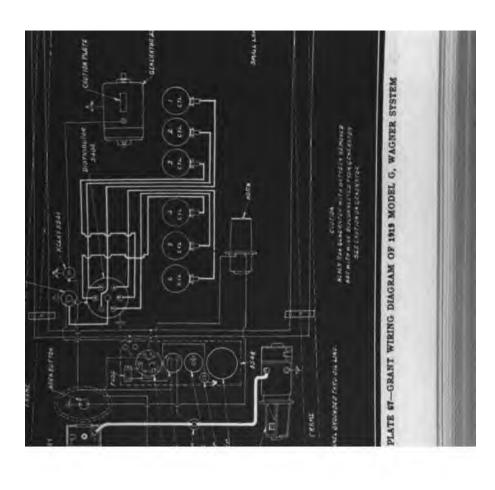


PLATE 58-HARROUN WIRING DIAGRAM OF 1818 MODET ANY SYSTEM

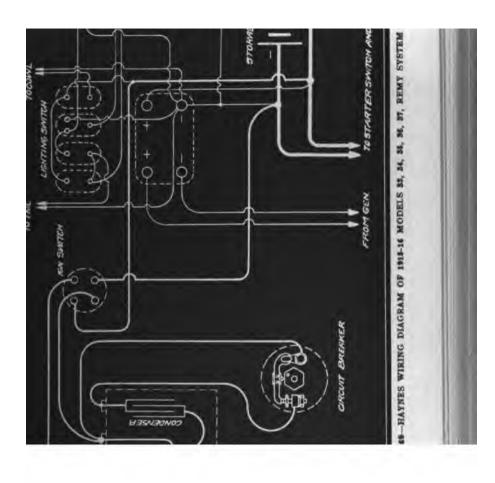

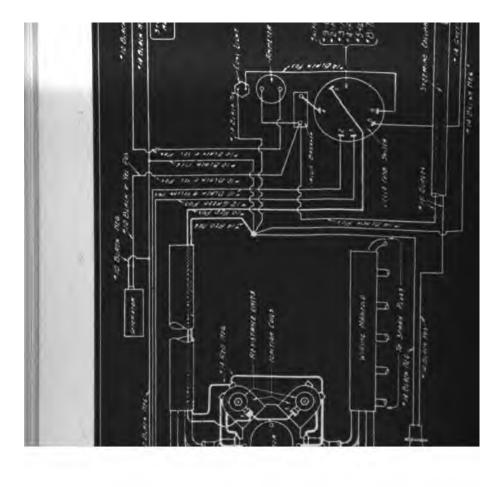


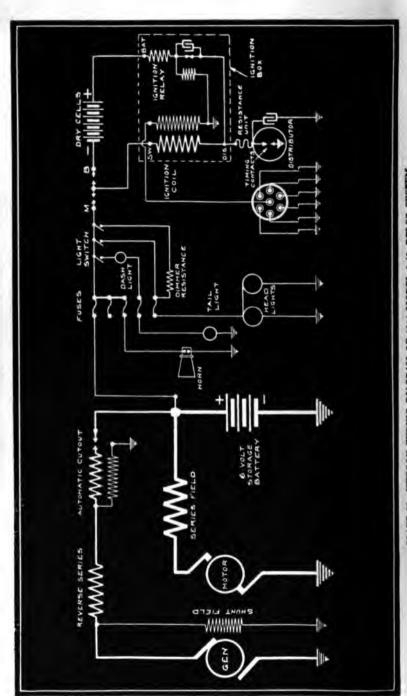


PLATE 72-HUDSON WIRING DIAGRAM OF 1914 MODEL 6-40, DELCO SYSTEM

PLATE TE-HUDSON WIRING DIAGRAM OF 1914 MODEL 6-84, DELCO SYSTEM

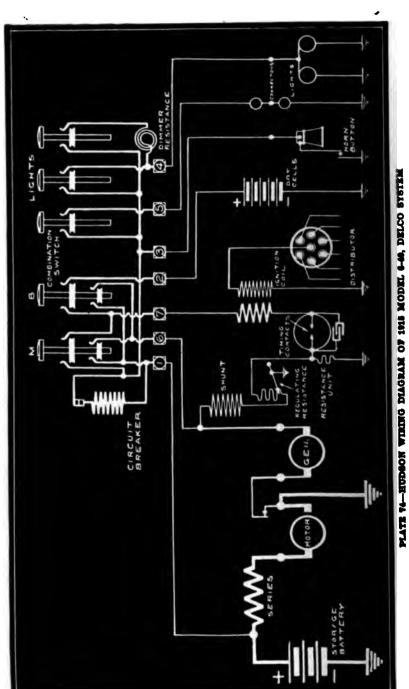




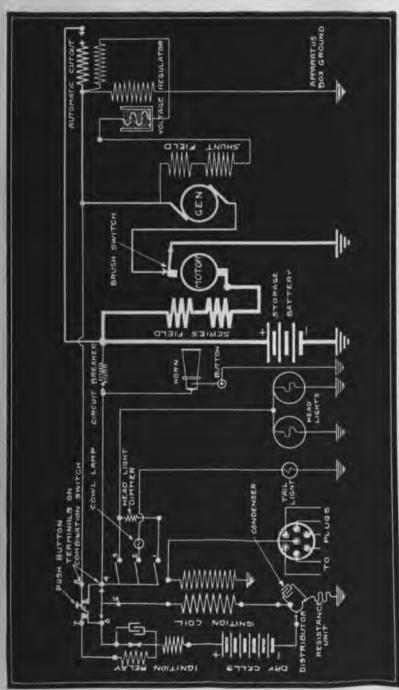


PLATE 15-HUDSON WIRING DIAGRAM OF 1915 MODEL 6-54, DELCO SYSTEM

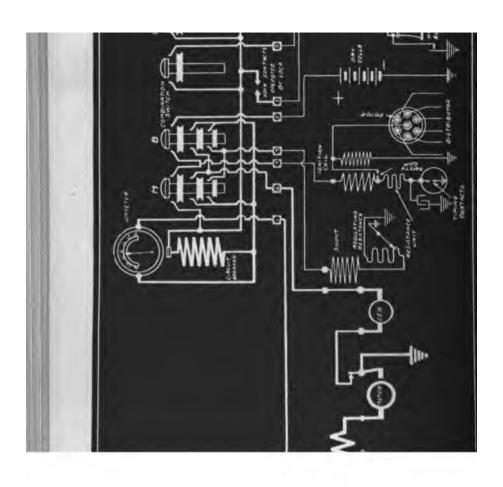

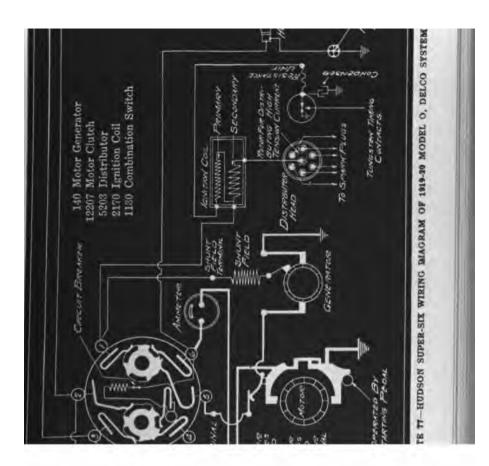

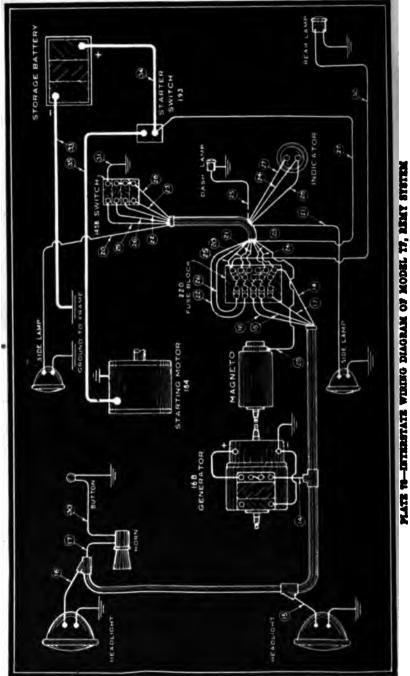

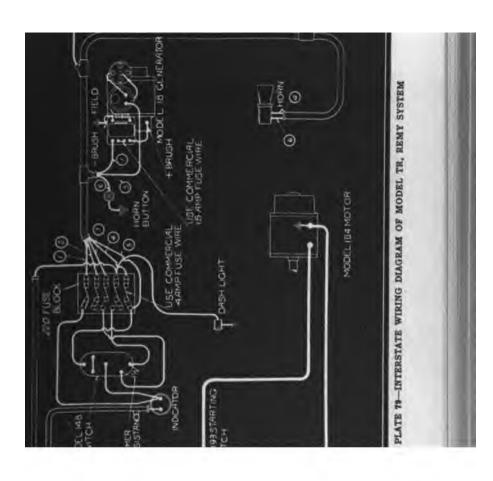


PLATE AS LACKSON WIRING DIAGRAM OF 1915 MODRIS 48, 6-40. DRICO SYSTEM

- A. Because the interrupter, or contact breaker, of the magneto of the elosed-circuit type, thus drawing current continuously, cept when the points open to break the circuit and induce a high-naion current in the secondary of the coil. In a system of this type, e dry cells are intended only for starting purposes.
- Q. Why can a modern battery system not be used with dry
- A. Because the interrupter is of the closed-circuit type, similar that of the magneto, and the demand for current (usually about 3 aperes) is practically constant. It is not so much the amount of rrent required that affects the dry cells, as the fact that they are most constantly on closed circuit, so that there is no opportunity r the depolarizing agent to work. This demand on the storage terry of the starting and lighting system (usually of 80- to 120-apere-hours capacity) is negligible. At a 3-ampere discharge te, the larger battery when fully charged and in good condition puld be capable of giving practically forty hours of continuous rvice. Under the same conditions, new dry cells would not prode efficient ignition for more than an hour.
- Q. Does the voltage, as well as the amperage, of the dry 11 fall off on closed circuit?
- A. The voltage is affected very slightly; a cell that is practically hausted will show almost 1½ volts so that a voltmeter test is no dication of the condition of the cell.

#### FORD IGNITION SYSTEM

While a great many of the causes of missing or breakdown, in e ignition system covered by the foregoing queries, apply to a great tent to all cars, such as loose wires, short-circuits and the like, the ord system is distinctive. It is based on the same fundamental inciples, of course, but it has many features not to be found on her cars so that there are causes of failure that could never be adily determined by experience gained on other makes of machines, ough long handling of ignition apparatus would naturally be of eat assistance. In working on the Ford ignition system it must be one in mind that it is a combination of the old-time battery system the amodern generator as the source of current supply, so that the any defections due, in the earlier days to the dry battery, are now eking.

### Q. Of what does the Ford ignition system consist?

- A. A multipolar alternating-current generator (magneto) built integral with the flywheel; a primary, or low-tension timer, in which a roller makes contact with the four stationary segments in the housing; four vibrator coils, one for each cylinder, plus the usual number of spark plugs and connections in the primary and secondary circuits.
- Q. Is the Ford ignition system efficient and reliable, or is it advisable when much trouble is experienced with it to replace it with any of the numerous accessories and complete ignition systems that are claimed to be improvements?
- A. While there are many ignition systems the parts of which are made with greater precision, and some in which the design and particularly the accessibility of the important essentials are superior, experience has proved the Ford system to be both efficient and reliable. With proper care, there should never be any necessity for replacing it with any system made by an accessory manufacturer, or for adding to it any one of the legion of devices advertised as improvements on it.

#### Timer

## Q. What are some of the commoner causes of failure of the Ford system?

A. One of the most frequent is due to the timer and is caused by failure to lubricate it. Contrary to the usual practice, which is to prevent oil getting on the contacts of a timer as it tends to insulate the latter, the Ford timer requires plenty of oil, and should be lubricated every day. There is no fear of giving it too much oil as the excess will leak out of the housing; it will continue to operate satisfactorily even though flooded with oil, while the slightest lack of it will cause trouble.

### Q. What is the nature of the trouble caused by the timer?

A. If not oiled at regular intervals, it will cause missing of various cylinders, and those that do fire will be late, as if the ignition were fully retarded, so that the motor develops very little power. An accumulation of gummed oil and dirt will produce a similar result. The timer housing should be taken off and the contacts cleaned; the roller contact also should be cleaned by squirting gasoline over it and wiping over well.

### O. Will lack of oil have any other result?

A. Besides the missing, usually most noticeable at higher eeds, failure to lubricate will result in very rapid wear of both the ller and its track (contacts in the stationary housing) so that its ceration will soon become unsatisfactory, even though subsequently ept oiled.

# Q. What are some other causes of faulty operation of the ner (generally referred to as a commutator)?

A. Weakening of the spring which holds the roller against its ack will cause missing at low speeds, while a loosening of the spring nich holds the timer housing in place is liable to cause erratic firing all speeds. This spring is held by a single cap screw passing rough the breather tube, which serves also as an oil filler for the ankcase. At its inner end it has a small boss which fits in a corsponding depression in the hub of the timer housing. This is the dy thing that holds the latter in place. The loosening of this cap rew is liable to let the housing drop out of place sufficiently to prent the roller making contact with all of the segments.

### Q. Does the weather have any effect on the operation of the ner?

A. Unless precautions are taken to lubricate it properly, cold rather will make starting difficult. This is due to ordinary lubriting oil becoming congealed in the housing, thus preventing the ller from coming into good contact with the segments. An indi-

tion of this sometimes is that the motor will fire only on two or

the brush points upward. This may be determined by removing the valve mechanism cover and noting the operation of the valve in question.

- Q. If parts show much wear, what should be done?
- A. Replace them; as they cost so little that it is far less expense to put in new parts than to attempt to make old ones serve by truing them up.
- Q. When examination reveals gummed oil and the weather is cold, what should be done?
- A. Clean out the housing and the roller-contact parts with gasoline, and use a mixture of  $\frac{1}{4}$  kerosene and  $\frac{3}{4}$  lubricating oil in the timer, as long as the weather is cold.
- Q. What other causes of trouble with the timer are more or less common?
- A. Short-circuiting of the primary wires which lead to the timer, or the loosening of these wires at the terminals on the housing. The position of the timer is such that the insulation of these wires is subjected to considerable wear by reason of the movement of the housing in advancing and retarding the time of ignition. The best method of remedying this is to replace the entire set of primary wires.

#### Vibrator Coils

- Q. Is irregular firing likely to be caused by any other part of the system than the timer?
- A. The vibrators of the induction coils may get out of adjustment and cause either erratic firing, or missing of one or more cylinders altogether, in case one or more vibrators cease to operate.
  - Q. How can this be determined?
- A. Run the motor slowly and watch the action of the vibrators; they should act regularly and with the same rapidity in each case, any stuttering or hesitation indicating either poor adjustment or points in poor condition.
- Q. How can the vibrators be utilized to determine which cylinder is missing, where the cause lies in some part of the system other than the vibrators themselves?
- A. Hold one vibrator down at a time with the finger; if the remaining three cylinders fire regularly, the one represented by the vibrator being held out of action is the one at fault. The cylinder can always be located quickly by holding down each vibrator in turn.

- Q. When the cylinders do not all fire regularly, but there is no perceptible difference between the action of the vibrators, how can the cylinder, or cylinders, at fault be determined?
- A. Hold down the vibrators in pairs, taking first Nos. 1 and 4, and then Nos. 2 and 3. This will cause the engine to run on two cylinders at a time, and any difference between the operation of the two pairs or between members of each pair will be apparent.
  - Q. What is the firing order of the Ford motor?
  - A. 1-2-4-3.
  - Q. How are the coil vibrators adjusted?
- A. The usual method is to turn the adjusting screw up until the vibrator stops buzzing; then turn the screw down again very slowly until the points just come together and the firing of that cylinder becomes regular; then give the screw an extra quarter-turn down, and lock in place.

In adjusting K-W coils, it is important to see that the little flat-cushion spring just underneath the vibrator bridge works back and forth every time the points make and break contact. This can be determined by taking the coil unit out of the box and holding the vibrator up to the light; press down the vibrator and observe the action of the cushion spring. It is important to adjust all the units alike or the motor will not develop its full power.

- Q. What is the effect of adjusting so that the contact points are too far apart; too close together?
- A. If too far apart, the cylinder will not fire regularly or with its usual power. If too close together the current is likely to arc at the contact points, thus preventing the breaking of the circuit when the armature is drawn down, burning the points themselves, and sometimes putting the coil out of action entirely.
  - Q. Does the vibrator adjustment affect starting?
- A. When the points are too close, more current is required to "make and break" the contact between them, and the motor must be turned over that much faster. For the best adjustment, the points should barely touch. If the adjustment is too light, they may not do this and a miss at that cylinder will result.
  - Q. If the vibrator buzzes constantly, what is the trouble?
- A. There may be a short-circuit at the timer or in the wire leading from that coil to it, or the coil itself may be defective. One

of the first symptoms of a defective coil is the buzzing of the vibrator, with no spark at the plug.

- O. How can a defective coil be determined?
- A. To make certain that the cause is in the coil, change the location of the units in the coil box. If another unit acts the same when substituted for the one giving trouble, the fault is not in the coil but in some other part of the system. Should the coil that is shifted, however, act the same in its new location, and the one that takes its place operates properly, the coil itself causes the trouble.
- Q. When there is an unusually heavy or "fat" bluish spark at the contact points, what is the cause?
- A. The current may be arcing at the points, due to their being adjusted too closely; or the condenser may have broken down. To make certain that the condenser has failed, disconnect the secondary cable from the spark plug and hold the terminal about  $\frac{1}{32}$  inch away from the metal end of the plug. If the condenser has failed, the spark occurring at this gap will be irregular.
- Q. What will happen if the contact points are allowed to become pitted and ragged, due to the burning effect of the current?
- A. They are liable to stick together and cause unnecessary difficulty in starting or occasional missing when running. They should be trued up with a very fine flat file or with an old piece of fine sandpaper. Never use emery.
- Q. When the vibrator points burn badly in a very short time, what is the cause?
- A. The owner of the car has probably replaced the original vibrators with cheaper substitutes having nickel or German-silver contact points. Nothing but platinum or platinum-iridium contacts will give satisfactory service, so that new parts from the makers should be installed.
- Q. When the engine will suddenly lag and pound, what is the cause?
- A. An intermittent short-circuit in the wiring or at the commutator. The pounding is caused by the premature explosion of the charge against the rising piston. The vibration causes the short-circuit to occur at some times, and not at others, so that the engine will run regularly for a few minutes and then pound again, until the movement once more temporarily eliminates the cause.

- Q. With all the vibrators properly adjusted and the timer and wiring in good condition, what is the cause of irregular firing?
- A. Provided the spark plugs are all in good condition, points not too far apart, etc., this is frequently caused by the top of the coil box coming loose. The coil units are provided with brass-strap terminals on the bottom of the wooden casing of the coil, and these terminals make contact with similar straps in the bottom of the coil box on the dash. They depend for good contact on the pressure exerted by the cover of the box, which must always be kept tightly snapped on.
- Q. When missing is not traceable to any of these causes, what is likely to be the cause?
- A. Something outside of the ignition system, such as a weak-valve spring, or a valve improperly seating, due to some other cause. Loss of compression at the cylinder-head gasket: run a little lubricating oil along the edge of the gasket and note whether bubbles appear. Replace with a new gasket if any leakage is apparent.

Magneto

- Q. How does the Ford magneto differ from the regulation type?
- A. The magnets are revolved instead of the armature; it has sixteen field poles and armature coils, and it revolves at crankshaft speed to fire a four-cylinder motor. It is not timed to the motor the same as an ordinary magneto, which is coupled to the camshaft, or other half-time shaft, and the distributor of which must rotate synchronously with the motor.
  - O. Of what does it consist?
- A. Two discs, one carrying sixteen magnets with their poles pointing outward, and the other sixteen coils of strap copper on oval cores, all of the coils being connected in series. The disc carrying the magnets is rotated by the flywheel to which it is attached, while the other disc is attached to the crankcase, and remains stationary. One end of the coil winding of the magneto is grounded on the supporting disc carrying the coils, while the other is led to a terminal which extends through the flywheel housing. A cable from this terminal or binding post, supplies current to the coils.
- Q. Is it ever necessary to remagnetize the magnets of the field, and how can it be done?

- A. Unless they have become demagnetized, due to some outside influence, it is rarely necessary to touch the magnets.
  - Q. How can they become demagnetized by an outside force?
- A. The attachment, by mistake, of a storage battery to the magneto terminal will send a current through the coil windings in the opposite direction, and will demagnetize them. When this happens, it is not advisable to attempt to remagnetize the old magnets, as it is much cheaper and quicker to replace them. The new set is supplied mounted on a board in exactly the position they should be installed.
  - Q. How can the magneto be dismounted?
- To do this, it is necessary to remove the power plant from the car. The radiator must be taken off by disconnecting its stay rod and taking out the two holding bolts at the frame, after uncoupling the hose connections. Remove the dash and loosen the steering-post bracket, fastened to the frame, permitting the dash and steering gear to be lifted off as a unit (wires having first been disconnected); take out bolts, holding front radius rod in socket underneath the crankcase; remove four bolts at the universal joint; remove pans on either side of cylinder casting; disconnect feed pipe from carburetor, and exhaust manifold from exhaust pipe, by unscrewing large brass nut; remove the bolts which hold the crankcase arms to the frame at the side; then pass a rope through the opening between the two middle cylinders, and tie it in a loose knot; through the rope pass a 2 by 4 timber or a heavy iron pipe about ten feet long; with a man at each end of this and a third at the starting crank, the whole power plant can readily be lifted out; then remove the crankcase and transmission cover, and take out the four cap screws that hold the flywheel to the crankshaft. This gives access to every part of the magneto mechanism. To take out the old magnets, simply remove the cap screw and bronze screw which holds each in place. When reassembling the magneto, great care must be taken to see that the disc or plate carrying the magnetos revolves them exactly  $\frac{1}{32}$  inch of the core faces of the coils.
- Q. How can it be determined whether the magnets are at fault or not?
- A. Whenever there is a partial failure of the current, remove the binding post by taking out the three screws which hold it in

ed under the contact spring. If this does not materially improve a running, test by comparing with battery ignition. Connect a terminal of a six-volt storage battery to the battery terminal the coil box (a battery of four or five fresh dry cells will serve ually well for a short test run), and ground the other terminal of a battery on the frame of the car, making certain that good electrical nnection is made. Run the engine at different speeds on the agneto, and, while running, throw the switch over suddenly to a battery point; any decided acceleration in the speed will indicate at the battery is supplying a much better current for ignition, and that the magneto is at fault. If used for any length of time for sting, a dry-cell battery will not give equally accurate results, as a cells are likely to run down very quickly, and the firing will then better on the magneto, even though the latter be weak.

- Q. When the engine suddenly fails to fire altogether, what is iely to be the cause?
- A. The cable leading from the binding post on the magneto s dropped off, either at the latter or at the coil; or some piece of reign matter has come between the contact spring attached to the ading post and its contact.
- Q. When the magneto gradually gets weaker and weaker in car that has seen a great deal of service, is it certain that the agnets have weakened?



connected at either end; in a dual system, the primary cable from the magneto to the coil may become disconnected, either at the magneto or at the coil; the secondary cable from the coil to the magneto distributor may loosen and drop off, either at the coil or at the magneto; this secondary cable may become grounded between the coil and the magneto: the switch may have loosened up, through vibration, and may jar open; the magneto may have become grounded internally, so that no current is delivered to the outside circuit. The magneto cam may have loosened up on its shaft, so that it no longer revolves with the latter, and, consequently, does not open the contact points in the breaker box. The primary cable from the magneto to the coil may have become grounded on the frame or short-circuited on another cable, due to wear from chafing, thus preventing the current from reaching the coil. In a dual system. the entire system may have become grounded through the metal of the dry cells coming in contact with the metal battery box or other metal part connected to the chassis of the car.

## Q. Do the foregoing constitute all of the possible causes for a sudden failure of the ignition system?

A. No brief résumé could possibly include all of the causes that may exist for a stoppage of this kind, but they include probably more than 90 per cent of all the commoner causes of such a failure, and, either as given above, or in some modified form of the same condition, will be found to represent by far the greater part of all the causes of sudden stoppage.

# Q. Of the causes given above, which are the most likely, in the order of their usual occurrence?

A. The loosening of a battery connection at the terminal or at the coil, or of a magneto and coil connection at either end; grounding or short-circuiting of either the primary or secondary main connection between magneto and coil, that of the secondary being more frequent owing to the high-tension current it carries. Grounding of the dry cells in the battery box; loosening of the switch so that it jars open. With the exception of the grounding of the primary or secondary cable between the magneto and the coil, all of the above are the direct result of vibration and jarring. In old four-cylinder motors, vibration is constant, and at times very severe, so that attention should first be directed to searching for loose con-

nections, as unless tightened up at intervals, they are very likely to shake off. Internal grounding of the magneto or loosening of the breaker-box cam, so that the interrupter does not operate; these are rarer causes of trouble, and a search for them should be deferred until after the commoner causes mentioned above have been thoroughly investigated.

- Q. Where all connections have been tightened up without overcoming the trouble, how can the other possible causes of stoppage be eliminated, in tracing the real seat of the failure to run?
- See that the dry batteries of a dual system are not touching any metal; inspect the magneto breaker box while another person slowly turns the motor over by hand, so that the operation of the interrupter may be noted. If working properly, disconnect the secondary cable from the magneto to the coil, and with the motor running, hold its terminal 1 inch away from the coil connection. In case there is no fault here, a bright spark will result at the gap. Note whether holding the cable away from the motor has been responsible and whether, when it is dropped back on the motor again, sparking occurs at any point along its length between the cable and the metal of the motor. Disconnect the primary cable from the magneto to the coil, and, with the motor running, wipe its end on the primary terminal of the coil; sparking should result if there is no break in the cable. Take the same precaution in putting it back as with the secondary cable to see that it is not grounding at some place along its length where it touches the motor. No visible spark will be produced in this case, but the condition of the insulation of the cable itself should be the best indication of this kind. Bend the wire along its length to detect any possible breaks in the copper wire under the insulation. Disconnect the ground cable from the coil to the magneto, and, while the motor is running, hold it close to either the magneto or the coil terminal; a high-tension spark will result if the cable is all right. Note, while the motor is running, whether there is any sparking at the safety gap, on the magneto itself, if on the high-tension type, or on the coil of a dual system. Note whether the primary and secondary cables cross each other, and whether there is any sparking between the two while the motor is running. Inspect the ends of all stranded cables carefully, and see whether one or more of the fine wires have not broken through

connected at either end; in a dual system, the primary cable fr magneto to the coil may become disconnected, either at the n or at the coil; the secondary cable from the coil to the n distributor may loosen and drop off, either at the coil or magneto; this secondary cable may become grounded betwee coil and the magneto; the switch may have loosened up, t vibration, and may jar open; the magneto may have become gr internally, so that no current is delivered to the outside The magneto cam may have loosened up on its shaft, so the longer revolves with the latter, and, consequently, does no the contact points in the breaker box. The primary cable fr magneto to the coil may have become grounded on the fr short-circuited on another cable, due to wear from chafin preventing the current from reaching the coil. In a dual : the entire system may have become grounded through the of the dry cells coming in contact with the metal battery other metal part connected to the chassis of the car.

# Q. Do the foregoing constitute all of the possible cau a sudden failure of the ignition system?

A. No brief résumé could possibly include all of the that may exist for a stoppage of this kind, but they include proper than 90 per cent of all the commoner causes of such a and, either as given above, or in some modified form of the condition, will be found to represent by far the greater par the causes of sudden stoppage.

### Q. Of the causes given above, which are the most libthe order of their usual occurrence?

A. The loosening of a battery connection at the term at the coil, or of a magneto and coil connection at either end; g ing or short-circuiting of either the primary or secondary connection between magneto and coil, that of the secondary more frequent owing to the high-tension current it carries. Ging of the dry cells in the battery box; loosening of the switch it jars open. With the exception of the grounding of the pror secondary cable between the magneto and the coil, all above are the direct result of vibration and jarring. In old cylinder motors, vibration is constant, and at times very seventhat attention should first be directed to searching for loos

: 3

- Q. Are symptoms of this nature ever due to a fault in the ignition system?
- A. They will result at times from the use of a set of dry cells that is almost exhausted. The storage battery also acts in a similar manner. Both the dry cell and the storage battery recuperate very rapidly even when practically exhausted, so that they will often provide sufficient current to run the motor properly for a very short time, will then cause it to miss badly, and shortly afterward again run regularly. If, when the switch is thrown over to the magneto, the motor runs smoothly and continuously, there is no doublt that the battery is at fault, and this may be verified by testing the cells with a pocket ammeter. Should they show much less than eight amperes on test, they are the cause of the trouble and should be discarded. This may also be due to the use of a storage battery that is practically exhausted, though it would be extremely bad practice to allow a storage battery to get this low. Test with the voltmeter: if the cells show 11 volts each or less they are badly in need of charging, and if they will not run the motor properly, should be immediately recharged from an outside source of current.
  - Q. What is meant by "pre-ignition", and what causes it?
- A. When the charge in the cylinder is ignited before the passing of the spark at the spark plug, it is said to be "pre-ignited", i.e., fired in advance of the proper time. As a result, the force of the explosion is partly exerted against the rising piston, as is evidenced by a heavy pounding accompanied by a decrease in the power. The cause is usually an accumulation of carbon in the form of a deposit on the piston head and results from excessive lubrication. The surplus oil finds its way into the combustion chamber and is burned. This condition is further aggravated by running with an over-rich mixture. If the motor is allowed to run very hot, these carbon deposits become incandescent, so that the fresh mixture is fired the noment it comes in contact with them. In some cases this becomes so bad that the motor cannot be stopped without shutting off the rasoline supply.
- Q. How can the pounding caused by pre-ignition be distinguished from other internal noises, such as those produced by a cose crankshaft or crankoin bearing?
  - A. Pre-ignition takes place only after the motor has been

running long enough to become very warm and with the thrott opened to any extent the pounding is very violent, jarring the who chassis. The noise produced is distinctive and can be identificately once it has been experienced. Unless very loose, a bear noise will practically disappear if the motor is allowed to idle ve slowly and will always increase in proportion to the load, becomi very severe when climbing a hill.

### Q. How can the condition which causes it be remedied?

A. By removing the carbon deposits. In many late-moven engines this can be done most readily by removing the cylind heads, usually a single casting. The carbon may be burned of with the oxygen-gas flame now in common use or it may be loosen by the use of kerosene in the motor. After the motor has run loosen enough to become hot, shut off the gasoline supply gradually, mea while feeding kerosene through the auxiliary-air inlet of the carbon retor until the motor is running on kerosene alone; feed an excess the latter and the carbon will be loosened and blown out throut the exhaust.

- Q. When a single cylinder continues to miss regularly, the others running properly, and inspection shows every prof the ignition system to be in good condition, what is likely be the cause?
- A. Failure of its valves to operate properly. Either the inle or the exhaust valve is not opening, or is sticking open (the result will be the same in either case). This may be caused by a we valve spring, a bent valve stem, derangement of the valve tapperson that it does not strike the valve-stem end, or by a piece of foreign matter, such as a piece of carbon, lodging on the seat of the valve so that the latter cannot close. Another, though rarer cause, is leak in the manifold, close to the inlet valve of the cylinder in question. This permits an excessive amount of air to be drawn into that paticular cylinder, so that the charge is too weak to fire. In any of the above cases, the result is that fuel either does not get into the cylind or it is exhausted before it can be fired, as with every part of the ignition system working properly, the only thing that can cause cylinder to miss is lack of fuel.
- Q. Mention one of the causes of irregular firing that is selde suspected, except by those who have experienced it previously?

L

ķ

لی

Ē

t


i

A. Excess oil finding its way into the combustion chambers in such quantities that it covers the spark-plug electrodes, thus preventing a spark from jumping the gap. The oil, particularly when fresh, is an excellent insulator and, if mixed with carbon so that it conducts the high-tension current, it does so without permitting the formation of a spark. Owing to the viscosity of heavy lubricating oil, it clings to the spark-plug points and when they are as close together as they should be (3 inch), it will often bridge the gap for some time, despite the vibration and succeeding compressions in the cylinder. This fault is particularly difficult to locate when not suspected, as jolting over a rough piece of road will shake the plug points free and the engine will fire regularly, again missing intermittently when on smooth going once more. When confined to one cylinder, it is usually an indication that the cylinder wall is scored, or that the lubricating-oil feed to that cylinder is deranged.
 
### Q. Mention a rare cause of what appears to be ignition failure?

When a motor has been taken down and all its working A. parts thoroughly cleaned with gasoline or kerosene, it will sometimes be found next to impossible to start it. The explosions are very weak and erratic, and the engine does not generate sufficient power to run more than a few revolutions at a time. The trouble has every indication of being due to a derangement of the ignition system and looks particularly as if it might be faulty timing, caused by misplacing the spark-plug leads. In one case of this kind experienced by the writer, all the spark plugs and wiring were renewed, fresh batteries put in, and every part of the ignition system checked by three experienced garage men, but the motor could not be made to run. The trouble was finally overcome by taking out the spark plugs and injecting two or three ounces of the heaviest cylinder oil into the combustion chambers. The motor was old and well-worn so that the pistons were loose; the cleaning process left all these parts wet with kerosene and there was enough of the latter left in the crankcase to thin out the fresh lubricating oil considerably. As a result there was no compression, and the force developed by the explosion was not sufficient to turn the motor over for more than a few revolutions: what little oil was splashed up by this was too thin to seal the space between the pistons and cylinders so that most of the power generated by the weak explosions leaked past the pistons. Trouble of this nature is most likely to occur in old and well-worn motors, and will sometimes result from excessive priming with gasoline, i.e., squirting gasoline in through the petcocks or spark-plug holes, as this washes all the lubricating oil from the cylinder walls into the crankcase and thins the oil in the latter.

- Q. When intermittent failure of the ignition is thought to be due to faults in the wiring which cannot be detected by an ordinary examination, how can the trouble be found most readily?
- A. Fit a handy length of cable—one that will span practically any two points in the ignition system—with spring-clip terminals. Disconnect each wire in turn, and substitute for it this length of cable as a temporary connection; satisfactory operation with the latter indicates that the wire it replaces is at fault.





TYPICAL REMY STARTING MOTOR
Courtesy of Remy Electric Company, Anderson. Indiana



TYPICAL GENERATOR FOR REMY STARTING AND LIGHTING SYSTEM

Courtesy of Remy Electric Company, Anderson, Indiana

# ELECTRICAL EQUIPMENT FOR GASOLINE CARS

### PART IV

# ELECTRIC STARTING AND LIGHTING SYSTEMS

### **GENERAL FEATURES**

Fundamental Characteristics. In the introduction to elementary electric principles, no attempt has been made to go beyond simple theory as applied to the generation of electric currents, the operation of electric motors, circuits and the auxiliary devices required by the lighting and starting systems employed on the automobile. A very large part of the theory of electricity and electrical action as given in the majority of textbooks is omitted altogether for the sake of clearness, only that part of it which bears directly on the subject of electrical equipment of the automobile being retained. In the presentation of the latter, a somewhat different method of handling the subject has been followed, particularly with a view to making it appeal to the practical man by citing examples and comparisons, the force of which is at once clear. The man whose time for study is limited has no opportunity to go into all branches of electrical phenomena, so that the subject is presented in the briefest and most practical manner.

Considering that the practical application of electric lighting on the automobile dates back to 1910 only and electric starting to 1912 models, in which year but one make of car was fitted with a complete system as regular equipment, there are a number of different types in use. Each is characterized by varying features of design in the generators, motors, and auxiliary devices. In many instances these are slight, in others they are radical, but in every case they merely represent a different application of the fundamental principles given in the introduction. Since they must first pass the test of practical use before being adopted by the automobile manufacturer, they all operate successfully. But, that they all do not

operate equally well, or, to put it better, all do not continue to show the same high degree of efficiency and reliability in service, goes without saying. Owing to the lack of standardization that prevails, it is necessary to become familiar with each system. A brief analysis of each of the systems in general use accordingly is given here, and it will be found valuable for reference.

### VARIATIONS OF OPERATING UNITS AND WIRING PLANS

Principal Differences. Before taking up the different systems in detail, an outline of the chief points on which they vary is given as an aid in distinguishing them when found in service on the various makes of automobiles of which they form a part. Electrical systems as a whole may be divided into two general classes. These are the single-unit and the two-unit types.

Single-Unit Type. The first type is characterized by the employment of a dynamotor—a single unit with generator and motor windings on the same armature and fields connected to independent commutators at each end of the armature, as in the Delco, (in some models, two concentric commutators at the same end) or to the same commutator, as in the Dyneto. The single-unit type is greatly in the minority, the two makes cited being the chief exponents of it, though both of them are also built in the double-unit type as well. When the ignition distributor is incorporated in the generator, as is now very generally the case, the single-unit types incorporate in one machine the three chief electrical functions required on the automobile, viz, charging the storage battery, turning the engine over to start, and distributing the ignition current.

Two-Unit Type. Owing to the difficulty of efficiently combining in one machine two functions so widely separated as the generation of a constant charging current of a value rarely exceeding 20 amperes, and the utilization of currents up to 350 amperes, such as are required for starting, the majority of systems are of the two-unit type. The latter also is generally favored owing to its greater convenience of installation, as the dynamo must run either at motor speed, or at 1½ times that, while it is necessary to gear the starting motor to the engine in the ratio of 30 or 40 to 1. As the term implies, an independent unit is employed for keeping the storage battery charged, light y the lamps (when running), and

distributing the ignition current, while a second unit is installed solely for the purpose of turning the gasoline engine over to start.

Single-Wire and Two-Wire Systems. The difference between these is pointed out in detail in the section on Wiring Diagrams, Part IV. Owing to its greater simplicity of installation, reduced cost for wiring, and the greater ease with which faults may be located, the single-wire system is largely in the majority. In fact, there are only one or two examples of two-wire systems in general use, of which the Bijur, as employed on the Packard, Jeffery, and other cars, may be cited as an instance. In the gradual approach to standardization that is being made each year, the number of cars on which the single-wire system is employed is constantly increasing. But differences will be found in these single-wire systems as well, some employing the frame of the car for the positive side of the circuit, and others for the negative. This must be borne in mind when testing for faults with the volt-ammeter.

Comparison of Systems. While inherently more dangerous, experience has demonstrated that the fire hazard with the single-wire system is more a matter of proper installation than of the comparative merits of the systems themselves, and quite a number of manufacturers who adopted the two-wire system at the outset have later become converts to the single-wire system. The Society of Automobile Engineers, which is now the Society of Automotive Engineers, considered the adoption of the single wire, or grounded return system, for about three years. This Society now recom-



with the Delco single-wire system, Fig. 145, which is employed on a great number of cars. Comparison cannot be made exactly on the


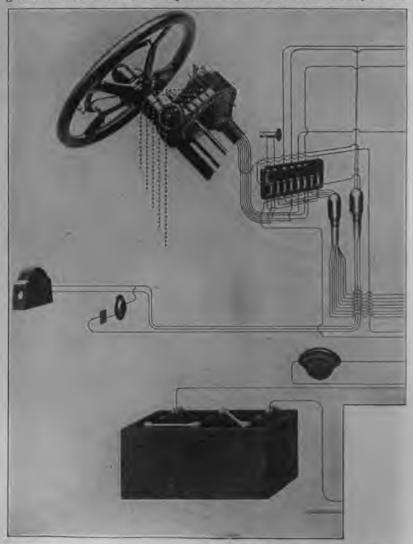


Fig. 14. Wiring of Packard (Biller) Two-Unit. Courteby of Packard Mater Cor

same basis in these two installations, however, as the Packard is what is known as a two-unit system, i.e., the generator and the electric starting-motor are independent, while the Delco is a com-

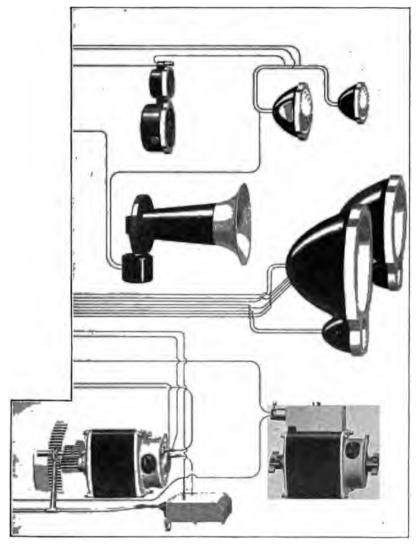bination generator, motor, and ignition unit. Moreover, the Packard has several additional lamps, being fitted with double bulb



Two-Wire Starting and Lighting System (1916 Model, Six-Cylinder) Company, Detroit, Michigan

headlights and side lights, which are not present in the Delco installation; but even omitting these considerations, it will be seen that the single-wire system has the advantage of simplicity in a marked degree.

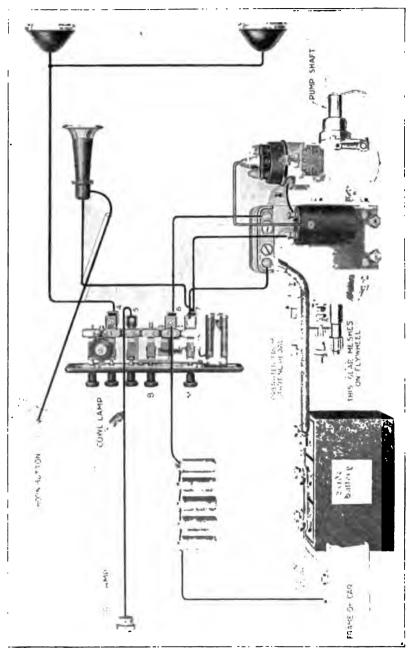


Fig. 145. Wiring of Delco Single-Unit Single-Wire System

#### METHODS OF REGULATION

Necessity for Control of Generator Output. In the section on Generator Principles, Part I, mention has been made of the fact that the speed with which the armature coils cut the lines of force of the magnetic field is the chief factor determining the e.m.f. and, in consequence, the current output of the generator. This, in connection with the heating effect of the current due to the resistance of the conductor, limits the amperage that the latter will carry safely. Beyond this point the insulation will take fire and, with a further increase in the temperature due to excessive current, the conductors themselves will fuse. With the extreme variation in speed presented by the operation of the automobile engine, the necessity for regulating the output of the generator will be apparent. There are almost as many methods of regulation as there are systems in use.

As explained in the section on Induction Sources of Ignition Current. Part II, the magneto is an electric generator that requires no current-controlling device, as the magnetic excitation of its fields is permanent. That is, barring gradual exhaustion through age, heat, and vibration, its magnetic field is constant, thus enabling it to generate a current at very low speeds; but the limitations of this type of field are such that electromagnetic fields are employed as in large direct-current generators. These fields depend for their excitation upon the current derived from the armature of the machine itself, and, as the amount developed by the latter increases in direct proportion to its speed, the fields become stronger as the speed increases and correspondingly more current is generated by the armature. As an automobile motor is driven at a great range of speeds, varying from 200 or 300 r.p.m. up to 2000 to 2500 r.p.m., or even higher, and the generator is usually geared in the ratio 1:11 so as to develop its rated output at the normal speed of the engine — its windings would be quickly burned out unless some provision were made to control its output.

Constant-Current Generator. Generators of the so-called constant-current type are frequently regulated by the winding alone. They are usually compound-wound, the series coil being so connected as to oppose the shunt. Assuming the coils to be in equally advantageous positions on the core, the limiting current then is one

which = to the and a the shund limitime 25. Win current o erably los

Motte peculiar di of roccoul



Tia. Id.

There are methods of me third-brush met ber of other form are now obsolete

A typical exar in Fig. 147. In the the armature is gove ever, this principle is that magnetizes the hell passes through the regul through the shunt field retuthe charging circuit which pass

but as the battery become till and secretar tapers of graduals. The hole is arrest flowing through the regular to may is low. The larger is the conwas and the lights will seems with a all usert sufficient session not be increasing Served the the output by mean of each

130. If Figs. 148 and 130 are some

in sinks except that the residen the charges over the seeds with the charging man. Its regulator and of the one perulation type consist of a lew turns of heart was ten the regulator coil of the tale

use type consists of a new her of turns of fine with

Referring again to I'm the current is collected at the positive bress of the posentior. As the same sermes, the magnetist of and regulator coil become d meson on the regulate uni resistance in the liw from the maine source, through the the generator, but through the point mints like the one wer mind rate and m mercane to be held and of that used Most Reny mire-brush nereof sufficient strength to overcome the spring tension that is holding the regulator points together, the points will open and cause the shunt current to flow through the shunt resistance before going through the shunt field. This cuts down the value of the current flowing through the shunt field and thereby decreases the amount of current generated at the positive main brush.

It must be remembered that the amount of current induced in any generator is dependent upon the number of magnetic lines of force cut per second, and the number of magnetic lines of force in a field are mainly determined by the strength of the current flowing around that field. When the shunt field is reduced in strength, the corresponding reduction in the charging rate causes the regulator core to become demagnetized and the regulator

points to close. The points open and close so fast that it is hardly visible, and this process causes the output of the generator to remain at a fairly constant value.

The vibrating regulation resistance type is divided into two classes. The method of connecting the regulator coil

A vibrating regulator whose

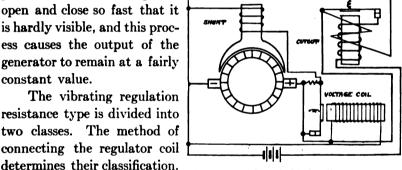


Fig. 148. Regulator Coil in Parallel with Battery

regulator coil is connected in parallel with the battery is shown in Fig. 148. This method of regulation is known as the constantpotential type. In other words, this system is regulated by means of constant voltage. The regulator coil is wound with a large number of turns of fine wire and the amount of current flowing through this coil is determined by the voltage of the battery and the voltage of the generator. There will be more current flowing through this coil with a fully charged battery, as a battery in this condition offers more resistance.

This type of regulator has been used for some time by Bijur Its main advantage is that the output of the generator is controlled to a great extent by the condition of the charge of the battery. A heavy charging current will be produced when the battery charge is low, but as the battery becomes fully charged the output of the generator tapers off gradually. This is due to the less amount of current flowing through the regulator coil when the charge of the battery is low. The battery in this system can be removed from the car and the lights will operate quite satisfactorily as the regulator will insert sufficient resistance into the circuit to prevent the output from increasing beyond the amount of current that the lights use.

The method of regulating the output by means of constant current is shown in Fig. 149. If Figs. 148 and 149 are compared, it will be noted that they are similar except that the regulator coil in Fig. 149 is connected in series with the charging circuit, while in Fig. 148 it is connected in parallel with the charging circuit. The

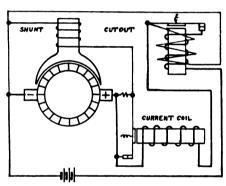


Fig. 149. Regulator Coil in Series with Battery

regulator coil of the currentregulation type consists of a few turns of heavy wire while the regulator coil of the voltage type consists of a number of turns of fine wire.

Referring again to Fig. 149, the current is collected at the positive brush of the generator. As the output increases, the magnetism of the regulator coil becomes of

sufficient strength to overcome the spring tension on the regulator points causing them to open and insert a shunt resistance in the shunt circuit. The shunt current will then flow from the positive brush of the generator through the shunt resistance, through the shunt fields and back to the negative brush of the generator; but when the points are closed the current will flow through the points instead of through the shunt resistance. These points, like the ones in the constant voltage regulator, operate at a very rapid rate and on account of this rapidity cause the output of the generator to be held within certain limits. This form of regulation is typical of that used on the Remy and other systems for several years. Most Remy systems, however, at the present time are of the third-brush regulation.

In order to increase the output of the current type of regulator, it is necessary to increase the spring tension on the regulator points. This will prevent them from opening until a higher value of current is obtained from the generator. In order to regulate the output of the voltage regulator, no attention should be paid to the amperes generated as this will depend entirely upon the condition of the battery. The regulator spring must be adjusted so that the voltage will not exceed 8 volts in the case of a 6-volt system.

There is, however, a certain disadvantage in the vibrating type of regulation, and manufacturers have been constantly experimenting with forms of regulation so that a method of control much simpler in operation and less expensive to manufacture could be produced. The result of this experimenting is the third-brush

method of regulation. Generators having this type of control have an extra brush called the third brush, located between the two main brushes. In case it is a four-pole four-brush machine the "third brush" would be the "fifth brush."

Referring to Fig. 150-a, the magnetic lines of force pass from the north field pole through the armature coils and into the south field pole. In


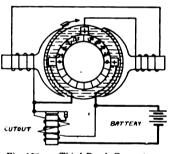


Fig. 150-a. Third-Brush Generator Running Slow

this illustration the armature is revolving at a slow rate of speed. The magnetic lines of force pass in straight parallel lines. The figures on the commutator bars represent the voltage drop between each bar. The sum of these voltage drops when one-half of the commutator is considered will equal the voltage between the main brushes. In Fig. 150-a, the generator is producing 8 volts. Attention is called to the fact that these figures are not absolutely accurate figures but have merely been selected as relative values for the sake of illustrating the principle of third-brush regulation. The third brush in Fig. 150-a is a positive brush; in other words, the current collected at the third brush has a voltage equivalent to the figures between the third brush and the negative main brush which, in this case, is 4 volts. Let us assume, for the sake of illustration, that the shunt field has a resistance of 1 ohm. We

will then have a current flow of 4 amperes through the s winding.

It is very evident that if water in a bucket is stirred wistick, the water will have a tendency to follow the stick are and as we increase the speed of stirring, the movement of the will also be increased. This is also true of magnetic lines of f As the speed of the armature increases, there is a greater tend for the magnetic lines of force to be twisted out of shape ar follow the movement of the armature than to pass straight a from the north to the south pole. Fig. 150-b shows the field with the armature is turning at a high rate of speed. At this time magnetic lines of force are not distributed evenly at all point the field but have a tendency to pile up at points A and B. Beat

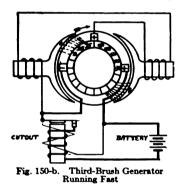

in mind that the greater the nur of magnetic lines of force cut second, the greater will be the put of the generator, it is at noticed that the output of the ar ture in Fig. 150-b would be much than that shown in Fig. 150-a. third brush is now bearing on a ment which has the same relative; tion but the voltage drop between commutator bars from the negative.

brush to the third brush is now only 1 volt. As the resistant our shunt field is 1 ohm there will be a current of 1 ampere flot through the shunt field instead of 4. This naturally decreases field strength, and the number of lines of force traveling from north to the south field is greatly reduced. As the armatul traveling at a higher rate of speed, it will still be cutting the snumber of lines of force per second and the output of the gener will be practically the same as in Fig. 150-a. As these magnines of force are twisted out of shape, the drop between the varies considerably.

Increasing the charging rate of a third-brush generator is easily accomplished. Referring to Fig. 150-b, it will be noted if the positive third brush is moved in the direction of rota there will be a greater voltage between this brush and the negative control of the results o

main brush. As this voltage is increased, the strength of the shunt field will be increased and the output of the generator also increased. If the output is to be reduced, moving the third brush in the opposite direction of rotation will reduce the current in the shunt field and the output accordingly.

A rather novel combination of regulation has recently been placed in the market by the Delco people, one of the typical installations being on the 1921 Pierce-Arrow cars. This regulation consists of a combination third-brush generator and a vibrating regulator.

The connections for this system as used on the Pierce-Arrow car are shown in Fig. 150-c. The regulator coil of this system is wound with sufficient resistance to prevent the regulator points

from being opened when the battery is discharged. The points then remain closed constantly and the generator acts as a simple third-brush machine, the output being controlled only by the third brush. As the battery becomes charged and approaches a specific gravity of approximately 1250, the resistance of the battery increases and more current will then be forced through the voltage coil of the

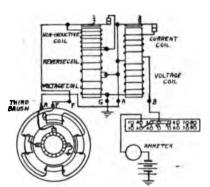


Fig. 150-c. Combination Third-Brush and Voltage Regulation

regulator. The regulator points then begin to vibrate, throwing the resistance in the shunt circuit and cutting down the output.

Referring to Fig. 150-c, the voltage coil consists mainly of an electromagnet having three windings and a set of contacts which are normally closed. The voltage coil consists of a large number of turns of fine copper wire connected directly across the main generator circuit; that is, in parallel. Another coil, a reversed winding, consists of a large number of turns of fine wire wound around the core in the opposite direction to the voltage winding. The last winding is a noninductive coil having half the turns wound in each direction around the core. The reverse and non-inductive windings are in parallel with the contacts and add resistance to the field circuit when the contacts are open. This prevents

the generator output from becoming too great at high car speeds. The noninductive winding is also used to prevent arcing at the contacts or regulator points.

#### PROTECTIVE DEVICES

Various Forms. When fully charged, the storage battery holds in chemical form the equivalent of two or more horsepower, i.e., 40 to 160 amperes at 6, 12, or 24 volts, according to the system employed and the capacity of the battery furnished. To guard against damage from short circuits, various forms of protective devices are employed, and the different systems vary as much in this respect as they do in others. In some instances, a circuit breaker is depended upon to take care of all the circuits. In others, protection is afforded by the employment of fuses.

Automatic Battery Cut-Out. It will be evident that, if the storage battery were at all times in direct connection with the generator, it would immediately discharge through the latter as soon as the driving speed fell to a point where the dynamo was no longer producing sufficient voltage to charge the battery. If the generator were free to run instead of being positively connected to the engine. it would become "motorized" and operate as an electric motor on the battery current. As it is so connected, the battery current would simply burn out its windings, owing to the low resistance of the latter at low speeds. Consequently it is necessary to insert an automatic switch in the circuit in order to connect the battery with the generator when the speed of the latter reaches a certain point. and to disconnect it as soon as it falls below that value. Such switches are termed automatic cut-outs or "reverse-current relays." In single-unit systems, such as the Dyneto, no battery cut-out is employed. A single hand-operated switch controls both the ignition and the generator-battery circuits, so that this switch is left closed as long as the engine is running. Should the engine stall, the battery current automatically "motorizes" the generator and re-starts the engine. With such systems the engine must not idle slowly and the starting switch must not be left closed after the engine has stopped.

Ward-Leonard Type. The Ward-Leonard, Fig. 149, is typical in that it clearly illustrates the principles upon which most of these devices are based, though their construction varies widely, as will be

ed by Fig. 153. The switch mechanism is shown at the left Fig. 149. In this device A is the coil, B the magnet core, C movable arm, and DD' the contacts. The dynamo generates ficient voltage at a car speed of approximately 7 miles per hour to ract C and hold it, closing the battery circuit through DD'.

Circuit Breaker. Circuit breaker, as employed in this connecn, must not be confused with "battery cut-out." The cut-out is rally a circuit breaker and is referred to as such by some manuturers in their instructions, but in electric terminology, as ployed in everyday use, the circuit breaker and the cut-out are irely different things. A circuit breaker is designed to operate

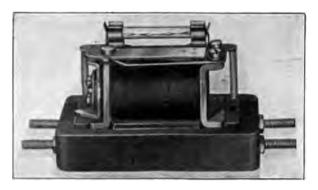


Fig. 153. Remy Reverse-Current Relay



ingly larger than those of a 9-cell or a 12-cell battery. We there are a few adherents of the higher voltage battery resented by the systems in use today, the majority favor the 6-standard.

Variation by Manufacturers. A final difference to be note that systems of totally different characteristics are turned out the same manufacturer. Automobile motors are still a long from reaching a degree of standardization that permits them to classified according to horsepower, dimensions, number of co ders, or any other easily applied standard so far as their requ ments from an electrical point of view are concerned. The ma facturer of electrical apparatus accordingly designs a starting lighting system to meet the requirements of a certain motor an will give the most efficient service only when applied to that ticular motor. This accounts for the major part of the great v ation in electrical systems that exists and particularly for the di ence between the equipment of the successive models of the s make of automobile. For that reason, it must never be conclu that a Delco, a Gray & Davis, a Bijur, a Wagner, or any of starting and lighting system is always the same on whatever ca may be found. Automobile manufacturers alter the characteristic their motors from year to year, and the manufacturer of electi apparatus not only keeps pace with this by redesigning his sys to correspond but also introduces various improvements sugge by experience and the development of the art. In consequence would be manifestly impossible to attempt to outline in detail features of every starting and lighting system to be found on the cars now running, thousands of which are three to five ve old. The following analysis accordingly covers only those of n recent manufacture, but by a study of these it will be easy to bee familiar with the general characteristics of all, and to note at a gla where improvements have been made from year to year.

#### STARTING MOTORS

Speaking broadly, there are three classes of starting dev worthy of mention, viz, the mechanical or spring-actuated devithe compressed fluid devices; and the electrical starters. While: employed to some extent abroad, compressed air and similar devi e now only of historical interest here as they have been displaced most entirely by the electric starter.

Modern Electric Starting System Anticipated Sixteen Years. Ithough it has only come into general use within the last few years, ie possibilities of the electric starter on the automobile were foreen at an early day. Those to whom it has appeared as a novel evelopment of very recent adoption will doubtless be surprised to arn that a car embodying many of the features of present-day ectrical systems was built in 1896. Indeed, the following descripton of it might well apply to the present U.S.L. system, which applys the flywheel type of dynamotor. The machine in question as a Diehl specially wound Gramme-ring type designed to operate 12 volts. The armature, which weighed 111 pounds, served as a flywheel of a two-cylinder horizontal opposed 6- by 7-inch otor. The system was described as follows:

"The flywheel is constructed as a dynamo, which by rotary ption charges a storage battery carried in the vehicle. At the time starting the carriage, the motorman turns a switch which disarges the storage battery through the dynamo, converting it for lew seconds into a motor, which, being upon the main crankshaft, wes rotation and does away with the necessity of starting the flyweel by hand. After the motor gives the crankshaft a few turns, e cylinders take up their work and the battery is disconnected on the dynamo, which then acts as a flywheel.

The flywheel dynamo furnishes the current for the induction

practice in all the essential points mentioned. In addition, the machine in question was provided with a magnetic clutch which automatically connected and disconnected the engine every time the gear-shifting lever was moved, thus anticipating the present-day electromagnetically operated gearbox.

Requirements in Design. The conditions in applying an electric starting motor to the gasoline engine bear no relation whatever to those of the lighting dynamo, so that the problem is not, as might be supposed, merely a question of reversing the functions of a single unit of the same characteristics. Practically the only requirements of the dynamo that differ from standard practice in other fields are that it shall commence to generate at a comparatively low (car) speed and that its output shall not exceed a safe limit no matter how high the speed at which it is turned over. The problem of the starting motor, on the other hand, involves conditions which have not had to be met in the application of electric motors to other forms of service. For example, a very high torque must be developed to overcome the inertia of the load, and the latter takes the form of intermittent rather than of steady resistance to the driving effort, owing to the alternate compression and expansion in the motor cylinders. The trolley car might be cited as a parallel to the heavy starting torque required, but the intermittent load, as well as the highly important limitations of weight. restricted current supply, voltage, and space considerations, are entirely lacking.

In the last analysis, the electric starter is nothing more nor less than a storage-battery starter, since most of its limitations are centered in that most important essential. The matters of driving mechanism, starting speed, and other equally important details can all be based on what is either accepted practice of long standing in other fields, or on the knowledge of starting requirements gained in the years of experience in applying manual effort to that end, but the storage battery will always constitute the chief limiting factor. This should be borne in mind in considering the forms that various solutions of the problem have taken, and, above all, it must be given first consideration in the successful maintenance of any electric starting system, as the majority of troubles met with have their origin in the neglect of the battery.

Wide Variation in Starting Speeds. In view of the long experience in hand-cranking the motor, it would seem that a definite basis for the starting speed would be an easy thing to establish, but this has not been the case. If "motor" briefly summed up in one word all of the varying characteristics to be found in the great variety of engine designs to which starters must be applied, this might have been easier of accomplishment. What suffices to start one make is. however, frequently found to be totally inadequate for others of apparently identical characteristics, so that in the different makes of starters this essential is found to range all the way from 25 r.p.m. to 200 r.p.m. or over. The necessary speed is largely influenced by the carburction, as with the stand-by battery ignition almost universally provided, dependence need not be placed on the magneto to start; but to draw a mixture from the carbureter of a cold engine calls for speeds in excess of the lower limit of the range given. most severe service demanded of the starter and the time when it is most needed are coincident, i.e., in winter use, and the equipment must naturally be designed to meet successfully the most unfavorable conditions. Even with starting speeds of 100 r.p.m. or over. it has been found impossible to start some motors without resort to priming. Some idea of the great variation in the speeds adopted will be evident from the fact that the North East starter, as originally built, was designed to turn the Marmon six-cylinder motor over at only 25 r.p.m.; the Hartford on a similar motor at 70 r.p.m.; the

Voltage. When an engine has been standing idle for some time at a temperature well below the freezing point, the lubricating oil becomes extremely viscous and the current required for starting at a low voltage is very high. The 6-volt standard inherited from dry-cell-ignition days accordingly appeared to be entirely too low at the outset, and several systems employing 12- and 24-volt batteries were developed. The higher efficiency of the latter in starting is opposed by certain disadvantages inherent in this type of installation. Experience has shown, however, that with proper installation and maintenance the 6-volt system affords advantages

tages which more than offset any increase of efficiency derived from the use of a higher voltage, and the majority of well-known starting systems are now designed to operate on a potential of 6 volts.

Motor Windings and Poles. The necessity for developing a powerful torque at low speeds naturally calls for a series-wound motor, such as is employed in streetrailway and electric-

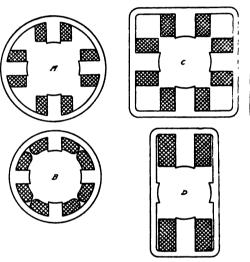


Fig. 154. Cross-Sections Typical Electric Starting Motor Courtesy The Automobile, New York City

automobile service, and all starting motors are of this type. Motors built to operate at such a low voltage being new to the electrical designer there is more variation in the form and size of starting motors than exists in power units running on current at commercial voltages.

Standard Designs. Briefly stated, the electrical requirements demand a concentrated and correctly proportioned mass of iron and copper in the minimum space. The cross-sections, Fig. 154, show how these requirements have been met in various instances. As the motor is only required to operate for very short periods, both the conductors and insulation can be kept down in size as compared with a motor designed to run constantly under heavy load.

Commercial Forms. The problem is to provide for a certain mber of ampere turns around the poles and a magnetic circuit rough the latter, as well as steel housing or frame of sufficient crosstion to carry the required degree of magnetization with the

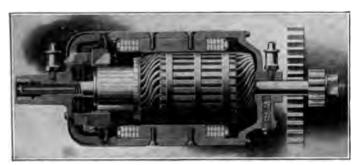


Fig. 155. Section of Bosch-Rushmore Starting Motor

present magnetic circuit. Consequently, shallow windings with a flat pole pieces are more efficient than the reverse of this form, reticularly as air space in the magnetic field lessens its intensity d calls for a heavier winding to magnetize the extra weight of stal to the same degree. Hence, the type represented by B, g. 154, is the most efficient, in theory at least, of the four forms ustrated.

Whether the windings be placed on two poles or on four poles is mething that each designer decides according to his own preferce in the matter. The Bosch-Rushmore starting motor, Fig. 155,



unwound pole pieces at the sides do not show very clearly in the illustration; they are of substantially the same form, though con-

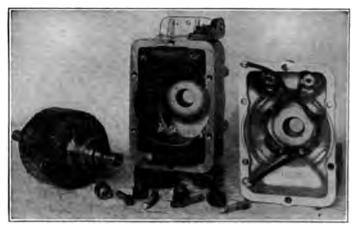


Fig. 157. Bipolar Type Westinghouse Starting Motor

siderably wider than those illustrated in the section in question. The for a more restricted space a straight rectangular bipolar type is

made, Fig. 157. From the standpoint of both electrical efficiency and space considerations, practice favors the cylindrical rather than the rectangular form.

## TRANSMISSION AND REGULATION DEVICES

Installation. As the driving requirements of starting with such a small power unit as space and weight limitations make necessary


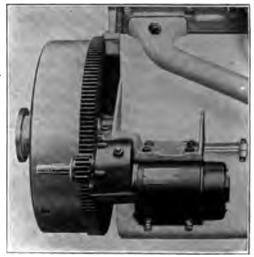


Fig. 158. Double-Reducing Gear Type Installation, Wagner Starting Motor

call for a high-speed motor and a high gear ratio to effect the necessary speed reduction, the mounting of the starting motor is totally

nt from that of the lighting dynamo. The electric motor t 1800 to 3000 r.p.m. or over, according to its design, while, as y mentioned, the engine starting speeds usually average 80 to p.m. The great speed reduction required is effected in the ity of instances by utilizing the flywheel as the driven gear, a eing bolted to it, as shown in Fig. 158, which illustrates the ation of a Wagner starter to the Moline-Knight 50 horsepower ylinder motor. Or the gear teeth may be cut directly in the ery of the flywheel itself, as shown by the Delco single-unit

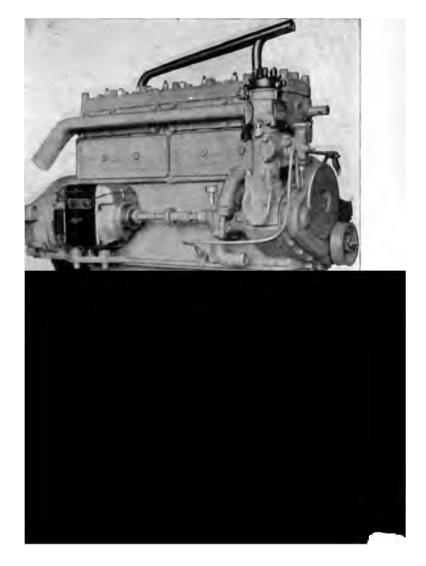

the pinion driving direct. In view of the large reduction available in a planetary gear, a starting motor of this type may be employed to

drive through a camshaft or similar location. Planetary gears are also utilized on some of the single-unit systems, such as the Northeast, the gear ratio used being something like 40 to 1 when the dynamotor is used for starting and 1 to  $1\frac{1}{2}$  or 2 when running as a generator, Fig. 162. Silent chains are made



Fig. 160. Reducing Gearing Attached to Ward-Leonard Starting Motor

use of in some cases, but this is done more frequently where a starting and lighting system is applied to an old car rather than to one

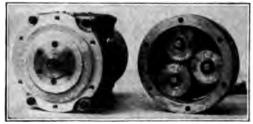


Fig. 161. Westinghouse Starting Motor with Planetary Reduction Gear

for which it has been especially designed. Where the starting motor is of a comparatively low-speed type, the single reduction between the motor pinion and the flywheel suffices. Fig. 163 shows a Ward-Leonard starting

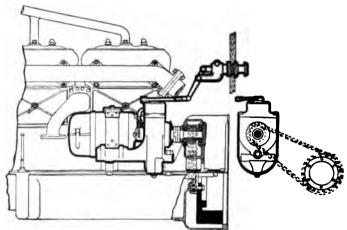


Fig. 162. Mounting and Drive of Northeast Dynamotor

motor designed for direct engagement with the flywheel gear. The purpose of the spring shown on the end of the shaft is to take up the shock when the power is applied to the starter, as explained in a following section.


Driving Connections. Except in the case of the single-unit type, which is in a permanent driving relation with the engine, it is neces-



Fig. 163. Ward-Leonard Starting Motor for Direct Engagement

sary to provide some form of driving connection with the engine in order that the electric motor may turn it over to start, and release it the moment the engine fires. The method of accomplishing this is made clear by a brief study of Fig. 164, which shows an Overland four-cylinder motor

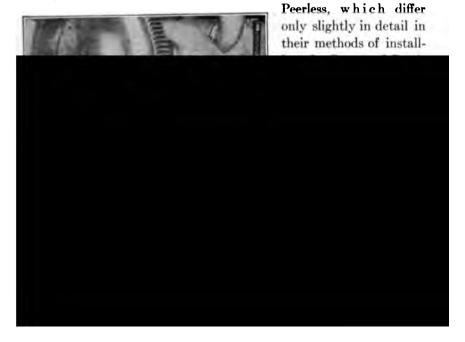with an Auto-Lite two-unit system, the starting motor only being shown. In this installation the control button or starting pedal serves both to connect the motor with the battery and to engage the driving pinion with the toothed ring of the flywheel. Typical examples of this form of control are found on the Locomobile and



over rapidly. Releasing the pedal automatically opens the switch contacts and disengages the starting motor from the flywheel. It is also frequently made in the form of a pedal and placed on the slope of the footboards under the cowl of the dash, the location in any case must be out of the way of the other controls.

Automatic Engagement. Auto-Lite Type. In Fig. 165 is illustrated a starter which eliminates the necessity of mechanically engaging the starting pinion with the flywheel gear. The armature shaft is extended and a sleeve having spiral-cut threads on its outer surface is placed over this armature shaft. One end of a coil



Fig. 165. Automatic Engagement and Release of Starting Mutor, Overland Engine

spring is fastened to this sleeve and the other end of this spring is fastened to the armature shaft. The driving pinion has a counterweight on one side and spiral threads inside to fit the sleeve. When the starting button is depressed, a direct circuit, having no resistance inserted, is completed, causing the armature to revolve at a high rate of speed. As

the driving pinion is counterweighted, it turns but little and is threaded into mesh with the teeth on the flywheel. When this pinion is in full mesh with the flywheel gear, the turning torque is transmitted through the spring, sleeve, and pinion to the flywheel. When the engine starts under its own power, the increased speed of the flywheel threads the pinion out of mesh with the flywheel gear. This is known as the Bendix drive and is now used by over 95 per cent of the manufacturers.

Bosch-Rushmore Type. Another form of automatic engagement, which is electrically operated in this instance, is that of the Bosch-Rushmore starter. By referring back to Fig. 155, which shows a section of this starting motor, it will be noted that there is a heavy spring on the left-hand end of the armature shaft and that the armature itself is normally held out of its usual running position by this spring. In other words, it is not centered in the armature tunnel but is two inches or more to the right of the center of the magnetic field. This is just sufficient to keep the pinion out of mesh when the motor is installed, as shown in Fig. 166. The first contact of the starting switch sends sufficient current for the field poles to exert enough magnetic drag on the armature to draw it back into its normal centered position, at the same time turning it over slowly, so that engagement is quickly effected automatically. The moment the current is shut off, the spring pushes the armature back and disengages the pinion. Exceptions to the practice reflected by the foregoing examples are to be found on cars like the Reo, in

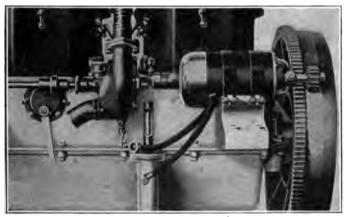


Fig. 166. Mounting of Bosch-Rushmore Starting Motor

which the Remy starting motor is mounted on the transmission housing and drives to one of its shafts through a worm and worm wheel. The latter lowers the speed sufficiently through a single reduction, and the revolution of the armature in starting picks up a clutch which automatically releases as soon as the engine starts.

Clutches. Necessity for Disengaging Device. To prevent the gasoline engine from driving the starting motor when the former takes up its cycle, some form of over-running clutch must be provided unless the starter is geared directly to the crankshaft or has a mechanical disengaging device, such as the Bendix or electrical, as the Bosch-Rushmore and Westinghouse. To take care of the speed reduction, assume that this gear ratio is 30 to 1 and that the throttle is half open

when the engine is being cranked. As soon as the explosions begin to take place, the engine will shortly speed up to about 500 r.p.m. Before the gasoline engine is started, however, the electric motor will be running pretty near its maximum rate, say 3000 r.p.m. An electric motor of this type will run as high as 5000 r.p.m. safely, but speeds in excess of this are liable to damage it. If the throttle of the engine should happen to be three-quarters of the way open when started and it should speed up to 1000 r.p.m. before the starting motor was disengaged, the armature shaft of the latter would attain a speed of 15,000 r.p.m., which is far beyond the safety limit. This makes it necessary to provide some device which, while permitting the starting motor

to drive the engine, will prevent the latter from driving the starting motor as soon as the former takes up its regular cycle.

A number of different devices are employed for this purpose, such as the jaw clutch similar to that employed on all handcranks, roller clutch, friction clutch, pawl and ratchet, inertia clutch, worm and worm wheel, and others. A description

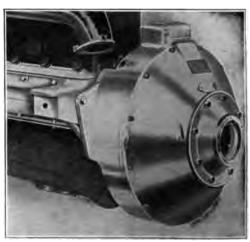


Fig. 167. U.S.L. Dynamo on Sheffield Simplex (British) Engine

of one or two types will suffice to make clear the principle on which most of the mechanical devices are based. The roller clutch and the over-running jaw clutch are most frequently used. With starters of the design of the U.S.L., shown on a Sheffield-Simplex (British) six-cylinder motor in Fig. 167, it is obviously unnecessary to provide any form of flexible coupling, as the armature is mounted directly on the crankshaft and consequently cannot exceed the speed of the latter.

Where the crankshaft is driven direct through a train of gears or a combination of gears and a silent chain, the clutch is usually placed between the last gear of the train and the crankshaft. None of the gears is then in operation except when starting. On the

flywheel-gear type of installation used in connection with a second-gear reduction by means of a countershaft, Fig. 158, the clutch is placed on the countershaft. Otherwise, it is mounted on the arma-


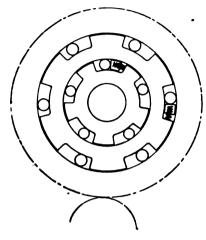


Fig. 168. North East Double Roller Over-Running Clutch (Horseless Age)

ture shaft. In the case of a worm and worm-wheel drive, it is incorporated in the worm wheel.

Roller Type. The roller type is the most commonly used and, as the various forms in which it is made differ but little, a description of one will suffice to make clear the principle employed. It consists of an inner driving member and an outer driven member, connected by a number of rollers when the driving member is rotated in one direction and disconnected when it is rotated in the opposite direction, i.e., when

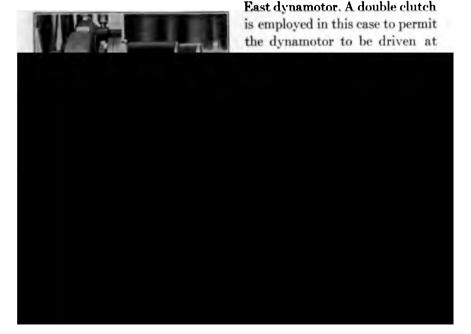the driven member tends to run faster than the driver. Fig. 168 shows the double-roller over-running clutch employed on the North



a back-kick release are found in practice. One of these on the Northeast starter is in the form of a friction clutch held in contact by springs. This clutch will slip under such circumstances. A fric-

tion disc clamped between two steel discs, similar to a shock absorber, is employed on the Hartford starter, this being required because of the irreversible worm and wormwheel drive used, as the teeth of the latter would be injured in case the engine "backkicked". Another device employs a brake band on the starting gears so designed that it holds in one direction only.

**Switches.** Two types of switches are employed in connection with starting and lighting systems—those designed to control the lighting circuits to the various lamps, and those employed to connect the battery with the As the first starting motor. type seldom carries more than 5 amperes at 6 volts and proportionately less at higher voltage, it does not differ from the standard forms of switches employed for house lighting, except that it is made much smaller in size. The starting switch,

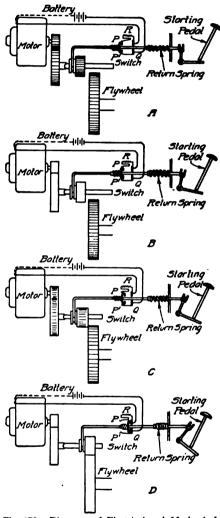


Fig. 170. Diagrams of Electrical and Mechanical Connections of Motor and Switch for Flywheel Drive with Double-Gear Reduction (Westinghouse)

on the other hand, has to carry currents ranging from 50 to 250 amperes or more at voltages varying from 6 to 24, so that such a switch must be well built mechanically and have liberal contact

cas. On account of the heavy currents handled by these switches ere is a tendency to destructive arcing at the contact points unless ovision is made to prevent it.

Westinghouse Starting Switch. For starting use, two forms of itches are employed according to the method by which the motor arts the engine. Where the motor is connected directly to the batry terminals by the switch, as in the case of single-unit systems such the Delco, only a single set of contacts is necessary; but in case are must be engaged before the starting motor can take the full attery current, two progressively operated sets of contacts are used. See first set completes the circuit through a heavy resistance to turn a starting motor over very slowly, and the second set cuts out this sistance, the driving gears then being engaged. The operation a switch of this type is graphically illustrated by a series of sketches,



Fig. 171. Details of Westinghouse Switch

g. 170, showing a Westinghouse starter installation. In sketch .1,

the driver when leaving the car to prevent tampering, a pin across the tube making it impossible to insert a pencil or stick. The resist-

ance mentioned is in the form of a ribbon and is incorporated in the switch.

Miscellaneous Starting Switches. The type of switch used in connection with the Remy system is shown in Fig. 172. Both this and the Westinghouse switch described are known as butt-contact switches. The knife type of switch is also employed in several systems, Fig. 173 showing the Dean switch of this class. somewhat unique form of contact is shown in the Gray and Davis switch, Fig. 174. There being no starting gears to mesh, it is only necessary to turn the current directly from the battery into the

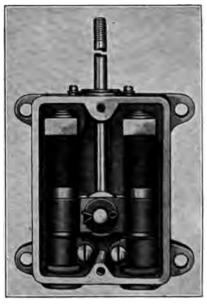


Fig. 172. Remy Starting Switch

motor to start. P is the foot button of the starter, F the floorboard of the car, and T and M the terminals of the switch from which cables are led to one side of the battery and to one of the motor brushes, the others being grounded, as this is a single-wire system. Into the cast

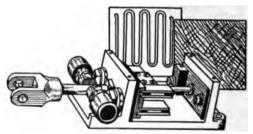


Fig. 173. Dean Knife Starting Switch

receptacle of the switch is fitted an insulating disc carrying the contacts C and O and also serving to insulate the terminals. These contacts are circular in form, and their free ends are turned away from each other so as to slip down over the knives R and S set in the insu-

#### ELECTRICAL EQUIPMENT

lated disc. The contacts are pressed downward by P, which is returned by the spring G pressing against the spindle P. The terminals T and M are fastened to the semicircular knives R and S, respectively, so that bringing down the contacts C and O upon these knives

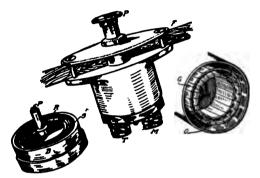


Fig. 174. Gray and Davis Button Starting Switch

completes the circuit from T to M. Several other forms of footoperated switches are also employed, the Gray and Davis laminated contact switch, Fig. 175, for flywheel-gear installations, and the Ward-Leonard "harpoon" type, Fig. 176; these are seldom used today.

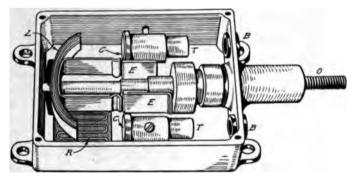


Fig. 175. Gray and Davis Laminated Type of Starting Switch

Courtesy of The Horseless Age

Electrically Operated Switches. In this type a conventional push-button switch, either on the dash or mounted on the steering column, as shown in Figs. 177 and 178, which illustrate the Packard and Overland control, respectively, takes the place of the foot button. This push-button switch, however, only handles a shunt current of low value, which energizes a solenoid to close the contacts of the main

switch and also to engage the gears where this is necessary. The Westinghouse magnetically operated switch is explained in detail

in connection with the description of that system. This form of control is employed on electricrailway trains and on electric automobiles. In addition housing the push-button switch of the starting system, the two steering column control units mentioned also incorporate all the switches necessary to control the entire electrical equipment of the car, as will be noted by the indications alongside the various buttons on the Overland controller. A complete wiring diagram of the Packard six-cylinder controller is shown in Fig. 144.

Where a higher potential than the usual 6-volt standard is employed, the switch has another function, which is that of chang-

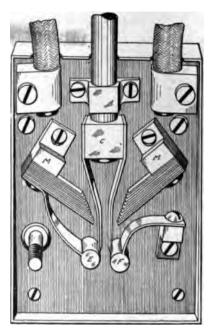


Fig. 176. Ward-Leonard "Harpoon" Starting Switch

ing the battery connections from the multiple arrangement used for lighting to the series connection necessary to send the full voltage and



Fig. 177. Packard Electrical Control

current of the battery through the starting motor. This is the case with the U.S.L. system, which is made in either 12—6-volt or 24—12-volt forms.

Fuses. Standard practice favors the employment of fuses on all the lighting circuits to protect the battery in case of short-circuits

in any of the wiring. They were originally considered unnecessary on two-wire systems, but have since been adopted on the latter as well as on the single-wire system. Such fuses are of the cartridge type of miniature size, as shown in Fig. 179, which represents a Westing-

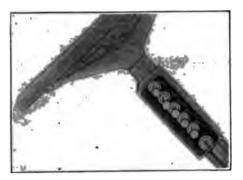


Fig. 178. Overland Electrical Control

house fuse block, and do not produce a flash when they blow, which is a safety feature of importance in the presence of gasoline. The appearance of a black spot on the label indicates that the fuse has burned out, or these fuses may be had in glass tubes through which the fuse wire is visible.

A double reading am-

meter, mounted on the dash and illuminated at night by a hooded lamp, shows whether current is being sent into the battery or being taken out of it, the needle usually moving over a scale to the right of the neutral line for charging and to the left for discharging, Fig. 180. This dash lamp is usually connected in series with the tail lamp,



Fig. 179. Type of Fuse Employed on Lighting Circuits

so that when it goes out it is an indication that the tail lamp is out as well. A voltmeter sometimes is provided to indicate the condition of the battery. In the Bosch system, this is combined with the lighting switches, as shown in Fig. 181.

In some systems, an indicator is employed instead of an ammeter, a movable target appearing at a small opening in the instrument and simply reading

"Off" and "On" or "Charge" and "Discharge". Such an instrument need not be so accurate as an ammeter and is more durable. These indicators never came into general use, however, and will be found on comparatively few cars, usually models of two or three years ago.

Electric Horns. The use of a storage battery which is of sufficient capacity for starting purposes and which is kept constantly charged by the lighting generator has made it possible to employ numerous auxiliary electrical devices. The electrical horn is the

chief of these, and it has to a very large extent displaced warning devices of every other class. Two different types of electric horns are used, in both of which the sound is produced by the vibrations of a sheet-metal diaphragm several inches in diameter. The only difference between the two forms lies in the method of causing this diaphragm to vibrate, one employing a small electric motor and the other a simple electric

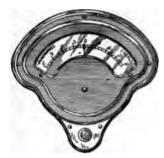


Fig. 180. Gray and Davis

magnet. Fig. 182, which is a phantom view of the operating mechanism of a Klaxon horn, shows the first type. On the upper end of the armature shaft of the electric motor is fastened a toothed wheel which strikes the button in the center of the dia-



Fig. 181. Bosch Voltmeter and Switches

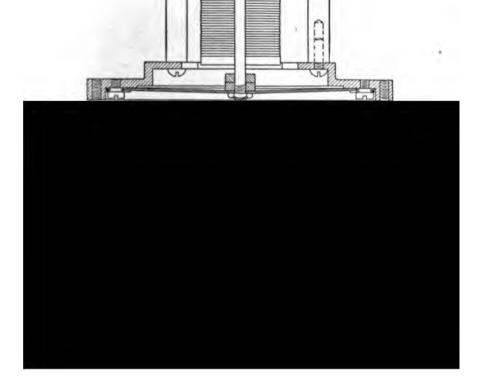


Fig. 182. Phantom View Klaxon Horn

phragm and sets it vibrating at the rate of several thousand times per minute, giving rise to the raucous squawk which has come to be identified with automobile warning signals. As shown in Fig. 183, which illustrates a section of the Apollo horn, this type is nothing more nor less than an ordinary buzzer on an enlarged scale.

The armature of the electromagnet vibrates at high speed producing a sound by taps on the rod attached to the diaphragm.

Care of the Electric Horn. As the operation of the electric horn is based upon exactly the same principles as the essentials of the starting and lighting systems, the instructions given for the care and adjustment of the latter will apply to it as well. In the case of the motor-driven type of horn, the commutator and brushes of the motor will require attention from time to time. Failure to operate may be due to a broken connection at the horn or at the battery; ground in the circuit between it and the battery; brushes not bearing properly on the commutator; or an excess of oil and dirt on the latter. If the motor runs properly, but the horn produces either no sound or a very weak sound, the trouble will be due to the poor contact of the toothed wheel with the button on the diaphragm. This button is made



#### LIGHTING

For automobile headlights, side lamps, tail lamps, and general illumination, electric lighting has superseded all other systems. In the best electric-lighting systems the current is supplied by a dynamo driven constantly by the engine, with a storage battery auxiliary.

Incandescent Lamps. Tungsten and Other Filaments. Incandescent lamps are usually provided with tungsten filaments. These filaments are much shorter and much stronger than in standard lamps, a condition that is further contributed to by the necessities of low voltage and high amperage, which require short and thick rather than long and thin filaments. A good tungsten lamp will afford 1 candle power of illumination for each 1.2 watts of current.

Mazda Type. Fig. 184 shows the standard types of lamps generally used. These are Westinghouse Mazda lamps for 6 volts, those at the left being 15 c.p. headlight lamps; the next two, 6 c.p.



Fig. 184. Westinghouse Lamps-Head, Side, and Tail

side-light lamps; and the smallest one is a 2 c.p. size designed for the tail light, meter light, and for interior lighting of closed cars. At 6 volts, the 15 c.p. lamps require 2.5 amperes, the 6 c.p. side lights 1.25 amperes, or where 4 c.p. lamps are employed—a better size for the purpose—.85 ampere; the 2 c.p. lamps take .42 ampere. The larger lamps have the filament in the form of a spiral coil occupying the minimum space so that the whole source of light can be placed at the exact focus point of the paraboloidal reflector.

Bosch Type. Fig. 185 shows the Bosch lamps, which are of special form. The headlight lamp at the right is of 25 c.p. and has the filament stretched horizontally across wire supports, while the side lamps of 8 c.p. have a loop of corrugated wire, and the tail lamp, of tubular form, a single filament running straight across it. Tail lamps are usually in series with the instrument lamp so that failure of the latter to light also indicates a failure of the tail lamp.

Lamp Voltages. When Edison was asked how he came to hit upon 110 volts as the standard for incandescent lighting, he said he "just guessed it". Evidently the 6-volt standard


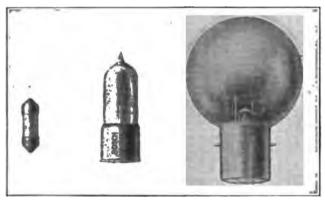


Fig. 185. Bosch Type Automobile Incandescent Bulbs

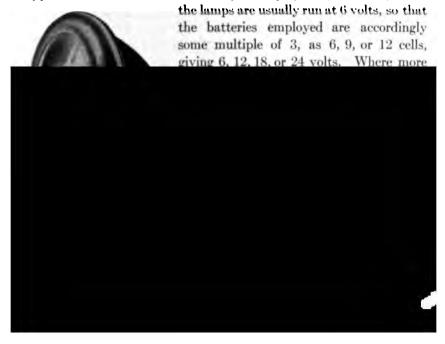came about in pretty much the same way. It is not practicable to operate small lamps at a high voltage, as the lamp of that type requires a long slender filament. Many manufacturers of starting apparatus have deemed it necessary to employ a higher voltage, but



Reflectors. Much attention has been directed to the problem of defining the best type of reflectors for automobile headlights, and the

conditions of lighting by acetylene gas have been determined to be very different from those involved when electric lighting is used.

Parabolic Type. A typical electric headlight for automobile use is that illustrated in Fig. 186. The plain form affords a minimum tendency to catch dirt and mud and greatly simplifies cleaning. The position of the lamp is adjusted to give correct focus, as this is essential to give a properly projected beam of light ahead on the road.

Comparison of Parabolic with Lens Type. The reflector in the foregoing lamp is of the deeply parabolic metal type, illustrated in Fig. 187. The advantage of this type of reflector is that it intercepts a much larger proportion of the light rays from the lamp than the lens-mirror type of reflector, Fig. 188.

Types for Various Locations. Fig. 189 -a, -b, -c, -d, and -e show the usual types of lamps employed. These are, in the order given, an outside side lamp, flushtype side lamp, two types of electric tail lamps, and a cowl or dash lamp for illuminating the instruments, such as the ammeter, oil

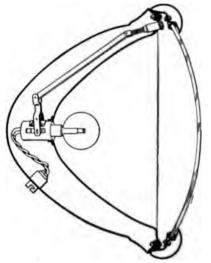


Fig. 187. Section of Fig. 186

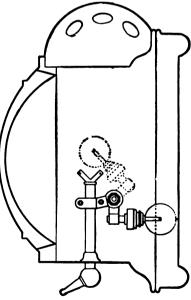


Fig. 188. Early Type of Reflector

telltale, and the like. Fig. 189-f shows a magnetic trouble-hunting lamp, the base of which attaches itself to any metal part of the chassis.

Headlight Glare. The increased efficiency of electric headlights has brought with it, in far more aggravated degree, the blinding



Fig. 189. Types of Side, Dash, Tail, and Trouble-Hunting Lamps

glare first experienced with the acetylene lamps. Originally, strong headlights bothered pedestrians; but since the introduction of electric



Dimming Devices. Owing to the fact that glare and illumination are so closely related and that there is no objection to glare on descrted country roads where the necessity for road illumination is greatest, permanently dimmed lights are naturally not practicable.

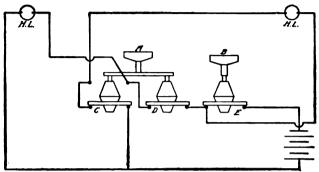


Fig. 191. Wiring Diagram of Parallel Control for Dimming Headlights

Courtesy of Horseless Age, New York City

What is required is a device under the control of the driver, so that either the full illuminating power of the head lamps or a subclued or dispersed light, free from glare, may be had as required.

A great many fundamentally different devices have been offered as a solution of the problem. While differing radically, practically

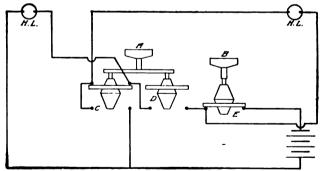



Fig. 192. Wiring Diagram of Series Control for Dimming Headlights

Courtesy of Horseless Age, New York City

all of them may be classed under two heads, i.e., electrical and mechanical.

Electrical Devices. One of the simplest of this class that has met with considerable favor is nothing more nor less than a resistance that may be inserted in the circuit of the headlights by turning a

small switch, mounted either on the steering wheel or in some other easily accessible location. This cuts the voltage down and causes the lamps to burn a dull red, instead of the filaments being the dazzling white reached at full incandescence. A dimmer of this type is shown in Fig. 190. An equally simple and practical device is a switch to throw the headlights into series for a dim light and back into parallel again when full illumination is desired. With the series connection, the current must pass through both lamps successively and each bulb thus receives but half the voltage and, as even a comparatively

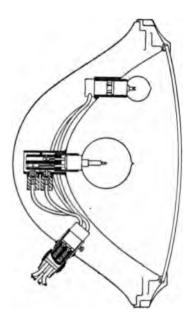

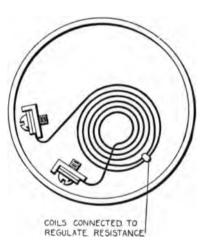


Fig. 194. Variable Dimming Resistance

Fig. 193. Section of Hall Double Headlight

slight drop in voltage causes the efficiency of an incandescent lamp to fall off very markedly, the same result is attained. It is equivalent to burning a 6-volt lamp on a 3-volt current. With the normal, or parallel, connection, the current flows through each lamp separately, and both receive the full voltage of the battery so that they burn at full brilliance. A switch of this kind is marketed by the Cutler-Hammer Company. Fig. 191 illustrates the connections for parallel arrangement, or full illumination, switches D and B being closed and the button A pulled out to make C contact with its lower set of

comestions. Fig. 182 shows the connections for series burning, effected by pulling out button B and pushing in A, this closing when E opening I and contacting I with the upper connections.

The use of two nulse or each headlepin is also commonly resorted to the method of effecting this being shown in Fig. 193. The second pulb is or the size ordinarily employed for side lights and is, moreover, entirely out of the focus of the reflectio, so that the diminished light to out-of is entirely without gives and is mostly diverted downward.

Inserting a resistance in the headilght circuit is also done to the treadilights. Fig. 184 shows a method of adjusting the mouse of the dimmers. The rolls are connected together by a new of virtue as shown. This cuts out some of the resistance and ones the lights to form freighter. Any desired intensity may be served to emperimenting with the position of this jumper.

# PRACTICAL ANALYSIS OF TYPES EXPLANATION OF WIRING DIAGRAMS

Symmatics of Symbols. To be successful in running down the true of before a in a starting and lighting system on a car to see first deal a involving of the most likely places to seek the truth. These the truthe is very apparent or becomes so upon that the subject tests, a process of elimination must be carried that the truthe subject tests, a process of elimination must be carried that the perfectly familiar with wiring system, the trouble hunter that the perfectly familiar with wiring systems in general. To the most true truther diagrams are nothing more than a jumble of lines, there is no the first thing to achieve. Their direct bearing upon the transfer relation of the essentials described in the introductory to fluctual Francisco. Part I, will at once be apparent.

the signs. — positive. — negative, scarcely call for any extended explanation. They in fleate the direction in which the current flows. It is of the utmost importance, where the manufacturers' directions are to connot certain apparatus with a given wire to the plus, or positive, side, and another wire to the negative, that these instructions be followed explicitly. Otherwise, the apparatus either will refuse to work or it may be damaged, as in the case of a storage battery on which the connections have been reversed. Wherever

### ELECTRICAL EQUIPMENT

315

Positive

Negative



Fig. 195. Battery, Either Storage or Dry Cells



Fig. 196. Generator, Commutator, and Brushes



Fig. 197. The Proper Method of Showing a Coil Which Surrounds an Iron Core but Very Seldom Used on Delco Drawings



Fig. 198. The Method Used in Showing a Coil Where There Is No Chance of Confusion—Used in Field Coils, Ignition Coils, Etc.



Fig. 199. The Method Used to Show Resistance Such as a Resistance Unit and Charging Resistances





Fig. 200. Ground Connection Where the Wire Is Connected to the Chassis, Engine, or Generator



Fig. 201. Contact Points Such as in Switches, Distributors, Etc.



Fig. 202. Method Used to Show Lighting Switches



the battery may be told at a glance. Other sources of such as generators, are indicated by a conventional sign of a circle with two short heavy lines tangent to its circulat opposite points and usually at an angle to the horist shown in Fig. 196. The origin of this sign will be appaare emblance to the end view of a commutator with a pair of bearing on it. This sign is also used to indicate a motor, case the letter M is inserted in the circle.

Coils. Coils which are wound on an iron core are indicated by a conventional sign consisting of a few loop as in Fig. 197, but this is only the case where such a coil of place in the circuit where there might be a chance of considentifying it. Where there is no possibility of confusion the case of the windings of a generator or motor, ignition the like—the sign shown in Fig. 198 is often used. When are heavy, a coarse wire, such as is employed for series will generators or motors, or the primary winding of an ignition is intended.

Resistance. Resistance in a circuit is usually show arbitrary sign, Fig. 199, similar in outline to a piece of the grid frequently used in charging resistances, though a shown as a coil and marked "resistance".

Grounds. The sign of a ground connection is the pyramid of short lines, Fig. 200, and indicates that the





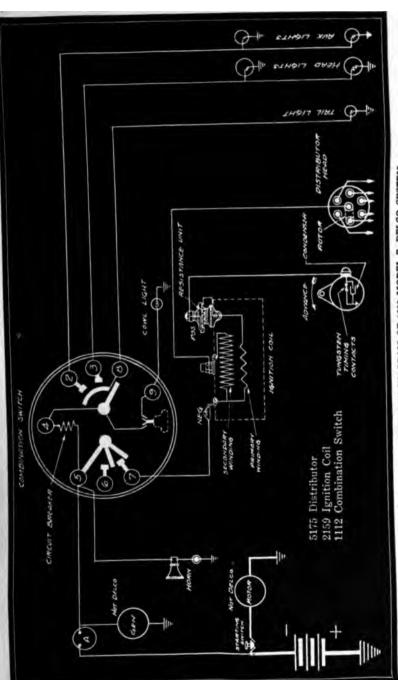


PLATE 81-JORDAN WIRING DIAGRAM OF 1980 MODEL F, DELCO SYSTEM

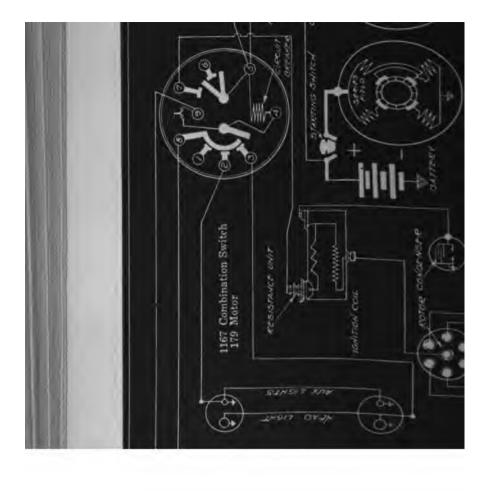

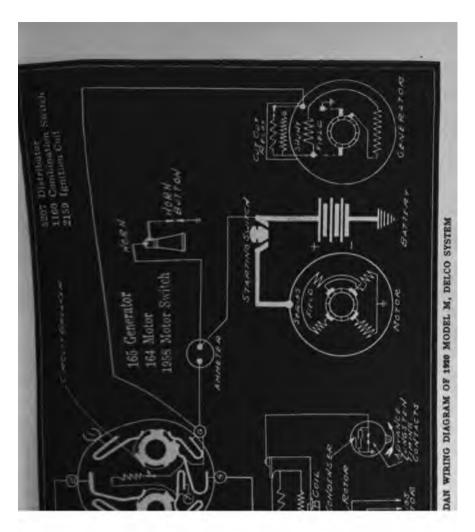

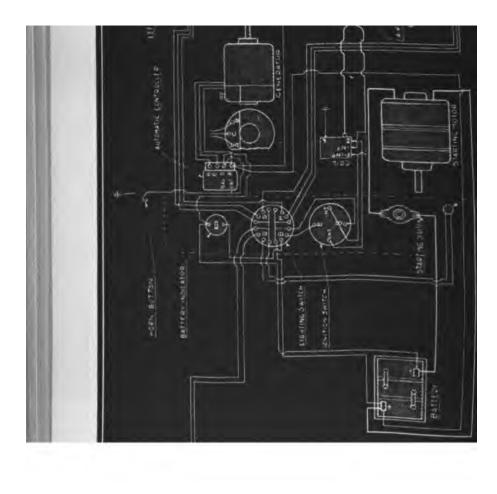

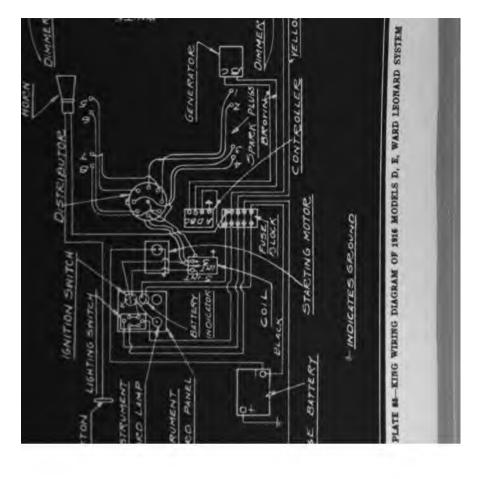

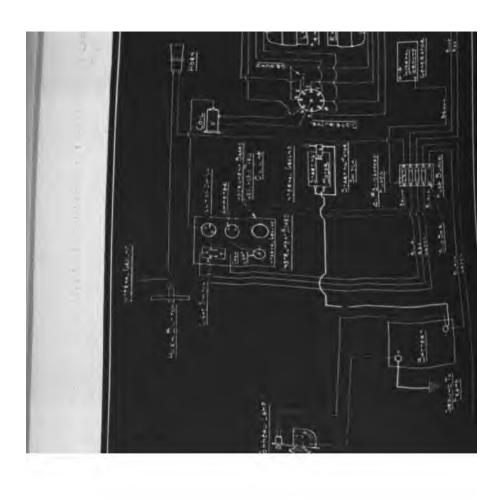


PLATE 87-KING WIRING DIAGRAM OF 1930 MODEL H, WESTINGHOUSE SYSTEM



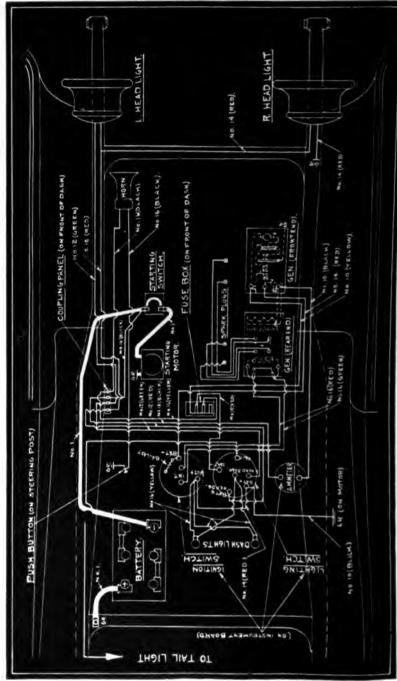


PLATE 88 KISSEL WIRING DIAGRAM FOR 1915 MODEL 4-36, WESTINGHOUSE SYSTEM

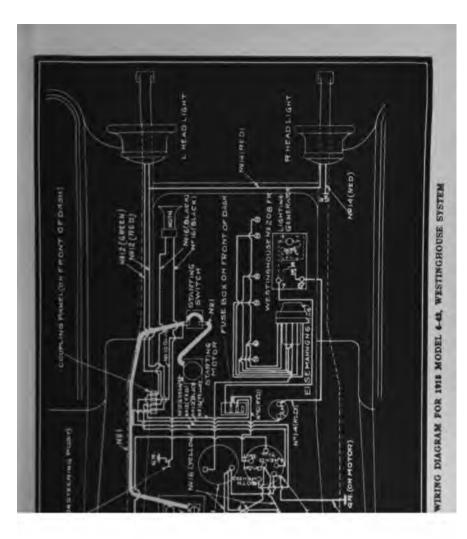

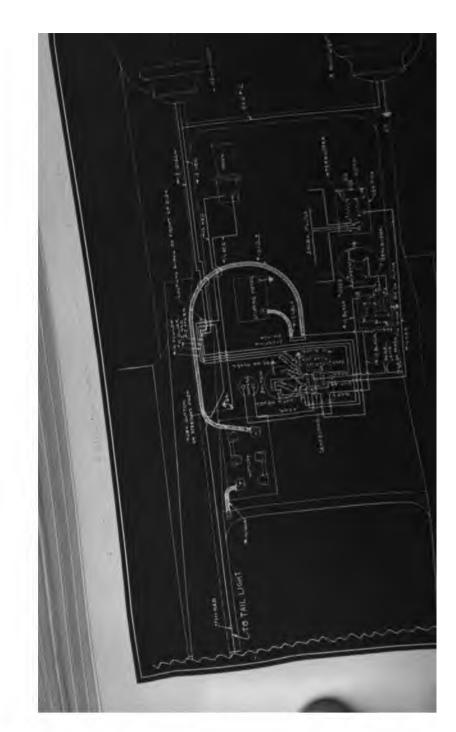


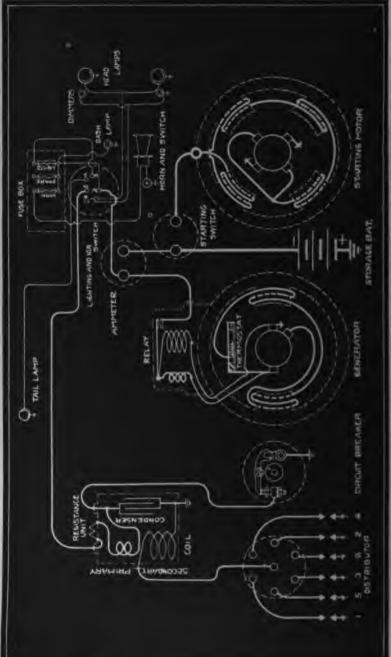


PLATE 49-EISSEL WIEING DIAGRAM FOR 1818 ONE HUNDRED POINT SIZ, REMY SYSTEM

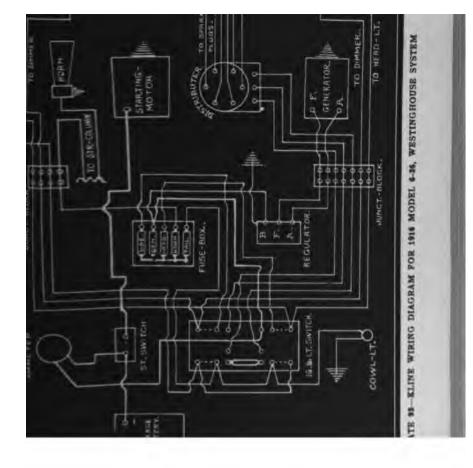


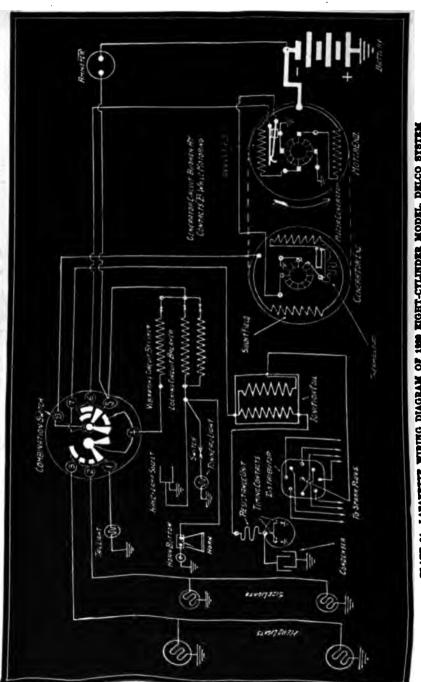


PLATE 94-LAFATETE WIRING DIAGRAM OF 1999 EIGHT-CTLINDER MODEL, DELCO STSTEM

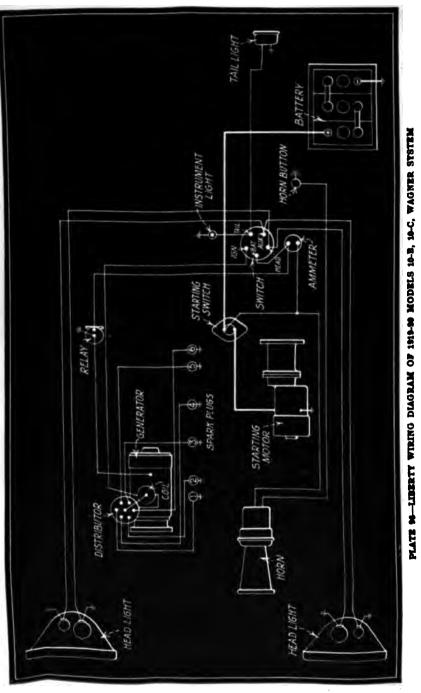

arbitrary character, such as Fig. 201, which shows contact such as used in switches, distributors, etc., and Fig. 202, which indicates a lighting switch (Delco diagrams); they usually will be found to bear sufficient resemblance to the apparatus itself to make their identification easy.

Induction Coil. Fine lines indicate a generator shunt winding, the secondary of an ignition coil, or the coil of a relay or cut-out. The primary and secondary windings of an induction coil as used for ignition are indicated by a fine and a coarse coil sign, as in Fig. 203.

Condenser. A condenser with its overlapping plates is shown in Fig. 204.


Crossed Wires. To show wires that cross one another without making connection, a half loop is made at that point to show that the wires do not touch, as in Fig. 205, while wires that are connected are shown by a black dot at the junction.

General and Special Usage. While these signs are not universally used in exactly the form shown here, their employment is very general and in the majority of cases, such as the positive and negative, battery, ground, generator, induction-coil windings, and foil signs, they are never changed. In some instances special signs are employed, such as that shown in Fig. 206, which indicates the motor commutator of the Delco single-unit machine or dynamotor, and shows the special brush lifting switch. Incandescent lamps

are almost always indicated by small circles, though the lamp itself

side of the diagram, the generator is shown with its shunt-field winding, one brush of the generator and the shunt coil being grounded. This is a complete circuit. but. as the shunt coil has a high resistance, only a very small part of the current flows through The series winding of the generator is shown at the top and the explanation that this is a "reverse" series coil means that it is wound to have a polarity opposite to that of the shunt coil. It accordingly opposes the shunt coil at the higher speeds and serves to regulate the output of the generator. This is the familiar bucking coil or "reversed compound winding".

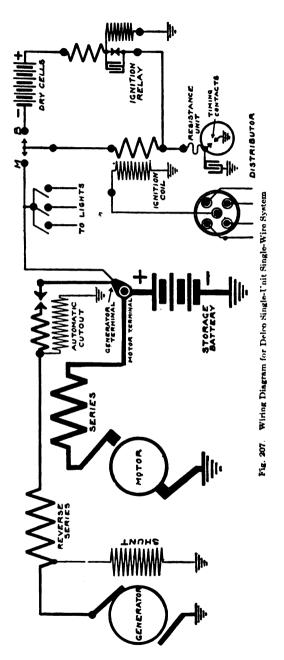
To reach the battery, the current from the generator must pass through the automatic cut-out, the two windings and the contact points of which are shown a little



further to the right along the top line. If the ammeter on the dash fails to register any charging current when the engine is running at a speed equivalent to 10 miles an hour or more, the automatic cutout would be the first place to seek a break in the system. Under
normal conditions of working, the cut-out closes the circuit as soon
as the generator reaches a certain speed and the 3-cell storage battery, one side of which is grounded, is then being charged, the current
entering at the plus or positive terminal and returning by way of the
minus terminal or pole through the ground connection. (In some
systems, such as the Gray & Davis, the frame of the car is the positive side of the circuit.)

Between the generator and battery circuits is shown the starting-motor circuit. The width of the lines employed indicates that very heavy conductors are used in this circuit and they are necessary owing to the extremely heavy currents handled. The series winding of the motor field is also short and of heavy wire. The upper brush of the motor being in a raised position indicates that the motor is brought into operation through a switching brush, and when this switch is closed to start, one of the generator brushes is raised from the commutator. This completes the generating, starting, and controlling circuits, all of which are shown to the left of the battery. The relative difference in thickness between the wires of these circuits at the left and those at the right for the lighting and ignition show the difference in the amount of current handled

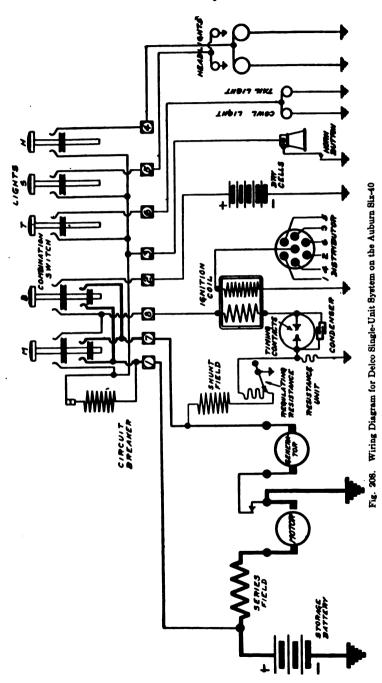by the two. The double set of contact points at the center clong




unit and the timer, and the latter directly—are plain. But it also will be noted that a condenser is shunted around the sparking contacts of the timer, one side being connected to the contact terminating the positive side of the circuit, while the other is grounded. The function of a condenser here is to absorb the charge or surge of current due to the sudden opening of the contacts (breaking of the circuit) and to prevent the formation of an arc which would burn the contact points away rapidly. Badly pitted or burned contact points accordingly are an indication that the condenser has broken down or become disconnected from the circuit. This also will be evident from the excessive sparking at these contacts when the engine is running. The secondary winding of the coil is grounded directly. At the right-hand end of the diagram is seen the independent circuit of the dry-cell battery for emergency use in starting. The current from this battery passes through a relay coil the contact points of which are also provided with a condenser for the purpose already explained.

Auburn-Deko Type. The wiring diagram of the Delco lighting, starting, and ignition system of the Auburn, Model 6-40, Fig. 208, is more completely shown than the one to which reference was made above, in that all the switching connections are indicated and the lamp circuits have been carried out. Examination will also show that it differs in other respects as well. For example, instead of a bucking-coil type of regulator winding, the generator output is controlled through a variable resistance in the shunt-field circuit, the

emount of resistance increasing with the speed. As the current

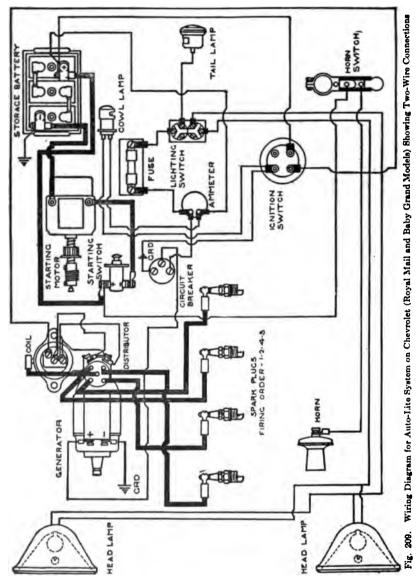"return" side of the circuit, the steel sections forming the frame of the car may be utilized for either the positive or negative side.



The wiring diagram, Fig. 209, which is that of the Auto-Lite system as applied to the Chevrolet is of the two-wire type. With

## ELECTRICAL EQUIPMENT

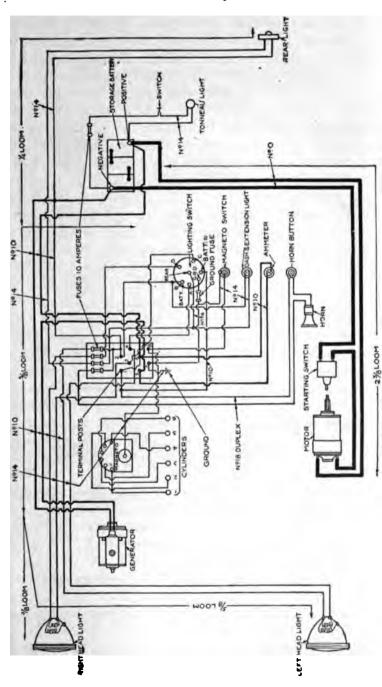


Fig. 210. Wiring Diagram for Bijur Two-Wire System on the Jeffery Chesterfield Six (1916 Model)

the exception of the ignition circuit, which is always grounded owing to the spark plugs completing the circuit by being screwed into the cylinder heads, it will be noted that two-wire connections are made. The ignition circuits are completed by a ground at the battery for the starting current, and by another at the generator for the current when running. The circuit breaker is also grounded.

Jeffery-Bijur Type. The two-wire system of the Bijur as installed on the Jeffery Chesterfield Six is shown in Fig. 210. lighting circuits are fused and there is also a fuse in the ground connection for the ignition. The numbers referring to the various circuits indicate the proper size of wire used in each circuit. This is an important item in every starting and lighting system, as, where any wires have to be replaced owing to mechanical or electrical injury, they must always be replaced with wire of the same size and character of insulation, as otherwise, further and more serious trouble is apt to follow. Thus, for the starting circuit No. 0 (Brown & Sharpe gage) cable is employed; for the charging circuit between the generator and battery No. 10; for the lighting circuits No. 14, which is the size ordinarily employed for incandescent-lamp circuits in house wiring; and for the horn No. 18. "Duplex" in this connection means that both wires of the circuit are enclosed in the same braided insulation. "Loom" is tubular fireproof insulation through which the wires are passed to afford further protection, and the sizes vary in accordance with the size of the wires.

#### USE OF PROTECTIVE AND TESTING DEVICES

Circuit Breaker. This is a protective device, the theory of which will be clear at once upon referring back to the explanation of an electromagnet in the introductory chapter. It consists of an electromagnet with a movable armature adapted to open the circuit by its movement, the latter being controlled in turn by the amount of current flowing in the circuit.

By referring back to the diagram, Fig. 208, and noting the particular function of the circuit breaker, an excellent example of the value of ability to trace wiring diagrams at a glance can be shown. Assume that when the button M of the combination switch, Fig. 212, is pulled out, the ignition fails to work. An examination of the diagram shows that when M is pulled out, its lower contact bridges

the wires No. 1 and No. 7 connecting the generator with the battery. At the same time its upper contact bridges a pair of terminals which insert the circuit breaker and the ignition coil on cable No. 8 in the circuit. Further examination of the ignition or lighting circuits shows that throwing on any one of these circuits includes the circuit breaker. The function of the latter is to prevent the discharge of the battery when the generator is standing idle or running too slowly to generate the necessary voltage to charge the battery. also serves to protect the lamps, ignition coil, and horn from damage, in case any of the wires leading to these essentials should become grounded, and in this rôle takes the place of fuses and fuse block. As it requires 25 amperes to operate the circuit breaker in this particular instance, it is not affected by the normal operation of the lamps, ignition, or electric horn. But in the case of a short circuit or ground, the whole output of the battery would pass through the circuit breaker, moving its armature and breaking the contacts. which open the circuit. This cuts off the current and a spring brings the contacts together again, when the operation is repeated, causing the circuit breaker to vibrate and pass an intermittent current of comparatively small value. While it will not break the circuit on less than 25 amperes, it will continue to vibrate on a current of 3 to 4 amperes. Its continued vibration is an indication that there is a ground in one of its circuits. Hence, no attempt should be made to stop this action by tightening the spring of the circuit breaker, but by locating the ground.

Tracing for Grounds. This can best be done by a process of elimination in which a knowledge of the wiring diagram will come handy. Referring again to Fig. 208, if the circuit breaker operates when switch M of the combination is pulled out, it will be apparent that the ground is located in either the main generator-battery circuit, or the ignition-coil circuit, as it will be seen that the lower contact member of the switch throws the former in the circuit and the upper contact member throws the latter in the same circuit with the circuit breaker. If pulling out M does not set the circuit breaker operating, but pulling out M does not set the circuit breaker operating, but pulling out M does, this would indicate a ground in the circuit of the tail and cowl lights, while the operation of the circuit breaker on pulling out either M or M, would indicate that the ground was located in the wiring of either the side lights

or the headlights depending on which switch caused the circuit breaker to respond. The combination switch B serves to connect the generator and storage battery in the circuit, the same as M, but it also includes the 5-cell dry battery in the ignition circuit. It will be noted that the distributor has six spark plug leads, indicating a 6-cylinder engine, also that the connection of the ignition timer in the circuit is somewhat different from the previous diagram, Fig. 207, in which it is on a branch circuit of the storage battery, whereas in this instance it is also in the generator circuit.

Having determined the particular circuit in which the fault lies it is next necessary to narrow it down to exactly the defection that is causing the ground. For work of this nature nothing handier can be devised than the simple testing set which is described later and which may be assembled at nominal expense.

Fuses. The lighting circuits of many cars are provided with fuses, designed to protect the battery. These fuses are usually of the enclosed type, consisting of a glass tube with brass caps at each end to which the fusible wire is connected, as shown in Fig. 211, Usually when a fuse "blows", due to excessive current caused by a ground or "short", the wire melts entirely and this will be visible. But at times it will simply melt at the soldered connec-

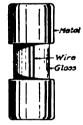


Fig. 211. Typical Fuse

tion and not show any fault. In beginning a test it is well to go over the fuses first, holding one of the test points of the lamp circuit on one end of the fuse and touching the opposite end of the fuse with the second test point. Failure of the lamp to light will indicate the defective fuse. On systems employing a circuit breaker as shown in the wiring diagram, Fig. 208, no fuses are necessary as the circuit breaker serves the same purpose and also gives an audible signal of trouble by its buzzing. Upon finding an open circuit where one is supposed to exist as shown on the wiring diagram, it is always well to verify this by again testing the trouble lamp itself before beginning to tear anything out. The rough handling to which such a lamp is subjected frequently causes the filament to break.

If immediately upon being replaced, a fuse again blows, it may indicate that one of the lamp circuits of the car is short-circuited or the lamp on that circuit is defective, having become short-circuited,

#### **ELECTRICAL EQUIPMENT**

the remedy being a new bulb. In some systems, fuses are used in other circuits, as in the case of the Bosch-Rushmore in which there is a fuse on the switch block to protect the main shunt winding of the generator. The blowing of this fuse indicates a broken battery connection, such as a loose or broken terminal or a corroded battery connection on the cells themselves.

Handy Test Set. Take a porcelain base socket, screw it to a piece of board to form a base. Connect one side of this lamp socket

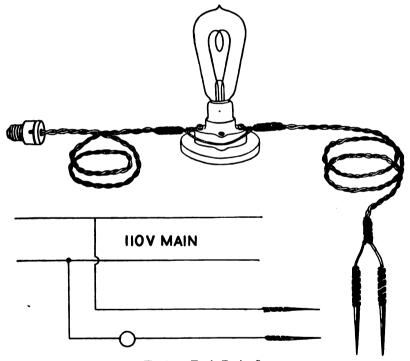


Fig. 212. Handy Testing Set

to a standard screw plug. Procure two pieces of brass or steel rod and file or grind them to a long tapering point. These rods should be about 6 inches long and tapering half their length to a sharp point. Connect the other side of the lamp socket to one of these points and connect the second point to the other terminal of the screw plug. Ordinary lamp cord can be used for the connections. For fastening to the test points it should be bared for several inches, wrapped solidly around the metal rods at their blunt ends, and

soldered fast in place. The joints should be heavily wrapped with tape or covered with other insulating material to form a handle, as shown in the illustration, Fig. 212, As shown by the diagram forming part of this illustration, it will be seen that the lamp is in series with one of the points, but that when the circuit is closed by bringing the two points together, the lamp is in multiple with the main circuit. The lamp should be of the carbon-filament type

owing to its greater durability. As a lamp of this type of 16 c-p. only consumes a little over 50 watts at 110 volts, or approximately half an ampere of current, there is no danger of injuring any of the apparatus on the automobile through its use. Sufficient cord should be allowed on either side of the lamp to permit of connecting it up with the outlet conveniently.

In using this test outfit, the two test points are pressed on places between which no current should pass, and if the lamp lights it indicates that there is a ground between those points. For example, in Fig. 208, if there were a ground between the generator and the switch so that no current reached the latter, the lamp would not light when the test points were placed on terminals 1 and 7 of the diagram, the generator then being in operation. But a little searching along this circuit would soon show where it was grounded, thus making it easy to locate the break or ground. Fig. 213 is a graphic illustration of a ground causing a short circuit,


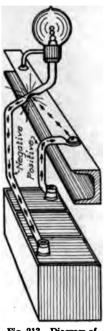


Fig. 213. Diagram of Ground or Short Circuit Courtesy of Gray and Davis Company

due to worn insulation. Much more satisfactory results can be obtained with a test set of this nature than with either an expensive hand ringing magneto test set, or with a set consisting of a bell or buzzer and a few dry cells. The former is unnecessarily expensive for the purpose while the latter has not sufficient potential to force the current through grounds or breaks that present too great a resistance, whereas the higher voltage of the lamp test set will cause it to give an indication where the battery set would not. With the aid of such a set, every circuit shown on even the most complicated of

wiring diagrams can be tested in fifteen to twenty minutes, maybe less, depending upon how accessible the connections of the various circuits happen to be.

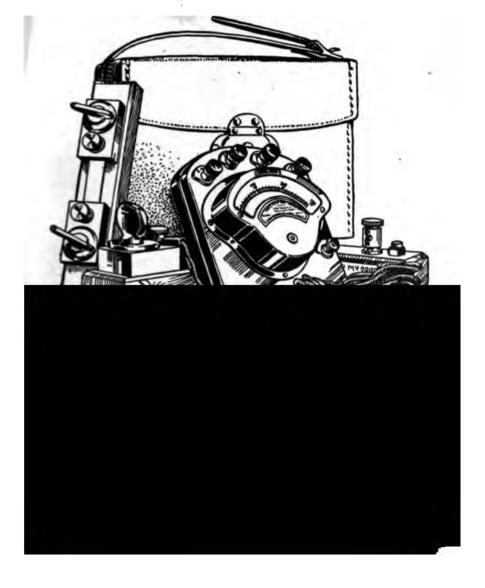If preferred, owing to greater convenience, a 6-volt lamp can be used in the socket of the test set and current from the car battery can be utilized for testing. In case the car happens to have either a 12-volt or a 24-volt system, connect lamp terminals to but three of the cells. Should the lamp not light to full incandescence it



Always Test the Lamp. Whether a standard 110-volt lamp or one of the 6-volt type (for which an adapter may be necessary to fit the standard socket) is used, it is a good precaution always to test the lamp itself before going over the wiring on the car. This will avoid the necessity for blaming things generally after failing to find any circuit at all—after fifteen miutes of trying everything

on the car—due to the lamp having a broken filament or one of its connections having loosened up.

Special Testing Instruments. For the garage that claims to be fully equipped to give all necessary attention to the electrical system of the modern car. something more than the simple lamp testing outfit is necessary. Portable voltammeters such as shown in Fig. 214 are made specially for this purpose. This is a Weston combination voltammeter. the voltmeter being provided with a 0-30. 0-3, and 0 to  $\frac{1}{10}$  scales for making voltage tests, together with three shunts having a capacity of 0-300, 0-30, and 0-3 amperes, respectively, which are used in connection with the

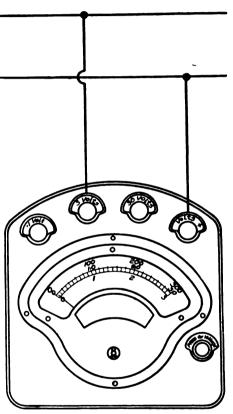


Fig. 215. Diagram Showing 3-Volt Scale Connected across a Circuit

To-volt scale for making current measurements. A special set of calibrated leads for use with these shunts is also provided. With the aid of such an outfit, accurate tests can be made covering the condition and performance of every part of a starting-lighting and ignition installation. For example, a starting system may be otherwise in perfect working condition, but its operation causes

such an excessive demand on the storage battery that the generator is not capable of keeping the latter sufficiently charged. Generator tests, which are described later, having failed to show anything wrong with the dynamo, a test of the starting motor, using the 0-300-ampere shunt of the instrument would doubtless show that an unnecessarily large amount of current was being demanded

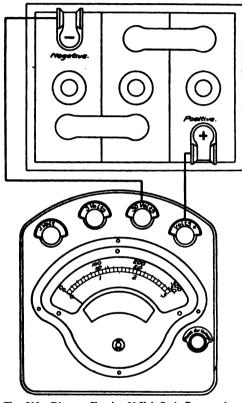


Fig. 216. Diagram Showing 30-Volt Scale Connected across Storage Battery Terminals

by the motor for its operation, and indicate a fault in the latter.

Voltage Tests. When the instrument is used as a voltmeter it is necessary to select the proper scale for the circuit, and if there is any doubt it is well to start with the 30-volt scale. For testing individual cells of the storage battery the 3-volt scale would naturally be used, while for testing the entire battery, the 30-volt scale would be the proper one to apply. The proper method of connecting the voltmeter to the circuit is shown by the diagrams, Figs. It is nec-215 and 216. essary to connect the positive side of the meter

to the positive side of the circuit and the other terminal to the negative. Where the polarity of the circuit is not known, this can be readily determined by a trial reading. If the pointer moves to the right, the connections are properly made; in case it moves to the left, it will be necessary to reverse the connections, which should be done at the circuit terminals and not at the meter, to avoid any accidental short circuits.

Ammeter Readings. When using the ammeter to determine the amount of current consumed by any of the apparatus, such as the starting motor or the lamps, it is necessary to first select the proper shunt. Should the value of the current to be measured be unknown, it is well always to start with the 300-ampere shunt

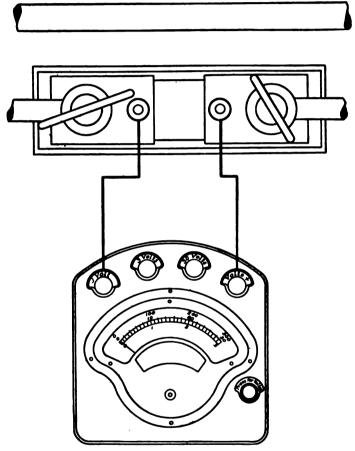


Fig. 217. Diagram Showing Method of Connecting Ammeter to 300-Ampere Shunt

and then insert the 30-ampere shunt in case the reading shows the current to be less than 30 amperes. These shunts are connected in the manner shown by Fig. 217, and as will be plain from this diagram, all shunts are connected in the circuit in a similar manner. The connections always remaining the same, it is only necessary

### ELECTRICAL EQUIPMENT

to substitute the different shunts as required by the circuit to be measured. If the polarity be reversed, it is only necessary to shift the connections from the ammeter to the shunt which should be done at the latter, there being no necessity to change the connections of the shunt itself to the circuit. The 300-ampere shunt must always be used for measuring the starting current, as the latter will rarely have a value of less than 200 amperes when the switch is first closed owing to the necessity of exerting great power at first to overcome the inertia of the gasoline engine, particularly at a low temperature when the lubricating oil has become gummed. Cables of the same size as those employed on the starting-motor circuit of the car should be provided for connecting up the shunt to make the tests. The 30-ampere shunt is employed for measuring the charging current to the battery, while the 3-ampere shunt is used for the individual lighting circuits or for the primary ignition current.

In the following section, the various systems in general use are described in detail.


# AUTO-LITE SYSTEM Six-Volt; Two-Unit; Single Wire


Generator. Three types of generators are furnished. One has a permanent magnetic field and resembles a magneto but can



Fig. 218. Auto-Lite Generator of the Bipolar Type Courtesy of Electric Auto-Lite Company, Tolcdo, Ohio

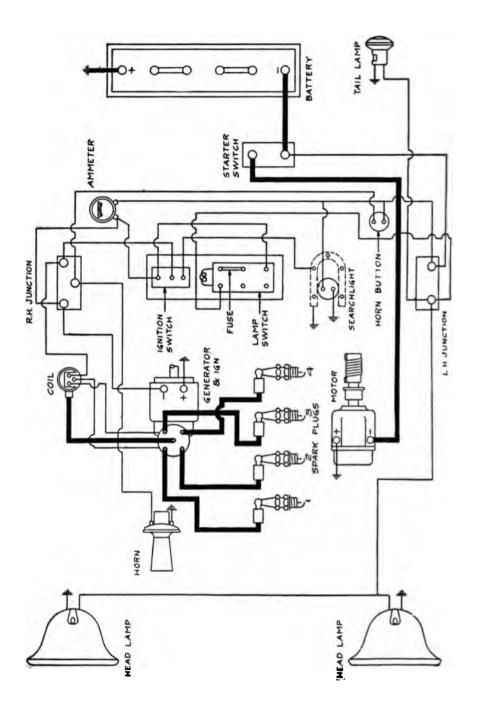be distinguished by its drive and governor, as well as the fact that it is fitted with a commutator and brushes instead of a contact



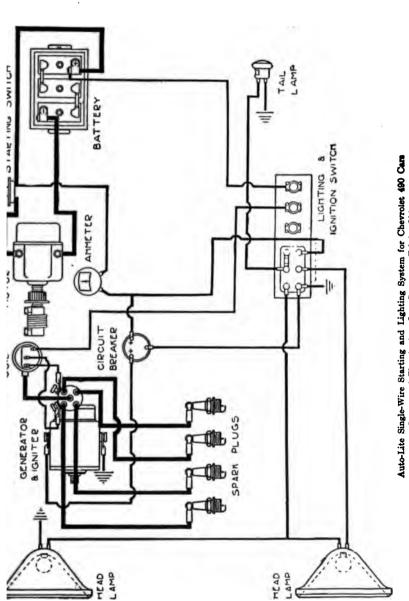

Courtesy of Electric Auto-Lute Company, Toledo, Ohio

breaker and distributor. It has been supplied chiefly for installation on cars which were not originally fitted with electric lighting and starting systems. The second is somewhat similar in design but has an excited field, the field magnets being of U-form and laminated; this type of generator is used on the Overland Model 82. There is a single field winding, as shown in Fig. 218. The third is a four-pole machine having two wound poles, usually termed salient poles and two consequent poles, which carry no windings. A diagrammatic section of this generator is shown in Fig. 219. The salient poles are those in the vertical plane while the consequent poles

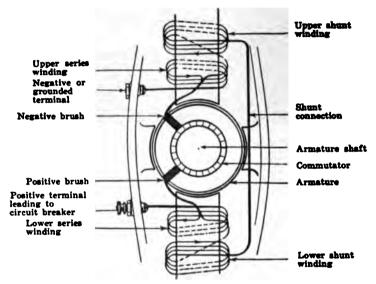


Fig. 219. Diagrammatic Section of Four-Pole Auto-Lite Generator

are horizontal. The diagram also shows the commutator, brushes, and the compound winding of the generator.

Regulation. The current output of the permanent-field type is regulated by a centrifugal governor; it should not drop below 10 amperes, nor exceed 12 amperes. Any falling off can be remedied frequently, simply by cleaning the governor out thoroughly with gasoline, allowing it to dry, and giving it a drop or two of light oil; if this does not increase the output sufficiently, the weights can be moved inward an eighth of an inch or more to decrease the pressure on the springs mounted in the governor arms, Fig. 220. This per-

mits the generator to run at a higher speed. The regulation of the other type is inherent and is due to the series windings of the field

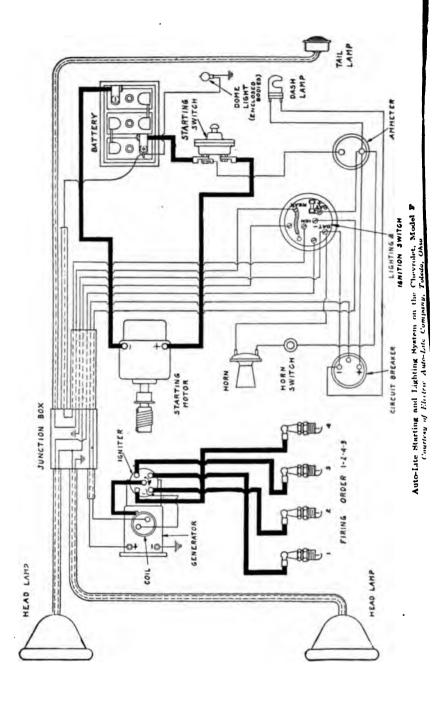



Fig. 220. Governor of Auto-Lite Permanent-Magnet Type Generator

being made in the reverse direction to that of the shunt windings, so that their polarity is reversed. This is commonly referred to as a bucking coil, also as a differential winding. As the speed increases, the magnetizing effect of the shunt coils is opposed by this bucking winding and thus kept within safe limits. This type of generator is used on the Overland Model 80 and Model 81, besides other cars.

Starting Motor. The starting motor

used on Overland Model 80 and Model 81). In this type the switch is combined directly with the motor, being mounted in a housing at the left end as shown in Fig. 221. It is also fitted with a special locking device, the details of which are illustrated in the sectional view, Fig. 222. One of the buttons on the control board on the steering column closes the circuit of the solenoid shown in this illustration; this causes the plunger to lift and release what is known as the gearlatch. The shaft carrying the switch also serves to shift the pinion on the end of the starting-motor shaft into mesh with the flywheel



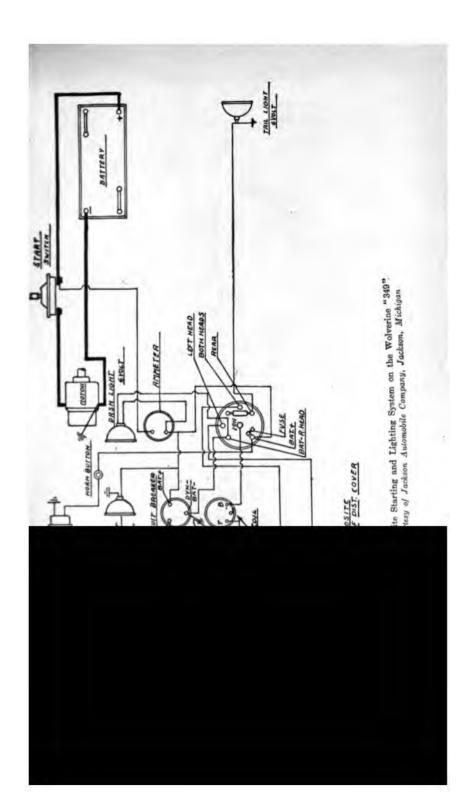

automatic operation which eliminates the necessity for gear-shifting devices actuated by the switch, when operating the starting motor.

The armature shaft has a threaded extension provided with an

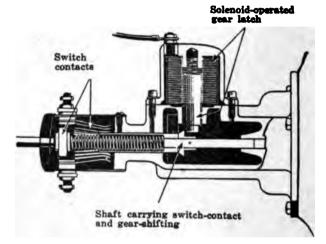


Fig. 222. Sectional View of Auto-Lite Starting Switch and Gear Release

outer bearing and carries a pinion. A weight is solidly attached to this pinion and the latter is loose enough on the shaft always to

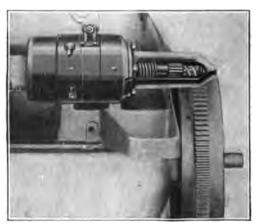


Fig. 223. Auto-Lite Starting Motor with Bendix Drive

occupy the position shown with the weight underneath when the shaft is idle. The leading screw has a triple thread. On starting the electric motor the inertia of the weight causes it and the pinion

## ELECTRICAL EQUIPMENT

to be carried along the shaft and into mesh with the gear on the flywheel in which relation it remains until the engine begins to run under its own power. This reverses the relation, the flywheel then driving instead of being driven, which automatically throws the pinion out of mesh. The coil spring shown is simply to take up the shock of starting and permits a slight play between the motor shaft and the threaded extension. Before the switch which is located on the footboards can be operated, a button on the control board must be pushed. This actuates a solenoid the plunger of which raises a latch, releasing the starting switch.

Battery Cut-out. The battery cut-out is shown in Fig. 224. As already explained, the majority of electric systems on the auto-


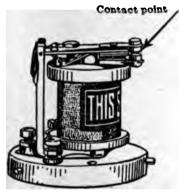


Fig. 224. Auto-Lite Battery Cut-Out (Circuit Breaker)


mobile must be provided with a cutout to protect the battery when the
generator speed falls below a certain
point. It is frequently referred to as a
circuit breaker, which it is in fact,
though the circuit breaker is a protective device used for another purpose,
as has been mentioned. The cut-out
may be compared to a check valve in
a water supply line between a pump
and a tank; the pump can force water
into the tank against its pressure but,
regardless of how great this pressure
becomes owing to the filling of the tank,

the water cannot run back through the pump when the latter is idle.

In principle, the battery cut-out is simply a magnetically operated switch. When the current passes through its winding the armature is attracted and brings a pair of contact points together. These will be seen at the upper right hand at the point of the arrow. In the best-grade apparatus, these points are of platinum or platinum and iridium as the latter is proof against oxidation as well as corrosion and resists pitting under the electrical current better than any other metal. As it costs more than gold, silver, which is next best for the purpose, is frequently employed. The cut-out in this case is set to close the circuit and allow the generator to charge the battery when the engine is driving the car at 7½ miles per hour, but

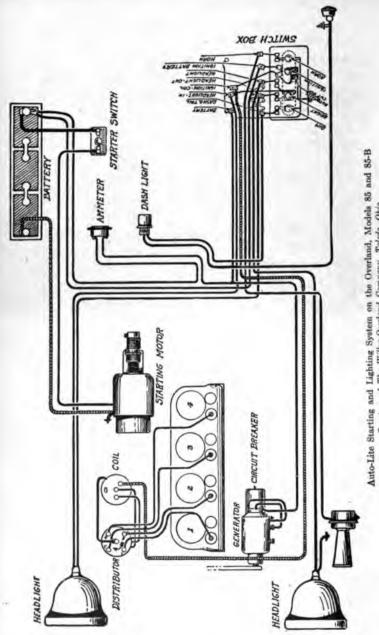

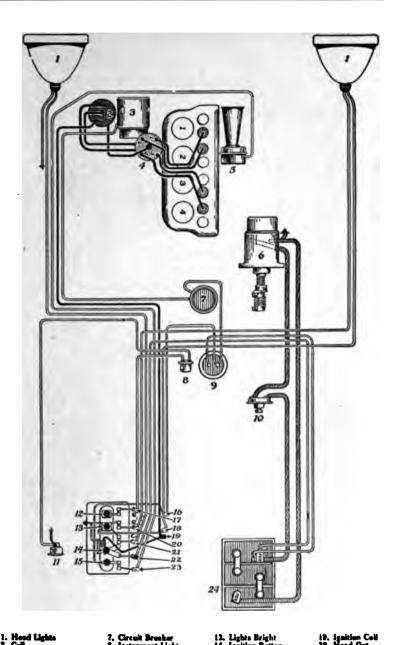Auto-Lite Starting and Lighting System on the Overland, Models 85 and 85-B Courtesy of The Willyn-Overland Company, Toledo, Ohio



Auto-Lite Starting and Lighting System on Overland Light Fours, Model 90-4 Courtesy of The Willys-Overland Company, Toledo, Ohio

when the speed is dropping it does not open the circuit until it falls to 6 miles per hour. This is to prevent the cut-out from operating continuously when the car is running at its opening speed of 7½ miles. The battery, however, governs to a large extent the running speed at which the cut-out will operate. When fully charged, owing to the higher resistance thus presented, the cut-out does not close the circuit until the car is running at 10 to 12 miles per hour. In case the cut-out is removed from the car for any reason, the latter must not be operated until a short piece of bare copper wire is securely connected from the wire terminal post of the generator to one of the brass screws in the name plate.


Instruments. The instrument regularly supplied is a double-reading ammeter showing *charge* and *discharge* from 0 to 15 amperes. When lamps are off with car running at 10 miles per hour or over, it should indicate *charge*.

Wiring Diagram. The connections are practically the same. regardless of the type of starting motor installed, so that the following description will cover all three of the Overland models mentioned, Fig. 225. The ignition system is entirely independent of the starting and lighting system, although it appears on the diagram. The connections are as follows: Cable 12072, battery negative to motor terminal: cable 12073, battery positive to starting switch: wire 12236, starting switch to fuse block; wire 12066, fuse to positive ammeter terminal; wire 12066, negative ammeter terminal through fuse: wire 12069, to battery cut-out: wire 12068, generator positive terminal to cut-out. The battery negative is grounded at the end of cable 12072, while the cut-out is grounded to the frame through the wire 12906 and the generator is grounded at its negative ter-This is an example of the frame of the car being employed for the negative side of the circuit, as compared with the Gray & Davis in which it is utilized for the positive side. While the ground connections of the lamps and horn are indicated as separate wires, in the case of the lamps the socket itself forms the ground connection. The location of the various fuses and the relation of the various essentials of the system will be clear upon tracing the diagram.

Instructions. While a car never comes into the shop to have its electrical equipment examined until some fault develops, and
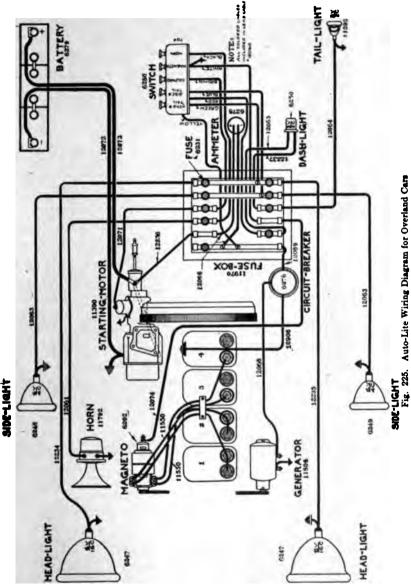
## ELECTRICAL EQUIPMENT

the man who has to locate the trouble seldom has occasion to run the car in ordinary service, still it is important that he should famil-



iarize himself with the instructions issued to the owner, in order that he may know rt a glance whether these instructions have been

carried out or not. It is safe to say that more than half the troubles that arise with this equipment are due to failure to follow instructions in its use. The average motorist ordinarily pays little attention to the workings of the apparatus until it goes wrong and then he is helpless. There is, however, another type—the man who is given to tinkering. He is responsible for not a few of the problems that come into the garage, and familiarity with the manufacturer's instructions will assist in tracing the result of his efforts.

Chain Drive. The silent-chain drive of the generator should be inspected occasionally and any slack taken up by loosening the screw which holds the generator on its bracket, and moving the generator over by means of the adjusting screw. The chain should be just slack enough to have no strain on its links when the engine is not running. Although the initial stretch of the chain is taken out at the factory by running it under load, these chains will continue to stretch slightly in service. After making the adjustment the holding screws should be re-tightened.

Commutator and Brushes. The commutator is the most vulnerable part of a direct-current machine. It should be examined first whenever there is any trouble with the generator, such as insufficient output of charging current, or with the starting motor, such as loss of power, the battery being in good condition. (No mention is made of battery instructions in this connection as the subject is fully dealt with in another volume, and in the summary following this section. The battery is, however, the cause of fully 80 per cent of all electrical-system troubles and neglect is at the root of most of these.)

The commutator is made accessible by the removal of a small plate—in this case, the name plate. If it is blackened and rough, the brushes first should be examined and trued up and the commutator should be smoothed down with fine sandpaper (never use emery cloth as it is metallic and will short-circuit the segments). The mica insulation should be carefully examined; if it is flush with the copper segments this is the cause of the roughened up brushes, and the mica should be undercut. Detailed instructions for smoothing the commutator, truing up the brushes and undercutting the mica insulation are given in connection with the Delco system. Any carbon dust from the brushes should be carefully blown out


this will tend to short-circuit the armature and field windings. e that the brush holders swing easily on the studs and that there just enough spring tension on the brushes to make good contact the commutator. Too much tension will cause unnecessary heatg and wear of the commutator and brushes. Keep the commutator and brush chamber free from dirt and grease. Never replace ushes with any but those supplied by the manufacturer. See at the brush holders are well insulated from their supports, replacing any of the insulating plates, bushings, or washers that may have scome damaged. Should the battery or generator be disconnected not run the engine until they are again connected. Should it be seessary to do so, connect a short piece of bare copper wire from a terminal of the generator to one of the brass screws in the name ate.

Generator Tests. The following tests will be found an aid in cating failure of the generator.


Field. To test the field coils, lift the brushes off the mmutator and insert a piece of fiber or clean dry wood. lose the battery cut-out by pressing the finger on the contacts. he ammeter should then register about one ampere if the coils e all right.

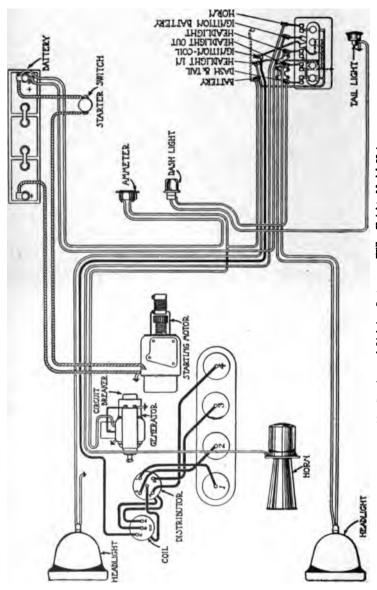Armature. To test the armature, remove the driving chain and ose the cut-out as before. This will motorize the generator and should then run at 650 to 750 r.p.m., drawing 3 to 3½ amperes, its windings are in good condition. This refers to the generator





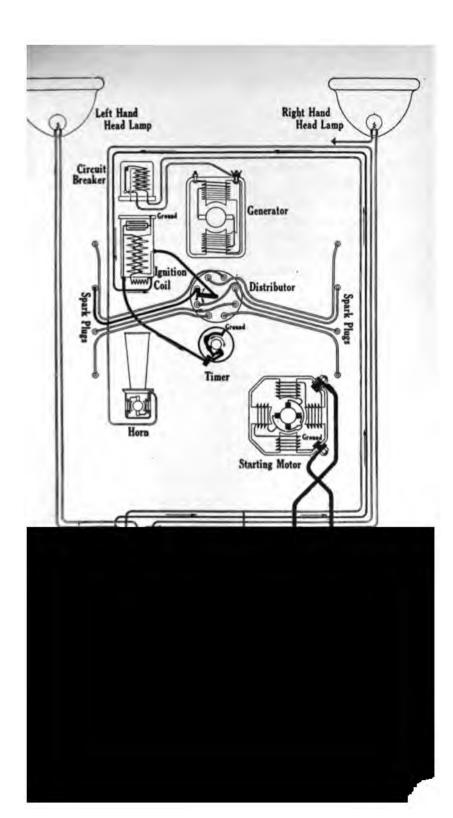Auto-Lite Starting and Lighting System on Willys-Knight, Model 88-4 Courtesy of The Willys-Overland Company, Toledo, Ohio



or the factory direct, as either armature or field winding is something that is beyond even the best equipped of garages.

Battery Cut-Out Tests. Failure of the battery cut-out to operate will most frequently result from pitted or blackened contact points. Clean and true up with fine sandpaper which should be drawn back and forth between them while slight pressure is applied to the upper one, taking care to keep the sandpaper at right angles to the vertical plane of the points, as otherwise they will be put out of true. See that the faces of both points come together over their entire surface when pressed together with the finger.

Operation. Test for operation by sending the current from five dry cells in series through the coil of the cut-out. The points should come together with a snap as soon as the circuit is completed and should hold fast as long as the current is on. This test should not be continued too long, however, as the dry cells will weaken. In case the armature is not attracted, leaving the points in the open position when the battery current is sent through it, inspect the connections from the binding posts to the coil. The wire is small and may have broken from vibration.

Should no circuit be found through the coil with the dry battery, try the test-lamp outfit on the 110-volt circuit, holding one point down on a binding post and just touching the other momentarily with the second point. If the lamp fails to light, there is a break in the coil and the cut-out should be returned to the manufacturer.

## **BIJUR SYSTEM**

6-Volt; Two-Unit; Single- or Double-Wire, According to Make of Car. Also 12-Volt; Single-Unit

Generator. The generator is a special reversible type. Due to the reversible characteristics of the machine it may be connected in either direction and it will assume the proper polarity for charging the storage battery.

Regulation. This is the constant-voltage type, the regulator and battery cut-out being mounted directly on the generator. The principle of this method of regulation is to maintain the voltage of the generator constant, the current output depending on the resistance of the circuit and varying with the state of charge of the battery. This is accomplished by the use of a magnetic vibrator

similar in principle to the ordinary electric bell, or buzzer, though it takes a different form, Fig. 226. H is the magnet winding, A the soft-iron core of the magnet, and G the vibrating armature. To prevent G from coming directly in contact with the pole piece on the upper end of A, a stop pin I is provided. C and F are the contacts, C being held against F by the tension spring E and is pulled away from F by the magnetic pull of coil H in armature G. These contacts are mounted on vibrating reeds (thin strips of spring brass) placed at right angles to each other. Contact C and its reed are attached to the armature G, and stop pins B limit the lateral movement of this contact. F and its reed are also mounted on an arm as shown.

When a current flows through the magnet coil the armature


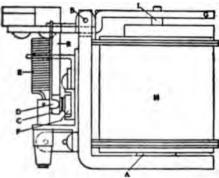



Fig. 226. Bijur Vibrator Voltage Regulator Courtesy of "The Horseless Age"

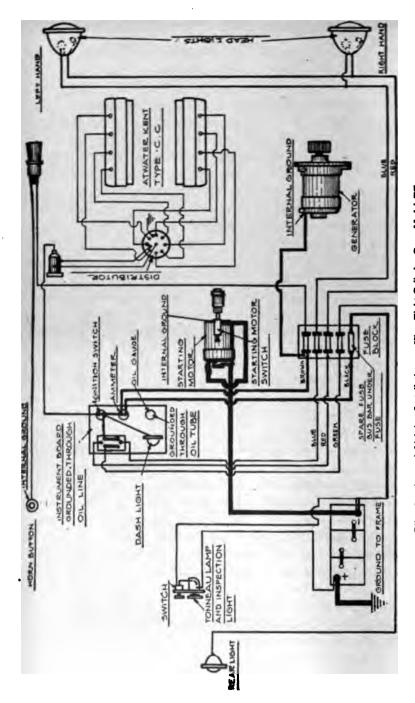the magnet con the armature G is attracted, automatically released by the breaking of the circuit, and again attracted so that it vibrates, the rate of vibration depending upon the amount of current. As the vibrator is included in the field circuit the current in the latter is accordingly pulsating, and as a field circuit, owing to its heavy iron core has consid-





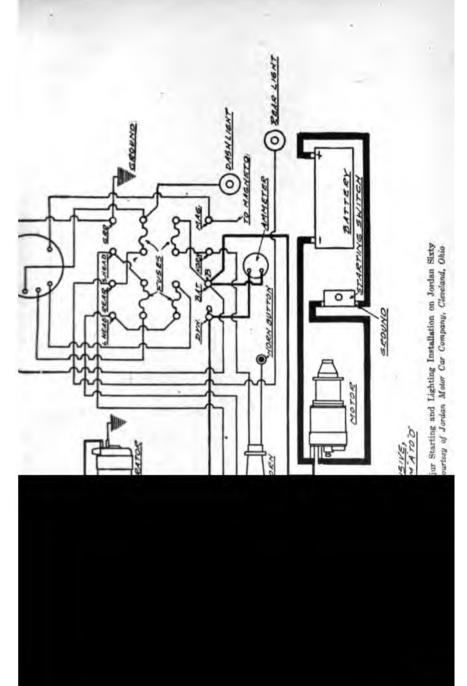Bliur Starting and Lighting Installation on King Eight-Cylinder Cars, Model EE Courtesy of Bijur Motor Lighking Company, Hoboken, New Jersey



Starting Motor. This is of the series-wound multipolar type. The installation of motor and starting switch as mounted on Hupp cars is shown in Fig. 227.

Instruments. A dash ammeter is supplied. With constant voltage control the amount of current delivered to the battery by the generator depends upon the condition of the former. With battery almost discharged, its voltage is lowered and the current reading may then be as high as 15 to 20 amperes. With battery fully charged and no lights on, the reading will decrease to 5 amperes or less, the charging current at all times depending upon the state of charge of the battery.

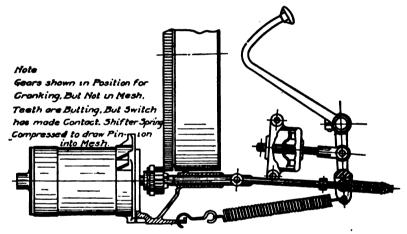


Fig. 227. Bijur Starting Motor as Installed on the Hupp

Wiring Diagrams. Winton. This, as shown in Fig. 228, is a single-wire system. The generator is located alongside the transmission case and is belt-driven, provision for belt adjustment being made by swinging generator to tighten belt. The numbers on the wires indicate the sizes of wire used for connecting the various apparatus. Ground connections are on engine and transmission case. In this installation the starting switch is mounted directly on the starting motor. A spare lamp circuit is provided on which a portable, trouble-hunting lamp may be connected. Fuses are provided on all lamp circuits.

Jeffery. Fig. 229 illustrates the six-volt two-wire system used on the Chesterfield Six Model. With the exception of the out-of-

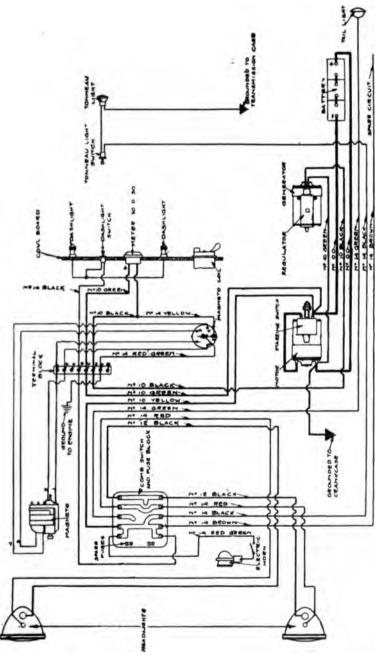


Fig. 228. Bijur System as Installed on the Winton

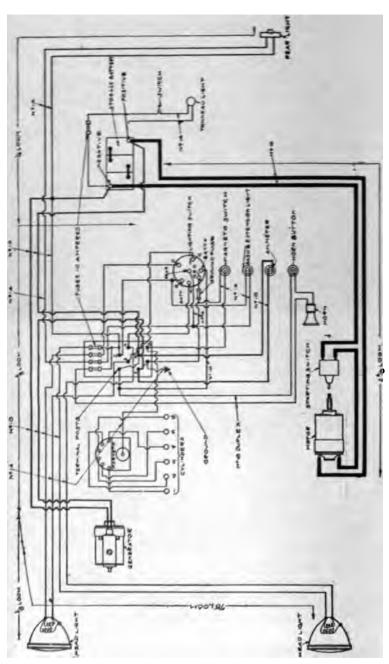



Fig. 229. Bijur Byntem (Two-Wire) Installed on the Jeffery Chesterfield Six

rus lamps in the headlights for city running which are on the ree-wire plan, one side being grounded, all apparatus is connected th two wires. In addition to lamp fuses, the ground connection also fused. The blowing of any of these fuses does not affect e ignition circuits. The generator is mounted on the right side the motor and is driven through a flexible coupling from the ning-gear shaft. At its rear end, the generator is connected rough a jaw coupling to the water pump, this shaft also serving drive the magneto. The starting switch is mounted on a housing vering the motor pinion, the starting motor being mounted on e left side of the engine. A five-way switch provides lamp ntrol.

Hupp. Fig. 230 shows the 6-volt single-wire system. This agram is simplified by the omission of the magneto, current from e battery being supplied to a single coil and distributor system this purpose. The generator is bolted to an extension on the this side forward of the engine and is driven by silent chain from e crankshaft. The generator is of the third-brush regulation type. It field windings are protected by a 12-ampere fuse. There is a ar-way switch for lighting circuits.


Apperson. The 6-volt two-wire system is shown in Fig. 231. ie generator is of the third-brush regulation type. A "charge licator" is fitted instead of an ammeter, having three readings—arge, floating, and discharge. Floating is the neutral position

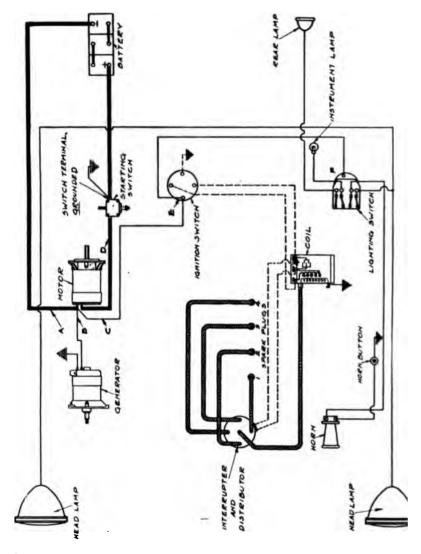field circuit is closed, and the ignition circuit is closed. This is the normal operating position. In the off position, all circuits are opened and the car cannot be run. Shifting the switch to the




idle position closes the ignition circuit so that the engine can be operated, but the dynamotor is disconnected from the batter and its field circuit is opened so that it generates no current

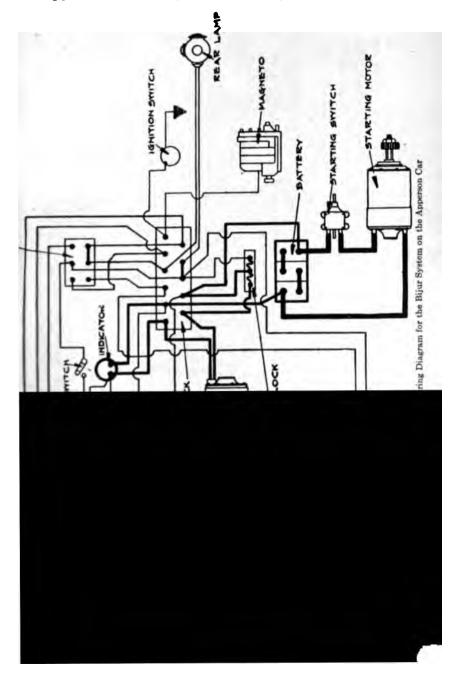
. 232 shows the wiring diagram as used on the earlier models of Scripps-Booth, while Fig. 233 is the diagram of later models



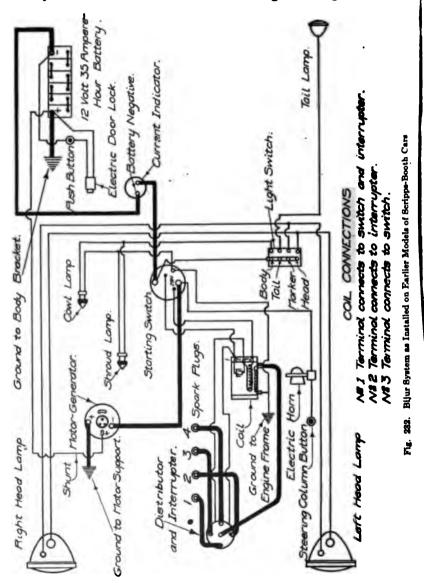erator produces current at 12 volts and charges the storage battery cells in series. Fourteen-volt tungsten lamps are used.



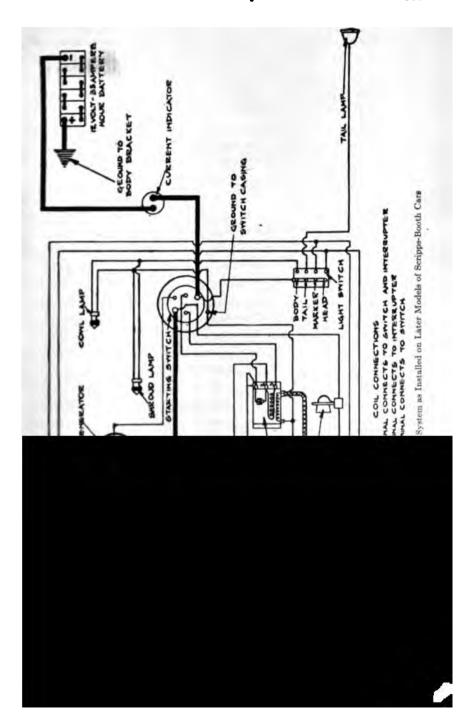Instructions. Winton. No charge reading will be indicated on the ammeter when the engine is running (on high gear or direct




drive) at a car speed of less than 10 miles per hour. Failure to indicate a charge at speeds higher than this is a sign that the generator belt is too loose or that the generator itself is inoperative. To determine this, remove No. 10 black wire, Fig. 228, connected to No. 6 post on the terminal block, which goes into the aluminum box Connect a voltmeter between this wire and the chassis and run the engine at a speed corresponding to a travel of 15 miles per hour on high gear. The voltmeter should indicate 7.3 to 7.4 Instructions regarding brushes, commutator, and tests of armature- and field-winding circuits with the aid of testing lamp as given in connection with the Auto-Lite system apply to determine the nature of the fault in the generator. A special disconnecting plug is incorporated in the regulator box on top of the generator. This plug has two flat parallel faces and should never rest in its receptacle so that these flat faces stand in a vertical position, but should be pushed in and turned in either direction past its central position until it locks. When making tests for generator faults see that this plug is in the proper position to close the generator circuit.


To remove the regulator box from the generator, the disconnecting plug should be pushed in and turned to its central position when the plug may be withdrawn from its socket. After removing the plug, the knurled screw on top of the regulator box should be loosened and the box lifted by grasping it and the plug receptacle at the same time. Do not hammer the receptacle in order to release the box. If the disconnecting plug is round and knurled on the portion extending from the receptacle, the plug may be withdrawn when the V-groove extending horizontally on the plug matches with the slot at the top of the receptacle. The plug should never be left in this position, but should be turned in either direction until it springs forward and locks. Every five hundred miles, this disconnecting plug should be pushed inwardly to unlock it, and turned past its vertical position until it springs forward and locks. In carrying out any repairs or tests involving the disconnection of any of the wires which might cause a short circuit by coming in contact with metal parts of the car, the cable connected to the positive terminal of the battery should be disconnected and its bare end taped. This naturally applies to all grounded electrical systems and not merely to the car under consideration.

Jeffery (Chesterfield Six). Instructions for failure of generator, starting motor, lamp circuits, etc., are the same as those given in connection with other installations, except that in making tests the fact that two-wire circuits are employed must be borne in mind and connections made accordingly. The headlights supplied are special double-filament lamps, one of the filaments being out of focus to provide a non-glaring light for city driving. Where emergency replacements are made with standard single-filament lamps (doublecontact type), the lamp controller should be turned to the in focus bright position when the head lamps are to be used. It is not possible to dim the lights under these conditions. In making a headlamp double-filament bulb replacement, the lamp controller should be turned to the out of focus dim position. The new bulb should then be inserted in its socket. The out-of-focus filament in each headlight should then burn dimly. If they do not, the last bulb inserted in its socket should be removed, reversed, and replaced. When bulbs are correctly inserted, the two out-of-focus filaments will burn dimly when the lamp controller is turned to the out of focus dim position. Instructions for the use of the disconnecting plug are the same as for the Winton.

To determine whether generator is inoperative remove wire leading from the ammeter to No. 5 post of the junction and fuse block, Fig. 229, then connect voltmeter to terminals 2 and 5 and run engine as previously directed. A fuse is in the ground circuit between the magneto tap and the lamp controller and this fuse will blow if an accidental ground is made on either side of the system. The blowing of this fuse when the lamp controller is in the off position, shows that the accidental ground causing it is on the positive side of the system. Should the ground fuse blow when the lamp controller is in the all bright or out of focus bright positions, it shows that the accidental ground is on the negative side of the system. In testing the wiring to locate grounds, the headlight bulbs should be removed and the ground wire leading to connecting post No. 7 of the fuse and terminal block should be disconnected, and the magneto switch should be placed in the running position. With the ground fuse blown, the following lighting conditions obtain. Controller at in focus bright position, lamps will burn normally. At out of focus bright position lamps will not light; at all bright position.

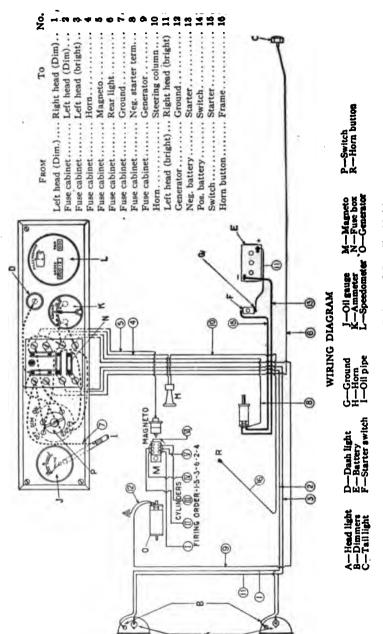

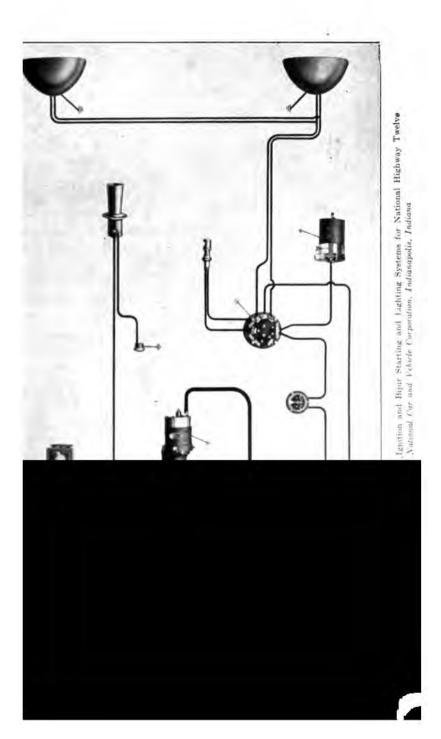- Bijur Starting and Lighting Installation on Jeffery Six, Model 671 Courtesy of Bijur Motor Lighting Company, Hobolem, New Jersey




only the in-focus filaments will light. At the out of focus dim position all the lamps will light.

Hupp. General instructions covering failure of generator, starter, or lamp circuits apply as already given. Many other important factors might be mentioned such as open circuit. loose connections. blown generator fuse, corroded battery terminal, and brushes not seated properly. If the starting motor is damaged so that its removal is necessary, it should be removed by disconnecting one of the battery terminals and the two small wires B and C as shown on the diagram, Fig. 230. Next remove heavy cables A and D from the starting motor. The holding nuts on the motor can then be loosened to permit its removal. In replacing a starting motor, the pinion riding on the square shaft of the motor should be tested to see that it has a free sliding fit on the shaft. Do not use a file but see that all surfaces are perfectly clean and well oiled. The pinion must be guided over the shaft before the motor is pushed into place. Connect the new motor in accordance with the wiring diagram. Do not make storage-battery connections until all other connections have been made and while repairs are being carried out battery terminals should be protected.


In case an inoperative starting motor is removed and a new one is not immediately available for installation, the car may be run with the hand-starting crank by proceeding as follows: Terminals on the end of cable A and the wires B and C must be connected together by binding tightly with bare copper wire and then thoroughly taping so as to form a good electrical joint that is well insulated. Secure the cables and wires to adjacent parts of the car with the aid of cord or insulating tape (not with wire) so that they cannot be chafed or otherwise injured by moving about while the car is running. The heavy cable D must be similarly taped and secured. The lighting system is then independent of the starting system. By making a study of the wiring diagram and carefully noting the different circuits, the starting circuit may be isolated from the lighting circuits on any car having a two-unit system. replacing a blown fuse always examine for grounds, short-circuits. or defective bulbs. Never replace a blown fuse with anything but another of the same capacity. If it is necessary to use the car before the trouble can be located, the grounded circuit can be left open by omitting its fuse. When all lights fail this is due to an open circuit between the battery and the fuse block. Examine the battery connections carefully and also connections of the cable A and wire C when they are connected to the starting motor; also examine the connections E at the ignition switch, F at the lighting switch, and the fuse block. If all of these connections are clean and tight, making good electrical contact, there is a broken wire between these points and the various circuits should be tried with the testing lamp.

Before making the usual tests for an inoperative generator see that the fuse protecting the field windings is intact. If this fuse has not blown and all connections are tight and properly made, remove wire from B which connects the generator to one terminal of the starting motor, and connect an ammeter in this circuit. Run the engine at a good speed, equivalent to 15 miles per hour or more. If the ammeter shows no current, while the commutator is bright, brushes bearing on it properly, and the battery connections are all right, test the armature and field windings with a lamp outfit to locate short-circuited windings. Do not remove the generator unless another is available for immediate installation. it is necessary to run the car with the generator inoperative, the field fuse should be removed as a precaution against damage. take the generator off, remove the circular cover plate from the front end of the chain case and take out the three bolts holding the generator to the rear side of the chain case. The driving chain

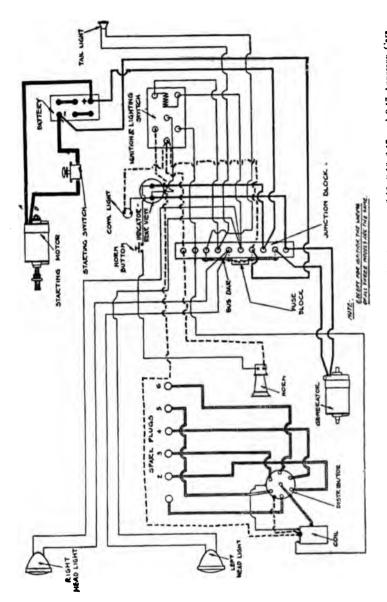

Wiring Dagram Showing Remy Ignition and Bijur Starting and Lighting Systems on 0-16, 8-10, 0-17, and 8-17 Apperson Cara Courtesy of Apperson Brothers Automobile Company, Kokomo, Induna

1

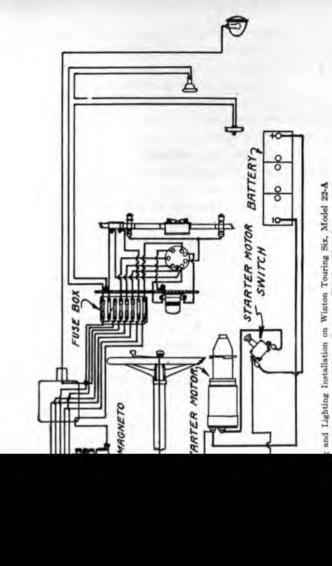

t and Lighting Installation on Winton Touring Six, Model 22-A y of Bijur Motor Lighting Company, Hoboken New Jersey

or other tool. Before replacing a blown fuse examine all connections and wiring to see that they are in good condition. The engine must never be run with the battery disconnected, as this will blow the generator-field fuse. These instructions apply to all generators equipped with field fuses, although the placing of the latter will naturally differ in other systems. Instructions for testing circuits are the same as those for other two-wire systems. There are no grounds except in the ignition system. Tests for inoperative generator or starting motor and instructions for the removal of either of these units are the same as already given.

Scripps-Booth. With the higher voltage battery supplied (12-volt) in the single-unit system employed on this car, the cells are of considerably smaller capacity (35-ampere-hour as compared with 80-ampere-hour on the Apperson and 120-ampere-hour on the Winton), so that if the car has been left standing for long periods with the lamps on, or is only run for short periods during the daytime, thus giving the battery no opportunity to become fully charged. it will not have sufficient capacity to start the engine. As the motorgenerator (dynamotor) automatically reverses its functions in accordance with the speed at which it is being driven by the engine. the latter should not be run with the switch in the on position at speeds corresponding to a travel of less than 10 miles per hour. Under such conditions, as when the car is left standing with the motor idling slowly, or when driving at a very slow pace as in congested traffic, the switch should be placed at the idle position. Should the engine stall when the switch is at the idle position, it should be shifted immediately to the on position. For failure of the current indicator to work see instructions on this point on page 353. The indicator should never show discharge when the car is running above 12 miles per hour.


If necessity requires the operation of the car with the battery disconnected, disconnect the wires from the generator at the machine, as otherwise it is liable to injury. On the earlier Scripps-Booth models, Fig. 232, the engine should not be used as a brake in running down hill except in emergencies, but on later models, Fig. 233, this may be done without injury to the dynamotor by throwing the switch to the off position. By referring to the wiring diagram it will be noted that the shroud-lamp and cowl-lamp bulbs

## ELECTRICAL EQUIPMENT


are of the double-contact type; all others are of the single-contact type. All must be 14-volt lamps, 15 c.p. and 4 c.p. in the headlights and 2 c.p. for the others.

Packard. Fig. 234 is the wiring diagram of the Packard twelvecylinder motor, showing all connections for the ignition, starting, and lighting. Beginning at the left, are the double headlights and their connections, just back of them, the twelve-cylinder distributor and its connections to the twelve spark plugs, in groups of six. This distributor is illustrated in the preceding ignition section. It is practically two six-cylinder distributor units, each of which has its own induction coil, though both naturally must run synchronously, i.e., they are timed together, as the ignition alternates from one group of cylinders to the other. The secondary cables are represented by double lines which are shown part solid and part open, to distinguish To the right of the two coils, in the lower them from other wires. central part of the diagram, is the junction box, incorporating all the lighting-circuit fuses. Further to the right of this, the "switchboard" is a unit mounted at the head of the steering column of the car and which brings to one convenient point within easy reach, all the lighting as well as the ignition switches.

To indicate the heavy cables of the starting circuit, a double line is used with cross lines at short intervals. Two-wire connections are used throughout the entire system, barring the ignition. On the motor the high- and low-tension wiring is readily distinguishable by the difference in size, the low-tension wires having the thinner insu-The low-tension current is carried in a complete two-wire circuit not grounded at any point. The high-tension current is grounded from the spark-plug body, through the motor to the coil bracket. The starting circuit may readily be traced by its heavy connections, and it will be noted that it is the shortest and most direct circuit in the system. Referring to the junction box, the strap shown connecting posts A and B is used in this way in all states the laws of which allow direct control of the tail light from the driver's seat. With this arrangement, the dash and tail lamps are in parallel and both are protected by the tail-lamp circuit fuse. For states requiring an independent tail-lamp circuit, such as Illinois, this strap is connected across posts B and C; with this arrangement, the dome-light fuse protects the tail light, while the

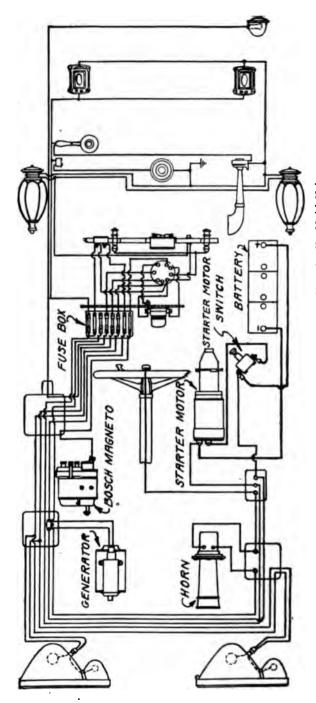

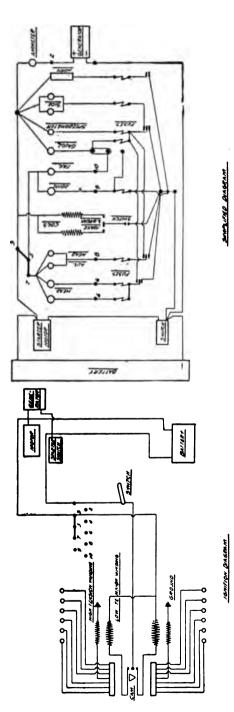Bijur Starting and Lighting Installation on Winton Limousine Six, Model 22-A Courtesy of Hijur Motor Lighting Company, Hoboken, New Jersey



Simplified Bijur Ignition, Starting, and Lighting Diagram for Packard "Twin Six", Models 2-35 and 2-25 Countery of Bijur Motor Lighting Company, Hoboken, New Jersey

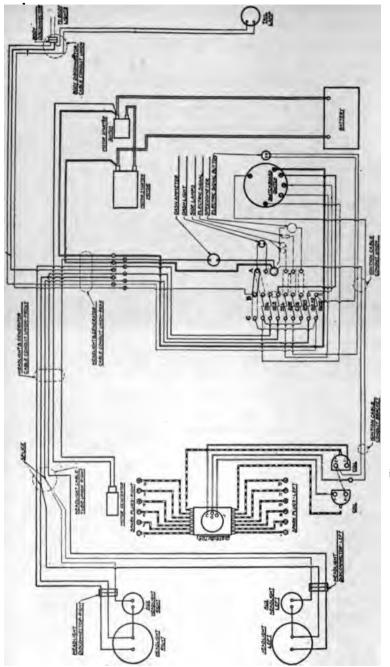


Fig. 284. Wiring Diagram of Bijur System for Packard "Twelves"

tail-light fuse protects the dash light. All wires are run in conduits, the various circuits enclosed in each conduit being indicated at different points on the diagram. High-tension wires from distributors to spark plugs are carried in tubes supported on the cylinder blocks.

#### **BOSCH-RUSHMORE SYSTEM**

#### Twelve-Volt; Two-Unit; Single-Wire

Generator. The bipolar shunt-wound type of generator is made in two sizes, one for driving from pump shaft, and the other for silent-chain or belt drive.

Regulation. Ballast Coil Employed. The regulation is the inherent type, using a bucking-coil winding in conjunction with a so-called "ballast coil" which automatically cuts the bucking coil in or out of the circuit, according to the resistance of the ballast coil. Mention has been made in Elementary Electrical Principles. Part I, that the resistance of certain metals increases greatly with an increase in their temperature. This is particularly the case with iron. and advantage has been taken of this fact in the Bosch-Rushmore generator. The ballast coil consists of a few turns of fine iron wire on a fluted porcelain rod. The bucking coil, which is simply a reversed field winding, has a polarity opposite to that of the winding employed to excite the field magnets. Consequently, when a current passes through it, the effect is to oppose the excitation of the field magnets. The bucking coil is connected as a shunt across the iron ballast coil, Fig. 148. The resistance of the bucking coil is considerably greater than that of the ballast coil when the iron wire is cold or only warm, so that at low engine speeds practically all the current generated passes through the shunt winding of the dynamo. However, the resistance of the wire increases at a constant rate with the current up to 10 amperes, after which it increases very suddenly owing to the heating effect of the current in the iron. Any current in excess of 10 amperes accordingly must pass through the bucking coil, which consequently tends to limit the output of the generator to that amount of current.

Starting Motor. Method of Operation. This is the serieswound bipolar type, as illustrated in section, Fig. 155, which shows the field windings as cut in half. As the illustration is to scale, the large size of the conductors in a series-wound field will be noted,

this being necessary owing to the heavy current required to operate a starting motor. The starter pinion is mounted directly on the armature shaft without any intermediate gearing and the engagement of this pinion with the flywheel gear is automatic, as will be made clear by referring to Fig. 155, and to Fig. 166, showing the mounting of the Bosch starter on an automobile motor.

Refer back for a moment to the description of magnetic fields under Electrical Principles, Part I. See also the description of the action of a solenoid. It will be noted that every magnet has a magnetic circuit and that the lines of force comprising it are most numerous in close proximity to the poles of the magnet. words, the magnetic attraction is most intense at those points. magnetic poles of the field of the Bosch starter are the metal projections each of which is held in place by two machine screws, top and bottom. as will be seen in the sectional view. It will also be plain that the armature of the starting motor is not directly in the magnetic field of these poles, and that it is held in this off-center position by the spring pressing against its shaft as seen at the left. The moment the switch is closed, however, and the field magnets are excited. the whole motor acts as a solenoid and forcibly pulls its armature into a central position against the spring, at the same time as it This gives ideal conditions for meshing the begins to revolve. starter pinion with the flywheel gear, as it is pulled against the latter and at the same time revolved, so that the moment its teeth correspond with spaces in the flywheel gear, it slips into engagement and begins to turn the engine over. As soon as the current is cut off by opening the switch, the spring returns the armature to its normal inoperative position and disengages the gears.

Starting Switch. There are two contacts on the starting switch, the first sending only a small amount of current through the starting motor, this being just sufficient to pull the armature into center and engage the gears, when a further movement of the switch sends the full current from the battery through the starting motor. This progressive movement of the switch and the two circuits between the battery and starting motor are shown in Figs. 235 and 236. It will be noted that the first movement of the switch throws the field of the starter in series with the battery, while the further movement of the switch places the field and armature in series with

the battery. Fig. 237 shows the actual wiring diagram of the starting-motor circuit. In actual operation, the movement of the


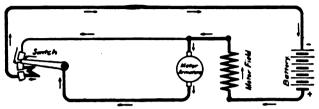


Fig. 235. Wiring Diagram for First Part of Downward Movement of Bosch Switch Pedal

switch is practically instantaneous. No damage will result in case the switch is held down after the engine starts, as the moment the latter begins to fire, the load on the starting motor is greatly reduced and the current consumption decreases to a point where the field coils no longer have sufficient pull to overcome the spring on the armature. The pinion on the shaft of the latter is automatically disengaged from the flywheel gear and the motor will only idle slowly, owing to the armature being off center.

Instruments and Protective Devices. A standard double-reading ammeter is supplied. The normal charging rate is approximately 20 amperes with the car running 20 to 25 miles an hour or over.

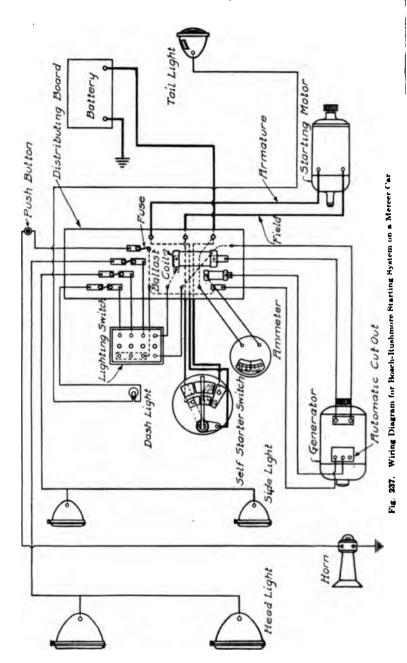
In addition to the usual battery cut-out which is an essential feature of most electric lighting and starting systems and will be found on most cars so equipped, whether it is specifically mentioned




putting it in the circuit the charging rate is reduced to 5 amperes. Where a great amount of day running is done, it is recommended that the ballast coil be left in circuit. All circuits, except starting motor, but including field coil of generator, are fused.

Wiring Diagram. The various circuits of the single-wire system, as employed in the Mercer installation, are shown in Fig. 237. The automatic cut-out for the battery circuit is mounted on the generator. Ground connections are not indicated in every instance, as in the case of the generator and the starter they are made within the apparatus itself, and this is also the case with the lamps, which are known as the single-contact type. The latter are employed in all single-wire systems. In this case, they must be 12-volt bulbs as six cells of battery are employed. In making lamp replacements, only bulbs of the proper type, i.e., single or double contact, depending on whether the system is one- or two-wire, and of the proper voltage must be used. This, of course, applies to all electric systems, as, where a 6-volt bulb is placed on a 12-volt system, it will be burned out immediately. A 12-volt bulb on a 6-volt circuit will burn very dimly, so that when only one headlight burns brightly the voltage of the dim burning bulb should be ascertained before looking for trouble elsewhere. If the manufacturer's label has disappeared from the bulb, it can be tested with dry cells, starting with four in series which should make a 6-volt bulb burn brightly, and increasing to eight in series for a 12-volt bulb.

Instructions. Battery Charging. With all lamps on, the lighting equipment consumes about 12 amperes; the side and tail lamps together take about 3 amperes, so that when the ammeter reading shows a consumption in excess of these figures for the conditions given, the usual tests should be made for short circuits or grounds. The latter will be the case also when the ammeter shows any discharge reading with all lamps off. Any discharge under such conditions is leakage. However small it may be, it should be investigated at once, as it will run the battery down. The trouble may consist of a short circuit in one of the lighting circuits or it may be due to current flowing back through the generator caused by the failure of the cut-out to work properly. In case the lamps burn dimly when the generator is at rest, it indicates that the charging rate is not sufficient to keep the battery up. This may be caused

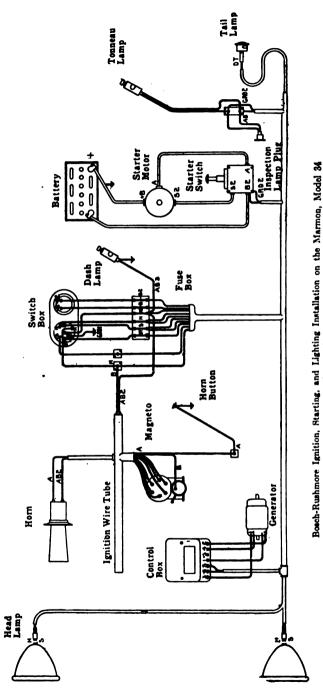

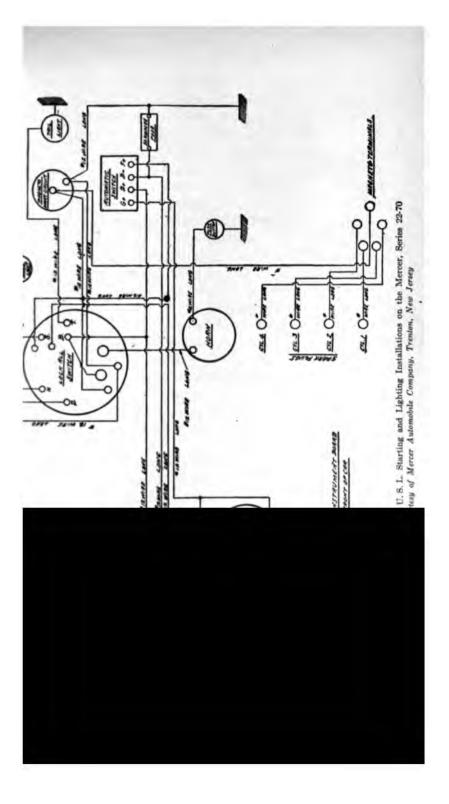Courtesy of Nordyke & Marmon Company, Indianapolis, Indiana



by a great deal of night running with the ballast coil in the charging circuit, as the charging rate is then only about 5 amperes. In the majority of instances, however, it will be found, probably, that the battery itself is responsible. For instructions on battery maintenance, see end of this article.

The battery furnished on the Mercer has a capacity of 120 ampere-hours. The starting motor takes approximately 200 amperes for its operation which, with the engine in good condition, should not consume more than 10 seconds for each start. To replenish the current consumed by starting twelve times in a day, or say a total of two minutes' operation of the starting motor at the 200-ampere rate, the engine would have to run only about half an hour at the average charging rate of 15 amperes. With the current consumed by the lamps, based upon their use for 5 hours per night, plus the natural deterioration losses of the battery, drop in efficiency through switches, contacts, and wiring, approximately two hours of daylight running would be required to keep the battery fully charged. Night running can be disregarded where battery charging is concerned, as the total consumption of the lamps is practically the equivalent of the average charging rate. An undue brilliancy of the lamps would indicate a battery wire off or loose and should be investigated.

Fuses. When ammeter shows no reading of charging current with the engine running, the most likely place to look for the trouble is the fuse protecting the generator field circuit. (This applies to all generators so equipped.) The field fuse of the Bosch-Rushmore generator is located on the distributing board, and it may be tested by short-circuiting the ends of the fuse cartridge with a pair of pliers, a screw driver, or other piece of metal. In case the ammeter then registers a charging current, the fuse has been blown out and should be replaced with another of the same type and capacity. circuits, except the starting motor, are fused, a similar test can be carried out in case of the failure of any of them. The blowing of a fuse is usually due to a short circuit, and before replacing it, the reading on the ammeter should be noted when the fuse terminals are short-circuited with the pliers, the generator being idle. short circuit will be indicated by the needle of the ammeter moving sharply to the limit of its travel on the scale. The use of the testing amp for finding short circuits is given in connection with the instructions under Auto-Lite, Delco, Gray & Davis, and other systems.

Gear Meshing. Fallure of the starting motor to operate will be iue to an exhausted battery in the majority of instances, but on ars that have seen considerable service, it may be caused by a ettling or distortion of the frame resulting in binding of the gear teeth too tightly. This may be corrected by readjusting the mounting of the starting motor in its supporting cradle so that the gears mesh quite loosely. It should always be possible to push the gears into mesh by hand without any effort. Unusually slow operation of the starting switch may also cause failure of the starting motor to pperate properly. The first contact of the switch places a small resistance in the circuit and too long a delay may overheat this resistance to such an extent as to burn it out. Over-rapid operation of the switch may also cause failure to start as the gears are not This will be indicated by their clashing and by dlowed to mesh. the spinning of the starting motor. The switch should be given a comparatively slow but steady movement from first to second contact.





TIPICAL BOXES ROSEMORE STANTING MOTOR



TYPICAL BOSCH MAGNETO INSTALLATION
Courtery of American Beach Magneto Corporation, Springfeld, Massachusette

## ELECTRICAL EQUIPMENT FOR GASOLINE CARS

PART V

### ELECTRIC STARTING AND LIGHTING SYSTEMS—(Continued)

#### PRACTICAL ANALYSIS OF TYPES—(Continued)

**DELCO SYSTEM** 

Six-Volt; Single-Unit; Single-Wire

Dynamotor. The dynamotor is usually referred to as a motorinator, though it is actually a generator-motor, i.e., a dynamoiter which has been shortened to dynamotor. This term has been inputed by the Society of Automobile Engineers to designate the mbination unit in question. A motor-generator as employed for insforming alternating current to direct current consists of two parate units: a motor driven by alternating current and a dynamonerating direct current, mounted on the same bed, and with their mature shafts directly coupled.



smaller of the two sliding gears is incorporated an over-running clutch which releases the starting motor from the engine in case the latter should be speeded up without disengaging the starting gears, thus preventing damage to the starting motor by running it at an excessive speed.

Control. The necessary switches for putting the generator in circuit to charge the battery, and to cut it out of this circuit and put the starting motor in circuit with the battery to turn the engine over, are built into the machine and take the form of lifting brushes. Their operation is as follows:

To start, the ignition button on the switch panel on the dash is first pulled out. This connects the storage battery with the ignition

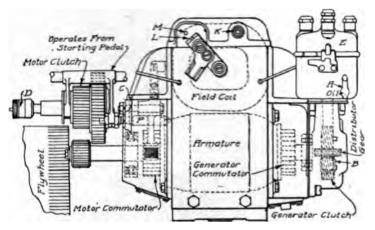


Fig. 238. Diagram of Delco Dynamotor for Single-Unit System

circuit and with the armature of the dynamotor through a resistance which permits only a current of small value to pass. This current motorizes the generator and causes its armature to rotate slowly, giving it just enough speed to facilitate the meshing of the starting generator. The starting pedal is then depressed and during the first part of its travel it serves to engage the gears, Fig. 238. Then it withdraws the pin P. Fig. 239, allowing the motor brush switch to make contact with the motor commutator. At the same time it causes the generator switch to open, thus cutting out the generator diagonal the cranking operation. As soon as the motor brush makes contact, the fall current from the battery passes through the series-

# ELECTRICAL EQUIPMENT FOR GASOLINE CARS

#### PART V

### ELECTRIC STARTING AND LIGHTING SYSTEMS—(Continued)

#### PRACTICAL ANALYSIS OF TYPES—(Continued)

**DELCO SYSTEM** 

Six-Volt; Single-Unit; Single-Wire

Dynamotor. The dynamotor is usually referred to as a motorgenerator, though it is actually a generator-motor, i.e., a dynamomotor which has been shortened to dynamotor. This term has been
adopted by the Society of Automobile Engineers to designate the
combination unit in question. A motor-generator as employed for
transforming alternating current to direct current consists of two
peparate units: a motor driven by alternating current and a dynamo
memorating direct current, mounted on the same bed, and with their
mature shafts directly coupled.

The Delco single-unit machine consists of two separate field sindings and two independent armature windings, the latter being innected to separate commutators at either end of the shaft. In imbination with this is an ignition timer and distributor mounted the generator end and driven from the armature shaft through siral gears. The generator is driven from the pump shaft of the ingine through an over-running clutch which permits the armature trun free when the unit is operating as a starting motor. At the starter end, the armature shaft carries a small pinion meshing with the larger unit of a pair of sliding gears, the smaller of which is adapted to slide into engagement with the gear ring of the flywheel. This arrangement is shown clearly in Fig. 238; it provides a double gear reduction between the starting motor and the engine. In the

smaller of the two sliding gears is incorporated an over-running clutch which releases the starting motor from the engine in case the latter should be speeded up without disengaging the starting gears, thus preventing damage to the starting motor by running it at an excessive speed.

Control. The necessary switches for putting the generator in circuit to charge the battery, and to cut it out of this circuit and put the starting motor in circuit with the battery to turn the engine over, are built into the machine and take the form of lifting brushes. Their operation is as follows:

To start, the ignition button on the switch panel on the dash is first pulled out. This connects the storage battery with the ignition


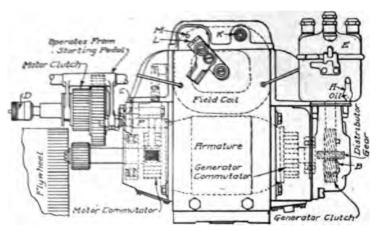


Fig. 238. Diagram of Delco Dynamotor for Single-Unit System

circuit and with the armature of the dynamotor through a resistance which permits only a current of small value to pass. This current motorizes the generator and causes its armature to rotate slowly, giving it just enough speed to facilitate the meshing of the starting gears. The starting pedal is then depressed and during the first part of its travel it serves to engage the gears, Fig. 238. Then it withdraws the pin P, Fig. 239, allowing the motor brush switch to make contact with the motor commutator. At the same time it causes the generator switch to open, thus cutting out the generator during the cranking operation. As soon as the motor brush makes contact, the full current from the battery passes through the series-

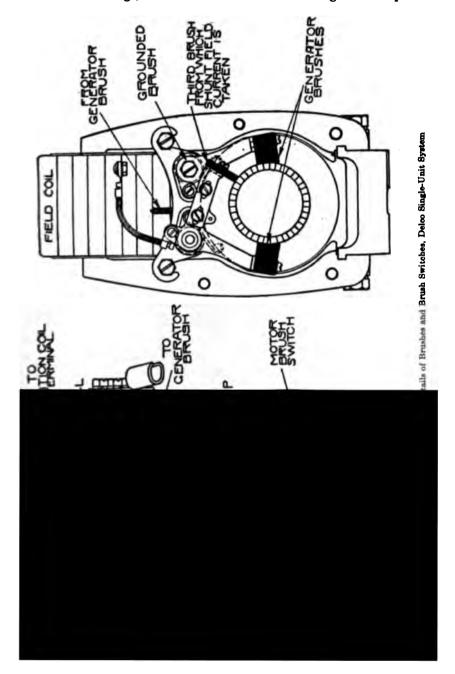field winding of the motor element and through the corresponding armature windings, and sets the armature rotating at full speed.





THE TALL THE PROPERTY SALES OF THE PROPERTY OF

Fig. 240. Section Showing Delco Mercury-Bath Voltage Regulator

Angelinting. Comment-Voltage Inani I ina. It the four types promeni the first employs a resistance THEREBY IN APPROPRIES. WITH the speed. The regulative massists of a solenoid the rise of which has a spool of restance wire women on its lower eni. Fig. 141. This care or plunger ( floats in a bath of mercury, and, in armediance with the depth to which is sinks in the mercury, more or less if the resistance wire is short-cirruined by the mercury. The solenoid winding A is connected in shunt airciss the generator terminals so the current flowing through it and the magnetic effect exerted by it are always proportional to the voltage at the generator terminals. The resistance wire on the plunger of the solenoid is in series with the shuntfield winding of the generator. there were no other forces than the buoyancy of the mercury and that of gravity acting upon the plunger it would remain at approximately the same height, but as the plunger is iron it is acted upon by the solenoid winding, the effect being to withdraw it from the mercury as the current through the winding of the solenoid

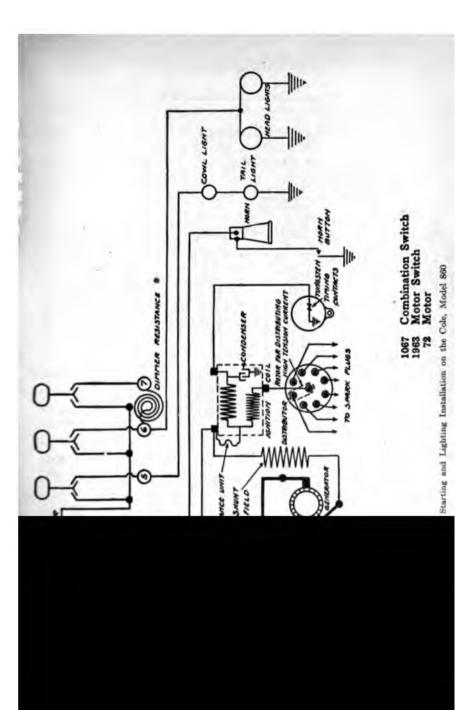increases, thus putting more and more of the turns of resistance wire on the spool in circuit. Hence, the greater the current flowing through the solenoid the greater will be the resistance in circuit with



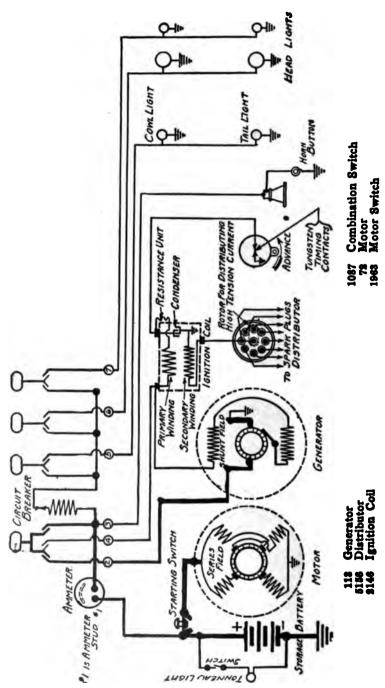


Delco Starting and Lighting Installation on the Cole, Model 880

he shunt-field winding of the generator. To overcome the effect of emperature variation on its operation which would cause the charging ate to be higher than intended at high temperatures, and vice versa, the olenoid is wound and connected in series with a resistance wire of pecial material having a negative temperature coefficient (i.e., whose lectrical resistance decreases with an increase in temperature), so hat the total resistance of the solenoid circuit remains the same egardless of temperature changes. With a few exceptions, such as he Olds 1915 Model 55, this method of voltage regulation is not mployed on cars subsequent to 1914.

Bucking-Coil Type. This is the type of regulation usually eferred to as inherent in that it is accomplished by the windings of he generator itself. The latter is compound wound but the series ield has a reversed polarity, so that its effect is to oppose that of he shunt winding.

Mechanically Varied Resistance. In this type the same priniple as that employed in the first type described is used, i.e., that if weakening the generator field by increasing the amount of resistance in circuit with it in accordance with the speed, except that it is aried by mechanical means instead of electrical. The regulator esistance is in the form of a rheostat, the arm of which is controlled by a centrifugal governor driven from the shaft of the ignition disributor. As the weighted element of the governor expands under the influence of the increasing speed, it moves the arm of the rheostat

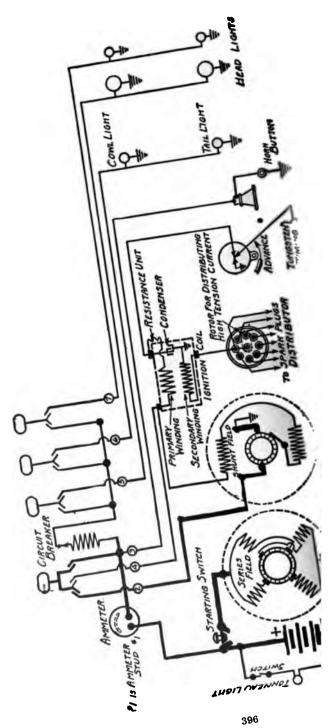

the shunt-field winding of the generator. To overcome the effect of temperature variation on its operation which would cause the charging rate to be higher than intended at high temperatures, and vice versa, the solenoid is wound and connected in series with a resistance wire of special material having a negative temperature coefficient (i.e., whose electrical resistance decreases with an increase in temperature), so that the total resistance of the solenoid circuit remains the same regardless of temperature changes. With a few exceptions, such as the Olds 1915 Model 55, this method of voltage regulation is not employed on cars subsequent to 1914.

Bucking-Coil Type. This is the type of regulation usually referred to as inherent in that it is accomplished by the windings of the generator itself. The latter is compound wound but the series field has a reversed polarity, so that its effect is to oppose that of the shunt winding.

Mechanically Varied Resistance. In this type the same principle as that employed in the first type described is used, i.e., that of weakening the generator field by increasing the amount of resistance in circuit with it in accordance with the speed, except that it is varied by mechanical means instead of electrical. The regulator resistance is in the form of a rheostat, the arm of which is controlled by a centrifugal governor driven from the shaft of the ignition distributor. As the weighted element of the governor expands under the influence of the increasing speed, it moves the arm of the rheostat over the contacts each of which represents an added resistance to the circuit.

Both the bucking-coil type and the mechanically varied type of regulation are employed in Delco systems installed on 1915 and subsequent cars, different models of the same make and the same year having different systems, so that instructions for their maintenance depend upon the system employed.

Third-Brush Method. As the voltage generated varies directly with the speed, it is evident that to maintain a nearly constant voltage with a variable speed, it becomes necessary to decrease the magnetic field as the speed increases. Since the magnetic field of the generator is produced by the current in the shunt-field winding, a decrease in this current as the speed increases will regulate the output. Bearing in mind that a current always produces a mag-

netic field, whether the latter is desired or not, the theory of this method of regulation will be clear from the following reference to Fig. 241. The full voltage of the generator is obtained from the brushes C and D. When the magnetic field from the pole pieces N and S is not disturbed by any other influence, each coil is generating uniformly as it passes under the pole pieces; the voltage from one commutator bar to the next is practically uniform all around the commutator. Therefore, the voltage from brush C to brush E is about 5 volts, when the total voltage between the main brushes C and D is  $6\frac{1}{2}$  volts and current at 5 volts' pressure is supplied to the


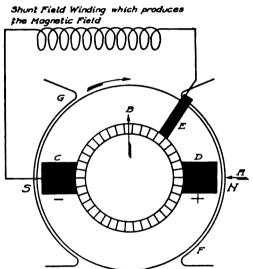



Fig. 241. Delco Third-Brush Regulator

shunt-field winding. This voltage is sufficient to cause approximately 12 amperes to flow through that winding.

As the speed increases, the voltage does likewise, charging the battery. This charging current flows through the armature winding causing a magnetic effect in the direction of the arrow B and the latter acts upon the main magnetic field, which is in the direction of A, with the

result that the latter is twisted or distorted out of its original position, in much the same manner as two streams of water meeting are deflected from their original directions. This deflection causes the magnetic field to be strong at the pole tips G and F, and weak at the opposite tips, with the result that the coils generate a very low voltage while passing from brush C to brush E (the coils at this time are under the pole tips having a weak field) and produce the greater part of their voltage while passing from brush E to brush E. The amount of this variation depends upon the speed at which the generator is driven, thus decreasing the current supplied to the shunt field as the speed increases.

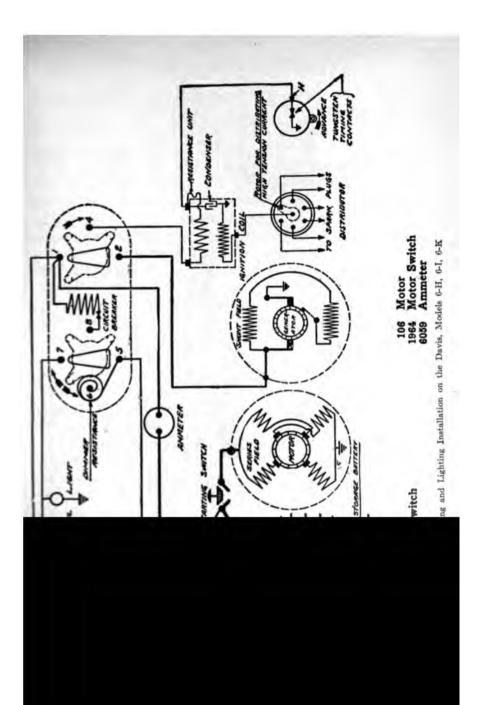

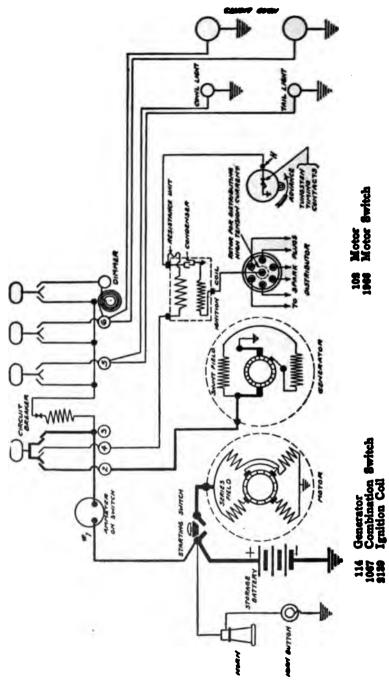

Deloo Starting and Lighting Installation on the Davis, Model 6-J

Protective Devices. Battery Cut-Out. In connection with Delco systems using the voltage regulator of the mercury type already described, a battery cut-out or a cut-out relay, as it is sometimes termed, is employed. Fig. 242 shows this cut-out together with a diagram of its windings. It consists essentially of a compound-wound electromagnet and a set of contacts designed to be closed by the movement of the pivoted armature of the magnet, and to be opened by a spring when the magnet is not excited. The compound winding consists of a voltage coil of a great many turns

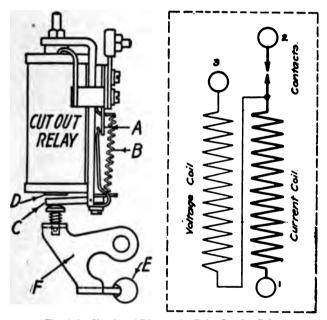


Fig. 242. Sketch and Diagram for Delco Cut-Out Relay

of fine wire, as shown at the left of the wiring diagram, and a current coil of a comparatively few turns of heavier wire. As soon as the engine begins to drive the generator the voltage of the latter "builds up" and when it reaches a value between  $6\frac{1}{2}$  and  $7\frac{3}{4}$  volts, the current passes through the voltage winding of the electromagnet and produces sufficient magnetism to overcome the tension of the spring B, attracting the armature C to the core D which closes the contacts at A. These contacts close the circuit between the generator and the storage battery and the whole output of the generator then flows

through the current coil, greatly increasing the magnetism in the core in the same direction thus strengthening the pull on the armature C and holding the contacts tightly closed. When the generator slows down and the voltage drops below that of the battery, current flows from the latter to the generator through the current coil in the reverse direction. But, as the voltage coil is directly in circuit with the generator, the flow of current through it continues in the same direction, so that the magnetizing effect of the battery current through the current coil opposes that produced by the voltage coil and the latter is not sufficient to hold the armature against the spring. This causes the contacts to open and prevents any further flow from the battery through the generator. The relay is designed


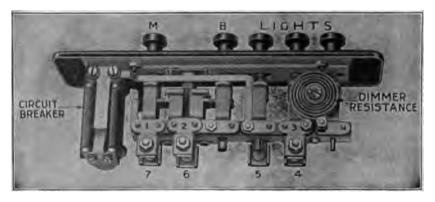



Fig. 243. Delco Combination Switch
Courtesy of Dayton Electrical Engineering Laboratorics Company, Dayton, Ohio

to cut out the battery before the discharge current reaches a value of 1 ampere. As mentioned previously, but few cars subsequent to 1914 are fitted with systems using the mercury voltage regulator and only these systems are equipped with a battery cut-out.

Circuit Breaker. Delco systems fitted to cars subsequent to 1914 are protected by a circuit breaker. This takes the place of the fuse block and fuses employed in most other systems. It is mounted on the combination switch controlling the ignition, generator, and lights, as shown by Fig. 243. The button *M* controls the magneto ignition circuit, and the button *B* the dry-battery circuit for the same purpose. In addition both these buttons control the circuit between the battery and the generator for the purpose of

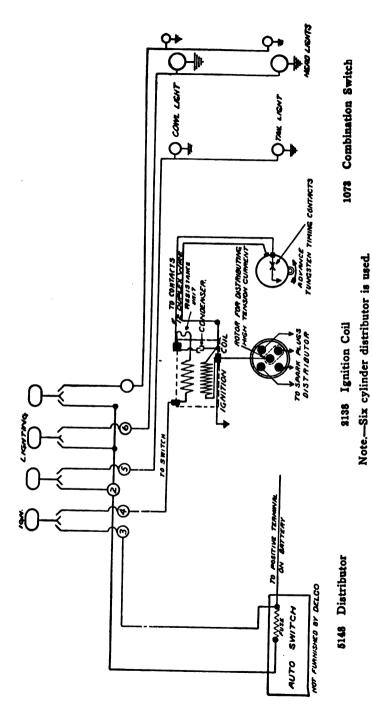

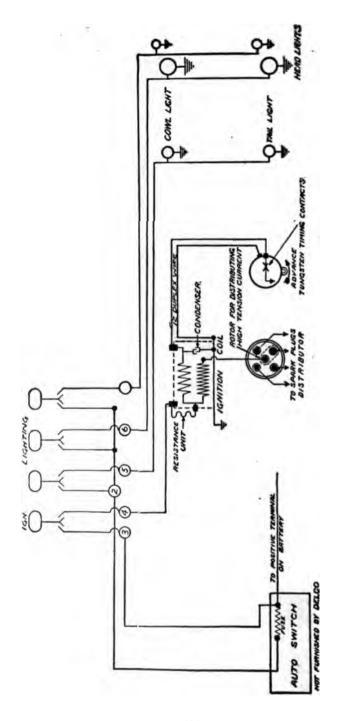
Delco Starting and Lighting Installation on the Elgin, Model 6-E-16



1084 Combination Switch. Deloo Starting and Lighting Installation on the Elkhart, 1917 Model 8118 Coll 6141 Distributor

otorizing the latter to start. When the circuit is closed by either itton M or button B, current flows from the battery to the genator, when the engine is not running and when it is running at eeds below 300 r.p.m., but the amount of current flowing at the west engine speeds possible is so small as to be negligible. With e engine stopped, pulling out the button M sends sufficient current rough the generator armature to run it slowly as a motor so that is gears may be meshed for starting. The amount of current thus nployed is limited by a resistance unit in series with the shunteld of the generator.

In principle the circuit breaker is the same as an ordinary electic bell or buzzer, but its winding and the spring controlling its mature are such that it comes into action only when a heavy irrent passes through it. It is included in every circuit of the ectrical system, including the ignition, with the exception of the arting-motor circuit, so that all the current used for every purpose cept starting passes through it. But as long as the lamps, ignion, and horn are consuming the normal amount of current, it is it affected. In case any of the wires of these circuits becomes ounded, however, a heavy current passes through the circuit eaker, thus producing a strong magnetic pull which attracts the mature and breaks the circuit. This cuts off the flow of current and e spring again closes the contacts, causing the circuit breaker to pass intermittent current by vibrating its armature. A current of 25

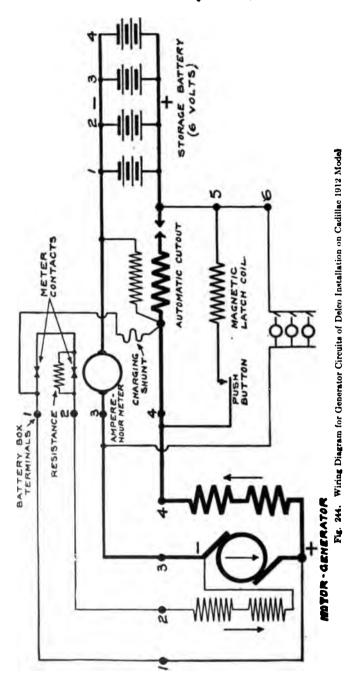

gressive steps represented by each succeeding year; also because there are a great many of these cars still in use. Twelve cells of battery were employed though the dynamo generated current at 7 to 8 volts (nominally a 6-volt system), and as shown by the diagram which illustrates the connections of the generator circuit, the battery was divided into four groups of three cells each in seriesmultiple for charging. An ampere-hour meter showed the state of charge of the battery and also indicated how much current was consumed by the various circuits, including the starting motor. Regulation was by means of extra resistance inserted in the field circuit of the generator and an automatic battery cut-out was employed. The diagram shown in Fig. 244 is applicable to the connections of all the Delco 6—24-volt systems in use, when the machine



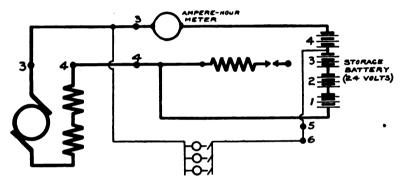


Fig. 245. Wiring Diagram of Starting Motor Circuit for All Delco 6-24-Volt Systems

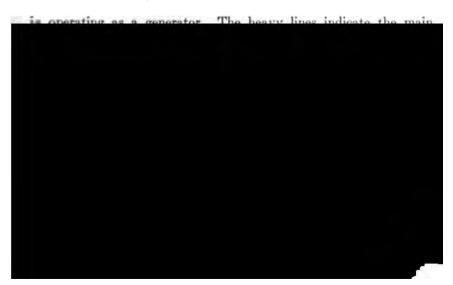

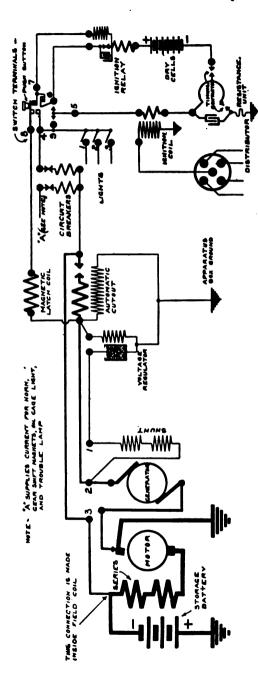


difference being the substitution of the motor brush switch for the external switch controlling the starting motor. The fuses were also replaced by two circuit breakers. one for the main lighting circuits and ignition, and the other for the auxiliary lamps, horn, and the gear-changing solenoids, the model of that year being equipped with an electric magnetic gear shift in the transmission.

Wiring Diagram for Deloo System on Cadillac 1914 Models

In the 1915 wiring diagram, Fig. 247, the method of regulating the generator has been changed to the mechanically varied resistance already described. One circuit breaker protects all fuses and a rotary form of combination switch controls all the circuits.

Buick. Two diferent types are employed on the 1915 models, the only distinction, however, being in the method of

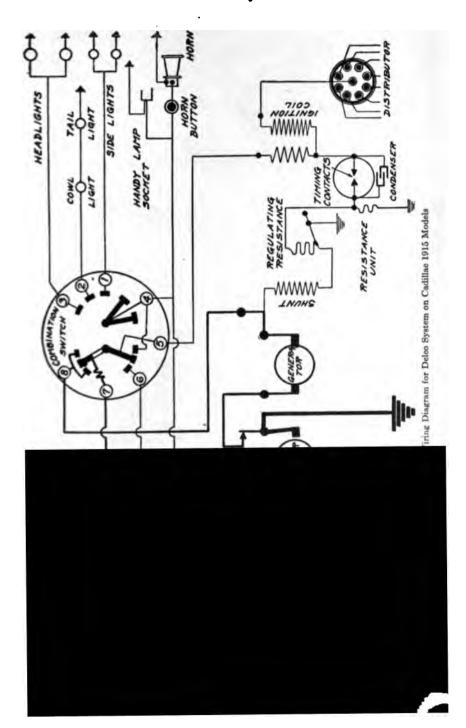


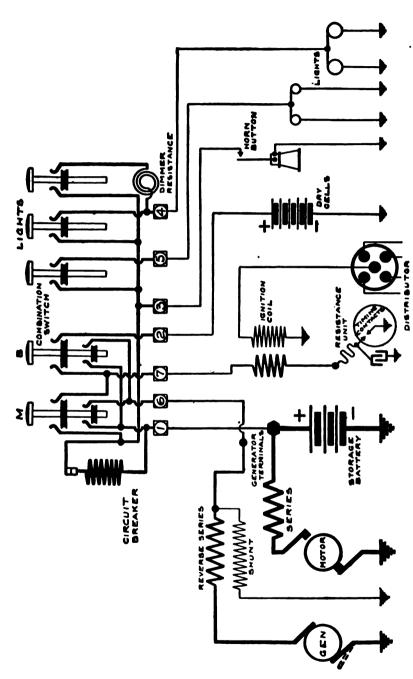


Fig. 248. Wiring Diagram for Delco Installation on the Buick Models C24 and C25

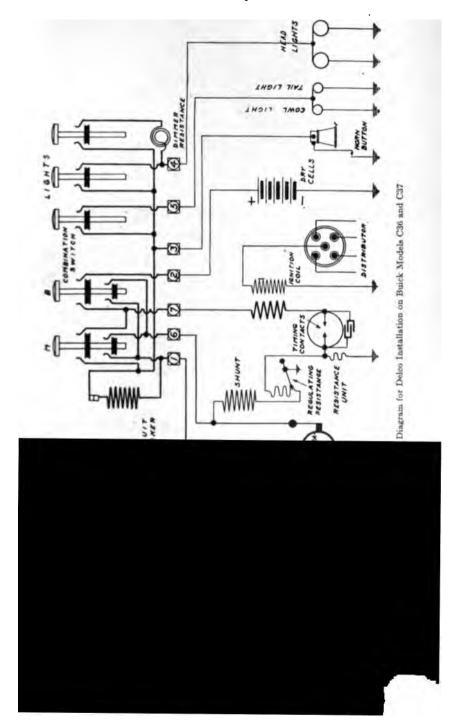



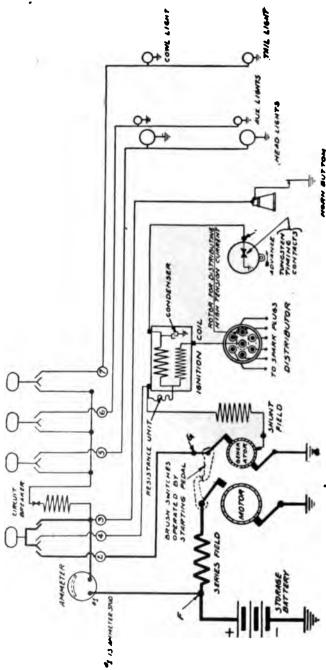


Fig. 250. Wiring Diagram for Delco Installations on Buick 1916 Models

412

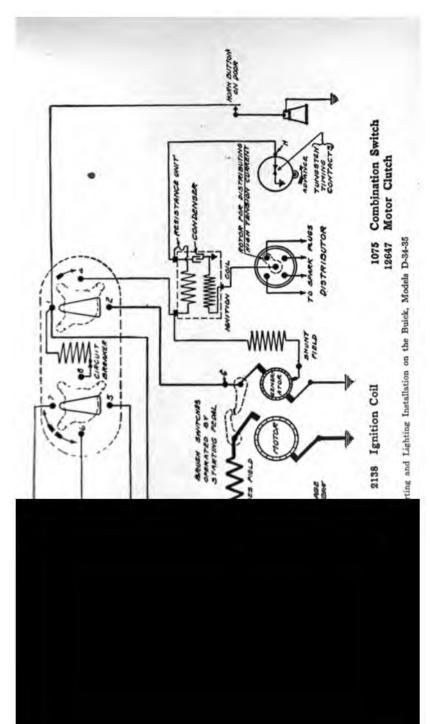

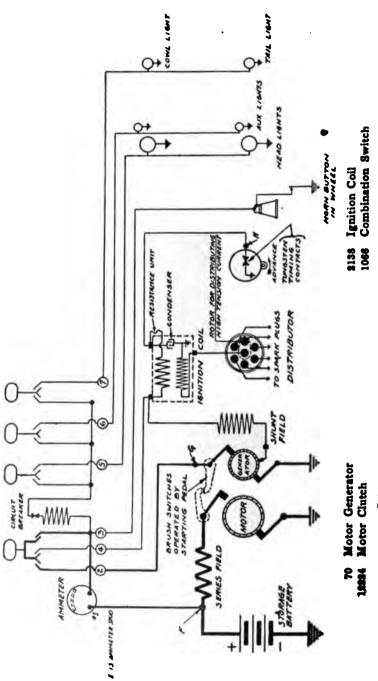

Delco Starting and Lighting Installation on the Buick, Modela D-44-45-46-47

generator regulation. That of Models C24 and C25 is by means of the reversed series-field winding or bucking coil, while that of Models C36 and C37 utilizes the mechanically varied resistance or rheostat operated by a centrifugal governor, as shown in Fig. 249. The buttons M and B, in each instance, control the ignition circuit, depending upon whether the storage or the dry battery is called upon for the ignition current as well as for the current to motorize the generator preliminary to starting. The remaining three buttons of the combination switch control the lights and dimming resistance and it will be noted that the circuit-breaker forms a part of every one of the circuits except that of the starting motor.

On the 1916 Buick models, the generator is regulated by the third-brush method; the brush switches are operated by the starting pedal; only the lighting circuits are protected by the circuit-breaker, and an ammeter is inserted in the circuit with the latter, Fig. 250. No mention is made of the details of any of the ignition circuits in these diagrams as that is taken up in the section on Ignition. Apart from the fact that the Oakland Model 50 has a 4-pole motor winding instead of the bipolar type shown in all the previous diagrams, the wiring diagrams of the Oakland models for 1916 are the same as those shown for the Buick. On the two 1915 models of the Cole, the distinction between the wiring diagrams is the same as that mentioned for the two classes of Buick models of the same year, i.e., one having the reversed series field, and the other the variable resistance controlled by the governor—the combination switch,

circuit beneficer and other connections of the diagrams being essen

same switch which closes the ignition circuit puts the generator in circuit, as explained in connection with the wiring diagram. If the generator armature could not revolve, its resistance would be very low, so that a heavy discharge would take place, but as it is permitted

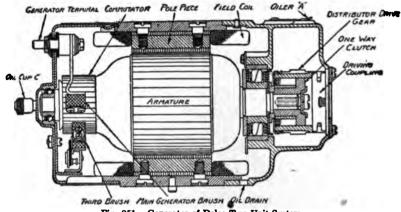


Fig. 251. Generator of Delco Two-Unit System Courtesy of Dayton Engineering Laboratories Company, Dayton, Okio

to become motorized, its armature builds up a strong counter e.m.f., as explained under Electric-Motor Principles, Part I, thus greatly increasing the resistance and greatly decreasing the amount of current that will pass through it.



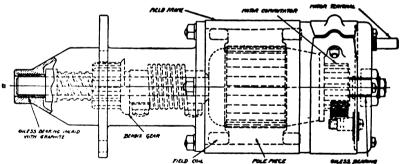


Fig. 252. Diagram of Starting Motor for Delco Two-Unit System

Regulation. The regulation is of the third-brush type, which has already been explained in detail in connection with the single-unit Delco system.

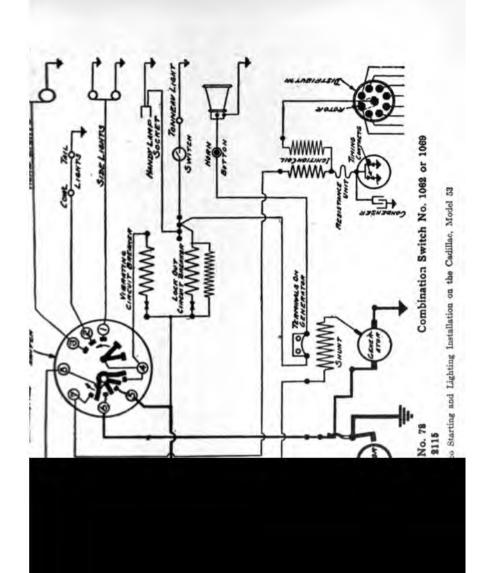Starting Motor. Fig. 252 shows a longitudinal view of the starting motor fitted with the Bendix drive, while an end view of the motor,



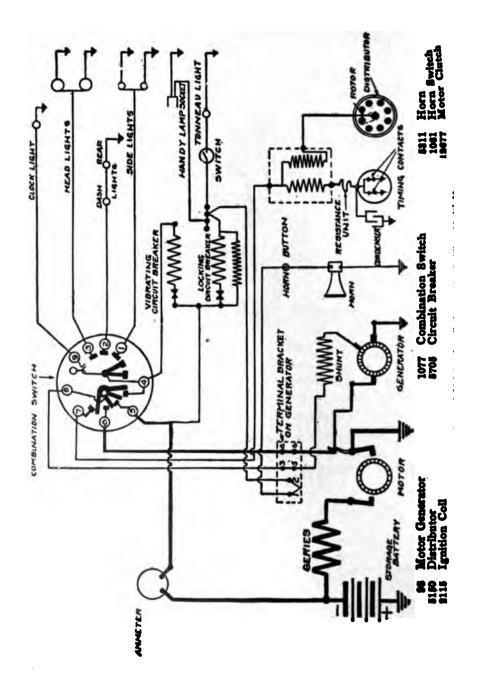

illustrating the commutator and brushes, is shown in Fig. 253. This motor is of the multipolar type, and its method of control differs from

the single-unit type in not employing the brush switch.

Starting Switch. pedal-operated plunger type of switch is employed, for which the advantage is claimed that its contacts are self-cleaning. The method of effecting this will be apparent from the part-sectional view of the switch, Fig. 254. The switch is in barrel form. with the springs incorporated in the plunger, while the stationary and movable contacts are given a contour that causes them to scrape against each other when coming into contact, thus keeping these surfaces bright.



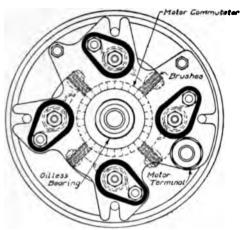


Fig. 253. End View of Delco Starting Motor, Showing Commutator and Brushes

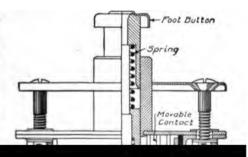

## ELECTRICAL EQUIPMENT

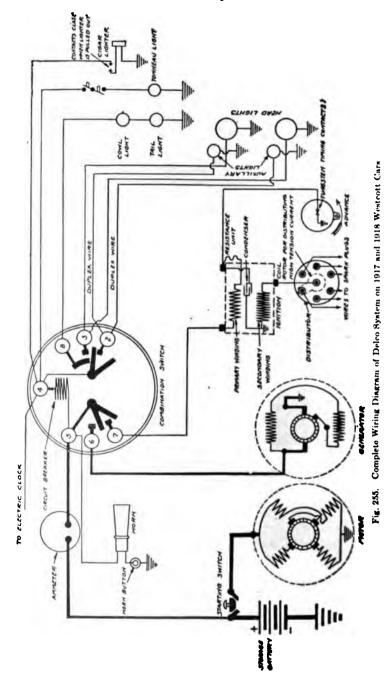

controlling them differs. Likewise that all of these, with the exception of the ignition, are protected by the circuit-breaker. The lighting circuits appear more complicated simply because there is an extra light (tonneau light) and two additional accessories, i.e., a connection for an electric cigar lighter and one for an electric clock.

The chief difference is in the generator and the starting-motor circuits. An unusual feature in this essential is a two-part switch member which controls the ignition and the generator circuits. By this method, opening the ignition switch opens the circuit between the storage battery and the generator, so that a battery cut-out is dispensed with. There is, even under the most favorable conditions, a perceptible interval between the closing of the ignition switch and

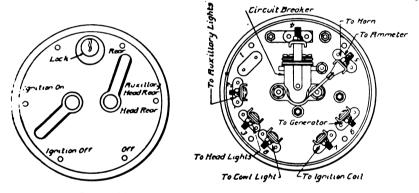


Fig. 256. Front and Reverse Face of Combination Switch for Delco Two-Unit System




The face of the starting switch and the details of the connections on its reverse are shown in Fig. 256.
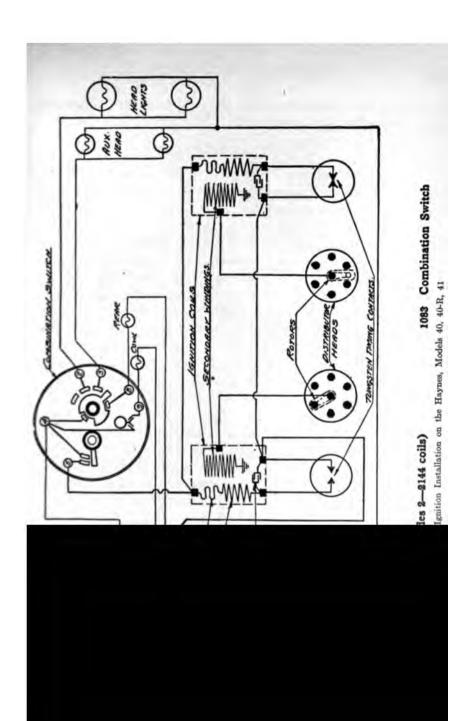
## **Delco Instructions**


١

General Instructions. If the starter, lights, and horn all fail, the trouble is in the storage battery or in its connections, one of the connections being loose or corroded, or one of the battery jars being broken. When the lights, ignition, and horn all work normally but the starter fails to operate, the trouble is in the motor-generator, or dynamotor, and may be caused by the motor brush switch not dropping on the commutator, or by dirt or grease on the commutator. Owing to the heavy current required by the motor in starting, if the lights are on at the time, they will become dim when the starting circuit is closed but remain so only momentarily. In case they go out or become very dim when the starting-motor circuit is closed, it indicates that the battery is practically depleted. When the motor fires properly on the M button of the combination switch, but not on the B button. the wiring between the dry cells or the connection from the dry cells to the combination switch must be at fault. When the ignition works all right on button B, but not on M, the trouble must be in the leads running from the storage battery to the generator. or in the lead running from the small terminal on the generator to the combination switch, or in the battery connections, either of the cells themselves or the ground connections. If the supply of current from both the dry cells and the storage battery is ample, yet both ignition systems fail, trouble should be sought first at the timer contacts, then the coil, resistance unit, and the condenser. examination of the timer contacts will show whether they are clean. square, and in good working condition; if badly burned and pitted. true them up square with a strip of fine emery cloth or a very fine flat file. The coil, resistance unit, and condenser may be tried out with the test-lamp outfit. If the lamp lights when contact is made through the terminals of the coil or the resistance unit, it indicates that nothing is wrong with them, but if it lights on the condenser it shows that the insulation of the latter has broken down, as there should be no circuit through the condenser. The only remedy is to replace it. All of the units mentioned work in the same capacity for each system of ignition.



424


If, for purposes of making tests, it becomes necessary to remove of the electrical apparatus from the car, or to make any adjust its, the storage battery should first be disconnected. This can done most conveniently by removing the ground connection an iding the bare terminal with electrician's tape so that it cannot ne in contact with anything that would cause a short-circuite car should not be run with the storage battery disconnecte

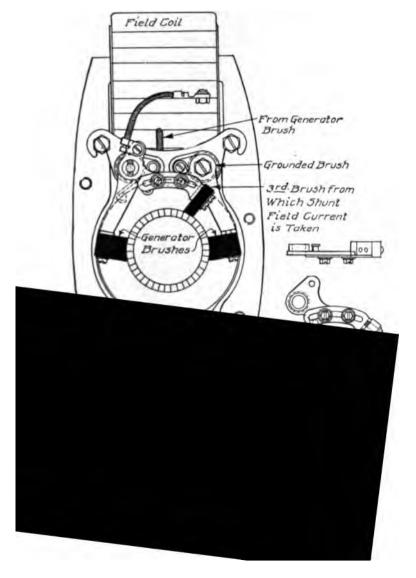


driven a great deal during the day and very little at night. As a result, considerable more current is generated than can be used to advantage. An indication of this will be found in the frequent necessity for adding water to the cells of the battery, or the fact that the battery is constantly gassing. In a case that recently came to the writer's attention, the owner of the car complained that the battery was no good because it was always boiling. It boiled so continually and so violently that it eventually had to be replaced. complaint, in the average case, is that the battery is undercharged rather than overcharged. Unless trouble is experienced because of the battery gassing too much or needing water too frequently, the charging rate should not be altered. When necessary, the alteration may be made as follows: It will be noted in Fig. 257 that the third brush is carried on a brush arm made in two pieces and that the part to which the brush is fastened has a slot through which pass two screws, attaching it to the other part. By loosening these screws, one part may be slid on the other, thus increasing or decreasing the length of the arm. When the arm is shortened, the charging rate is decreased: and when the arm is lengthened the charging rate is increased. should be taken to sand-in the brush whenever it has been shifted in order to insure good contact with the commutator. (See Instructions for Seating Generator and Motor Brushes.) The screws on the brush arm must be firmly tightened after adjusting to prevent slipping.

The charging rate of this type of Delco generator is higher at low-car speeds than on some machines of an earlier type, so that the maximum should be kept somewhat below the value that would be used for earlier machines. In most cases 14 to 16 amperes will be ample, and in no case should it exceed 20 amperes. Readings should be taken at the ammeter on the cowl switch, which indicates the amount of current going to the battery but does not include the ignition current.

The foregoing instructions for altering the charging rate apply only to machines having the third brush mounted on an adjustable arm, as different methods of moving the brush are provided on other types. The principle of adjustment, however, is always the same, i.e., moving the third brush closer to the nearest main brush increases the output and moving it away from this brush, decreases it. The third brush must never be allowed to come in contact with the main

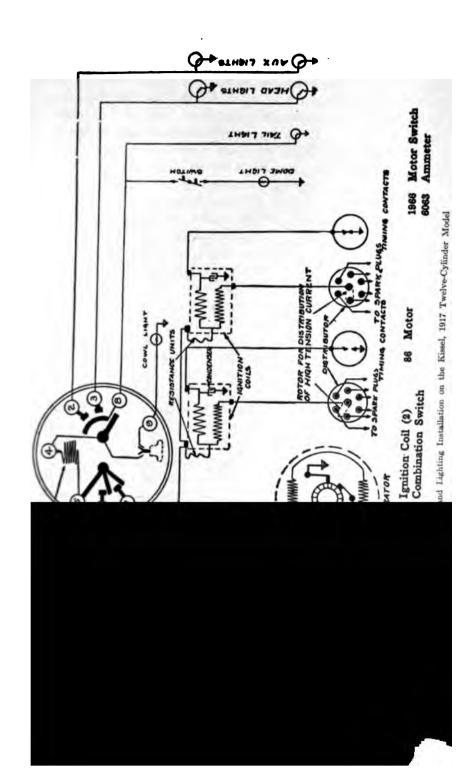

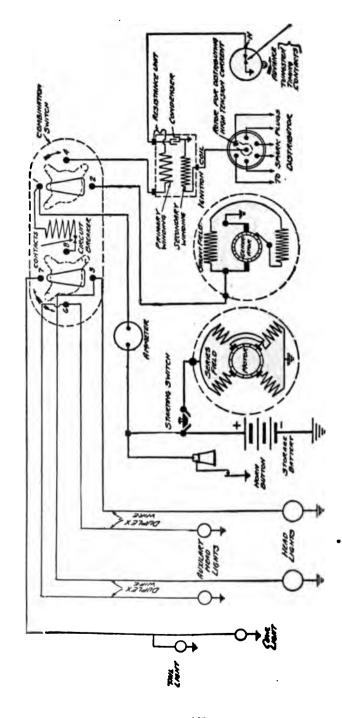

Delco Starting and Lighting Installation on the Liberty, 1917 Model

brush. In the case of the Delco generator under consideration, the charging rate should reach a maximum at a speed of 15 to 20 miles per hour and then drop off as the speed increases beyond this point.

Tests of Wiring. Locating Grounds. By referring to any of the Delco diagrams of the one-wire type, it will be noted that certain parts of the circuits are normally grounded, i.e., they are connected to the common return represented by the chassis of the car. For example, the negative battery terminal, one terminal of each lamp, one motor, one generator brush, one timer contact, one terminal of the horn push button, and one terminal of the condenser in the coil are grounded. Before testing the wiring for grounds, it will accordingly be necessary to remove these normal, or intentional, grounds. This is carried out, in the order in which they are mentioned, by disconnecting the negative battery lead and removing all the lamps, placing a piece of cardboard between each generator and each motor brush, including the third brush of the former and the commutator against which it ordinarily bears, disconnecting the leads from the horn button and from the distributor, and raising the base of the ignition coil so that it is insulated from the top cover of the generator motor. The system will then be in the condition shown in Fig. 258.

One of the test points is then placed on the frame of the car and the other point on the negative terminal A of the battery. If the lamp lights, it will indicate a ground somewhere on the switch or in the motor windings (all of the switch buttons being pushed in). Then, with one test point still grounded on the frame of the car, test

with the other point the different terminals of the combination


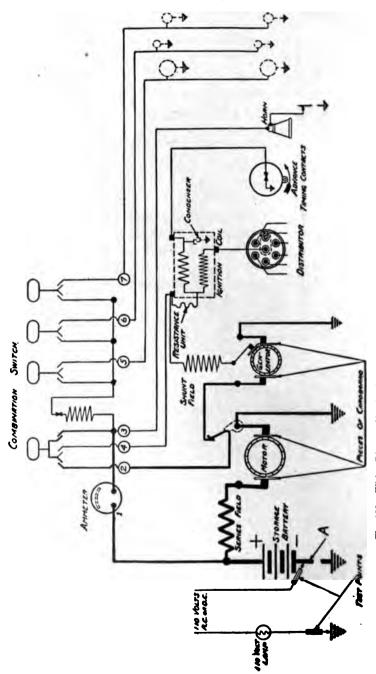



Fig. 258. Wiring Diagram Showing Method of Using Lamp-Testing Set for Locating Grounds Courtesy of Dayton Engineering Laboratories Company, Dayton, Ohio

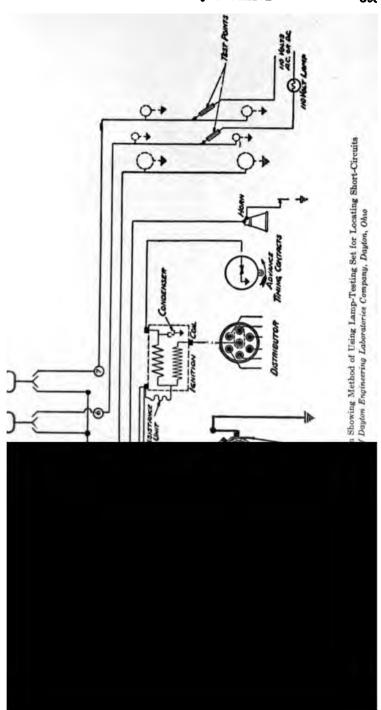



Locating Breaks in Wires. Where the failure of the apparatus in a particular circuit makes it apparent that a wire, or lead, may be broken, it may be tested by placing one of the points on each end of the wire in question. The lighting of the lamp will indicate that there is a complete circuit through the wire, while its failure to light is evidence of a break in the wire. If at all difficult to locate the break the easiest method of repairing it is to replace the wire with a new lead of the same size and type of insulation. The method of carrying out this last test is illustrated in Fig. 260 and it is naturally applicable to any of the wires, not only of this type of installation but of any other lighting and starting system. In making this test, care must be taken not to apply the points at places on the terminals where a ground connection will result, as this will complete the circuit through the lamp without the current passing through the wire supposedly This method of locating grounds, short-circuits, or open circuits will be found much better than the use of a buzzer, bell. or magneto, and it is recommended wherever a 110-volt current is available. However, where it is not available, a lamp, bell, buzzer. or the portable voltmeter may be used in connection with the storage battery on the car, after detaching its usual connections to the system.

Testing Cut-Out. If the battery is not charging properly, the generator being in good condition, or it is discharging too much current through the cut-out, the latter should be tested and adjusted to remedy the trouble. The cut-out is designed to close when the voltage across the terminals of the voltage coil is 6½ to 7½ volts. To check this a voltmeter should be connected across the terminals, noting the reading at the point that the contacts close. It is designed to break the circuit when the discharge current is less than I ampere, preferably as close to the zero mark as possible to reduce the arc on breaking the contacts. This can be checked by placing an ammeter in the circuit in series with the current coil of the cut-out, noting the value of the current at the moment that the contacts separate. When properly adjusted the air gap should be ½ inch.

To adjust the cut-out, the influence of both the air gap and of the spring tension must be taken into consideration. The air gap has little or no effect upon the point of cut-out, this being governed almost entirely by the spring tension, whereas the point of cutting

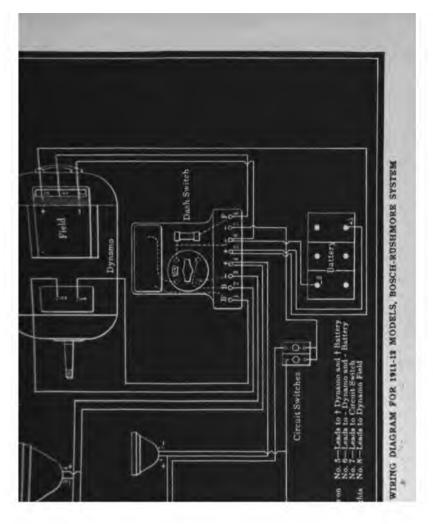

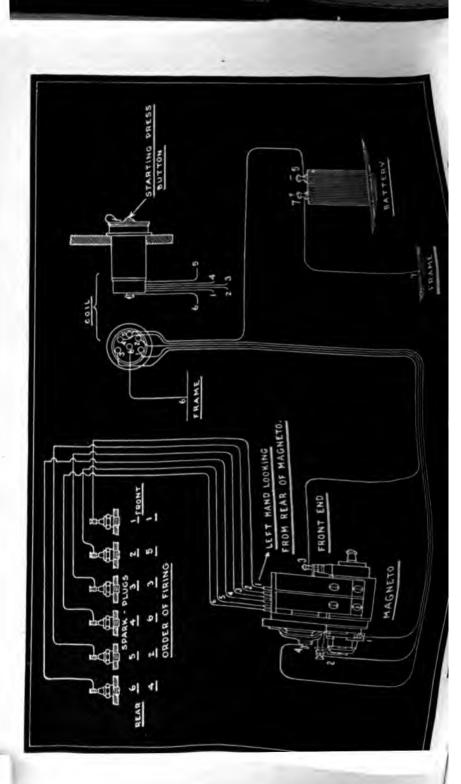

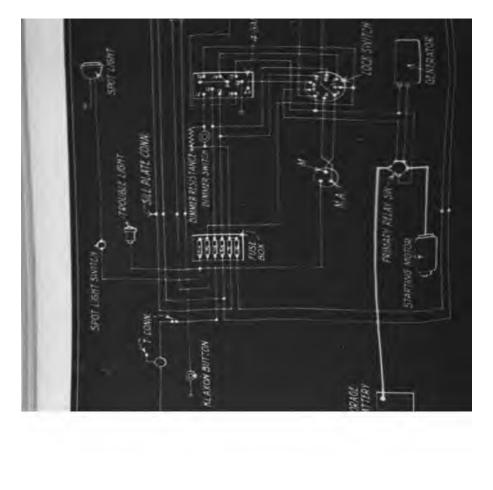


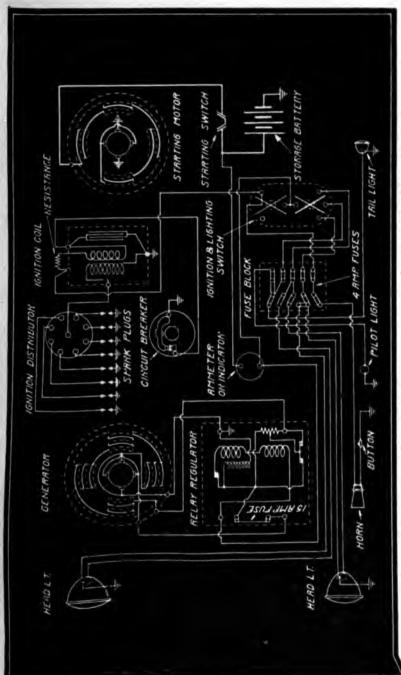


PLATE 101-MADISON WIRING DIAGRAM FOR 1916-17-18 MODELS, 4- 8-CYLINDER, REMY SYSTEM

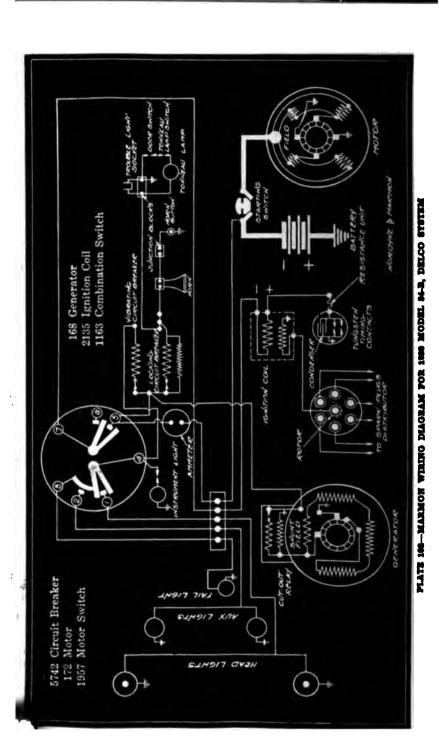


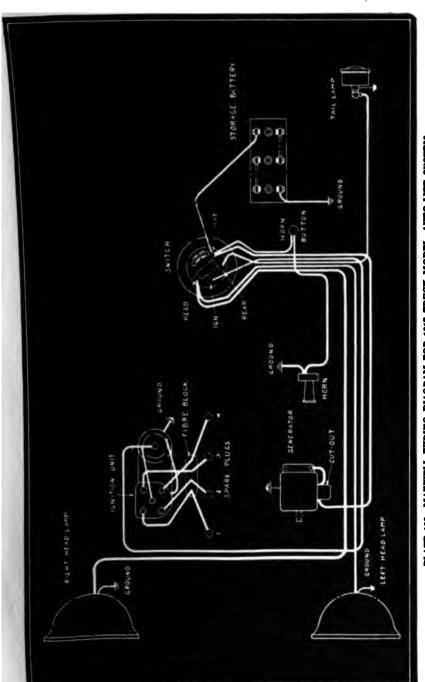


PLATE 105-MAXWELL WIRING DIAGRAM FOR 1917 TRUCK MODEL, AUTO-LITE SYSTEM

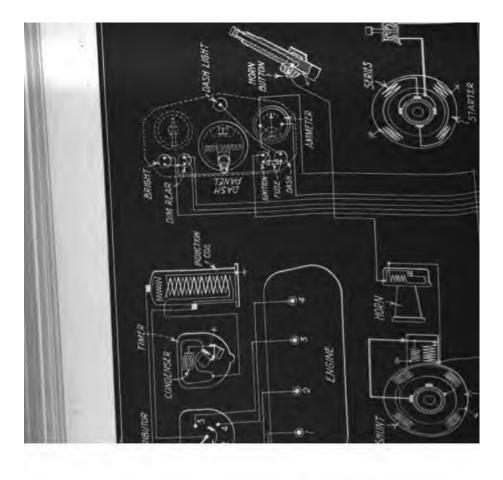




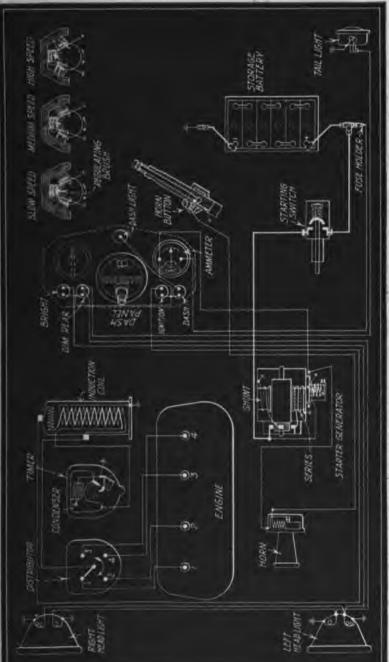



PLATE 104-MAXWELL WIRING DIAGRAM OF 1999 SINGLE-UNIT THIRD-BRUSH, SIMMS-HUPF STARTING AND LIGHTING, ATWATER-KENT IGNITION SYSTEMS

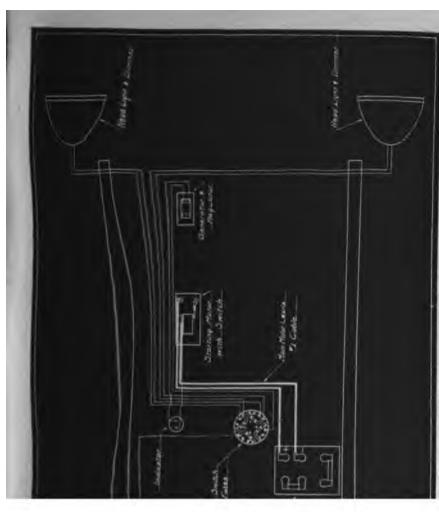


story mention thinks on see that

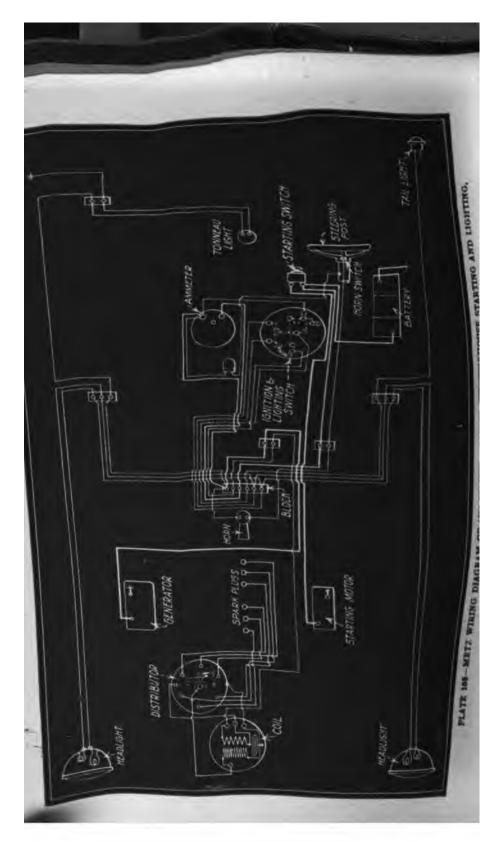

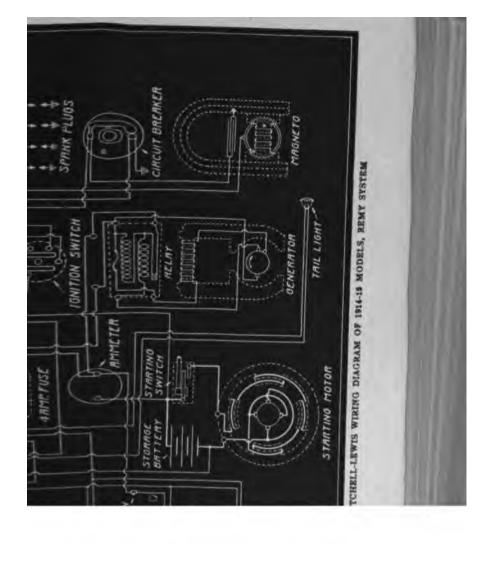

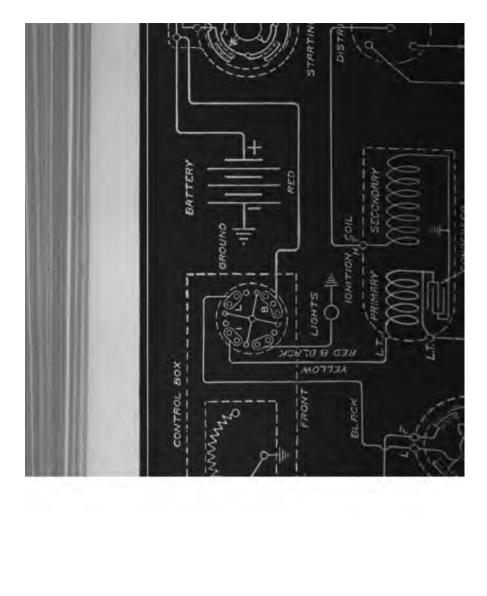

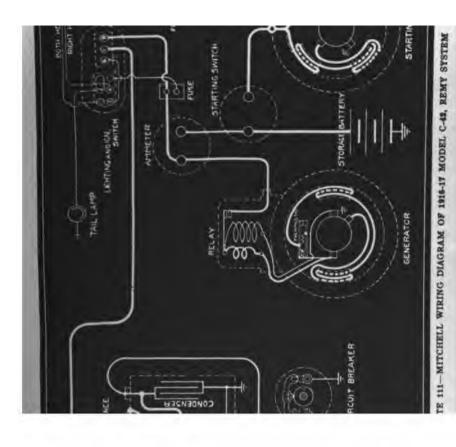


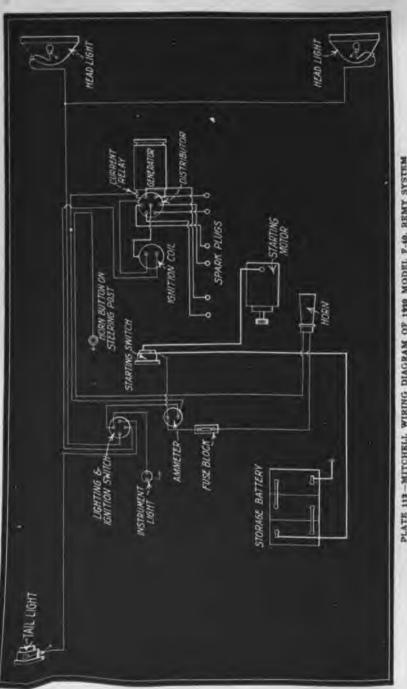


PLATE 112-MITCHELL WIRING DIAGRAM OF 1930 MODEL F-40, REMY SYSTEM

## ELECTRICAL EQUIPMENT

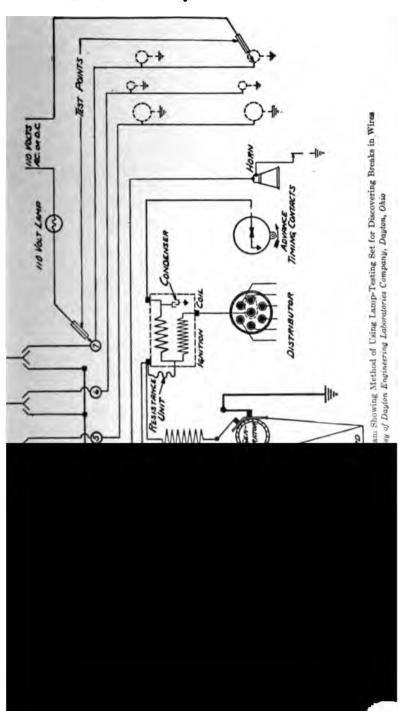

in is governed by both the air gap and the spring tension. The following examples will illustrate the adjustments necessary in cases of excess voltage and current, excess voltage alone, insufficient voltage and excess current, and insufficient voltage alone.

Where the relay cuts in at 8 volts and cuts out when the discharge current is 2 amperes: Decrease the air gap, as this will lower the voltage of the cut-in point, but it will also increase the discharge current on cutting out. To overcome the latter, increase the spring tension slightly, noting the effect on the ammeter until the latter registers less than 1 ampere on cutting out.


Where the relay cuts in at 8 volts and cuts out at 1 ampere: Decrease the spring tension as this will cause the relay to cut in at a lower voltage and also to cut out after the current starts to discharge through it.


Where the relay cuts in at 6 volts and cuts out at 2 amperes: Increase the spring tension, causing the relay to cut in at a higher voltage and also to cut out at a discharge-current value of less than 2 amperes.

Where the relay cuts in at 6 volts and cuts out with a discharge current of 1 ampere: Increase the air gap slightly and also increase the spring tension so as to cause the relay to cut in at a higher voltage and also cut out at a discharge current of less than 1 ampere.

In this connection cut in signifies the closing of the contacts when the voltage coil becomes energized as the generator starts up; cut out indicates the opening of the generator battery circuit when the current from the battery reverses the polarity of the current coil of the relay, thus opening the circuit and cutting out the generator from the battery circuit when the generator slows down and there is insufficient voltage for charging the battery. While these instructions apply particularly to the Delco relay or cut-out, all devices of this nature operate on the same principles.

Before making any adjustments, the contact points should be examined. If they are blackened or pitted, take two narrow strips of emery cloth about  $\frac{3}{8}$  inch wide and both the same length. Place them together, emery sides out, insert between the contacts and while an assistant holds the points together, draw back and forth. If no assistance be obtainable, use a single strip and apply alternately to each contact point until its face is bright all over and true

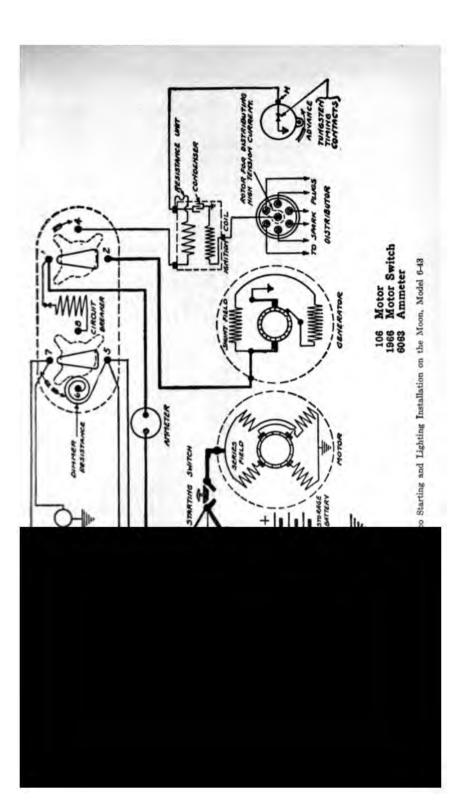

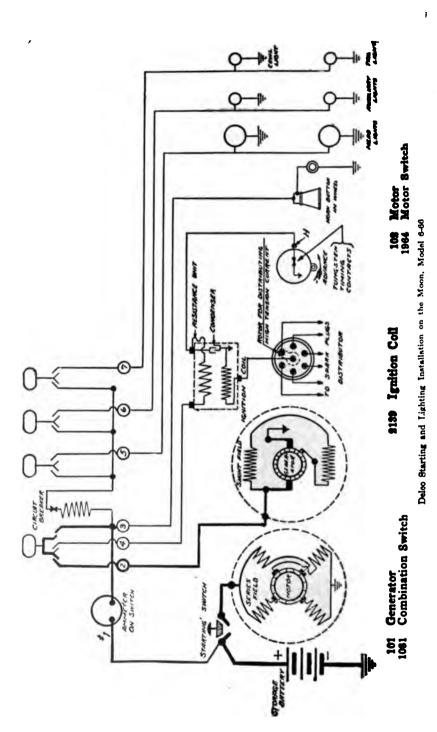

so that when the two points come together they touch evenly all over their surfaces. Do not take off any more than is necessary for this purpose, particularly where the contacts are platinum, as this simply wears them away uselessly and they are very expensive to replace. After cleaning, test for cutting in voltage and cutting out current and it frequently will be found that no adjustment is necessary.

These instructions regarding the cleaning of contact points apply with equal force to all instruments having contacts by means of which the circuit is frequently made and broken, for even platinum is burned away by the electrical action of the current which tends to carry the metal of the positive contact over to the negative in finely divided form, thus making a hole, or crater, on the positive and a cone, or peak, on the negative.


If the contacts are too badly burned to permit of their being put in good condition in this way, it will be necessary to replace them. After the relay has been reassembled with the new contacts, it should be adjusted in accordance with the instructions already given. When the contacts are correctly adjusted, both pairs will make contact at the same instant and clear across the line of contact so that when the relay is held up to the light, it is impossible to see light passing through any portion of the line of contact. When adjusting the relay make sure that all insulating bushings are in good condition and that the connections and coil terminals are free from breaks or grounds, as these would cause uncertainty in its




not open on a current of less than 25 amperes. If the ammeter reading indicates that it does so, increase the tension of the spring until the current necessary to operate it shows that it is properly adjusted. In case the instrument shows that the circuit-breaker is opening at the proper point but still continues to vibrate, another series of tests for a ground must be made as the latter is the cause of the trouble.

Seating the Brushes. To insure proper operation of the machine either as a generator or as a motor, it is necessary that the brushes fit the commutator exactly and that they make good contact over their entire surface. If they do not, sparking will occur and the commutator will become burned and blackened, cutting down the The brushes are the only wearing parts efficiency of the machine. of a direct-current generator or motor, and, as this wear on them is constant, they will require attention at intervals to keep them in good condition. Whenever sufficient wear has taken place to make the contact uneven, the brushes must be fitted to the commutator Cut a sheet of No. 00 sandpaper in strips slightly or sanded-in. wider than the brush. Emery cloth must never be used for this purpose. It is metallic and will tend to cause short-circuits in the commutator. The strip of sandpaper is wrapped around the commutator so as to make contact with at least half of its circumference in the manner illustrated in (a) and (c) of Fig. 261. The smooth side of the paper is laid on the commutator so that the sanded side rubs the brush. By drawing the sandpaper back and forth, it is possible to fit the brush very accurately to the commutator. It will be obvious that if the sandpaper be applied to the commutator, as shown in (b) and (d) of the same illustration, that the brush will only touch at its center and there will be excessive sparking between the gaps thus formed.


A high squeaking note caused by the operation of either the generator or motor is an indication that either the brushes or the commutator need sanding-in as the latter will become roughened from the wear. It should be smoothed up by taking strips of the same grade of sandpaper sufficiently wide to cover the commutator, applying them by wrapping in the same manner but with the sanded surface on the commutator bars. This can be done most effectively by running the machine through its other commutator

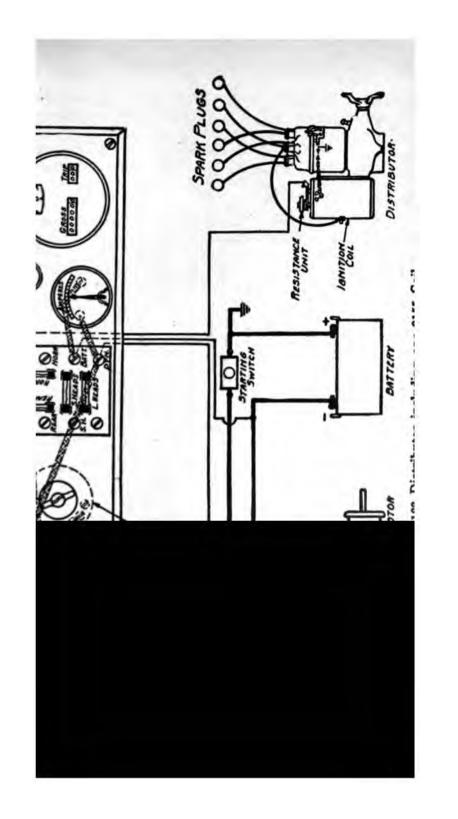

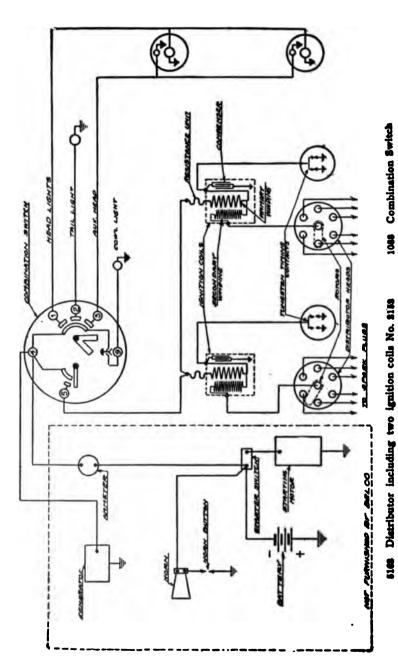

Delco Ignition Installation on National Twelve-Cylinder Care, Series A-K

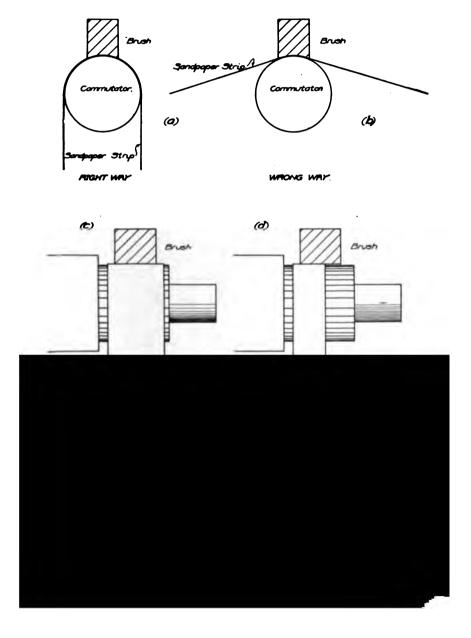for a few moments while holding the sandpaper strip in place on the first. If, after this smoothing up, the mica insulation between the bars of the commutator is flush with the surface of the copper bars, it must be undercut as directed in the following section. On most of the Delco machines it will be found possible to sand-in the upper



Commutator Maintenance. In the course of time, the commutator bars of the generator will wear down until they are flush with the mica insulation separating them. When this occurs there will be excessive arcing in the brushes which, in turn, will cause the copper to be burned away until it is level with, or below, the surface of the mica. This condition will be indicated by a rusty black color on the commutator bars. To prevent this condition, the commutator should be cleaned occasionally with sandpaper as directed. If the mica is high, it should be undercut as follows:

The armature is removed from the machine and placed in a lathe, truing up both commutators until they are perfectly concentric. This should be done carefully and then as fine a cut as possible taken to avoid wasting the copper



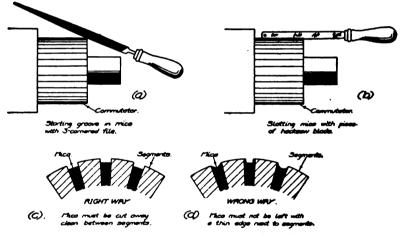


Fig. 262. Method of Undercutting Mica Insulation on Commutator Courtesy of Auto Electric Systems Publishing Company, Dayton, Ohio

needlessly. When the commutators have been trued up in the lathe, cut out mica between the commutator bars of the generator only. For this purpose a piece of hacksaw blade should be fixed in a handle, as shown in Fig. 262, and its teeth ground off until they will cut a slot that is just slightly wider than the mica insulation. The cut need not be more than  $\frac{1}{32}$  inch deep. In this way a rectangular slot, free from mica, will be obtained between each two adjacent commutator bars. After undercutting the mica, the edges of these slots should be beveled very slightly with a three-cornered file in order to remove any burrs which would cause excessive wear of the brushes.

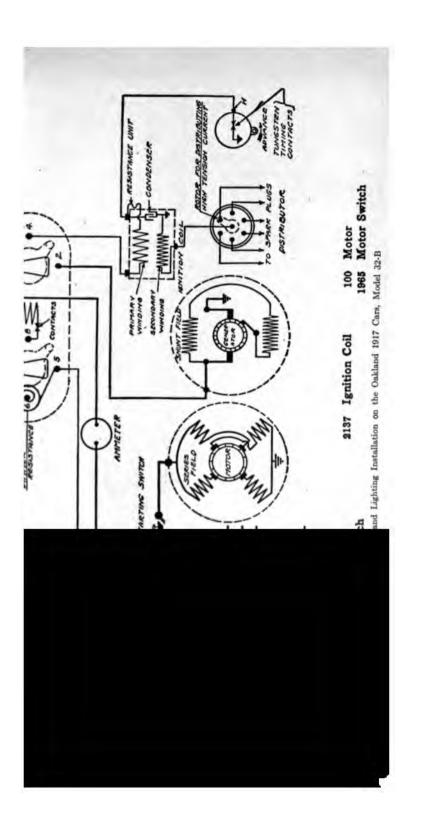It is unnecessary to undercut the mica on the motor commutator, as, wherever metal or metallic brushes are used on Delco machines, they are sufficiently hard to keep the mica flush with the surface of the copper as it wears down without any undue arcing at the brushes, whereas in the case of generators provided with



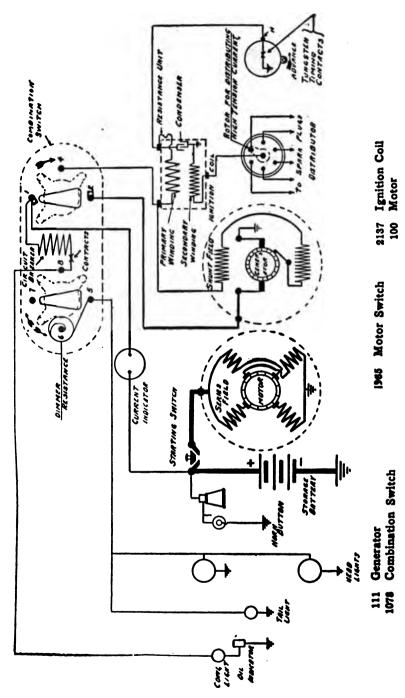

Delco Starting and Lighting Installation on the Oakland, Model 34

Carbon brushes, the carbon is not hard enough to do this. After completing the undercutting, the commutator when viewed from the end should show clean-cut rectangular slots between the bars, as in the left-hand view, Fig. 262. The machine should then be reassembled and the brushes sanded-in to the commutator, as previously described. This operation of fitting the brushes to the commutator will be necessary whenever anything has been done to the commutator, when new brushes are installed, or when the third-brush location is readjusted to vary the output of the machine on generators having this type of regulation.

These instructions for fitting the brushes, cleaning the commutator, and undercutting the mica of the commutator of any machine equipped with soft-carbon brushes, apply with equal force to all makes of generators and starting motors employed on auto-Next to the battery the brushes and commutators will be found to demand most attention—or to put it another way, they will be found to constitute a cause of trouble only second in importance to the battery. It must not be assumed, however, that all blackening of the commutator is caused always by high mica. of the following conditions may cause the commutator to assume an appearance similar to that produced by high mica: (1) generator brushes of improper size or material, as where replacements other than those supplied by the manufacturer of the machine have been installed; (2) insufficient spring tension on brushes—all springs slacken up in time and they should be examined at intervals to see that the brushes are being held firmly against the commutator; (3) overloading of the generator caused by partial failure of the regulating device or other cause; and (4) an open- or short-circuit in the



the like, which temporarily put the system out of commission, so the every part of the system which might be at fault should be invest gated before attempting to test the armature for faults. To car out these tests, the voltmeter and the lamp-testing set are necessar Where no previous experience has been had in making tests with the aids, it will be well to become familiar with the detailed instruction given for their use in connection with the determination of oth faults, as already described. It is not necessary to remove the dyn motor from the car for this purpose. When tests of the remaind of the system indicate no faults and when grounds in the armatu


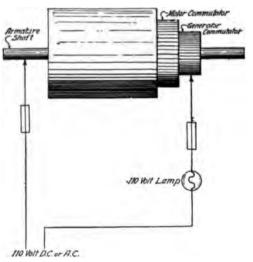



Fig. 263. Diagram for Locating Grounded Generator Coil with Lamp-Testing Set

windings or short-circui between them are no suspected, raise all th brushes from the commi tator and slip pieces cardboard between th brushes and the commi tator so as to insular them from each othe These instructions cover the single-unit Dela machine, so the foregoin applies as well to testing for short-circuits betwee generator and moto armature windings. For greater simplicity, th

possible faults and the tests for locating them are treated undedifferent heads, as follows:

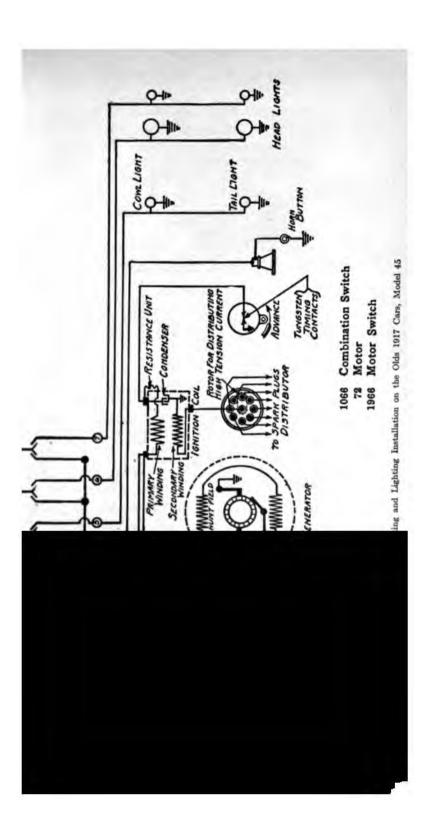(a) Grounded Generator Coil. On one-wire systems of the single-unit type, the presence of a grounded generator coil will materially reduce the charging rate to the battery and will also result is slow cranking of the engine. To determine whether a generate coil has become grounded, place one of the test points on the frame con the armature shaft, both of which are grounded, and the other of the generator commutator, as shown in Fig. 263. If the lamp light it indicates a ground on the commutator. The test of the generate of a two-unit set would be carried out in exactly the same manner.



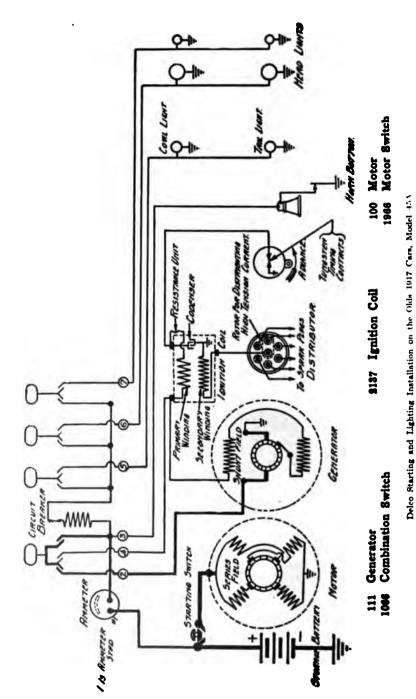

) Grounded Motor Coil. According to the nature of the fault, aded motor coil may either prevent operation of the starting

altogether or it esult only in an ve consumption of for starting. The carried out in the anner as described generator, except the second point of the set is placed on performed to the starting motor tested in the same


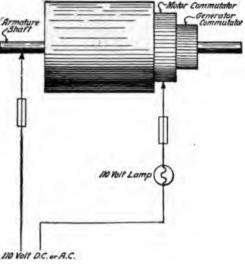


Fig. 264. Diagram for Locating Grounded Motor Coil with Lamp-Testing Set

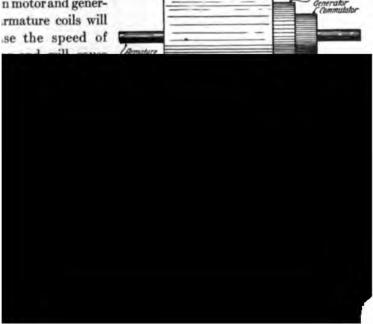Motor and Genermature Coils. In ases short-circuits n motor and generrmature coils will se the speed of



naturally only applicable to single-unit machines having two independent windings on the same armature core, as in the case of the Delco, the type in question.

(d) Open- or Short-Circuited Generator Armature Coils. When testing for open- or short-circuited generator armature coils, the generator brushes should be left in contact with the commutator, but the storage battery should be disconnected from the system, carefully taping the loose battery terminals before proceeding. Then disconnect the shunt field from the brushes and tape these terminals so that they do not accidentally come in contact with the frame or other parts

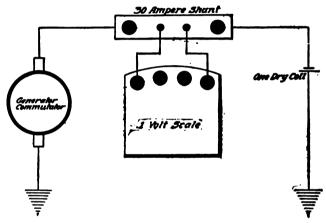


Fig. 266. Diagram for Testing Open- or Short-Circuited Generator
Armature Coil with Ammeter

of the unit. Connect up a dry cell and the portable ammeter, using the 30-ampere shunt, as shown in Fig. 266. Turn the armature over slowly by hand. If the commutator is clean and bright and the brushes are making good contact with it, a very noticeable change in the ammeter reading will indicate an open- or a short-circuited armature coil. To determine whether the coil is open- or short-circuited, the following tests should be made:

(1) Open-Circuited Coils. Connect the brushes to the terminals of the dry cell so that a current of about 10 amperes is flowing through the brushes. The field should be entirely disconnected and its terminals either taped or held out of the way. Then, with a special pair of points connected to the voltmeter,


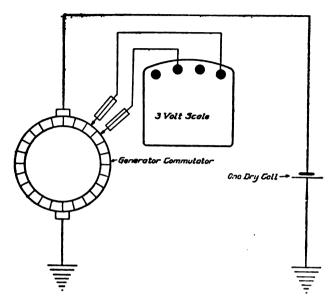


Fig. 267. Diagram of Set-Up when Coils Are Open-Circuited

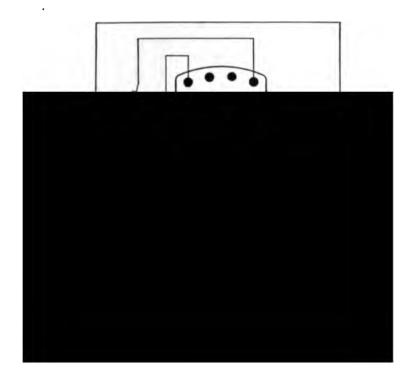

using the 3-volt scale, measure the voltage across each two adjacent commutator bars. If there is an open-circuited coil in the armature, the voltage reading will increase considerably, Fig. 267.

(2) Short-Circuited Coils. If there are no open-circuited coils and the preceding tests indicate that there is trouble with the armature, it should be tested for short-circuited coils. should be done only after the preceding tests have been made, as an open-circuited coil might cause the .1-volt scale of the voltmeter to burn out if this test were made first. The armature is connected as indicated in(1) above, but for this test the .1 -volt scale instead of the 3-volt scale of the voltmeter is used. Fig. 268. The voltage drop between adjacent commutator bars is then measured by slowly turning the commutator over by hand. The readings should be approximately the same. If any of them drop nearly to zero, it will indicate that one or more of the armature coils are short-circuited. In taking these readings, care must be observed to keep the points always on adjacent commutator bars and not allow them to span more than two bars at any time; otherwise, the voltage drop may be sufficient to injure the voltmeter.

Should any of these tests indicate open- or short-circuited coils in the armature, it is advisable to send the armature to the manufacturer for repairs, or to install a new armature. Unless the fault is plainly visible, as where a coil-terminal connection at the commutator bar has broken or become short-circuited, the average establishment will find the repair entirely beyond its facilities to make, so that time and expense will be saved by promptly referring it to the factory. Special equipment and skill in the handling of such repairs are indispensable and are beyond the province of the garage man.

Testing Field Coils. The tests of field coils are simpler than those of the armature, and they apply in large measure to practically any system.

Open-Circuits in Fields. To test for open-circuits in fields, the test set is the only apparatus required, and the points should be placed as shown in Fig. 269. By placing one point on each terminal of the particular winding to be tested, failure of the lamp to light

will indicate that the coil is open-circuited, as the wire of the coil will afford a path for the current, unless broken. The fact that the lamp

may not light to full brilliance in some of these coil tests is no indication of trouble, as the difference is simply due to the additional resistance represented by the coil itself. In case an open-circuited coil is found, the only remedy is to return it to the manufacturer for repair or replacement.

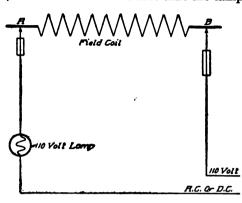


Fig. 269. Diagram for Locating Open Circuits in Field Coils with Lamp-Testing Set

Grounded Fields. To


Coils with Lamp-Testing Set


test for grounds in the field windings, place one test point on the
frame of the machine and the other on a terminal of the field coil.

Before doing this, however, all intentional ground connections made
by the terminals should be removed. These can be located by
referring to the winding diagram. If the lamp lights, it will indicate


a ground. The manner of applying the test points is shown in Fig. 270.

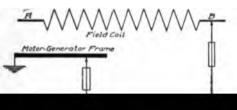Short-Circuits between Windings. To test for



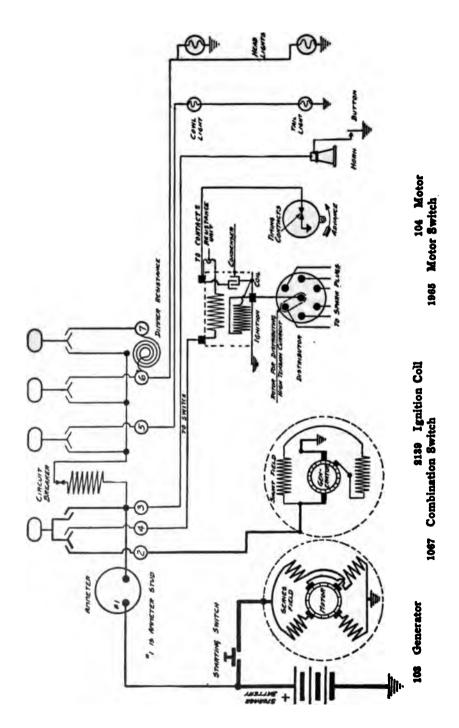

naturally be much less. In other words, the value of the voltmeter reading will always depend upon the amount of resistance offered by the coil or other circuit that is being tested. When there is no circuit, as with the free ends held apart in the hands, there will be no indication on the voltmeter scale. An open-circuited coil will accordingly be indicated by a zero reading of the voltmeter when the two free ends, or points, are placed upon the terminals of the coil, Fig. 272. If, on the other hand, the voltmeter reading is nearly half of that of the battery voltage, the coil is in good condition. This test corresponds to that with the lamp-testing set using the 110-volt

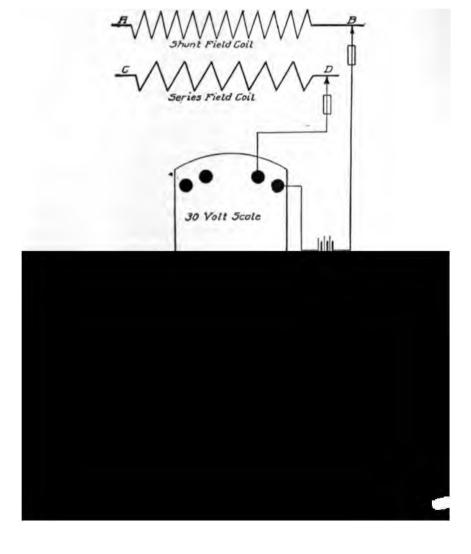

all lighting generators have more than one winding on their fields, i.e., shunt and series windings (the latter termed "bucking coils" when reversed), these tests are equally applicable to all makes.

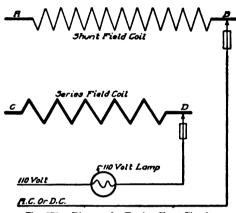


Fig. 271. Diagram for Testing Short-Circuits between Windings

Voltmeter Field Tests. The method of employing the voltmeter for making field tests, shown in Figs. 272 and 273, is as follows:

To test for an opencircuited field, connect up as shown in Fig. 272. The positive terminal of the voltmeter is connected to the positive terminal of the battery. An insulated copper wire of convenient length, with the insulation

stripped off for about one inch at each end, is then attached to the terminal of the voltmeter marked "30 volts", and a similar wire is

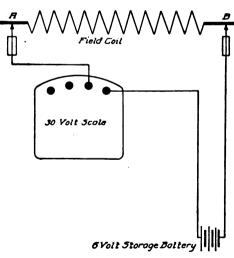


Fig. 272. Voltmeter Test Diagram for Open-Circuited Field

attached to the negative terminal of the battery. The free ends of these wires are then used in the same manner as the points of the test set, except that the voltmeter reading is the indication sought instead of the lighting of a lamp. Before making the test, touch the free ends of the wires together. This reading will be the total voltage of the storage battery, and it should be kept in mind when making the tests.

If, instead of touching the free ends of the wire together, they are placed on the terminals of a high resistance, the voltmeter reading will

naturally be much less. In other words, the value of the voltmeter reading will always depend upon the amount of resistance offered by the coil or other circuit that is being tested. When there is no circuit, as with the free ends held apart in the hands, there will be no indication on the voltmeter scale. An open-circuited coil will accordingly be indicated by a zero reading of the voltmeter when the two free ends, or points, are placed upon the terminals of the coil, Fig. 272. If, on the other hand, the voltmeter reading is nearly half of that of the battery voltage, the coil is in good condition. This test corresponds to that with the lamp-testing set using the 110-volt

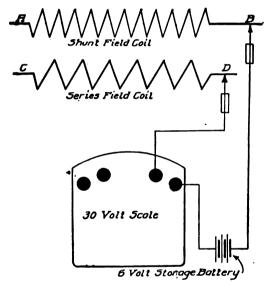


Fig. 273. Voltmeter Test Diagram for Short-Circuit between Coils


current, illustrated in Fig. 269. It is a method which also permits one coil to be checked against another of the same kind, as the readings given by the two coils should be approximately the same. Where neither a 110-volt current nor a portable voltmeter are available, these tests may be carried out with the aid of a 6-volt bulb in connection with the storage battery, as shown for the voltmeter tests. In this case, the lamp will light brightly when the free ends of the wires are brought together, but it will dim in proportion to the amount of extra resistance added to the circuit, as represented by the coil under test. While not so accurate as the tests with the voltmeter, comparative


tests are also possible with the low-voltage lamp, a very perceptible difference in the lighting of the lamp indicating a greatly increased resistance. When using current from a storage battery for testing, care must be taken to have the points of the test set, or ends of the wire, clean and bright, and to make good, firm contact. If necessary, places on the machine at which the test points are to be applied should first be scraped or filed clean, otherwise, additional resistance will be inserted by the poor contact at the points, as for example, where the latter are applied to a painted surface.

To test for grounds in a field, after having removed all ground connections, as mentioned in a previous paragraph, place one end, or point, on a terminal of the field coil and the other on the frame of the machine. The method of making the test is identical with that shown in Fig. 270, except for the substitution of the voltmeter for the 110-volt light circuit. If the coil is free from grounds, the voltmeter needle will remain at zero; in case, there is a ground, there will be an indication on the instrument and the worse the ground the greater the value of this reading will be. This test corresponds to that illustrated in Fig. 264.

Short-Circuits between Coils. The test for short-circuits between coils is similar to that shown in Fig. 265 and naturally applies to all lighting generators where the two windings of the fields are concerned. Place one end, or point, on the terminal of one winding and the other end on the terminal of the other winding, as shown in Fig. 273. If there is no connection between the coils, as should be the case, the voltmeter needle will remain stationary. Any movement of the voltmeter needle indicates a short-circuit and the greater the value of the reading, the more complete is the short-circuit between the two coils.

In order to make these tests without removing the machine from the car, first, disconnect the storage battery and tape the disconnected terminals; then, insulate all the brushes by placing pieces of cardboard between them and the commutators. Disconnect all wires leading to generator terminals, and, likewise, all wires leading to field-coil terminals. By referring to the circuit and wiring diagrams for the particular car under consideration, all these leads can readily be identified, and after disconnecting them, the field coils of the machine can be tested. When the tests indicate that the field coils

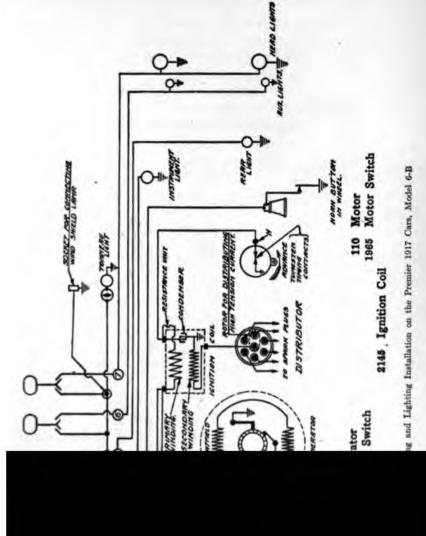

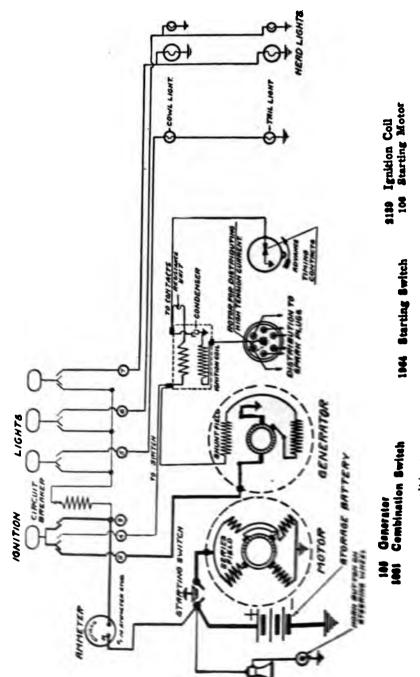

Deline Starting and Lighting Installation on the Stephens, 1917 Medici

e not in perfect condition, it will usually be found advisable to nove the field coils from the machine and send them to the manufacrer for repair or replacement, for unless the fault is plainly apparent, nich will seldom be the case, the repair will usually be found to be yond the average garage facilities.

#### DISCO SYSTEM

## Twelve-Volt; Single-Unit

**Dynamotor.** The dynamotor is bipolar with both windings nnected to the same commutator.

Regulation. Constant current-control regulation by means of a brating regulator is employed. (See description of the Ward-conard regulator, Fig. 149, Part IV.)

Operating Devices. Battery Cut-Out. The cut-out is of the nventional type, combined with the current-control regulator.

Switch. The switch is the spring-controlled type which is only sed for starting.

### Six-Volt; Two-Unit

Units. Both the generator and the starting motor are of the polar type, the motor being designed to operate through a Bendix ive.

Instructions. As both types of the system are characterized standard features throughout, instructions given in connection



to turn the engine over, this characteristic being termed the "non-stalling" feature of the system. Provided the battery is sufficiently charged, the dynamotor will always act as a starter (the switch being closed) whenever the engine is inadvertently stalled or its speed drops below the generating point of the machine.

Instructions. The switch must never be left closed with the engine stopped, and when the car is stopped, the engine must not be allowed to idle at a very low speed, as in either case the battery will be run down. Instructions for lack of generator capacity the location of grounds or short-circuits, and the like, are the same as for other systems.

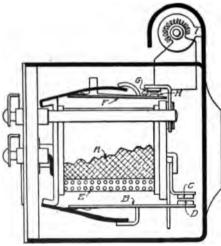



Fig. 274. Sectional View Showing Details of Dyneto Regulator-Cut-Out

#### Six-Volt: Two-Unit


Generator. The generator is a standard shunt-wound machine of the four-pole type, having two wound, or salient poles, and two consequent poles. (See Fig. 219, Part IV.) It is ordinarily designed to be driven at one and one-half times engine speed, but, in common with other makes, machines wound for higher or lower speeds are furnished, according to the

requirements of the engine on which it is mounted.

Regulation. Regulation is effected by means of a vibrating regulator, which is combined with the battery cut-out. This cuts in at a speed equivalent to 10 miles per hour, and the generator reaches its maximum normal output of 10 to 12 amperes between 12 and 15 miles per hour. The regulator does not become operative until the current flow increases to 10 to 12 amperes, at which point it is held regardless of the speed. The details of the combined regulator and cut-out are shown in Fig. 274, while all the connections are shown in the diagram, Fig. 275. As soon as the dynamo runs fast enough to cause it to generate, a portion of the current passes through the

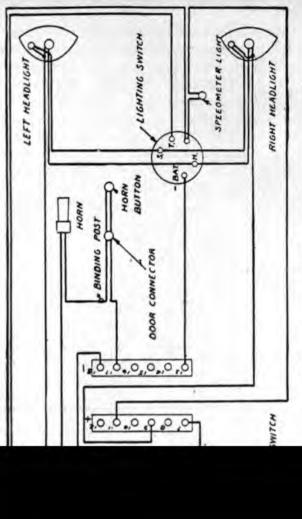

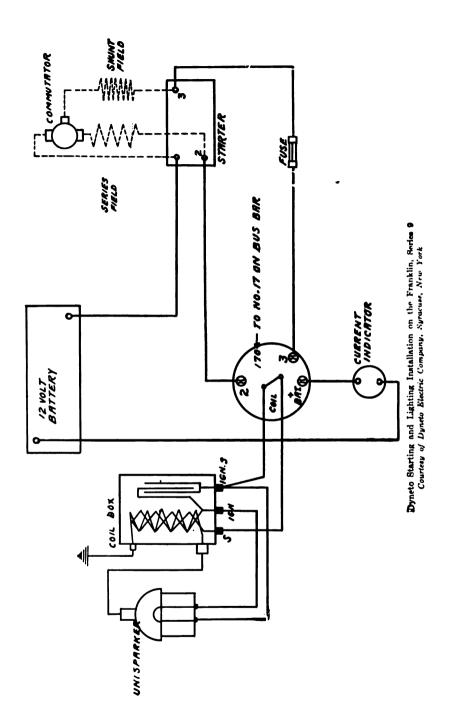
arting and Lighting Installation on the Franklin, Series 8




winding A of the cut-out, Fig. 274. This is ordinarily known as the voltage winding and is of fine wire, so that very little current is required to energize the core and attract the armature B, which closes the contact points C and D. These points close the circuit through the coil E, which is of heavy wire and is known as the current coil. As the current in both coils is in the same direction, their exciting effect on the magnet core is cumulative, and the points are held together that much more firmly.

On the upper side of the magnet will be noted another armature F and a set of contact points G and H. This armature is subject to the same magnetic attraction, but the tension of its controlling spring is

Dynamo

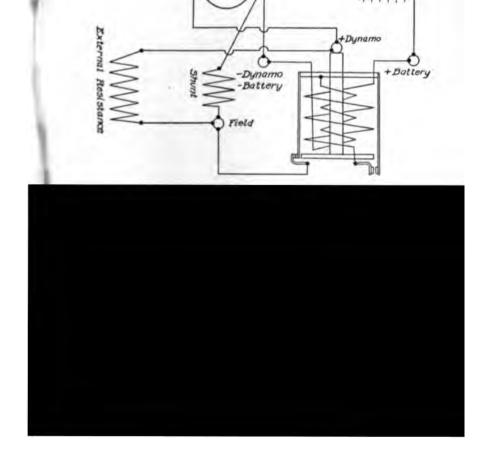

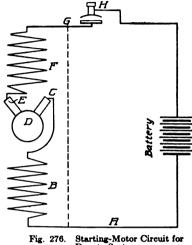field windings, thus keeping the output within the required limits. When the generator speed falls below the normal rate, the voltage drops correspondingly and the battery current overcomes that from




Starting-Motor Circuit for Dyneto System

the generator and reverses the current flow through the current coil E. This reverses the magnetic effect produced, bucking that caused by the generator current in the coil A, and, as the battery current is then superior to the latter, the magnetic effect of A is neutralized and the armature B is forced away, opening the contacts C and D.

Starting Motor. This starting motor is of the standard series-wound type of the same characteristics of design as the generator. In Fig. 276 is shown

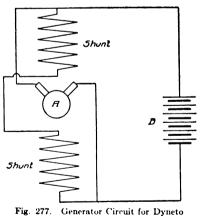the wiring diagram of the starting circuit and illustrates plainly the relation of the series fields B and F to the armsture D and



the brushes E and C. H is the starting switch and A and G are the cables of a two-wire starting system. Compare Fig. 276 with Fig. 277, which shows the shunt windings of the generator and their relation to the armature and battery. In Fig. 276 the dotted line from G to A illustrates a supposed short-circuit caused by chafing, or abrasion, of the insulation of the wires.

Wiring Diagrams. Either the single- or the two-wire system

of wiring is employed, according to the car on which the system is installed. Fig. 278 shows the one-wire, or grounded, system, and Fig. 279 shows the two-wire system.

Instructions. In case of failure to start, the switch should always be released instantly and the battery tested to determine its condition


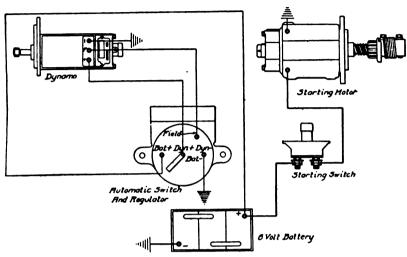


Fig. 278. Wiring Diagram for Dyneto One-Wire System

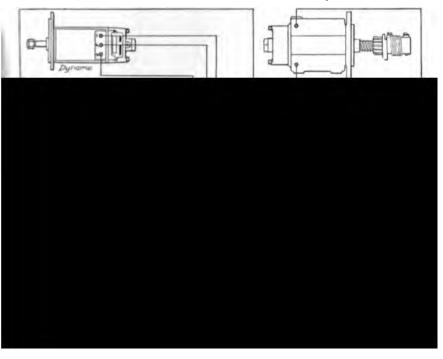of charge. If the battery is not run down, examine all connections and wiring, for, if a short-circuit exists as indicated by the dotted line



on the starting motor and inspect the brushes. Lift each brush holder a trifle (if they are in proper condition, they should spring back when released) and press the brushes firmly against the commutator. (See Gray & Davis instructions for Spring Pressures on Starting Motors. These pressures are not the same on all makes, but this will give some idea of the high pressure necessary to make the contact required to handle the heavy currents used in the starting motor.) See that the commutator is clean and the brushes are making uniform contact all over their surfaces. Make sure that the two leads from the field coils to the brush holders are screwed down tightly.

When it is necessary to renew the brushes, remove the eight screws shown holding the end plate. Remove this commutator housing, or end plate, leaving the brush unit in place on the commutator. Remove only one brush at a time and replace it with a new Note bearing of brushes on commutator and sand-in to a true and uniform bearing over the entire surface of the end of each brush. When this has been done, carefully clean out all traces of carbon dust, using a rag wet with gasoline, if necessary; a small bellows may be used to advantage to blow this dust out dry, and will be more likely to get it out of the nooks and crannies then wiping. After the brushes have been sanded-in and the dust all cleaned out, see that both brush leads are tight and then replace the housing. New brushes should be necessary only after a year or two of service, sometimes longer; old brushes will operate just as efficiently as new ones, provided they have a bearing all over their surface and are held firmly against the commutator. A brush becomes too short for further use only when the spring can no longer hold it in good contact against the commutator. When ordering brushes, it must always be specified whether they are wanted for the generator or for the motor, and the type of machine, as stamped on the name plate, must be given. This applies equally to the brushes needed for any make of generator or starting motor, and no other brushes than those supplied by the maker for the machine in question should ever be used.

# GRAY AND DAVIS SYSTEM Six-Volt; Two-Unit; Single-Wire

Generator. The bipolar generator is designed for drive by silent chain, as shown in Fig. 280, or when combined with ignition distributor from the pump shaft, Fig. 281.

FIELD COIL

RMATURE

Regulation. Earlier types, including the original lighting generator, were of the constant-speed type regulated by a governor and slipping clutch, which maintained the speed of the generator constant. The 1914 and subsequent models are controlled by a combination regulator cut-out, usually mounted directly on the generator itself. The regulator increases the resistance of the generator-field windings in proportion to the increase in speed, thus maintaining a steady output.


Starting Motor. The series-wound bipolar motor is made for either open or enclosed flywheel drive, according to the type of car. In Fig. 282 is shown the open flywheel type. The illustrations of

REGULATOR


CUT-OUT

COMMUTATOR

MELD YOKE

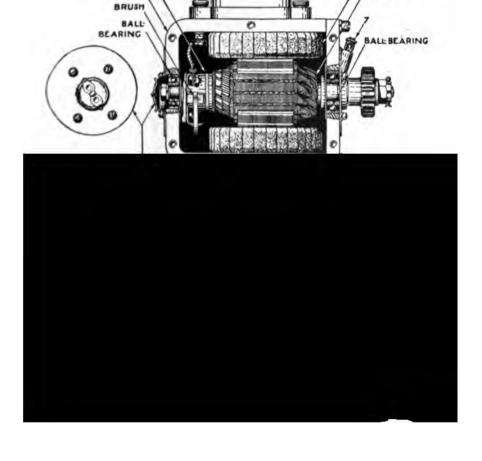


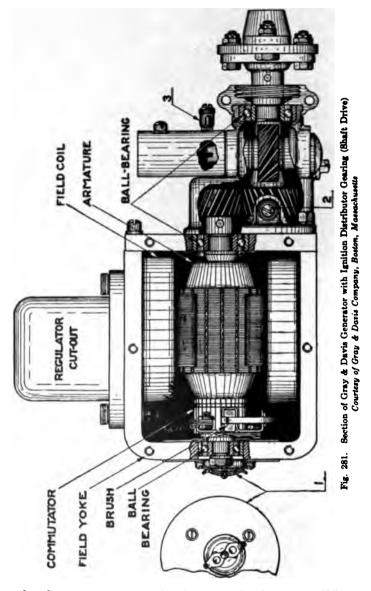per hour, lights on, charge at 3½ amperes. Under the last-named condition, the lights are being supplied directly by the generator



and only the excess current is charging the battery. Whenever the generator output drops below a point where it is supplying

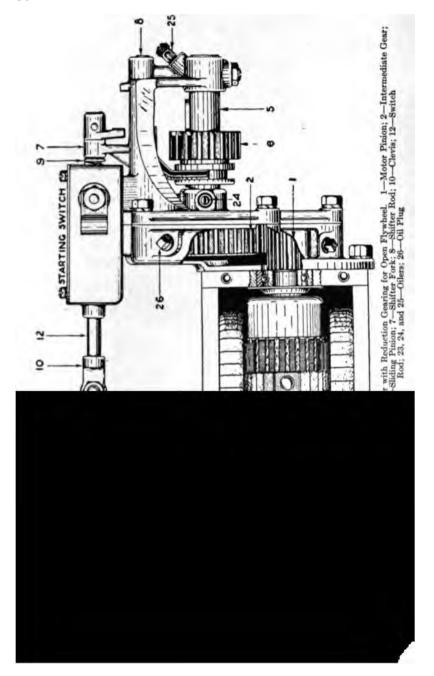ifficient current to light all the lamps that are on, the battery ipplies the balance. The battery is thus said to be floated on the



Regulator Cut-Out. The regulator is of the constant-current type and on the Chandler, Metz, and Chalmers cars is set to allow the generator to produce a minimum of 8.5 amperes and a maximum of 11 amperes; on the Paige the minimum is the same, but the maximum is 12 amperes.

To Check for Adjustment. Insert the portable ammeter with the 30-ampere shunt in the circuit between the generator and the regulator and switch on all the lamps. Speed the engine up so that the generator is running above 1750 r.p.m. Open the upper set of points by inserting a match or using the finger, then adjust the lower set of points in accordance with the reading of the ammeter. Open the lower set and adjust the upper in the same way. Run the machine


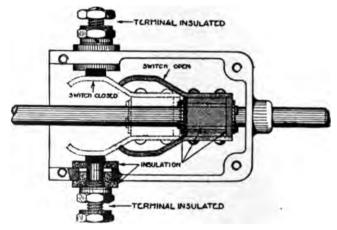



Fig. 283. Gray & Davis Starting Switch with Both Terminals Insulated

with both sets free, and the ammeter reading should fall within the limits above given.

To Check Candle Power of Lamps. These instructions are given by the manufacturers in connection with a special bench testing set using three 15-c.p. lamps in multiple. Check the candle power of the lamps on the car to see that their total does not exceed 45 c.p., as 25-c.p. headlights are sometimes used. The employment of headlights of this high power should be discouraged by the garage man, as they needlessly increase the load on the battery and cause a blinding glare.

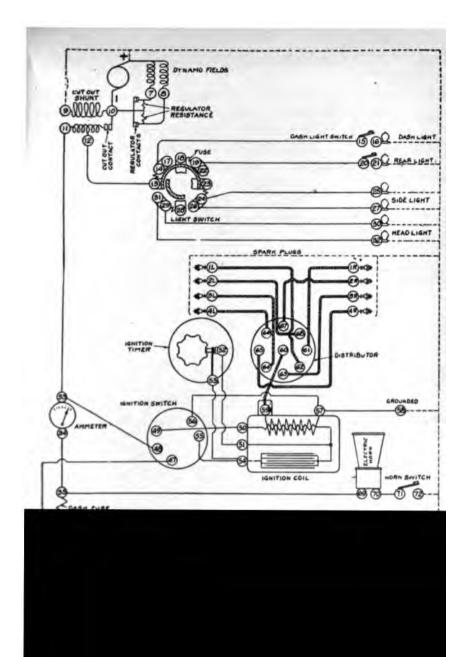To Check for Closing Voltage. The points of the battery cut-out are designed to close at 6½ to 6 volts from the generator and are



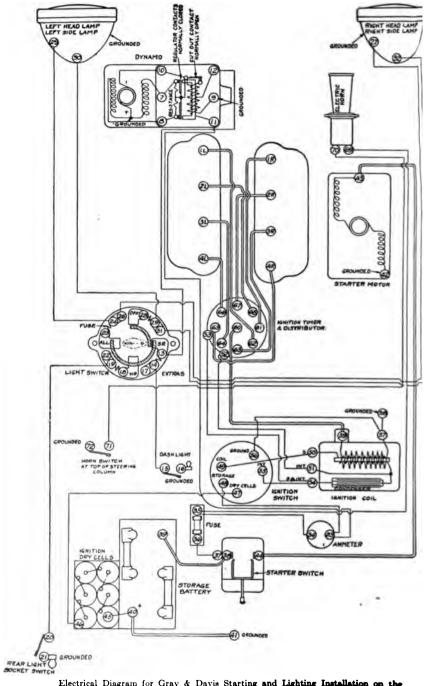


Electrical Diagram for Gray & Davis Starting and Lighting Installation on the Peerless, Model 56

Courtesy of Gray & Davis, Inc., Boston, Massachusette

designed to open on a current of \( \frac{1}{2} \) to 2 amperes from the battery on discharge. Connect the low-reading voltmeter, scale 1 to 10 volts, across the generator brushes. Gradually speed up the generator and note the voltmeter reading to determine the voltage at which the points close. If not correct, adjust the cut-out spring to bring the closing voltage within the above limits.

To Check the Cutting-Out Point. Connect ammeter in battery and cut-out circuit, using low-reading shunt, 1 to 3 amperes. Have the machine running at a speed at which points are closed, and gradually slow down, observing the ammeter reading when the points

Air gap at point 015

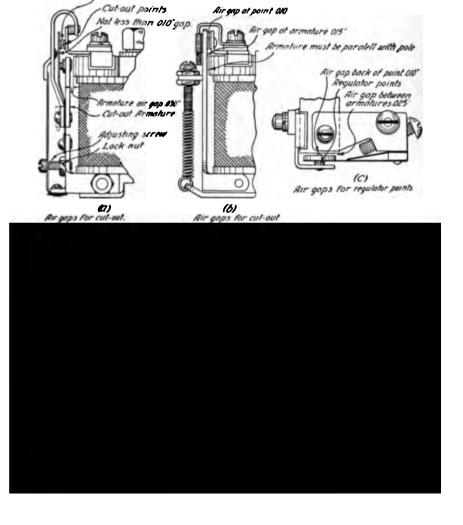

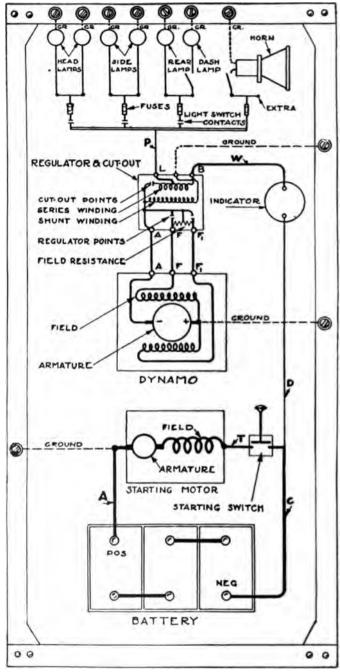


Fig. 285 Wiring Diagram for Gray & Davis Single-Wire System with Grounded Motor

naturally impossible to give complete lists of installations in any case, so that only one or two representative makes are mentioned to enable certain systems to be identified in the garage when desired.

Grounded-Motor Arrangement. Fig. 285 shows the Gray & Davis wiring diagram with grounded motor. Cable A from the battery positive terminal connects to the grounded terminal of the starting motor. Cable T connects an insulated terminal on the starting motor to one of the starting-switch terminals. Cable T from the starting switch terminal connects to the battery negative terminal, thus completing the circuit. On some makes of cars, cable T instead of

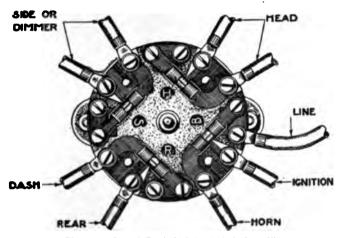


Fig. 286. Gray & Davis Lighting Switch, Rear View



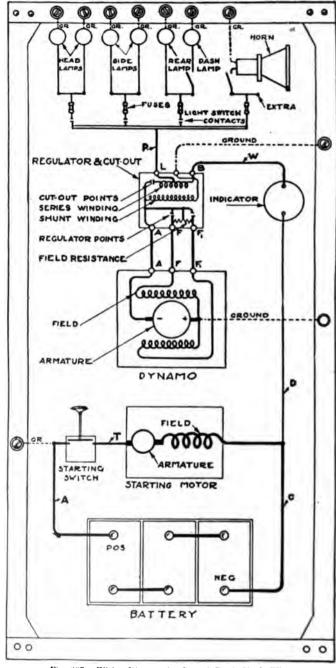


Fig. 287. Wiring Diagram for Gray & Davis Single-Wire System with Grounded Switch

connected to the fused side of B. The various ground connections are as follows: battery positive by cable A to frame at grounded terminal of starting motor; generator positive terminal to the frame of the dynamo itself; one side of all lamps to frame of car.

Grounded-Switch Arrangement. Fig. 287 is the Gray & Davis wiring diagram of the grounded-switch type. The only difference between this and the other diagram is that the ground connection is taken from the terminal of the cable A to the switch instead of from the motor.

Instructions. When the indicator does not indicate charge though the engine is speeded up, but indicates discharge with the engine stopped, the dynamo or the regulator may not be working properly. To verify this, turn on all the lights, run the engine at a speed equivalent to 10 miles per hour, disconnect the wire from terminal B. Fig. 285, at the regulator cut-out; if the lights fail, either the dynamo or the regulator is at fault. Reconnect the wire to terminal B and remove the side plate from the dynamo to examine the brushes. Slide the brushes in and out, and see that they slide freely in the brush holders and make good contact with the commutator and that the wires from the brush holders and the fields to the dynamo terminals are firmly connected. If the dynamo is belt-driven, the belt may not be tight enough to rotate the dynamo at sufficient speed to charge the battery. The commutator, if coated or dirty, may be cleaned while rotating by holding a cloth slightly moistened with oil against it.


Should there touts fail to some du trouble connect a mire at the


But if, under conditions just given, the indicator, or ammeter, shows neither charge nor discharge, the dynamo circuit is open. This may be from poor brush contact or from a loose or broken connection at some other point. If the indicator shows discharge, reduce the engine speed to the equivalent of 8 or 9 miles an hour; then while the engine is running, connect another wire from the dynamo terminals F and  $F_1$  to terminal A. If the indicator then shows charge, the regulator is at fault, as this wire cuts the regulator out of the charging circuit. While making this test, care must be taken not to run the engine any faster than mentioned, as the dynamo is not protected by the regulator. If in this test, the indicator still shows discharge, it signifies that the dynamo field circuit is open or that the armature is short-circuited.


Loose Connections. If with the engine speeded up the indicator does not show charge and with the engine stopped and the lights turned on it does not indicate discharge, there is an open or loose connection in the battery circuit. See that all the wires are firmly connected and that the contact faces are clean. Or the indicator itself may be at fault. Verify this by disconnecting one wire from it and if it then returns to neutral, it indicates that some part of the wiring is grounded on the frame of the car and is causing a short-circuit which is discharging the battery. But if after disconnecting this wire the indicator shows discharge, it is at fault. See if the pointer is bent. This probably will be the case if it indicates charge with the engine stopped.


Short-Circuits. If the ammeter discharge reading is above normal, it may indicate that higher candle-power lamps have been substituted for the standard bulbs, or that some of the lamp wires are short-circuited. Intermittent jerking of the pointer from charge to neutral while the engine is being speeded up also indicates a short-circuit. Repeated blowing of fuses indicates short-circuited lamp wires or defective lamps. Trace the wires along their entire length and try new bulbs.

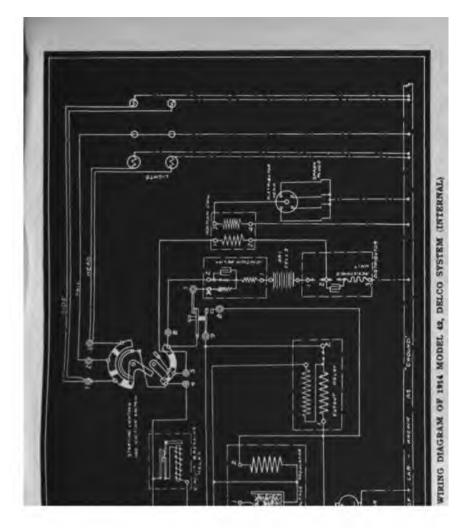Starting-Motor Faults. If the motor does not rotate, the battery may be discharged. In case the engine has been overhauled just before, main bearings may have been put up so tight that the starting motor has not sufficient power to turn it over. The starting switch may not be making good contact, the motor brushes may not be




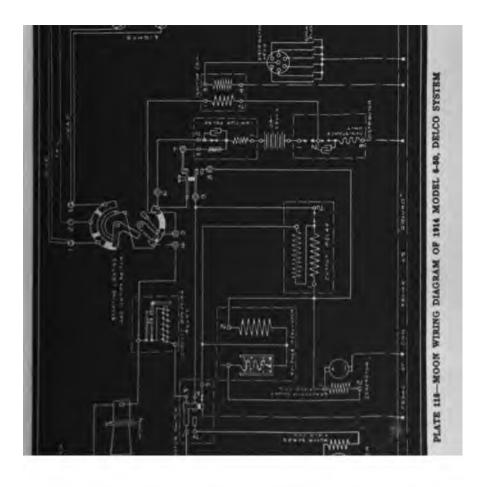


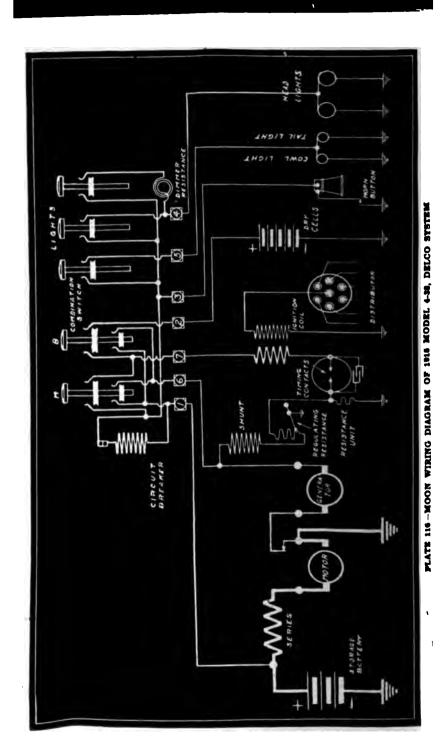

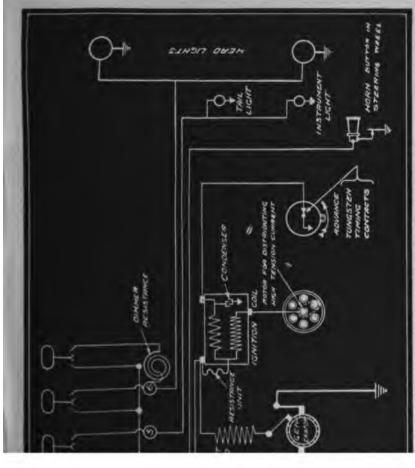

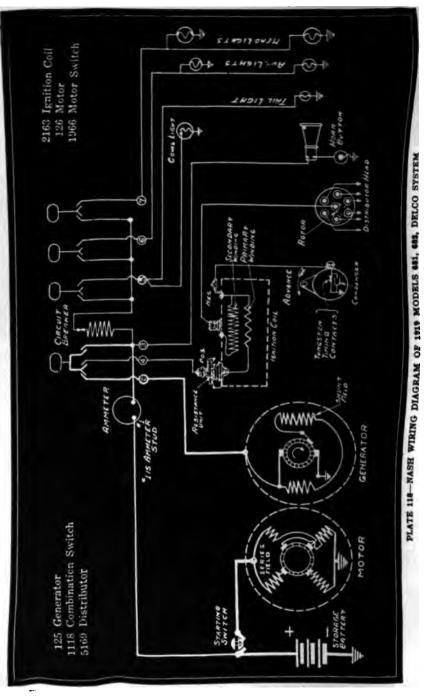WIRING DIAGRAM OF 1914 MODELS 4-30, 4-40, DELCO SYSTEM



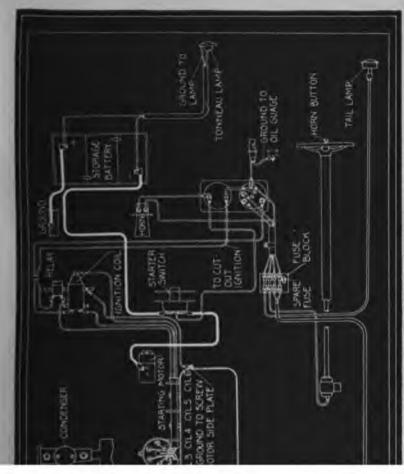

I WIRING DIAGRAM OF 1920 MODELS 681, 682, WAGNER SYSTEM



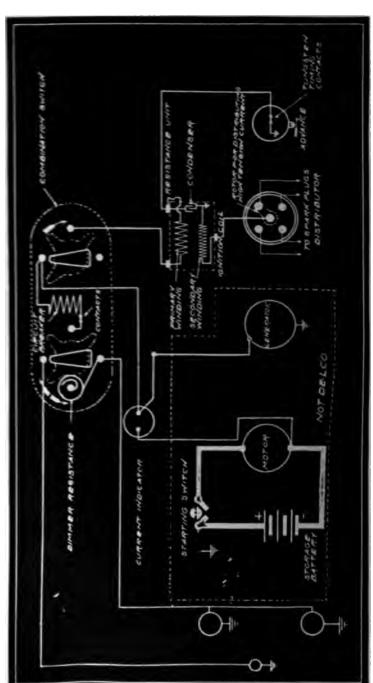


PLATE 156 -HASH WIRING DIAGRAM OF TRUCK MODEL, DELCO STRIEM

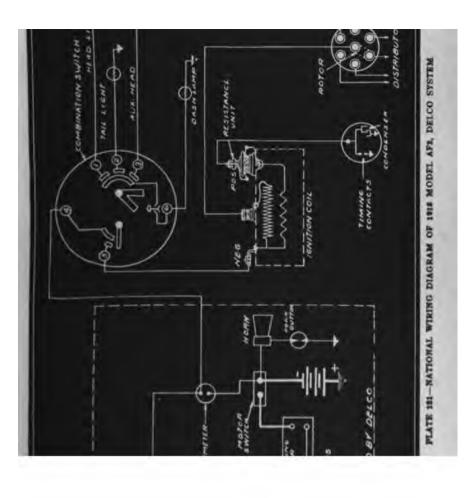

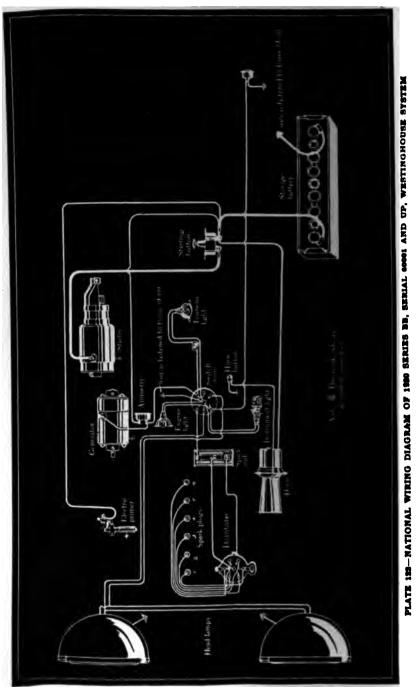



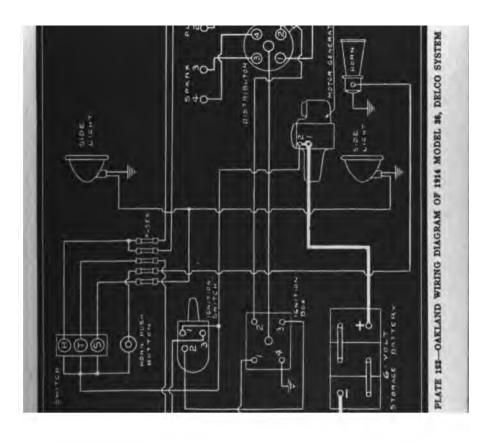


PLATE 194-OAKLAND WIRING DIAGRAM OF 1914 MODELS 46-68, DELCO SYSTEM

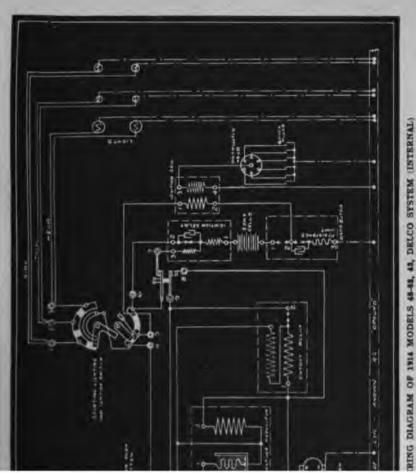

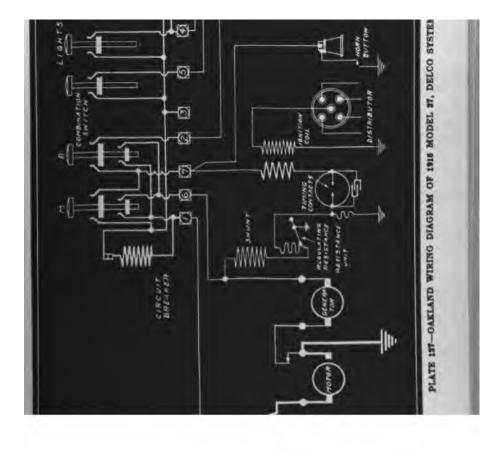



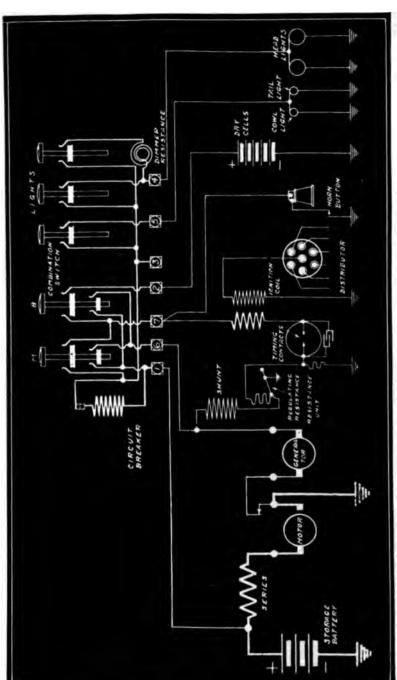


PLATE 186-OAKLAND WIRING DIAGRAM OF 1916 MODEL 49, DELCO SYSTEM

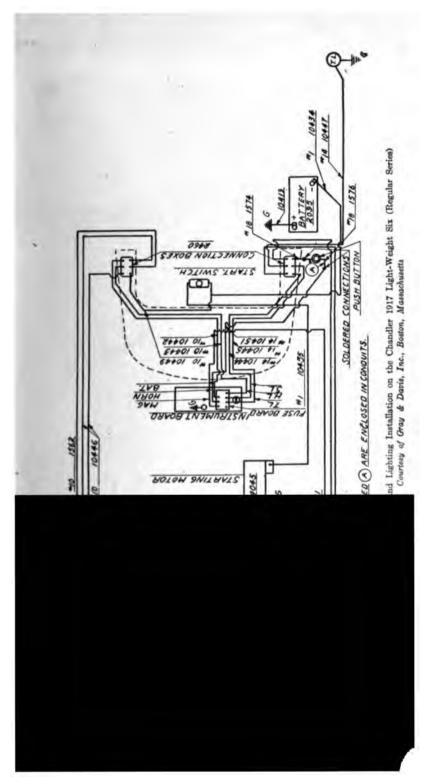

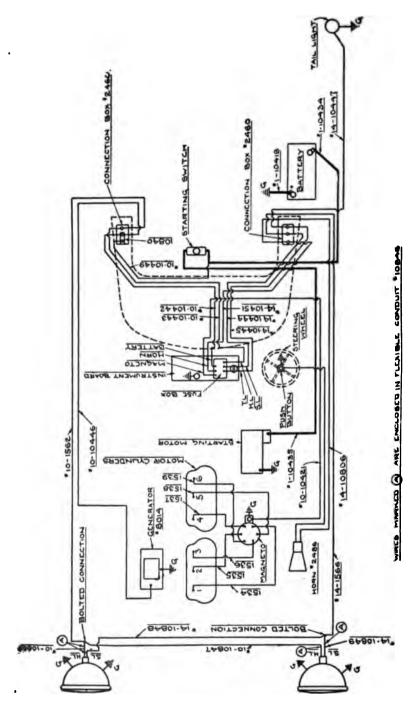

Gray & Davis Starting and Lighting Installation on the Chandler 1917 Light-Weight Siz (for Cars Numbered from 35001 to 60009) Courtesy of Gray & Davis, Inc., Boston, Massachusetts

bearing properly on the commutator, or the battery terminals may not be tight. If the starting motor rotates but does not crank the engine, the over-running clutch may not be running properly or the engaging gears do not mesh. When the starting motor cranks the engine a few turns and stops, the battery is almost discharged. Unless the engine starts after the first few revolutions, do not continue to run

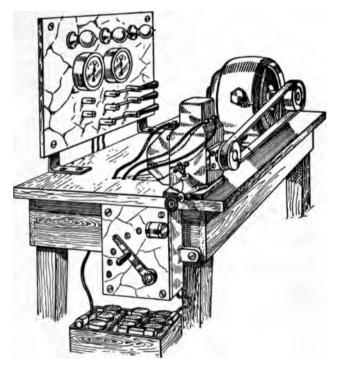


Fig. 288. Diagram of Layout for Testing Gray & Davis Generator Courtesy of Gray & Davis, Boston, Massachusetts

the starting motor, as it will exhaust the battery very quickly. Look for causes of engine trouble—lack of gasoline, ignition circuit open, or the like.

Gray & Davis Service Tests. Garages caring for fifty or more cars find it profitable to install the equipment to carry out the necessary tests of electrical apparatus instead of referring every case that is beyond the ordinary requirements to the manufacturer or to one of its service stations. The makers recommend for testing generators and motors when removed from the car, the following apparatus:

(1) One \(\frac{1}{2}\)-h.p. electric motor with variable speed rheostat (direct current) giving a speed range of 600 to 1800 r.p.m. This is where only one machine is to be tested at a time; for running several from a countershaft, a 1- to 2-h.p. motor is necessary. (2) Three motor pulleys, 2, 3, and 7\frac{1}{2} inches in diameter, respectively, and three generator pulleys, 2\frac{1}{4}, 3, and 5 inches in diameter. (3) Adjustable bases for holding generators. (These can be obtained from Gray & Davis.) (4) Portable voltmeter with a 15-volt scale. The instrument described for general testing will fill this requirement as well. (5) Ammeter with a charge and discharge reading to 25 amperes, i.e., 25—0—25. (6) One tachometer, or revolution counter. (7) Four Ediswan base sockets and three 15-c.p. 7-volt lamps. (8) One single-pole single-throw switch and two single-pole double-throw switches, all of 15-ampere capacity. (9) One 80-ampere-hour 6-volt storage battery. (10) Sufficient No. 10 flexible cable for making the necessary connections.

The above apparatus is more particularly for the generator tests. For making motor tests, the following are necessary:

(1) Ammeter reading to 400 amperes.
 (2) One spring scale reading to 20 pounds.
 (3) One single-pole single-throw switch of 200-ampere capacity.
 (4) Steel clamp and base for motor.
 (5) One 6-inch flanged iron pulley.
 (6) Sufficient No. 1 flexible cable for connections.

Generator Test Chart. In order to enable the tester to check the performance of the generator, the test chart, Table III, has been supplied. The method of mounting the ½-h.p. motor, switches, instruments, rheostat, and storage battery is shown in Fig. 288, while the wiring diagram showing the method of connecting up the various units is illustrated in Fig. 289. Referring to the test chart, Table III, column 1 gives the types of generators manufactured by Gray & Davis. To determine the type number, it is necessary to note only the first three numbers on the name plate. For instance, 2221541 indicates type 222, machine 1541. This applies to all machines of this make turned out since September, 1915.

Column 2 shows the amount of current required to run the generator as a motor, or to "motorize" it. To take this reading, the posts AF and F-1 should be connected together with a copper wire and the wire from the battery connected to the post A. The ampere reading and the speed should be within 10 per cent of the figures given in column 2. If not, remove the regulator and repeat the test, column 3 showing the proper speed. If the armature is shorted it will take excessive current, the ammeter needle will fluctuate, and the speed will be below normal. If the current is excessive but steady and the speed is high, it will show a defect in the fields or the field connections, as indicated in succeeding paragraphs.

## ELECTRICAL EQUIPMENT

## TABLE III

### Test Chart for Gray & Davis Generators

#### Information for Service Stations

1	2	3	4	5	6	7	8	9	10
TYPE OF GENERATOR	RUNNING LIGHT AS A MOTOR AT 6 VOLTS			AMPERES CHARGE TO BATTERY WITH 71 AMP. LAMP LOAD		SHUNT FIELD CURRENT AT 6 VOLTS		OUTPUT OF DYNAMO WITH 71 AMP. LOAD	
	Amp.	Speed (r.p.m.)	10 AMP.	Max.	Min.	Max.	Min.	Max.	Min.
Chandler S	3	320	750	4.5	1	1.32	1.09	11	8.5
Paige S	3	320	750	6	1	1.32	1.09	12	8.5
Chalmers T	3	650	1300	4.5	î	1.30	1.04	11	8.5
Metz T	3	650	1300	4.5	i	1.30	1.04	11	8.5
CONTRACTOR LAND			8 Amp.	1	î	1.20	.96	11	8.5
M.G.9	10	700 }	1575	4.5	-	1.20	.50	- **	0.0
300	10	700	8 Amp.	4.5	1	1.20	,96	11	8.5
		1	1575	1	1	1.20	.96	11	8.5
301	10	700 }	8 Amp. 1575	4.5		1.20	.90	11	0.0
210	3	320	750	6	1	1.32	1.09	12	8.5
211	3	650	1300	4.5	î	1.30	1.04	11	8.5
212	3	650	1300	6	î	1.30	1.04	12	8.5
213	3	650-	1300	6	i	1.30	1.04	12	8.5
214	3	650	1300	6	1	1.30	1.04	12	8.5
216	3	650	1300	6	1	1.30	1.04	12	8.5
					1			12	
217	3	650	1300	6	1	1.30	1.04		8.5
218	3	650	1300	6	1	1.30	1.04	12	8.5
219	3	650	1300	4.5	1	1.30	1.04	11	8.5
220	3	300	600	4.5	1	1.02	.77	11	8.5
222	3	335	700	4.5	1	1.02	.77	11	8.5
223	3	335	700	6	1	1.02	.77	12	8.5
224	3	300	600	6	1	1.02	.77	12	8.5
225	3	300	600	4.5	1	1.02	.77	11	8.5
226	3	335	700	4.5	1	1.02	.77	11	8.5
227	3	650	1300	6	1	1.30	1.04	12	8.5
228	3	650	1300	4.5	1	1.30	1.04	11	8.5
229	3	335	700	4.5	i	1.02	.77	11	8.5
230	3	335	700	6	i	1.02	.77	12	8.5
231	3	335	700	6	i	1.02	77	12	8.5
232	3	300	600	6	1	1.02	.77	12	8.5
233	3	335	700		1	1.02	.77	11	8.5
234	3	650	1300	4.5	1	1.30	1.04	11	8.5
201	0	600	1000	9.0		1.00	1.04	4.4	0.0

Column 4 affords a check on other defects in the machine. To take this reading, connect posts A F and F-1 together in order to give full field current, place machine on test bench, and run with belt. Speed the machine up until the ammeter indicates 10 amperes with the three 15-c.p. lamps in circuit and the battery testing 1.250 or over with the hydrometer. Take a reading of the speed. This should not be higher than that given in column 4. A higher reading will indicate

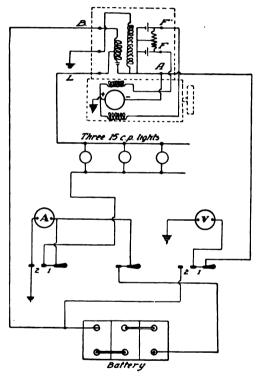


Fig. 289. Wiring Diagram for Gray & Davis Dynamo and Regulator

defective fields, a highresistance armature, pole pieces loose in frame, slight short-circuit in armature, defective brush or brush contact at commutator, or dirty commutator.

The purpose of columns 5 and 6 is to check the action of the regulator. To take this reading, turn on the three 15-c.p. lamps, giving a load of 7½ amperes, and observe the amount of current passing into the battery with the ammeter switch in position 2. The reading should be within the limits shown in columns 5 and 6.

Columns 7 and 8 show the current taken

by the field coils. Connect one side of the battery to the frame of the generator and the other side through the ammeter to terminal F. The reading should not be greater than column 7 or less than column 8. Repeat the test at terminal F-1. A high reading will show a short-circuit, and a low reading will show a poor connection or a high resistance in the field. No reading at all will indicate an open circuit in the field.

TABLE IV

Test Chart for Gray & Davis Starting Motor

1	2	3	4	5	6	7	8	9	
Type OF Motor	RUNNING FREE READING				Minimum Bruan	GEAR REDUCTION	1½ LB. TORQUE READ- ING AT 5% VOLTS		
	Max. Amp.	Speed 3 Volts	Speed 5.5 Volts	Speed 6 Volts	PRESSURE (lb.)	IN GEAR HOUSING	Amperes	Speed (r.p.m.)	
100	35	3500	6600	7000	3½	None	137	2400	
101	35	3500	6600	7000	3½	49–14	137	2400	
102	35	3500	6600	7000	31	47-16	137	2400	
103	35	3500	6600	7000	31	50-13	137	2400	
104	35	3500	6600	7000	3 <del>1</del>	50-13	137	2400	
105	35	3500	6600	7000	31	84-12	137	2400	
106	35	3500	6600	7000	31	51-12	137	2400	
107	35	3500	6600	7000	3 1	51-12	137	2400	
108	35	3500	6600	7000	3 1	50-13	137	2400	
109	35	3500	6600	7000	3 1 3 1 3 1 3 1 3 1 3 1 3 1 3 1 3 1 3 1	50-13	137	2400	
110	35	1900	3800	4100		51-24	98	1980	
113	35	3500	6600	7000	3 <del>1</del>	50-13	137	2400	
115	35	3500	6600	7000	3 <del>1</del>	50-13	137	2400	
116	35	3500	6600	7000	3½	51-12	137	2400	
117	35	3500	6600	7000	3½	51-12	137	2400	
118	35	3500	6600	7000	31/2	50-13	137	2400	
119	35	2200	4500	5000	2 <del>1</del>	None	100	1660	
120	35	2200	4500	5000	2 <del>1</del>	Direct	100	1660	
121	35	2200	4500	5000	2 <del>1</del>	Direct	100	1660	
122	35	1900	3800	4100	3 <del>1</del>	Direct	98	1980	
123	35	3500	6600	7000	$\frac{3\frac{1}{2}}{3\frac{1}{2}}$	49–14	137	2400	
124	35	3500	6600	7000		51–12	137	2400	
125	35	3500	6600	7000	3 ½	50–13	137	2400	
126	35	2200	4500	5000	2 ½	Direct	100	1660	
127	35	2200	4500	5000	21	Direct	100	1660	
128	35	3500	6600	7000	31	51-12	137	2400	
129	35	2200	4500	5000	2 <del>1</del> 2 <del>1</del> 2 1	54–12	100	1660	
130	35	2200	4500	5000		Direct	100	1660	
131	35	2200	4500	5000	21	Direct	100	1660	
132	35	2200	4500	5000	21	Direct	100	1660	
133	35	3500	6600	7000	31	50-13	137	2400	
134	35	3500	6600	7000	3 ½	50-13	137	2400	
135	35	3500	6600	7000	3 ½	49-14	137	2400	
136	35	3500	6600	7000	3½	49-14	137	2400	
137	35	3500	6600	7000	3½	50-13	137	2400	
138	35	2230	4500	5000	2 <del>1</del>	Direct	100	1660	
139	35	2230	4500	5000	21	Direct	100	1660	
140	35	2230	4500	5000	2 <del>1</del>	Direct	100	1660	
141	35	1900	3800	4100	3 <del>1</del>	Direct		1980	
142	35	1900	3800	4100	31/3	51-24	98	1980	
L			<u> </u>		l	L	L	L	

Columns 9 and 10 show the current output for which the generator is set at the factory. To test this, place the ammeter switch in position 1 and with the three 15-c.p. lamps turned on speed the machine above 1750 r.p.m. If the reading does not fall within

the limits given, adjust the regulator in accordance with instructions given below.

Starting-Motor Test Chart. Table IV is provided for reference in cases where the motor trouble is of such a nature that it cannot be located except by a test, i.e., in the windings. Column 1 gives the types of starting motors, which may be identified in manner the same as the generators. The type number covers the motor and the speed reducer.

Column 2 shows the current required to run the motor free. The reading should not vary by more than 25 per cent from the figures given. A high reading will indicate tight bearings, short-circuited armature, or field.

Columns 3, 4, and 5 show the speed when running light with current at 3 volts,  $5\frac{1}{2}$  volts, and 6 volts. The test should be made with either two or three cells of the battery. A low-speed reading with normal current will indicate loose connections, poor brush contact, dirty commutator, or high resistance in armature. A high-speed reading will indicate a short-circuit in the field windings.


Column 6 gives the spring pressure on the brushes. Where the brushes show a tendency to spark, this brush pressure should be checked. This reading is taken with a small spring scale hooked on to the brush screw. Read the number of pounds required to just lift the brush from the commutator. The reading should not be less than the figures given in column 6. Column 7 gives the reduction between the starting-motor shaft and the countershaft which carries the sliding gear.

Columns 8 and 9 are readings showing whether or not the motor is capable of delivering its rated power on normal current consumption and at normal speed. The reading is taken by putting on the shaft a load requiring a turning power of 1½ pounds at a 1-foot radius. To take this reading the flanged pulley, spring scale, and a cord are employed in the manner shown in Fig. 290. The reading on the scale corresponding to 1½ foot-pounds will be 6 pounds. Thus: 1½ foot-pounds times 12 inches equals 18 inch-pounds, which divided by 3 inches (radius of pulley) gives 6 pounds (scale reading).

To take the reading, close the switch and put just enough tension on the cord A to make the scale read 6 pounds and, holding this steady, read volts, amperes, and speed. The speed given in column 3

is taken at 5½ volts, which is what would be obtained with a battery showing 1,250 or over on the hydrometer test. A lower voltage will cause a lower speed reading. In the majority of cases, tests made with the motor running free will show any defects, but in case these tests do not reveal any trouble and the motor still fails to operate satisfactorily, the tests for which the proper figures are given in columns 8 and 9 should be carried out.

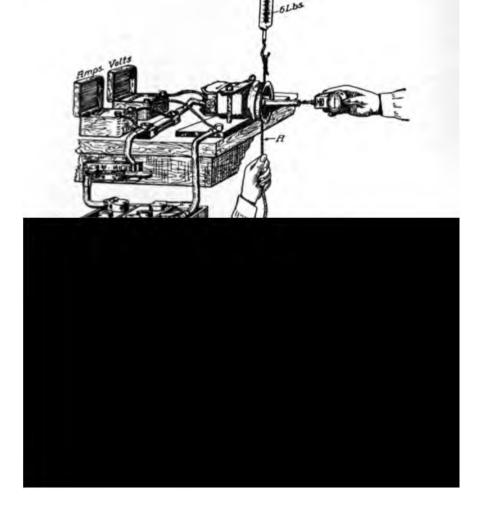To Adjust Cut-Out. The contact points should close to permit the battery to charge at 6 to 6½ volts; they should open the circuit between the battery and the generator on a discharge of ½ to 2



not obtainable after several attempts at adjusting the spring, check the air-gap distances, as given below. Correct these and test again.


To Adjust Regulator. With all connections made and the ammeter switch in position 1, turn on the three 15-c.p. lamps and speed the machine up to above 1750 r.p.m. Open the upper set of points with the aid of a match or by using the finger. Adjust the lower set of points by the ammeter reading so as to bring it within the limits given in columns 9 and 10 of the generator test chart. Repeat the adjustment on the upper set, opening the lower set while the test is being made. Run the machine with both sets of points free and the reading should fall within the limits given in columns 9 and 10.

## HEINZE-SPRINGFIELD SYSTEM Six-Volt; Two-Unit; Single-Wire

The generator is of the multipolar shunt-wound type (four poles) with brushes spaced 90 degrees apart, bringing both on the left side of the commutator to make them more accessible. The negative, or lower, brush of the generator, Fig. 291, is grounded to the brush holder, which, in turn, is grounded on the generator From the positive, or upper, brush a wire runs to the terminal GEN. BR.+ of the regulator and cut-out. Fig. 292. From this terminal, the charging circuit leads to the cut-out contacts and through the latter and the series winding to the terminal BAT+ of the regulator cut-out. As the negative brush of the generator is grounded, the negative terminal of the battery and one side of all the lights are grounded. One end of the generator shunt field is grounded inside to the generator frame. The other end comes out through the hole provided for it in the brush head, runs to the terminal FLD of the regulator cut-out, and thence to the contacts of the current regulator if they are closed, or through a resistance if they are open.

Starting Motor. The starting motor is of the four-pole serieswound type with the brushes at 90 degrees apart, as on the generator. The positive brush is on top of the commutator and carries a terminal to which is connected the starting cable. The lead from the negative brush divides, part of the current passing around two of the four poles to the ground, while the other part passes through the other two poles to the ground connection. On starting motors bearing serial numbers

# ELECTRICAL EQUIPMENT

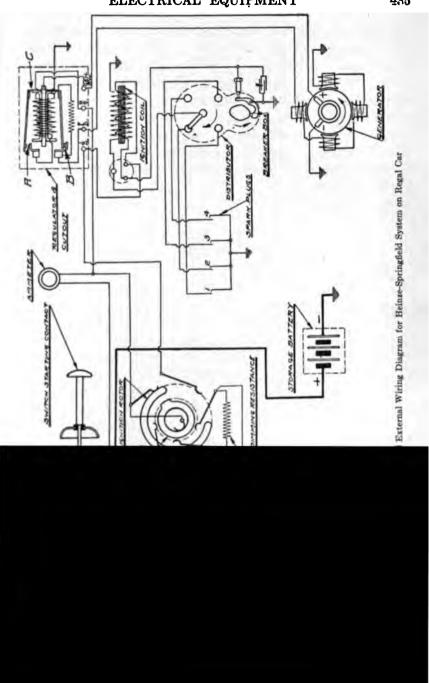

below 5471, the grounded ends of the series fields were soldered to the pole pieces, but this has since been altered by securing the two ends of the series field to a ground lead, which, in turn, is secured to the bottom of the motor brush head by means of a hexagonal nut and lock washer.

While the system is of the two-unit type and the units are independent of each other electrically, they are combined mechanically by making the rear heads of both in one casting. The starting motor is the upper of the two units, the lighting generator being placed directly beneath it. This refers to the set supplied for installation on the Ford.

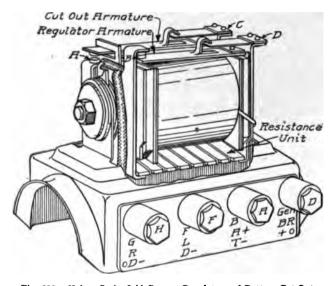


Fig. 292. Heinze-Springfield Current Regulator and Battery Cut-Out

Method of Operation. Drive is by means of a silent chain directly to the sprocket on the generator shaft. In addition to the sprocket in question, the generator shaft carries also a large gear adapted to mesh with the small pinion on the shaft of the Bendix drive mounted on the shaft of the starting motor. When the starting motor rotates, the Bendix pinion automatically engages the gear on the generator shaft and drives to the engine through the silent chain, the engagement being broken as soon as the engine turns over under its own power.

Regulation. Voltage Regulator and Resistance. The current regulator is combined with the battery cut-out and the combined unit

is mounted directly on the starting motor, Fig. 292. The regulator side of the relay consists of two contacts B, which are normally held together by spring tension so that the charging current does not exceed 10 to 12 amperes. When the voltage rises above a certain value owing to the increased speed of the engine, the regulator armature is drawn down, separating the contacts, and the current must then pass through the resistance unit shown beneath the coil. This keeps the charging current down to the value mentioned.

On the battery cut-out side, the relay consists of two contacts A, which are normally held apart by spring tension when the engine is not running or is running too slowly to charge the battery. As soon as it is running fast enough to generate sufficient voltage to overcome that of the storage battery, the regulator armature is drawn down, closing the contacts. This occurs at an engine speed equivalent to about 6 miles per hour, at or above which the battery is always charging. When the speed decreases to below this point, the pull on the armature is not sufficient to hold it down, and the contacts are separated by the spring C.

Starting Switch. The starting switch is a combination dash switch designed to control the starting, lighting, and ignition. In the Ford set, the current for starting and lighting is furnished by the battery, while the current for ignition comes from the Ford magneto. Starting is accomplished by depressing the button in the center of the switch, while the lights are controlled by rotating the switch lever. By rotating the switch lever, the ignition rotor connects the contacts M and C, Fig. 399, in the IGN. ON position and allows current to flow from the magneto through the switch, coil, and plug connections. The lighting rotor of the switch is always supplied with current from the battery through a sliding contact of the wiping type. When at the "Lights Dim" position, the current passes through the dimming resistance, the ignition remaining undisturbed by this change. The switch is designed to lock both the starting contact and the lighting and ignition lever in the IGN. OFF "Lights Dim" position for parking at night, and in the OFF position for the daytime.

Instruments and Protective Devices. Unless specially ordered, an ammeter is not provided with the system designed for the Ford but may be had at an extra cost in the form of a combination panel

carrying the switch, the ammeter, and a dash light. The regulator and the cut-out serve to protect the generator and the battery, respectively.

Wiring Diagram. As installed on the Ford, including an ammeter and dash lamp as just mentioned, the details of the wiring are shown in Fig. 401. The negative side of both the generator and the starting motor are grounded, the connection being split in the latter case and two grounds made. The negative side of the battery and one side of all the lamps and the horn as well are accordingly grounded. As ignition current is supplied by the magneto, the only connection of the ignition system with the lighting and starting system is at the combination switch. The charging current from the generator passes through the regulator (lower set of contacts) and when the engine is running at a speed equivalent to 6 miles an hour or more, the armature of the cut-out is pulled down and the upper set of contacts closes. This sends the charging current through the battery. Should the car be driven at a speed which causes the output of the generator to exceed 10 to 12 amperes, the regulator armsture is attracted and the regulator contacts separate, thus shunting the current through a resistance which immediately serves to decrease the excitation of the generator fields and correspondingly reduces the current output of the latter. When the speed of the engine drops below a point where the voltage generated is insufficient to charge the battery, the cut-out contacts are separated by the spring, as the pull of the magnet is then not strong enough to hold it down. The lights are supplied directly from the battery, as will be noted, the diagram making clear the various positions of the rotating switch to give the different combinations The various connections and their significance will be clear upon comparing this with other and similar wiring diagrams.

Instructions. Failure of the starting motor to operate is usually caused by lack of current in the storage battery, although this fault may be due to several causes, acting either separately or together. Lack of charge in the battery is usually caused by over-frequent use of the starting system with but little driving between, so that the generator is not given an opportunity to charge the battery. Other causes of failure are treated under Starting and Lighting Storage Batteries, in another section.

Starting Motor. The starting motor may not operate because of internal trouble. This may take the form of an open- or short-

circuited armature or field, dirty commutator, insufficient tension on brushes, brushes not bearing on commutator, or grounded brush holders, armature, or field. Of these various causes of failure, the first is liable to be the most rare. For their correction see the various sections on testing for grounds and short-circuits with the aid of the ammeter also on care of commutator and brushes, given in connection with the description of other systems. The attention required is identical in practically every case and, where the brushes and the commutator are concerned, does not vary even in detail on the different systems.

Bendix Drive. Failure of the Bendix drive to operate properly may be due to lubricating the screw shaft, on which no oil or grease is necessary, since it will work better without it. Putting oil on this shaft makes impossible the "running start", which is the great advantage of the Bendix drive; i.e., the starting motor should almost instantly attain a high speed the moment the current is turned on, but the Bendix pinion will not move for a perceptible interval. When the Bendix pinion does move, the starting motor is running so fast that, at the moment the pinion engages suddenly, owing to the action of the spring, the engine is turned over the first compression very much easier than if the motor had to start nuder load.


Generator. Trouble in the generator will usually be manifested by the failure of the machine to generate a terminal voltage. first warning would be the absence of any reading at the ammeter when the generator should be charging, the engine then running at a speed equivalent to 6 miles an hour, or over. If no ammeter is employed, the discharged condition of the battery may be traced either to the generator or to failure to drive the car sufficiently during the daytime and between starts to keep the battery charged. If, upon test with the hydrometer, the battery indicates rapid recuperation after the engine has been running for 15 to 30 minutes, the generator is not at fault. Should the battery specific-gravity test not show any improvement after running 30 minutes, the fault may be either in the generator or in the regulator cut-out. As is the case with the starting motor, defects in the generator may take the form of a dirty commutator, badly worn brushes, insufficient tension of brush springs to keep the brushes bearing on the commutator; the positive brush may be grounded; or there may be open-circuits or grounds, or short-circuits or grounds in the field or armature. In any case, the attention necessary will be the same as that already outlined for similar faults on other systems.

Regulator and Cut-Out. The regulator and cut-out consist of a single electromagnet with a split core on which there are two windings. The primary is in series with main charging circuit and the secondary is shunted across the motor brushes. If the generator is at fault. the battery cut-out naturally will not work, as there will be no voltage to operate it; but there will be times when the generator is working all right and the regulator is at fault, although it may be difficult at first sight to make sure which is the cause of the trouble. To determine this, with the engine running at a speed equivalent to 6 miles an hour or more, press the battery cut-out contacts together with the fingers. If the ammeter then shows a charge reading, and there is no dash ammeter, a weight may be placed on the cut-out armature to keep the contacts together for 30 minutes or so, and if the battery then shows that it is charging, the cut-out and not the generator If, with the cut-out contacts thus held together. there is no sign of charging the battery, the generator is the cause of the trouble.

To adjust the regulator and cut-out, first adjust the regulator side, as the cut-out is dependent upon the regulator adjustment. Before starting the engine, remove the regulator and the cut-out cover, then remove the wire to the terminal "BAT+" and insert an ammeter in the charging circuit at this point, though if there be an ammeter on the dash, it may be used. Start the engine and run it very slowly. See that the regulator contacts are together, Fig. 292. At a speed equivalent to 6 miles an hour or over, the cut-out contacts A should close, and with the contacts at B closed, the ammeter should show a reading of 4 amperes. If contacts A do not close at this point, there may be too much tension on the spring, which may be remedied by bending the spring-holding support upward at C. Should the ammeter reading go above 10 to 12 amperes as the speed increases, this is due to the contacts B of the regulator not opening as they should. The tension of the armature spring of the regulator should then be lessened by bending the spring-holding support slightly upward at D. Note very carefully as the engine speed is decreased that there is enough spring tension on the cut-out armature to open the contacts A when the relay is demagnetized, due to the voltage of the battery exceeding that of the generator.

Trouble in the regulator and cut-out will manifest itself in two ways—insufficient charging current or no charging current reaching the battery and too much current at the higher car speeds. It may be due to several causes, acting either separately or collectively—the armatures springs may be out of adjustment; the current or voltage windings may be short-circuited, open, or grounded; the two sets of contacts may be dirty; or the resistance unit may be open. If the ammeter reading fluctuates though the engine speed remains constant, it is an indication of dirty contacts. They should be trued up with a file. If the regulator has failed, the current may have attained a value of 30 to 40 amperes and caused the contacts to fuse together. Separate and file clean.



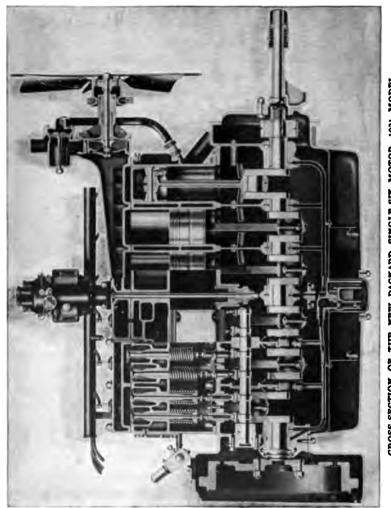

CROSS-SECTION OF THE NEW PACKARD SINGLE-SIX MOTOR, 1921 MODEL, SHOWING THE METHOD OF DRIVE OF THE IGNITION SYSTEM

# ELECTRICAL EQUIPMENT FOR GASOLINE CARS

#### PART VI

# ELECTRIC STARTING AND LIGHTING SYSTEMS—(Continued)

PRACTICAL ANALYSIS OF TYPES—(Continued)

LEECE-NEVILLE SYSTEM

Six-Volt: Two-Unit: Two-Wire

Generator. Standard shunt-wound bipolar type, combined with ignition timer and distributor driven by a worm gear on the armature shaft. The generator is mounted on the left side of the engine and is driven by the pump shaft (Haynes 1913 installation, and subsequent models to date).

It differs from the standard shunt-wound machine in that the shunt field is connected to the regulating third brush. This brush collects current from the commutator and excites the field, so that a strong shunt field is provided at comparatively low speeds. As the speed increases, the voltage supplied to the shunt field decreases, even though the total voltage between the main brushes may have increased. This weakens the field and prevents the output of the generator from increasing with the increased speed. At higher speeds it acts somewhat similarly to a bucking-coil winding in that it further weakens the field and causes the generator output to decrease still more. The closer the third brush is set to the main brush just above, the greater will be the output of the machine; moving it away from the main brush decreases the output.

Regulation. Generators of the 1915 and 1916 models are controlled by armature reaction through a third brush, the field coils receiving their exciting current from the armature through this brush. The position of the latter on the commutator is shown at B, Fig. 293. A slight rotation of this brush relative to the com-

mutator changes the electrical output of the machine. As adjusted at the factory this brush is set to give a maximum output of 15

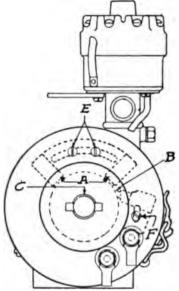


Diagram of Arrangement of Brushes on Leece-Neville 6-Volt Generator

amperes at 7½ volts. (All generators for 6-volt systems are wound to produce an e.m.f. of 71 volts, or thereabout, in order that the voltage of the generator may exceed that of the battery when the latter is fully charged. The e.m.f. of generators for 12-volt and 24-volt systems also exceeds that of their batteries in about the same proportion. Otherwise, the generator would not be able to force current through the battery.)

Starting Motor. The motor is of the bipolar series-wound type driving the engine through a roller chain and an over-running clutch.

Instruments. An indicating type of battery cut-out is employed. thus combining the functions of the

cut-out and ammeter in one device. The details of this device are O is the winding or coil of the electromagnet shown in Fig. 294.

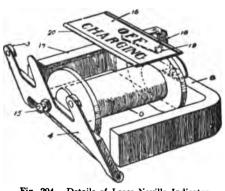



Fig. 294. Details of Leece-Neville Indicator

of which the U-shaped bar 8 forms the magnetic circuit. At 4 is the pivoted armature. normally held in the OFF position as shown by a spring, when no current is passing. and adapted to be drawn against the pole pieces of the magnet when the latter is excited by the charging current. As the two-wire system is employed, the cut-out

breaks both sides of the battery-charging circuit and it is provided with six current-carrying contacts on each of the sides of the circuit Four of these, which carry most of the current, are copper to bronze, while those that take the spark in breaking the circuit are cophite to iron and are actuated by a spring. The indicating target 16 is held in the OFF position by the spring 19 when no current is passing, and this reading appears in the opening of the panel on the cover. When the generator starts and the cut-out closes, the target is moved to bring the word CHARGING in the opening. The same panel also carries the three-way lighting switch controlled by buttons. The central button closes the circuit to the headlights and tail lights in the usual manner, while the upper button throws the headlights in series-parallel connection. As this doubles the resistance, it halves the voltage passing through the lamps, and they, accordingly, burn dimly. The lower button controls the cowl light over the instruments on the dash.

Wiring Diagram. Fig. 295 illustrates the Haynes 1915 installation. While two wires are employed for connecting all the apparatus, it will be noted that the storage battery and the dry-cell battery are grounded by a common ground connection. This is to permit using current from the storage battery for ignition, the corresponding ground to complete the circuit being noted at the ignition coil, close to the distributor. The connections G and B on the panel board are those of the generator and the battery to the indicating battery cut-out, the connections of three lighting switches being shown just to the right. In Fig. 296 is shown the Leece-Neville installation in White cars.

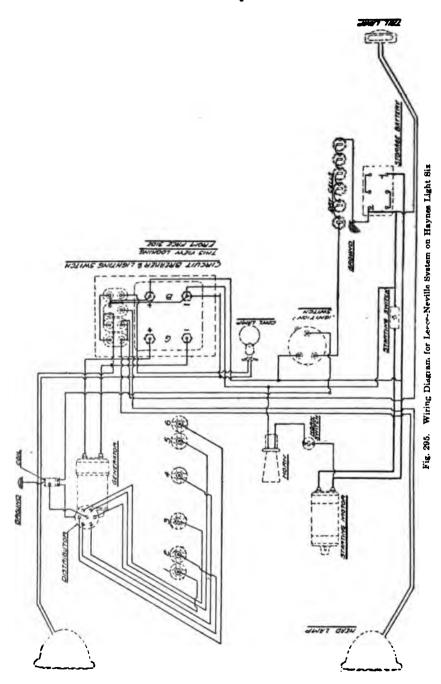Instructions Never run the engine when the generator is dis-



When this fuse blows out, both the generator and the circuit-breaker become inoperative. Any one of the following conditions may cause

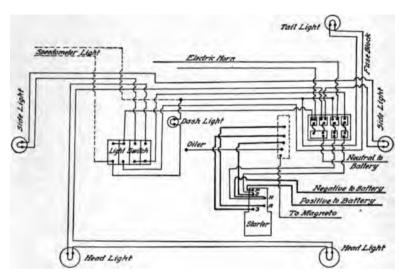


Fig. 296. Wiring Diagram of Leece-Neville System on White Cars

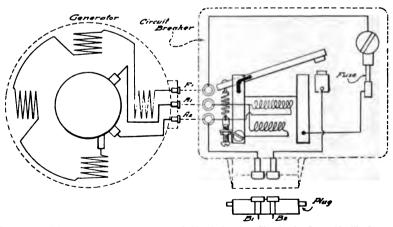


Fig. 297. Wiring Diagram of Generator and Circuit-Breaker Circuits for Leece-Neville System

Courteey of The Leece-Neville Company, Cleveland, Ohio


this fuse to blow out: loose or corroded connections at the battery; an open circuit in the wiring on the battery side of the cut-out; not sufficient water in the battery; output of the generator too high;


allowing the main brush directly above the third brush to stick in its holder; a loose connection at the point  $A_2$ , Fig. 297; improper insulation between the wires  $B_1$  and  $B_2$  in the connector plug, Fig. 297. By an open circuit is meant an actual break at a connector or a terminal, or in the wiring itself, while a loose connection signifies an insecurely fastened terminal or wire, at a junction box, or at any other part of the system. If there is a short-circuit in the field winding of the generator, this also will cause the fuse to blow out.

Testing the Field Winding. While a short-circuit in the field winding of any generator is a rare fault, there are times when the trouble cannot be traced to any other part of the system. To test the Leece-Neville generator for this, connect the negative terminal of the portable testing ammeter to  $F_1$ , Fig. 297, while the positive terminal of the motor must be connected to the positive terminal of a 6-volt storage battery; the negative terminal of the battery is to be connected to the third brush when drawn from its holder. If the indication of the ammeter is above 4 amperes, there is a short-circuit in the field windings. In such a case, the generator should be returned to the manufacturers for repairs.

With the engine running, the working of the generatof should be inspected from time to time. In case there is excessive sparking or "arcing" between the brushes and the commutator, examine the connections at  $F_1$  and  $A_1$  and see that the screws are perfectly tight, as these screws sometimes work loose and are responsible for this arcing which is destructive to the commutator. The loosening of the connections at  $F_1$  and  $A_1$  will have no effect on the fuse; but if the connection at A<sub>2</sub> loosens, the fuse will burn out. When inspecting the operation of the generator, see that the brushes are making good even contact with the commutator, and wipe away all particles of dust and grit from around the brushes and their holders. With the engine stopped, see that the brushes move freely in their holders. should always be done where a car has been laid up for some time (before starting the engine) as the brushes, through disuse, will have a tendency to stick.

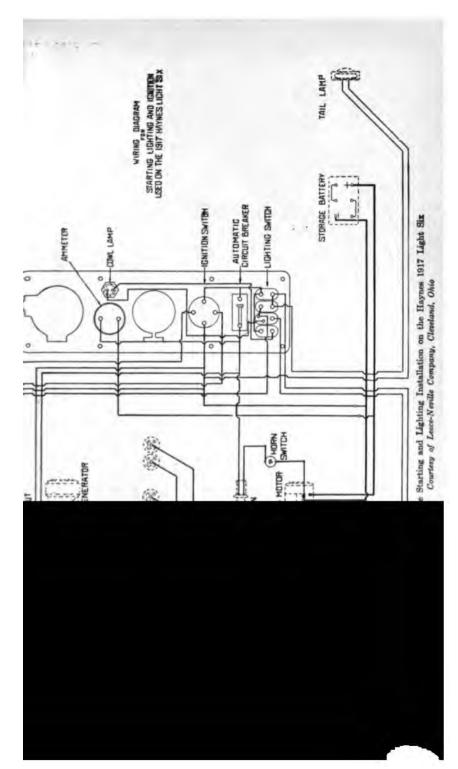The fuse in the circuit-breaker has no effect whatever on the output of the generator, so that a larger fuse must not be inserted in case the generator is not delivering its rated output or more. The makers supply a 5-ampere fuse for this purpose, and if a fuse of



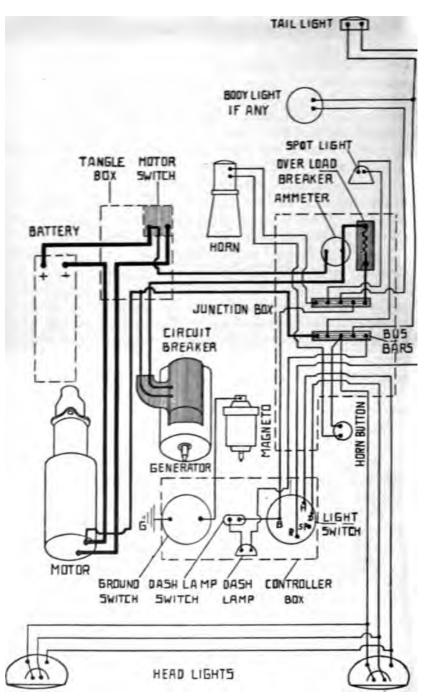

Lecce-Neville Starting and Lighting System on White Cars, Model G-M Courtesy of Lecce-Nextle Company, Cleveland, Ohio

heavier capacity is employed, it will cause both the circuit-breaker and the generator to burn out. This will be the case also where a "jumper" is resorted to, i.e., a piece of wire or other metal bridging the fuse clips so that the fuse is cut out of the circuit. It must be borne in mind, however, that these fuses are more or less fragile and are likely to become damaged by careless handling. A fuse whose connections have been loosened up is likely to blow out on that account, so before inserting a fuse in the clips of the circuit, it should be examined to see that the ferrules on each end of the cartridge are perfectly tight. Where a good fuse has been inserted and it blows out, the cause should be ascertained before inserting another fuse.

Regulating Brush. In case the generator output falls off as shown by its inability to keep the battery properly charged, the battery itself and all connections being in good condition, and a proper amount of day running being done to provide the necessary charging current, the trouble may be in the regulating brush of the generator. Test by inserting an ammeter, such as the Weston portable or any other good instrument with a scale reading to 30 amperes, in the line between the generator and the battery. Run the engine at a speed corresponding to 20 miles per hour, at which rate the ammeter should record a current of approximately 15 amperes. If the ammeter needle butts against the controlling pin at the left end of the scale instead of showing a reading, it indicates that the polarity is wrong, and the connections should be reversed.

from the third brush until there is no danger of their touching. After securing the desired adjustment, fasten the third brush in place again, stop the engine, and then reconnect the generator to the battery. Do not cut the ammeter out of the circuit while the generator is running.

To Adjust Third Brush. Before making any adjustment of the third brush when it is suspected that any trouble with the current supply is due to the generator, the output of the generator should be tested. On a car equipped with lamps totaling 250 candle power or more (this refers to White busses), the generator should produce 20 amperes. Run the engine at a speed sufficient to drive the car 15 o 16 miles per hour on direct drive and note the reading of the dash ammeter. In case the car has seen considerable service, it may be well to check the dash ammeter with the more accurate portable ammeter described in connection with other tests in previous and subsequent sections. Where the car lighting system totals 250 c.p. or over, and the ammeter reading shows more than four amperes above or below 20, the generator should be adjusted to give its rated capacity of 20 amperes—as every 15 c.p. less than 250 c.p. used on the car, lower the output of the generator by one ampere. By making the adjustments in this manner, the storage battery will be amply protected.

Before making any generator adjustments, test the storage battery with the hydrometer. Do not add any distilled water just previous to making this test unless the level of electrolyte is right down to the plates so that sufficient liquid cannot be drawn into the hydrometer; in this case, add water and charge the battery for at least one hour before making the hydrometer test. If the specific gravity of the electrolyte is 1.250 or over, and the generator is found to be delivering less than the rated lamp load, no adjustment of the generator should be made.

To increase the output of the generator, rotate the third brush in the direction of rotation of the armature; to decrease the output, move the brush against the direction of rotation. Adjustments should be made with the engine standing. Loosen the screw at the rear of the commutator housing shown at the point F, Fig. 293. This releases the third brush holder, and the brush may then be moved in the direction desired. It should be moved only a short distance,

and the generator then should be tested until the desired output is secured. In case the third brush should come in contact with the main brush above in the course of adjustment, it will be necessary to move the main brushes. To do this, loosen the two set screws E, Fig. 293, and move the main brush holder far enough away from the third brush so that there is no possibility of contact between them. When the desired location is found, sand-in the third brush to the commutator and also clean the commutator with a piece of worn sand-paper as described in the section on Sanding-In the Brushes (Delco instructions); if it has been necessary to move the main brushes, they should be sanded-in also. The brush holder screws should be well tightened after making any adjustments to prevent any possibility of the vibration and jolting loosening them up and throwing the generator out of adjustment again.

Brush Replacements. Never replace any of the brushes on either the generator or starting motor with any but those supplied by the manufacturer of the system for this purpose. Motors and generators adapted for use on electric-lighting circuits are usually fitted with plain carbon brushes. These are not suitable for use on automobile generators or starting motors owing to their resistance being much higher. Due to the low voltage of electric apparatus on the automobile, special brushes of carbon combined with soft copper are usually employed. Brushes also differ greatly in hardness, and a harder brush than that for which the commutator is designed will be liable to score it badly besides producing a great deal of carbon dust, which is dangerous to the windings. This, of course, applies to all makes of apparatus and not merely to that under consideration.

Generator or Motor Failure. For failure of the generator or of the starting motor, see instructions under Auto-Lite, Delco, and Gray & Davis, bearing in mind, however, that the system under consideration is of the two-wire type, so that in using the test lamp to locate short-circuits a connection to the frame or ground is not always necessary. The short-circuit may be between two adjacent wires of different circuits. Given properly installed wires and cables, there is less likelihood of short-circuits in the wiring of a two-wire system. Defective lamps will not infrequently prove to be the cause, as, in burning out, a lamp often becomes short-circuited.

#### **NORTH EAST SYSTEM\***

Twelve-Volt, Sixteen-Volt, or Twenty-Four-Volt; Single-Unit; Single-Wire or Two-Wire, According to the Installation

Dynamotor. The dynamotor is of the four-pole type, with both windings connected to the same commutator. It is designed for installation either with silent-chain drive—as on the Dodge, Fig. 298, in which case the drive is direct either as a generator or as a motor—or with a special reducing gear and clutch for driving from the pump or magneto shaft of the engine. In the latter type, the starting switch is mounted on the gear housing, which is integral with

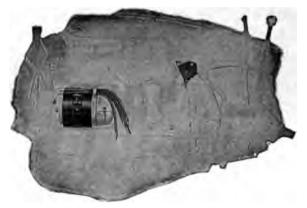


Fig. 298. North East Dynamotor with Silent-Chain Drive. Starting Switch Shown at Right Courtesy of North East Electric Company, Rochester, New York

the bedplate of the dynamotor. In this case the drive as a generator is  $1\frac{1}{2}$  times engine speed, while as a starting motor the reduction through the gear is approximately 40:1.

Regulation. The regulation is by means of a differential winding or bucking coil, in connection with an external resistance automatically cut into the shunt-field circuit by a relay in series with the battery cut-out. See "limiting relay", Fig. 299. The "master relay" is the battery cut-out, and the condenser is to reduce sparking at the contacts of these relays.

Protective Devices. There is a fuse in the field circuit of the generator, but fuses are not employed on the lighting circuits.

<sup>\*</sup>The voltage of any system may be determined by counting the number of cells in the storage battery, and multiplying by 2 in the case of a lead battery, or multiplying by 1½ where an Edison battery is used.

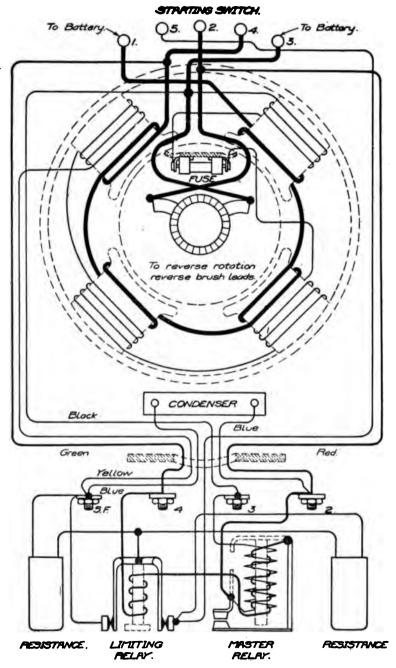


Fig. 299. Diagrammatic Section of North East Dynamotor, Showing Regulator (Limiting Relay) and C'"-Out (Master Relay)

### Wiring Diagrams. A graphic diagram of the North East

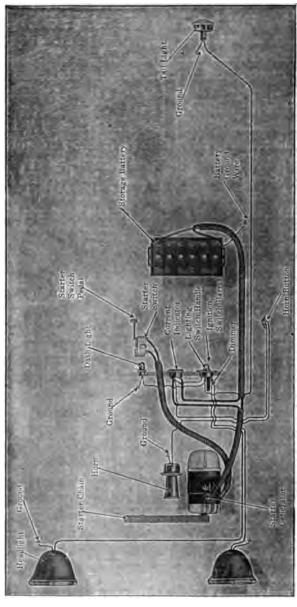


Fig. 300. Diagrammatic Layout of North East Installation on Dodge Cars Courtesy of North East Electric Company, Rochaster, New York

installation on the Dodge is shown in Fig. 300. This is a 6-cell or 12-volt system single-wire type. The sprocket on the forward end

Fig. 301. Diagrammatic Layout of North East 12-Volt Installation on Krit 1915 Automobiles (14-Volt Lamps)

of the machine drives from a similar but much larger sprocket on the forward end of the crankshaft of the engine through a silent chain. The wiring diagram of the Krit 1915, Fig. 301, will be

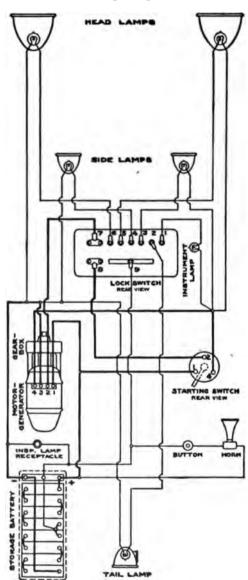


Fig. 302 Wiring Diagram for 16-Volt North East System Using 8½—9-Volt Lamps

recognized as being the same as the Dodge, except for the use of two wires throughout. Fig. 302 shows the wiring diagram of an 8-cell or 16-volt system, but the battery is divided for the lighting circuits so that 81-9-volt lamps are used, whereas 14-volt bulbs are necessary on the Dodge installation as the entire battery is used in series for lighting. The wiring of the 12-cell or 24-volt system is shown in Fig. 303. In this case the battery is divided for lighting so that 7-volt lamps are employed. Such a system is usually designated as 24-6-volt, while the previous one would be a 16-6-volt. The North East installation for Ford cars is 24-14-volt. With the exception of the Dodge. the two-wire system is employed on the installations mentioned.

Instructions. The indicator shows when the battery is charging or discharging and accordingly should indicate OFF when

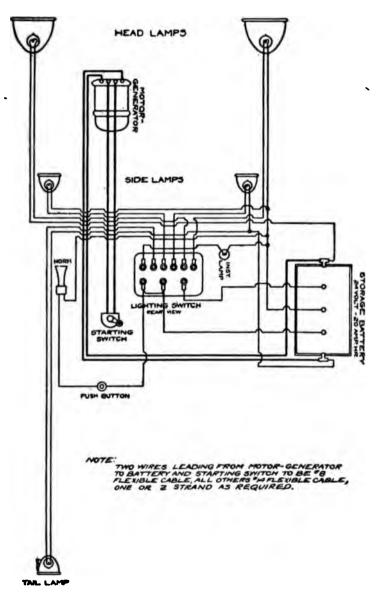



Fig. 303. Wiring Diagram for 24-Volt North East System Using 7-Volt Lamps

the engine is idle and no lamps are lighted. A discharge reading under such conditions would indicate the presence of a ground, short-circuit, or failure of the battery cut-out to release. Should the generator fail to charge the battery, note whether the field fuse has been blown by short-circuiting the fuse clips with the pliers or a piece of wire while the engine is running at a moderate speed. Look for cause of failure before replacing the fuse. If the fuse has not blown, see whether battery cut-out is operating; look for loose connections at generator, cut-out, and battery. If the battery is properly charged, loose connections are also most likely to be the cause of failure of the starting motor; or, any of the instructions covering brushes, commutator, etc., as given previously, may apply.


Battery Cut-Out and Regulator (Relays). In every case where it is necessary to make repairs on starter-generators equipped with the earlier type cut-out and regulator (relays), 1283 (12-volt), 1860 (16-volt), 2501 (24-volt), 1900 (16-volt), and 2503 (12 and 24-volt), it is advisable to replace the cut-out entirely, installing a later and improved type, 1196 (12-volt), or 1197 (24-volt and 16-volt). In order to adapt the starter-generator to the 1196 and 1197 cut-out, or relay units, it is necessary to cut out the bosses on the commutator end bearing in which the studs holding the original relay were screwed. This will provide the clearance required to prevent grounding of the nuts which secure the units to their baseboard. As a further precaution against grounding, it will be necessary to cut away that portion of the gasket retainer which would be liable to come into contact with the armature of the master relay.

Fasten down the baseboard which carries the relays by screwing the resistance unit studs into the holes which were used for the former resistance studs. Before making connections on the relay, draw tight all leads which come from inside the starter-generator so as to take up whatever slack they have; then tie them together with string to prevent their slipping back. No loose wire must be left inside the starter-generator, because of its tendency to be drawn in between the armature and the pole pieces. The connections on the four-terminal type starter-generator are made as follows:

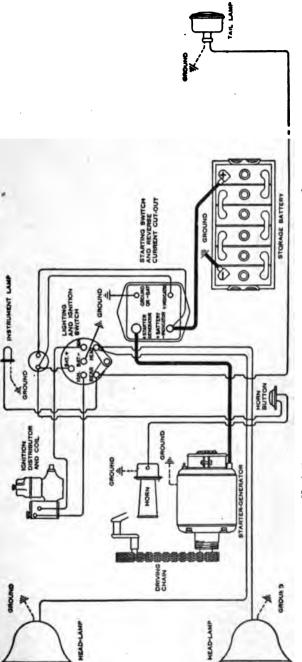Looking at the starter-generator from the driving sprocket end, the main terminals 1, 2, 4, and 3 of the starter-generator are considered as being numbered in anti-clockwise rotation, Fig. 304. Viewing



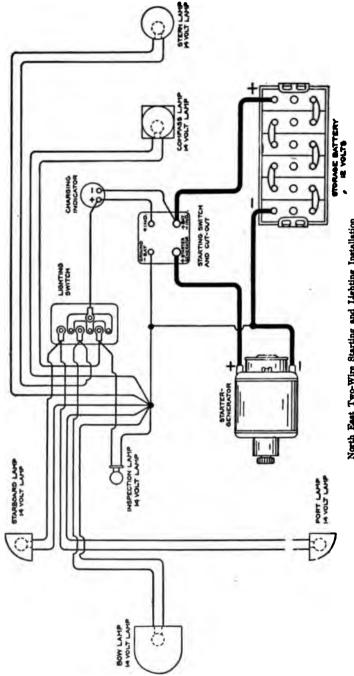North East Single-Wire Starting and Lighting System on Dodge 1917 Cars Courtesy of North East Electric Company, Rochaster, New York




North East Two-Wire Starting and Lighting Installation Courtesy of Nort's East Electric Company, Rockester, New York

the relay unit as mounted on the starter-generator with the larger, or master relay, at the left, the four binding posts a, b, c, and d are designated from left to right in the same illustration. To relay binding post a, connect lead (red) coming from starter-generator terminal

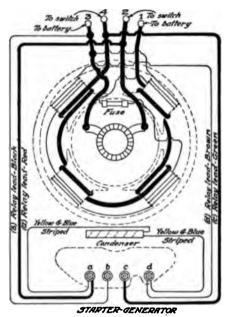
2. To relay binding post b, connect lead (black) coming direct from starter-generator terminal 3. To relay binding post c, connect lead (green) from starter-generator terminal 4. To relay binding post d, connect lead (yellow) from starter-generator shuntfield coils. It is always advisable to check the identity of the leads by inspection and test.

In order to make a positive distinction between the d lead and the b lead, both of which are in electrical connection with the starter-generator terminal 3, the following test should be made: Using the test-lamp outfit, send current





mounted on the starter-generator with the master relay at the left, the four binding posts a, b, c, and d are designated from left to right as shown in the illustration. Proceed with the instructions as given for the four-terminal type starter-generator as given. The new type relays 1196 and 1197 are regularly furnished with local connec-

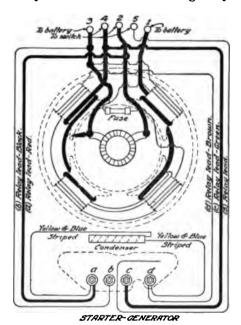


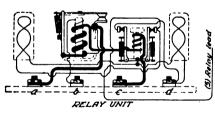


Fig. 305. Internal Wiring Diagram for Model "B" Starter-Generator

tions, as shown in Fig. 304, but it will be necessary to make the following alterations when applied to the five-terminal type startergenerator, so that the relay connections will conform to the diagram in Fig. Remove the jumper lead that connects the frame of the master relay to the rear contact terminal on the limiting relay; remove from relay binding post a the left-hand resistance-unit lead. Lengthen this lead by splicing a piece of the same kind of wire to it, and solder it to the limiting relay contact terminal, from which the jumper has been removed. To this terminal must also be soldered the lead coming from starter-generator terminal 5. (In some starter-generators this lead includes the field fuse.)

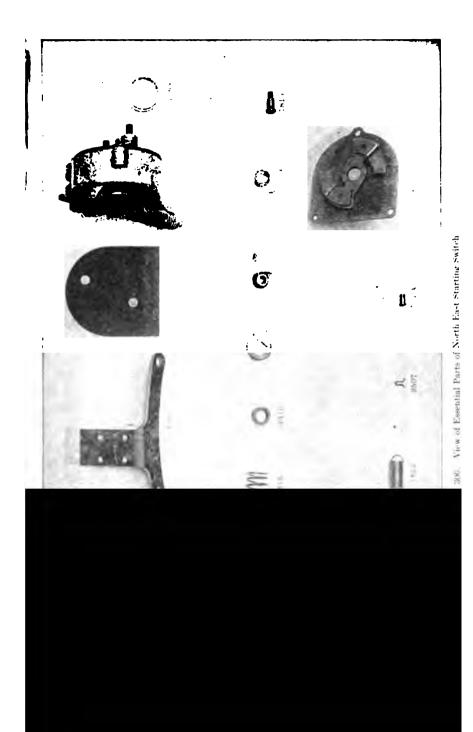The condenser in the early models is mounted between the field coils. One condenser lead must either be connected to the relay binding post a as shown in either Fig. 304 or Fig. 305 or be spliced to the wire leading to it. The other condenser lead must either be connected to the relay binding post d or spliced to the shunt-field wire leading to it.



Starting Switch. When its operation indicates that the contactor blades have worn, the starting switch should be dismounted, and, if necessary, new blades should be inserted. To disassemble the switch, proceed as follows: (1) Remove the spring 2265, Fig. 306, on the switch case 2365; (2) remove the cotter pin from the collar 2416; (3) withdraw the shaft and lever 2401, together with the spring 1818; (4) remove the three screws which hold the cover 2404 in place,

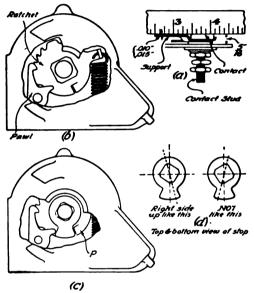


Fig. 307. Assembly of Starting Switch Courtesy of North East Electric Company, Rochester, New York

and remove the cover; (5) remove the stop 2457; and (6) disconnect the spring 1813 from the arm of the ratchet and remove the contactor member 2344.

If, upon inspection, the contacts are found to be in such a condition that their renewal is necessary, make a replacement of the entire cover member 2404 and the entire contactor 2344. Before placing these new parts in the switch, the following points should receive careful attention:

the front edges of the contact blocks should be slightly rounded so as to eliminate the possibility of these edges catching on each other when the switch is being operated. The supports on the cover must be adjusted so that they lie parallel with the faces of the contact blocks.

The upper surfaces of the supports must be .010 to .015 inch lower than the contact surface of the block. Care should be taken that the upper surface of the contact blocks are  $\frac{5}{16}$  inch above the inner surface of the cover. A small steel straightedge laid upon the face of the contact block and extended over the supports, as shown in Fig. 307 (a), will serve as a means of checking these dimensions.

Before placing in service, the contact surfaces must be carefully cleaned and lubricated with a very small quantity of vaseline. reassemble the switch: (1) Connect the spring 1813, Fig. 306, to the arm of the ratchet; (2) place the contactor member 2344 in the switch case in such a position that the ratchet will lie against the pawl 1830; and (3) hold the switch case in the left hand, lever side up, and insert the right forefinger through the hole in the switch case and introduce the pawl into the first notch of the ratchet, Fig. 307 (b); (4) hold these parts carefully in position and replace the cover 2404. Fig. 306, fastening it to the switch case by means of the three screws: (5) insert the stop through the hole in the switch case and replace it upon the ratchet plate in such a position that the elongated portion of the stop will lie between the raised projection which is found on the ratchet plate and the end of the short lever on the pawl as shown in Fig. 307 (c). It is very important that the stop be placed in the switch right side up, Fig. 307 (d) illustrating the proper method of doing this. (6) Place the spring on the shaft and replace the shaft in the switch, taking care while entering the shaft not to disturb the arrangement of any of the switch parts; (7) replace the collar and the cotter pin; and (8) connect the spring 2265 with the lug on the switch case. A drop of light oil should be applied to the bearing point at each end of the switch shaft 2401.

Switch Tests. To determine whether the switch has been assembled correctly, pull the lever through the full length of its stroke

## ELECTRICAL EQUIPMENT

TABLE V
Characteristics of North East Starting and Lighting Apparatus

		MI	CHANIC	MECHANICAL CHARACTERISTICS	RACTER	ISTICS		-			APPROX	APPROXIMATE ELECTRICAL CHARACTERISTICS	AL CRA	RACTERI	STICS		
Shown		1			Armi		9			Torque		MASTER RELAY	ELAY		Lim.R1	Resis. Unit	Unit
on Plate	Model	Drg.	Volts	Rota- tion	Dia.	Style	Termi- nals		Rate Amp.	FtLb.	10	Cuts in Pos. Amp.	Cuts Out Neg.A	Gap (	Gap (in.)	No. of Spools	Total Resis.
118, 127	Y	1000	16	C.C.	33	Shaft	4 Post,	7	-	12 46	3 to 4	i @ 1000 r.p.m.	0	.030	.025	1	146
18, 127	A	2000	16	Ö	31	Shaft	4 Post	7	-	12 46	3 to 4	@ 1000 r.p.m.	0	.030	.025	1	146
	A-4	1070	16	c'	31	Oldham	5 Lead	d 7	-	12 46	3 to 4	@ 1000 r.p.m.	0	.030	.025	1	148
	V-4	1080	16	C.C.	31	Oldham	5 Lead	d 7	1	2 46	3 to 4	(@ 1000 r.p.m.	0	.030	.025	1	146
123	B-1	1102	16	Ü	33	Oldham	5 Post	9	2	22 90	3 to 4	6 1000 r.p.m.	0	.030	.025	1	361
123	B-1	1103	16	C.C.	33	Oldham	5 Post	9	21	2 90	3 to 4	@ 1000 r.p.m.	0	.630	.025	1	396
123	B-2	1106	24	Ö	23	Oldham	5 Post	9	63		3 to 4	@ 1250 r.p.m.	ī	.030	.025	59	286
123	B-2	1109	24	C.C.	31	Oldham	5 Post	t 6	50	6 150	3 to 4	@ 1250 r.p.m.	7	.030	.025	24	286
126	F-1	1210	24	c.	3,00	Sprocket	4 Post	1 4	3	6 150	3 to 4	(@ 1250 r.p.m.	1	.030	.025	2	286
125	5	1220	24	Ö	33	Oldham	4 Post	4	3	36 150	3 to 4	6 1250 r.p.m.	-	.030	.025	23	286
125	D-1	1221	24	C.C.	34	Oldham	4 Post	4	2	150	_	@ 1250 r.p.m.	7	.030	.025	53	288
124	D-6	1223	24	Ö	3.5	Flange	4 Post		.3		3 to 4	@ 1250 r.p.m.	7	.030	,025	63	286
124	D-6	1224	24	C.C.	53	Flange	4 Post	2 5	60	36 150	3 to 4	@ 1250 r.p.m.	-	.030	.025	2	288
123	B-3	1246	12	Ö	+	Oldbam	5 Post	1 7	. 8	35 210	3 to 4	@ 1000 r.p.m.	0	.030	.025	69	361
123	B-3	1247	12	C.C.	4	Oldham	5 Post.	7			3 to 4	@ 1000 r.p.m.	0	.030	.025	2	361
123		1248	12	Ö	33	Oldham	5 Post	7		32 200	_	@ 1000 r.p.m.	0	.030	.025	63	196
123		1249	12	C.C.	3.5	Oldham	5 Post.	1 7		2000	3 to 4	( @ 1000 r.p.m.	0	.030	.025	69	361
125	D-2	1250	12	Ö	4	Oldham	4 Post.	1 7		5 210	3 to 4	@ 1000 r.p.m.	0	.030	.025	64	360
125	D-2	1251	12	C.C.	4	Oldham	4 Post.	7	.00		3 to 4	6 (0 1000 r.p.m.	0	.030	.026	63	361
126, 126-A	F-2	1252	12	Ö.	4	Sprocket	4 Post.		.00	5 210	_	6 @ 1000 r.p.m.	0	.030	.025	61	361
100	-			0			4 Lead.	d	· ·		_					ß	
126-A	7-4	1233	12	3	+	Sprocket	4 Post.	T		35 210	3 to 4	(@ 1000 r.p.m.	0	.030	.025	64	361
124	D-7	1254	12	Ö	*	Flange	4 Post.	7	3	5 210	3 to 4	@ 1000 r.p.m.	0	.030	.025	64	196
124	D-7	1255	12	C.C.	*	Flango	4 Post	7	.00	35 210	_		0	.030	.025	63	1960
125	D-2	1256	12	0	34	Oldham	4 Post	-	22		-	m 1000 r.m.m.	0	030	200	•	

# ELECTRICAL EQUIPMENT

TABLE V—(Continued)
Characteristics of North East Starting and Lighting Apparatus

	Resis. Unit	No. of Total Spools Resis.	2 190	-	_	3 19 &																				mitto be
HETICE	-	Gap (ii.)	.025	.025	.025		_			<del></del>	<del></del>	<del></del>		<del></del>						<del></del>						
RACTER		Gap (in.)	.030	8	.030	-		 89.		8 8 8		080.	080 080 080 080 080			080 080 080 080 080 080	080. 080. 080.	080 080 080 080 080 080 080	080 080 080 080 080 080 080 080 080 080	080. 080. 080. 080. 080. 080. 080.	080. 080. 080. 080. 080. 080. 080.	080	889. 989. 989. 989. 989. 989. 989. 989.	85.00 85	080. 080. 080. 080. 080. 080. 080. 080.	889. 899. 899. 899. 899. 899. 899. 899. 899. 899. 899. 899. 899. 899. 899. 899. 899. 899. 899. 899.
L CHA	ELAY	Cuts Out Neg.A.	0	•	•	-		•	• •	007	100	1 100	7 700	7 7 700	7 7 700	7 7 700	77 77 700	007 7 7 777	007 7 7777	007 7 77777	••1 1 177777	••1 1 1777777 	•• 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7	•• 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7	•• 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7	•• 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7
APPROXIMATE ELECTRICAL CHARACTERISTICS	MASTER RELAY	Cute in Pos. Amp.	3 to 4 @ 1000 r.p.m.	3 to 4 @ 1000 г.р.т.	3 to 4 @ 1000 r.p.m.																			-	refer refer	refer refer
<	rgue	ED.	200	3	200			210	210	200 200 200 200 200	210 210 200	210 200 200	210 200 200	200 200 200 200 200	200 200 200 200	200 200 200 200 200 200	200 200 200 200 200 200 200 200 200 200	200 200 200 200 200 200 200 200 200 200	8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8	210 210 200 200 200 200 200 240	210 210 200 200 200 200 200 200 200 200	200 200 200 200 200 200 200 200 200 200	200 200 200 200 200 200 200 200 200 200	2 2 2 2 2 2 2 2 2 2 2 2 2 2 2 2 2 2 2	210 210 210 200 200 200 200 200 200 200	2210 2210 2210 2210 2210 2210 2210 2210
	Torque FtLb.		32	32	32			35	35	35 55	35.55	35 55 55	35 55 55 55	35 55 55 55 55	35 55 55 55	55 55 55 55 55 55 55 55	55 55 55 55 55 55 55 55 55 55 55 55 55	8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8		88888888884	8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8	8 8 8 8 8 8 8 8 8 8 8 8 8 8 8	88 88 88 88 88 88 88 88 88 88 88 88 88	8888 88 88 88 88 88 88 88 88 88 88 88 8	888888888888888888888888888888888888888	8888 2 2 22 22 24 24 28 8 22
	S. P. S.	Charge Rate Amp.		2	7			6.5	6.5	6.5	6.5	6.5	6.5	6.5	6.5	3.1-0 4 9 9	8 4 9 9 9	80 10 10 10 10 10 10 10 10 10 10 10 10 10	80 4 8 8 8 8 8	80 4 9 9 9 9 9 7	0 0 0 0 0	8 8 8 8 8 8 8 8 8 8		8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8	8 2 2 4 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8	
	Style Termi- nals		4 Post	4 Post	4 Lead	4 Post	4 Post	4 Lead	4 Lead 4 Lead 4 Lead	4 Lead 4 Lead 4 Lead 4 Lead	4 Post 4 Lead 4 Lead 4 Post 4 Lead	4 Post 4 Lead 4 Lead 4 Lead 4 Post 4 Post	4 Post 4 Lead 4 Lead 4 Lead 4 Post 4 Post 4 Lead	4 Post 4 Lead 4 Lead 4 Lead 4 Post 4 Lead 4 Post 4 Post	4 Post 4 Lead 4 Lead 4 Lead 4 Post 4 Lead 4 Post 4 Lead	# Post # Lead # Lead # Lead # Post # Post # Post # Post	4 Fost 4 Lead 4 Lead 4 Lead 4 Fost 4 Lead 4 Lead 4 Lead 4 Lead 4 Lead 4 Lead 5 Fost	4 Fost 4 Lead 4 Lead 4 Lead 4 Lead 4 Fost 4 Fost 6 Fost 6 Fost 7 Fost	4 Fost 4 Lead 4 Lead 4 Lead 4 Lead 4 Fost 4 Lead 4 Fost 4 Lead 4 Fost	4 Fost 4 Lead 4 Lead 4 Lead 4 Lead 4 Fost 4 Fost 6 Fost 6 Fost 7 Fost	4 Fost 4 Lead 4 Lead 4 Lead 4 Fost 4 Fost 4 Lead 5 Fost 5 Fost 5 Fost 6 Fost 6 Fost 6 Fost 6 Fost 7 Fost 7 Fost 7 Fost 7 Fost 8	4 Fost 4 Lead 4 Lead 4 Lead 4 Lead 4 Fost 6 Fost 6 Fost 7 Fost	4 Fost 4 Lead 4 Lead 4 Lead 4 Lead 4 Fost 4 Fost 6 Fost 6 Fost 7 Fost	4 Fost 4 Lead 4 Lead 4 Lead 4 Lead 4 Fost 4 Fost 6 Fost 7	4 Fost 4 Lead 4 Lead 4 Lead 4 Fost 4 Fost 4 Fost 5 Fost 5 Fost 6 Fost 6 Fost 6 Fost 7 Fost 7 Fost 7 Fost 7 Fost 7 Fost 8	4 Fost 4 Lead 4 Lead 4 Lead 4 Fost 5 Fost 5 Fost 6 Fost 4 Lead 6 Fost 7 Fost 7 Fost 7 Fost 7 Fost 7 Fost 8 Fost 8 Fost 7 Fost 8
IBTICS		Style Coupling	Oldham	Sprocket	Sprocket			Sprocket	Sprocket	Sprocket	Sprocket Sprocket	Sprocket Sprocket Sprocket	SprocketSprocketSprocket	Sprocket Sprocket Sprocket Sprocket	Sprocket Sprocket Sprocket Sprocket Sprocket	Sprocket Sprocket Sprocket Sprocket	Sprocket Sprocket Sprocket Sprocket Oldham	Sprocket Sprocket Sprocket Sprocket Oldham	Sprocket. Sprocket. Sprocket. Sprocket. Oldham. Oldham.	Sprocket Sprocket Sprocket Sprocket Chan Sprocket Sprocket Sprocket Sprocket Oldham Oldham Oldham Oldham Oldham	Sprocket Sprocket Sprocket Sprocket Oldham Oldham Oldham Oldham Oldham Oldham	Sprocket Sprocket Sprocket Sprocket Sprocket Oldham Oldham Oldham Oldham Sprocket	Sprocket Sprocket Sprocket Sprocket Sprocket Oldham Oldham Oldham Oldham Sprocket Sprocket	Sprocket Sprocket Sprocket Sprocket Coldham Oldham Oldham Oldham Oldham Oldham Sprocket Sprocket Sprocket Sprocket	Sprocket Sprocket Sprocket Sprocket Oldham Oldham Oldham Oldham Oldham Oldham Sprocket Sprocket Sprocket	Sprocket Sprocket Sprocket Sprocket Sprocket Oldham Oldham Oldham Sprocket Sprocket Sprocket Sprocket Sprocket Sprocket Sprocket
MECHANICAL CHARACTERISTICS		Dia. (in.)	3	3	3.	•	•	4	, 44	444	* 444	, यसक क	, ककक क	' ययय य य	' ययय य य	' ययय य य	' जिंचच च च चच	' जिचच च च चचच	चिचच च च चचचच	' चिचच च च चचचच	' जिचच च च चचचचच	' जिचच च च चचचचचचच	' जिचच च च चचचचचचचच		444 4 4 4444444449000000000000000000000	8.8.8.8 090 090 090
}	Rota- tion		C.C.	ပ	C.C.	1.1	!	ပ	ပ္ပင္ပ		ပ်ပ္ပံပဲ		0 0 0 0	000000	00000	0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0		000 0 0 000	000 0 0 00000	000 0 0 000000	ပတ္လပ္ ပ ပ လွတ္လပ္လွပ္	ပတ္ပံ ပ ပ တွဲတွဲပဲစတ္တဲ့ပံပ	ပတ္တပ ပ ပ တိုက္ခံပတ္လွိပတ္ပ	တ <sup>တ္</sup> ပ ပ ပ လွတ္ပတ <b>္</b> ပတ္ပတ	တတ္တ တ တ တွ်တွ်တစ်တွ်တစ်တစ်တွ်	ပတ္ပံ ပ ပ ပွဲပွဲပံပံပွဲပံပံပံပံပံပံ
CHANIC		Volts	12	12	13			21	2 2	21 22																
ME	-	No.	1257	1258	1259			1264	1264 3520	1264 3520 3500	1264 3520 3500	1264 3520 3500	1264 3520 3500 3500F	1264 3520 3500 3500F	1264 3520 3500 3500Fl	1264 3520 3500 3500F  3502	1264 3520 3500 3500F  3502 3505 3505	1264 3520 3500 3500Fl 3502 3505 3505 3505	1264 3520 3500 3500F  3502 3502 3505 3505 3508 3508	1264 3520 3500 3500Fl 3502 3505 3505 3505 3506 3508	1264 3520 3500 3500Fl 3502 3505 3505 3508 3510 3510 3510 3551	1264 3520 3500 3500F  3502 3505 3505 3510 3551 3550	1264 3520 3500 3500 3502 3505 3505 3510 3550 3550 3550	1264 3520 3500 3500 3502 3505 3505 3508 3510 3551 3552 3556 3556 3556	3500 3500 3500 3500 3500 3505 3505 3508 3510 3550 3550 3550 3550 3550 3550 3550	1264 3520 3500 3500Fl 3502 3505 3505 3510 3510 3550 3550 3550 3550
		Model	D-2					<u>р.</u>	ក្នុង	D-9 F-3																
	Shown	on Plate	125	126	126-A 126		126-A	126-A 80-A	126-A 80-A 80-A	126-A 80-A 80-A 126	126-A 80-A 80-A 126	126-A 80-A 80-A 126 126-A	126-A 80-A 80-A 126 126-A 126-A	126-A 80-A 80-A 126-A 126-A 126-A 126-A	126-A 80-A 80-A 126-A 126-A 126-A 126-A 126-A	126-A 80-A 80-A 126 126-A 126-A 126-A 126-A 126-A	126-A 80-A 80-A 126 126-A 126-A 126-A 126-A 126-A 126-A 126-A 126-A 126-A 127-A 127-A 123-A 123-A 123-A 123-A 123-A 123-A 123-A 123-A	126-A 80-A 80-A 126-A 126-A 126-A 126-A 126-A 123 123	126-A 80-A 80-A 126- 126-A 126-A 126-A 129-A 123 123	126-A 80-A 80-A 126 126-A 126-A 126 128-A 123 123 123	126-A 80-A 80-A 126-A 126-A 126-A 128-A 123 123 123	126-A 80-A 80-A 126 126-A 126 126-A 123 123 123 124 124	126-A 80-A 80-A 126 126-A 126-A 128 128 128 128 128 128 128 128 80-A	126-A 80-A 80-A 126 126-A 126-A 126-A 123 126-A 124 125 126-A 80-A 841	126-A 80-A 80-A 126 126-A 126-A 128-A 123 123 124 124 80-A 841	126-A 80-A 80-A 126 126-A 128 128-A 123 123 123 124 124 126-A 80-A 841 841

Replacing Dodge Chain. When the driving chain on any equipment operated in this manner has worn to a point where it no longer makes proper contact with the sprockets (the chain being adjusted to the correct tension), it will be necessary to replace it. While the following instructions for "fishing" the chain through the housing apply particularly to the Dodge car, with little modifications here and there they will be found equally applicable to all similar installations.

Having removed the old chain, pass a short piece of wire through the end of the new chain, Fig. 308. Then start the chain on the lower side of the sprocket, as shown in the illustration, hooking the wire through the sprocket to keep the chain in mesh, and slowly turn the engine over by hand until the chain appears at the top of the sprocket. Then remove the wire from the sprocket, hold the end of the chain, and continue to turn the engine over until the chain is in


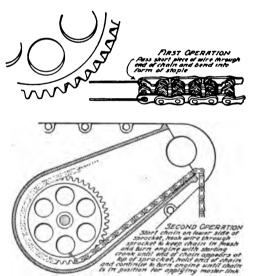



Fig. 308.—Diagram Showing Method of Inserting Chain in North East Equipment on Dodge Cars


a position to apply the master link.


Mechanical and Electrical Characteristics. When it is desired to make bench tests of any of the North East apparatus with the aid of the outfit described in connection with the Gray & Davis tests, the data shown in Table V will be found valuable for checking purposes. left-hand columns give the mechanical characteristics, with the aid of which the unit may be

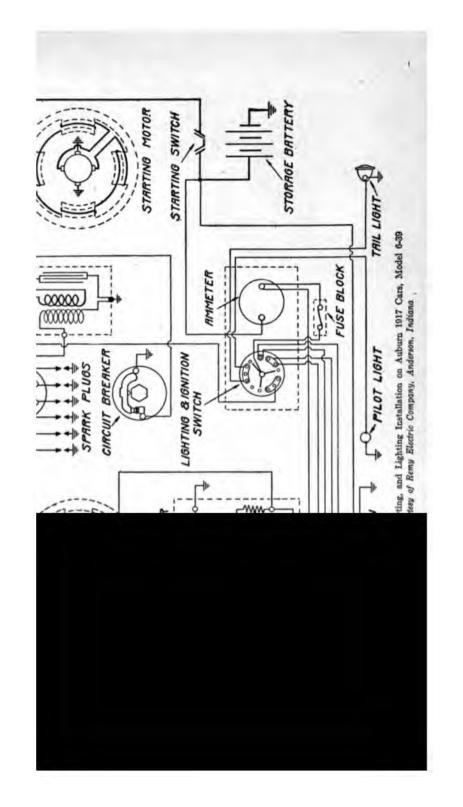
identified, while the right-hand columns give the electrical characteristics, such as the charging rate, torque in foot-pounds with given current input, cutting-in and cutting-out points of the master relay (battery cut-out), air gaps for the limitation relay, and the resistance of the units.




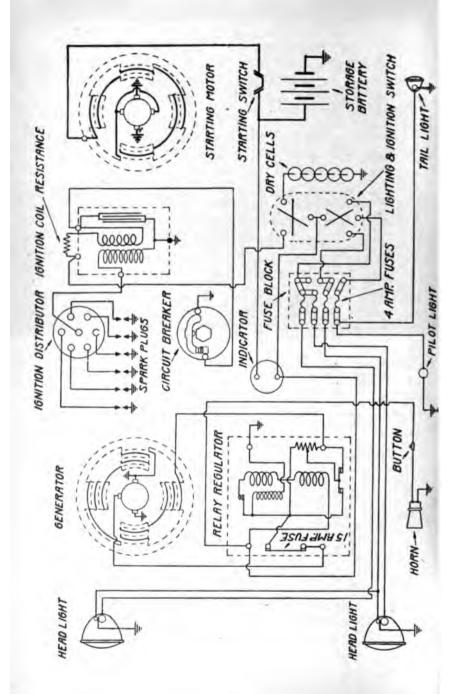


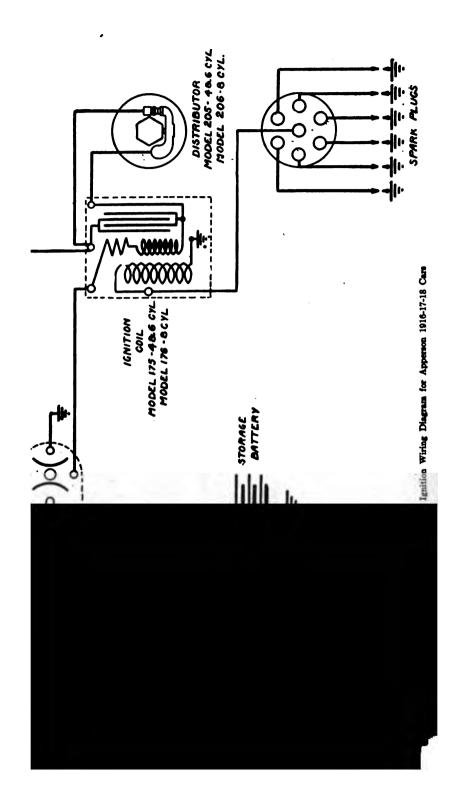


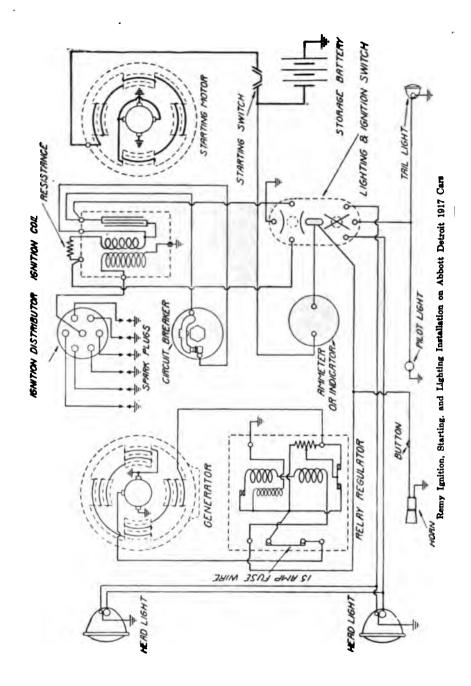

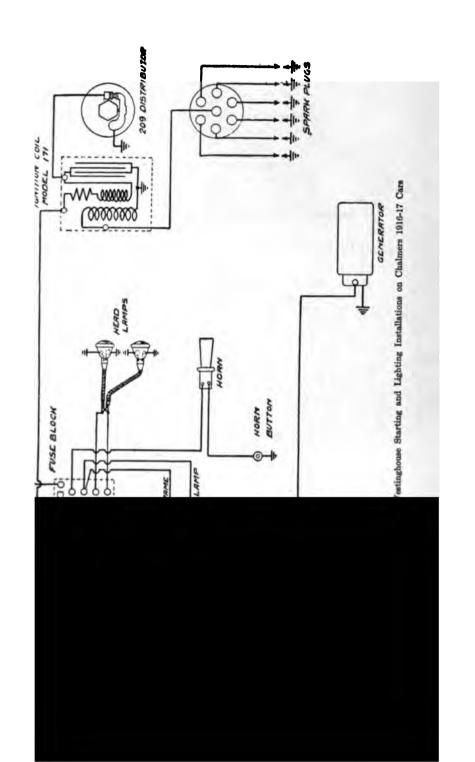

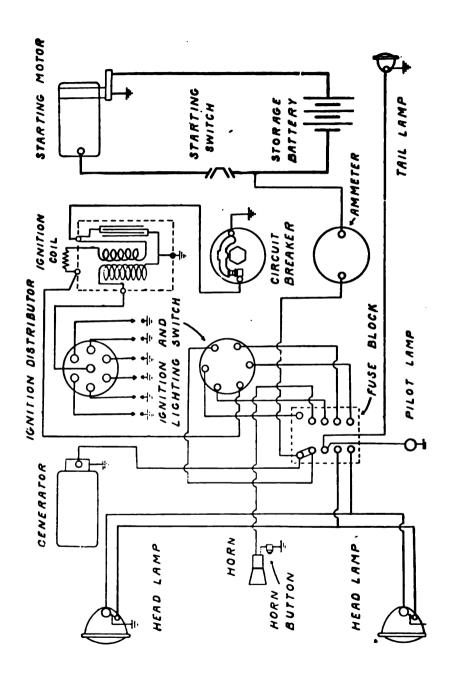

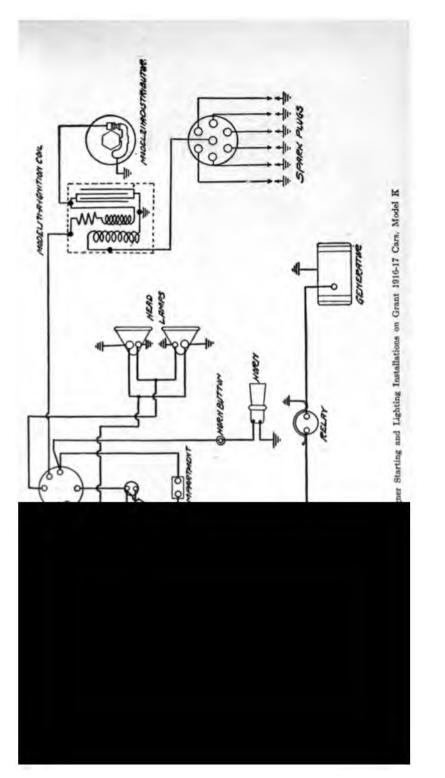

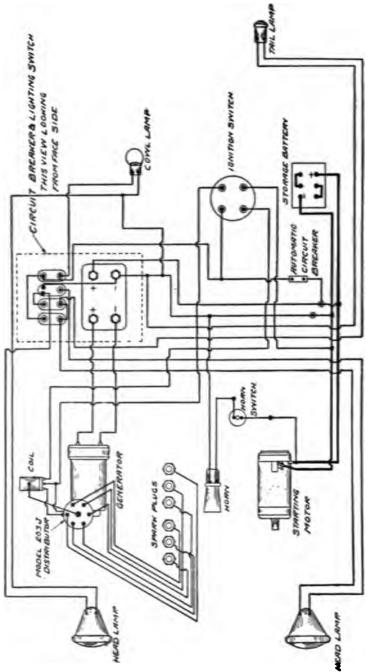

Remy Ignition Wiring Diagram for Haynes 1916-17 Care

## REMY SYSTEM

Six-Volt; Two-Unit; Single-Wire

Generator. Of the multipolar (four-pole) shunt-wound type of generator combined with ignition timer and distributor and designed to be driven at 1½ times crankshaft speed, several models are made, of which one is shown in Fig. 309. In this case, both the regulator for the generator and the battery cut-out are mounted directly on the generator. On some of the models only the regulator is so mounted, the cut-out being placed on the dash of the car,

while on others no independent regulating device is required as the third-brush type of regulation is employed (on bipolar generator).

Regulation.
In accordance with the model of generator and the requirements of the engine to which it is to be




Fig. 309. Remy Ignition Generator and Distributor Courtesy of Remy Electric Company, Anderson, Indiana


which it is to be fitted, either the constant-voltage method of

pull the armature down. This separates the contacts and causes the field current to pass through the resistance unit, thus decreasing the field current and, in turning, decreasing the generator output, which reduces the exciting effect on the electromagnet and causes it to release its armature, cutting the resistance out of the field circuit. The latter immediately builds up again, and the operation is repeated as long as the speed remains excessive for the generator, which is thus supplied with a pulsating current to excite its fields, and its output is held at a practically constant value.

Third-Brush Method. The third-brush method of regulation is based upon the distortion of the magnetic field of a generator at high speeds. When running at low speeds, the magnetic flux of a generator is evenly distributed along the faces of its field pole pieces, but at high speeds there is a tendency to drag it out of line in the direction of the rotation of the armature. It is then said to be distorted. The third brush, which supplies the exciting current to the field winding, is so located with relation to the main-line brush of opposite polarity that this distortion of the magnetic flux reduces the current which it supplies to the fields. This decrease in the exciting current of the field causes a corresponding decrease in the output of the generator, and as the distortion of the magnetic flux is proportional to the increase in speed, the generator output falls off rapidly the faster it is driven above a certain point, so that it is not damaged when the automobile engine is raced.

Thermostatic Switch. More of the current produced by the generator is used for lighting purposes in winter than in summer, in the proportion that the demands for house lighting vary with the change of the seasons. Added to the decreased efficiency of the storage battery in cold weather, this tends to place a greatly increased load on the generator in the winter months. If the generator, as installed, were regulated to produce sufficient current to take care of this maximum demand, it would keep the storage battery in a constant state of overcharge in summer and would be likely to ruin the plates through excessive gassing. The Remy engineers have accordingly developed a method of regulation that will automatically compensate for the difference in the demand with the changing seasons, consisting of a thermostatic switch in connection with the third-brush control; it will be found, among others, on the Reo 1917 models.

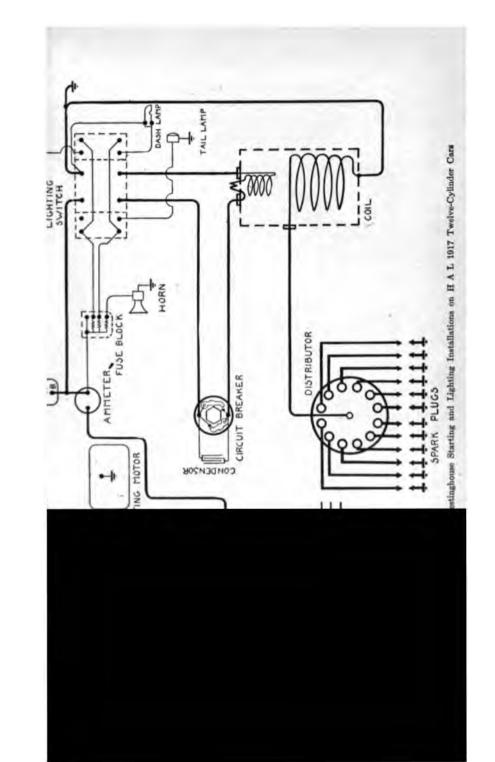

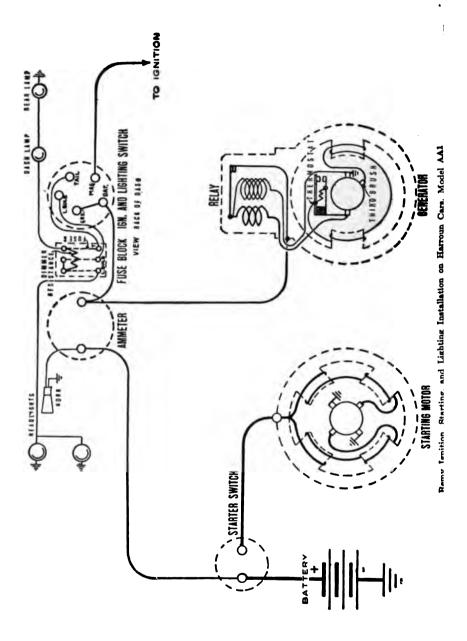

To gain a clear idea of the action of an electric thermostat, the heating effect of the current must be kept in mind; also that different metals have different coefficients of expansion, i.e., some will expand more than others under the influence of the same degree of heat.

Electric thermostats have been in use for years as automatic fire alarms and as temperature-controlling devices in incubators and for residence heating, and within the past few years they have come into use on the automobile to control the circulation of the cooling water and the suction of the engine in accordance with variations in the temperature. The device consists of a thermal member, or blade, of


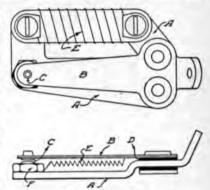


Fig. 310. Details of Remy Thermostatic Switch

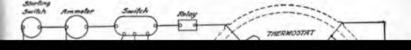two different metals riveted together at their ends. This member is held fast at one end and at the other it carries a contact point, designed to complete the circuit by touching a stationary contact. Under the influence of an increase in temperature, one of the metals



a strip of steel A. A also carries the resistance unit E, which is a short coil of high-resistance wire wound on heavy mica insulation. A and B are riveted together at the end D so as to insulate them from each other. The two metals composing B are spring brass and nickel steel, the strip of spring brass being placed on the lower side of the blade. Sufficient tension is placed on this strip, by means of the adjusting nut F, to keep the points firmly in contact at temperatures below  $150^{\circ}$  F. This adjustment is made by the manufacturer and is permanent.

As shown in the wiring diagram, Fig. 311, which illustrates the relation of the thermo-switch to the third-brush method of regulation, it will be noticed that the switch is placed near the commutator of the generator, as that is the hottest part of the machine when it is in



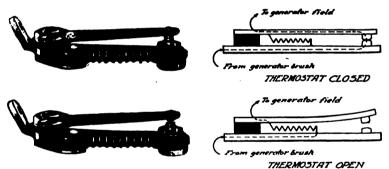


Fig. 312. Photographic Reproductions and Diagrams of Action of Thermostatic Switch
When Closed and Opened
Courtesy of Remy Electric Company, Anderson, Indiana

operation. It will be noticed also that when the contact points of the thermo-switch are open, as shown in the illustration, the current supplied to the field by the third brush must pass through the resistance unit of the switch, thus cutting it down. This is the position for warm-weather running, when not so much of the current is required for lighting, and when the storage battery is at its best. When the temperature of the air about the thermo-switch exceeds 150° F., the movable blade is warped upward, owing to the greater coefficient of expansion of the brass as compared with that of the nickel steel. The contact points will accordingly remain open as long as the temperature exceeds this degree. When it falls below that point, the quicker contraction of the brass pulls the blade down, and the points again make contact, cutting out the resistance and increasing the output

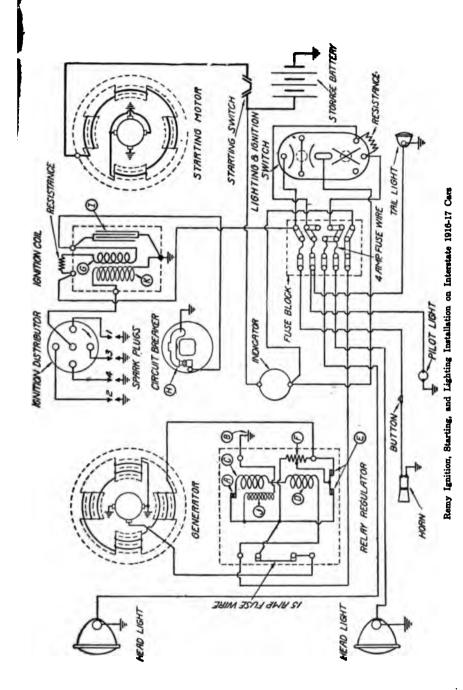

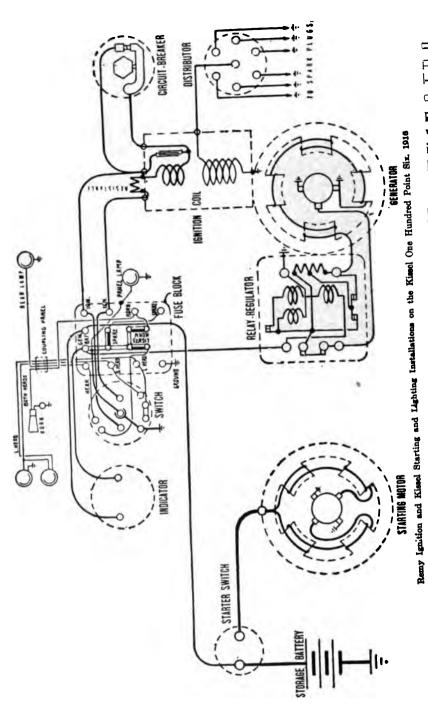

the generator, diagrams of the thermo-switch in its closed and open ositions being shown at the right, and a halftone of the switch at the ft in Fig. 312, while the curves, Fig. 313, show the increase in the irrent output brought about by the closing of the thermo-switch pints. The path taken by the current when the points are open and

hen they are closed is dicated by the dotted nes in the diagrams, Fig. 12. The curves show at with the thermoritch open, the maximum current output of the generator is limited 14 to 15 amperes, hile with the switch osed it rises to 20 to

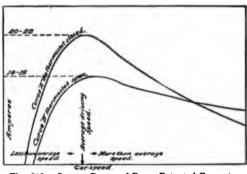


Fig. 313. Output Curves of Remy Patented Generator

! amperes. The switch will normally remain closed after the engine is been idle for any length of time; but in summer it will open after iving a few miles, while in winter it will probably remain closed, matter how much the car is driven.

Starting Motor. The motor is the 6-volt 4-pole series-wound rpe, illustrated in Fig. 314, mounted either with gear reduction



to indicate any discharge, in all except the starting-motor circuit, due to grounds or short-circuits. All lamp circuits are fused, and a fuse is inserted in the regulator circuit.

## Remy Single-Unit

A Mechanical Combination. While termed a single-unit type, this is actually two independent units combined, mechanically and not electrically, so that it bears no resemblance to the single unit on which both field and armature windings are carried on the same pole pieces and armature core. The field frame for the two units is a single

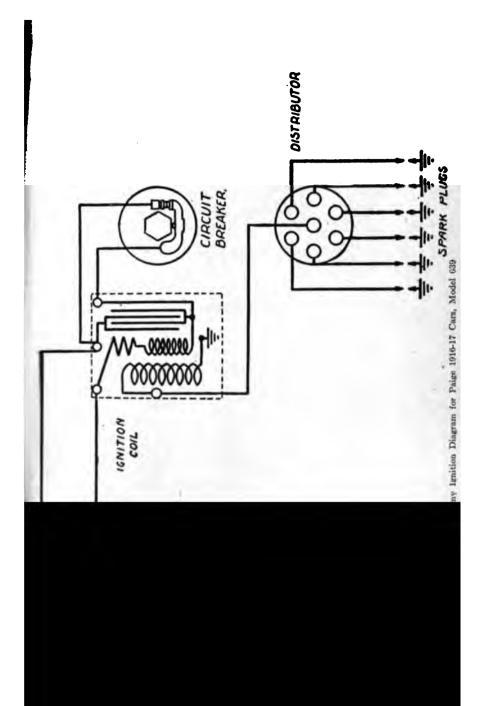



Fig. 315. Combined Field Frame of Generator and Motor for Remy Single-Unit System


casting, Fig. 315, but the magnetic circuits of both the generator and the motor are entirely independent, and each is a separate unit. They are combined in this manner solely for convenience in mounting where space is limited. The vibrating type of voltage regulator is employed in connection with the generator, while the starting motor operates through a train of reducing gears and an over-running clutch. Apart from the combination of the two units and the method of starting drive which this entails, the sys-

tem is the same in its essentials as where the units are mounted independently.

Wiring Diagrams. Velie. Fig. 316 shows the installation on Velie, Model 22, and the details will be plain with further explanation. The "ratchet reversing switch", shown in the diagram, is for controlling the ignition current, and it is designed to reverse the direction of this current each time the switch is turned on in order to prevent the formation of a crater and cone on the ignition interrupter contacts, as previously described, thus keeping the points in good work-



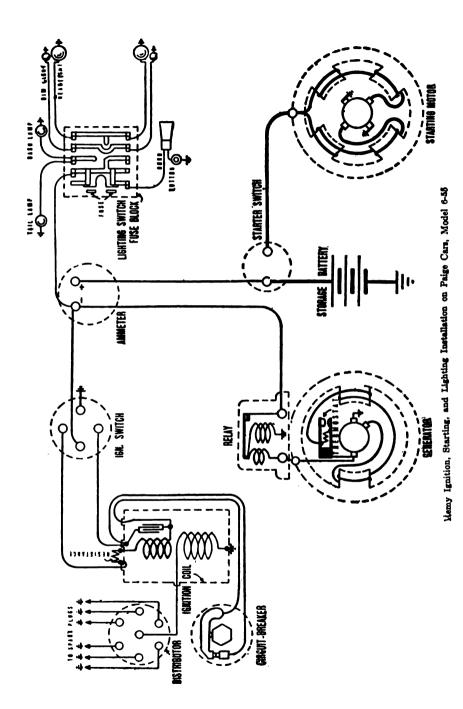

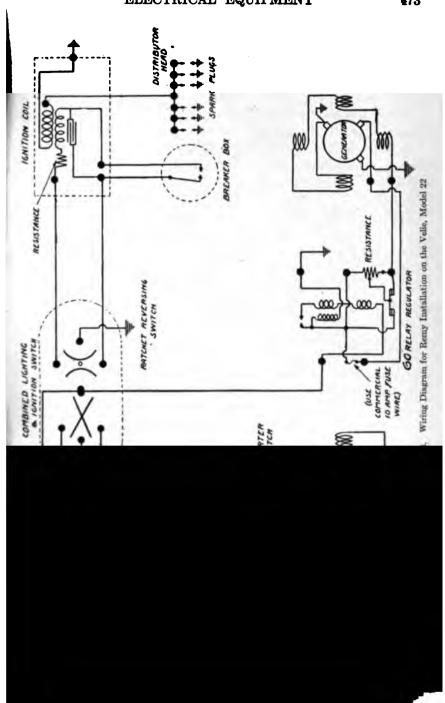

ing order for a much longer period. The dash and tail lights are 3}-volt lamps, wired in series, so that the failure of one puts the other out, thus giving an indication at the dash of the failure of the tail light.


Oakland. The Remy installation on Oakland Model 32 is shown in Fig. 317. The chief distinction between this and the previous diagram is the employment of a single 10-ampere fuse on the lighting circuits instead of independent fuses on each circuit. "Breaker box" refers to the ignition-circuit contact-breaker, or interrupter, as it is variously termed. The starting motor in this case is fitted with the Bendix drive.


Reo. On the Reo installation, Fig. 318, the starting motor is mounted on the transmission housing and drives to a shaft of the latter through a worm gear. In this case the starting switch is mounted directly on the starting motor, and an ammeter is supplied on the charging circuit instead of a telltale, or indicator.

National. A typical installation of the single unit, or so-called double-deck unit, is shown in Fig. 319. This is on the National six-cylinder model and is a two-wire system. It is not interconnected with the ignition system, so there are no ground connections, and no fuses are employed.


Instructions. These instructions cover the systems which include the ignition. For instructions applying to the double-wire system on cars having an entirely independent ignition system, like the National, see instructions under Auto-Lite, Delco, Gray & Davis, and others, for failure of generator or motor, short-circuits, and the like.

Battery Discharge. In systems of this type, discharge of the battery may be due to failure to open the ignition switch after stopping the car. The amount of current consumed is small but in time it will run the battery down. The indicator or the ammeter, according to which is fitted, will show a discharge. An entire failure of the current may indicate: a loose connection at battery terminals, at battery side of starting switch in connection with a blown main fuse (Oakland), or a loose battery ground connection; a loose connection at motor side of starting switch or at starting motor, or a broken wire between the switches. (See previous instructions on other makes for testing with lamp set for broken or grounded circuits.)

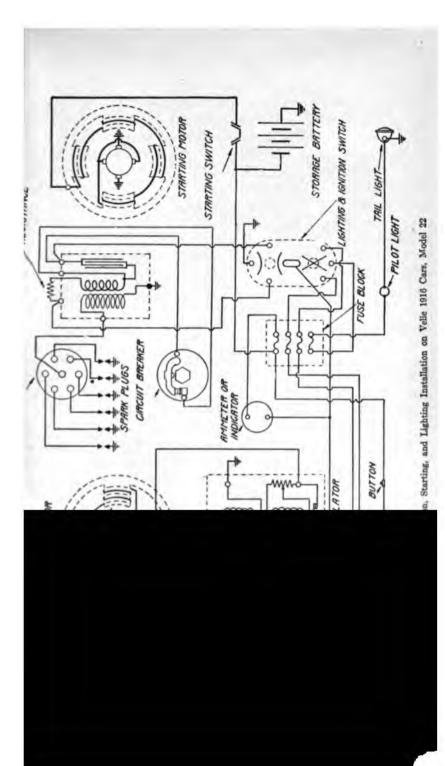


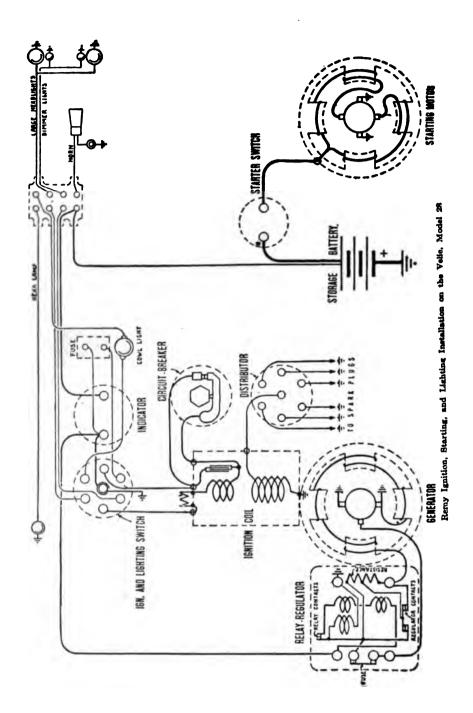


たたり

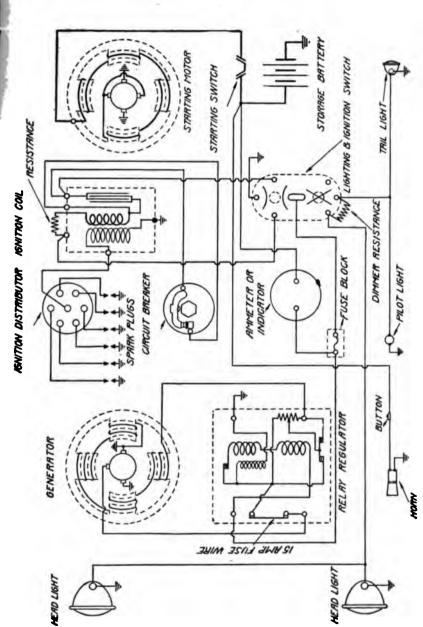

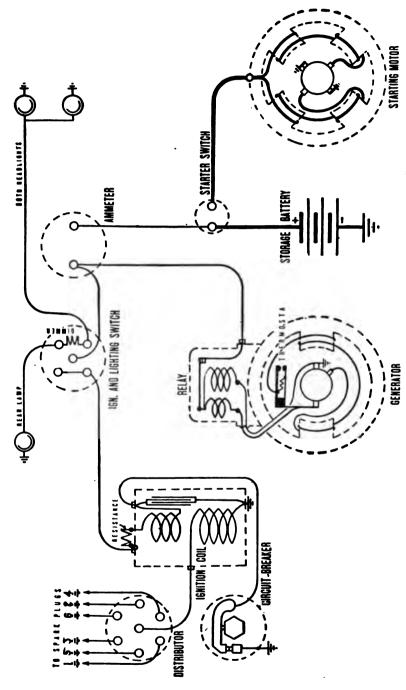Remy Ignition, Starting, and Lighting Installation on Oakland Model 32, and McLaughlin Cars



Remy Ignition, Starting, and Lighting Installation on Oakland 1917, Model 34-B

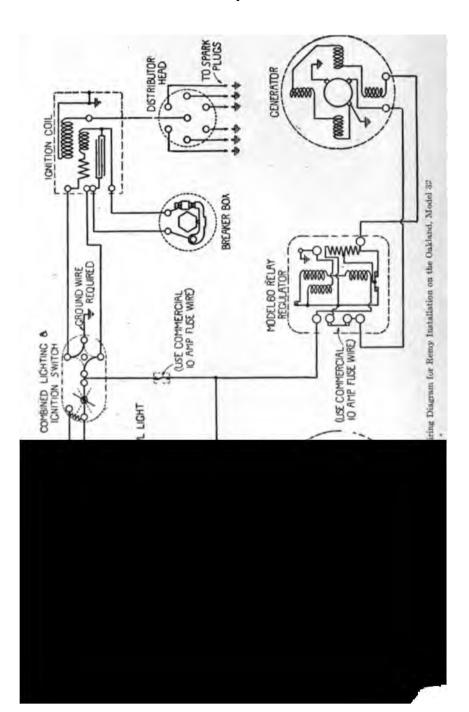




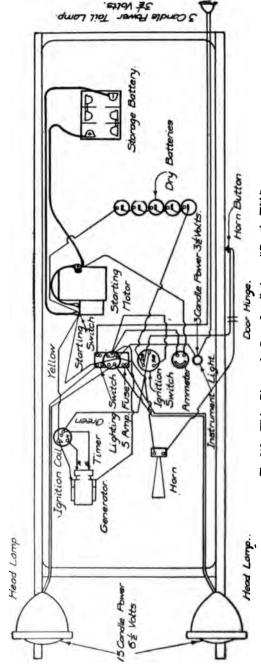



Fig. 318. Wiring Diagram for Remy Installation on "Reo the Fifth"

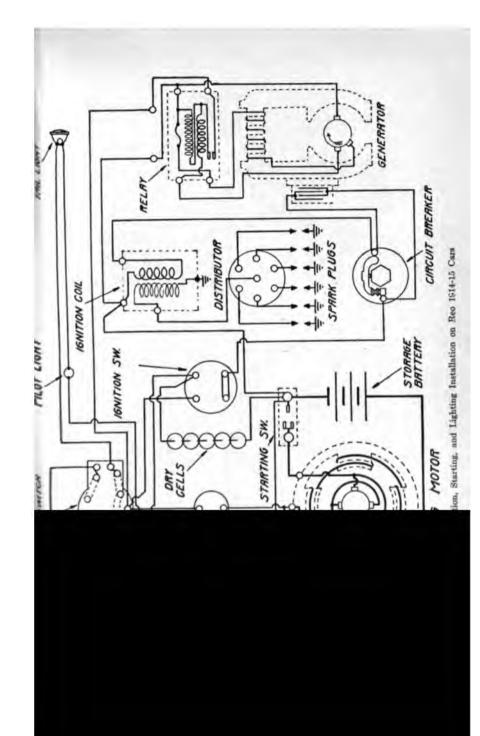

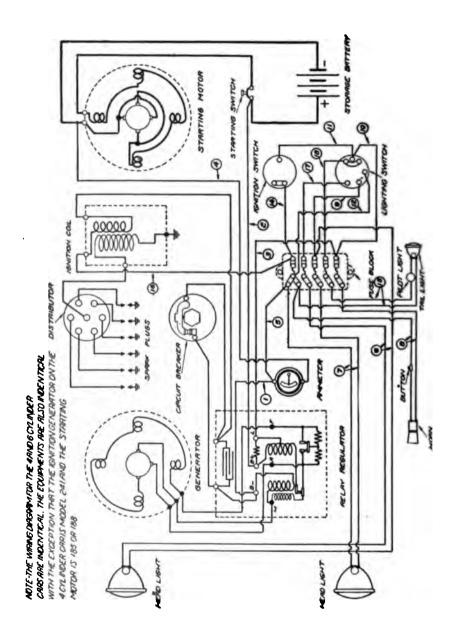

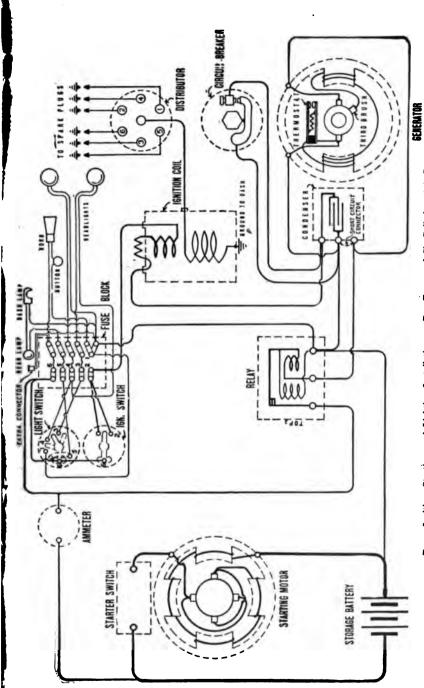

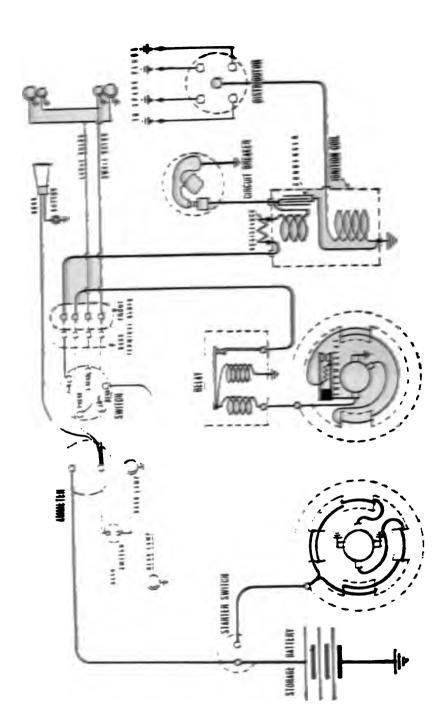Remy Ignition, Starting, and Lighting Installation on Reo Four- and Six-Cylinder 1917 Cars




559


Failure of Lighting, Ignition, Starting. When the lights and ignition fail but the starting motor operates, it indicates a short or open circuit between the starting switch and the main fuse (Oakland). This fuse should first be examined and, if blown, a search should be made for the ground or short-circuit causing it, before putting in a new fuse. The fault will be in the wiring between the switch, lights, and ignition distributor. See that all connections, including those on fuse block, are tight. When the lights fail but the ignition and starting motor operate, the trouble will be found either in the circuits between the lighting switch and lamps; in the lamps themselves, as a burned-out bulb causes a short-circuit; or from loose connections in these circuits. Failure of the ignition. with the remainder of the system operating, may be traced to loose connections at the ignition switch, coil, or distributor; poor ground ing of the ignition switch on the speedometer support screw; or to open or short-circuits between the ignition switch and the distributor. Further detail instructions on ignition are given in Ignition, Part II.


Dim Lights. When all the lights burn dimly, the most probable cause is the battery, but if a test shows this to be properly charged, a ground between the battery and the starting switch or between the latter and the generator may be responsible for leakage. Other causes are the use of higher candle-power lamps than those specified, the use of low efficiency carbon-filament bulbs, or failure of the generator to charge properly.

Examine generator-field fuse and if blown, look for short-circuits before replacing, as previously instructed. A simple test of the generator may be made by switching on all the lights with the engine standing. Start the engine and run at a speed equivalent to 15 miles per hour or over. If the lights then brighten perceptibly, the generator is operating properly. This test must be made in the garage or preferably at night, as the difference would not be sufficiently noticeable in daylight.

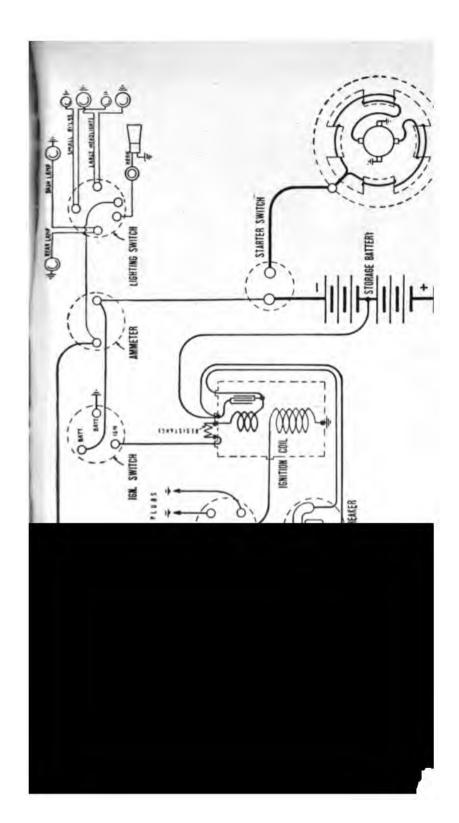
If the generator fuse is intact, examine the regulator relay contacts. If the points are stuck together, open by releasing the relay blade with the finger. Clean and true up points as previously instructed and clean out all dust or dirt from relay before replacing cover. Particles of dirt lodged between the points will prevent the generator from charging properly.



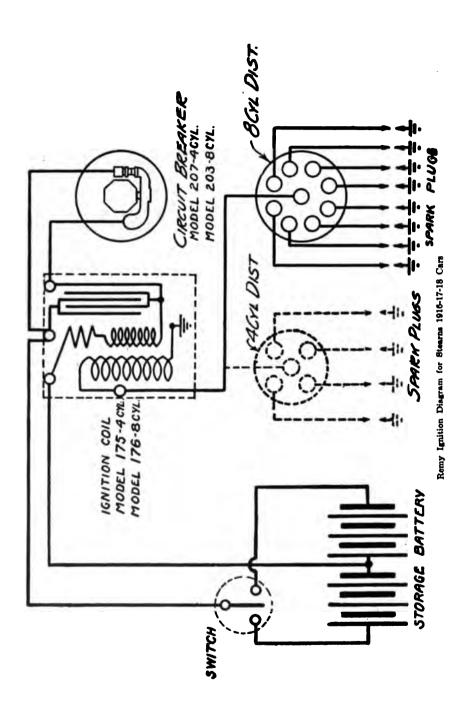

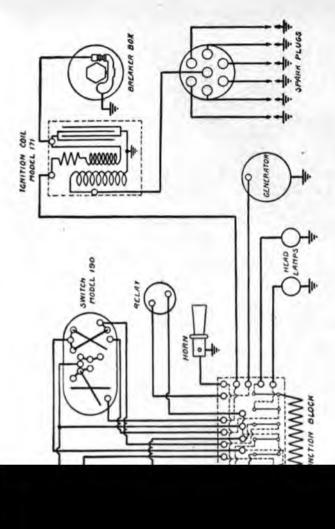

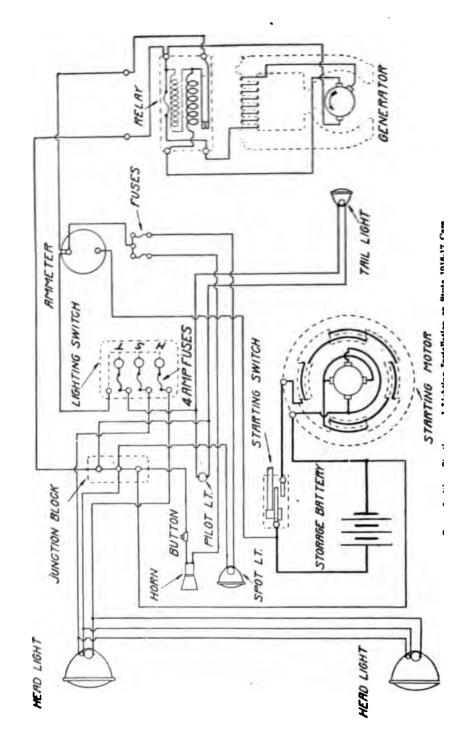ny Ignition Wiring Diagram for Studebaker 1916-17 Cars



The failure, flickering, or dim burning of any single lamp will be due to a burned-out bulb, to loose or frayed connections at lamp or switch, to a bulb loose in its socket, or to an intermittent ground or short-circuit in the wiring of that particular lamp, or to the frame of the lamp nor being grounded properly. Where dash and tail lamps are in series, examine both bulbs and replace the one that has burned out. Test with two dry cells connected in series.

Ammeter. When the indicator, or ammeter, does not register a charge with the engine running with all the lights out, stop the engine and switch on the lights. If the instrument gives no discharge reading, it is faulty. If it shows a discharge, the trouble is in the generator or connections. In case the ammeter registers a discharge with all the lights off, ignition switch open, and engine idle, examine relay contacts to see if they remain closed. If not, disconnect the battery. This should cause the ammeter hand to return to zero; if it does not, the instrument is out of adjustment. With the ammeter, or indicator, working properly, and the relay contacts in good condition, a discharge then indicates a ground or short-circuit. When examining the relay for trouble, do not change the adjustment of the relay blade.

## SIMMS-HUFF SYSTEM Twelve-Volt; Single-Unit; Single-Wire

Dynamotor. The dynamotor is of the multipolar type having



Dynamotor Connections. The dynamotor has two connections, one at the bottom of the forward end plate, marked DYN+, and the other on top of the field yoke designated as FILED. As the system is a single-wire type, the opposite sides of both circuits are grounded within the machine itself. The terminals on the cut-out are marked BAT+, DYN+, and DYN-, BAT-, and FLD.



Fig. 320. Field Frame, Poles, and Windings for Simms-Huff Dynamotor




Fig. 321. Brush Rigging for Simms-Huff Dynamotor



Fig. 322. Simms-Huff Dynamotor with Commutator Housing Plates Removed Courtesy of Simms Magneto Company, East Orange, New Jersey

BAT+ connects through a 12-gage wire to the negative side of the ammeter and thence to a terminal on the starting switch. This connects it permanently to +R of the battery through the ammeter. This wire supplies the current to the distributing panel, from which

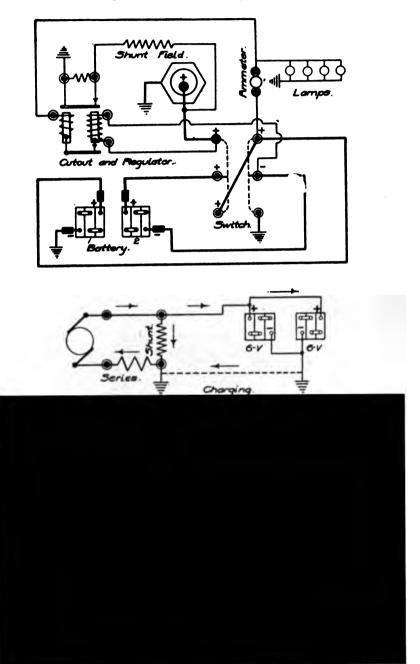current is supplied to the lamps and horn. DYN+ connects through a similar wire to the plus terminal of the dynamo, while DYN- and



starting at 12 volts. There are accordingly 6 cells in the storage battery, and the latter is charged by placing the two halves of it, consisting of two 3-cell units, in parallel. This is indicated in the


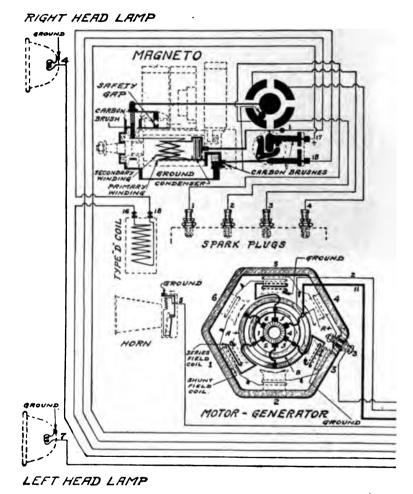


Fig. 324a. Complete Wiring Diagram for 1916-17 Maxwell Cars (see Fig. 324b)

Courtesy of Simms Magneto Company, Bast Orange, New Jersey

upper diagram, Fig. 323, also in the middle diagram, which shows the connections for charging. In the lower diagram of the figure are shown the starting connections, the switch being connected to throw the 6 cells of the battery in series, so that the unit receives current at

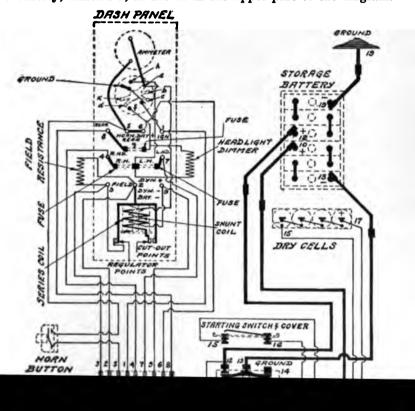12 volts for starting, thus doubling its power. Six-volt lamps are employed and are supplied with current from the left-hand section of the battery, marked 1, as shown in the upper part of the diagram.




battery in circuit with the ignition system so that, as soon as the engine starts and the switch is released, it automatically disconnects the battery from the ignition, and the engine then runs on the magneto (dual ignition system).


Wiring Diagram. Fig. 324a and Fig. 324b show the wiring diagram complete of the ignition, starting, and lighting systems as installed on the 1916 and 1917 Maxwell cars. The heavy lines indicate the starting-system connections, while the light lines are the wires leading from the generator to the battery (through the regulator and cut-out), and the various connections for the ignition and the lamps. They show very plainly, upon tracing them out, the relation of the regulator and cut-out to the generator and the battery, as well as the method of dividing the six cells of the battery into two units for lighting service, and the coupling of all the cells in series for starting. It will be noted also that the storage battery is not utilized for ignition, as the starting switch closes the circuit of a dry battery of four cells for ignition when starting the engine. As the starting switch automatically opens this circuit when released, there is no danger of this battery being inadvertently left in circuit.

At the upper left-hand corner of the diagram, complete details of the ignition circuit and of the magneto itself are shown. The magneto (Simins) is of the true high-tension type, having primary and secondary windings on the armature core, as well as a condenser incorporated in it. As this sketch shows not only the relation of high-tension type of magneto to the plugs but also that of the essential parts of the magneto, as well as the relation of the ignition system to the starting and lighting systems through the combination starting and ignition switch, it will repay close study. The number of wires makes it appear as if this were a two-wire system, but upon noting the ground connections at the various terminals it will be evident that it is not.


Instructions. The Simms-Huff system as above described is standard equipment on the Maxwell cars. The combination cutout and regulator is mounted on the rear of the dash panel carrying the ammeter and switch. It consists of two distinct devices, the cut-out serving the usual purpose of protecting the battery when the generator voltage drops, and the regulator limiting the current output of the dynamo as the engine speed increases. In connection

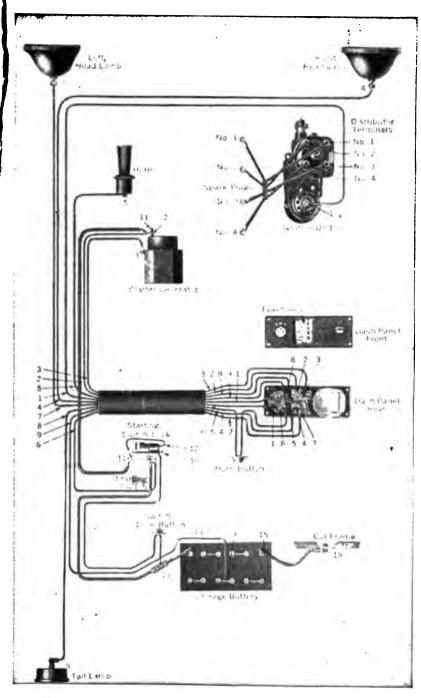

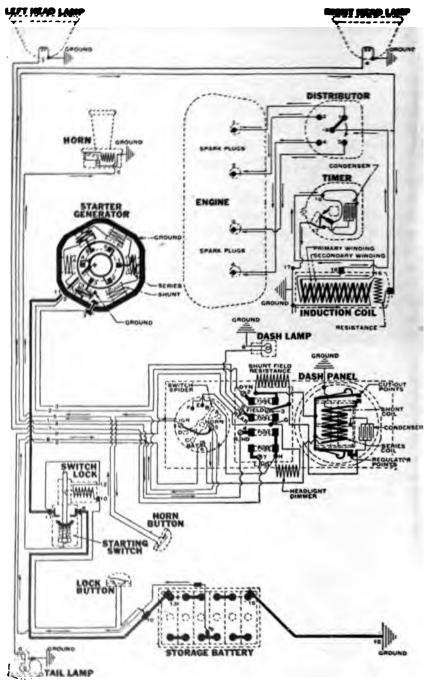Simms-Huff Ignition, Starting, and Lighting Installation on Maxwell 1918 Cars Courtesy of Maxwell Motor Company, Detroit, Michigan



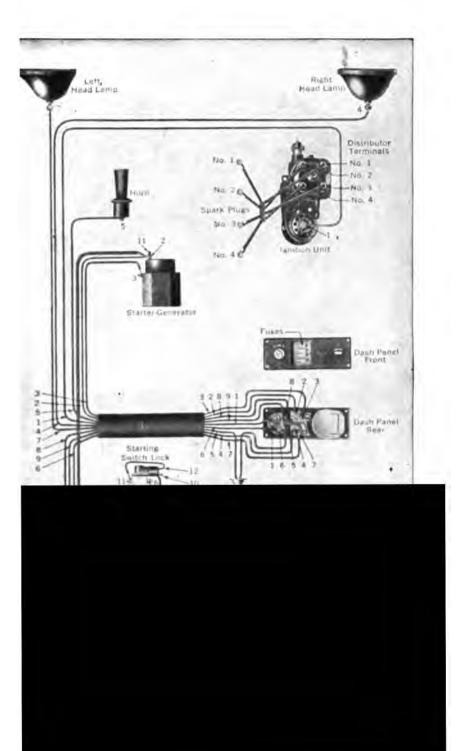Wiring Diagram for Simms-Huff Starting and Lighting Installation on Maxwell 1918 Corn Courtesy of Maxwell Motor Company, Debroit, Michigan



the socket. A good rule is always to test the lamp itself first; sometimes the connecting plug of the set is not properly screwed into the socket.

While the above test for the armature, if properly carried out, will show whether the latter is grounded or not, it will not give any indication of an internal short-circuit in the armature itself. To determine this, connect the shunt fields and run the unit idle as a motor, with the portable ammeter in the circuit, using the 30-ampere shunt. While running without any load the motor should not consume more than 7 amperes at 6 volts, i.e., using half the battery. Tests for grounds in the shunt field may be made with the lamp-test set, but to determine whether there is a short-circuit in the field, it is necessary to measure the resistance of its windings. If there is neither a short-circuit nor a ground in the field, the resistance of the windings should calculate approximately  $6\frac{1}{2}$  ohms on units with serial numbers up to 27,000, and approximately 4.8 ohms on starters above this serial number.


The Simms-Huff is one of the very few, if not the only unit, that is belt-driven as a generator. Its normal output is 10 to 15 amperes; so when the dash ammeter shows any falling off in this rate, with the engine running at the proper speed to give the maximum charging current, the belt drive of the generator should be inspected. If the ammeter reading falls off as the engine speed increases, it is a certain indication that the belt is slipping and that the generator itself is not being driven fast enough. Adjust the tension of the belt and test again. If this does not increase the output to normal, inspect the commutator and brushes, brush connections and springs, etc. See that the brushes have not worn down too far, and if necessary, sand-in. Failing improvement from any of these expedients, inspect the regulator. This should not be adjusted to give more current until every other possible cause has been eliminated; and before making any change in the adjustment of the contacts, see if cleaning and truing them up will not remedy the trouble. necessary to adjust, do so very carefully, as increasing the current output by this means will also increase the voltage, and if the voltage exceeds the normal by any substantial percentage, all the lamps will be burned out at once. Trouble in the electrical unit itself will be most likely to appear in the brush holder.

Whenever it is necessary to remove the front end plate over the commutator to inspect the commutator or the brushes, be sure that this plate is put back the same way, and not accidentally turned round a sixth of a revolution, which would cause the motor to run backward. There is a slot in the front end of this plate to permit the brush holder to be moved backward or forward so as to give the best brush setting as a generator and as a motor. On most of the Simms-Huff units, a chisel mark will be found on each side of the fiber insulator under the main terminal post, indicating the factory brush setting. Checking this brush setting should be one of the further tests undertaken before resorting to adjustment of the regulator. To do this, connect the portable ammeter in the charging circuit (30-ampere shunt) or, if one of these instruments is not available, the dash ammeter may be relied upon.

Run the engine at a speed high enough for the maximum normal output; loosen the brush holder and move very slowly backward and forward, meanwhile noting the effect on the reading of the ammeter; and mark the point at which the best output is obtained. To test as a motor, connect the ammeter in circuit with half of the battery and run idle. Move brush holder backward or forward to obtain best setting point, as shown by the ammeter reading, which, in this case, will be the minimum instead of the maximum. The unit should not draw more than 7 amperes when tested in this manner. If the best points for generating and running as a motor, as shown by these tests,

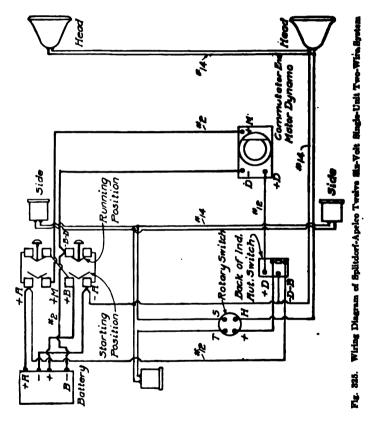
## Six-Volt; Two-Unit


Control. Switch. The starting switch is mounted on a starting motor. This switch automatically breaks the circuit soon as the engine starts. The starting gear slides on spiral splin on the armature shaft, so that when the engine gear over-runs the starting gear is forced out of engagement. This gear is connect





to a drive rod which also engages a switch rod, so that when t gear is forced out of mesh with the flywheel, it carries the swit rod with it and automatically opens the circuit. The switch contactannot stick, and no damage can result from holding down the swit pedal after the engine has started.

Regulation. On the earlier models, a vibrating regulator w built in the generator, as illustrated in the section on Constar

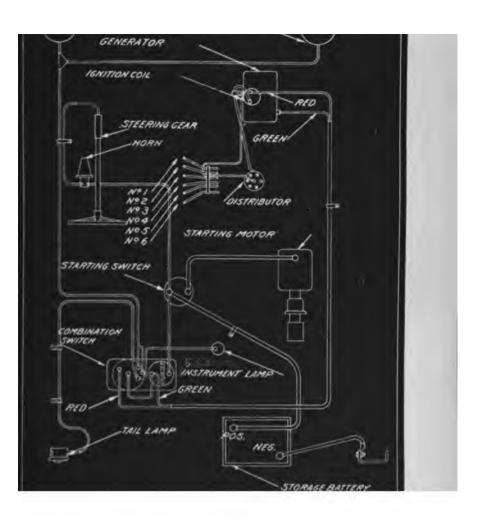

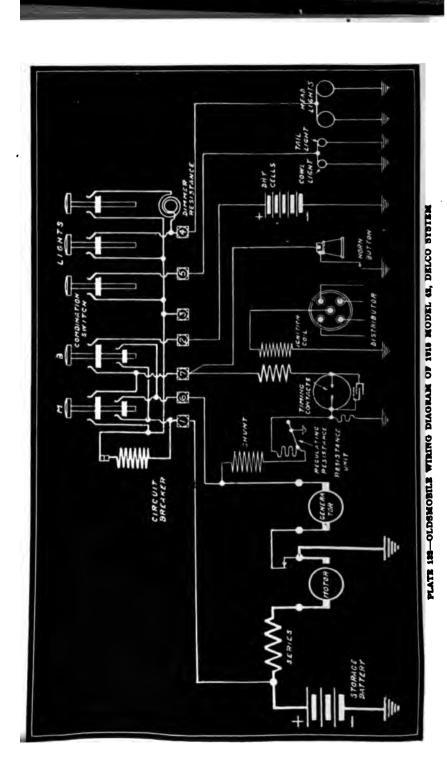

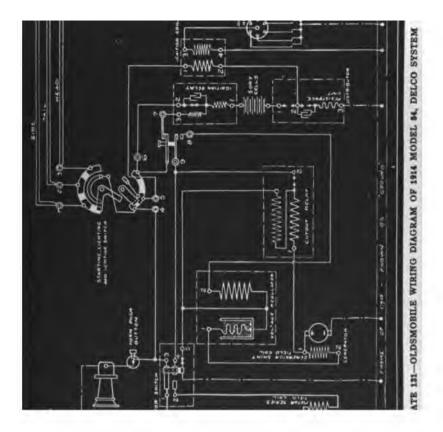

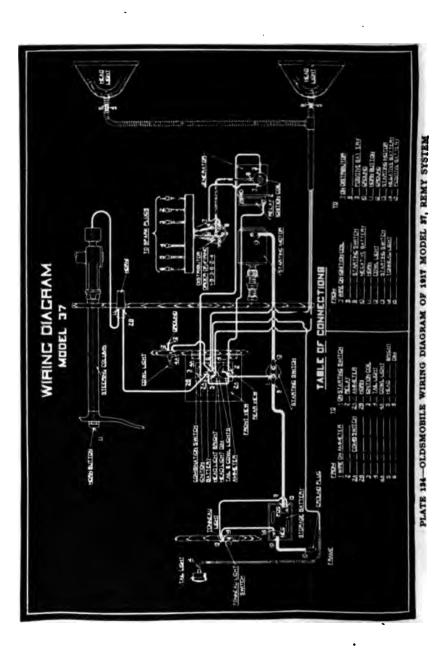

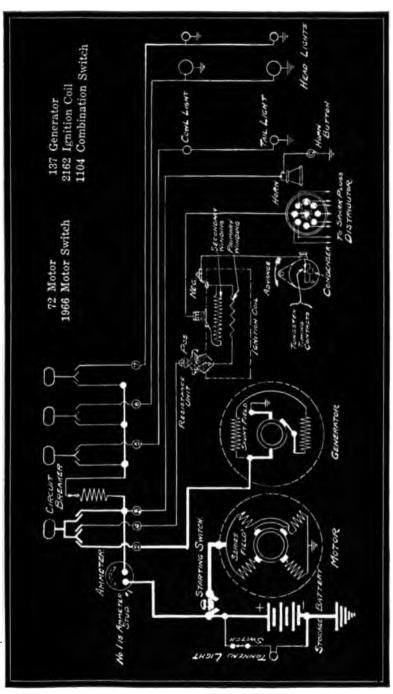


PLATE 126-OLDSMOBILE WIRING DIAGRAM OF 1919 MODEL 45-A, DELCO SYSTEM

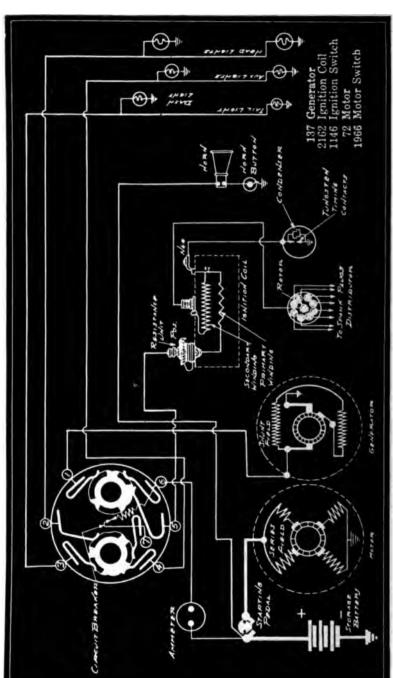


PLATE 156-CLDSMORILE WINING DIAGRAM OF 1919 MODEL 46-B, DELCO STETEM




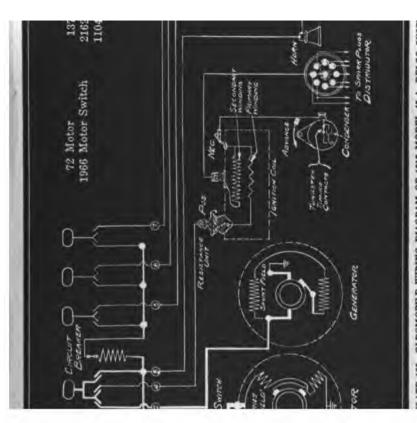



PLATE 185-OLDSMOBILE WIRING DIAGRAM OF 1919 MODEL 45-A, DELCO SYST.

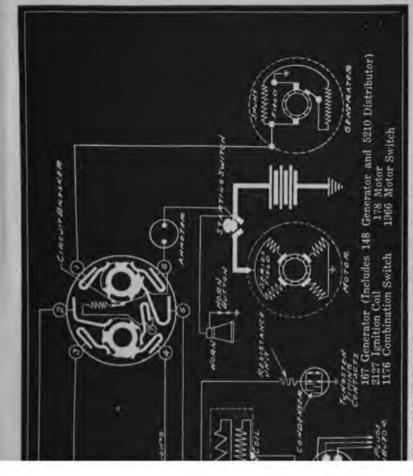


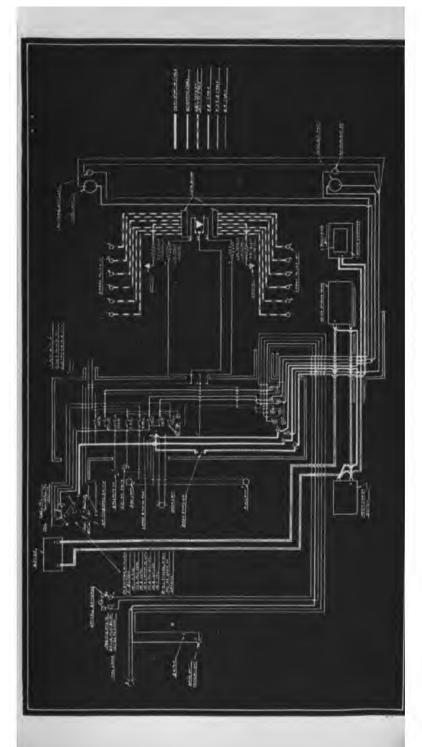
MOBILE WIRING DIAGRAM OF 1920 MODEL 45-B, DELCO SYSTEM



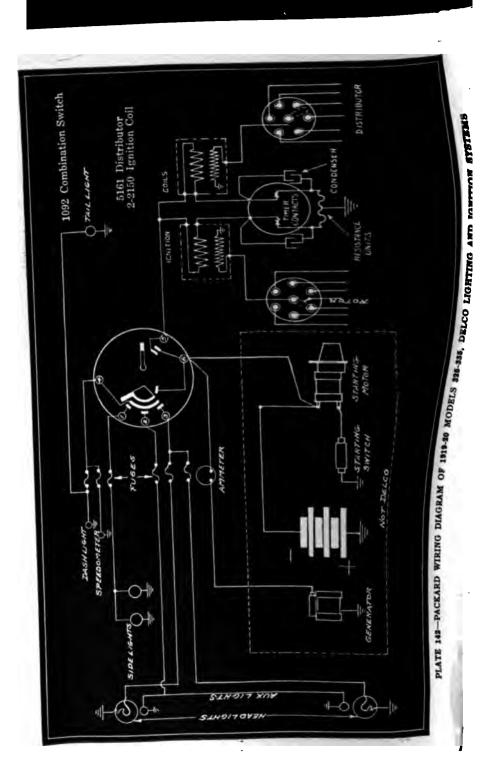

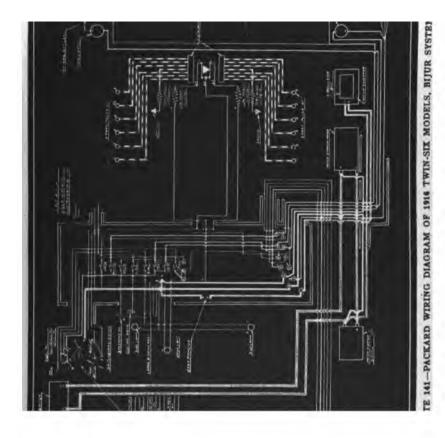

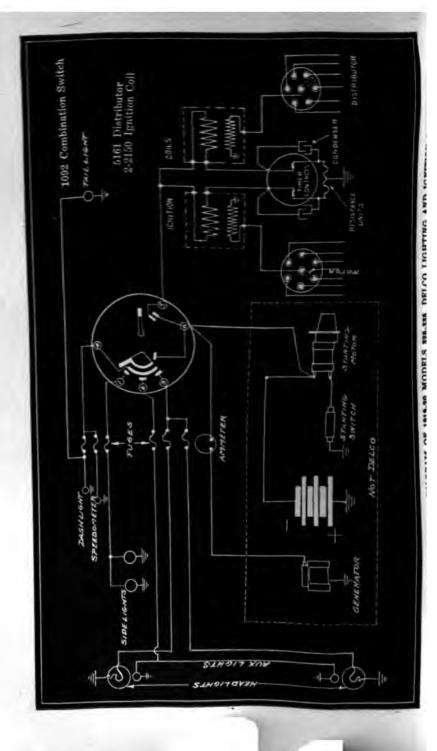

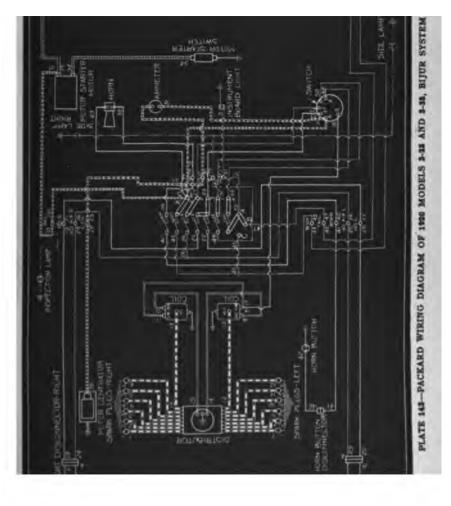

tacts should not require attention on an average oftener than once a year, but it would be well to examine them occasionally.

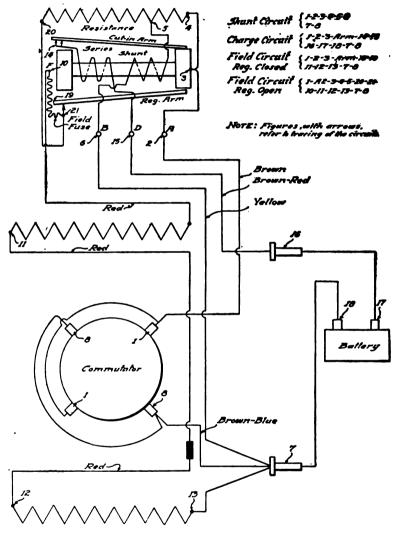


Fig. 327. Wiring Diagram of Splitdorf Lighting Generator and VR Regulator

By referring to Fig. 327, which is a diagram of the wiring of the generator and battery, the relation of these essentials to the regulator and cut-out are made clear. The field fuse shown on this diagram is

also indicated at F in Fig. 326. This fuse is a small piece of soft-alloy wire mounted between the post F and the contact-breaker. referring to the wiring diagram, it will be noted that this fuse is in the shunt-field circuit, so that if it has been blown, the machine will not It is designed to blow only at high speed with the battery off the line and the vibrator contact R stuck. In actual practice. the regulator cut-out is mounted directly on the generator itself. The colors mentioned alongside the different wires are for purposes of identification so that there will be no mistakes in making the various connections.

Starting Motor. The starting motor is of the series-wound type and is similar in design to the generator. It is supplied with a Bendix drive as shown in Fig. 328.

The starting motor is constructed so that when the operator presses the starting switch, the starting circuit is completed and



Courtesy of Splitdorf Electric Company, Newark, New Jersey


amount of current actually required for turning over the engine is thus controlled by the engine itself, and on account of the positive connection between one element of the switch and the starting gear, all possibility of the jaws of the starting switch sticking is eliminated.


Instructions. Apart from the special adjustments of the starting switch, as mentioned in the description of its operation, the instructions for maintenance are the same as those for other systems. In case this switch does not operate properly, the sequence of operations as mentioned should be checked up, and the distances given verified. In case these distances have become greater through wear, they should be adjusted. To replace the brushes, remove the cover stap over the commutator end of the unit, either generator or motor, put the two screws holding the rocker disc in place, disconnect the brush leads, and withdraw the brushes from the holders. It is important that the brushes slide freely in the holders and that the brush-lead terminals are clean and bright before replacing the terminal screws. See that the springs rest fairly on the ends of the brushes and that their tension has not weakened. Follow instructions given in connection with other systems for care of the commutator.

Failure of Engine to Start. When the starting motor cranks the engine after the starting pedal is depressed but fails to start the engine after a reasonable time, release the starting pedal and ascertain the cause, which may be due to the following: Ignition off, lack of fuel, fuel supply choked, cylinders needing priming due to weather conditions, or cylinders flooded from too much priming.

Should the starting motor fail to crank the engine when the starting pedal is fully depressed, there is a possibility that the battery is run down (which condition will be indicated by an excessive dimming of the lights), that there is a loose connection in the starting circuit, or that the starting switch is not making proper contact. The various tests previously given will probably take care of all these conditions.

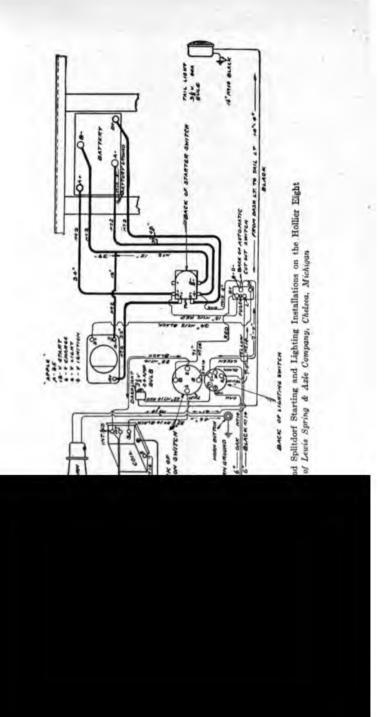Oiling of Starting Motor. The starting motor should be oiled once every 500 miles with any medium high-grade oil by applying oil to the cups, switch rods, guide rods, and pawl; also on the compensating device. Starting motors equipped with the Bendix drive are fitted with oil cups at each end of the unit.



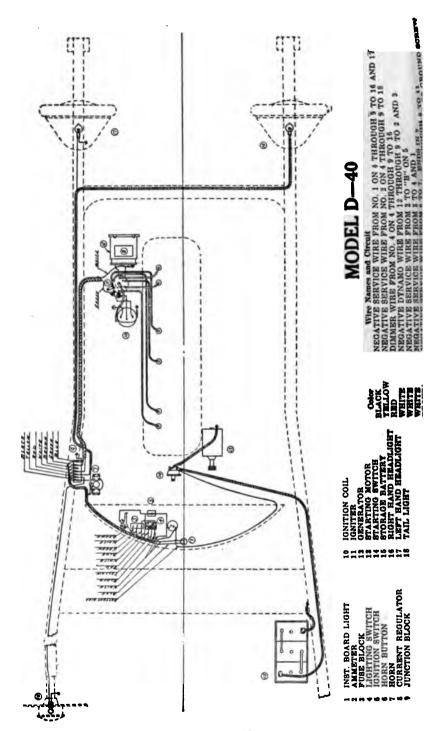

## U.S.L. SYSTEM

Twenty-Four—Twelve-Volt, and Twelve—Six-Volt; Single-Unit; Two-Wire

Variations. The 24—12-volt signifies that the starting voltage is 24 and the generating voltage 12, the battery of twelve cells being divided into two groups of six each in series-parallel for charging, while 12—6 signifies that the starting voltage is 12 and the generating voltage 6, the 6-cell battery being divided in the same manner.

The foregoing systems will be found on cars prior to, and including, 1915 models. For 1916 and 1917 models, a 12—12-volt system of the same single-unit two-wire type is standard. In this system the complete battery is used for the lighting as well as the starting, so that charging, lighting, and starting are all at the same voltage, using the complete battery of 6 cells for both of the former.

Generator-Starting Motor. The machine is multipolar (either six or eight poles) and is designed to take the place of the flywheel of



One of the advantages of this type of machine, owing to its large size, is its ability to generate an amount of current far in excess of any ordinary requirement. This permits the employment in the inher-

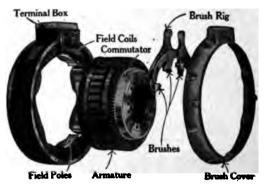


Fig. 330. U.S.I. Inside Armature Type Dynamotor (External Regulator)

ently regulated type of only three brushes, Fig. 331, when the unit is running as a generator, while all the brushes are employed when it operates as a starting motor. In the types equipped with an external

3 Generating Brushes


Fig. 331. Location of Generating Brushes in U.S.L. Dynamotor regulator, all the brushes are employed for generating as well as for starting.

Regulation. The 24—12-volt unit in the U.S.L. system is made with two types of regulation, one type using an external regulator, which is usually mounted on the dash, and the other of the inherent type. The 12—6-volt type has an external regulator. These two types may be distinguished by the presence of the regulator in the charging circuit, which, however, must not be confused with the automatic switch, or battery cut-

out, which is only employed on the inherently regulated type. The details of the regulator are shown in Fig. 332, and it will be noted that the regulator also incorporates the battery cut-out as well as an indicating pointer which shows whether the regulator is working properly or not. In operation, the regulator cuts into the generator field

ircuit a variable resistance consisting of an adjustable carbon pile. The connections of the regulator are shown in the wiring diagrams.


The regulation of the U.S.L. inherent type is accomplished by the combination of a Gramme ring armature, a special arrangement of connections and of the field windings, and the use of only a part of the armature and fields for generating. This method is, of course, special on this make and could not be used on other types of construction. The regulation obtained is based on armature reaction and is similar to that resulting from the third-brush method, but the machine

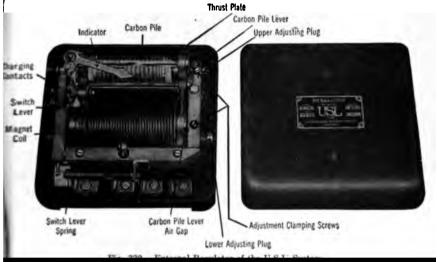

Lower Adjusting Plug

Wiring Diagrams. Figs. 333, 334, and 335 show the standard wiring diagrams of the three types mentioned, being, respectively, the 24—12-volt externally regulated type, the 12—6-volt external regulator and internal-armature type, and the 24—12-volt inherently regulated type. In the diagram proper of each of the 24—12-volt types is indicated the layout for using 7-volt lamps, while the extra diagram at the side shows the method of connecting for 14-volt lamps. The "touring switch" shown on the first two diagrams is a hand-operated switch in the charging circuit and is designed to prevent overcharging of the battery when on long day runs. The inherently regulated type requires very little field current, and on most of these the touring switch is of the miniature push-button type, like a lighting switch.

Touring Switch. On the types equipped with Instructions. the touring switch, this enables the driver to control the charge. Pulling out the button closes the switch and permits the generator to charge the battery when the engine reaches the proper speed; pushing it in opens the circuit. This switch must always be closed before starting the engine, and it must be kept closed whenever the lights are on and also under average city driving conditions where stops are frequent and but little driving is done at speed. When touring, the switch should be closed for an hour or two and then allowed to remain open during the remainder of the day, as this is sufficient to keep the battery charged, and there is no need for further charging until the lamps are lighted. The best indication of the necessity for opening the touring switch is the state of charge as shown by the hydrometer. The driver should not start on a long day's run with the battery almost fully charged, without first opening the touring switch, as the unnecessary charging will overheat the battery. This switch should be inspected at least once a season. Push in the button to open the circuits, remove the screw at the back and take off the cover. The switch fingers should be bright and make good contact with the contact block; if they do not do so, remove and clean them, as well as the contact pieces on the block. Do not allow tools or other metal to come in contact with the switch parts during the operation, for even though the switch is open, a short-circuit may result; then one of the fuses will blow. In replacing the fingers, bend sufficiently to make good firm contact.

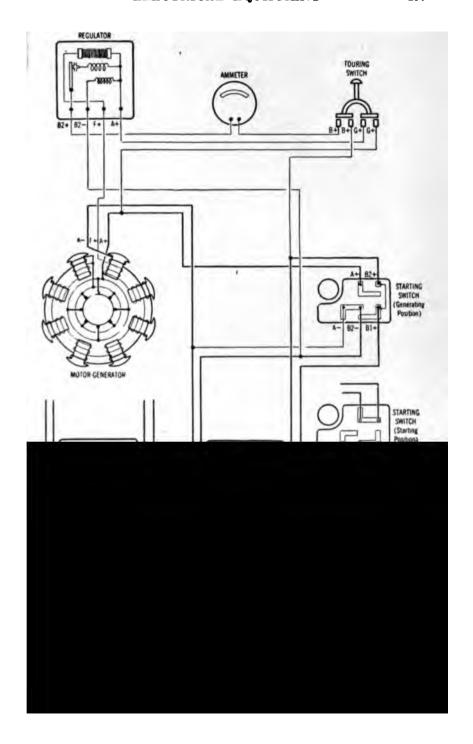


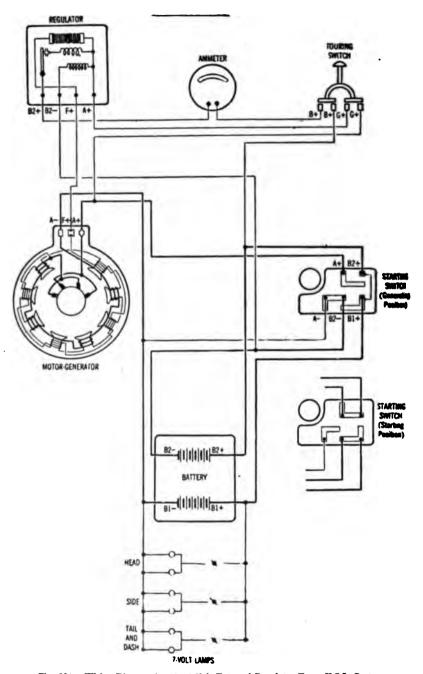


Fig. 334. Wiring Diagram for 12-6-Volt External Regulator Type, U.S.L. System

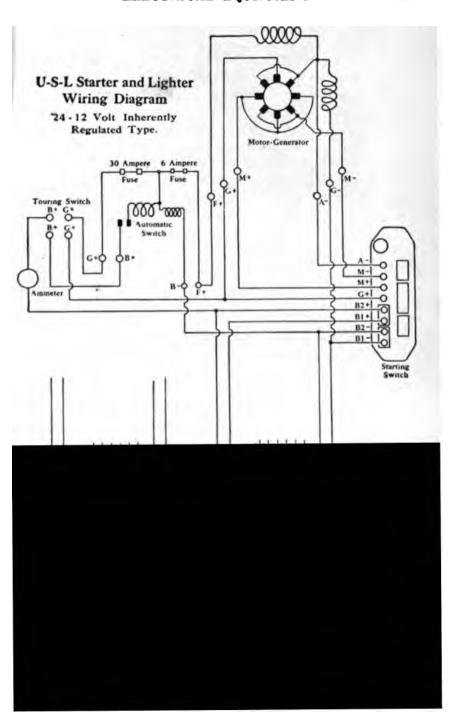

Starting Switch. The starting switch is filled with oil, and this should be renewed once a year. To do this, the switch must be disconnected, and the screws A, Fig. 336, removed; in case the box sticks, insert a screwdriver point between the top of the box and the bottom of the frame and pry loose. To guard against the switch dropping when these screws are removed, hold the hand beneath it while taking them out. Before attempting to remove the switch, disconnect the positive battery connections B1+ and B2+ at the battery as shown in Fig. 335. These are the two main terminals in the center. It is unnecessary to tape them, as a short-circuit cannot occur. Pour out the old oil, clean out thoroughly with gasoline, allow to dry, and refill with transformer oil or light motor oil to the proper level with the switch box standing plumb. The proper height on the Type E-2 or E-3 box is  $1\frac{5}{2}$  inches, on E-4 box  $2\frac{3}{4}$  inches. Before



Fig. 336. U.S.L. Oil-Filled Starting

putting in the new oil, however, the drum and finger contacts should be examined, and, if pitted or dirty, should be cleaned with a fine file. Make sure that all fingers bear firmly against the drum so as to make good contact; if they do not, remove and bend them slightly to


insure this. If the starting switch is abused in operation, or if improper oil containing water or other impurities be used, the contacts will burn and fail to make good electrical connection. The switch box is the only place in the system requiring oil.

Brush Pressures. There is only one adjustment on the generator, viz, the tension of the brush fingers. The brushes should fit freely in their holders so as to transmit the full pressure of the spring against the commutator. The adjustment as made at the factory should not need correction under one or two years of service. Pressures required on the various machines are as follows: for Type E-12 external regulator,  $1\frac{3}{4}$  pounds on each brush;  $1\frac{1}{4}$  pounds on brushes of all other external-regulator machines;  $1\frac{3}{4}$  pounds on each of the three lowest brushes on the inherently regulated type, these being the only brushes used in generating the charging current;  $1\frac{1}{4}$  pounds on each of the remaining brushes of the inherently regulated generator. Keep commutator clean, as the chief cause of


ilure of the inherently regulated type is an excess of oil or dirt or oth accumulating on it.

Radial and Angular Brushes. The brushes employed are of two pes—radial and angular. Radial brushes are used on external-gulator type generators other than those having "Type E-49" on e name plate; angular brushes are used on Type E-49 and all inheritly regulated generators. Each radial brush should bear squarely ainst that side of its holder toward which the commutator rotates.

ach angular brush should ear squarely against that de of its pocket away from hich the commutator tates. [To sand-in old ushes or fit new brushes operly, insert a strip of o. 00 sandpaper (never use nery, paper, or cloth), beveen the commutator and the brush, press down on p of brush and draw sandpaper under it, Fig. 337. If the brush is radial, draw the ndpaper in the direction commutator rotation; if

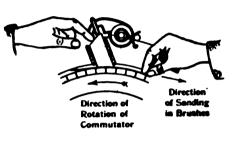

Angular Brush

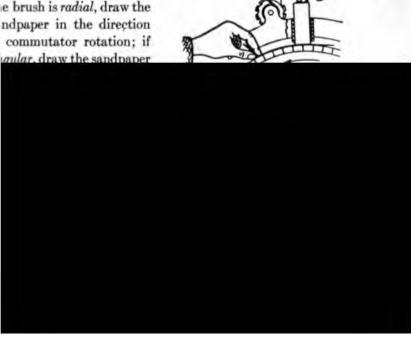






by the switch lever in closing, and when it appears in to through the sight glass on the cover, the battery is the switch lever opens, the pointer drops against its st


When the battery shows a lack of capacity, the and all connections and fuses being in good condition amount of charging current indicated by the amount maximum current (external-regulator type) shown by does not exceed 10 to 12 amperes at full engine spengine has been running for fifteen minutes, see the and commutator are in good condition—wipe off the with a dry cloth, and, if necessary, sand-in the brushes If this does not increase the generator output as ammeter, test the latter as already noted, i.e., see whet is binding and, if not, check with the portable test or another ammeter of the dash type. Should none dies correct the fault, screw in the lower adjustine carbon-pile lever slowly, noting the effect on the are as the adjustment is made.

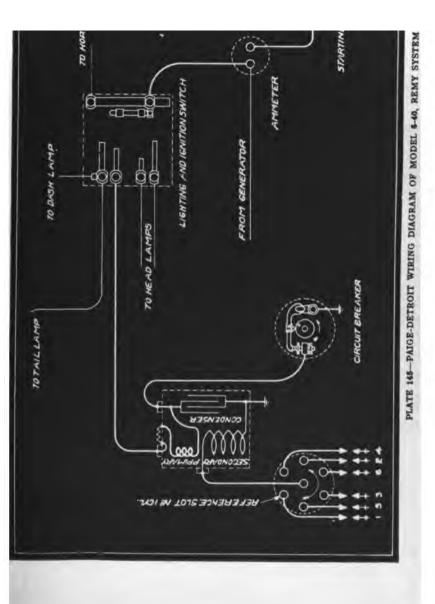
With the external regulator, the charging curre exceed 18 amperes at the highest engine speed. If the ammeter shows a higher reading than this, screw adjusting plug of the carbon-pile lever slowly to decrent, stopping when the indication does not go about full enough




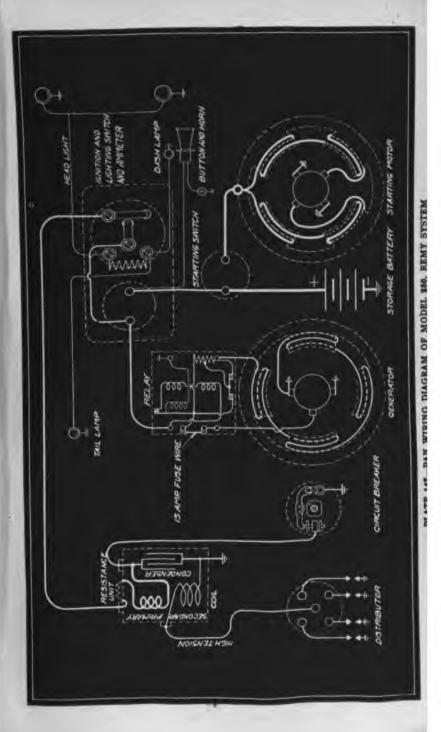


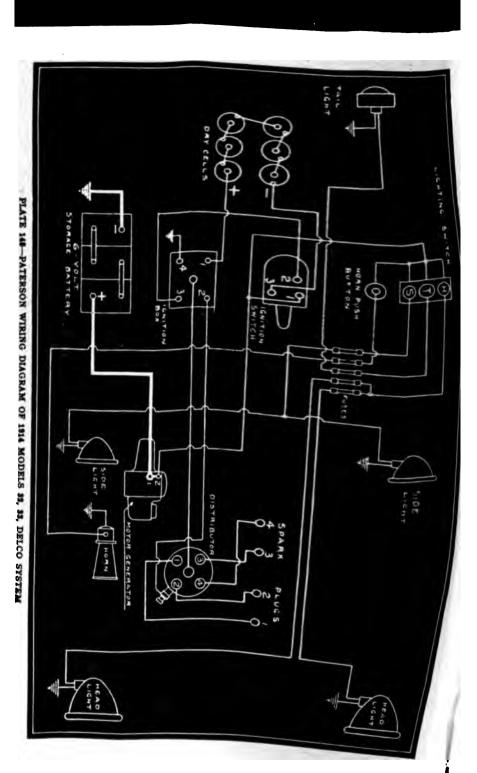


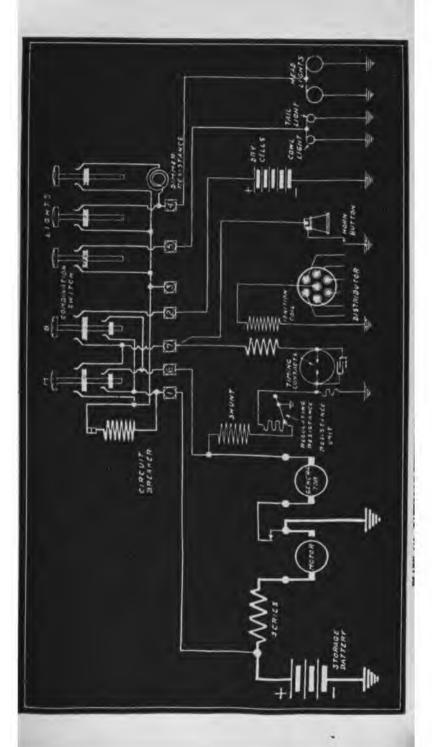

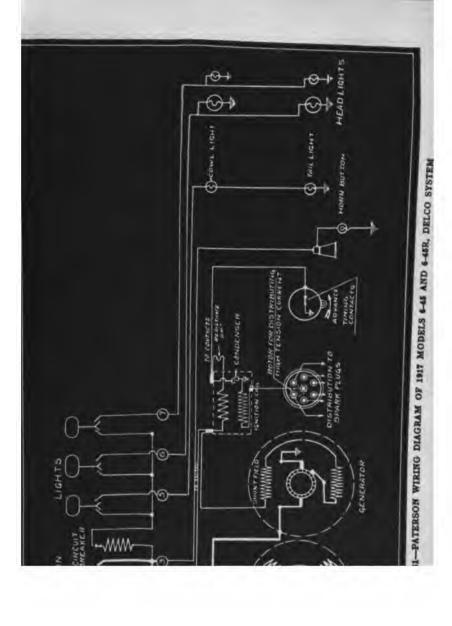


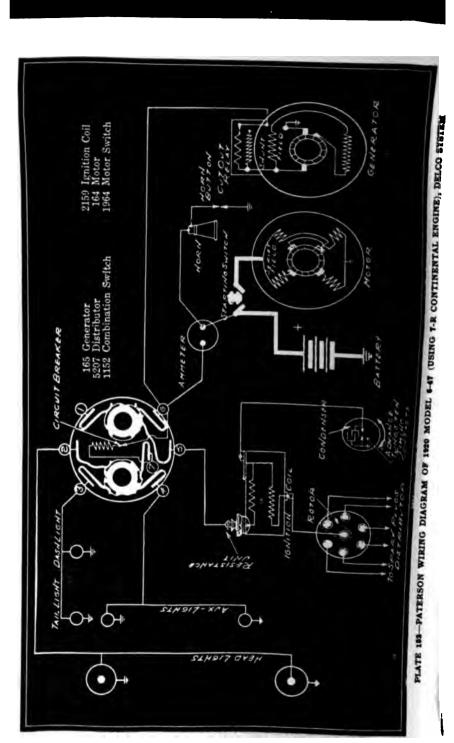


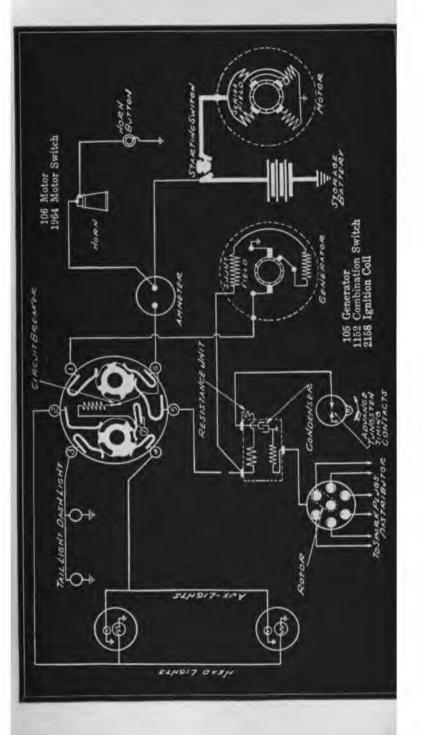


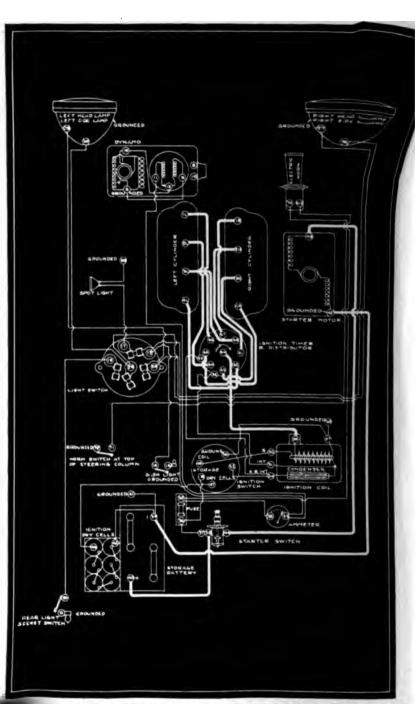


M-PEERLESS WIRING DIAGRAM OF 1917 SERIES 2, 3, AUTO-LITE SYSTEM

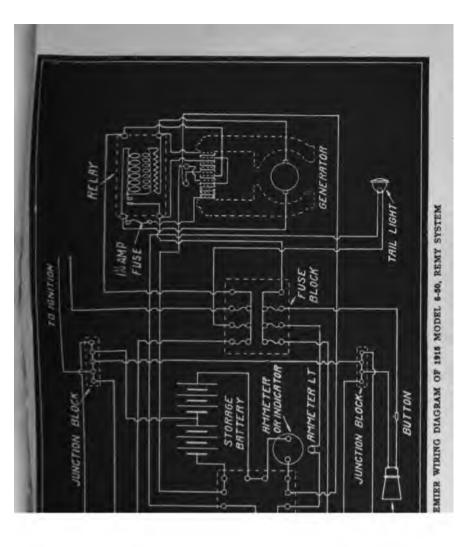

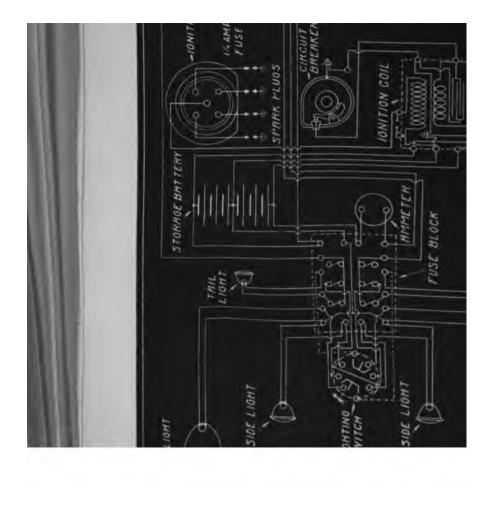

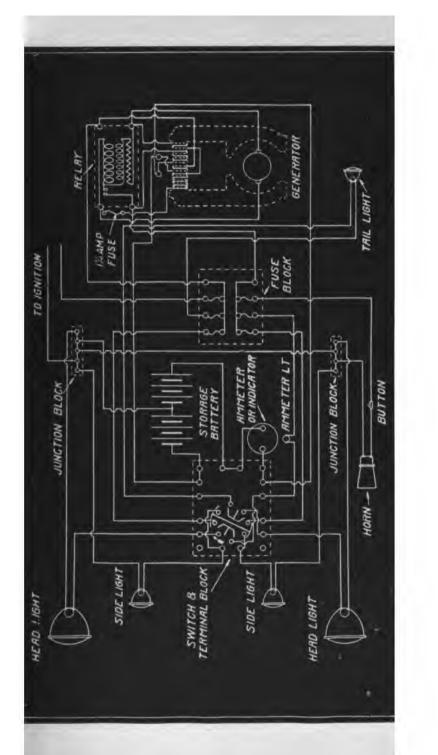

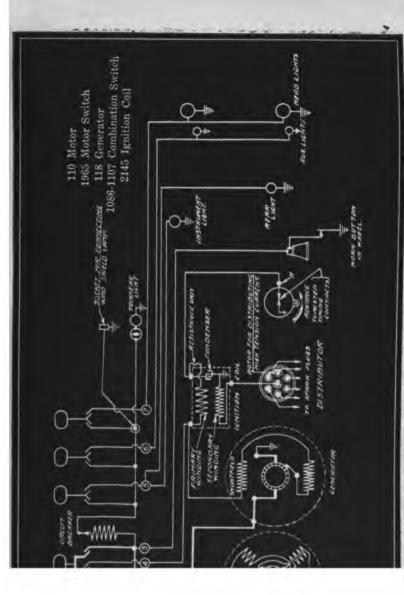

LATE 189-PREMIER WIRING DIAGRAM OF 1919 MODELS 6-8, 6-C, DELCO SYSTEM

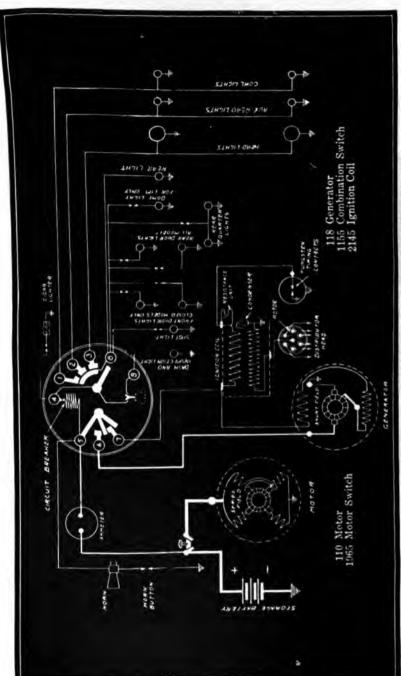



PLATE 146-PREMIER WIRING DIAGRAM OF 1910 MODEL 4-D, DELCO SYSTEM

8 8


adjustment clamping screws after setting either of the adjusting

Testing Carbon Pile. If the automatic-switch unit of the generr does not cut in with the engine running at speed equivalent to 10
14 miles per hour, test the carbon pile by short-circuiting the
ninals F+ and A+ of the generator with the blade of a screwrer. Speed up the engine slowly and note whether the generator
s in much sooner than when the terminals are not short-circuited.
not run the engine at high speed, nor for any length of time with
terminals short-circuited, as an excessive amount of current
ald be generated. If the generator does cut in much earlier
h the terminals short-circuited than without this, the carbon pile
ds cleaning. Should the generator not cut in earlier or should
ail to operate altogether, when the carbon pile is short-circuited
trouble is probably in the brushes of the generator or in the
ring switch.

To clean the carbon pile, proceed as follows: Unscrew the plug he upper end of the glass rod and remove the rod; if any of the discs pitted or burned, rub them together or against a smooth board to ce them smooth and flat. Remove the end carbons and clean the ss plates with fine sandpaper, if necessary. In replacing end cars, make sure that they fit firmly against the brass end plates and t the screw heads do not project beyond the faces of the carbon s. After reassembling the carbon pile, the regulator will need astment for current output, as previously noted.

 

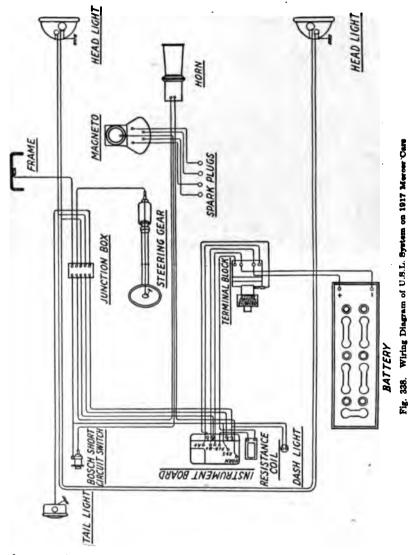
of known accuracy. To do this, disconnect the positive wire from the ammeter on the dash and connect it to the positive terminal of the standard ammeter used for testing; then connect a wire between



the negative terminal of the standard ammeter and the positive terminal of the dash ammeter. With the engine running at various speeds, take simultaneous readings of both instruments; any differbetween the two should be taken into consideration thereafter n reading the dash ammeter. Unless a test of this kind is carried the battery may be receiving either an insufficient or an excessive rge while the ammeter indicates the proper amount.

U.S.L. 12-Volt System. The U.S.L. 12-volt system generates

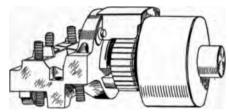starts at 12 volts and is idard on the 1916 and 7 models of the Mercer. 338. It differs from the er systems in having a metically operated startswitch and a centralized trol unit, which incor-



U.S.L. Type E-14 Starting Switch

ites all the controlling devices of the entire system, the cut-out, ammeter, fuse blocks for generator and lighting circuits, starting ch, touring switch, head, side, and tail-light switches, all of ch are operated by push buttons. All of these switch buttons, rell as the fuses, are locked in place, while the buttons may be ed in any desired combination of positions.

Starting Switch. This is of the magnetically operated type and ounted on the top of the field-mounting frame. It operates by

ns of a solenoid and ger, as illustrated in Fig.

Control is by means of ring push button on the



fuses, a large one 9 of 30-ampere capacity in the generator-battery charging circuit, and a smaller one 8 of 5-ampere capacity in the generator shunt-field circuit. Should either fuse blow, immediately push in the touring-switch button, as a short-circuit or an open or a

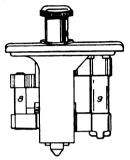


Fig. 341. U.S.L. Generator Fuse Block

loose connection is probably the cause. After locating the trouble, remove the generator fuse block from the instrument board. To do this, unlock the knob, press it inward, and turn ½ revolution to the right or to the left. Replace with spare fuses carried in the light fuse block, return the generator fuse block to its original position, and lock.

The light fuse block, which is shown in Fig. 342, carries a total of seven fuses, of which four are in active use, while the remaining three

are spare fuses for use in replacing blown fuses. On the right-side view of this fuse block there appear two large fuses 6 and 7. Fuse 7 is a protecting link in the ground-return wire of the lighting and horn circuits. The small fuse 5 is of 10-ampere capacity and, together with



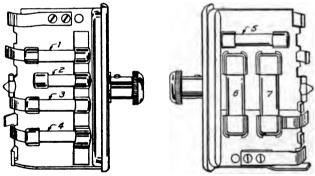


Fig. 342. U.S.L. Left-Hand Side and Right-Hand Side Light Fuse Blocks

fuse 6 of 30-ampere capacity, is a spare fuse for emergency use. On the left side of the block are three active fuses 1,3, and 4 of 10-ampere capacity; and one spare fuse 2 of 5-ampere capacity. Fuse 1 is in the horn circuit, fuse 3 in the headlight circuit, and fuse 4 is common to the tail-, dash-, and side-light circuits. Should any of the fuses on this block blow, the trouble is probably a short-circuit on the frame of the car which should be remedied before the fuse is replaced. Instructions

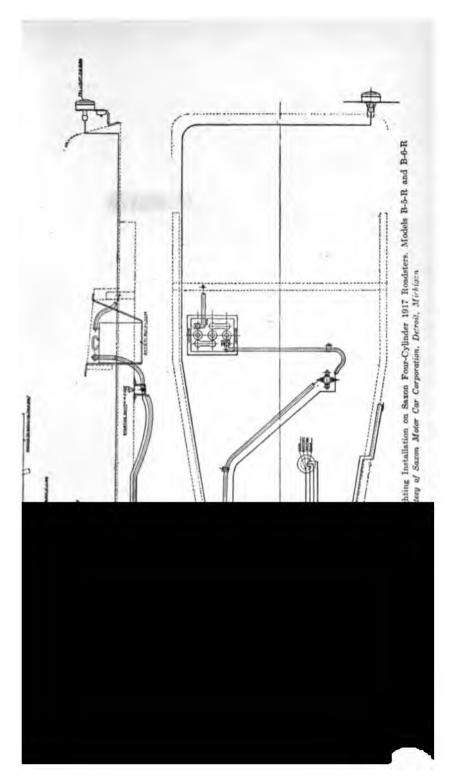

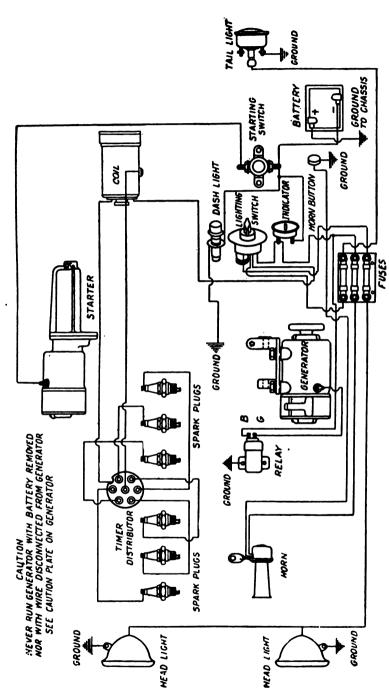

Wagner Ignition, Starting, and Lighting Installation on Saxon 1917 Six-Cylinder Cars, Models S-3-T, S-4-T and S-4-R Courtesy of Saxon Motor Car Corporation, Detroit, Michigan

Ĉ

1

for the use of the touring switch in this system are the same as previously given.

U.S. Nelson System. This type has been specially designed for the Nelson car, which first appeared in 1917, and it differs radically from those already described in that it is carried on the forward end of the engine crankshaft instead of at the rear. The brushes bear on the inside face of the commutator and may be reached through three openings in the armature support. To clean the commutator in this type, it is necessary to turn the armature so that three of the six brushes appear opposite these openings. Fold a small piece of sandpaper into a square over one of the brushes and allow the engine to turn over for a few minutes. Stop the engine and remove the sandpaper through one of the openings. The engine carries a flywheel at the rear, as usual, and this provision of flywheel weight at both ends of the crankshaft is said to minimize vibration almost to the vanishing point while making possible extremely high speeds.

## WAGNER SYSTEM

Twelve-Volt; Single-Unit; Two-Wire (Early Model)

Dynamotor. The bipolar-type dynamotor has both the series and the shunt-windings, i.e., of generator and motor, connected to the same commutator. It is driven direct as a generator, and through a special planetary gear when operating as a starting motor.

Regulation. The regulation is of the inherent type, utilizing

the switch connect the generator for charging. Fig. 345 shows the details of this switch: A, B, and C are the contacts on the starting side, while H, G, and F are the running-position contacts, as shown in Fig. 343. The segments E and L on the drum contact with


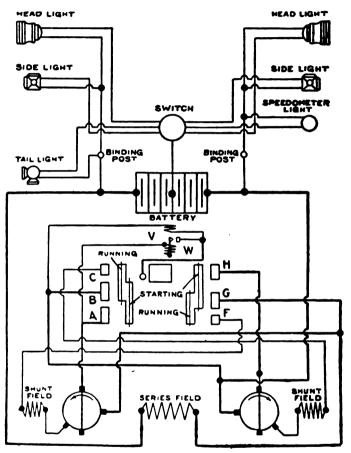


Fig. 343. Wiring Diagram for Wagner Twelve-Volt Single-Unit Two-Wire System (Early Model)

the fingers mentioned when the drum is revolved part way in either direction by the lever, shown at the right, which engages the shaft M.

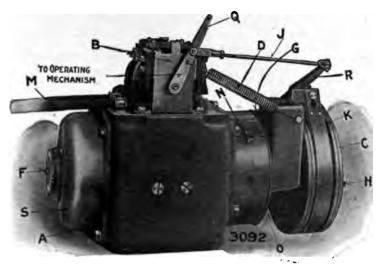Battery Cut-Out. This is of conventional design. For description and explanation of operation, see previous systems in which a battery cut-out, or automatic switch, is employed. Methods of locating trouble are given in connection with instructions farther along.



ig. 344. Wagner Control Switch of Drum Type. A—Starter Frame; B—Switch Support; C—
Outside End Plate Gear Box; D—Return Spring; F—Oil Hole Screw; G—Self-Closing Oiler;
H—Oil Plug; J—Connecting-Rod; K—Brake Band; M—Battery Leads; N—End Plate Screws;
O—Back End Plate Shield; Q—Starting Switch Lever; R—Brake Band Lever; S—Front End
Plate Shield

Courtesy of Wagner Electric Manufacturing Company, S. Louis, Missouri



Planetary Gear. The external form of the different gear boxes used on the early-model single-unit Wagner starter is the same, but

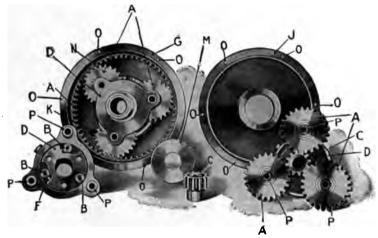


Fig. 346. Exploded View of Planetary Gear Transmission. A—Planetary Pinion; B—Rollisg Pawl; C—Center Pinion; D—Planetary Hub; E—Pawl Seat; F—Pawl Plunger; G—Internal Gear; H—Inside End Plate; J—Outside End Plate; K—Oil Plug; M—Sheet-Steel Disc

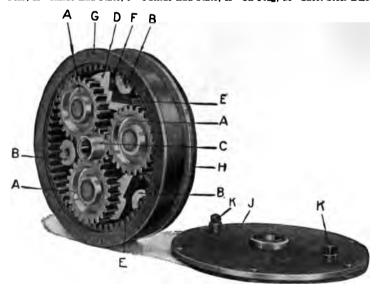


Fig. 347. Assembled Planetary Gear. Letters same as Fig. 346

their internal construction differs somewhat. The details of the two types employed are shown in Figs. 346 and 347. The principle employed is that of the planetary gear as used to obtain first,

or low, and high speeds on early-model light cars. The unit consists of a central, or sun, gear C, Fig. 347, and three planet pinions A meshing with the central gear and also with the internal gear ring G. For starting, the tightening of the brake band on the outer groove of the internal gear holds it fast, so that the drive is through the central gear and the reducing pinions in engagement with it and the gear ring, while, for running, the rollers B in the clutch D lock the gears together so that when generating the gear revolves idly as a unit.

Instructions. The instructions previously given in connection with other systems apply here. For failure to generate, lack of capacity, grounds, or short-circuits in windings, and for keeping the

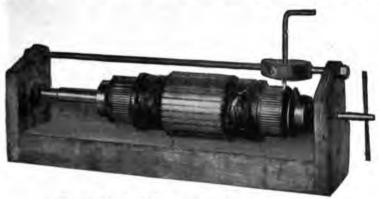


Fig. 348. Jie for Holding Armature and Tooling Commutator

forward on its guide in the same manner as a planer or shaper tool, and the armature is rotated one segment at a time to bring the mica sections under the tool successively. Where there is not sufficient work of this nature to make it worth while to build the jig, a simple

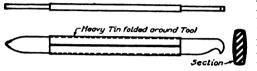


Fig. 349. Diagram of Simple Hand Device for Tooling Commutator

hand tool may be used, Fig. 349. This can be made of a discarded hacksaw blade or a new one, about 8 inches long. One of the ends is

ground similarly to the cutter described for the jig, while the other should be shaped like a hook, having the same kind of point as the cutter end. Around the center of this tool should be folded a piece of heavy tin (sheet iron) and the whole wrapped with electric tape. This will prevent the brittle saw blade from breaking and make it much easier to handle. The mica is removed by forcing the sharp end of the tool from the outer edge of the commutator surface to the inner edge, and the rough cut thus made is finished by drawing the hooked end of the tool back through the groove in the opposite direction. To do the job properly, the armature should be held in a vise, otherwise it is liable to move, or the tool is liable to slip, and the copper be cut away with very poor results. Fig. 350 shows the commutator

before and after undercutting the mica.

A needle-pointed

A needle-pointed tool should never be used, as it will simply, make a V-shaped cut in the mica, removing too much in depth and not enough in width. The mica must be cut out clean and square, and a small magnifying glass should be used to see that all of the



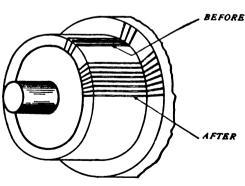


Fig. 350. Diagram Showing Commutator Sections before and after Tooling

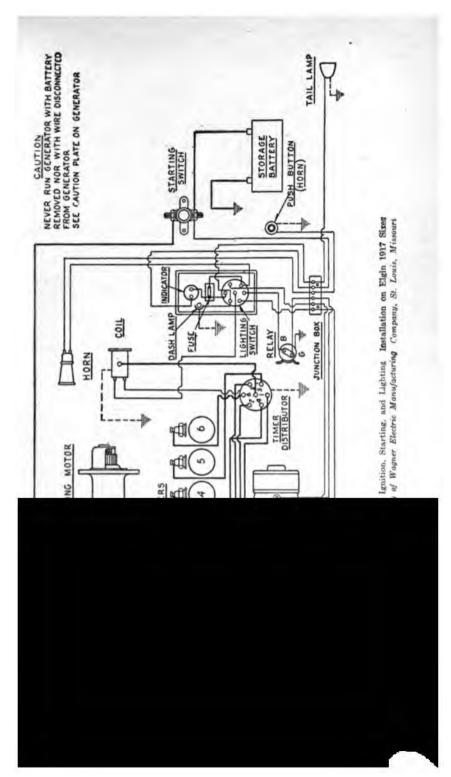the commutators, i.e., just enough to remove all roughness



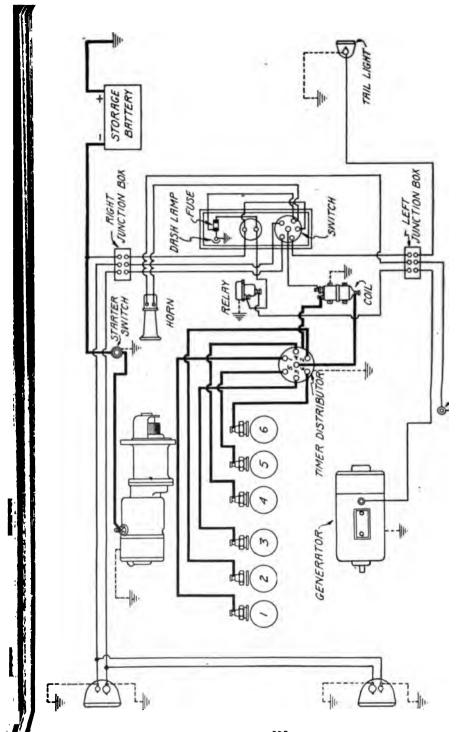

and flat spots. The cutting tool employed should be very sharp, so that the soft copper will not be dragged from one segment to another. After turning, fine sandpaper should be used to smooth the commutator. Whether the brushes are replaced with new ones or the old ones are retained, they must be sanded-in to the commutator (see Delco instructions). The springs also should be tested for tension; they must never be allowed to become loose enough to permit the brushes to chatter when the generator is running, as this would interfere seriously with its output.

Lack of Capacity through Faulty Gear Box. Should the battery not charge properly, note whether in starting the lights brighten



probably is in the gear box. Remove the front end plate and note if the commutator is rotating. If not, and the reason therefor is not apparent on an inspection of the gears, it may be necessary to remove the gear box. A "come along", such as is employed for taking off Ford wheels, is necessary for this, Fig. 351. It may be found that some of the parts need replacement, or that an entirely new gear


3102 G H


Fig. 352. Details of Wagner Starting Switch. A and B—Large Contact Finger; C—Auxiliary Contact Finger; D—Auxiliary Contact; E—Drum Switch; F, G, and H—Drum Switch Studa; J—Screw Leading to C; Q—Starting Switch Lever

box is necessary. Failure Due to Battery Cut-Out. If the failure to charge the battery be not due to the gear box. remove the cover of the cut-out and see if it is operating properly. When the engine is running at a speed equivalent to 15 miles per hour, the contact should spring away from the adjusting screw. If it does not, connect a voltmeter across the terminals B and H of the switch, Fig. 352. Should the voltmeter needle not move, examine

the contact fingers connected to the studs C and F and see that they make firm contact with the drum of the switch. Place the end of a pencil on the contact finger D and bear down lightly; if the main contact maker then springs away from the adjusting screw, the cause of the trouble is an open circuit at this contact. Bend D so that it bears down on the drum segments; should the contacts not close on making this test, the trouble will be an open connection, either in the generator itself or between the generator and the cut-out (switch).

PLATE 161-REGAL WIRING DIAGRAM OF 1917 MODEL J, HEINZE-SPRINGFIELD SYS

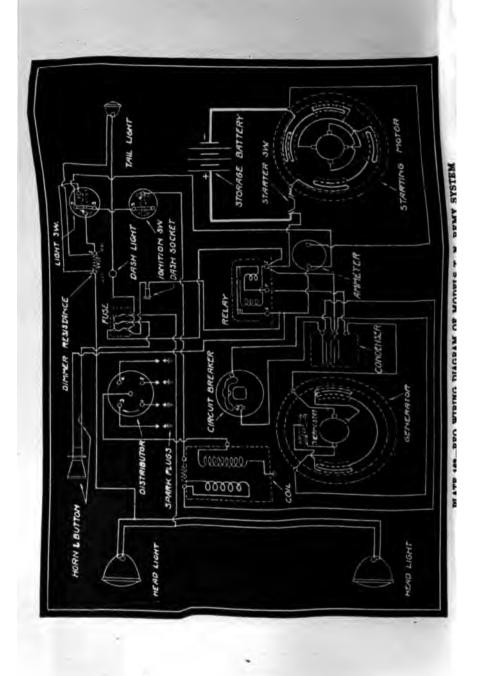

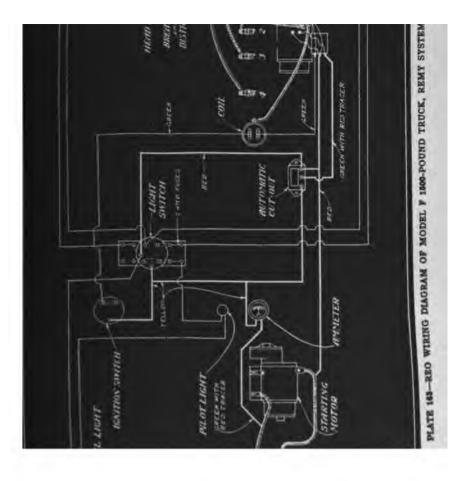





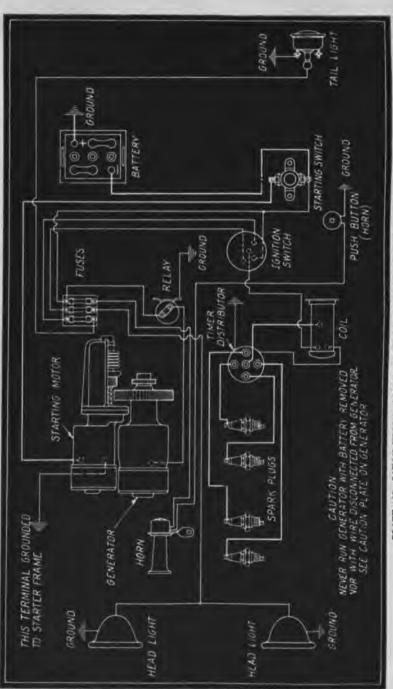


PLATE 165-SAXON WIRING DIAGRAM OF 1916 MODEL 14, WAGNER SYSTEM

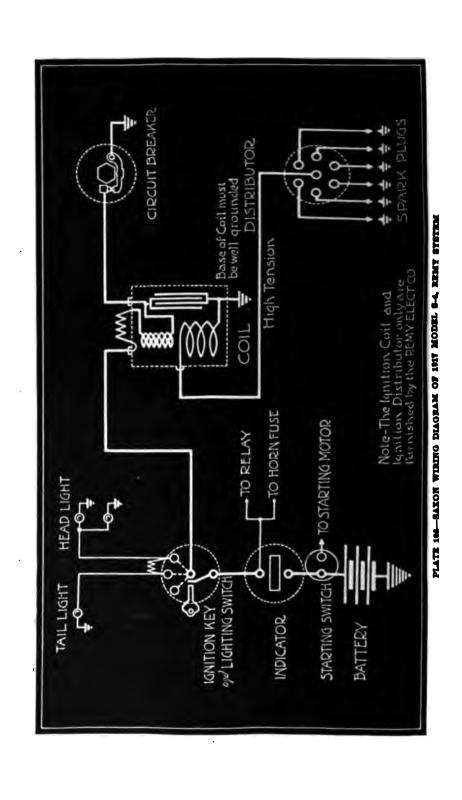

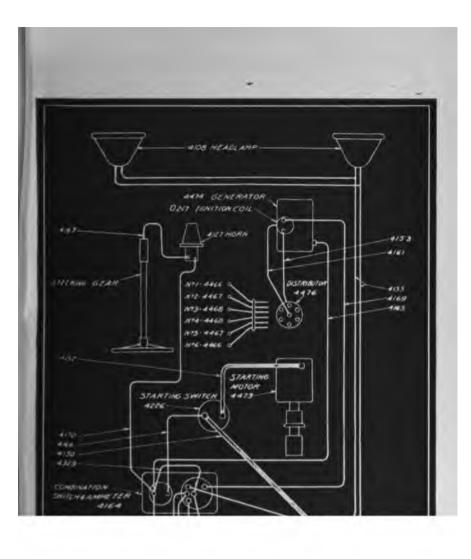

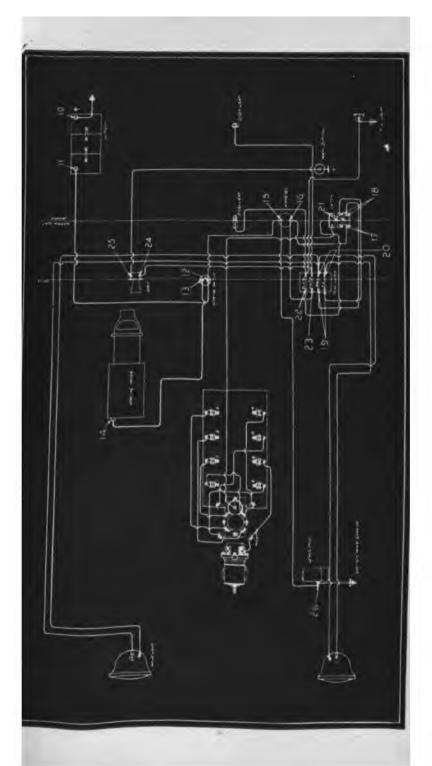

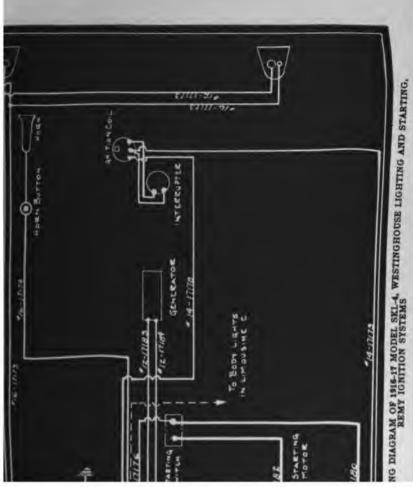

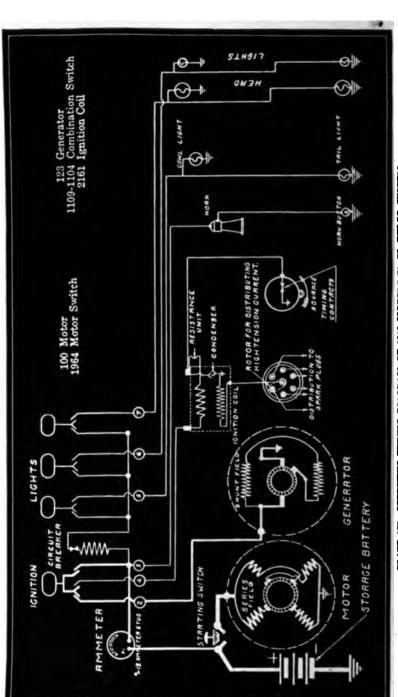


PLATE 179-STEPHENS WINING DIAGRAM OF 1919 MODELS 76, 76, DELCO STETEM

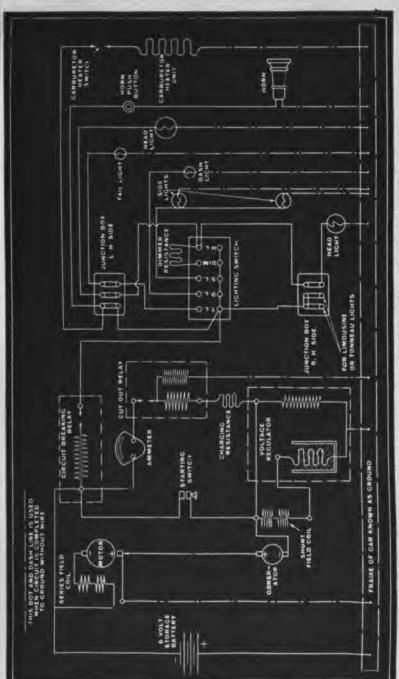


PLATE 173-STEVENS-DURYEA WIRING DIAGRAM OF 1915 MODEL D6, DELCO SYSTEM (INTERNAL)

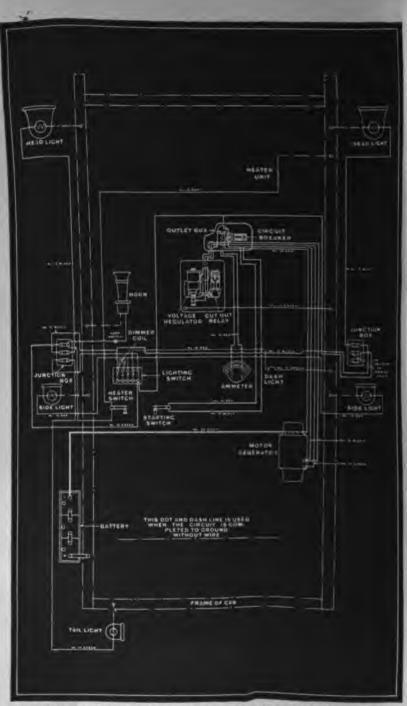


PLATE 174-STEVENS-DURYEA WIRING DIAGRAM OF 1915 MODEL D6, DELCO


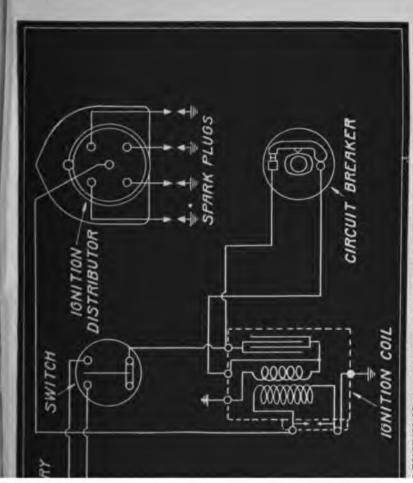


DIAGRAM OF 1914-15 MODELS, GROUNDED BATTERY, REMY IGNITION SYSTEM

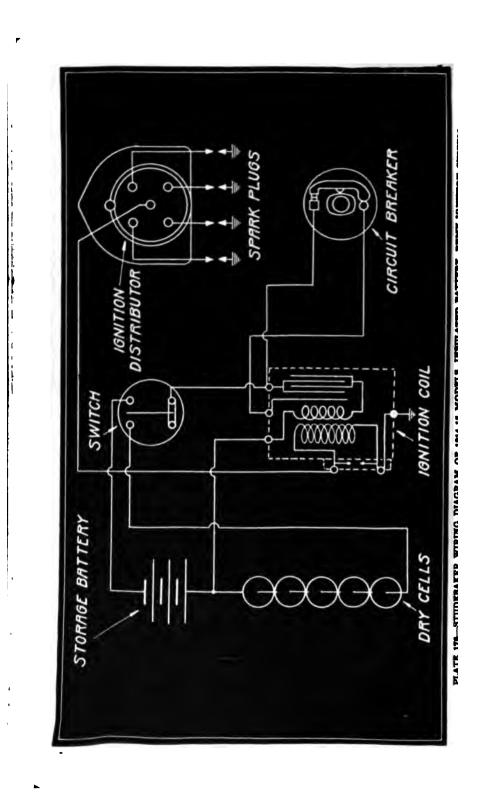

Should the voltmeter give a reading of 6 volts while the contacts do not close, it shows that the shunt coil of the cut-out is open and indicates that its connections are broken or that the trouble is in the coil itself. This may be confirmed by operating the contacts by hand—pushing the contact away from the adjusting screw until it touches the stationary contact. If it remains in that position, the generator is charging the battery, but the shunt coil of the cut-out is out of action and the cut-out will function automatically as it should.

If, under the conditions mentioned in the first paragraph under this heading, the cut-out closes, connect the voltmeter as described and accelerate the engine to a speed corresponding to 25 miles per hour. If the reading is then 15 to 20 volts, the trouble may be looked for in a break in the generator connection to the cut-out. Should it not be possible to locate any break, it may be in the series coil of the cut-out, in which case a new cut-out will be necessary.

Switch or Generator Parts to Be Adjusted. If the starting lever of the switch is not returning to the proper position for running after starting the engine, it will be indicated by a low battery and dim lights. Adjust so that the lever will go to correct position for running and see that the contact fingers of the switch are making proper contact with the drum.

In case the battery does not get sufficient charge, connect an ammeter to the terminal D of the switch and to W of the cut-out. At a speed equivalent to 15 miles per hour, the ammeter should read 7 to 9 amperes if the generator is working properly. If it does not, examine the commutator, brushes, and wiring, as previously described.

#### Six-Volt: Two-Unit

General Characteristics. This type is similar in characteristics to most of the other makes of this class already described.

Generator. The generator is the multipolar (four-pole) shunt-wound type.

Regulation. The regulation is of the inherent or bucking-coil type, integral with the field windings of the generator.

Starting Motor. The motor is four-pole and series-wound, driving through a reducing gear mounted on the motor housing, Fig. 353.

Control. Battery Cut-Out. The complete instrument, minus its cover, is shown in Fig. 354. It is of standard design and is intended

to be mounted in the tool box under the driver's seat. As shown in the photograph, the upper binding post is the series-coil connection, the central binding post just below it is the shunt-coil connection.





Fig. 353. Wagner Six-Volt Two-Unit Type Starting Motor. Left—Commutator End; Right—Gear End Courtesy of Wagner Blectric Manufacturing Company, St. Louis, Missouri

while the lowest binding post is a connection completing the circuit through both coils to the battery.

Switch. The switch is of the circular knife-blade type, two sets of spring contacts close together being pressed down over the stationary contact against the spring, as shown in Fig. 355 which illus-

trates the parts of the switch.

switch.

Wirt
typical w
the Wag
tem as i
Scripps-I
eight-cyl
shown ir
only dir
wiring of

Fig. 354. Wagner Cut-Out


Wiring Diagram. A typical wiring diagram of the Wagner two-unit system as installed on the Scripps-Booth four- and eight-cylinder models is shown in Fig. 356. The only difference in the wiring of the two models has to do with the igni-


tion and merely affects the distributor connections, as illustrated by the panel in the upper right-hand corner, which shows the distributor and connections for the four-cylinder car. As the system is a singlewire type, one side of every circuit is grounded, the spark plugs themselves representing the grounded side of the high-tension ignition Should the voltmeter give a reading of 6 volts while the contacts to not close, it shows that the shunt coil of the cut-out is open and indicates that its connections are broken or that the trouble is in the will itself. This may be confirmed by operating the contacts by and—pushing the contact away from the adjusting screw until it touches the stationary contact. If it remains in that position, the generator is charging the battery, but the shunt coil of the cut-out is sut of action and the cut-out will function automatically as it should.


If, under the conditions mentioned in the first paragraph under this heading, the cut-out closes, connect the voltmeter as described and accelerate the engine to a speed corresponding to 25 miles per hour. If the reading is then 15 to 20 volts, the trouble may be cooked for in a break in the generator connection to the cut-out. Should it not be possible to locate any break, it may be in the series coil of the cut-out, in which case a new cut-out will be necessary.

Switch or Generator Parts to Be Adjusted. If the starting lever of the switch is not returning to the proper position for running after starting the engine, it will be indicated by a low battery and dim lights. Adjust so that the lever will go to correct position for running and see that the contact fingers of the switch are making proper contact with the drum.

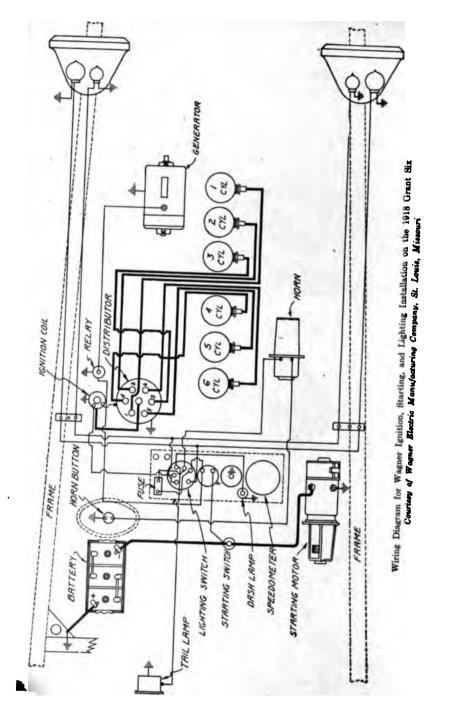In case the battery does not get sufficient charge, connect an immeter to the terminal D of the switch and to W of the cut-out. It a speed equivalent to 15 miles per hour, the ammeter should read



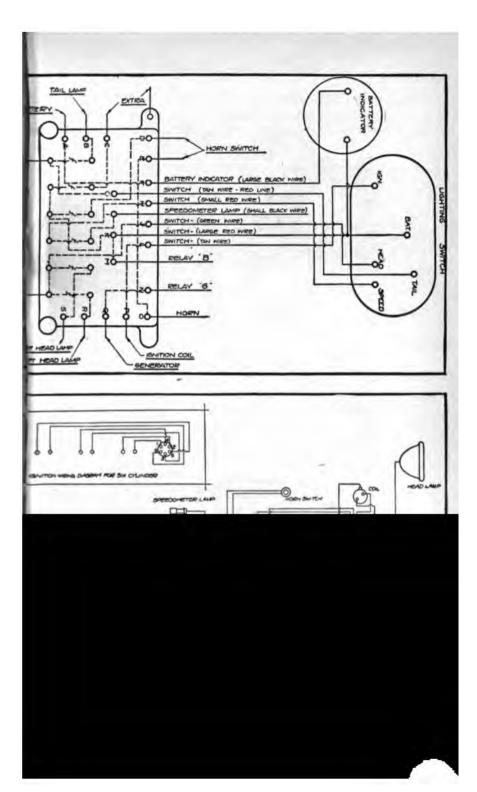

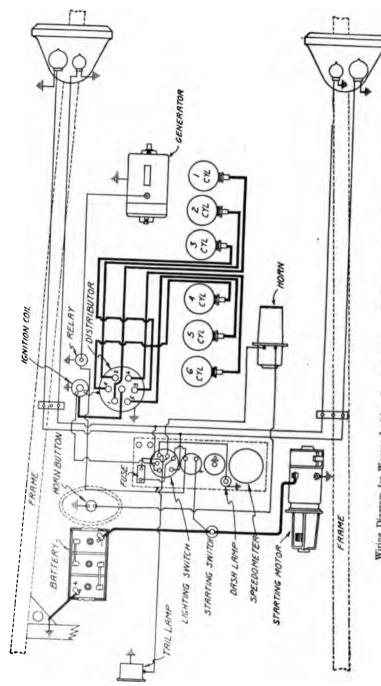

Wiring Diagram for Wagner Ignition, Starting, and Lighting Installation on the 1918 Grant Six Courtesy of Wagner Electric Manufacturing Company. St. Louis, Missuuri


circuit. The caution on the diagram—Never run generator with battery removed from car nor with wire disconnected from generator—applies not only to the Wagner system but to practically every other system as well.

Instructions. Ground in Starting or in Lighting Circuits. When the blowing of a fuse on one of the lighting circuits is due to a ground, or a similar fault is suspected in the starting system, it may be tested for either with the lamp outfit already described or with the lowreading voltmeter, as follows:

Disconnect one battery terminal, taping the bare end to prevent contact with any metal parts of the car, and connect one side of the voltmeter to this terminal. Attach a length of wire having a bared end to the other terminal of the voltmeter, as shown in Fig. 357.



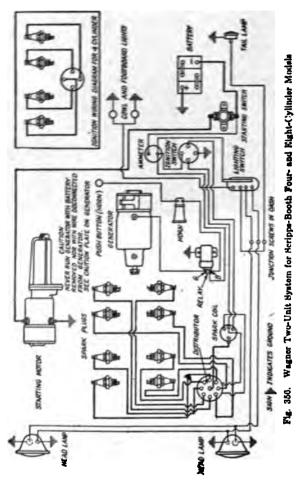volts but more than \( \frac{1}{2} \) volt, all wiring and connections should be carefully inspected for faults. This test should be repeated by reversing the connections, that is, by reconnecting the wires on the side of the battery circuit that has been opened and disconnecting the other side.



Localizing Any Ground. To localize any fault that the reading of the voltmeter may show, reconnect the wires to the starting motor and close the starting switch; any reading of the voltmeter with such connections will indicate that the ground is in this circuit. Should no ground be indicated with these connections, disconnect e starter again and reconnect the generator; if the voltmeter cords any voltage, the ground is in the generator circuit. With oth starter and generator disconnected, the voltmeter being con-


ected first to one side the battery and then the other, operate ic lighting switches, the nition switch, and the orn, one at a time, and the whether the volteter needle moves upon osing any of these vitches. A voltage readg upon closing any of ese switches will indite a ground in that parcular circuit.

Short-Circuit Tests.



Fig. 357. Testing for Grounds with Voltmeter in Two-Wire System

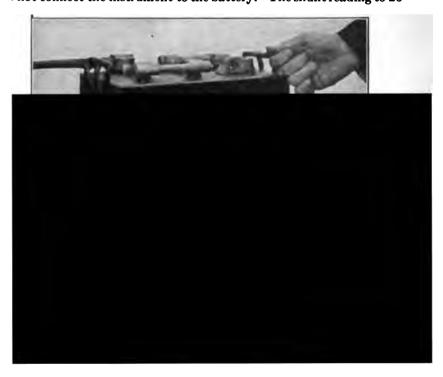o test for short-circuits, substitute the ammeter for the voltmeter, but not connect the instrument to the battery. The shunt reading to 20




tery, Fig. 358. Disconnect the starter and the generator and open all the switches, then touch the bare end of the wire to the battery terminal on the open side as shown. Any reading, no matter how small, will indicate a short-circuit (two-wire system) in the wiring between the battery and junction box or between the latter and the starter, or generator. If the ammeter reading shows a heavy current, there is a severe short-circuit.


Localizing a Short-Circuit. The short-circuit may be localized in the same manner as described for the voltmeter test, i.e., connect the starter and test; disconnect the starter, connect the generator and test. A reading on the generator test may be due to the contacts of the cut-out sticking together. If the cut-out contacts are open and the ammeter registers, there is a short-circuit in the generator windings.


Disconnect the generator again, remove all the lamps from the sockets, and turn on the lighting-circuit switches one at a time, touching the wire to the battery terminal after closing each switch. A reading with any particular switch on indicates a short-circuit in the wiring of the lamps controlled by that switch. Only one switch should be closed at a time, all others then being open. This test should be made also with the ignition switch on but with the engine idle. The ammeter then should register the ignition current, which should not exceed 4 to 5 amperes. If greater than this, the ignition circuit should be examined.


Cautions. Do not attempt to test the starter circuit with the ammeter as it will damage the instrument. To test the starter circuit, reconnect as for operating, removing the ammeter. Close the starting switch; a short-circuit in the wiring will result either in failure to operate or in slow turning over of the engine. See that the switch parts are clean and that they make good contact. If the short-circuit is in the winding of the starting motor, there will be an odor of burning insulation or smoke.

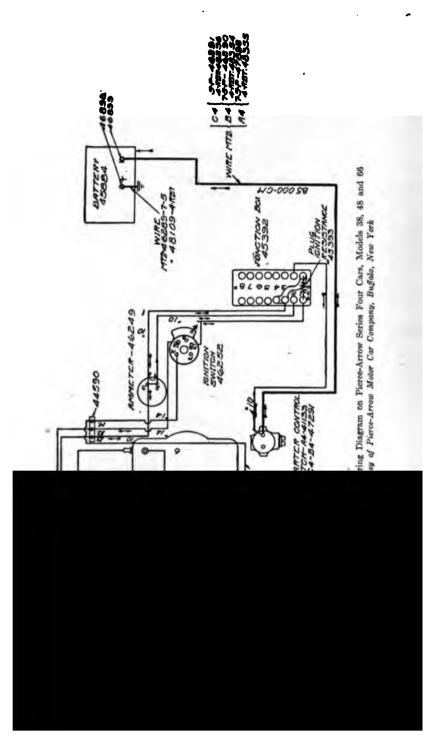The battery must be fully charged for making any of these tests. While the effect either of a ground or of a short-circuit will be substantially the same, its location and the remedy will be more easily determined by ascertaining whether it is the one or the other. Instructions for making these tests have already been discussed in the Gray & Davis section.



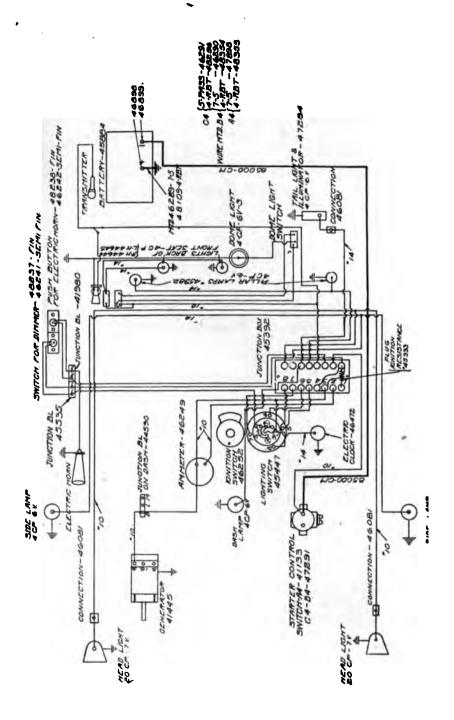

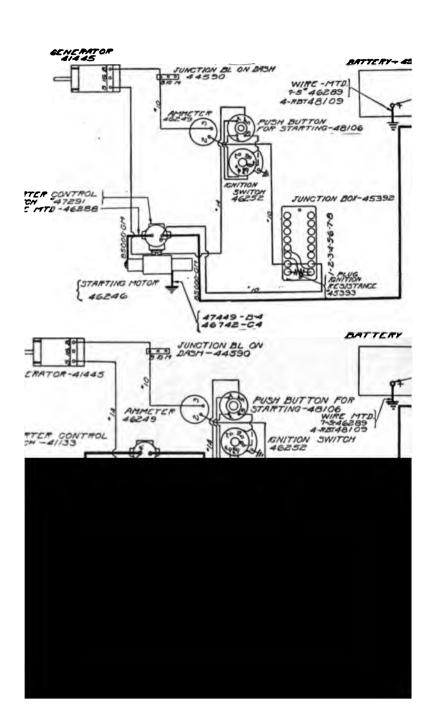


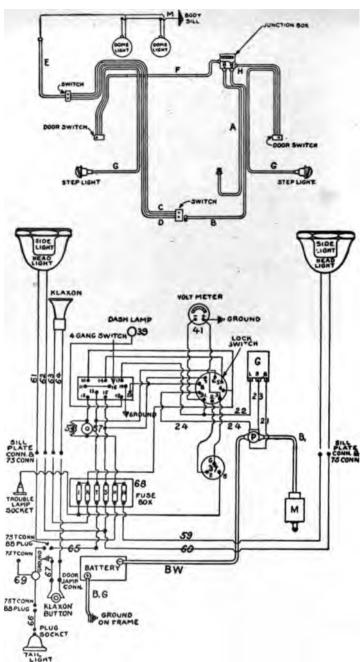


Westinghouse Starting and Lighting Installation on Locomobile Series Two Six-Cylinder Cars, Models 38 and 48. Upper Diagram Layout of Cables on Closed Cars:

Lower Diagram Complete Wiring Circuits for Open Cars

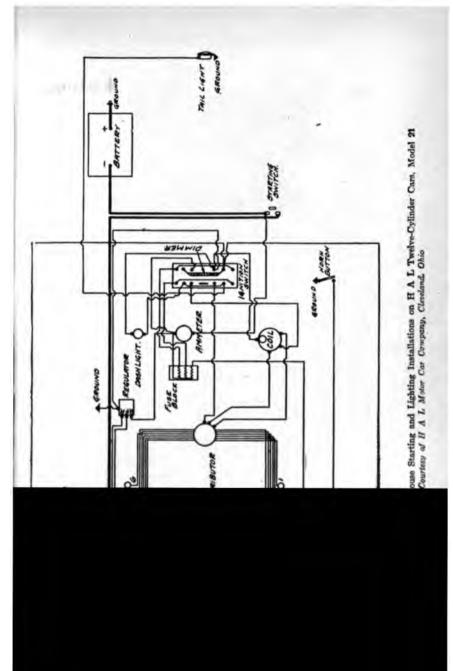Courtesy of The Locomobile Company of America, Bridgeport, Connecticus



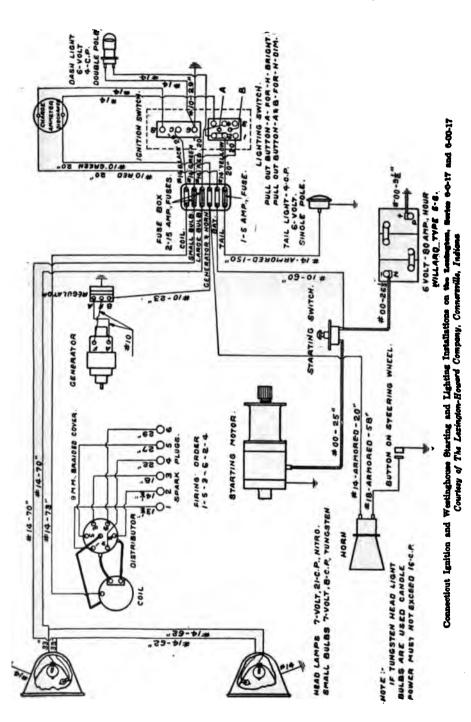

22

## WESTINGHOUSE SYSTEM

## Twelve-Volt; Single-Unit; Single-Wire

Dynamotor. The single unit of the 12-volt system, or the "motor-and-generator" as the manufacturers term it, is a bipolar machine, both the generator and starting-motor windings of which are connected to the same commutator. Installation is usually by means of a silent chain, as on the Hupp (1915 and earlier). The characteristics of this type of machine are such that when running at a speed equivalent to 9 miles per hour or less, it acts as a motor and when the speed increases, it automatically becomes a generator and begins to charge the battery.

Regulation. The third-brush method of regulation is employed the amount of current supplied to the shunt fields by this brush

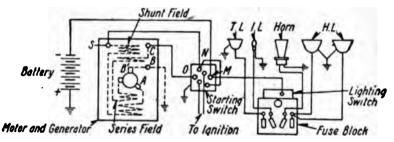


Fig. 359. Wiring Diagram for Westinghouse Single-Unit System on Hupmobile

decreasing as the magnetic field of the generator becomes distorted owing to increased speed.

Control. The switch employed with this type of combined unit is the regular single-throw single-pole switch used on lighting plant switchboards. This switch controls both the ignition and the starting-motor circuits and, at starting, is thrown on and left closed as long as the car is running.

Wiring Diagram. The connections of the Hupp installation are shown in Fig. 359.

Instructions. Battery Charging. As the unit acts as a motor to drive the engine when the latter is running at a speed of less than the equivalent of 9 miles per hour on high gear, slow driving or permitting the engine to idle at a very low speed when the car is standing will discharge the battery. Where no fault in the wiring or connections exists and the battery will not stay charged to

generator, of course, working properly), this practice may be the cause of the trouble. If the voltage drops to 10 or 11 volts, with the headlights on but with the engine stopped, it indicates that the battery is practically discharged. This voltage reading will be somewhat higher in summer than in winter. The remedy is to run with fewer lights at night or to run the engine for longer periods in the daytime, or at higher speeds. Running solely at night will not keep the battery sufficiently charged, as most of the generator output is consumed by the lamps. Should the battery become discharged to a point where it cannot operate the starting motor, disconnect the wires C and S at the dynamotor, taping their terminals to prevent contact with any part of the engine or chassis. Start the engine by hand and, when running at a speed of about 500 r.p.m., reconnect these wires, being sure to connect wire S first, when the battery will begin to charge.

Fire Prevention. Gasoline or kerosene is frequently employed to wash automobile engines. Before doing so, be sure that the starting switch is open, and disconnect the negative terminal of the battery, taking care that it does not come in contact with any metal parts of the car. To make certain of this, it is better to tape the metal terminal. Allow the gasoline to evaporate entirely before reconnecting the battery, as a flash or spark would be liable to ignite the vapor. This naturally applies to all cars, although only such as are equipped with the Westinghouse single-unit or the Dyneto single-unit have starting switches which remain closed all the time the engine is running.

Weak Current. If the dynamotor fails to operate when the starting switch is closed, open the switch and test with the portable voltmeter. If it indicates less than 11 volts, the battery is run down; if it indicates 12 volts or over, look for a loose connection or an open circuit (broken wire) either in the connection from the battery to the starting switch, from the switch to the dynamotor, from the latter to the ground, or from the battery to the ground, in the order named. Dim burning of the lamps when the engine is stopped also indicates a discharged battery. When this is the case, it is advisable to recharge at once from an outside source, if possible.

A quick method of determining whether there is a ground in the wiring is to disconnect the battery wire and, the engine being stopped

### WESTINGHOUSE SYSTEM

Twelve-Volt; Single-Unit; Single-Wire

Dynamotor. The single unit of the 12-volt system, or the "motor-and-generator" as the manufacturers term it, is a bipolar machine, both the generator and starting-motor windings of which are connected to the same commutator. Installation is usually by means of a silent chain, as on the Hupp (1915 and earlier). The characteristics of this type of machine are such that when running at a speed equivalent to 9 miles per hour or less, it acts as a motor, and when the speed increases, it automatically becomes a generator and begins to charge the battery.

Regulation. The third-brush method of regulation is employed, the amount of current supplied to the shunt fields by this brush



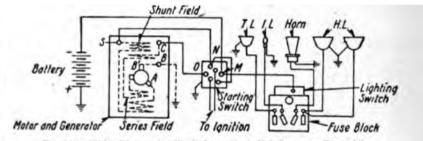


Fig. 359. Wiring Diagram for Westinghouse Single-Unit System on Hupmobile

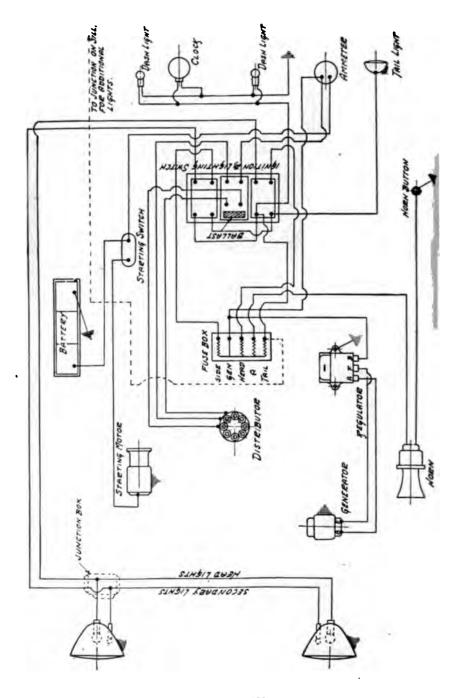decreasing as the magnetic field of the generator becomes distorted



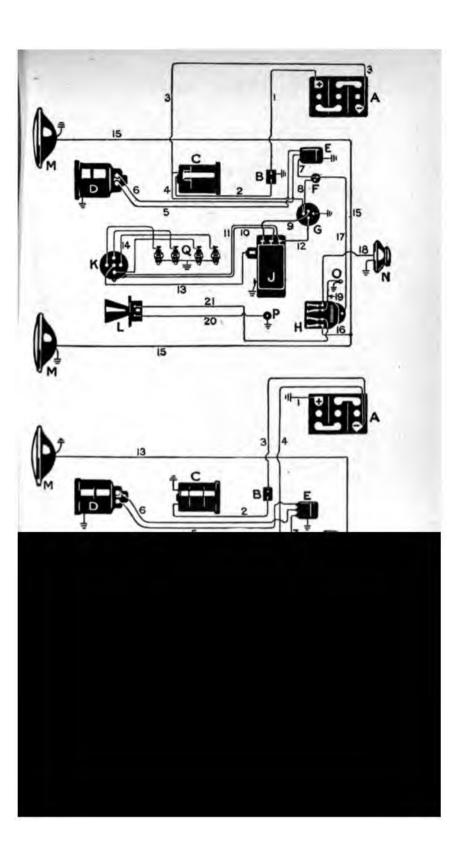

# **ELECTRICAL EQUIPMENT**

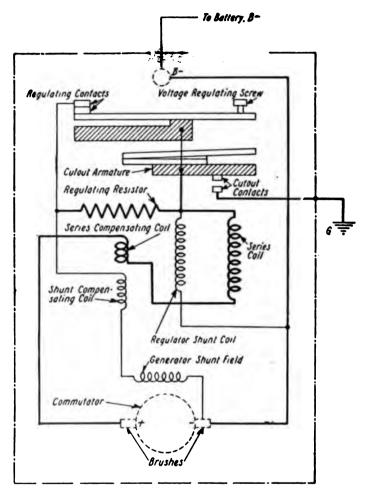


Fig. 361. Wiring Diagram for Westinghouse Generator with Self-Contained Regulator

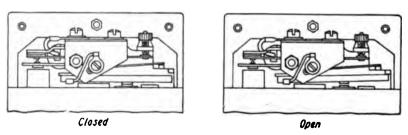


Fig. 362. Closed and Open Position of Westinghouse Cut-Out Switch

and all lights turned off, touch the disconnected wire to the terminal lightly. A spark, when this contact is made, will indicate a ground between the battery and the dynamotor or the switch. The testing lamp should then be used to locate the circuit in which the ground exists.

Failure to charge properly may be due also to imperfect contact at the brushes or to a break in the shunt-field circuit of the generator, as explained in previous instructions. If the shunt-field circuit is found open, the trouble doubtless has been caused either by a ground between the battery and the generator or by running the generator when it was disconnected.

To remove the brushes, lift the spring that holds the brush in the guide and take out the screw holding the brush shunt, when the brush

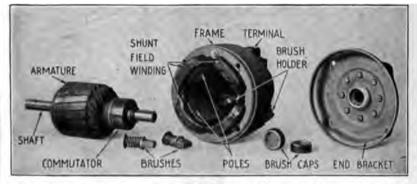


Fig. 360. Westinghouse Four-Pole Generator for Six-Volt Double-Unit Single-Wire System Courtesy of Westinghouse Electric and Manufacturing Company, East Pittsburgh, Pennsylvania

can be slipped out. Care should be taken to replace houshes in the

third, and the third-brush method on the fourth. This regulator is either self-contained, i.e., built in the generator, or is mounted independently. The connections of the built-in regulator are shown in Fig. 361. The open and closed positions of the contacts of the external cut-out are shown in Fig. 362.

Wiring Diagram. Fig. 363 shows the connections of the separately mounted regulator together with the charging and lighting circuits.



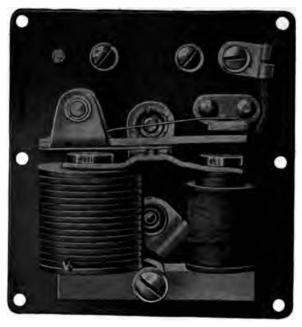


Fig. 364. Westinghouse Cut-Out Switch of Generator with Third-Brush Regulation


Battery Cut-Out. The type of automatic cut-out used with the type of generator employing the third-brush method of regulation is illustrated in Fig. 364. This may or may not be combined with a starting switch mounted on the engine side of the dash or some similar location. Fig. 365 is a wiring diagram showing the connections of the separately mounted cut-out with the third-brush generator. The cutting-in speed varies from five to ten miles per hour on high gear, varying with the gear ratio and wheel diameter of the car. This speed may be determined by running the car slowly and speeding up very gradually, meanwhile observing the increase in 1 on the speedometer. The point at which the contacts close

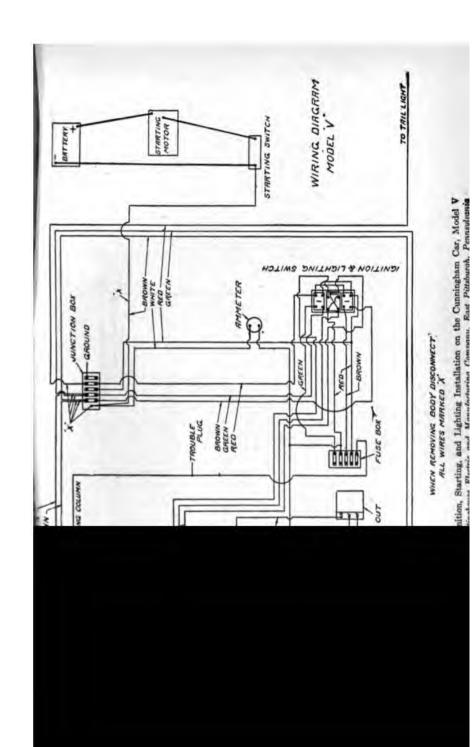

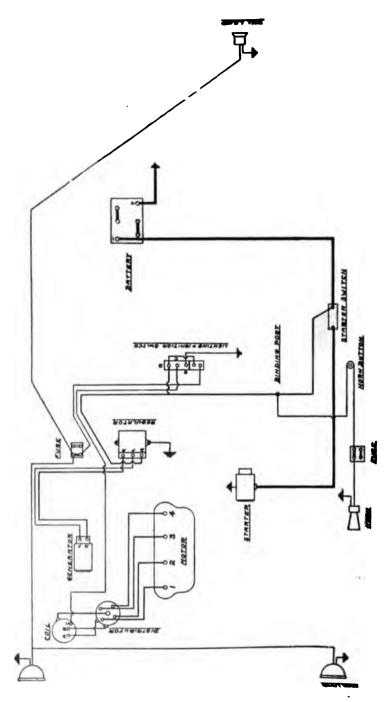

Two-Brush Generator Wiring Diagram for Connecticut Ignition and Westinghouse Starter Installations on Dort 1916-17 Cars. Company, Plans, Michigan

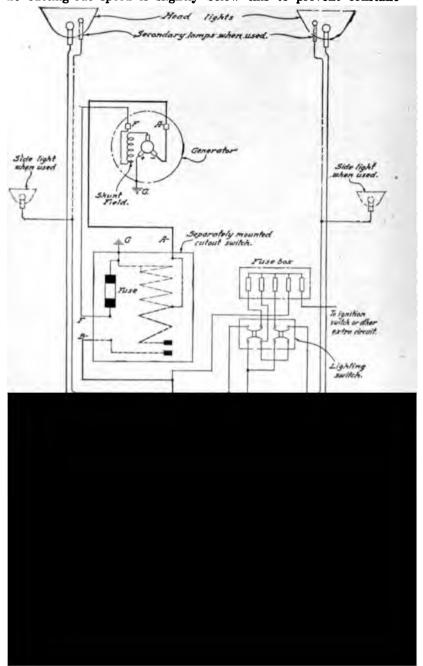ill be indicated by a slight quick movement of the ammeter needle. he cutting-out speed is slightly below this to prevent constant



Starting Motors. Variations. Several types are built to meet varying requirements; i.e., with self-contained reduction gearing, with single-reduction automatic screw pinion shift (Bendix drive), and with automatic electromagnetic pinion shift. The first two will be familiar from the descriptions already given of other makes. The third is similar in principle to the Bosch-Rushmore, but an independent magnet is employed instead of utilizing the armature of the motor itself for this purpose.

Magnetic Engaging Type. This type, as well as the other types of starting motors mentioned, may be operated either by a foot controlled switch or by a magnetically controlled switch put in action by a push button. The wiring diagrams, Fig. 366, show the circuits of both installations and also make clear the operation of the auto-



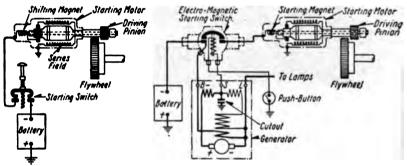



Fig. 366. Wiring Diagrams of Motor Connections for Automatic Electromagnetic Pinion Shift


matic engagement. The armature is mounted on a hollow shaft; and on the end of this shaft is carried a splined pinion designed to engage the flywheel gear. This pinion is caused to slide along the shaft by a shifting rod which is attached to the pinion and passes through the hollow shaft. The other end of this shifting rod acts as the core of the shifting magnet and will be recognized as the plunger of a solenoid. When the motor is idle, a spring holds the pinion at the right-hand end of the shaft and clear of the flywheel gear.

As shown diagrammatically in Fig. 366, when the starting switch is closed, the circuit is completed from the negative terminal of the battery, through the switch, the shifting solenoid, the armature, and the series field of the motor to the frame of the car on which the positive side of the battery is grounded. The large amount of current necessary for starting energizes the shifting solenoid suffi-

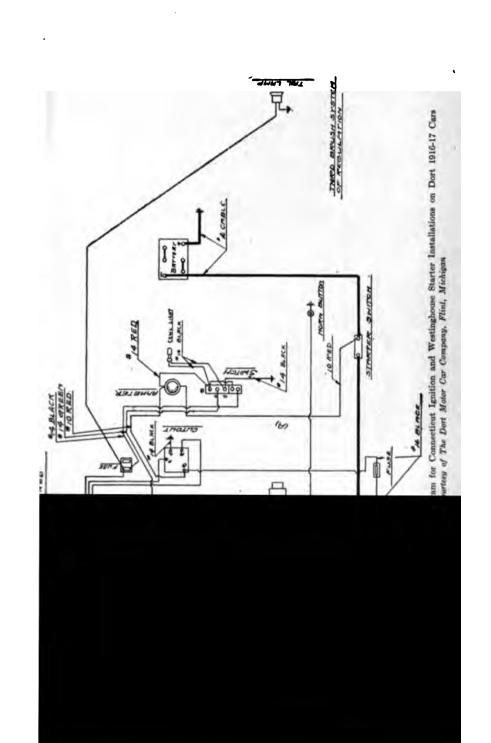

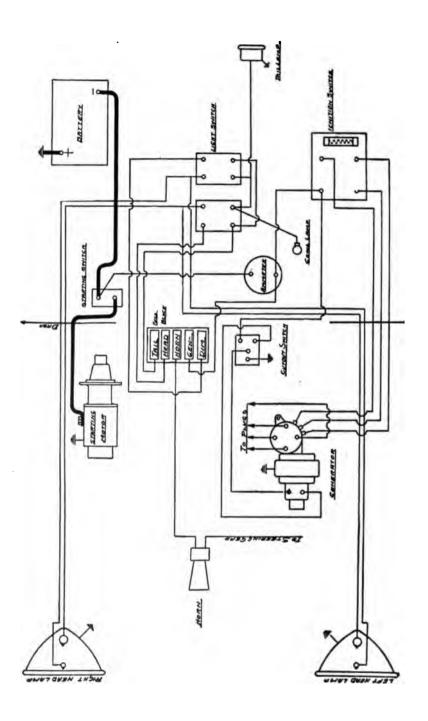

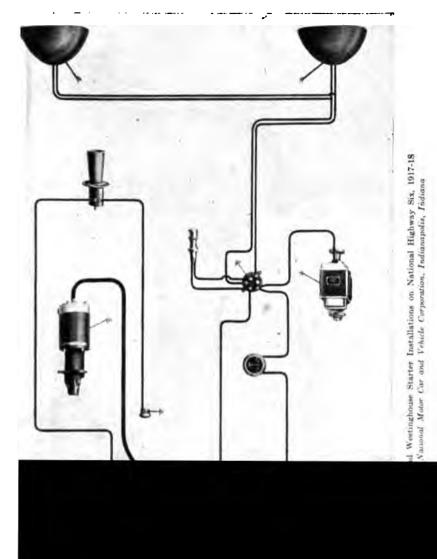

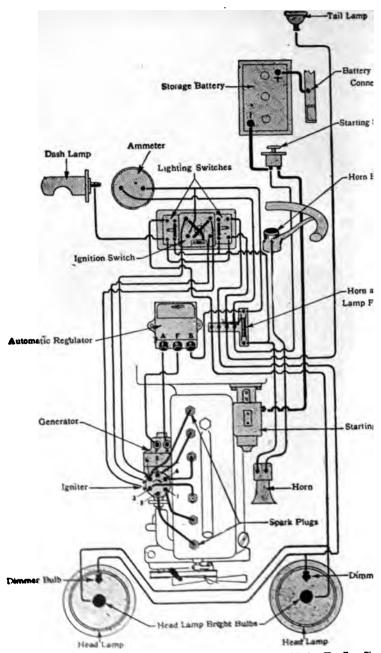

Westingsbouse Ignition Starting and Lighting Installation on Marion-Handley Sir Country of Die Marial Motors Company, Jackson, Machigan

ciently to overcome the force of the spring so that it draws the shifting rod to the right through the hollow shaft, meshing the pinion with the flywheel gear. When the engine speeds up to the no-load speed of the starting motor, the current in the latter falls off so that the pull of the solenoid is less than that of the spring, and the pinion is automatically disengaged, though the motor will continue to revolve until the starting switch is opened.

Electromagnetic Switch. In principle, the electromagnetic switch is the same as that of the automatic engaging device for the pinion. The movable double-pole contact, instead of being attached to a rod for foot operation, is mounted on the plunger of a solenoid and normally is held open by a spring. This solenoid requires but a small amount of current for its operation and is connected on an independent circuit with the battery. It is controlled by a push button, and when the circuit is closed by means of the latter, the plunger of the solenoid is drawn into the coil against the pull of the spring, thus bringing the contacts together and holding them there as long as the solenoid is energized.

Instructions. Regulator. When the generator of the voltageregulator type fails to charge the battery properly, all parts of the circuits and connections having been examined to determine that they are in proper condition, the regulator may be tested for faults. With the aid of the portable voltmeter, note at what voltage the contacts of the cut-out close or cut in, and at what voltage they

### SPECIAL SYSTEMS FOR FORD CARS


#### FORD SYSTEM


General Instructions. On the latest model enclosed Ford cars such as the sedan and the coupé, an electric lighting and starting system is now being furnished as a regular part of the equipment. As will be noted by the illustration, Fig. 367, this has been designed especially for the Ford motor and is combined with it in a manner that makes it practically integral. The system is a standard two-unit six-volt single-wire type that is of conventional design throughout so that any repairman who is familiar with the other system previously described will at once recognize the layout of the Ford system and have no difficulty in handling it. The details of the generator and starting motor are shown in Fig. 368, while the complete wiring diagram is illustrated in Fig. 369. The battery is a 6-volt 13-plate Exide.


The precautions mentioned in connection with other systems of this type apply to the care and handling of the Ford. If for any reason the generator is disconnected from the battery, the engine must not be run unless the generator is grounded as otherwise it is apt to be burned out. A piece of wire, preferably flexible copper cable and in no case less than  $\frac{1}{16}$ -inch in diameter, should be run from the terminal on the generator to one of the valve cover stud nuts, making sure that the wire is tightly held at both ends.

Removal of Starting Motor. It is necessary to remove the starting motor to replace the transmission bands. To do this, first remove the engine pan on the left side of the engine and then take out the four small screws holding the shaft cover to the transmission cover. Upon removing the cover and gasket, turn the Bendix driveshaft around so that the set screw on the end of the shaft is in the position shown in the illustration, Fig. 368. Immediately under the set screw is placed a washer of the locking type, having lips or extensions oppositely placed on its circumference. One of these is turned against the collar and the other is turned up against the side of the screw head. Bend back the lip which has been forced against the screw and remove the set screw. A new lock washer of this type must be used when replacing the starting motor.

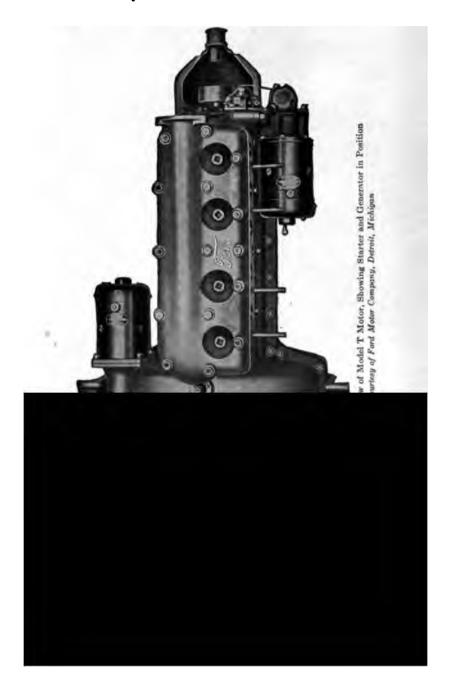Pull the Bendix assembly out of the housing, taking care to that the small key is not lost. Remove the four screws which



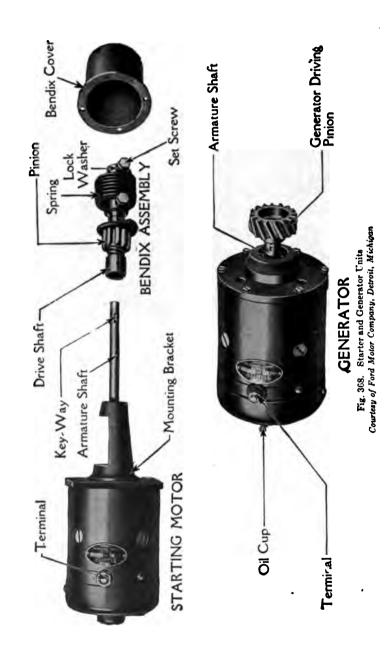

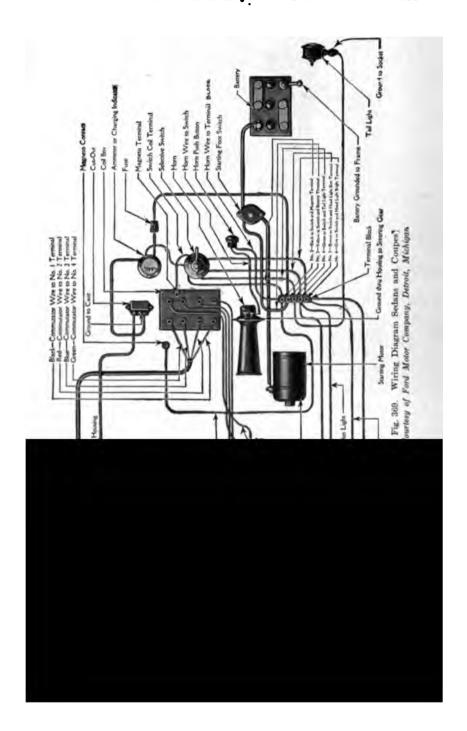

the reason for removing the engine pan. In replacing the starting motor, note that the terminal for the electric cable must be placed on top. If the motor is placed in any other position, the cable will not reach to the terminal. In case it is necessary to run the car without the starting motor in place, transmission cover plates supplied for the purpose should be put in place to exclude dirt and prevent the waste of oil.

Removing Generator. To take the generator off the engine first take out the three cap screws holding it to the front end cover and by placing the point of a screw driver between the generator and the front end cover, the generator may be forced of the engine assembly. Always start at the top of the generator and force it backward and downward at the same time. In case it is necessary to run the car without the generator in place, a plate may be had to cover the opening thus left in the timing gear case. Should the battery be removed, the engine must not be run without grounding the generator in the manner already explained.

The generator is driven from the large timing gear to which the camshaft is attached and is set to cut into the battery circuit when the speed of the motor is equivalent to 10 miles an hour on the direct drive, while it reaches its maximum at 20 miles per hour. Both the generator and the starting motor are lubricated by the splash system of the engine itself, but an additional oil cup is placed on the rear end bearing of the generator and should be given a few drops of oil at short intervals.

Lighting and Ignition. The lighting system consists of two double-bulb headlights and a small taillight controlled by a combination lighting and ignition switch mounted on the instrument board and the connections of which will be noted in the wiring diagram. All of the lamps are connected in parallel, current being supplied for them by the battery. The lamps should never be connected to the magneto, as the higher voltage of the latter will burn out the bulbs and it may discharge the magnets.

Reference to the wiring diagram will show the connection between the battery and the combination lighting and ignition switch by means of which the battery current may be sent through the induction coils for starting. On models equipped with

starting and lighting systems, the magneto is employed solely for ignition. Whenever any adjustments or repairs are to be made to the wiring, the cable leading to the positive side of the battery should first be disconnected and protected with insulating tape. Otherwise, the battery current is apt to be passed through the magnet coils, and this will result in discharging the magnets.

The operation of the system is checked by means of an ammeter mounted on the instrument board. When the lights are burning and the engine is not running at a speed in excess of the equivalent of 10 miles an hour, the ammeter will show discharge. At a speed of 15 miles per hour or faster, the ammeter should show a reading of 10 to 12 amperes, even with the lights burning. When the ammeter fails to give a charge reading with the engine running at a speed of 15 miles an hour or better, the generator should be tested, if an examination fails to reveal any loose connections at the ammeter or on its line. To make the generator test, the cable is disconnected from its terminal on the generator and the engine run at a moderate speed. With a pair of pliers, short-circuit the generator by placing against the terminal stud and against the housing of the generator at the same time. If the generator is in good working condition, a bright spark will result. The engine should at once be stopped, as the generator should not be run in this condition a moment longer than necessary. An inspection of the connections and wiring as outlined in previous sections will be found equally effective in discovering short-circuits or grounds as in any of the other systems mentioned

Bendix drive shaft to engage with the teeth on the flywheel, thus turning over the crankshaft. When the engine is cold, it may be necessary to prime it by pulling out the carburetor priming rod, which is located on the instrument board. In order to avoid flooding the engine with an over-rich mixture of gas, the priming rod should only be held out for a few seconds at a time.

#### GRAY AND DAVIS


General Instructions. Grav and Davis and some of the other leading manufacturers who make the starting and lighting equipment for larger cars also manufacture a special type designed for the Ford. These special Ford systems are simple and compact. and everything necessary to install them on the machine is provided by the maker of the apparatus so that they may be installed. either by the owner of the machine or by the local garage man whose electrical experience is limited. This necessitates the removal of the radiator, radiator brace rod, hose connections, fan, fan pulleys and belt, cylinder head, and in some cases the timing-gear housing. The ground connection of the headlights, which is soldered to the back of the radiator on 1915 and subsequent models provided with electric headlights supplied by the Ford magneto, must be discarded altogether, as the lights are to be supplied by the storage battery. In cases where it is necessary to remove the timer (this must be done when the timing-gear housing has to be removed), both the timer and the carburetor should be adjusted for efficient running before starting to dismantle the engine, and if the latter is turned over while the timer is off, the ignition timing must be readjusted when the timer is put back. As the removal of all the parts mentioned is a simple matter fully covered in the Ford instruction books and familiar to practically every garage man in the country, they are not repeated here.

Installation. Preparing Engine. Remove the radiator, disconnecting the ground wire from it; disconnect the wires from the head lamps and remove the head lamps and supports. Take off the bracket and fan, Fig. 370, and turn the engine by hand until the pin 2 in the fan pulley is straight up and down; remove the pin from the jaw clutch and remove the starting-crank 4, belt 5, and the cotter pin, 3; take the pin from the fan pulley and remove the pulley 6. Remove

the second, fourth, and fifth bolts from the crankcase flange 7, the left and front bolt from the side-water connections 8 and 9, as well as the second cylinder-head bolt 10.

NOTE—The numerals refer to the parts to be removed or replaced, as well as the sequence in which the operations are to be carried out, as shown on the sketches. Each illustration, however, has its own series of the same numbers, which should not be confused with those on other views.

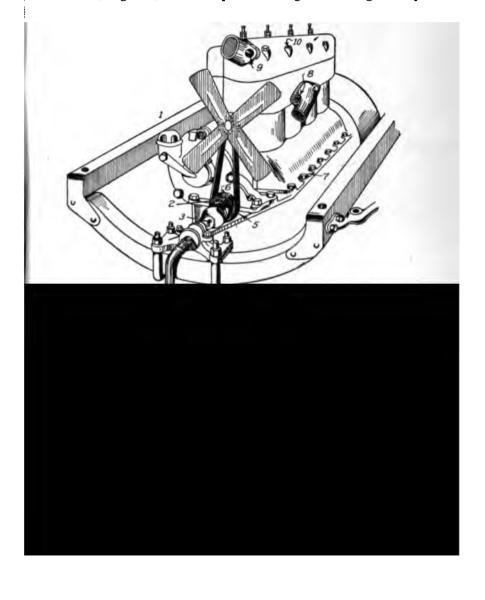Lay the chain 1 in the rear of the engine support around the crank-shaft, Fig. 371, and then place the original starting-crank jaw



## **ELECTRICAL EQUIPMENT**

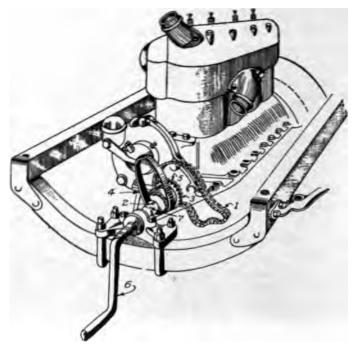


Fig 371. Putting Driving Chain on Crankshaft Sprocket in Gray & Davis Ford Installation


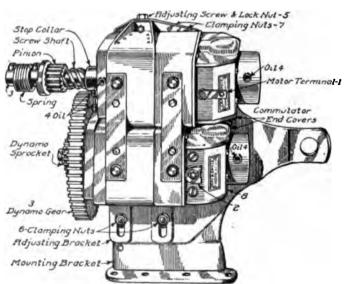


Fig. 372. Details of Gray & Davis Generator Unit for Ford Starter

the motor terminal 1 is free from contact with any other metal; also that the dynamo terminal 2 and insulation are not injured. Test the shaft and gears 3 to see that they turn freely, and then fill the oil cups 4 with oil.

Release the top adjusting screw 5, also two lower clamping lock nuts 6 (front), as well as the two upper clamping lock nuts 7 (rear) and the single middle clamping lock nut 8 (front). The units must be in the lowest position possible on the bracket before placing it on the car. In Fig. 373 is shown the starter-generator unit in place on the engine with the bolts and nuts all tightened. This is carried out as follows:

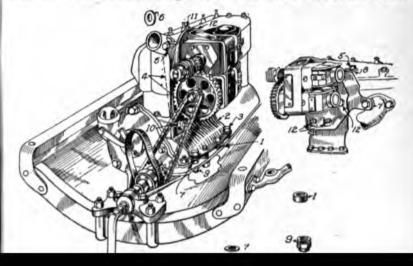

so that the chain will be tight when the units are in the lowest possible position. Use washers 8 as shims between the bracket and the cylinder-head link. Secure the three lower bracket bolts 9 witl lock washers and nuts, also secure the water-connection bolts 6 and 7 and the cylinder-head bolt 5. Adjust the bracket stay bolt 16 adjust the chain 11 to moderate the tension and lock adjustment securely tighten five clamping bracket nuts, and then crank the engin slowly by hand to see that everything turns smoothly. If, through some irregularity in the engine casting the bracket should not sea properly, it may be necessary to file the bracket holes to meet thi condition. Be sure that the sprockets are in true alignment, or the

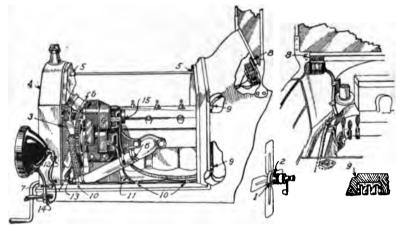


Fig. 374. Installing Gray & Davis Wiring and Lighting Switch on Ford Car


uneven strain may cause injury. If necessary, elongate the holes is the bracket or shim bracket as needed to insure perfect alignmen of chain.

When adjusting the bracket stay bolt 10, make sure that it rest against the engine casting without strain and secure it with nuts or each side of the bracket. Bend the ignition timing to clear the chain if necessary, but after bending, the distance between the ends of the rod in a straight line must be equal to its original length. Adjust the chain to moderate tension and secure both the adjustment lock nut at the top. If all five nuts holding the adjustable bracket are no released before adjusting, uneven strain may cause injury. Securely

tighten the sliding-bracket nuts 12—two at the bottom front side, two at the top rear, and one at the front end. Test by turning the engine over by hand slowly.

Remounting Engine Parts. Fit split pulley 1 to the hub of the fan, Fig. 374, and attach split pulley 2 with four screws; slip a new belt over the fan pulley, attach the fan, and adjust. Place the radiator 4 on its support and screw the radiator rod into the radiator and secure with check nut 3; secure the hose clamps at the top and side water connection 6; place the radiator nuts and secure with cotter pins. Attach the lighting switch at the cowl (left) with  $\frac{3}{16}$ -inch screws

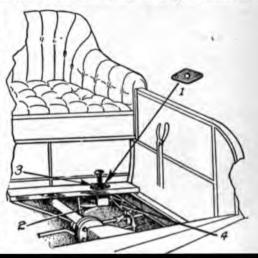and attach three lightingcable clips on the rear of the dash, using 1-inch wood screws; cut the corner from the toe board for clearance. Attach three wire clips 10 to the left side of the frame and attach green wire 11 to the dynamo terminal. Then connect the short black and red wire to the left head lamp. Pass a long black and red wire through the radiator tube



the cable clip holding the two wires, and secure the spring and th knob with a pin.

Priming Device. Connect the priming device 1, Fig. 376. Dri a  $\frac{7}{82}$ -inch hole in the dash two inches to the right of the coil box an six inches above the toe board and pass the upper rod through. Connect the lever arm 2 vertically to the foremost exhaust manifold bo with stationary member in horizontal position; then connect the lower od 3 to the carburetor priming lever. Work it back and forth sever times to make sure that it returns to normal position when releases

Battery. Place the battery box on the right-hand running board Fig. 377, to permit easy opening of doors and access to battery box


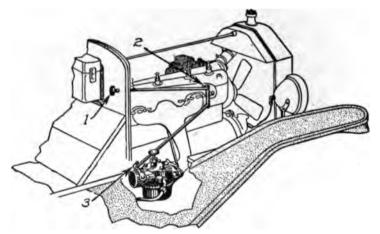


Fig. 376. Replacement of Carburetor Timing Rod on Dash Courtesy of Gray & Davis, Boston, Massachusetts

then mark four holes with the center punch. Drill four holes  $\frac{1}{2}$  ind in diameter in the running board 2, using a jack or prop to suppor the running board while drilling. Replace the battery box on th running board in order to mark the holes in mud guard for insulatin cable bushings 3, then make two holes  $1\frac{2}{3}$  inches in diameter. Inser insulating-cable bushing 4 in left hole and secure with round wooder nut; do the same with the right-hand bushing 5. Secure wood nuts with a wire twisted around the thread. A coat of heavy paint will also hold the nut in place and preserve the insulator. Place the two flat wood cleats 7 with holes at each end between the battery box and the running board; then pass four bolts 8, sinch by  $1\frac{1}{2}$  inches, through

the battery box, cleats, and running board, and secure them with four nuts and lock washers. Place two special-shaped wood cleats 9 inside the battery box, one at each end for the battery to rest upon, so that holes in the cleats will fit over the bolt heads. Raise springs 10 and hang on the side of the battery box, placing the battery in the box and inserting two ½-inch wood strips, one each side between the battery and the battery box. Attach two springs 11 at opposite ends

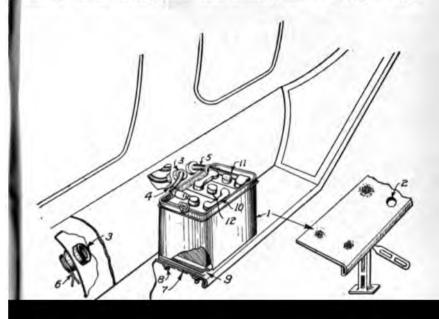

# ELECTRICAL EQUIPMENT



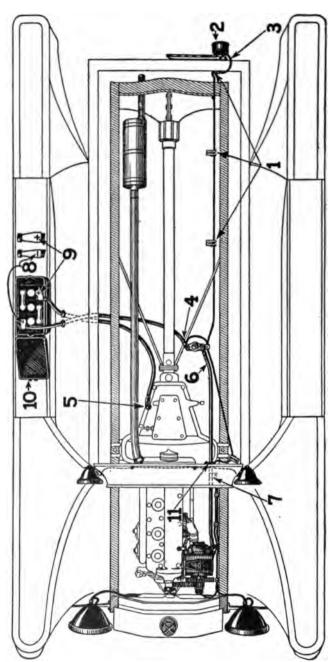



Fig. 378. Plan View of Complete Wiring System for Gray & Davis Ford Installation Courtesy of Gray & Davis, Boston, Massachusetts

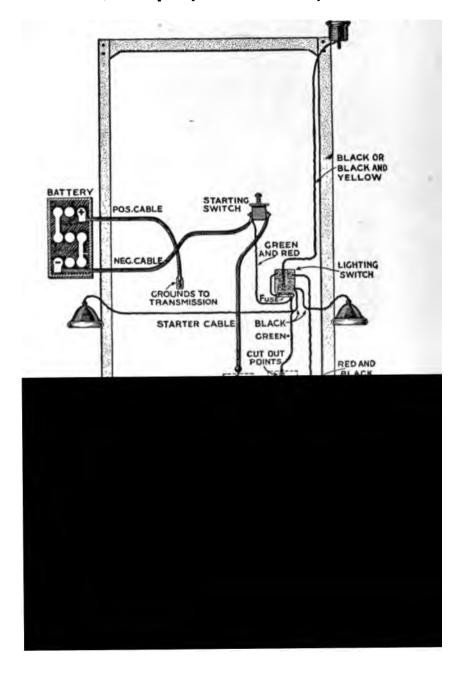tail-light wire; see that the wire does not make contact with any metal edges. Attach the electric light 2. If the tail lamp has a one-point wire connector, the lamp body must be metallically connected with



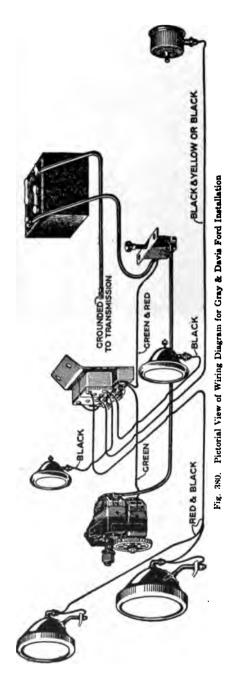

should run from the secon terminal of the connector toth metal framework of the ca Connect the short starting cable 4 (negative) and th green and red wire to the star ing-switch terminal nearest th battery. Then pass the end the battery cable through th foremost insulator in the mu guard. Attach the end of th starting cable 5, leading through the rear hole in th mud guard, to the second bo in the transmission case. Us a lock washer and a plai washer under the head of th bolt to insure permanent con tact. This is the positive cabl which connects to the + term nal 9 of the battery. Then pas the end of the cable throug the rear insulator in the mu guard and under the exhaus pipe, which it must not toucl Attach to the starting-switch terminal 6, securely, the en of the cable which runs to th starter. Support the starte cable 7 by a clip to the insid curved edge of the dash. Whe connecting cables to the bat tery, be sure that the terminal securely fastened—firm contact must be made. Th battery terminals are made lead and must be handled care fully. Battery-cable terminal

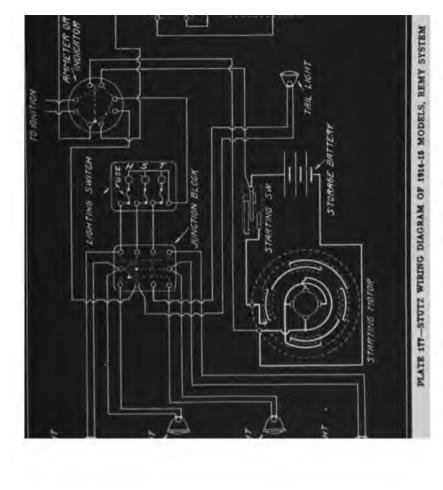

LIGHTING AND HEN SWITCH THE EREVEE STOL MILCHT




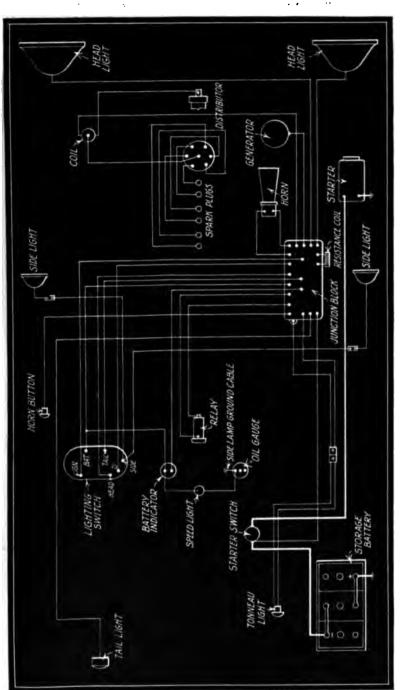


Plate 179—Studeraker wiring diagram of 1996 series 59, wagner starting and lighting, remy ignition systems

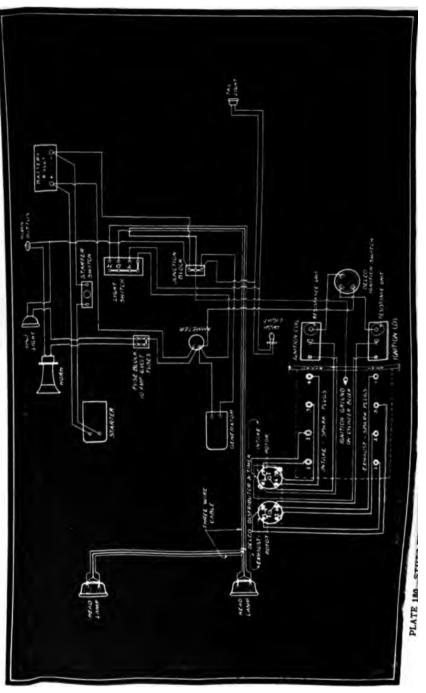

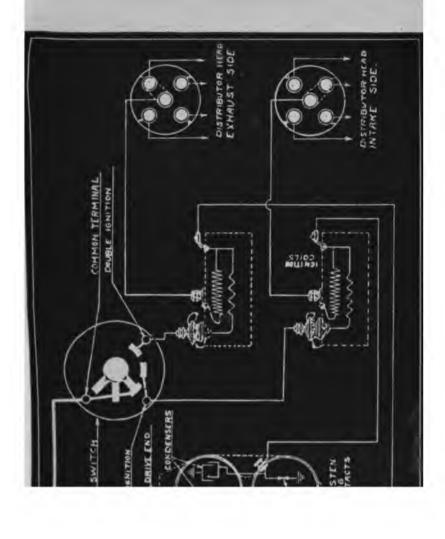

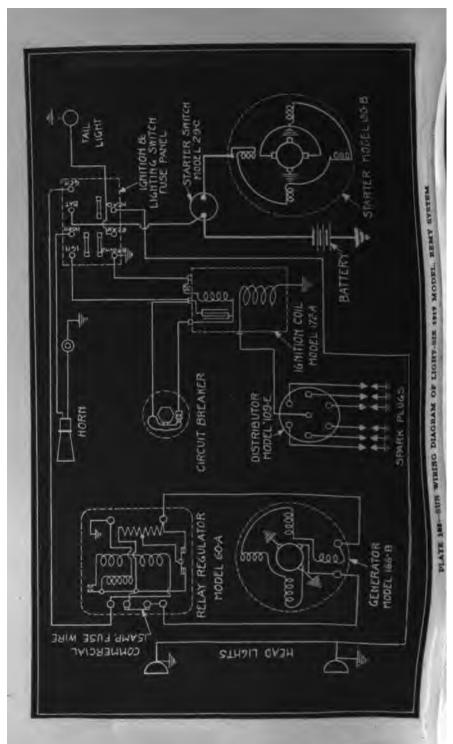

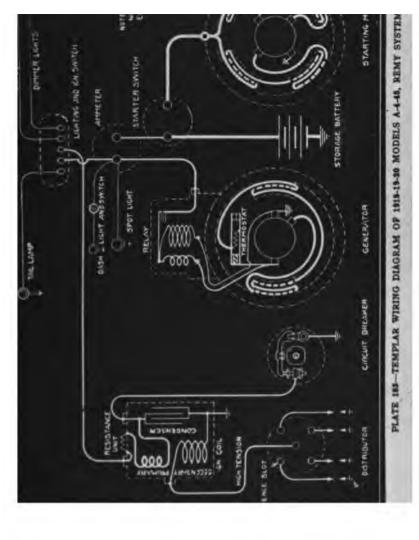


PLATE 184 -VELIE WIRING DIAGRAM OF 1918-19 MODETS .. ...



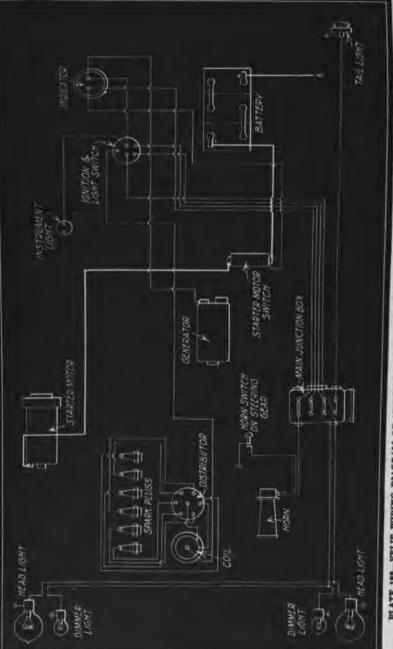


PLATE 188-VELIE WIRING DIAGRAM OF 1898'MODEL 48, BIJUR STARTING AND LIGHTING, ATWATER RENT IGNITION SYSTEMS

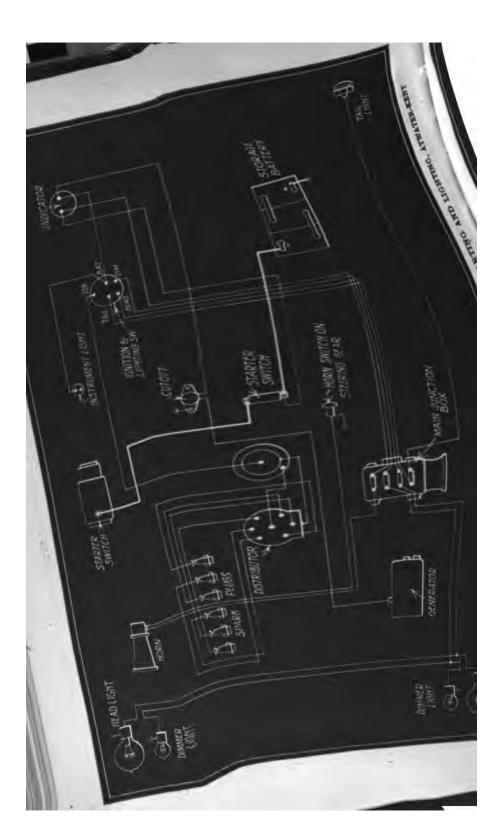

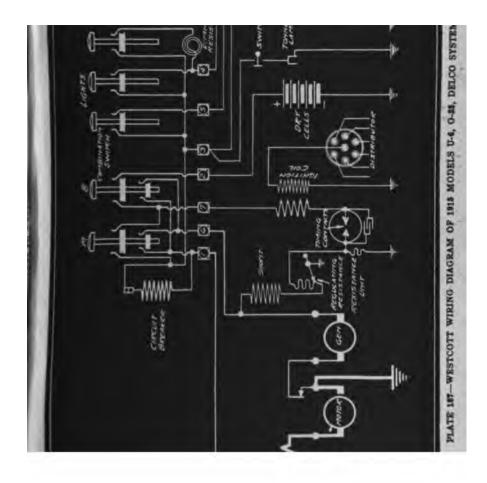



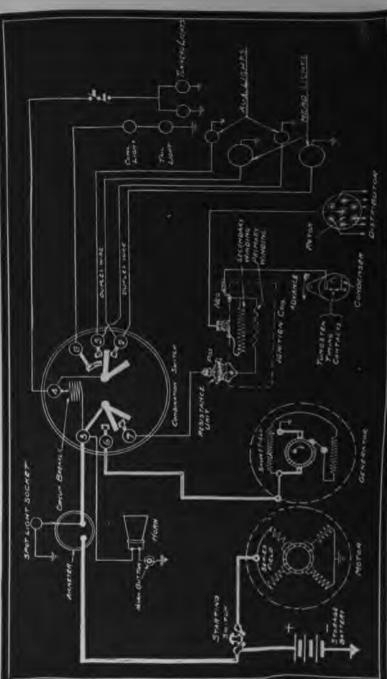


PLATE 146-WESTCOTT WINING DIAGRAM OF SPRING 14, DRICO SVETEM

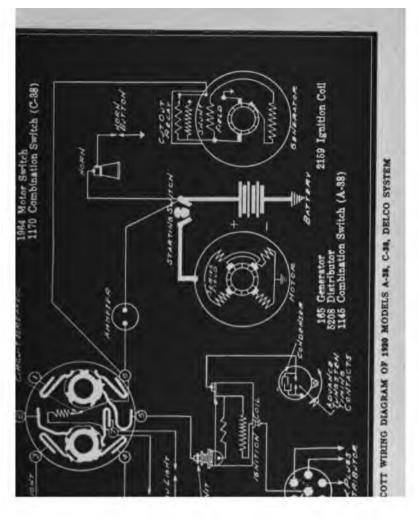

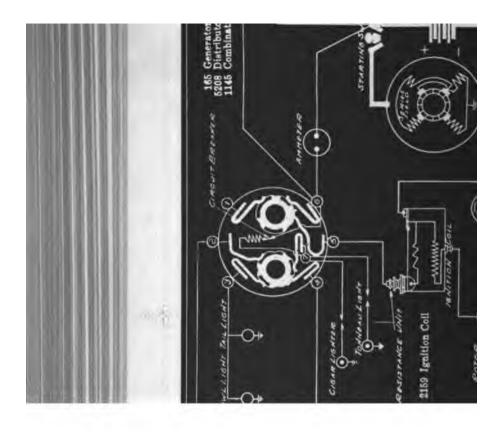


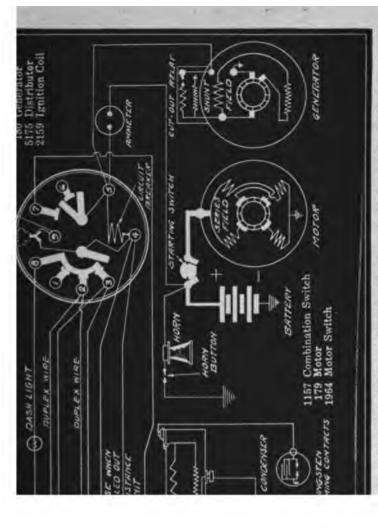


DIAGRAM OF 1930 MODEL C-48, DELCO SYSTEM (USING 9N CONTINENTAL ENGINE)

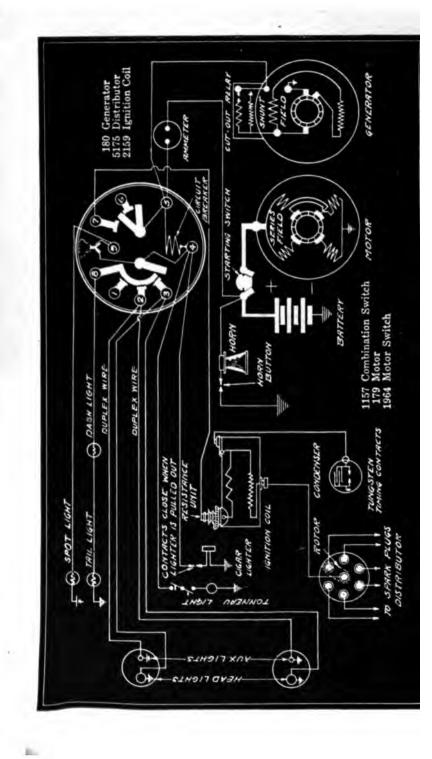

r slightly in size and correspond to the holes in the battery inal, the negative-cable terminal being the smaller. Pass the most cables 8 through the battery-box insulator and connect a firmly to the negative battery terminal. Do not connect positive cable to the battery or insert the fuses until the instalmass been made in accordance with the instructions and tests that wires are not in contact with the frame of the car. Turn lighting switch off and touch the positive terminal lightly to the ery terminal. If there is a spark, it indicates a short-circuit or ound, caused by a wire coming in contact with the frame. Ledy the trouble before connecting up the battery. If there is park, permanent connection may be made. The lamp-test set

be used to determine ther there are any inds or short-circuits, re connecting up the ery.

When all indications that the installation been made properly, sect the positive startable to the positive sinal 9 of the battery.

e and secure the matter of the battery.

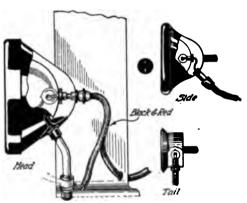


Fig. 381. Details of Gray & Davis Ford Lamps

screw at the top of the bracket and tighten the check nut and adjing screw to lock the adjustment. Then retighten all five clampanuts securely. Turn the engine by hand to determine whether chain runs smoothly; the chain should not be too tight. After I service, when all chain adjustment has been taken up, the chain I be shortened by taking out a pair of links. The latest type of chais supplied with a removable pair of links, retained in position by removable pins. These pins are a trifle longer than the regriveted pins.

Where the chain has been shortened, it is sometimes necess to lower the supporting bracket slightly by removing some of  $\frac{1}{32}$ -inch washers under the bracket or by filing the spacers slightly that the chain will be tight when the unit is in the lowest poss position.


Wires are subject to dislodgement and injury, hence they she be examined carefully to see that they are not resting on sharp ec of metal and that the insulation is not worn or injured. See that n of the wires are swinging or rubbing against metal, as this is likely injure the insulation. Also examine the cables leading through battery box and mud guards; the bushings must be intact and in p to protect the cables from short-circuiting. Wherever injury to part of the insulation is found, wrap the spot carefully with insulat tape and bend away from the metal to provide sufficient clearance prevent further damage.

If the lamps fail to light when the lighting switch is operathe fuse on the back of the lighting switch should be examined; it r be burned out, broken, or not properly clamped in its fuse cl. The wires may not be properly connected (this should be checked wiring diagram), the bulbs may be burned out, or the filaments r be broken. The lamp wiring may be short-circuited or the charge circuit may be open.

Do not run the engine with the battery disconnected or off car without first insulating or removing two of the generator brus to prevent the generator from generating a current. To determ if generator is operating properly, turn on the head and tail lar while the engine is idle. Start the engine and accelerate to charg speed or over; a perceptible brightening of the lamps will indic that the machine is generating sufficient current both to charge battery and to light the lamps. Do not open the charging circuit at any time when the engine is running.

Testing Generator with Ammeter. A more accurate determination may be made by connecting an ammeter in the circuit. Disconnect the red and green wire connected to the fuse terminal on the back of the lighting switch and connect it to one terminal of the ammeter. From the other terminal of the ammeter, connect a wire to the fuse terminal to which the red and green wire was previously connected. Turn the lights on with the engine idle. The ammeter should register "discharge", the reading representing the amount consumed by the lamps turned on, i.e., head and tail lamps, 5 to 6 amperes; side and tail lamps, 1½ to 2 amperes. If the ammeter indicated "charge" instead of "discharge", with the lamps turned on and the engine idle, reverse the wires connected to the ammeter terminals. In case the ammeter does not register, see that the pointer is not jammed, otherwise, the circuit is open at some point or the battery is exhausted.

Run the engine at a speed corresponding to 12 to 15 miles per hour, the lights being turned off. If the ammeter registers "charge", the generator is then charging the battery. Increase the engine speed to a car speed corresponding to 13 to 18 miles per hour. The ammeter reading should then be from 12 to 15 amperes. As the engine speed is increased above 18 miles per hour, the charging rate will decrease gradually to approximately 10 amperes at very high speed. With the engine running at 12 miles an hour or faster, turn the lights on;

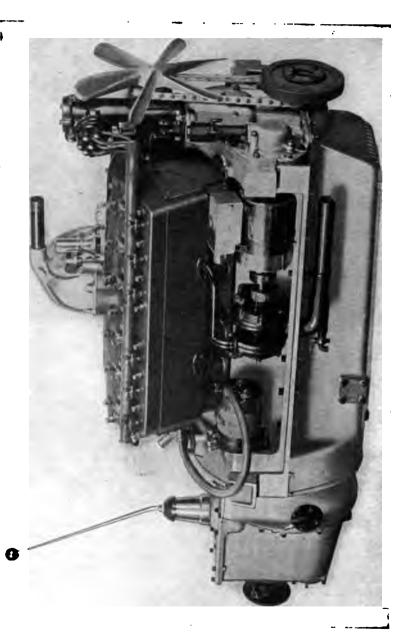

# ELECTRICAL EQUIPMENT FOR GASOLINE CARS

PART VII

# ELECTRIC STARTING AND LIGHTING SYSTEMS—(Continued)

## STARTING AND LIGHTING STORAGE BATTERIES

Importance of the Battery in Starting and Lighting. In the last analysis, every electric lighting and starting system on the automobile is necessarily a battery system. An electric starter is, first and last, a battery starter, since no system can be any more powerful than its source of energy. In other words, the storage battery is the business end of every electrical starting and lighting system. Just as the most elaborate and reliable ignition apparatus is of doubtful value with poor spark plugs, so the finest generators, motors, and auxiliaries become useless if the battery is not in proper working order.

Storage Battery Requires Careful Attention. A little experience in the maintenance of electric starting and lighting systems will

Other things being equal, the successful operation of any startir and lighting system centers almost wholly in the proper maintenance the storage battery. Not all the defections that this part of the ele trical equipment of the car suffers are caused by the battery, but unle properly cared for, it will be responsible for such a large proportion that the shortcomings of the rest of the system will be entirely for gotten. To make it even stronger, it may well be said that unle the storage battery is kept in good condition, the rest of the syste will not have an opportunity to run long enough to suffer from wes In a great many cases that come to the repair man's attention, the battery is ruined in the first six months' service, usually through neglect. For this reason, considerable attention is devoted to the battery and its care in this connection, despite the fact that it very fully covered in the volume on Electric Vehicles. tions of operation, however, are totally unlike in the two case In one instance, the energy of the battery is called for only at a ra of discharge which is moderate by comparison with the ampere-ho capacity, while the battery itself is constantly under the care of skilled attendant. In the other instance, the demand for current not alone excessive but wholly disproportionate to the total capaciof the battery when it is used for starting, and intelligent care usually conspicuous by its absence.

### PRINCIPLES AND CONSTRUCTION

Function of Storage Battery. In the sense in which it is common understood, a battery does not actually store a charge of electricit The process is entirely one of chemical action and reaction. A batter is divided into units termed cells. Each cell is complete in itse and is uniform with every other cell in the battery, and one of the chief objects of the care outlined subsequently is to maintain the uniformity. Each cell consists of certain elements which, when current of electricity of a given value is sent through them in ordirection for a certain length of time, will produce a current electricity in the opposite direction if the terminals of the batter are connected to a motor, lamps, or other resistance. The cell wi of course, also produce a current if its terminals are simply brought together without any outside resistance. This, however, wou represent a dead short-circuit and would permit the battery to di

charge itself so rapidly as to ruin its elements. This is one of the things that must be carefully guarded against. When attending a battery, see that its terminals are not left exposed where tools may accidentally drop on them. When the current is being sent into the battery, as mentioned above, it is said to be charging; when it is connected to an outside resistance, it is discharging.

Parts of Cell. Elements. These are known as the positive and negative plates and correspond to the positive and negative electrodes of a primary battery. They consist of a foundation com-

posed of a casting of metallic lead in the form of a grid, the outer edges and the connecting lug being of solid lead, while the remainder of the grid is like two sections of lattice work so placed that the openings do not correspond. Every manufacturer has different patterns of grids, but this description will apply equally well to all of them. Fig. 382 illustrates the grid of the Philadelphia battery. The object in giving them this form is to make the active material of the plates most accessible to

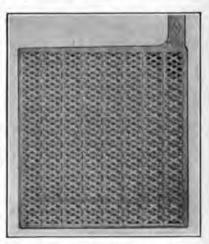


Fig. 382. Lead Grid Ready for Active Material Courtesy of Philodelphia Storage Battery

of the positive plates, there is always one more negative plate that positive plates in a cell. The lead connectors of each of the plate is burned to its neighbor of the same kind, thus forming the positive and negative groups which constitute the elements of the cell.

Separators. As the elements must not be allowed to come in contact with each other in the cell because to do so would cause as internal short-circuit to which reference is made later, and as the maximum capacity must be obtained in the minimum space, the plates are placed very close together with wood and perforated hard rubber separators between them. These are designed to fivery snugly, so that the combined group of positive and negative plates is a very compact unit. When reassembling a cell, it is important that these separators be properly cared for in accordance with the directions given later.

Electrolyte. To complete the cell, the grouped elements with their separators are immersed in a jar holding the electrolyte. This is a solution consisting of water and sulphuric acid in certain pro portions, both the acid and the water being chemically pure to a certain standard. This is the grade of acid sold by manufacturers as battery acid and in drug stores as C.P. (chemically pure), while the water should be either distilled, be cleanly caught rain water or melted artificial ice. In this connection, the expression "chemically pure" acid is sometimes erroneously used simply to indicate acid of full strength, i.e., undiluted, or before adding water to make the electrolyte. It will be apparent that whether at its origina strength or diluted with distilled water, it is still chemically pure In mixing electrolyte, a glass, porcelain, or earthenware vesse must be used and the acid must always be poured into the water. Never attempt to pour the water into the acid, but always add the acid a little at a time, to the water. The addition of the acid to the water does not make simply a mechanical mixture of the two but creates solution in the formation of which a considerable amount of heat is liberated. Consequently, if the acid be poured into the water to fast, the containing vessel may be broken by the heat. For the same reason, if the water be poured into the acid, the chemical reaction will be very violent, and the acid itself will be spattered about Sulphuric acid is highly corrosive; it will cause painful burns whenever it comes in contact (even in dilute solution) with the skin and wil quickly destroy any fabric or metal on which it falls. It will also attack wood, for which reason nothing but glass, earthenware, or hard rubber containers should be employed.

Specific Gravity. The weight of a liquid as compared with distilled water is known as its specific gravity. Distilled water at 60° F. is 1. or unity. Liquids heavier than distilled water have a specific gravity greater than unity; lighter liquids, such as gasoline, have a specific gravity less than that of distilled water. Concentrated sulphuric acid (battery acid, as received from the manufacturer) is a heavy oily liquid having a specific gravity of about 1.835. battery will not operate properly on acid of full strength, and it is therefore diluted with sufficient water to bring it down to 1.275. This, however, is the specific gravity of the electrolyte only when the battery is fully charged. The specific gravity of the electrolyte affords the most certain indication of the condition of the battery at any time, and its importance in this connection is outlined at considerable length under the head of Hydrometer Tests. The desired specific gravity can be easily secured by adding concentrated sulphuric acid to the water. Never add the water to the acid as it will cause undue heat.

Action of Cell on Charge. When the elements described are immersed in a jar of electrolyte of the proper specific gravity, and terminals are provided for connecting to the outside circuit, the cell is complete. As the lead-plate storage battery produces current at a potential of but two volts per cell, however, a single cell is

out of the plates into the electrolyte, thus raising the specific gravity of the electrolyte. When practically all of this acid has been transferred from the active material of the plates to the solution, or electrolyte, the cell is said to be fully charged and should then show a specific gravity reading of 1.275 to 1.300. The foregoing refers of course to the initial charge. After the cell has once been discharged, the active material of both groups of plates has been converted into lead sulphate. The action on charge then consists of driving the acid out of the plates and at the same time reconverting the lead sulphate into peroxide of lead in the positive plates and into spongy metallic lead in the negative plates.

Action of Cell on Discharge. The action of the cell on discharge consists of a reversal of the process just described. The acid which has been forced out of the plates into the electrolyte by the charging current again combines with the active material of the plates. when the cell is connected for discharge to produce a current. When the sulphuric acid in the electrolyte combines with the lead of the active material, a new compound, lead sulphate, is formed at both plates. This lead sulphate is formed in the same way that sulphuric acid, dropped on the copper-wire terminals, forms copper sulphate. or dropped on the iron work of the car, forms iron sulphate. In cases of this kind, it will always be noted that the amount of sulphate formed is all out of proportion to the quantity of metal eaten away. In the same manner, when the sulphuric acid of the electrolyte combines with the lead in the plates to form lead sulphate, the volume is such as to completely fill the pores of the active material when the cell is entirely discharged. This makes it difficult for the charging current to reach all parts of the active material and accounts for the manufacturers' instructions, never to discharge the battery below a certain point.


As the discharge progresses, the electrolyte becomes weaker by the amount of acid that is absorbed by the active material of the plates in the formation of lead sulphate, which is a compound of acid and lead. This lead sulphate continues to increase in bulk, filling the pores of the plates, and as these pores are stopped up by the sulphate, the free circulation of the acid is retarded. Since the acid cannot reach the active material of the plates fast enough to maintain the normal action, the battery becomes less active.

which is indicated by a rapid falling off in the voltage. Starting at slightly over 2 volts per cell when fully charged, this voltage will be maintained at normal discharge rates with but a slight drop, until the lead sulphate begins to fill the plates. As this occurs, the voltage gradually drops to 1.8 volts per cell and from that point on will drop very rapidly. A voltage of 1:7 volts per cell indicates practically complete discharge, or that the plates of the cell are filled with lead sulphate and that the battery should be placed on charge immediately.

During the normal discharge, the amount of acid used from the electrolyte will cause the specific gravity of the solution to drop 100 to 150 points, so that if the hydrometer showed a reading of 1.280 when the cell was fully charged, it will indicate but 1.130 to 1.180 when it is exhausted, or completely discharged. The electrolyte is then very weak; in fact, it is little more than pure water. Practically all of the available acid has been combined with the active material of the plates. While the acid and the lead combine with each other in definite proportions in producing the current on discharge, it is naturally not possible to provide them in such quantities that both are wholly exhausted when the cell is fully discharged. Toward the end of the discharge, the electrolyte becomes so weak that it is no longer capable of producing current at a rate sufficient for any practical purpose. For this reason, an amount of acid in excess of that actually used in the plates during discharge is provided. This is likewise true of the active material.

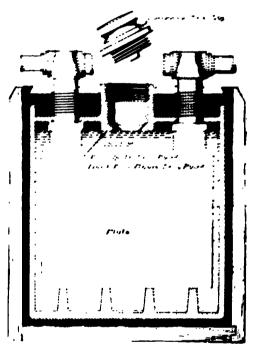٠.

colors con a connected in so implement, a fire sine is material to the refer to a connecting in the cells in energy of the refer to a connecting in the cells in energy of the refer to the cells of the refer to the energy of the respect to the energy of the respect to the energy of the respect of the refer to the energy of the respect of the refer to the energy of the respect of the refer to the refer to the respect to the refer to the respect to the refer to the respect to the refer to the refe



the 1999 of George Willard Starting Dattery, the cone Mod Space

ur the time OF BELLEVILLE agua. I universi fie 5 nounce of a management for Minour out is the faware maa n moreleel they that a terribular collecthe managery of the batterr falls till. The battery in question would not produce of appeared of current for 2 hours. This . . . . . . . . . . . . . . . that the heavy discharge produces lead sulphate si rapidly and in such large quantities that it quickly fills the pores of the active material and prevents further access of the acid to it. Thus while it will not product

attempt to soft current for "hours on continuous discharge, it will be capable of a discharge as great or greater than this by considerable, it allowed periods of rest between. When on open circuit, the storage battery recuperates very rapidly. It is for this reason that when terms to sent the watch should never be kept closed for more than a few econds it a time. Fen trials of 10 seconds each with a half-minute interval between them will exhaust the battery less than will printing, the motor steadily for a minute and forty seconds.

ually overcharged and may need the addition of water to the electrolyte as often as every three days, whereas, in ordinary service, once a week would be sufficient. Even with intermittent use, the battery should not be allowed to run more than two weeks without an inspection of the level of the electrolyte and the addition of distilled water, if necessary. Distilled water is always specified, since the presence of impurities in the water would be harmful to the battery, this being particularly the case where they take the form of iron salts. Where it is not convenient to procure distilled or rain water in sufficient quantities, samples of the local water supply may be submitted to any battery manufacturer for analysis.

While it is necessary to maintain the electrolyte one-half inch over the plates, care must be taken not to exceed this, for, if filled above this level, the battery will flood when charged, owing to the expansion with the increasing temperature. The best time for adding water is just before the car is to be taken out for several hours of use. It may be done most conveniently with a glass and rubber syringe of the type used with the hydrometer. Care should be taken when washing the car to see that no water is allowed to enter the battery box, as it is likely to short-circuit the cells across their lead connectors and to carry impurities into the cells themselves.

Adding Acid. When the level of the electrolyte in the cell becomes low, it is, under normal conditions, caused by the evaporation of the water, and this loss should be replaced with water only. There being no loss of acid, it should never be necessary to add acid to the

Edison Cell Not Available. It will be noted that the foregoing description has been confined entirely to the lead-plate type of storage battery and that no mention has been made of the Edison cell. The latter is not available for starting service on the automobile, because its internal resistance is too high to permit the extremely heavy discharge rate that is necessary. In extremely cold weather or where the engine is unusually stiff for other reasons, this may be as high as 300 amperes momentarily, while, under ordinary conditions, it will reach 150 to 200 amperes at the moment of closing the switch The efficiency of the Edison cell also drops off very markedly in cold

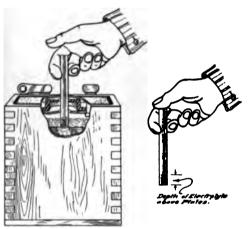


Fig. 385. Diagram Showing Method of Measuring Height of Electrolyte over Plates

Courtesy of U. S. Light and Heat Corporation,
Niagara Falls, New York


weather, though this is also true to a lesser extent of the lead-plate type

#### CARE OF THE BATTERY

The following instructions are given about in the order in which it is necessary to apply them in the care of a storage battery.

Adding Distilled Water. In order to function properly, the plates in the cells must be covered by the electrolyte at

all times to a depth of half an inch. Fig. 385 shows a handy method of determining this definitely. A small piece of glass tube, open at both ends, is inserted in the vent hole of the battery until it rests on the tops of the plates. A finger is then pressed tightly on top of the upper end of the tube, and the tube is withdrawn. It will bring with it at its lower end an amount of acid equivalent to the depth over the plates. This should always be returned to the same cell from which it was taken. The electrolyte consists of sulphuric acid and water. The acid does not evaporate, but the water does. The rapidity with which the water evaporates will depend upon the conditions of charging. For example, if a car is constantly driven on long day runs and gets very little night use, the storage battery is likely to be contin-

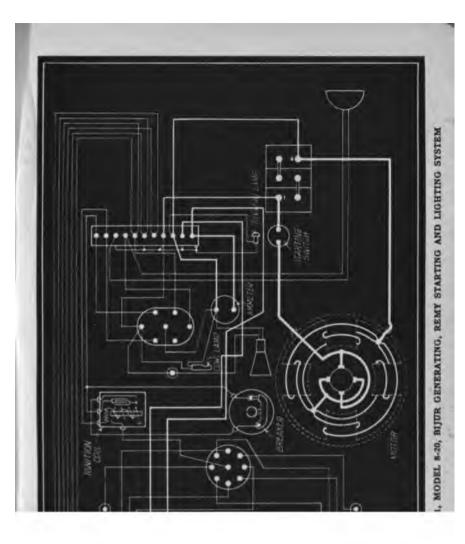

test the condition of the cells with the hydrometer. This is termed taking the specific gravity and is one of the most important tests in connection with the care of the battery. The specific gravity of a liquid is determined by means of an instrument consisting of a weighted glass tube having a scale marked on it. This instrument is the hydrometer, and in distilled water at 60 degrees it should sink until the scale comes to rest at the surface of the liquid at the division 1.000. The lighter the liquid, the further the instrument will sink

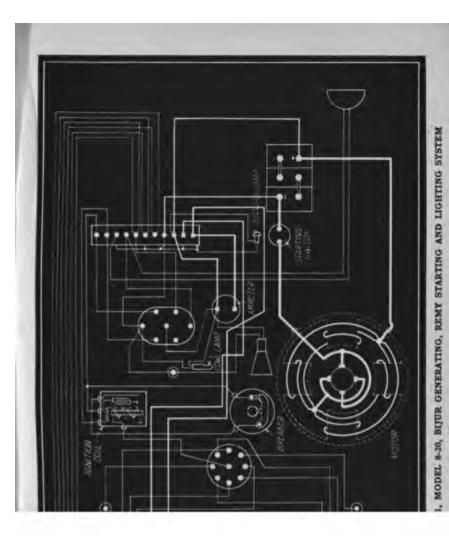



Fig. 386. Syringe Hydrometer Set

in it; the heavier the liquid, the higher the instrument will float. For constant use in connection with the care of lighting and starting batteries, the hydrometer shown in Fig. 386 will be found the most convenient. Where the battery is located on the running board of the car, the test may be made without removing the syringe from the cell. but care must be taken to hold it vertical to prevent the hydrometer from sticking to the sides of the glass barrel. Wherever possible, the reading should be made without removing the syringe from the vent hole of the cell, so that the electrolyte thus withdrawn may always be returned to the same cell. Where the battery is located in a position difficult of access, as under the floor boards, the syringe may be drawn full of electrolyte and then lifted out; as the soft rubber plug in the bottom of the glass barre is in the form of a trap, when the instrument is held vertical, the solution will not

run out while the reading is being taken.

Failure to replace the electrolyte in the same cell from which it was taken will result in destroying the uniformity of the cells For example, if electrolyte has been withdrawn from cell No. 1 of the battery and, after taking the reading, it is put into cell No. 2 the amount taken from No. 1 must later be made up by adding water and the solution will be that much weaker, while the electrolyte of No. 2 will be correspondingly stronger.



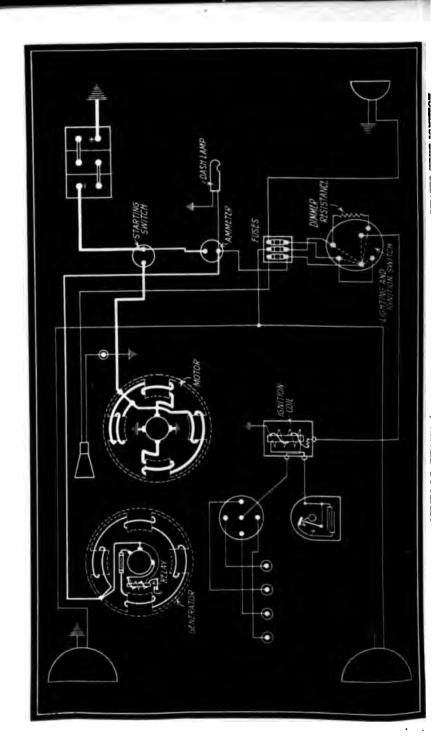





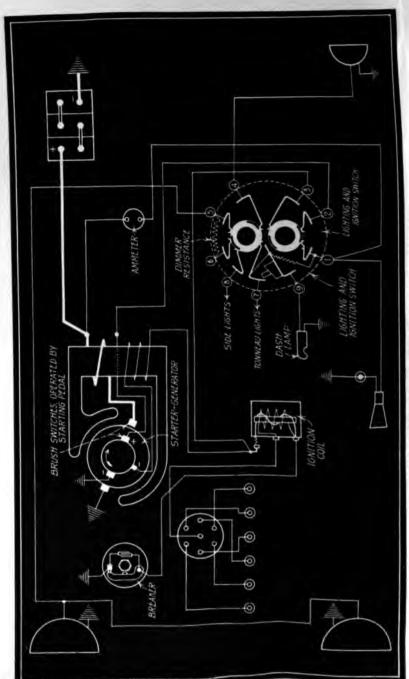



PLATE 196 BUICK 1922, MODEL 22-6, DELCO SYSTEM

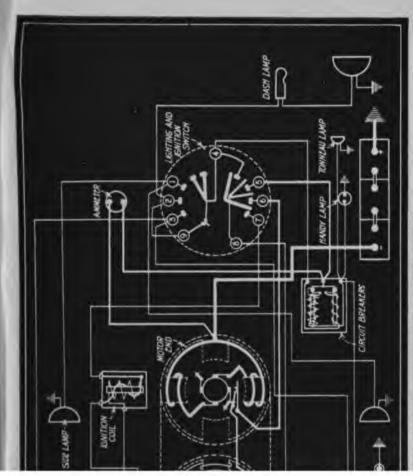


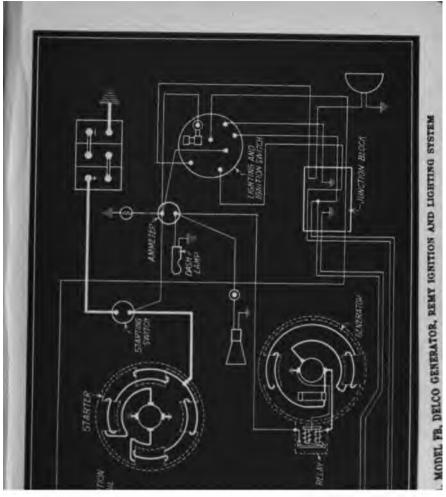
E 197-CADILLAC 1920-21, MODEL 59, DELCO SYSTEM







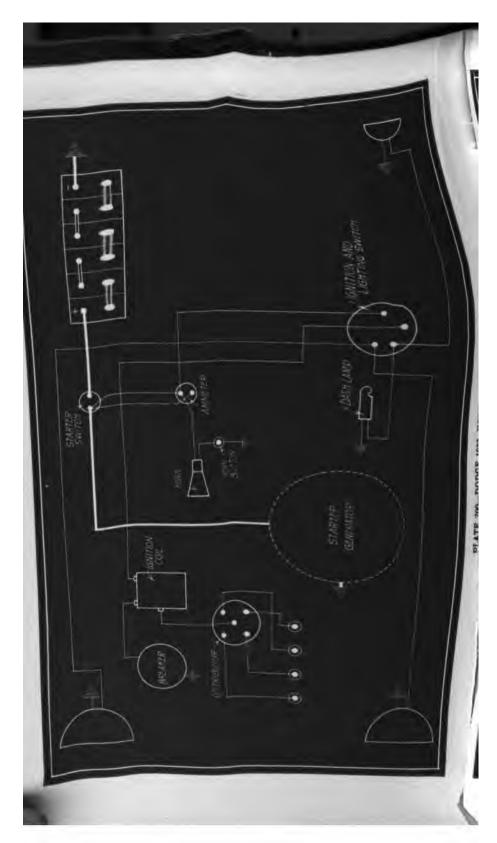


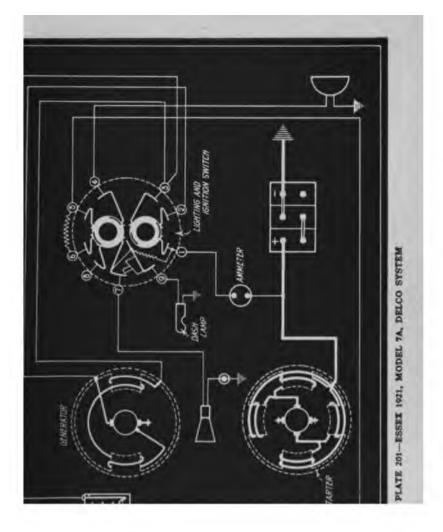

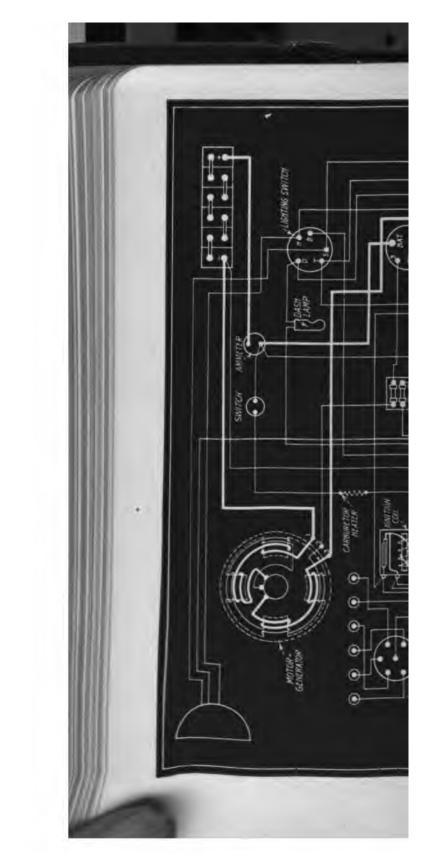


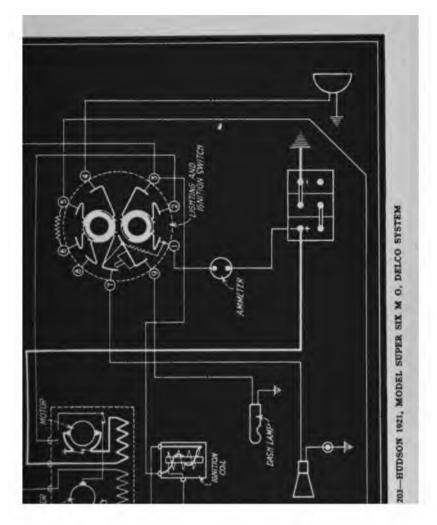


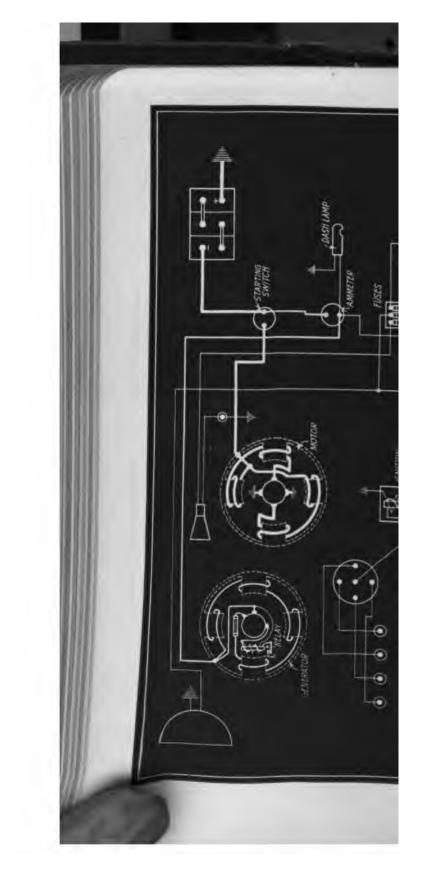


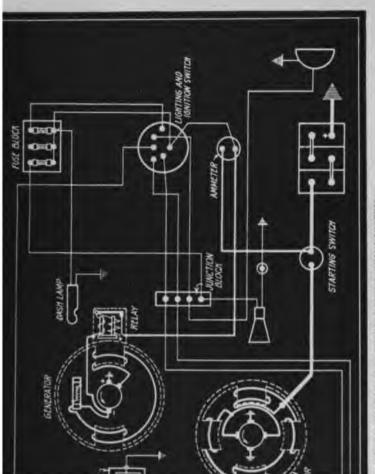

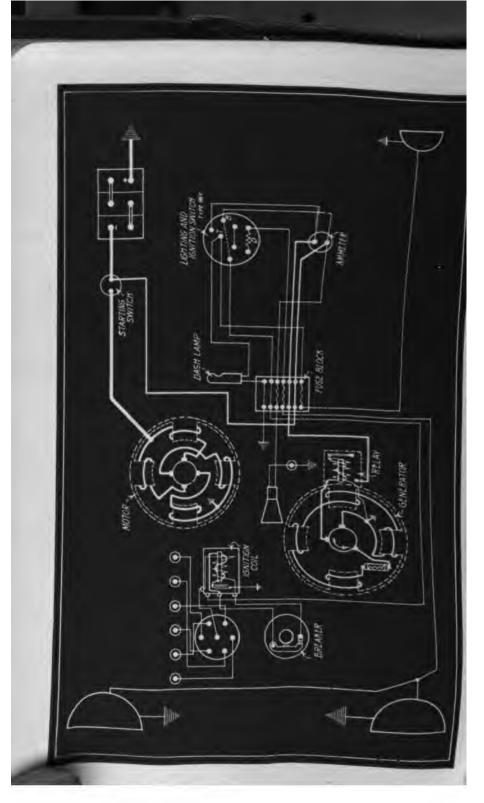E 205-KISSEL KAR 1921, CUSTOM BUILT, REMY SYSTEM



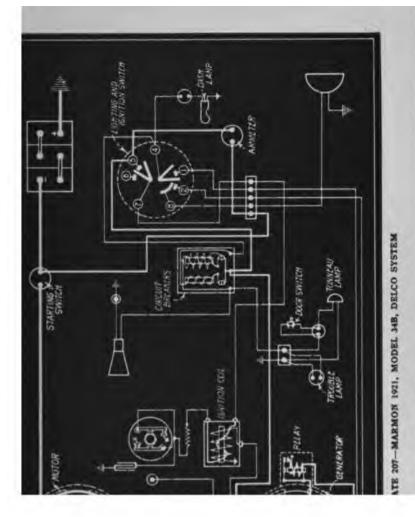

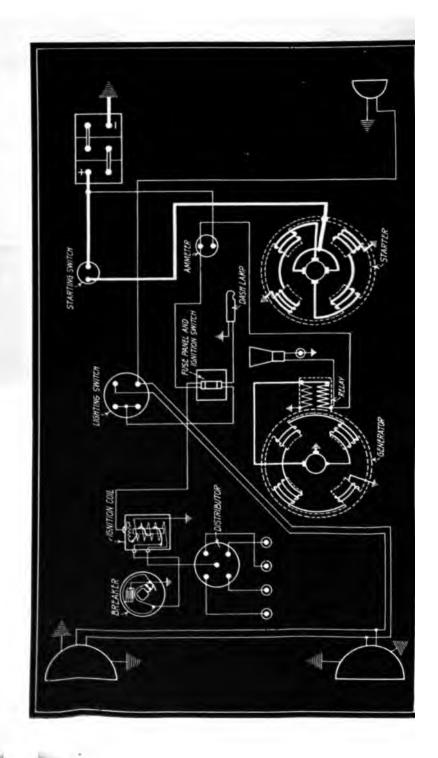

Hudrometer Tests. In taking a hydrometer reading, first see that the instrument is not held by the sides of the glass syringe harrel; then note the level of the instrument in the liquid by looking at it from below, i.e., hold it up above the level of the eye. Reading the hydrometer in this way is found to give more accurate results than looking down upon it. While the hydrometer affords the best single indication of the condition of the battery—the cells should test 1.250 to 1.300 when fully charged and 1.150 when fully discharged, below which point they should never be allowed to gothere are conditions under which the instrument may be entirely misleading. For example, when fresh distilled water is added to a cell to bring the solution up to the proper level, the additional water does not actually combine with the electrolyte until the cell has been on charge for some time. Consequently, if a hydrometer reading were taken of that particular cell just after the water had been added, the test would be misleading, as it would apparently show the cell to be nearer the fully discharged state than it actually was, owing to the low specific gravity of the electrolyte. If, on the other hand, fresh electrolyte or pure acid has been added to a cell just prior to taking readings, and without the knowledge, of the tester the reading would apparently show the battery to be fully charged. whereas the reverse might be the case. In this instance, the specific gravity would be higher than it should be. To determine accurately the condition of the cells in such circumstances, the hydrometer readings would have to be checked by making tests with the voltthe cause of which may be definitely assigned one way or the other by the aid of the hydrometer is that "the battery is not holding its charge". Except where it is allowed to stand for long periods without use, as where a car is laid up for a month or more, there is no substantial decrease in the capacity simply through standing unless the battery is allowed to stand in a discharged condition.

Consequently, the owner's impression that the charge of the battery is mysteriously leaking away overnight through some short coming of the cells themselves is not correct. If there is a fault, it is probably in the wiring; or a switch may have been left on inadvert ently; or, as is very often the case, the car is not driven long enough in daylight to permit the generator to charge the battery sufficiently When driving at night with all lights on, as is commonly the custom the generator supplies very little current in excess of that required by the lamps. As a result, the battery receives but a fraction of its normal charge, so that one or two attempts to use the starting motor exhaust it. A hydrometer test made just before using the starting motor will show that there is only a small fraction of a charge in the cells, so that they are not capable of supplying sufficient current to turn the engine over longer than a few seconds. The hydrometer is equally valuable in indicating when a battery is being overcharged. though this is a condition which carries its own indication, known as gassing, which is described in detail under that head.

Variations in Readings. Specific-gravity readings between 1.275 and 1.300 indicate that the battery is fully charged; between 1.200 and 1.225, that the battery is more than half discharged between 1.150 and 1.200, that the battery is quickly nearing a fully discharged condition and must be recharged very shortly, otherwise injury will result. Below 1.150 the battery is entirely exhausted and must be recharged immediately to prevent the plates from becoming sulphated, as explained in the section covering that condition.

Where the specific gravity in any cell tests more than 25 points lower than the average of the other cells in the battery, it is an indication that this cell is out of order. Dependence should not be placed, however, on a single reading where there is any question as to the specific gravity. Take several readings and average them. Variations in cell readings may be caused by internal short-circuits in the cell; by putting too much water in the cell and causing a loss

of electrolyte through flooding or overflowing; or by loss of electrolyte from a cracked or leaky jar. Internal short-circuits may result from a broken separator or from an accumulation of sediment in the mud space of the jars reaching the bottom of the plates.

Quite a substantial percentage of all the troubles experienced with starting batteries, which are only too often neglected until they give out, is caused by letting the electrolyte get too low in the jars. The effect of this is to weaken the battery, causing it to discharge more readily, and frequently resulting in harmful sulphating of the plates and injury to the separators. When such sulphating occurs, it permits the plates to come into contact with each other, and an internal short-circuit results. The importance of always maintaining the electrolyte one-half inch above the tops of the plates will be apparent from this.

One of the most frequent causes of low electrolyte in a single cell is the presence of a cracked or leaky jar. If one of the cells requires more frequent addition of water than the others to maintain the level of its electrolyte, it is an indication that it is leaking. Where all the cells of a battery require the addition of water at unusually short intervals, it is an indication that the battery is being constantly overcharged. (See Gassing.) Unless a leaky jar is replaced immediately, the cell itself will be ruined, and it may cause serious damage to the remainder of the battery. Jars are often broken owing to the hold-down bolts or straps becoming loose, thus allowing the

care should be taken to keep it constantly in a charged condition A variation in the temperature also affects the hydrometer reading themselves. The effect of the temperature on the hydrometer test is explained under Adjusting the Specific Gravity.

Low Cells. When one cell of the battery tests more than 2 points below the specific gravity of the others, as shown by th average of several readings taken of each, it should be placed of charge separately from an outside source of current. This may b done without removing it from the car or disconnecting it from th other cells, since the charging leads may be clipped to its termina posts. If no other facilities are available and direct-current service is at hand, use carbon lamps as a resistance in the manner illustrate on another page. As the normal charging rate of the average startin battery is 10 to 15 amperes or more, that many 32-c.p. carbo filament lamps may be used in the circuit. Where only alternatin current is available, a small rectifier, as described under Chargin from Outside Sources, will be found most convenient in garage not having enough of this work to warrant the installation of motor-generator. After the low cell has been on charge for an hou or two, note whether or not its specific gravity is rising, by taking hydrometer reading. If, after several hours of charging, its specifi gravity has not risen to that of the other cells, it is an indication that there is something wrong with the cell, and it should be cu out. (See Replacing a Jar and Overhauling the Battery.)

Adjusting the Specific Gravity. Except in such cases as thos mentioned under Hydrometer, where water has been added to the electrolyte just before testing, or electrolyte has been added without the knowledge of the tester, specific gravity of the electrolyte is the best indication of the condition of the cell, and the treatment to be given should always be governed by it. As explained in the section on Action on Charge and Discharge, the acid of the electrolyte combines with the active material of the plates to produce the current of discharge. The further the cell is discharged the more acid there will be in the plates, and the less in the solution. Consequently low-gravity readings practically always mean lack of acid in the solution, and that implies lack of charge. Unless there is something wrong with the cell, charging will restore the acid to the electrolyte and bring the specific-gravity readings up to normal. In case a joint of the condition of the case and the condition of the case and the case

is leaking or has been overturned and lost some of its electrolyte, no amount of charging will bring its specific gravity up to the proper point.

The gravity readings of the cells vary somewhat in summer and winter, and they also decrease with the age of the plates, but the battery will continue to give good service as long as its specific gravity rises to between 1.250 and 1.300 when fully charged. In case it rises above 1.300, there is an indication that excess acid has been added to the electrolyte, and this must be corrected by drawing off some of the electrolyte with the syringe and replacing it with distilled water. A gradually decreasing specific gravity in all the cells of a battery is an indication that sediment is accumulating in the bottom of the jars and that the battery, if of the old type with low mud space, requires washing; if of the later type with high mud space, that its elements require renewal. Before accepting this conclusion, however, make certain that the low reading is not due to insufficient charging. In actual practice, starter batteries seldom remain long enough in service without overhauling ever to need washing.

Many starter batteries are kept in an undercharged condition so constantly, owing to frequent use of the starting motor with but short periods of driving in between, that they should be put on charge from an outside source at regular intervals. In fact, this is the only method of determining definitely whether the battery itself is really at fault or whether it is the unfavorable conditions The necessity for adjusting the specific gravity of the electrolyte in a cell can only be determined by first bringing it to its true maximum. To do this with a starter battery, it must be put on charge from an outside source at a low rate, say 5 amperes, and kept on charge continuously until tests show that the specific gravity of the electrolyte has ceased to rise. This may take more than twenty-four hours, and readings should be taken every hour or so, toward the end of the charge. Should the battery begin to gas violently while tests show that the specific gravity is still rising, the charging current should be reduced to stop the gassing, or, if necessary, stopped altogether for a short time and then renewed.

If after this prolonged charge, the specific gravity is not more than 25 points below normal, some of the solution may be drawn off with the syringe and replaced with small quantities of 1.300 electrolyte, which should be added very gradually to prevent bringing about an excess. Should the specific gravity be too high at the end of the charge, draw off some of the electrolyte and replace it with distilled water to the usual level of one-half inch over the plates. A charge of this kind is usually referred to as a conditioning charge and, given once a month, will be found very greatly to improve starter batteries that are constantly undercharged in service.

Temperature Corrections. All specific-gravity readings mentioned are based upon a temperature of 70° F. of the electrolyte, and as the electrolyte, like most other substances, expands with the heat and contracts with the cold, its specific gravity is affected by variations of temperature. This, of course, does not affect its strength, but as its strength is judged by its specific gravity, the effect of the temperature must be taken into consideration when making the tests. The temperature in this connection is not that of the surrounding air but that of the electrolyte itself, and as the plates and solution of a battery increase in temperature under charge, the electrolyte may be 70° F. or higher, even though the outside air is close to zero. Consequently, the only method of checking this factor accurately is to insert a battery thermometer in the vent hole of the cell. If, on the other hand, the battery has been standing idle for some time in a cold place, the electrolyte has the same temperature as the surrounding air, and a hydrometer reading taken without a temperature correction would be very misleading.

For example, assume that the car is standing in a barn in which the temperature is 20° F, and that it has not been running for some time so that the electrolyte is as cold as the surrounding air. hydrometer reading shows the specific gravity of the electrolyte to be 1.265, which would indicate that the battery was approximately fully charged. But the correction for temperature amounts to one point (.001) for each three degrees above or below 70° F., and in this case a difference of 50 degrees would have to be allowed for. This amounts to practically 18 points, and the specific gravity of the cells is 1.265 minus 18, or 1.247. The battery is accordingly threequarters charged, instead of fully charged as the uncorrected reading would appear to indicate. The electrolyte contracts with the drop in temperature, and its specific gravity becomes correspondingly higher without any actual increase in its strength. The opposite condition will be found when the battery has commenced to gas so violently that the temperature of the electrolyte is raised to 100° to 105° F. At the former figure there would be a difference of 30 degrees, or 10 points, to allow for, in which case a specific gravity reading of 1.265 would actually be 1.275. Hydrometer scales, with a a temperature scale showing at a glance the corresponding correction necessary, simplify the task of correcting the readings; but to do this properly a battery thermometer must be employed, as the temperature of the electrolyte itself is the only factor to be considered.

Gassing. When an electric current is sent through a storage-



a point is reached at which there is no longer sufficient sulphate remaining to utilize all the current that is passing through the cell.

The excess current will then begin to do the next easiest thing, which is to decompose the water of the electrolyte and liberate hydrogen gas. This gassing is not owing to any defect in the battery, as some owners seem to think, but is simply the result of overcharging it. In one instance, a car owner condemned the starting battery with which his machine was equipped, for the reason that it was "always boiling". In fact, it "boiled" itself to pieces and had to be replaced by the manufacturer of the car after only a few months of service; while, as a matter of fact, the conditions under which the car was driven were wholly responsible. It was used for long runs in the day time with infrequent stops, and was rarely run at night; therefore, the battery was continually charging but seldom had an opportunity to discharge.

This erroneous impression is also closely interlinked with another that is equally common and equally harmful. This is that one of the functions of the battery cut-out is to break the circuit and prevent the battery from becoming overcharged. It is hardly necessary to add that this is not one of its functions, but that as long as the generator is being driven above a certain speed, the cut-out will keep the battery in circuit, and the generator will continue to charge it. Its only purpose is to prevent the battery from discharging itself through the generator when the speed of the generator falls to a point where its voltage would be overcome by that of the battery unless the battery were automatically disconnected. The cut-out does not protect the battery from being overcharged; only the driver or the garage man can do that by noting the conditions under which the car is operated and taking precautions to prevent the battery from overcharging.

Gassing is simply an indication that too much current is being sent into the battery. Another indication of the same condition is the necessity for refilling the cells with distilled water at very short intervals, as an excess charge raises the temperature of the electrolyte and causes rapid losses by evaporation. That is the reason why it is likely to be so harmful to the battery unless remedied, as if allowed to exceed 110° F., the active material is likely to be forced the grids, and the cells to be ruined. While it is essential

that the battery be fully charged at intervals and that it be always kept well charged, continuously overcharging it is likely to be as harmful as allowing it to stand undercharged. Where the conditions of service cannot be altered to remedy the trouble, the regulator of the generator should be adjusted to lower the charging rate, or, if nothing else will suffice, additional resistance, controlled by an independent switch, may be inserted in the charging circuit. (The U.S.L. system has a provision to safeguard the battery against overcharge, termed the touring switch.)

Higher Charge Needed in Cold Weather. While the regulator of the generator is set by the manufacturer to give the best average results, and some makers warn the user against altering its adjustment, experience has demonstrated that a fixed adjustment of the regulation will not suffice for cars driven under all sorts of service conditions, nor for the same car as used at different seasons of the year. The efficiency of the storage battery is at its lowest in cold weather, which is the time when the demand upon it is greatest. A battery that would be constantly overcharged during the summer may not get more than sufficient current to keep it properly charged in winter, though driven under similar conditions in both seasons. On the other hand, a battery that is generally undercharged under summer conditions of driving will be practically useless in winter, as it will not have sufficient current to meet the demands upon it.

It may be put down as a simple and definite rule that if the battery of a starting system never reaches the gassing stage, it is constantly undercharged and is rapidly losing its efficiency, as the sulphate remaining on the plates becomes harder with age and prevents the circulation of the electrolyte. Even when in the best condition, the electrolyte cannot reach all of the active material in the plates, so that any reduction means a serious falling off. Likewise, when a battery is constantly gassing, it is in a continuous state of overcharge and is apt to be entirely ruined in a comparatively short time. The danger from undercharging is known as sulphating—the plates become covered with a hard coating of lead sulphate that the electrolyte cannot penetrate—while that from overcharging is due to the electrolyte and the plates reaching a dangerous temperature (105° F. or over) at which the active material is apt to be stripped from the grids. The conditions of service, on the average, are such

that a battery can seldom be kept in good condition for any length of time on the charging current from the generator alone.

The hydrometer should be used frequently to keep track of its condition and, at least once a month, it should be given a long conditioning, or equalizing, charge, as it is variously termed. This charge is required because of the fact that, under ordinary conditions, a battery seldom receives a complete charge and that every time it is discharged without this being followed by a charge which is prolonged until the electrolyte has reached its maximum specific gravity, more lead sulphate accumulates in the plates. The object of the long charge is to convert this lead sulphate into peroxide of lead at the positive plate and into spongy metallic lead at the negative plate, as explained further under the head of Sulphating.

Sulphating. At the end of a discharge, both sets of plates are covered with lead sulphate. This conversion of the active material of the plates into lead sulphate, which takes place during the discharge, is a normal reaction and, as such, occasions no damage. But if the cells are allowed to stand for any length of time in a discharged condition, the sulphate not only continues to increase in bulk, but becomes hard. It is also likely to turn white, so that white spots on the plates of a battery when it is dismantled are an indication that the cells have been neglected. In this condition, the plates have lost their porosity to a certain extent and it is correspondingly more difficult for the charging current to penetrate the active material. When a battery has stood in a discharged condition for any length of time, it becomes sulphated. The less current it has in it at the time and the longer it stands, the more likely it is to be seriously damaged.

Where a car is used but little in the daytime, and then only for short runs with more or less frequent stops, the battery never has an opportunity to become fully charged. The demands of the starting motor and the lights are such that the battery is never more than half charged at any time. Consequently, there is always a certain proportion of the lead sulphate that is not reconverted, but which remains constantly in the plates. As already mentioned, this condition does not remain stationary; the sulphate increases in amount and the older portions of it harden. This represents

of capacity which finally reaches a point where the cells are

no longer capable of supplying sufficient current (holding enough of the charge, as the owner usually puts it) to operate the starting motor. A battery that has been operating under conditions of this kind is not prepared for the winter's service, which accounts for the great number of complaints about the poor service rendered by starting systems in the early part of every winter. As long as the weather is warm, the battery continues to supply sufficient current in spite of the abuse to which it is subjected, but when cold weather further reduces its efficiency, it is no longer able to meet the demand.

The only method of preventing this and of remedying it after it has occurred is the equalizing charge mentioned in the previous section. Long continued and persistent charging at a low rate will cure practically any condition of sulphate, the time necessary being proportionate to the degree to which it has been allowed to extend. It is entirely a question of time, and, as a high rate would only produce gassing, which would be a disadvantage, the rate of charge must be low. In case the cells show any signs of gassing, the charge must be further reduced.

Extra Time Necessary for Charging. The additional length of time necessary for charging a battery that has been constantly kept in an undercharged condition is strikingly illustrated by the following test made with an electric vehicle battery: The cells were charged to the maximum, and the specific gravity regulated to exactly 1.275 with the electrolyte just \(\frac{1}{2}\) inch above the tops of the plates, this height being carefully marked. The battery was then discharged and recharged to 1.265 at the normal rate in each case. The specific gravity rose from 1.265 to 1.275 during the last hour and a half of the charge. During the following twelve weeks. the battery was charged and discharged daily, each charge being only to 1.265, thus leaving 10 points of acid still in the plates. the end of the twelve weeks, the charge was continued to determine the time required to regain the 10 points and thus restore the specific gravity to the original 1.275. Eleven hours were needed, as compared with the hour and half needed at first. This test further illustrates why it is necessary to give a battery an occasional overcharge or equalizing charge to prevent it becoming sulphated. Had the battery in question been charged daily to its maximum of 1.275 and discharged to the same extent during the twelve weeks, 9½ hours of the last charge would have been saved. These periods of time, of course, refer to the charging of the electric-vehicle battery, but they indicate in a corresponding manner the loss of efficiency suffered by the starting battery owing to its being continually kept in an undercharged condition.

Restoring Sulphated Battery. There are only three ways in which a battery may become sulphated: The first and most common of these is that it has not been properly charged; second, excess acid has been added to the electrolyte; third, an individual cell may become sulphated through an internal short-circuit or by drying out, as might be caused by failure to replace evaporation with water, or failure to replace promptly a cracked jar. The foregoing only holds good, however, where the sediment has not been allowed to reach the bottom of the plates, and where the level of the electrolyte has been properly maintained by replacing evaporation with distilled water.

To determine whether a battery is sulphated or not—it having been previously ascertained that it does not need cleaning (washing) it should be removed from the car (the generator should not be run with the battery off the car without complying with the manufacturer's instructions in each case, usually to short-circuit or bridge certain terminals on the generator itself) and given an equalizing charge at its normal rate. The normal rate will usually be found on the name plate of the battery. If the battery begins to gas at this rate, the rate must be reduced to prevent gassing, and lowered further each time the cells gas. Frequent hydrometer readings should be taken, and the charge should be continued as long as the specific gravity continues to increase. A battery is sulphated only when there is acid retained in the plates. When the specific gravity reaches its maximum, it indicates that there is no more sulphate to be acted upon, since, during the charge, the electrolyte receives acid from no other source. With a badly sulphated battery, the charge should be continued until there has been no further rise in the specific gravity of any of the cells for a period of at least twelve hours. Maintain the level of the electrolyte at a constant height by adding pure water after each test with the hydrometer (if water were added just before taking readings, the water would rise to the top of the solution

and the reading would be valueless). With a battery on a long charge, the battery thermometer should be used at intervals to check the temperature of the electrolyte, and the hydrometer readings should be corrected in accordance with the temperature.

Specific Gravity too High. Should the specific gravity of any of the cells rise above 1.300, draw off the electrolyte down to the top of the plates and put in as much distilled water as possible without flooding the cell. Continue the charge and, if the specific gravity again exceeds 1.300, this indicates that acid has been added during the previous operation of the battery. The electrolyte should then be emptied out and replaced with distilled water and the charge continued. The battery can only be considered as restored to efficient working condition when there has been no rise in the specific gravity of any of the cells during a period of at least twelve hours of continuous charging.

Upon completion of the treatment, the specific gravity of the electrolyte should be adjusted to its proper value of 1.280, using distilled water or 1.300 acid, as necessary. In cases where one cell has become sulphated while the balance of the battery is in good condition, it is usually an indication that there is a short-circuit or other internal trouble in the cell, though this does not necessarily follow. To determine whether or not it is necessary to dismantle the cell, it may first be subjected to a prolonged charge, as above described. If its specific gravity rises to the usual maximum, the

reading of all the cells being within at least 25 points of each other sulphating may be avoided entirely.

Internal Damage. This trouble is usually caused by a short circuit, owing either to an accumulation of sediment reaching the plates or to the breaking of a separator, which may be caused by the active material being forced out of the grid, usually termed buckling which is caused by overheating. It is important to be able to determine whether or not the low efficiency of a certain cell is caused by internal trouble without having to dismantle the cell. The reparaman's most important aid for this class of work is the high-grad portable voltmeter mentioned in connection with other tests of the starting and lighting system.

Voltage Tests. Under some conditions, the voltmeter will ak indicate whether the battery is practically discharged or not, bu like the hydrometer, it should not be relied upon alone. To insur accuracy, it must be used in conjunction with the hydromete Since a variation as low as .1 (one-tenth) volt makes considerable difference in what the reading indicates regarding the condition the battery, it will be apparent that a cheap and inaccurate voltmet would be a detriment rather than an aid. The instrument illustrate in connection with tests of other parts of starting and lighting system (see Delco) is of the type required for this service. Complet instructions for its use will be received with the instrument, and the must be followed very carefully to avoid injuring it. For example on the three-volt scale, but one cell should be tested; attempting to test the voltage of more than one cell on this scale is apt to bur out the three-volt coil in the meter. The total voltage of the number of cells to be tested must never exceed the reading of the particula scale being used at the time; otherwise, the coil of the scale in questio will suffer, and the burning out of one coil will make it necessar to rebuild the entire instrument.

Clean Contacts Necessary. Where the voltage to be tested is so low, a very slight increase in the resistance will affect it considerable and thus destroy the accuracy of the reading. Make certain that the place on the connector selected for the contact point is clean and bright, and press the contact down on it firmly. To insure clean bright contact point, use a fine file on the lead connector. The contact will be improved by filing the test points tairly share.

Even a thin film of dirt or a weak contact will increase the resistance to a point where the test is bound to be misleading. The positive terminal of the voltmeter must be brought into contact with the positive terminal of the battery, and the negative terminal of the voltmeter with the negative of the battery. If the markings of the cell terminals are indistinct, connect the voltmeter across any one cell. In case the pointer butts up against the stop at the left instead of giving a reading, the connections are wrong and should be reversed; if the instrument shows a reading for one cell, the positive terminal of the voltmeter is in contact with the positive of the battery. This test can be made with a voltmeter without any risk of short-circuiting the cell, as the voltmeter is wound to a high resistance and will pass very little current. Connecting an ammeter directly across a cell, however, would short-circuit it and instantly burn out the instrument.

How to Take Readings. It is one of the peculiarities of the storage cell that when on "open circuit", i.e., not connected in circuit with a load of any kind, it will always show approximately two volts, regardless of whether it is almost fully charged or almost the reverse. Consequently, voltage readings taken when the battery is on open circuit, i.e., neither charging nor discharging, are valueless, except when a cell is out of order. Therefore, a load should be put on the battery before making these tests. This can be done by switching on all the lamps. With the lights on, connect the voltmeter, as already directed, and test the individual cells. If the battery is in good condition, the voltage readings, after the load

when any battery trouble is suspected. Then test again with the voltmeter. If the voltage of each cell does not rise to approximatel two volts after the battery has been on charge for ten minutes of more, it is an indication of internal trouble which can be remedie only by dismantling the cell. (See instructions under that heading

Temperature Variations in Voltage Test. When making voltage tests, it must be borne in mind that the voltage of a cold battery rise slightly above normal on charge and falls below normal on discharge. The reverse is true of a warm battery in hot weather, i.e., the voltage will be slightly less than normal on charge and higher than normal on discharge. As explained in connection with hydrometer test of the electrolyte, the normal temperature of the electrolyte make be regarded as 70° F., but this refers only to the temperature of the liquid itself as shown by the battery thermometer, and not the temperature of the surrounding air. For the purpose of simple tests for condition, voltage readings on discharge are preferable as variations in readings on charge mean little except to one experienced in the handling of storage batteries.

Joint Hydrometer and Voltmeter Tests. As already explained above, neither the hydrometer nor the voltmeter reading alon can always be taken as conclusive evidence of the condition of the battery. There are conditions under which one must be supple mented by the other to obtain an accurate indication of the stat of the battery. In making any of the joint tests described below it is important to take into consideration the four points following

- (1) The effect of temperature on both voltage and hydromete readings.
- (2) Voltage readings should be taken only with the batter, discharging, as voltage readings on an idle battery in good condition indicate little or nothing.
- (3) Never attempt to use the starting motor to supply discharge load for the battery, because the discharge rate of th battery is so high while the starting motor is being used that ever in a fully charged battery it will cause the voltage to drop rapidly
- (4) The voltage of the charging current will cause the voltag of a battery in good condition to rise to normal or above the momen it is placed on charge, so that readings taken under such circumstance are not a good indication of the condition of the battery.

In any battery which is in good condition, the voltage of each cell at a normally low discharge rate, i.e., 5 to 10 amperes for a starter battery of the 6-volt type or slightly less for a higher voltage battery, will remain between 2.1 and 1.9 volts per cell until it begins to approach the discharged condition. A voltage of less than 1.9 volts per cell indicates either that the battery is nearly discharged or is in a bad condition. The same state is also indicated when the voltage drops rapidly after the load has been on for a few minutes. The following joint hydrometer and voltmeter tests issued by the Prest-O-Lite Company of Indianapolis will be found to cover the majority of cases met with in actual practice.

(1) A voltage of 2 to 2.2 volts per cell with a hydrometer reading of 1.275 to 1.300 indicates that the battery is fully charged and in good condition.

(2) A voltage reading of less than 1.9 volts per cell, with a hydrometer reading of 1.200 or less indicates that the battery is almost completely discharged.

(3) A voltage reading of 1.9 volts or less per cell, with a hydrometer reading of 1.220 or more, indicates that excess acid has been added to the cell. Under these conditions, lights will burn dimly, although the hydrometer reading alone would appear to indicate that the battery was more than half charged.

(4) Regardless of voltage—high, low, or normal—any hydrometer reading of over 1.300 indicates that an excessive amount of acid has been added.

(5) Where a low voltage reading is found, as mentioned in cases 2 and 3, to determine whether the battery is in bad order or merely discharged, stop the discharge by switching off the load, and put the battery on charge, cranking the engine by hand, and note whether the voltage of each cell rises promptly to 2 volts or more. If not, the cell is probably short-circuited or otherwise in bad condition.



thus become badly sulphated, or they ar where the temperature passes the danger hot, the acid attacks and injures the wo average life is about one year. Excepti those cases where the battery has been which results in unusually long life without the cells for either cleaning or the insertion cases are so in the minority, however, that usually recommend that the car owner overhauled in the fall to put it in the best as well as for the following year. Even



Fig. 387. Drilling Off Cont Courtesy of Electric Storage Battery Company, Pl

given conscientious attention, the condiautomobile are likely to vary so radically t impossible to keep the cells in a good st considered the best practice to give all hauling once a year. The method of d succeeding sections.

Replacing a Jar. When a cell require water more often than the other cells of test to the same specific gravity as the other tion that there is a leak in the jar. Failure gravity reading is not proof of this cond

low from other causes, but the loss of electrolyte is certain evidence of it. The only remedy is to replace the jar at fault.

After locating the cell in question, carefully mark the connectors so as to be sure to replace them the same way. Disconnect the cell from the others in the battery. This may be done either with the aid of brace and bit, which is used to drill down through the post of the connector, Fig. 387, or with a gasoline torch which should be applied carefully to the strap at the post. When the metal has become molten, pry the strap up on the post with a piece of wood. Do not use a screwdriver or other metal for this purpose as it is apt to short-circuit one or more of the cells. Care must also be taken not to apply so much heat that the post itself will be melted as this would make it difficult to reconnect the cell. For one not

accustomed to handling the torch, it will be safer to drill out the post, as illustrated. Lift the complete cell out of the battery box and then use the torch to warm the jar around the top to soften the sealing compound that holds the cover, Fig. 388. Grip the jar between the feet, take hold of the two connectors and pull the element almost out



melt in some more lead until the eye of the connector is filled level. This is termed lead burning and is described at greater length in a succeeding section. Where no facilities are at hand for carrying it out, it may be done with an ordinary soldering copper. The copper is brought to a red heat so that all the tinning is burned off, and no flux of any kind is used. The method of handling the soldering copper and the lead-burning strip to supply the extra metal required to fill the eye is shown in Fig. 391.






Fig. 389. Lifting Elements out of Jar by Hand

Fig. 390. Installing Elements in Jar Courtesy of Electric Storage Battery Company, Philadelphia, Pennsylvania

Put the battery on charge from an outside source, and when the cells begin to gas freely, reduce the current to half the finishing rate given on the battery name plate and charge at this rate as long as there is any rise in the specific gravity of the electrolyte in this or any of the other cells. The maximum gravity has been reached when there has been no rise in the specific gravity for a period of three hours. If the gravity of the cell having the new jar is then over 1.280, draw off some of the electrolyte and replace it with distilled water. If the gravity is below 1.270, draw off some of the electrolyte and replace it with 1.300 electrolyte. If necessary to put in 1.300 electrolyte, allow the battery to continue charging for about one-half hour longer at a rate sufficient to cause gassing, which will cause the stronger acid to become thoroughly mixed with the rest of the electrolyte in the cell.

 Overhauling the Battery. As already mentioned, it will be found desirable to overhaul the majority of starter batteries at least once a year. The expense to the car owner will be less than





Dismounting Cells. Remove the connectors by drilling, heating, or pulling (in the same manner as a wheel is pulled), and loosen the jar covers by heating or running a hot putty knife around their edges so that they may be lifted off. The covers should be washed in hot water and then stacked one on top of the other with heavy weight on them to press them flat. Lift the jars out of the battery box and note whether any of them have been leaking. A cracked jar should of course be replaced. Treat one cell at a time, by pulling the element out of the jar with the aid of the pliers, meanwhile holding the jar with the feet. Lay the element on the bench and





spread the plates slightly to permit removing the separators, taking care not to injure the rubber sheets, Fig. 392. Separate the positive group from the negative. If the active material of the negative be swollen beyond the surface of the grid, press it back into position before it has a chance to dry, placing boards of suitable thickness between the plates and carefully squeezing the group between heavy boards in a vise or press, as shown in Fig. 393. Boards of sufficient size and thickness must be used between the plates or breakage will result. Charged negative plates will become hot in a short time when exposed to the air and, in this event, should be allowed to cool before reassembling. Remove any loose particles adhering

to the positive plates by passing a smooth wood paddle over the surface but do not wash the positive plates.

Treating the Plates. If the positive plates show signs of buckling or stripping of the active matter, or if the negative plates have the light spotted appearance indicative of sulphating, it may be necessary to replace them altogether. In case sulphating appears to be the only trouble, the groups should be reassembled in an open jar with distilled water and given a long, slow charge, testing with the hydrometer at frequent intervals to note whether the specific gravity is

rising or not. Twenty-four hours or more may be necessary for this charge, and two or three days will be nothing unusual. This charging, of course, is carried on from the lighting mains through a rectifier or a motor-generator, unless direct-current service is available. If it is necessary to prolong the charge over two or three days, and the specific gravity still continues to rise slowly, it may be preferable to replace the plates.

Reassembling Battery. Wash



The separators should be practically flush with the bottoms of the plates to bring their tops against the hold-down below the strap and must extend to or beyond the side edge of the plates. Grit the element near the bottom to prevent the plates flaring out while placing the element in the jar. Fill the cell to within one-half incl of the top of the jar, using electrolyte of 1.250 specific gravity. I the negative plates show signs of sulphating, but not enough to cal for the special treatment mentioned above, use water instead of the electrolyte. After all of the cells have been given the same treatmen and reassembled, return them to the battery box in their prope positions, so that the positive of each cell will be connected to the negative of the adjoining cell and connect temporarily by pressing the old connecting straps in place by hand.

Checking the Connections. Put the battery on charge at it finishing rate (usually about 5 amperes) and, after charging abou fifteen minutes, note the voltage of each cell. This is to insurhaving reconnected the cells properly with regard to their polarity If this be the case, they should all read approximately 2 volts. Any cell that reads less is likely to have been connected backward. When the cells begin to gas freely and uniformly, take a hydrometer reading of each cell and a temperature reading of one of them. Reduce the current to one-half the finishing rate. Should the temperature o the electrolyte reach 100° F., reduce the charge, or interrupt i temporarily, to prevent the cells getting any hotter. Both hydrometer and temperature readings must be taken at regular intervals, say four to six hours apart, to determine if the specific gravity is stil rising or if it has reached its maximum. Continue the charge and the readings until there has been no further rise for a period of a least twelve hours. Maintain the height of the electrolyte constant by adding water after each reading. (If water were added before the reading, it would not have time to mix with the electrolyte and the reading would not be correct.)

Should the specific gravity rise to about 1.300 in any cell, draw off the electrolyte down to the level of the tops of the plates and refill with as much water as possible without overflowing. Continue the charge, and if the specific gravity again exceeds 1.300, dump out all the electrolyte in that cell, replace it with water, and continue the charge. The charge can be considered complete only when

there has been no rise in the gravity of any of the cells during a period of at least twelve hours of continuous charging. Upon completion

of the charge, the electrolyte should have its specific gravity adjusted to its proper value (1.270 to 1.280) using water or 1.300 acid, as may be necessary, and the level of the electrolyte adjusted to a uniform ½ inch above the plates.

Discharge the battery at its normal discharge rate to determine if there are any low cells caused by defective assembly. The normal discharge rate of the battery is usually given on its name plate. To discharge the battery, the current may be passed through a rheostat, as in Fig. 395, or if no panel board of this type be available, through a water resistance, as shown in Fig. 396.


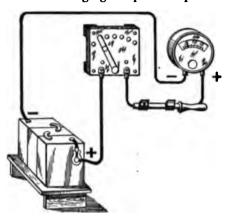


Fig. 395. Wiring Diagram for Discharging Battery through Rhecetat

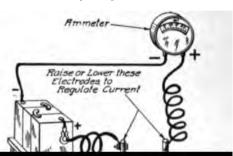


by the voltmeter test (they should all register two volts or slightly over at the beginning of the discharge and should fall off slowly) such cells should be remedied at once. Recharge the battery and ther remove the temporary connectors, wipe the inside edges of the jar dry, and put the rubber covers in place. Heat the sealing compound which is supplied for this purpose and apply around the edges of the covers, smoothing it down with a hot putty knife. Care must be taken not to burn the sealing compound when heating it.

Reconnecting Cells. If the old lead connecting straps have bee removed carefully, they may be used again, though in many case it will be found preferable to employ new straps. Before puttin the straps in place, scrape the posts clean with a knife and clea out the eyes of the straps themselves. When the connectors hav been put in place, tap them down firmly to insure good contact Before reburning the connectors in place, test each cell with a low reading voltmeter to make certain that the cells have been connecte in the right direction, i.e., that their polarity has not been reversed It is not sufficient to note that the voltage of each cell is correct i.e., 2 volts per cell or over, but care must be taken also to note tha it is in the right direction. With a voltmeter having a needle tha moves in both directions from zero, one polarity will be evidence by the needle moving over the scale to the right of the neutral line while if the polarity be reversed, the needle will move to the left One cell having the proper polarity should accordingly be tested and then, to be correct, the remaining cells should cause the needl to move in the same direction and to approximate the same voltage when the instrument leads are held to the same terminals in th same way for each. Where the voltmeter needle can move in bu one direction, i.e., to the right, a change of polarity will be indicated by the needle of the instrument attempting to move to the lef and, in so doing, butting up against the stop provided to preven this. Complete the reassembly of the cells by burning the connector together, as detailed under the head of Lead Burning.

Renewals. In many cases it will be found necessary upon overhauling a battery to renew the elements. These may be purchase either as loose plates or as groups ready to assemble in the battery Except in garages doing a large amount of this work, it will no be advisable to buy the loose plates and burn them into groups

The new groups should be assembled with rubber sheets and wood separators, as directed in overhauling the battery, the jars filled with fresh electrolyte of the proper specific gravity and the battery given a test charge and discharge with temporary connections. The electrolyte should be of 1.250 specific gravity, or seven parts of water to two of pure sulphuric acid by volume. If the test charge has been carried to a point where the specific gravity has ceased to rise for several hours, and the discharge shows no defectively assembled cells, the cells may be permanently connected.

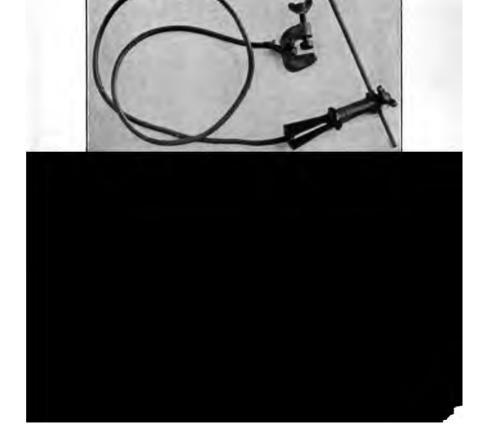Lead Burning. Type of Outfit. In the manufacture of storage batteries, and in garages where a large number of batteries are



connected by a flexible cable. This simple outfit can be employed in two ways, the second being preferable for the beginner, at leas until sufficient amount of skill has been acquired to use the ar without danger of melting the straps.

First Method of Burning. In the first method, a potential c from 28 to 30 volts (12 to 15 cells) is required.\* The clamp should therefore, be fastened to the positive pole of the twelfth to th fifteenth cell away from the joint to be burned, counting toward th negative terminal of the battery. The carbon then forms the negative terminal of the circuit. Otherwise particles of carbon will be carrie into the joint, as the carbon rod quickly disintegrates when it form the positive pole. The carbon should project 3 or 4 inches from th holder. The surfaces of the parts to be burned should be scrape clean and bright, and small pieces of clean lead about 1 to 1 inc square provided for filling the joint. The carbon is then touched t the strap to be burned and immediately withdrawn, forming a electric arc which melts the lead very rapidly. By moving the carbo back and forth the arc is made to travel over the joint as desired, th small pieces of lead being dropped in to fill the gap as required Owing to the high temperature generated, the work must be carrie out very quickly, otherwise the whole strap is liable to melt and rur

As this method is difficult and requires practice to secure goo results, the beginner should try his hand on some scrap pieces clead before attempting to operate on a cell. Its advantages ar that when properly carried out it takes but a short time to do th work, and the result is a neat and workmanlike joint. It is extremel hard on the eyes and smoked or colored glasses must be used.

Second Method of Burning. The second method, utilizing the hot point of the carbon rod instead of the arc, is recommended for general practice. Scrape the parts to be joined and connect the clamp between the third and fourth cells from the joint. With this method it is not necessary to determine the polarity of the carbon. The latter is simply touched to the joint and held there; on account of the heavy flow of current it rapidly becomes red and then white hot. By moving it around and always keeping it in contact with the metal, the joint can be puddled. To supply lead to fill the joint

<sup>\*</sup>This voltage may be obtained from an electric vehicle battery in the garage or from th lighting mains through a suitable resistance, first converting to direct current where the suppl is alternating.

an ordinary lead-burning strip can be used, simply introducing the end into the puddle of molten lead, touching the hot carbon. The carbon projecting out of the holder should be only one inch, or even less, in length. After the joint has been made, it can be smoothed off by running the carbon over it a second time.

Use of Forms to Cover Joint. In joining a strap which has been cut in the center, it is best to make a form around the strap by means of a piece of asbestos sheeting soaked in water and fastened around the strap in the shape of a cup, which will prevent the lead from running down. It will be found that sheet asbestos paper is thick enough, but it should be fairly wet when applied. By this means a neat joint can be easily made. The asbestos will adhere very tightly to the metal owing to the heat, but can be removed by wetting it again. When burning a pillar post to a strap, a form may be made around the end of the strap in the same manner, though this is not necessary if reasonable care is used. Two or three pieces of the inch strap iron about one inch wide, and some iron nuts about one inch square are also of service in making the joint, the strap iron to be used under the joints, and the nuts at the side or ends to confine the molten lead. Clay can also be used in place of asbestos, wetting it to a stiff paste. As the holder is liable to become so hot from constant use as to damage the insulation, besides making it uncomfortable to hold, a pail of water should be handy, and the carbon dipped into it from time to time. This will not affect its operation in any way, as the carbon becomes hot again immediately the current passes through it.

Illuminating Gas Outfit. Heretofore it has not been possible to do good work in lead burning with illuminating gas, but a special type of burner has recently been perfected by the Electric Storage Battery Company, which permits the use of illuminating gas with satisfactory results. The outfit consists of a special burning tip and mixing valve. Sufficient 15-inch rubber hose should be provided, and the rubber should be wired firmly to the corrugated connections, Fig. 398, as the air is used at a comparatively high pressure. A supply of compressed air is necessary, the proper pressure ranging from 5 to 10 pounds, depending upon the length of hose and the size of the parts to be burned. When air from a compressor used for pumping tires is utilized for this purpose, a suitable reducing valve must be introduced.

in the supply line. This outfit is designed for use with ordinar; illuminating gas and cannot be employed with natural gas.

Connect the air hose to the right-hand cock and the gas hose to the left-hand cock. The leader hose, about five or six feet long, is connected to the lower pipe and to the upper end of the burning tip. When the air pressure at the source is properly adjusted, close the air cock and turn the gas cock on full. Light the gas at the tip and turn on the air. If the flame blows out, reduce the air pressure preferably at the source. With the gas turned on full, the flame

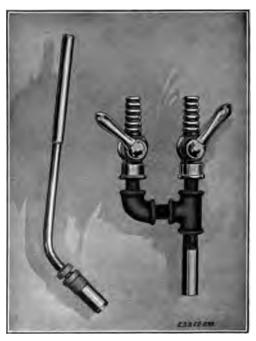


Fig. 398. Lead-Burning Outfit for Use with Illuminating Gas Courtesy of Electric Storage Battery Company, Philadelphia, Pennsylvania

will have a ragged appearance and show a waist about  $\frac{1}{2}$  inch from the end of the tip, the flame converging there and spreading our beyond. Such a flame is not good for lead burning.

Slowly turn the gas off until the outer portion at the waist breaks and spreads with an inner tongue of flame issuing through the outer ring. The flame will now have a greenish color and is properly adjusted for burning. If the gas is turned off further or if too much


air is turned on, the flame assumes a blue color gradually becoming invisible and is then deficient in heating power. When properly adjusted, the hottest part of the flame is just past the end of the inner point. Do not hold the flame too close to the work when burning, as its heating effect is greatly reduced and the flame is spread so as to make control difficult. The burning tip has at its lower end an outer sleeve and lock nut; this sleeve can be taken off in case any of the holes in the tip become clogged. The position of this sleeve is adjustable, the best position varying with the pressure of the flame, and it should be determined by experiment.

Hydrogen Gas Outfit. Hydrogen gas gives a hotter flame and therefore permits of more rapid work, so that where burning is done on a large scale, it is still preferred. The essentials of such an outfit are: first, a hydrogen generator; second, a method of producing air pressure at approximately 2 pounds to the square inch; and third, the usual pipe and tips for burning. If hydrogen gas is purchased in a tank and compressed air is available, only the blowpipe, tips, and a reducing valve on the air line are necessary. This is an expensive method to purchase hydrogen, however, so that it is usually generated, and a water bottle is needed between the generator and the blowpipe to wash the gas and to prevent the flame from traveling back to the generator.

For this purpose hydrogen gas is generated by placing zinc in a sulphuric-acid solution. The generator usually employed for vehicle-battery burning requires 50 pounds of zinc, 2 gallons of sulphuric

pour in the acid, taking care to avoid splashing. Always pour the water in first.


In running the hose from K to N, arrange it so that there we be no low points for the water of condensation to collect in; in oth words, this hose should drain back at every point to the water bottle If, however, water should collect in the hose to such an extent as interfere with the flame and it cannot readily be drained off, kink those between T and U and detach it from K; close the stop cock W and pump until a strong pressure is obtained in the tank; then clo

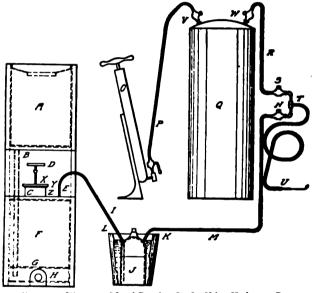



Tig. 399. Diagram of Lead-Burning Outfit, Using Hydrogen Gas


the cock at V, opening those at S and N and, finally, quickly open W the pressure in the air tank will then force the water out of the hose. The length of the hose from T to U should be such that the mixin cocks at S and N are always within easy reach of the man handlin the flame.

In preparing the flame for burning, close the air cock at S an open N wide, hold a match to the gas until it lights, then add ai and adjust the gas cock slowly, turning toward the closed positio until the flame, when tried on a piece of lead, melts the metal an leaves a clean surface. The tip to be used depends on the work, bu most vehicle-battery work is done with the medium tip. Replenis

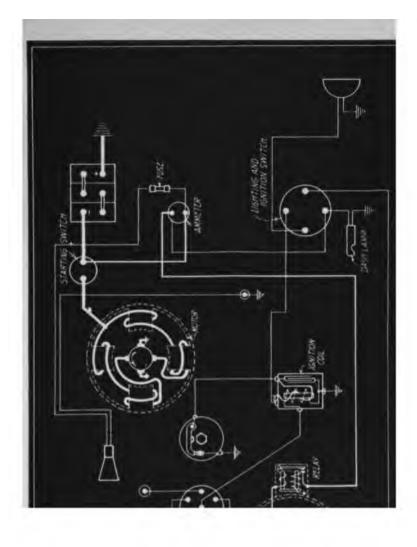

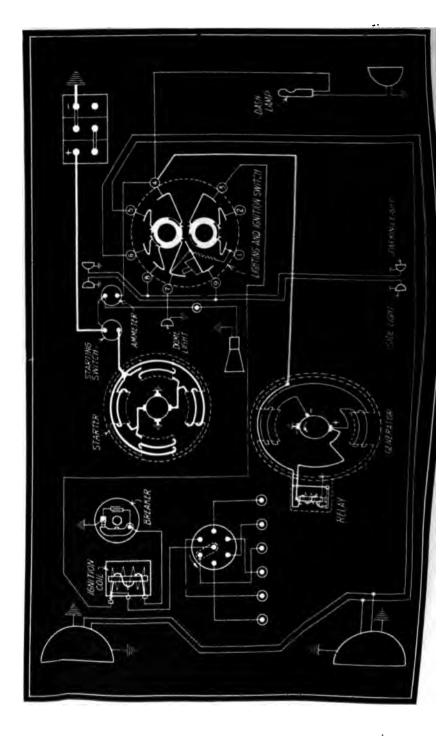


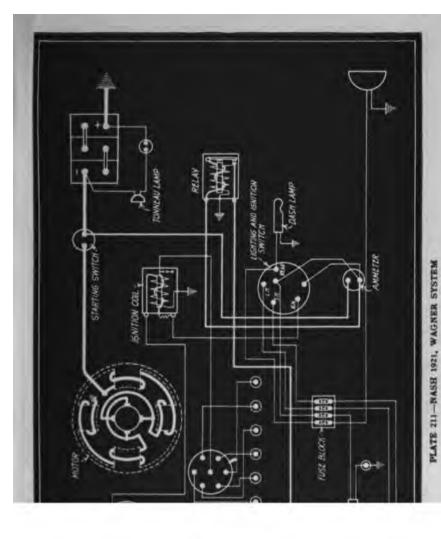


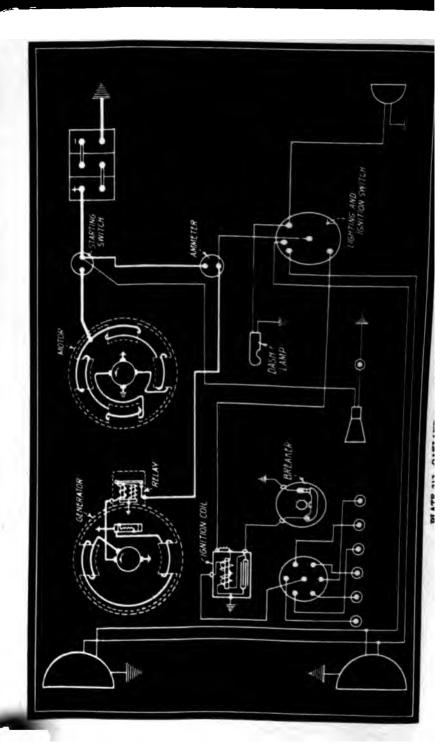







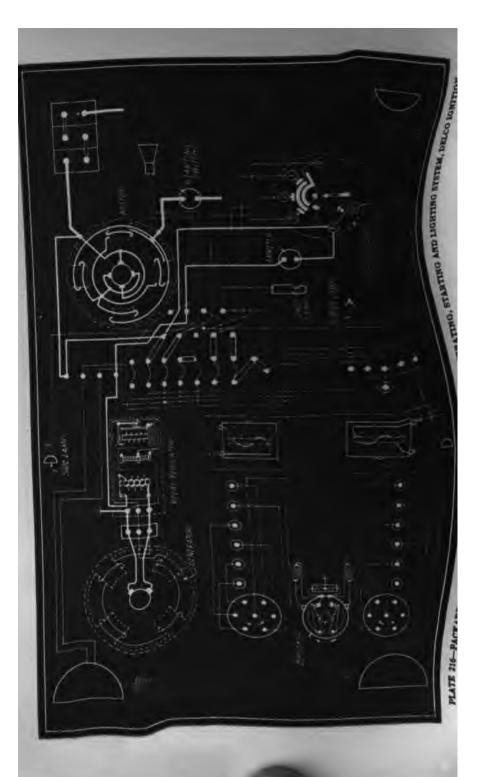


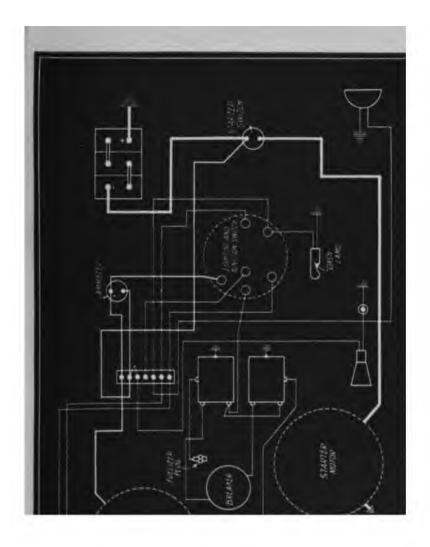


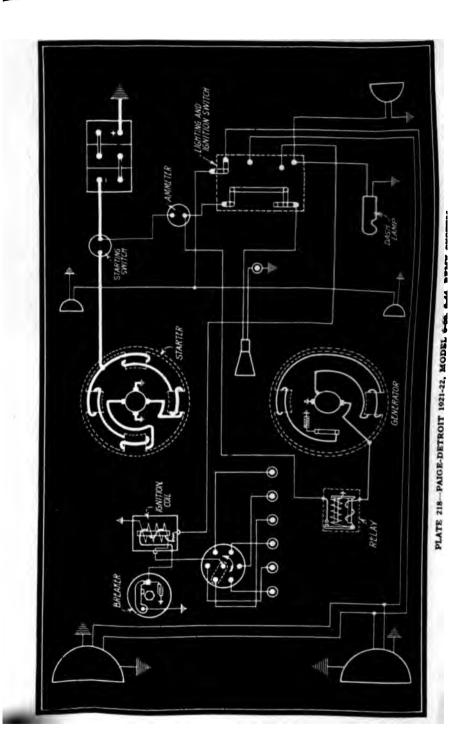


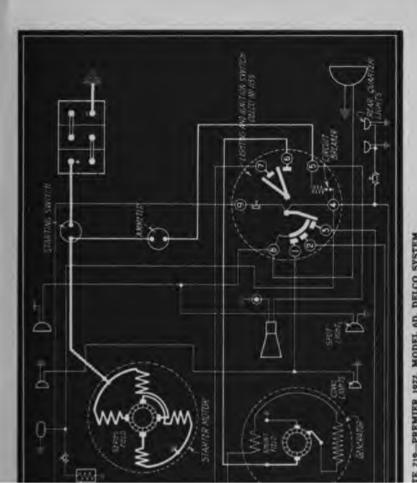


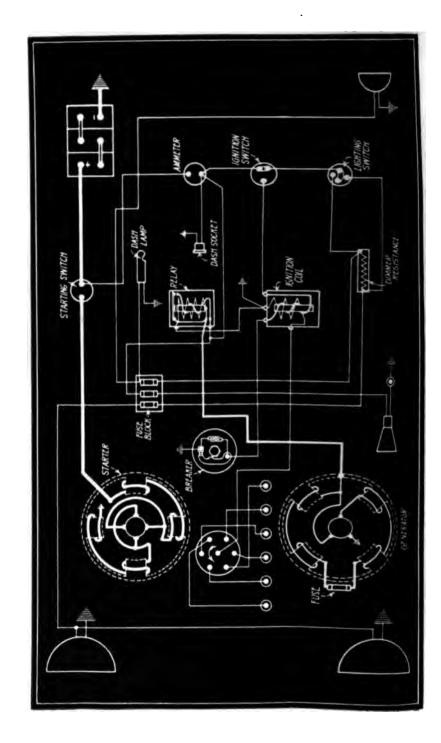
TE 219-PREMIER 1922, MODEL 6D, DELCO SYSTEM



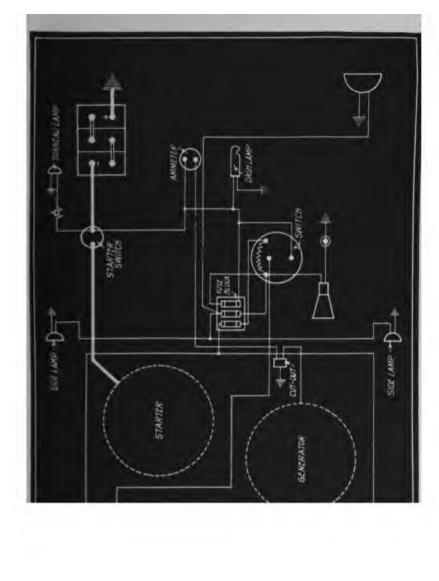

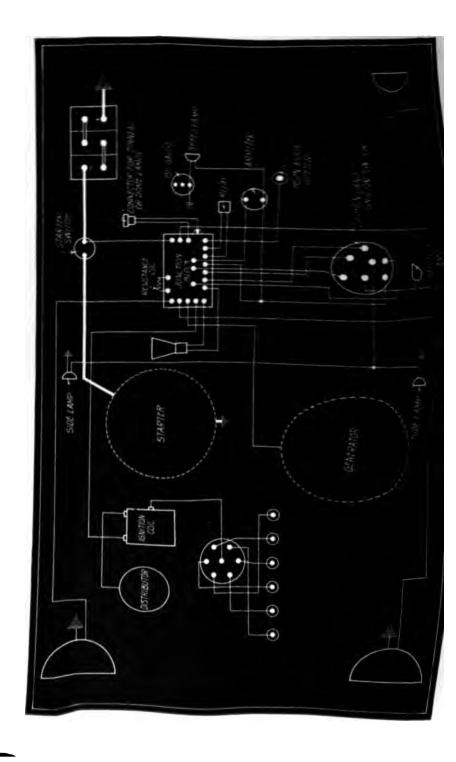

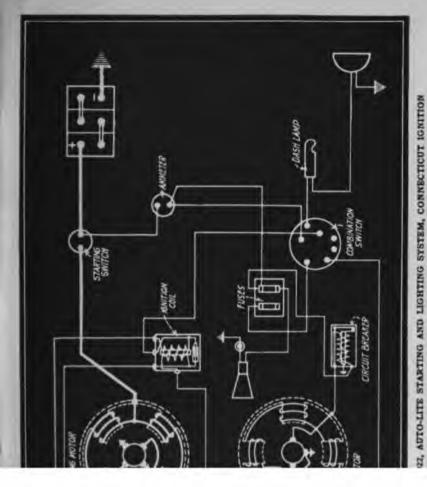

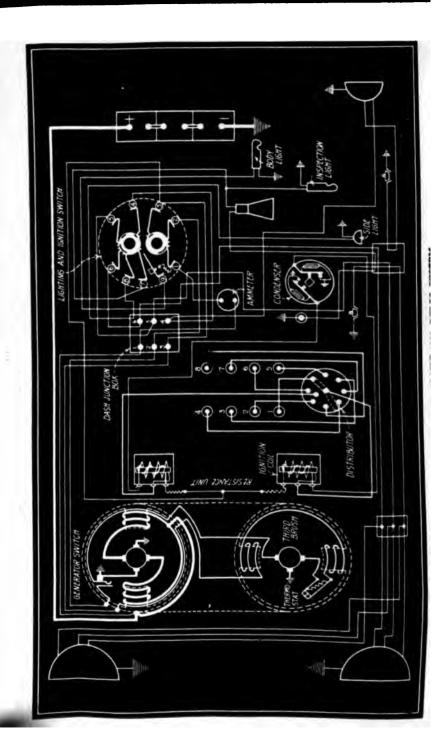

the sinc every few days, keeping it up to the required amount. When a charge is exhausted or the generator is to be laid up for the night, the old solution should be drawn off before making up a new charge and the generator thoroughly flushed out by running water through A. The new charge should not be put in until the generator is to be used again. To empty the generator, first pull off the hose at the nipple K, then at E, and finally the rubber plug at H. Care shou'd be taken not to allow the solution to splash on anything and not to dump the generator where the contents will damage cement, asphalt, or wood walks.

Installing New Battery. In not a few instances, it will be necessary to renew the entire battery. As received from the manufacturer, the battery is in a charged condition, i.e., it was fully charged just previous to being shipped, but it must be inspected and tested before being installed on the car. Care must be taken in unpacking it to avoid spilling any of the electrolyte. After cleaning off the packing from the tops of the cells, take out the rubber plugs and see that the electrolyte is \( \frac{1}{2} \) inch over the plates. If it is uniformly or approximately below the proper level in all the cells, this is simply the loss due to evaporation. But if low in only one or two cells, this is evidently caused by loss of electrolyte. In case this loss has resulted from the case being turned over in shipment, it will be indicated by the presence of acid on the packing on top of the battery (the acid does not evaporate), and some of the electrolyte will have

been lost from all the cells. Replace the amount lost by refilling the

represented by its electrolyte; that pouring off the electrolyte takes the charge with it; that, in case it is desired to store a battery, all that is necessary is to pour off the electrolyte and store the empty battery and the solution separately; and when it is desired to put the battery back in commission, it is then only necessary to pour the electrolyte back into the cells and, prestol they are ready to start the engine right away. Unfortunately for this theory, the charge is in the active material of the plates and not in the electrolyte.

It is frequently necessary to allow the battery to remain idle for a considerable length of time, in which case it should be put out of commission. If the battery itself is in good condition at the time and if it may be wanted for service again at short notice, this need only consist of giving it a long equalizing charge until the specific gravity has ceased to rise for several hours, then filling the cells to the top with distilled water and putting the battery away in a handy place. It should be given a freshening charge every two weeks or, at least, as often as once a month. If it is actually to be stored, there are two ways of doing this.

One is known as the wet storage method, and the other as the dry, the one to be adopted depending upon the condition of the battery and the length of time it is to be out of commission. The wet storage method is usually applied to any battery that is to be out of commission less than a year, provided that it will not soon require repairs necessitating dismantling it. The dry storage method is used for any battery that is to be out of commission for more than a year, regardless of its condition, and it is also applied to any battery that will shortly require repairs necessitating its dismantling. It will be apparent that this last-named class includes most starter batteries after they have seen several months of service, so that the majority can be placed in dry storage when necessary to put them out of commission.

Examine the condition of the plates and the separators and also the amount of sediment in the bottom of the jars. If it is found that there is very little sediment and the plates and separators are in sufficiently good condition to give considerable additional service, the battery may be put into wet storage by giving it an equalizing charge and covering it to exclude dust. Replace evaporation periodically to maintain the level of the electrolyte ½ inch above the

tops of the plates. At least once every four months, charge the battery at one-half its normal finishing rate (see name plate on battery box) until all the cells have gassed continuously for at least three hours. Any cells not gassing should be examined, and the trouble remedied.

When examination shows that the battery will soon require dismantling, it should be put into dry storage. Dismantle the cells in accordance with the instructions already given. If the positive plates show much wear, they should be scrapped; if not, remove any loose particles adhering to them by passing a smooth wood paddle over the surface, but do not wash the positive plates. Charged negative plates will become hot in a short time when exposed to the air. They should be allowed to stand in the air until cooled.

Empty all the electrolyte out of the jars into a glass or glazed earthenware jar or a lead-lined tank and save it for giving the negative plates their final treatment before storage. Wash all the sediment out of the jars and wash the rubber separators carefully, then dry them and tie them in bundles. Place the positive groups together in pairs, put them in the jars, and store them away. Then put the negative groups together in the same way, place them in the remaining jars, and cover them with the electrolyte saved for the purpose, allowing them to stand in it for five hours, at least. Then pour off the electrolyte, which may now be discarded, and store away the jars containing the negatives. If the negative plates show any

except the lowest starting speeds and should accordingly always be fully charged. The generator is designed to take care of the storage battery and usually has sufficient capacity to light all the Practice, however, does not bear out thi lamps in addition. theoretical view of the favorable conditions under which the starte battery is supposed to operate. It will be apparent at the veroutset that the method of charging and discharging is not beneficial To insure long life to a storage battery, it should be fully charged and then discharged to at least seventy-five per cent of its maximum capacity before recharging. It should never be allowed to stand discharged for any length of time. If exhausted, it should b recharged immediately. It should not be charged to half its capacit and then discharged. It should not be overcharged to the poin where it continues to gas violently nor where its temperature exceed 100° F.

All of these are things that should not be done to the storag battery, but it will take only a little experience to enable the garag man to recognize that all these are things which are constantly bein done to the majority of storage batteries on gasoline automobiles. Most batteries receive treatment that reaches one extreme or the other, though it will be apparent that the middle course is almost as injurious to the battery. Either a battery is constantly kep undercharged so that it has insufficient charge to spin the engin more than once, and its operation is accordingly unsatisfactory, of it is constantly kept overcharged with the result that the hot acid makes comparatively short work of the plates, and they must be renewed in considerably less than a year of service. The mean cours between these two is found in the case of the battery that is only charged to about half its capacity before being discharged again by the use of the starting motor. This treatment results in sulphating

To keep the storage battery of the starting system in anythin like efficient operating condition, it cannot be left on the running board with nothing but the generator of the starting and lighting system to charge it. Hydrometer and voltage tests will be valueles unless the conditions they indicate are remedied, and this cannot be done with the car generator as the sole source of charging current Here is a typical instance: The battery is in good condition and it is fully charged. On a cold morning, it is drawn on intermittently

for almost fifteen minutes by the starting motor before the engine fires. As a result, it is practically discharged. The car is driven only a few miles, stopped and after a rest started again. What charge the battery received by the short run is again lost. The car is run for a little longer time and returned to the garage. The battery has received about one-fourth its normal charge. It stands this way for several days.

The weather being warmer, the engine starts in a much shorter time, but not before the starting motor has exhausted the small amount of charge in the battery. It is not run enough that day to charge the battery nor when taken out again that night, as all the lights are switched on, and under such conditions the battery receives very little current. Multiply this treatment by five or ten representing the number of days the car is driven during the month. At the end of that time, the battery no longer has sufficient charge to operate the starting motor at all and is condemned, as usual, by the car owner as being worthless. This is only one instance of many that are so similar that a few changes in detail would cover them all. No battery ever made could possibly operate efficiently under such conditions. After the car in question had been used a few days, a hydrometer test of the battery would have indicated its need of charging.

Equalizing Charges Necessary. Even where a battery receives almost 100 per cent of its normal charge before being discharged again,



to give it an equalizing charge once a month. The constantly overcharged condition is quite as injurious as its opposite, and it can be cured only by cutting down the output of the generator or increasing the demand upon the battery for current.

Methods of Charging. The apparatus employed for charging starter batteries will naturally vary in accordance with the number that are looked after in the garage. It may range from the makeshift consisting of a bank of lamps up to an elaborate panel board designed to provide charging connections for a dozen or more batteries at once. Where direct current is available—and only a few starter batteries need this attention—a bank of lamps in connection with a fused double-pole switch will be found to fill all the requirements. Note the charging rate (finishing) given on the name plate of the battery and make the number of lamps in accordance. A 32 c.p. in the circuit is practically the equivalent of one ampere of current entering the battery, i.e., it requires one ampere to light a lamp of this size and type (carbon filament) to incandescence. A number of standard lamp sockets should be mounted on a board, connected in multiple. and the group connected in series with the switch and the battery. (See illustration in résumé of questions and answers on the battery.) As many lamps as necessary may then be screwed into the sockets. The more current needed, the more lamps and the higher power lamps will be necessary. Tungsten lamps may be employed as well as the carbon-filament type, but as they take so much less current. lamps of higher candle power will be needed. For example, to replace a 32-c.p. carbon-filament lamp, a 100-watt tungsten lamp will be required.

Charging in Series for Economy. Where several starter batteries are to be charged at the same time, it will be found more economical to connect them in series and charge them all at once. The difference between the 110-volt potential of the lighting mains and the 6 to 8 volts needed to charge a single three-cell battery represents that much waste, as the drop in voltage has to be dissipated, through a resistance, to no purpose. In this way, any number of 6-volt storage batteries, up to twelve, can be charged from a 110-volt circuit (direct-current) with the same expenditure of current as would be required for a single battery. This is owing to the fact that, in any storage battery, the capacity of the battery is the capacity of one cell,

where all are connected in series. Consequently, it will take 10 to 15 amperes to charge one 6-volt battery from the lighting circuit, and when several more units of the same size are connected in series with it, the current consumption will still be the same, but a smaller part of the voltage will have to be wasted through a resistance.

Motor-Generator. Direct current will be found available in comparatively few places to-day, so that some means of rectifying an alternating current, in order to use it for charging batteries, will be necessary. Where quite a number of batteries are to be cared for, the motor-generator will be found to give the highest efficiency, besides proving more economical in other ways. As its name indicates, it consists of a motor wound for alternating current and fed from the supply mains of the garage, and a direct-current generator which is driven at its normal generating speed by the a.c. motor. There is no electrical connection between the two units. Electrical power in the form of an alternating current is converted into mechanical power in the a.c. motor which drives the armature of the d.c. generator and again converts it into electrical power in the form of a direct current. The first cost of a motor-generator is such that its use is usually confined to large establishments handling quite a number of batteries, though motor generators are now made in much smaller sizes than formerly.

A.C. Rectifiers. Where the amount of charging to be done does not warrant the investment in a motor-generator, a rectifier



one. This is a bulb exhausted of air and filled with a special gas in which a heavy tungsten-wire filament is brought to incandescence by the passage of the alternating current. This filament is very short and thick, its diameter depending upon the capacity of the



Fig. 400. Front View of Large Size G. E. Tungar Rectifier

rectifier, and it is placed horizontally. It constitutes the cathode of the couple. Directly opposite it, but a short distance away, is the anode of graphite in the form of a button, the lower face of which is presented to the tungsten wire. It is made in three sizes, the smallest of which has a capacity of but 2 amperes and is designed for charging the batteries of small portable lamps, such as are used by miners; and for charging ignition, call bell, burglar alarm batteries, and the like.

In the larger size, as shown in Fig. 400, the bulb is mounted in an iron case,

on the face of which are mounted the switch for alternating current; an ammeter on the d.c. side, showing the charge received by the battery; and a dial switch for adjusting the voltage to the number of batteries to be charged. There is a compensator with 15 taps, and the current is adjustable by steps up to 6 amperes. Anything from a single three-cell battery up to ten of such units



Fig. 401. Interior View of Small Size G. E. Tungar Rectifier Courtesy of General Electric Company, Schenectady, New York

(30 cells in all) may be charged at once. The batteries must be connected in series and then it is only necessary to turn the switch of the a.c. circuit. In case the alternating-current supply should fail the battery cannot discharge through the rectifier, and the latter

will assume its task again automatically as soon as the current comes on. This is the 6-ampere 75-volt size. It is also made in a 6-ampere 15-volt size designed for the charging of a three- or six-cell starter battery in the home garage. Fig. 401 shows an interior view of this

size, illustrating the position of the converting bulb, the compensator, the reactance coil, and the fuses, while Fig. 402 illustrates the 6-ampere 75-volt size, showing the panel instrument, i.e., switch, ammeter, and regulating handle, as well as the bulb and fuses. A closer view of the bulb itself is shown in Fig. 403.

Care of Battery in Winter. There is a more or less general impression that special treatment must be given the storage battery



Fig. 402. Interior View of Large Size G.E. Tungar Rectifier

during cold weather. This is probably owing to the fact that lack of attention makes itself apparent much more readily in winter than in summer because of the lower efficiency of the battery resulting from the lower temperature. The care necessary in winter does not

vary in any respect from



Make the usual hydrometer and voltage tests, as described under the headings in question, and see that the battery is constantly kept more fully charged than would be necessary to render satisfactory service in warmer weather. This is important for two reasons: first, because of the greatly increased drain on the battery owing to the difficulty of starting the engine when cold; and second, because of the liability of the electrolyte to freeze if the battery is allowed to stand discharged in very cold weather. There is not the same excess supply of current available for charging the battery in winter as there is in summer, as the lights are in use during a much greater part of the time and not so much driving is likely to be done during the day. As the lamp load consumes almost the entire output of the generator in the average starting and lighting system, there is very little left for the battery when all the lamps are in use. The practice of turning on all the lights on the car-headlights, side lights spot light, and instrument lights—whether they are necessary or not, should be discouraged in winter, as it is likely to result in exhausting the battery. The instrument lights are usually in series with the tail light, and so cannot be dispensed with, but it is never necessary to have the headlights and side lights going at the same time, and this also applies to the spot light, which consumes almost as much current as one of the headlights and should be restricted to the use for which it is intended, i.e., reading signs by the roadside.

Unless the lamp load is reduced, it may be necessary to increase the charging rate of the generator during the cold months, and this is not beneficial to the battery, as it may cause severe gassing and injury to the plates when continued too long. In case the car is not driven enough to keep the battery properly charged, it may be necessary to charge it from an outside source or, if the latter be not available, to run the engine with the car idle just for this purpose. Care must be taken to prevent any danger of freezing, and the best method of doing this is to keep the battery fully charged, as when in this condition it will freeze only at very low temperatures. The more nearly discharged a battery is, the higher the temperature at which it will freeze, and freezing will ruin the cells, regardless of whether it happens to crack the jars or not.

Why Starting Is Harder in Cold Weather. The electric starting and lighting system, or rather the storage battery, which is its main-

stay, is much more severely taxed in winter than in summer for the following four reasons:

- (1) The efficiency of the storage battery decreases with a decrease in temperature, because the action of the storage battery is chemical, and chemical action is dependent upon heat and, therefore, always decreases as the temperature decreases.
- (2) The lower the temperature the stiffer the lubricating oil, which gums the moving parts together, adding a very considerable load to the ordinary amount of inertia which the starting motor must overcome and likewise adding to the difficulty of turning the engine past compression.
- (3) Gasoline will not vaporize readily at a low temperature, so that it is necessary to turn the engine over a great many revolutions before the cylinders become sufficiently warmed from the friction and the repeated compression to create an explosive mixture. The better the mixture the more readily it will fire, and consequently a greater heat value is required in the spark to ignite it where the mixture is poor or only partly vaporized. Anything that reduces the efficiency of the storage battery likewise reduces the heat value of the ignition spark.
- (4) Low heat value of the spark often makes it difficult to start an engine when cold. This lack of heat in the spark is caused by a partially discharged battery as well as the lower efficiency of the battery caused by the cold weather; also by the necessity for

reported ansestion of the starting motor, whomeha the voltage of the

of the starting and lighting system are designed to give satisfactory service in cold weather, but as a very low temperature brings about conditions representing the maximum for which the system is designed, more skillful handling is necessary in winter than in summer to obtain equally good results.

To Test Rate of Discharge. If the battery terminals are removable, take off either the positive or the negative terminal, and connect the shunt of the ammeter to the terminal post and to the cable which has been removed, binding or wiring it tightly in place to insure good contact. Where the battery terminals are not easily removable, insert the shunt in the first joint in the line,

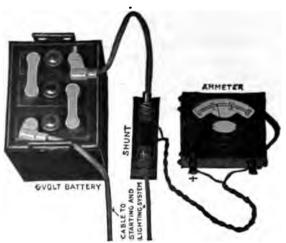


Fig. 404. Setup for Testing Rate of Discharge of Small Storage Battery

Courtesy of Prest-O-Lite Company, Indianapolis, Indiana

as shown in the illustration, Fig. 404. Then connect the ammeter terminals to the shunt. In case the instrument shows a reverse reading, reverse the connections to the shunt. When the ammeter is connected to test for discharge, the starter must never be used unless the 300-ampere shunt is in circuit, as otherwise the instrument is likely to be damaged. If a shunt of smaller capacity or a self-contained ammeter, i.e., one designed to be connected directly in the line is employed, and it is necessary to start the engine, either crank by hand or disconnect the ammeter before using the starting motor.

When the ammeter is connected to show the discharge and no lights are on, the engine being idle, no current is being used for any purpose, and the pointer of the ammeter should remain at zero. If any flow of current (discharge) is indicated, it shows that there is a ground or a short-circuit (a leak) somewhere in the system. In such a case, apply the usual tests described under the appropriate headings for locating grounds and short-circuits.

With the ammeter connected up as shown in the illustration, the discharge rate of the battery under the various loads it is called upon to carry may be checked up, and, if it proves to be excessive in any case, the trouble may be remedied. For example, with the 300-ampere shunt in the line, the amount of energy consumed by the starting motor may be checked. Without knowing how much current a certain make of starting motor should consume in turning over a given type of engine, it will naturally be impossible to make any intelligent comparisons with the result of the tests. This information, however, is readily obtainable from the manufacturer of the starting system, and it will be found advantageous to obtain details of this nature covering the various systems in general use in your locality, as it will enable you to make these tests valuable in correcting faults. While the starting loads imposed on the electric motor by different engines will vary greatly, the general nature of the load will be practically the same in all cases. When the starter switch is closed, there will be an excessive discharge rate from the will require more power to move it at first than if it had been running only a few minutes before. As a general rule, more power will always be needed in winter than in summer, unless the tests are carried out in a well-heated garage. The condition of the engine itself will also have an important bearing on the significance of the tests, as, if the engine has been overhauled recently, its main bearing may have been tightened up to a point where the engine as a whole is very stiff.

Note also whether the discharge rate falls off as quickly as i should when the engine begins to turn over rapidly. If it does not this also is an indication of tight bearings, gummed lubricating oil or similar causes, rendering the engine harder to turn over. It the case of a cold engine, stiffness due to the lubricating oil may be remedied by running it for ten or fifteen minutes, and a subsequent test should then agree with the manufacturer's rating. Where the discharge rate does not drop to a nominal amperage within a few seconds from the time of closing the switch, it is simply an indication that the essentials of the engine are not in the best of working order. The carburetor may not be working properly, or the ignition may be sluggish.

In case the discharge rate is very much less than that called fo by the manufacturer for that particular engine, it is an indication that the starting system itself is not in the best condition. connections, worn brushes, loose brush springs, a dirty switch, or some similar cause is greatly increasing the resistance in the starting circuit, thus cutting down materially the amount of current that the battery can force through it. In such circumstances, the discharge may not reach so high a rate as that called for by the manufacturer but to effect a start, even with the engine in normally good condition a high rate will have to be continued longer, to the correspondingly greater detriment of the battery. In other words, a great deal more current must be drawn from the battery each time the engine is started. Thus, testing the rate of discharge may be made to serve as an indication of the condition of both the starting system and the engine itself. Should it be necessary to make more than eight or ten starts to determine definitely the cause of any variation between the discharge rates shown and those that should be indicated, with everything in normally good condition, the battery should be fully

recharged before proceeding any further, as using it for this purpose when almost exhausted is very likely to damage it. Tests of this kind show also whether the efficiency of the battery has fallen off substantially or not, as indicated by its condition after making several starts in succession. When this has been done, the battery may be tested with the voltmeter and hydrometer to ascertain how far it has been discharged. The fact that after having been in service for some time a starting system will not start the engine so many times without exhausting the battery as it would when new may be due either to a loss of efficiency in the battery or to the poor condition of the other essentials of the system. In the majority of cases, however, it will be due to the condition of the battery.

By substituting the 30-ampere shunt for the 300-ampere, the load put on the battery by the lights when switched on in various combinations may be checked and compared with the manufacturer's ratings. Where the discharge rate for the lights is less than it should be, it may be due to the use of bulbs which have seen a great deal of service, the resistance of the filaments increasing with age, or other causes which place more resistance in the circuit, such as poor connections, loose or dirty switches, and the like. Tests may also be made of the ignition system where the battery is called upon to supply current to a distributor and coil by putting the 3-ampere shunt in the circuit. The amount of current required by the ignition system is very small when everything is in normal working order,

accordingly when noting the instrument on the road. In case it is very large, the dash ammeter itself should be adjusted, which can frequently be done merely by bending the pointer.

With the engine running fast enough to give the maximum charging rate, which is indicated by the fact that the ammeter needle stops rising, check the charging rate shown on the portable ammeter, bearing the following in mind: In the majority of cars the generator is regulated to charge the battery at from 10 to 15 amperes. Some are designed to charge at as low a rate as 7 amperes Unless the proper charging rate is definitely known, whatever maximum the portable ammeter shows may usually be assumed to be correct. Where the rate is less than 7 amperes it may generally be taken for granted, however, that the battery is undercharging and the various tests, described in detail under appropriate headings may be applied to locate the trouble either in the generator or in the automatic cut-out. This applies where the charging rate is too high as well as where it is too low.

The charging rates mentioned above naturally apply only to a 6-volt battery, or to a battery having a greater number of cells which is connected in series multiple so as to charge at 6 volts. In the case of a six-cell battery permanently connected in series so that it both charges and discharges at 12 volts, the above figures must be cut in half. Twelve-cell batteries are employed in some cases, but the total voltage of the battery is used only for starting the cells being divided into four groups in series multiple so that each group of three cells charges at 6 volts.

With the generator charging at 10 to 15 amperes, turn on al the lights. If more current is being drawn from the battery that is being supplied by the generator, this will be indicated by the ammeter showing a reverse reading or discharge. It signifies that there is a short-circuit in the lighting switch or the lamps, or in the wiring between the switch and the lamps, or that additional lights, other than those furnished originally with the system, have been added, or larger candle-power bulbs substituted, thus placing too great a demand on the battery.

If the system has been out of adjustment for any length o time, it is quite likely that the battery will shortly need repairs or replacement, because charging at an excessive rate causes the plate

to buckle and break through the separators, forming an internal short-circuit, while charging at too low a rate causes a constantly discharged condition of the battery, due to more current being normally called for than is put in. This results in injurious sulphating of the plates.

In case additional equipment has been added, the entire equipment should be turned on, and the total current required should be noted when making discharge-rate tests. Where the generator cannot supply sufficient current to permit the battery to take care of this extra equipment, the battery should be charged from an outside source at regular intervals. It is poor practice to increase

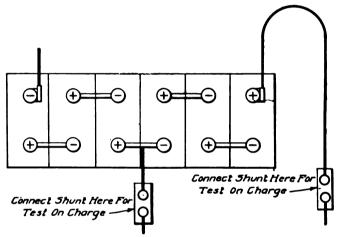


Fig. 405. Setup for Twelve-Volt Battery Wired to Charge and Discharge

Connections for Two-Voltage Batteries. Where the battery is of either three or six cells, all connected permanently in series, the foregoing suggestions for connecting the testing instruments apply. They must be varied, however, where tests are to be made of batteries connected in series multiple, which may be termed two-voltage batteries since they supply current at one voltage for lighting and at another for starting. In Fig. 405 is shown a battery of this type which is connected so as to charge and discharge through the starting motor at 12 volts, but which discharges at 6 volts to supply the lamps through a neutral lead in the center of the battery. The sketch indicates where to connect the ammeter shunt on charge at

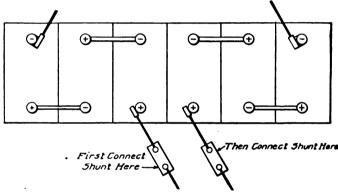


Fig. 406. Twelve-Volt Battery Connected Up to Make Two 6-Volt Batteries in Parallel

12 volts and on discharge at 6 volts. When testing the starting-motor discharge, it would be connected for 12 volts.

Test the 12-volt circuit with the engine running to get the charging rate; stop the engine, reverse the ammeter terminals and see whether there is any discharge indicating a short-circuit. Also test the discharge rate on the 6-volt circuit with the lights turned off and again with all lights on. These tests should show whether or not there is a short-circuit in the system. Before attempting to test the discharge rate of the starting motor, be certain that the 300-ampere shunt is in the circuit. A 12-volt battery will discharge only about half the current necessary to start the engine with a 6-volt battery, but no shunt smaller than the 300-ampere size can be depended upon to carry the load safely and protect the instrument.

Fig. 406 shows a 12-volt battery connected up in such a manner that it is practically two 6-volt batteries in parallel. The battery is charged at 6 volts, and both the lights and horn are supplied with current at this voltage, but the discharge through the starting motor is at 12 volts. Note the two positive cables leading to the center of the battery. To test the charging rate, the ammeter shunt should be connected first in one of these cables and then in the other, and the two readings added together to obtain the charging rate for the entire battery. The same locations for the shunt, and the same method of adding the readings also apply on discharge. Ammeter readings in the connections shown will indicate whether or not there are any short-circuits, except, of course, in the starting-motor cable.

Voltage Tests. An equally important instrument for the testing of the storage battery is the voltmeter. It is chiefly useful in showing whether a cell is short-circuited or otherwise in bad condition. Under some conditions, it indicates when the battery is practically discharged, but, like the hydrometer, it must not be relied upon alone. It should be used in conjunction with the hydrometer readings to insure accuracy. Since a variation as low as .1 (one-tenth) of a volt makes considerable difference in what the reading indicates as to the condition of the battery, it will be apparent that a cheap and inaccurate voltmeter is likely to be misleading rather than helpful. For garage use, a good reliable instrument with several

in contact with the positive terminal of the battery, and the negative terminal of the voltmeter with the negative terminal of the battery. If the markings of the cell terminals are indistinct, the proper terminals may be determined by connecting the voltmeter across any one cell. Should the pointer not give any voltage reading, butting up against the stop at the left instead, the connections are wrong and should be reversed; if the instrument shows a reading for one cell, the positive terminal of the voltmeter is in contact with the positive of the cell. This test can be made with a voltmeter without any risk of short-circuiting the cell, since the voltmeter is wound to a high resistance and will pass very little current. This is not the case with an ammeter,

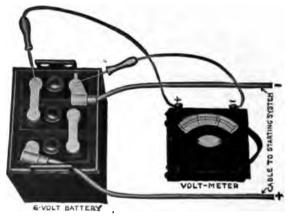


Fig. 407. Proper Setup for Testing Voltage of Batteries

however, as connecting such an instrument directly across the terminals of the battery will immediately burn out the ammeter.

Inasmuch as any cell, when idle, will show approximately 2 volts, regardless of whether it is fully charged or not, voltage readings taken when the battery is on open circuit, i.e., neither charging nor discharging, are practically valueless, except when a cell is out of order. Therefore, a load, such as switching on the lamps, should be put on the battery before making voltage tests. With the lights on, connect the voltmeter as explained above and test the individual cells, Fig. 407 (Prest-O-Lite). If the battery is in good condition, the voltage readings after the load has been on for about five minutes will be but slightly lower (about one-tenth of a volt) than if the battery were on open circuit. If any of the cells are completely discharged,

the voltage of these cells will drop rapidly when the load is first put on and, sometimes when a cell is out of order, even show reverse readings. Where the battery is nearly discharged, the voltage of each cell will be considerably lower than if the battery were on open circuit after the load has been on for five minutes. In the case of an electric-vehicle battery, the lights alone would not provide sufficient load for making an accurate test, so that one of the rear wheels may be jacked up and the brake set lightly until the ammeter on the dash of the car shows 50 to 70 per cent of the usual normal reading. To do this, start the motor on first speed with the brakes loose, and apply the brakes slowly until the desired load is shown by the ammeter reading. Never, under any circumstances, attempt to start with the brakes locked or on hard, as both the battery and the motor will be damaged. In the case of a starting-system battery, the lights alone are sufficient load, as they consume about 10 amperes.

To distinguish the difference between cells that are merely discharged and those that are out of order, put the battery on charge (crank the engine by hand in the case of a starter battery) and test again with the voltmeter. If the voltage does not rise to approximately 2 volts per cell within a short time, it is evidence of internal trouble which can be remedied only by dismantling the cell.

Temperature Variations in Voltage. It must be considered, in making voltage tests, that the voltage of a cold battery rises slightly above normal on discharge. The reverse is true of a really warm




directed, as they are the result of several years' experience in this work, and considerable care has been used in checking them. The sizes of the tanks given are merely indicative of what a very large repair shop would require and are comparative only. They will naturally vary with the amount of work to be done.

Cleaning Outfit. The cleaning outfit should consist of three sheet-steel tanks, Fig. 408, of suitable size (35 gallons for a large shop) mounted so that their contents may be kept heated to the desired temperature, three stone jars of approximately 15 gallons capacity, and a sawdust box. Two of the steel tanks should be equipped with overflow pipes so that they can be kept about two-thirds full at all times. These are tanks No. 1 and No. 2. They are used for clear hot water for rinsing parts after they have been cleaned. The third tank does not require a drain nor an overflow pipe and is used for the potash or caustic soda solution. This can be used for a long time without changing by simply adding a small amount of soda as the solution weakens. All three tanks are maintained at a temperature of 180° to 212° F., or approximately the boiling point.

The three jars mentioned are used for the acid solutions and are referred to as jars No. 1, No. 2, and No. 3. A wood tank large enough to hold the three jars and divided into two compartments, as shown in Fig. 408, should be provided. This is important, as the parts cannot be rinsed in the same cold water after being immersed in the different acid solutions. The solutions recommended are in tanks 1 and 2, clear hot water; tank 3, a solution consisting of one pound of caustic soda per gallon of water. Jar No. 1 is filled with a solution consisting of four gallons of nitric acid, one gallon of water, and six gallons of sulphuric acid. The water is placed in the jar first, the nitric acid is added slowly, and the sulphuric acid is poured in last. This order must be strictly followed, as it is dangerous to mix a solution of these acids in any other manner. In jar No. 2, the solution is one gallon of hydrochloric acid to three gallons of water, while jar No. 3 contains a solution of one-half pound of cyanide to a gallon Tank No. 2 should be used only for parts which have been in the potash solution and for no other purpose. Tank No. 1 is for general rinsing purposes.

Method of Cleaning Parts. Various metals are cleaned as follows: Steel is boiled in the potash solution until the dirt is removed, which should require only a few minutes. The steel part is then rinsed in tank No. 2 and dried in sawdust. Cast iron parts are boiled in the potash solution to remove dirt, rinsed in tank No. 2, dipped in the acid solution in jar No. 1, rinsed thoroughly in cold clear water, dipped in the cyanide solution, rinsed again in cold clear water, then rinsed in tank No. 1 and dried in sawdust. Copper can be cleaned in the same manner. Polished aluminum should first be thoroughly washed in gasoline, rinsed in tank No. 1, dipped in the acid solution in jar No. 1, rinsed thoroughly in cold clear water, rinsed in tank No. 1, and dried in sawdust. Plain aluminum, unpolished, should be dipped in the potash solution, rinsed in tank No. 2, dipped for a few seconds in the acid solution, rinsed in tank No. 2, dipped for a few seconds in the acid solution in Jar No. 1, rinsed in cold water, then rinsed in tank No. 1, and dried in sawdust.

It will be noticed that when aluminum is put into the potash solution the metal is attacked and eaten away rapidly, so that polished parts of this metal should not be put into this solution, and any aluminum parts should not be left in for a moment longer than necessary. Where the parts are covered with caked deposits of hard grease, they should first be washed in gasoline. Aluminum parts should never be put into the potash solution unless they can be put through the acid immediately after, as the acid dip neutralizes the effect of the potash solution. Parts should only be held in the

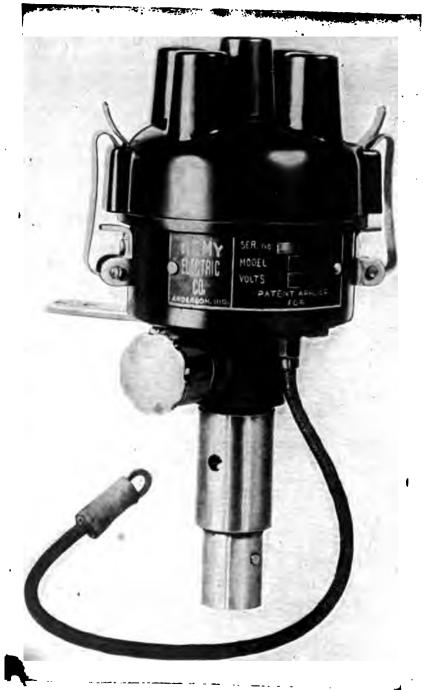

REMY IGNITION DISTRIBUTOR, MODEL 355-B Courtesy of Remy Electric Company, Anderson, Indiana

# ELECTRICAL EQUIPMENT FOR GASOLINE CARS

#### PART VIII

## ELECTRIC STARTING AND LIGHTING SYSTEMS—(Continued)

## SUMMARY OF INSTRUCTIONS ON ELECTRIC STARTING AND LIGHTING

It will be apparent from the foregoing description of the various systems that while the majority differ more or less in detail all are based on a comparatively small number of well-defined principles, and that once these are mastered their application in any system under consideration will be clear. To avoid unnecessary duplication in the instructions covering points that are common to all, general instructions have been given only in connection with one or two systems, and it will be understood that descriptions of the methods of locating short-circuits or grounds, of caring for brushes and commutator, and of testing with a portable lamp or with the volt-ammeter are equally applicable to all. The instructions given with other systems accordingly are limited to special references to the details of installation that will make it easier to locate faults in that particular system.

In order to bring the two together in such form that the par-



wound, cumulative compound-wound, and the like, that is, all lighting generators have a shunt and a series winding on their fields, but the relation of these windings to one another differs, depending upon the characteristics of the remainder of the system.

### Q. What is a differential compound-wound generator?

A. One in which the series winding is reversed, i.e., wound in a direction opposite to that of the shunt winding so that its exciting effect on the field magnets opposes that of the shunt winding. The series winding is then termed a bucking coil because it bucks, or opposes, the exciting effect of the shunt winding on the field magnets as the speed increases. The series winding in this case is used simply for regulating the generator output.

### Q. What is a cumulative compound-wound generator?

A. One in which the exciting effect of the series coil is added to that of the shunt coil, the series coil in this case having no connection with the regulation of the generator output.

- Q. As one of the chief requirements of an efficiently operating system is the control of the generator output under widely varying speeds, how is a generator of the cumulative compound-wound type employed on the automobile?
- A. The series winding is in practically an independent circuit in connection with the lamps of the car so that its exciting effect is not added to the field magnets except when the lights are switched on. This automatically increases the generator output in accordance with the number of lights turned on so that the lights have no effect on the battery charging rate, which remains the same whether the lights are on or off. An external regulator is employed to control the battery-charging rate.

### Q. How does the generator differ from the motor?

A. Its essentials are all the same, i.e., it has a wound armature revolving in a magnetic field, commutator, brushes, etc., exactly the same as the generator.

## Q. This being the case, why are the two not interchangeable?

A. To a certain extent they are, that is, when a current is sent through the generator from an outside source, it becomes motorized and will run as a motor. But the two are far from being interchangeable on the automobile, owing to the widely differing requirements for which they are designed. The generator is wound to produce a cur-

rent seldom exceeding a value of 20 amperes while being driven over a wide range of speeds, and it is in constant operation. The starting motor, on the other hand, is designed to utilize an extremely heavy current, ranging up to 300 amperes or more at the moment of starting and is only used for very short periods.

- Q. How are these widely varying requirements reconciled in the single-unit type, in which both the generator and the motor are combined in one machine?
- A. The machine is practically two units in one, i.e., there are two totally different windings on the same magnet cores, a fine winding with shunt fields for the generator, and a very heavy simple series winding for the motor end. In some cases, as in the Delco, the different windings on the armature are brought out to independent commutators. While combined on one set of magnet cores, there is no connection whatever between the two windings in such a machine, so that when operating as a generator the motor windings are dead, and the reverse is true when being used as a starting motor.
- Q. What are the characteristics of the single-unit type of machine which is simply placed in circuit with the battery by a hand-operated switch when starting and left in that relation as long as the engine is running?
- A. This is a variable-potential type in which the relation that it bears to the battery and to the engine is entirely dependent upon the speed of the engine, that is, the speed at which the machine is driven. When the switch is closed, current from the battery operates the machine as a starting motor; as soon as the engine starts and attains

at generator, regulator, cut-out, ground, or battery terminals failure of cut-out to operate at proper voltage; worn or pitted contacts in regulator or cut-out; loose connections at brush holder short-circuited coils in the armature; some of the armature-or connections broken away from the commutator; short-circuit bars in the commutator.

### O. How can the generator output be tested?

- A. The simplest method is to switch on all the lamps with the engine idle. Start the engine and speed up to equivalent 15 miles per hour. The lights should brighten very perceptibl the test being made indoors in the daytime with the lights direct against a dark wall, or preferably at night. A more accurate te can be made with the portable volt-ammeter, using the 30-ampe shunt. Most generators have an average current output of 10 12 amperes, but the normal output as given by the maker shou be checked before making the test. Generators having a constant voltage control will show a greatly increased output if the batter charge is low, running up to 20 amperes or over. On such machine the condition of the battery should be checked either with the hydrometer or with the voltmeter before making the test. The charging current should be 10 to 12 amperes with a fully charge battery, and more in proportion when only partly charged.
- Q. What other simple method is there of determining quick whether the generator is producing its normal output or not?
- A. On generators having an accessibly located field fuse (the are several makes) lift this fuse out and, with the engine running at a speed equivalent to 10 miles per hour or more, touch the fusterminals lightly to the clips. If the machine is generating properly there will be a bright hot spark. Should no spark appear, replact the fuse and bridge the terminals with a pair of pliers by touching the jaws to the fuse clips; if a spark appears, the fuse has blown. Before replacing with a new fuse, find the short-circuit or other caus
- Q. Granting that the fuse has not blown, that the cut-ou regulator, and wiring are all in good condition, and still the generator does not produce any current, what is likely to be the cause
- A. One of the brushes may not be touching the commutato a brush connection may have broken, or carbon dust may have shor circuited the armature or field windings. Test for short-circuit

- Q. If the machine is generating current, and the auxiliary devices and wiring are in good condition, but the battery does not charge, what is the cause?
- A. Short-circuit in the battery due to active material having been forced out of the plates, or accumulation of sediment touching plates at their lower ends. (See Battery Instructions.)
- Q. Is the regulator ever responsible for a falling off in the current or for generation of excessive current?
- A. Yes. Any irregularity in the operation of the regulator will affect the output of the generator.
  - Q. How can this be overcome?
- This will depend upon the type of regulation employed A. (see Regulation). Where the method of regulation is inherent, i.e., forming part of the construction of the generator itself, such as the third-brush method, or a bucking coil, it may be remedied by cleaning and seating the brush properly or by testing the buckingcoil winding to see if its connections are tight and clean, or if it is short-circuited (see Windings). If cleaning and sanding-in the brush do not cause the generator to produce its normal output, the brush itself may be adjusted by shifting its location. Moving it backward or against the direction of rotation of the commutator will reduce the output; moving it forward or in the direction of rotation will increase the output. This refers specifically to the Delco regulation already described. To adjust properly, the portable ammeter should be put in circuit, and the effect on the reading noted as the brush is moved, clamping it back in place when the proper point is found. The brush should then be sanded-in to the commutator, as it will not have a good bearing if its original location has been disturbed.

#### Methods of Regulation

#### Q. Why is it necessary to control the output of the generator?

A. As explained in the section on electric generators, the amount of current produced depends upon the excitation of the fields, and the faster the armature revolves before the pole faces of the field magnets, the greater the amount of current that is sent through the windings of the magnets. As the speed of the automobile engine varies between such extremely wide limits, it will readily be seen that

it may rise to a point where this increase in the field excitation will cause so much current to be generated that the armature windings will be literally burned up. This happened very frequently in the early attempts to produce a lighting dynamo for automobile service. Regardless of how fast the generator may be driven, it is essential that its current output does not exceed a certain safe limit.

- Q. What is the usual safe limit in the majority of generators?
- A. Most automobile lighting-system generators are designed to produce 10 to 15 amperes at a normal speed, i.e., sufficient to light all the lamps and still provide a slight excess for charging the battery. No matter how fast its armature revolves, it must not exceed this by more than ten to twenty-five per cent, as a rule, this being well within its factor of safety. In some instances, where a voltage system of regulation is employed, the output of the generator depends upon the condition of charge of the battery. If the battery is practically discharged, the generator will charge the battery at a rate of twenty amperes or over. As the charge proceeds, the battery voltage increases and the resistance is increased correspondingly, thus cutting down the amount of current that the generator can force into the battery.
- Q. How is the current-generated kept from exceeding this safe limit?
- A. Mechanical methods were employed at first, a centrifugal governor being used to operate a slipping clutch. The generator was driven through this clutch, and the speed at which the armature revolved depended upon the engagement of the clutch; at low speeds both shafts would turn at the same rate. As the driving-shaft speed increased, the governor decreased the pressure on the clutch spring, and the clutch faces slipped on one another, so that the driven shaft turned proportionately slower than the driving shaft. The earliest types of governors, employed about 1903 to 1905, were not successful, but about 1908 a type was developed that worked effectively on thousands of cars. It has since been superseded by electrical methods of regulation, and practically all of those now in use are electrically operated.
- Q. How many electrical methods of regulating the amount of current generated are in general use?
  - A. So far as their principle goes, practically all are the same.

They depend upon weakening the excitation of the fields of the generator to cut down the output. It is in the methods of accomplishing this that they differ. In the latter respect they may be divided into two general classes: those that are inherent in the design of the machine, i.e., the regulating device is actually a part of the machine itself; and those in which an external regulator is employed. Those most commonly employed are, in the first class, the bucking-coil winding and the third-brush method; in the second, an external regulator is usually combined with the battery cut-out and designed to keep either the voltage or the current at a uniform value, usually the voltage.

#### Q. What is a bucking-coil winding, and why is it so called?

A. We have seen that in a series-wound machine all of the current generated in the armature passes through the field windings and energizes the field magnets; in the shunt-wound machine the wires carry only a part of the current which is proportional to the resistance that the shunt winding of the fields bears to the resistance of the outside circuit. As this outside resistance (the load) increases, more current will be diverted through the path of lesser resistance, or the shunt-wound field, and the output of the machine will increase accordingly. In the compound-wound machine, the relation of the series to the shunt winding is such that it is called upon chiefly to help carry any extra load. In other words, as the demands upon the machine increase, the series winding adds its energizing effect to that

third brush is employed, the main brushes are not in shunt with the fields, and they are not depended upon to supply the exciting curren for the latter. The third brush instead is used for this purpose. As i well known, the output of a generator depends very largely upon th position of its brushes. In the immediate vicinity of the proper loca tion for a brush, there is a short zone of maximum intensity. As we ge away from this toward the next brush, it decreases until at a poin midway between the two there is a neutral zone. The third brush i accordingly placed between the two main brushes, and its distance from the nearest main brush determines the amount of current that i diverts from the armature to the field windings. See illustration of Delco generator in section on Methods of Regulation. method has the advantage of supplying a strong shunt field at lov speeds. As the speed increases, the voltage applied to the shunt field decreases, even though that between the two main brushes may hav increased.

#### Regulators

### Q. What is a regulator, and what is its purpose?

A. It is an instrument somewhat similar to a battery cut-out and its purpose is to regulate the output of the generator in order tha the latter may not exceed safe limits at high speeds. The regulato is usually combined with the cut-out.

## Q. How does the constant-voltage type of regulator operate?

A. The instrument consists of a magnet winding and a pivoted armature, normally held open by a spring and a resistance unit. The winding of the magnet has sufficient resistance to prevent the core becoming energized to a degree where it will attract the armature unless the voltage exceeds the safe limit determined for the circuit. The voltage increases with the speed of the generator, so that when the latter is driven too fast the attraction of the magnet core for the armature becomes sufficient to overcome the pull of the spring which normally holds the contacts apart. (See description of Bijur voltage regulator.) When the contacts come together, the field circuit of the generator is shunted through the resistance unit; this cuts down the amount of current energizing the fields, the voltage falls off, and the contacts again separate. Unless the speed of the generator is decreased, this action is rapidly repeated, so that the regulator arma

ture vibrates at a high speed as long as the voltage is sufficiently high to energize the magnet.

- Q. What is the principle on which this type of regulator operates?
- A. The principle that in a circuit having considerable self-induction the amount of current which may be sent through the circuit will decrease if the current be pulsating instead of steady. Every time the contacts of the regulator open, a pulsation, or surge, or current is sent through the field windings of the generator; when they close because of the higher voltage, the current is shunted through the resistance unit, thus cutting it down. The decrease in the amount of current is in proportion to the number of pulsations per minute, i.e., the rapidity with which the vibrating contact operates. The circuit having considerable self-induction is that of the field winding of the generator, owing to its heavy iron core. (See Induction.)
- Q. What is the constant-current type of regulator, and how does it differ from the constant-voltage, or potential, type?
- A. It consists of an electromagnet and a spring-controlled pivoted armature, so that it is of practically the same construction as the constant-potential type, but it is connected in circuit with the armature of the generator and it is wound to operate under the influence of the current rather than the voltage. Consequently, the pivoted armature is attracted, opening the circuit when the cur-

employed, but the regulators differ more or less in design and opention. For example, in the Bosch-Rushmore generator, a bucking coil is employed in connection with what is termed a hallss registor, or resistance unit. This is of iron wire, and it is based on the fact that resistance increases very rapidly with the temperature The size of the wire is such that it allows 10 amperes to flow withou undue heating, so that its resistance is practically unchanged; above this point it heats rapidly and increases in resistance so greatly that a excess current is shunted through the bucking coil. In the Splitdo generator, the regulator is built in, projections of the pole pieces of th field being utilized in connection with special windings, instead of a independent electromagnet as in the Ward-Leonard and the Biju In the U.S.L. generator of the inherently regulated type, regulation accomplished by the combination of a Gramme ring armature. special arrangement of connections and of the field windings, and th use of only a part of the fields and armature for generating curren The regulation obtained is based on armature reaction and is similar in effect to the third-brush method. The U.S.L. external type c regulator cuts into the generator field circuit a variable resistance consisting of an adjustable carbon pile. In the Adlake regulator which is of the constant-potential type, a solenoid operates a swite over the contacts of a variable resistance. The plunger of the sole noid is counterbalanced by a weight, which must be raised to operat It is adjustable by increasing the weight of this counter balance.

### Q. What attention does the regulation of the generator require


A. This will depend upon the method employed in each cass Where an external regulator is employed, whether of the constant potential or the constant-current type, the attention required i practically the same as in the case of the battery cut-out. See that the points are not sticking, and when badly burned or pitted, smoot and true up, taking off as little of the contact point as possible to effect this. When the points have become so badly pitted that this cannot be done, new parts will be necessary.

With the third-brush method, the attention required by thi brush is the same as that which must be given the other brushes, i.e sanding-in at intervals and replacement when worn too short t permit the spring to hold the brush firmly against the commutator

Where the generator fails to produce sufficient current to keep the battery charged, all other parts of the system being in good condition and the car driven long enough in daylight to charge the battery under normal conditions, the position of the third brush may be shifted to increase the output. Care must be taken not to let it come in contact with the main brush. (See Delco instructions.) In the case of a bucking-coil winding, no attention is necessary, as this is an integral part of the machine itself. As the Splitdorf regulator has moving contact points, the attention necessary is the same as that required for an external regulator of this type. Special regulators, such as the U.S.L. external type, require attention covered by the maker's instructions. (See U.S.L. system.)

- Q. When the generator fails to keep the battery charged properly, a normal amount of daylight driving being given the car, is the fault most likely to be found in the regulator?
- A. No. It is much more likely to be caused by a dirty commutator, worn brushes, loose connections, or some similar cause which inserts extra resistance in the charging circuit. The movement of the regulator armature is very slight, and the current handled by the contact points is small, so that it will seldom be the cause of the trouble. Other causes, such as those above enumerated, should always be sought first. (See instructions under Generator.)

#### Windings

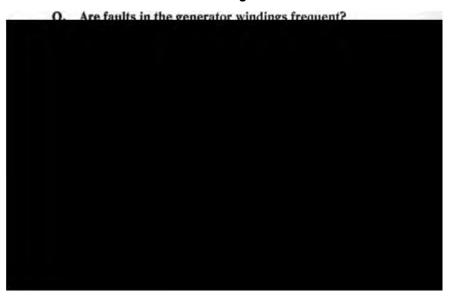

and make it break at that point, due to the vibration. Unless cleane out at intervals, fine carbon dust from the wear of the brushes ma accumulate in the interstices of the windings, and, when aggravate by moisture, this is apt to cause short-circuits.

### O. What are the usual indications of such faults?

A. With a short-circuited generator coil (armature), all oth parts of the apparatus and circuits being in good condition, the charging rate will be lower than normal. The ammeter needle we wibrate violently when the engine is running at low speeds, and two or more adjacent commutator bars will burn and blacken. With an open armature coil (broken wire), the indications will be pratically the same, and there will be severe sparking at the brushe causing serious burning of the commutator bar corresponding the open coil. A grounded armature coil will give the same gener indications, and if the machine is a single-unit type, the cranking ability of the starting motor will be seriously impaired. The ammeter, however, will not vibrate as in the former cases. The will be practically no charge from the generator, and the batter will be discharged very rapidly by the starting motor.

In a single-unit machine, when the windings of the generate and the starting motor become interconnected, the indication will be practically the same as those of a grounded armature co If the motor windings of a single-unit machine become grounde there will be an excessive discharge from the battery, while the motor will develop but little power.

## Q. How may such faults be located?

A. With the aid of the testing-lamp outfit. Remove the brushes (when replacing them later, be sure to put each brushack in the holder from which it was taken), or the brushes make insulated from the commutator by placing paper under them. For a grounded coil, place one test point on the commutator are the other on the frame; if grounded, the lamp will light. For inteconnected motor and generator windings in a single-unit maching having two commutators, insulate the brushes as mentioned an place the test points one on each commutator. The light will but if the two windings are connected. For a grounded-motor winding test from the motor commutator to the frame; the light should burn if the insulation is all right. For a break or open circu

in the field winding, touch the terminals of the latter with the test points, the commutator being insulated or the armature removed. The lamp should light. For a blown field fuse on machines so equipped, place the points on the clips; if the fuse is intact, the lamp will light.

#### Q. Are these tests conclusive?

A. No. They will indicate any of the faults mentioned, but they will not reveal an internal short-circuit in the windings, which cuts some of the armature or field turns out of action but does not break the circuit as a whole. Such a short-circuit reduces the output of the generator and can be determined definitely only by measuring the resistance of the windings. This requires special and expensive testing instruments, such as the Wheatstone bridge, so that where all other tests fail to reveal the cause of a falling off in the output of the generator, it should be sent to the maker for inspection.

#### Commutator and Brushes

- Q. What does a blackened and dirty commutator indicate?
- A. Sparking at the brushes or an accumulation of carbon dust due to putting lubricant on the commutator.
  - Q. What is the cause of sparking at the brushes?
- A. Poor brush contact, due to worn brushes; brush-holder springs too loose, so that brushes are not held firmly against the commutator; excessive vibration, which may be due to a bent shaft, an unbalanced gear pinion, or improper mounting; using too much

oil or using greese in the hell bearings, which gets on the commutator.

- Q. Why do some commutators need undercutting and others not?
- A. Undercutting is required only on machines equipped with brushes that are softer than the mica. Copper-carbon brushes, as employed on starting motors to reduce the brush resistance, are hard enough to keep the mica worn down with the copper of the commutator itself.
- Q. If, after smoothing off and undercutting the mica, the commutator still has an uneven and irregular surface, what is the remedy?
- A. The armature should be removed from the machine, and the commutator trued up in the lathe, taking as light a cut as possible consistent with obtaining a true round and smooth surface.
  - Q. How can excessive commutator wear be prevented?
- A. Inspect at regular intervals and on the first sign of sparking smooth up the surface and sand-in the brushes. Keep the commutator clean and do not permit carbon dust or oil to accumulate in the commutator and brush housing. Never replace brushes or brush springs with any but those supplied by the manufacturer for that particular model. The machine will work with any old brush and any old spring that fits, but they will prove detrimental to its operation in a comparatively short time, and its working under such conditions will never be satisfactory.
- Q. Is discoloration of the commutator ever caused by anything else than sparking?
- A. Not actual discoloration which requires cleaning, but the normal operation of the machine produces a purplish blue tinge on the bars, which is sometimes mistaken for discoloration by the inexperienced. This color, in connection with a high polish of the metal, indicates that the commutator is in the best of condition. Once the commutator takes on this high polish, it will operate for long periods without other attention than the removal of dirt by wiping with a clean rag. Sanding to remove this purple tinge is a mistake, as it only destroys the polish without having any beneficial effect.
  - Q. Is it necessary to lubricate the surface of the commutator?
- A. No. The brushes employed are usually of what are termed ting type and require no attention in this respect.

- Q. Will any harm result from putting light grease, vaseline, or lubricating oil on the surface of the commutator?
- A. As all lubricants are insulators to a greater or less extent, the efficiency of the machine will be reduced and, as the voltage is very low, but a slight falling off is necessary to represent a very substantial percentage of the maximum. The use of lubricant of any nature on the commutator also has another harmful effect in that it collects the carbon dust resulting from the wear of the brushes, causing it to lodge against them as well as between the commutator bars.
- Q. Why should particular care be taken to remove all carbon dust from the commutator housing of both the generator and the motor (two-unit system) or the single unit where both functions are combined in one machine?
- A. Carbon dust is an excellent conductor of electric current and, when spread over the surface of an insulator, it causes the latter to become conducting as well. Consequently, it is likely to short-circuit the commutator bars by lodging between them. It will cause leakage across fiber or other insulating bushing of brush holders when a sufficient deposit accumulates on them. It will penetrate the armature and field windings of the machine and may cause trouble by grounding or short-circuiting them. Especial care should be taken to remove all traces of carbon dust after sanding-in the brushes.
  - Q. How often should the commutator be inspected?
- A. The commutator is the most vulnerable part of any directcurrent machine, whether it be a generator or motor, and it should

The second of th

ind narrow of different inalization is until the crushes. Sense it describes inalization of the crushes of the crushes are to produce the same fixed the narrow of the crushes are to produce to the same relation of the crushes the same relation of the crushes the crushes are to the crushes the crushes are the crushes

į

١

İ

ì

", I by a trust adventile it use trustes ther than this impolied by he manufacturer is implacements in a machine?"

The maintain tall the control of the

1) When inspection shows that the brushes have worn down unionally, that should be done?

The month of anded in eith a strip of fine sandpaper in him in the preferable already council the brushes are very soft to a more traction for dange the properly in connection with machine at different modes. To more should be removed than is absolutely more are to broughthe end of the brush to a firm contact all over it bearing author on the commutator, and the end of the brush, after the ampletion of the operation, should not show any deep scratche expirement. This is the surface resmooth and true, injurious spark into additional contract the endance of the machine will be decreased.

O It with a smooth and true surface, the brush still fails to make good contact, what is the fromble?

A the beach by probably worn down until it is too short for the promessions with a whole a took against it to hold it against the • commutator properly, or the spring itself may be at fault. Wear of the brush beyond the point where it is any longer of service will most often be the cause.

- Q. Where the brushes are true and are making good contact against the commutator, but the machine is inoperative, all other parts of the system being in good condition, what is likely to be the trouble?
- A. One of the pigtails, or short flexible connections, of the brushes may have shaken out from under its spring clip. This breaks the circuit, just as a parted wire or a ruptured connection at a terminal in any other part of the system would.
  - Q. How often is it necessary to replace the brushes?
- A. This differs so much with different makes of machines that it cannot be answered definitely, even as an average. On two-unit systems, the generator brushes will naturally require replacements much sooner than those of the starting motor, as the starting motor is only in operation for very short periods, while the generator is working constantly. On single-unit types, this naturally does not apply, as, whether the armature has one or two sets, they are always in use. Ordinarily, brushes should not require replacement under a year, and frequent instances are known of their having lasted for two years or more. It depends upon the care given the commutator and brushes quite as much as upon the mileage covered, as, if allowed to run dirty for any length of time, the brushes will wear away much faster than if kept in good condition. The best rule for the replacement of the


- A. It is a carbon brush of the same nature as the others used on the same machine, and the care required to keep it in good condition does not differ. However, it is mounted in an independently adjustable holder so that it may be moved backward or forward with relation to the main brushes in order to increase or decrease the output of the generator. (See instructions [Delco] on this point.)
- Q. Is it ever necessary to alter the location of the brushes of a machine?
- A. Except on generators fitted with the third-brush method of regulation, on which it may be necessary to shift the main brushes slightly to avoid having the third brush come in contact with one of them when moved to change the output, it should never be necessary to shift the location of the brushes. Brush location has an important bearing on the operation of the machine, and, in designing it, the maker has fixed the location of the brushes to conform to its other characteristics. Many machines have no provision for adjusting the brushes in this respect, while some manufacturers caution the user particularly against altering their location.
- Q. How much spring pressure is usually employed to hold the brushes of the generator and starting motor against the commutator?
- A. This varies with different makes of machines and should be ascertained from the maker's instructions in every case in order to check up properly. In the various models of the Gray & Davis starting motors, this spring pressure ranges from 2½ to 3½ pounds, which is the minimum necessary. In other words, the brush must be held against the commutator with this amount of pressure in order to operate efficiently. While there will be a loss if the pressure drops below the minimum, there is no advantage in greatly exceeding it, as excess pressure simply causes greater friction loss without any compensating gain in power. Generator-brush pressures are much less than those employed on starting motors, owing to the smaller amount of current handled.
- Q. How can the proper spring pressure of the brushes be checked?
- A. With the aid of an ordinary spring scale of the direct-pull type, in which the pull on the hook draws the pointer down over the scale. A scale reading to five pounds is adequate for the purpose; one intended for heavy weights is not likely to be so accurate. Attach

the hook of the scale to the brush and pull until the brush is just clear of the commutator. The scale will then register the pull in pounds. Where there is nothing on the brush to which to attach the hook, such as a screw, place a thin piece of wood on the brush face before passing the hook of the scale around it, to prevent injuring the contact face of the brush. In this case, the spring pressure as shown on the scale will exceed the necessary minimum, as the spring must be compressed further than it would be when in operation, in order to operate the scale. This should be allowed for when taking the reading.

- Q. When is it advisable to check the spring pressure of the brushes?
- A. When there is undue sparking at the commutator, while the commutator and brushes are all in proper condition, i. e., clean, and bearing uniformly over their entire surface so that the sparking is not due to any fault in either of these essentials.
- Q. When the brushes and commutator are in good condition and the spring-scale test shows that the brushes are being held against the commutator with the necessary amount of pressure, what is likely to be the cause of the sparking?
  - A. There may be a short-circuited or open coil in the armature.
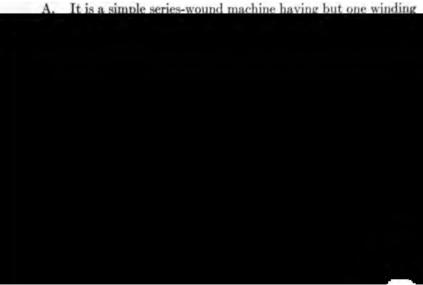
#### STARTING MOTOR

Q. In what way does the starting motor of a two-unit system differ from the generator?



wholly discharged battery will be responsible. If the battery is all right, a loose connection at the battery, switch, or motor, or a short-circuit in some part of this wiring may be the cause. Should the battery be properly charged, all wiring and connections in goo condition, switch contacts clean, etc., the starting gears may be binding, owing to dirt or lack of alignment between the motor shall and the flywheel of the engine. In this case, the motor will attemp to start when the current is first turned on, but will be held fas Loosen the holding bolts and line up the motor, cleaning the geat teeth if necessary.

- Q What is likely to be the cause of the starting motor runnin slowly and with very little power?
- A. Exhausted battery, poor switch contacts, loose connections, partial ground or short-circuit in wiring causing leakage improperly meshing gears, dirty commutator, brushes making poc contact owing to weak springs or worn brushes, or a ground in the motor itself. The remedies for all these faults have been given already
- Q. When the battery and all connections and wiring are i good condition, but the motor fails to crank the engine, what is likel to be the cause?
- A. The engine may be too stiff. If it has been overhaule just previously, the main bearings may have been set up too tight Test with the starting crank to see if it can be turned over easily by hand. If unusual effort is required, easing off the bearings should remedy the trouble. Should the engine not turn over as soon a the switch is closed, release immediately, as otherwise the battery will be damaged.
- Q. When the engine does not start within a few seconds, wh is it better to use the starting motor intermittently than to run it con tinuously until the engine does fire?
- A. The intermittent use of the starting motor, say ten second at a time, with a pause of half a minute or a minute between attempt is easier on the battery. If allowed to rest for a short period, the storage battery recuperates very rapidly. Consequently, the operation of the starting motor for two minutes, divided into twelve period of ten seconds each, will not run the battery down to anything like the extent that its continuous operation for the same length of time would Moreover, this intermittent method of operation increases the chance

Of starting under adverse conditions, as, in very cold weather, every time the battery is allowed to rest, it will be able to spin the engine at its normal starting speed, whereas if the starting motor is operated continuously, the battery will become so weak that the engine will be turned over very slowly toward the end of the period in question.

- Q. Why is it that a starting motor capable of turning an engine over at a speed anywhere from 75 to 150 r.p.m. will sometimes fail to start the engine, whereas hand cranking subsequently resorted to will succeed?
- It must be borne in mind that the operation of starting an engine in cold weather involves several factors. (1) The pistons, crankpins and crankshaft (bearings) must be broken away, i.e., forcibly released from the hold that the gummed lubricating oil has on them, before they can be moved. The great difference between the power required to do this in summer and in winter is shown by the greatly increased amount of current used by the starting motor. (2) Gasoline and air must be drawn into the cylinders, to effect which in sufficient quantity to start the engine requires quite a number of revolutions. (3) The gasoline must be vaporized so that it will mix with the air, which involves more turning of the engine to create the necessary heat by compression in the combustion chambers and the friction of the moving parts. In the application of energy in any form, two factors are always involved, i.e., the unit, or quantity of power applied, and the length of time during which it is applied. starting motor cranks the engine at a comparatively high speed for a

heiof poriod - In hand combing a smaller unit of a smaller makes

A. A simple series-wound machine (practically ali electric star ing motors are of this type) is capable of standing exceedingly heav overloads for short periods, it being nothing unusual for these small motors to have a factor of safety of five, or even seven, for a limit time, that is, they will take five to seven times the normal amou of current for a brief period without injury. As a matter of fact, t starting motor can utilize all the current the battery is capable supplying, provided the motor is free to move. If the engine is stufast or some part of the starting system has gone wrong so that t electric motor cannot turn over, then there is danger that the mot may be damaged unless the switch is opened at once. This, togeth with the fact that the maximum load which may be placed on t motor at different times is such a variable quantity, would make it difficult matter to provide a fuse that would not blow unnecessaril The only object of the fuse would be to protect the motor winding and, as the latter can stand all the current the battery can supply, the only source of danger is the possibility of the motor being held fa so that its armature cannot revolve.

## WIRING SYSTEMS

#### Different Plans

- Q. What is the difference between the single-wire and tl two-wire systems?
- A. In the single-wire there is but one connection to the operating circuit by means of a wire or cable, the circuit being complete in every instance by grounding the other side of the circuit. F this reason the single-wire is also referred to as a grounded system. In the two-wire system, copper wires or cables are employed to complete the circuits between the generator and battery and between the battery and the starting motor, as well as to the lamps.
  - Q. What forms the return circuit of a single-wire system?
  - A. The steel frame of the chassis.
  - Q. How are the various circuits grounded?
- A. In the case of the battery, a special ground connection usually made by drilling the frame and fastening a clamp to i The ground cable from the battery is attached to this clamp. The generator and starting motor are grounded internally, i.e., the er of a winding or of a brush lead that would be taken out to form the

return side of a two-wire system is connected to the frame of the machine, and the latter completes the connection to the chassis through its holding bolts or other means of attachment. One side of all lamp sockets is usually grounded, so that the bulb itself completes the connection when fastened in place. Sometimes there is a special ground connection from the battery for the return side of the ignition or lighting circuits, and this ground wire is fused.

## Q. What are the advantages and disadvantages of the single-wire system?

A. It greatly simplifies the wiring, as but one wire connection is necessary to the apparatus for each circuit, but this advantage renders it more susceptible to derangement through unintentional grounds or short-circuits, since the touching of any metal part of the chassis by a bare wire will cause a short-circuit. This depends to a very great extent, however, on the thoroughness with which the wiring is protected, and, with the armored cables or loom and the junction boxes used on modern installations, it is reduced to a point where both systems are practically on a par in this respect.

## Q. What are the advantages and disadvantages of the two-wire system?

A. Each circuit is complete in itself thus rendering it easier to locate faults, while no one connection coming in contact with a metal part of the chassis will cause a ground. The wiring itself, however, is much more complicated, and, with the small space available on the bulb connections, it is more difficult to insulate them properly.

## Q. Which system of wiring is favored?

A. The single-wire system will be found on the majority of cars, and the number of makers adopting it is steadily increasing.

#### Faults in Circuit

## Q. What is the difference between a ground and a short-circuit?

A. So far as the effect produced is concerned, they are the same; the difference in the terms referring solely to the method of producing it. For example, if the cable of the starting motor circuit becomes abraded and the bare part touches the chassis or some

connecting part of metal, this is a ground. But it is also a short-circuit in that the circuit to the battery is completed through a shorter path than that intended. On the other hand, if, in a two-wire system, the two cables of the same circuit become chafed close together and their bared parts touch, this is a short-circuit, but it is not a ground. For all practical purposes, however, the two terms are really interchangeable when applied to faults in the circuit. (See Gray & Davis instructions.)

## Q. How may grounds be located in a single-wire system?

In any of the fused circuits, the fuse will immediately blow out. Remove the fuse cartridge and shake it: if it rattles. the fuse wire has melted and the fuse is blown. If it does not rattle, short-circuit the fuse clips with the pliers or a piece of metal; a spark will indicate the completion of the circuit and will also indicate that the fuse has blown. If, on bridging the fuse clips. the lamp lights, or other apparatus on the circuit operates, the short-circuit was only temporary. This does not mean, however. that the fault has been remedied; the vibration of the car may have shaken whatever caused it out of contact and further vibration sooner or later will renew the contact with the same result. Inspect the wiring of that particular circuit and note whether the insulation is intact throughout its length. See that no frayed ends are making contact at any of the connections and that the latter are all tight and clean. In case the lamp does not light on bridging the fuse clips, see if the bulb has blown out; if not, use the test lamp by applying one point to the terminal and the other to various points along the wiring.

## Q. Does the blowing of a fuse always indicate a fault in the wiring?

A. No. A bulb, in blowing out, frequently will cause a temporary short-circuit that will blow the fuse. To determine this, apply the points of the test-lamp outfit to the bulb contacts; if the test lamp lights, the bulb is short-circuited, and a new fuse and bulb may be inserted without further inspection of the circuit. In case the test lamp does not light on this test, it does not necessarily indicate a fault in the wiring of that circuit, though inspection is recommended before putting in new fuse and bulb. The blowing out of the bulb may cause a short-circuit, which is ruptured by the

current burning away the light metal parts that were in contact, such as a small piece of the filament.

- Q. Can a short-circuit or ground occur without blowing a fuse?
- A. Yes. No fuses are employed on starting-motor circuits owing to the very heavy current used and its great variation depending upon the conditions, such as extreme cold gumming the lubricating oil, tight bearings, binding of the pinion and gear, sprung shaft, starting motor out of alignment, or the like. On other circuits, the amount of current leaking through the fault in the circuit may not be sufficient to blow the fuse, as the capacity of the latter is such that it will carry the maximum current which the apparatus in that circuit will carry without damage—usually 5 or 10 amperes on lighting circuits and 10 amperes on generator-field circuits.
  - O. How can such faults be noted?

ŗ

- A. The ammeter, or indicator, will show a discharge reading when the engine is idle and all lamps are switched off.
  - Q. What is the usual nature of such a fault?
- A. The battery cut-out may have failed to open the circuit completely; a frayed end of the stranded wire at one of its connections may be making light contact which will permit a small amount of current to pass; a particle of foreign matter of high resistance may be bridging a gap either at the cut-out or some other part of the circuit; or the ignition switch may have been left on the battery contact so that current is flowing through the



## Q. What is one of the most frequent causes of short-circuits in a two-wire system?

A. The bulbs and their sockets, owing to the very small amount of space available for the insulation. Dirt or particles of metal may be bridging the small gaps between their insulated contacts. A blown-out bulb also may be responsible, as previously mentioned.

#### **Proper Conduction**

## Q. Why are different sizes of wire employed in the various circuits?

A. To permit the passage of the maximum current necessary in each circuit consistent with the minimum drop in voltage due to the resistance of the wire and its connections. The voltages employed are so low that any substantial drop due to this cause would seriously impair the efficiency of the system and particularly of the starting motor. For the latter the cables employed are not only large, but they are also made as short and direct as possible to save current as well as expense in the installation.

## Q. What is the smallest wire that should be employed in automobile wiring?

A. No. 14 B. & S. gage, and this should be used only for the tail lamp, dash lamp, primary circuit of the ignition, or similar purpose. No. 10 or No. 12 is usually employed for the other lighting circuits.

## Q. When, in making alterations on a car, it becomes necessary to extend a circuit, what should be done?

A. The ends of the wires should be scraped clean and bright for at least 2 inches, and a lineman's joint made with the aid of the pliers to insure having it tight. A lineman's joint is made by crossing the bared ends of the wires at their centers at right angles to each other, then wrapping or coiling each extending end tight around the opposite wire; the joint then should be soldered and well taped. A circuit should be extended only by using wire of the same size and character of insulation. None of the foregoing applies to the starting-motor circuit. It is inadvisable to lengthen this circuit if avoidable, but in the rare instances when it would be necessary, new cable of the same size or larger and with the same insulation should be cut to the proper length and the old cable

discarded. All terminals should be solidly fastened to the new cable by soldering.

- Q. Why is it necessary to use such heavy cable for the connection of the starting motor to the battery?
- A. It is essential that the exceedingly heavy starting current be transmitted with the minimum of loss.
- Q. What is considered the minimum permissible loss in the starting-system wiring?
- A. One maker specifies that the starting cable must be large enough to transmit a maximum current of 400 amperes with not over one-fourth volt total loss.
- Q. Why is it important to hold the voltage drop down to a maximum so small as to be negligible in almost any other application?
- A. Owing to the heavy current necessary, as a drop of but ½ volt in potential with a current of 400 amperes represents a loss of 100 watts, or close to ½ horsepower. Of course, the current seldom reaches such a high value as this except when a motor is exceptionally stiff, as in severe cold weather or just after its bearings have been set up very tight; moreover, this loss takes place at the instant of starting only, but it is just at this time that the highest efficiency and full battery power is needed to start without spinning the engine too much.
- Q. On some of the early systems whose efficiency was not of the best, how can the proper size of cable to use between the starting motor and battery be determined?
- A. Test the starting motor with a high-reading ammeter (scale should read to at least 300 amperes) after having made certain by hydrometer and voltage tests that the storage battery is fully charged. (See instructions regarding this.) Carefully note ammeter reading exactly at instant of closing switch, to determine maximum current flow. Measure the length of cable between the battery and the starting motor, i.e., both sides of starting switch. Then maximum starting current times 10.7 times number of feet of cable used, divided by .25 will give the cross-section of the wire in circular mills. For example, assume that the starting motor required a maximum of 300 amperes momentarily to break away the engine, and five feet of cable are employed for the connections. Then

$$\frac{300\times10.7\times5}{25} = 128,400 \text{ circular mills}$$

By referring to Table I, Part I, which gives the various size wires in circular mills and their equivalent in gage sizes, it will be noted that the closest approach to this is No. 00 cable, which is 133,079 circular mills, so that the largest size cable would have to be used. If the starting cable used on an old system which does not show particularly good efficiency is much smaller than this, it would probably be an advantage to replace it with larger cable, assuming, of course, that every other part of the system is in good condition and working properly.

### Q. Why should connections be inspected frequently?

A. The vibration and jolting to which they are subjected in service is so severe that no mechanical joint can be depended upon to remain tight indefinitely.

### Q. What harm does a loose or dirty connection occasion?

A. A loose connection causes the formation of an arc between its contacts whenever vibration causes the parts to separate temporarily. This wastes current and burns the metal away, leaving oxidized surfaces which are partially insulating, thus increasing the resistance at the connection. Dirt getting between the surfaces of the connector has the same effect; the resistance is increased and there is a correspondingly increased drop in the voltage of the circuit, which cuts down its efficiency.

# Q. Why should all terminals be well taped when the battery, starting motor, generator, or other apparatus is temporarily disconnected for purposes of inspection or test?

A. To prevent accidental short-circuits which would be caused by these terminals coming in contact with any metal part of the chassis on a single-wire system. Such a short-circuit would ruin the battery and burn out any lamps that happened to be included in the circuit. This precaution applies with equal force to the two-wire systems, as in this case the terminals of the different wires might come together, or there might be a ground connection in the system.

#### PROTECTIVE AND OPERATIVE DEVICES

- Q. What are the protective devices usually employed on electric systems?
  - A. Fuses in the separate lamp circuits, in the ground con-

#### ELECTRICAL EQUIPMENT

ection, and in the field circuit of the generator on some machine attery cut-out for the charging circuit; circuit-breaker whice akes the place of the fuses.

#### **Fuses**

- O. What is a fuse and what is its function?
- A. A fuse consists of a piece of wire of an alloy which melat a low temperature and which will only carry a certain amount current without melting, the latter depending upon the diamete of the wire, i.e., cross-section and the nature of the alloy. The fus is usually in the form of a cartridge, the wire being encased in a insulating tube having brass ends, to which the ends of the wire as soldered. These brass ends are pressed into spring clips to put the fuse in circuit. In some cases open fuse blocks are employed, the wire itself simply being clamped under the screw connectors on the porcelain block. The function of the fuse is to protect the batter and the lamps when, by reason of a ground or short-circuit in the wiring, an excessive amount of current flows.
  - O. When a fuse blows out what should be done?
- A. Investigate the cause before replacing it with a new on (See Wiring Systems.)
- Q. Is it permissible to bridge the fuse gap with a piece copper wire when no replacements are at hand?
- A. Only in cases of emergency and after the short-circ
  seaused the fuse to blow has been remedied. The fin
  such as a single strand from a piece
  heing no gro

fuse may be inserted without instantly blowing, as it would do were the short-circuit constant. This is often the case as the car is stopped to inspect the wiring and insert the new fuse, and standing still lets the part drop out of contact; starting up shakes it into contact once more and blows the new fuse. Loose connections, wires with abraded insulation, and bulbs loosely inserted in their sockets are apt to cause trouble of this nature.

## Q. Does the blowing out of a fuse necessarily indicate a fault in the wiring or in some other part of the system?

A. No, since a bulb in burning out will frequently cause the fuse to blow out. This is due to the fact that in breaking, the end of the parted filament of the bulb may fall across the other terminal where it comes through the glass, thus causing either a short-circuit or such a reduction in the ordinary resistance as to permit a much heavier rush of current than normal, with the result that the fuse goes. To test, leave burnt-out bulb in place temporarily; short-circuit fuse clips with screw driver or pliers, just touching them momentarily; if no spark results, replace bulb with a new one and test again; if a spark occurs, remove old bulb and test again with no lamp in place; then if no spark occurs in bridging the fuse terminals, the circuit is all right, and the fuse may be replaced.

## Q. When all the lighting fuses blow out at once, what does this indicate?

A. A short-circuit across the lighting-switch terminals would cause this. In some switches with exposed rear terminals, it is possible to place a screwdriver or similar piece of metal in such a position that it bridges practically all the switch terminals. If the lighting switches were all closed at the time, this would short-circuit them.

#### Circuit-Breaker

#### Q. What is a circuit-breaker, and what is its function?

A. The circuit-breaker is an electromagnet with a pivoted armature and contacts, similar in principle to the battery cut-out. All the current used in the various circuits, except that of the starting motor, passes through it, and its contacts normally remain closed. The winding of the magnet coil is such that the normal current used by the lamps or ignition does not affect it, but the passage of an excessive amount of current will energize the magnet, attract

the armature, and break the circuit. The spring holding the armature away from the magnet will again close the circuit, and the circuit-breaker will vibrate until the cause has been removed. This is usually a ground or short-circuit. The function of the circuit-breaker is to protect the battery and lamps in place of the usual fuses.

- Q. If the circuit-breaker operates when there are no faults in the wiring, what is likely to be the cause?
- A. Its spring may have become weakened so that the vibration of the car causes it to operate on less current. The Delco circuit-breaker is designed to operate on 25 amperes or more, but, once started, a current of 3 to 5 amperes will keep it vibrating. If tests show that no faults in the wiring or connections exist, increase the spring tension with the ammeter in circuit until the reading of the latter indicates that the circuit-breaker is not operating on the current of less value than that intended. See that the contacts are clean and true.

#### **Battery Cut-Out**

- Q. What is a battery cut-out?
- A. It is an automatic double-acting switch which is closed by the voltage of the generator and opened by the current from the battery.
  - O. Of what does it consist?
- A. It is essentially a double-wound electromagnet with a

coil and closes the contacts, cutting in the current coil, which further excites the magnet and holds the contacts firmly together. The closing of these contacts puts the battery in circuit and it begins to charge. As soon as the generator speed falls below the point necessary for charging, the battery voltage overcomes that of the generator and sends a current in the reverse direction through the current coil, causing the contacts to separate and cutting the battery out of the charging circuit.

- Q. If the generator is run for any length of time at or near this critical speed, what is to prevent the cut-out from vibrating constantly instead of working positively one way or the other?
- A. The resistance of the windings is so proportioned that there is a difference of 1 to 2 volts between the cutting-in and the cutting-out points.
- Q. What is the result when the battery cut-out—which is variously termed a cut-out, a circuit-breaker, an automatic switch, and a reverse-current relay or an automatic relay—fails to operate?
- A. If it fails to cut in, i.e., the contacts do not come together, the battery does not charge and will quickly show a falling-off in capacity, such as inability to operate the starting motor properly of to light the lamps to full brilliance. If it fails to cut out, the battery charge will be wasted through the generator windings with the same indications of lack of capacity.

### Q. What is the most frequent cause of trouble?

A. Automatic cut-outs have been perfected to a point where but little trouble occurs. Freezing or sticking together of the contacts due to excessive current will most often be found to be the cause of the device failing to cut out when the generator is stopped. The points should be cleaned and trued up as described in previous instructions. Loose or dirty connections making poor contact may insert sufficient extra resistance in the circuit to prevent the device from cutting in at the proper point. Excessive vibration, particularly when the cut-out is mounted on the dash, may prevent the contacts from staying together as they should when the engine is running at or above the proper speed. See that the cut-out is solidly mounted. Temporary loss of battery capacity may be due to slow driving over rough roads at about the speed at which the cut-out is designed to put the battery in circuit.

- Q. None of the above causes existing, what further tests may be made?
- A. The windings may be tested as already described for the generator windings, but trouble from this source is equally rare. If the contacts are clean and true and the connections are tight, look for a loose connection elsewhere, as at the generator or battery or the ground on the frame. A loose connection vibrates when the car is moving, constantly opening and closing the circuit and causing the cut-out to do likewise, so that the battery does not charge. A wire from which the insulation has been abraded will also vibrate, owing to the movement, causing an intermittent short-circuit. With all contacts and connections in good condition, failure to cut out indicates a ground or short-circuit between the battery and cut-out; failure to cut in indicates similar trouble between the generator and the cut-out.
  - Q. Is a battery cut-out necessary on every electrical system?
- A. No. On single-unit systems of the type of the Dyneto, in which the generator becomes motorized as soon as its speed and consequently its voltage drops below a certain point, the battery is always in circuit. A plain knife-blade switch, which also controls the ignition, is closed to start and left closed as long as the car is running. But the engine must not be allowed to run at a speed below which it generates sufficient voltage to charge the battery, nor must the switch be left closed when the engine is not running; otherwise, the battery will discharge through the generator windings.

refer to the flexible, or spring-arm type, while in the solid-arm type of the same make, they are .010 for the distance between the contact points and .015 for the armature air gap, it being necessary that the armature should be set parallel with the pole face of the magnet.

- Q. How can these small distances be accurately determined with the facilities ordinarily found in a repair shop?
- A. The manufacturers usually supply a small adjusting wrench, the different edges of which have been ground to varying thicknesses representing the proper distances for the various gaps. Lacking one of these, small pieces of strip brass or steel may be ground or filed down to the proper size and gauged with a micrometer, which should be part of the equipment of every garage. The strips should be stamped with the dimensions and name of gap for identification.
- Q. How often will the point of a battery cut-out need adjustment, or truing up?
- A. Service conditions vary so greatly that it is impossible to give any definite average for this, particularly as the instruments themselves also are a variable quantity, but, under ordinarily favorable conditions, they should not require attention more than once a year.

#### Contact Points

- Q. Why is it necessary to make contact points of such an expensive metal as platinum, and why is the latter sometimes alloyed with irridium?
- A. There is no other metal which withstands the oxidizing effect of the electric arc and still maintains a clean and bright conducting surface as does platinum. Irridium is added to make the platinum harder, so that it will be more durable. On cheaply made instruments in which no platinum has been used in the contacts, trouble will be experienced constantly with the contacts.
- Q. Is there any substitute for platinum or any metal that approaches it in adaptability for contact points?
- A. There is no substitute for platinum, and the only metal that approaches it is silver. Where contact points only separate occasionally at intervals, as in the Remy thermoelectric switch, the use of silver contacts is permissible; but in a battery cut-out, or a regulator in which the vibration of the points is more or less constant, nothing will serve so reliably as platinum.

- Q. What is the cause of the pratinum contacts burning into such irregular ragged forms?
- A. When a current of electricity passes through a contact of this nature, the material of the positive electrode (i.e., contact point connected to the positive side of the circuit) is carried over by the current in the shape of metallic vapor, or infinitely fine particles, and deposited on the negative electrode. The positive consequently takes on the form of a sharp point, while the negative has a depression formed in it, usually referred to as a "peak and crater", which the two points resemble in miniature after long use. This peak and crater effect is much more noticeable in an old-style carbon arc lamp after it has been burning only a few hours.
  - Q. What can be done to prevent this?
- A. The passing of the metal from one electrode to the other cannot be prevented, as it is a function of any arc or spark. It can be minimized, however, by keeping the contacts in good condition so that the sparking is reduced to a minimum.
- Q. Can the formation of the pack and crater effect, which so greatly reduces the efficiency of the contacts, be avoided?
- A. The use of a reversing switch in the circuit, as in the case of the magneto or the battery-type interrupter which changes the direction in which the current flows through the points every time it is turned on, will overcome this. Where there is no reversing switch in the ignition circuit or where one cannot be used, attention to the

to make true parallel surfaces, the points need not be replaced the means for adjustment permits utilizing them when worn far down

- Q. What is the cause of the points freezing, or stickin together?
- A. Permitting them to wear down to a point where they are very poor condition and where the gap between parts of their surface causes the formation of a heavy arc, or hot flash of current, whi practically welds them together. By giving them the necessal attention at regular intervals, this may be avoided.
  - Q. How often should the contact points need attention?
- A. When new, they should run for a year or more without a attention. After they have been trued up, the succeeding intervil often depend upon the skill and care with which this has be carried out.

#### **Switches**

- Q. How do switches as employed on the automobile diffin principle and operation?
- A. Starting-circuit switches are either of the knife-blade the flat-contact type, while in the majority of cases the lighti switches are of the push-button type, though knife-blade switch are used for this purpose also. In some instances, one of the brush of the machine is made to serve as a switch, as in the Delco. Or narily, the switch is normally held open by a spring and is clos by foot pressure, the spring returning it to the open position soon as released. A variation of this is the Westinghouse electr magnetically operated switch in which a solenoid takes the place foot operation. The circuit of the solenoid is controlled by a sprin push button, which is normally held out of contact. Single-un systems, such as the Dyneto, in which the machine automatical becomes motorized when the speed drops below a certain poin are controlled by a standard single-throw single-pole knife-blad switch which is left closed as long as the machine is running.
  - Q. What faults may be looked for in switches?
- A. Loose connections; weakening of the spring; burning the contact faces in the knife-blade type, due to arcing caused t releasing too slowly; dirt or other insulating substance accumulating on the contact faces of the flat-contact type; failure to release throug binding.

ŗ

- Q. Why is it important to keep the switch contact faces clean and bright?
- A. Dirt or burned surfaces increase the resistance and cause a drop in the voltage at the starting motor. The energy represented by an electric current is a measure of the volume or amperes times the voltage or pressure under which it flows, and, as such low voltages are used, only a slight falling off represents a serious percentage of the total potential. With a dirty switch or one that makes poor contact, current that should be utilized in the starting motor is wasted in overcoming the resistance of the switch.
- Q. Why is it inadvisable to insert an extra switch in the starting circuit, as is done in some cases by owners to insure against theft?
- A. Because of the drop in voltage. The loss in switches as designed for lighting circuits is about 1 per cent, or a little over 1 volt. If the same switch is used on the low voltage of the starter system, the loss is then equivalent to about 10 per cent.

## LIGHTING AND INDICATORS Lamps

- Q. How many types of bulbs are there in general use on automobiles?
- A. Four: miniature and candelabra screw base, and singleand double-contact bayonet-lock base, both of the latter being of the candelabra size.

- Q. Are these the only voltages in which the bulbs are made?
- A. No. They are the types that are being standardize to reduce the stock of replacements that it is necessary for a garage to carry. It has been customary for the lamp manufacturer supply bulbs made exactly for any voltage that the maker of the electric system ordered. Taking into consideration only the standassizes now listed for use on 3-, 6-, and 9-cell systems, and the differe bases regularly used, there are about twenty-four different bull that should be stocked by a garage. In addition, about forty oth sizes are in general use, and if individual voltages had to be supplied, considering the different standard bases, a stock of ov two-hundred different bulb sizes would be required.
- Q. Why is the voltage of a bulb expressed as "6-8", "12-16", etc.?
- A. Owing to the rise and fall of the battery voltage according to its state of charge, this variation must be provided for, or the lamps would be burned out when the battery was fully charge Headlight bulbs for 3-cell systems are made for 6½ volts, while the side, rear, and speedometer lights are made for 6½ volts, owing the lesser voltage drop in their circuits, but they will all opera satisfactorily on a potential that does not exceed 8 volts or does not drop below 6 volts.
  - Q. When all the lamps burn dimly, what is the cause?
- A. The battery is nearly exhausted, in which case its voltarial will be only 5.2 to 5.5 volts for a 3-cell system. The car should I run with as few lights as necessary to permit the generator to character battery quickly.
  - Q. What is the cause of one light failing?
- A. Bulb burned out or its fuse blown; examine the fuse beforeplacing the bulb and if blown, examine the wiring before puttir in a new bulb. Poor contact; see that the lamp is put in proper and turned to lock it in place. A double-contact bulb may hav been put in single-contact socket, or vice versa.
  - Q. Why will one lamp burn much brighter than the other?
- A. A replacement may have been made with a bulb of higher voltage; a 12-volt bulb will give only a dull red glow on a 3-ce system. Where the difference is not so marked as this, but sti very perceptible, it may be due to the difference in the age of the

- lamps. As a bulb grows old in service, its filament resistance increases, so that it does not take so much current and will not burn as brightly as when new.
- Q. Will the failure of a bulb cause its fuse to blow though there is no fault in its circuit?
- A. This sometimes happens owing to the breaking down of the filament, causing a short-circuit when the lamp fails.
- Q. Can the proper voltage bulbs needed for any system always be told simply by taking the total voltage of the battery, i.e., the number of cells times 2?
- A. No. Always examine the burned out bulb and replace with one of the same kind. Many 6-cell systems use 6-volt lamps and are known as 12—6-volt systems. The battery is divided into two groups in series parallel for lighting and sometimes for charging, all the cells being in series for starting. Other arbitrary voltages are also adopted; for example, 14-volt bulbs are used on 12-cell systems, the battery being divided in the same manner, so that this would be a 24—12-volt system. The only safe way to order replacements is to give the voltage on the printed label on the old bulb and state the make of the system on which it is to be used.
- Q. What type of bulb is used where the current is taken from the magneto, as on the Ford?
- A. As supplied by the maker, only the headlights are wired, and they are in series, and in recent models a 9-volt bulb is used, but the above instructions for replacements will apply here also

focal length of the reflector is made greater than this to permit of adjustment. The center of the filament should be back of the focus of the reflector to spread the beam of light. In this position a greater number of the light rays are utilized and redirected by the reflector, producing a higher beam candlepower. If the center of the filament is forward of the focus, the lower part of the reflector will produce the most glare and throw it into the eyes of pedestrian and approaching drivers.

## Q. How can the headlights be focused?

A. Place the car in position where light can be directed agains a wall about 100 feet distant. Adjust the bulbs backward or forward until the spotlight on the wall is most brilliant and free from black rings and streaks. When this position is found, lock the bulb securely in place. Focus each headlight separately. See that the lamp brackets are set so that the light is being projected directly ahead

# Q. How can metal headlight reflectors be cleaned when discolored?

A. Wash by directing a gentle stream of cold water agains the surfaces and allow to dry without touching them. The reflector should never be rubbed with cloth or paper as it will scratch the highly polished surfaces. If they become very dull, it will be necessary to have them replated.

# Q. What is the meaning of the identification marks usually placed on bulbs, in addition to the voltage, such as "G-6"?

A. This refers to the size and shape of the bulb. The diamete of the glass bulb is expressed in eighths of an inch and its shape by a prefixed G for round (globular), T for tubular, S for straight side, etc. Thus, G-6 is a round bulb  $\frac{6}{5}$  inch or  $\frac{3}{4}$  inch in diameter

#### Instruments

# Q. What instruments ordinarily are employed in connection with electric systems on the automobile?

A. Either a double-reading ammeter, a volt-ammeter, or ar indicator, the first named being employed generally. The ammeter shows whether the battery is charging or discharging or whether no current is passing; the indicator reads either Off or On; while the voltammeter gives the voltage, usually upon pressing a button to put it into operation, in addition to the readings already mentioned.

- Q. On what circuits are the indicating instruments placed?
- A. The charging circuit from the generator to the battery, and the lamp and ignition circuits.
  - Q. Why is an ammeter not used for the starting-motor circuit?
- A. The current is so heavy and varies so greatly with the conditions that an ammeter designed to give an accurate reading of it would not be sensitive enough to indicate the smaller amounts of current used by the lamps, or produced by the generator for charging. Furthermore, the starting motor is intended only to be used for very short periods, while the other circuits are in constant use.
  - Q. Do the small ammeters employed fail very often?
- A. Considering the unusually severe treatment to which they are subjected by the vibration and jolting of the car, their failure is comparatively rare, but as the conditions are so severe for a sensitive indicating instrument, too much dependence should not be placed on the ammeter reading when making tests.
  - O. What are the usual causes of failure?
- A. Failure to indicate—the generator, wiring, and other parts of the circuit being in good operative condition—may be caused by the pointer becoming bent, so as to bind it; the pointer may have been shaken off its base altogether by the jolting, or one of its connections may have sprung loose from the same cause.
  - Q. How can the ammeter reading be checked?
- A. By inserting the portable testing voltammeter in circuit

resistance coil permits only a small amount of current to pass. A ammeter reading from a storage battery gives no indication whatever of its condition, whereas the voltage affords a close check on the state of charge, varying from 1.75 for a completely discharged ce to 2.55 volts for a fully charged one, the readings always bein taken when the battery is either charging or discharging. The voltage on discharge will not be as high as on charge, the condition otherwise being the same.

- Q. Why are indicators employed on some systems instea of ammeters?
- A. As the indicator is not designed to give a quantitativ reading, it need not be so sensitive as an ammeter and according can be made more durable.
- Q. What are the most frequent causes of failure of an ind cator?
- A. Usually of a mechanical nature caused by the jolting, suc as the target being shaken off its bearings, broken wire, etc.
- Q. When the engine is running slowly, and the ammeter or the indicator flutters constantly, going from "On" to "Off" at short intervals, in the case of the indicator, or from a small charging current to zero, in the case of the ammeter, what does this signify?
- A. That the setting of the battery cut-out is very sensitive and that the engine is then running at or about the speed that the instrument should cut-in. Since the speed of an engine varies considerably when running slowly, picking up momentarily and the falling off for a longer period, there is a corresponding variation in the potential, causing the cut-out to operate intermittently. This is condition that seldom occurs and results in no harm when it does.
- Q. When the ammeter or indicator flutters in the same mannewith the engine running at medium or at high speed, what does indicate?
- A. That there is a loose connection between the generator an the cut-out, or an intermittent short-circuit or ground caused by chafed wire alternately making contact with some metal part owin to the vibration. It is much more likely to be simply a loose connection and will be found most often on the back of the cut-out itsel. This should be remedied at once. If neglected, it will cause abnorms wear of the platinum points in the cut-out.

- Q. When the ammeter does not indicate "Charge" though the engine is speeded up, but does register a discharge when the lights are turned on and the engine is idle, what is the nature of the trouble?
- A. Either the generator is not producing current or the regulator (where an external type is employed) is not working properly. The generator brushes may not be making proper contact with the commutator, or there may be a loose, corroded, or broken connection in the generator cut-out battery circuit. Where a belt drives the generator, it may be too loose to run the machine at its proper speed.
- Q. When the ammeter gives no charging indication though the lamps are off and the engine is speeded up, and gives no discharging indication though the engine is idle and lamps are switched on, what is likely to be the cause?
- A. There is an open or a loose connection in the battery circuit or in the battery itself. The ammeter may be at fault. See that its indicating pointer has not become jammed nor dropped off its bearings.
- Q. In case the ammeter indicates "Discharge" though the engine be idle and all lights turned off, what is the trouble?
- A. There is a short-circuit or a ground somewhere in the lighting circuits or between the battery and the ammeter, as the discharge reading in such circumstances indicates a leakage of current; or the cut-out has failed to operate and still has the battery in circuit with the generator, though the engine is stopped. The ammeter pointer may be bent.



- A. There may be a short-circuited cell in the battery, or a short in the charging circuit, or the regulator (external type) may not be working properly.
- Q. What will cause the discharge reading of the ammeter to become abnormally high?
- A. The lamp load may be excessive, as where higher candle-power bulbs are used, or more lights than originally intended are put in the circuit. There may be leakage in some part of the lighting Circuit, or the cutout contacts may be stuck together, permitting a discharge through it or through the generator.

#### **ELECTRIC GEAR-SHIFT**

- Q. What is the operating principle upon which the electric gearshifting mechanism is based?
- A. That of the solenoid and its attraction for its core when a current is passed through its winding.
- Q. What is the source of current supply for the electric gearshift?
- A. The storage battery of the lighting system. The operation of gear-shifting is carried out so quickly that only a nominal additional demand is made on the battery.
  - Q. How is the electric gear-shift controlled?
- A. By a series of buttons corresponding to the various speeds and located on the steering wheel, and by a master switch.
  - Q. What is the object of the buttons, and what are they termed?
- A. To partly close the circuit to the particular solenoid of the speed desired. They are termed "selector switches" since they permit selecting in advance the speed desired.
  - Q. Why is a master switch employed, and why is it so called?
- A. To avoid the complication which would otherwise result from the necessity of providing two switches for each change of speed, i.e., a selector switch and an operating switch. It is termed a master switch because it controls the current supply to all of the circuits.
- Q. Why is a neutral button provided in addition to the buttons for the various speeds on the selector switch?
- A. To return any of the selector buttons to neutral without the necessity of going through that speed in case it is not desired to engage the speed in question after the button has been pushed. Also

to open any of the selector switches that may be closed when it is desired to stop.

- Q. What is the neutralizing device?
- A. It is a mechanism incorporated with the shifting mechanism to open the master switch automatically after the gears have been engaged.
  - Q. Why is the neutralizing device necessary?
- A. If it were not provided, the master switch would remain closed, causing a constant drain on the battery and rendering the mechanism inoperative after one shift had been made.
- Q. How many solenoids are provided in the standard three-speed and reverse gear box?
  - A. One for every movement necessary.
- Q. Is the current sent through a solenoid in one direction to pull the shifting bar into it and then in the opposite direction to move the bar the other way?
- A. No, the current is not reversed through the same solenoid. After the left-hand solenoid, operating the first-speed gear, for example, has pulled the shifter bar to the left, a second solenoid, on the opposite end of the same bar, is energized to pull it back to the right, to shift to second or intermediate. The current is sent through a different solenoid by means of the selector switches for each shift desired.
- Q. When the electric gear-shift failed to operate, where would

broken under the insulation, but, until experience has been gained in its use, it will be nothing unusual to find that the points have been touched to connecting pieces of metal which have no relation to the circuit. As such metal will complete the circuit through the lamp, the latter will light, but without indicating anything of value to the trouble hunter. Always test the lamp itself before proceeding. It may have become partly unscrewed in its socket or its filament may have been broken.

## BATTERY Electrolyte

- Q. Why is it necessary to refill the battery jars at regula intervals?
- A. Because the heat generated in the cells evaporates the water from the electrolyte, and, if the latter is permitted to fall below the tops of the plates, they will dry out where they are exposed, and the heat of charging will then cause them to disinte grate, ruining the battery.
- Q. Why should this be done at intervals of not less that two weeks?
- A. Because the limited amount of electrolyte permitted by the restricted size of the cells over the plates—usually one-hal inch—will be evaporated in that period by a battery that is in more or less constant use.
- Q. Why should water alone and never acid or electrolyte be used to make up this loss?
- A. Only the water evaporates, so that if either acid or fresh electrolyte is added, it will disturb the specific gravity of the solution in the cells and totally alter their condition.
- Q. What is the reason that battery manufacturers insist that only distilled water or its nearest equivalent, rain water or melted artificial ice, be used for this purpose?
- A. Because ordinary water contains impurities that are apt to harm the plates, such as iron salts, or alkaline salts that will affect both the plates and the electrolyte.
- Q. What should be done to a battery that has had its efficiency impaired by being filled with impure water?
- A. The cells should be taken apart, the separators discarded, the plates thoroughly washed for hours in clean running water

without exposing them to the air where they would dry, the jars washed out, the plates reassembled with new separators, the jars filled with fresh electrolyte of the proper specific gravity, and the battery put on a long slow charge from an outside charging source, i.e., not on the car itself. Unless there are proper facilities for carrying this out, it will be preferable to ship the battery back to the maker so that it can be given proper treatment, particularly as it is necessary to reseal the cells.

## Q. How is electrolyte prepared?

A. By adding pure sulphuric acid a very little at a time to distilled water until the proper specific gravity is reached, and then permitting the solution to cool before using. The mixture must always be made in a porcelain, hard rubber, or glass jar; never in a metal vessel. Commercial sulphuric acid or vitriol should not be employed, as it is far from pure. Never add water to acid. When the two are brought together, their chemical combination evolves a great amount of heat, and the acid will be violently spattered about.

## Q. How often should distilled or rain water be added to the cells?

A. This will vary not alone with different systems but with different cars equipped with the same system, owing to the difference in conditions of operation. The only way to determine this definitely is to inspect the cells at short intervals and note how long they will

may take the form of a small-resistance unit consisting of Germa silver or other high-resistance wire wound on a porcelain tul and mounted on the forward side of the dash. A single-pole kni switch should be placed in the circuit with the resistance so the the latter can be cut in or out of the generator circuit as circum stances may require.

- Q. With conditions as in the preceding question, how can the amount of resistance to be inserted in the circuit be figured?
- A. By the use of Ohm's law. In this case, it would be  $R = \frac{1}{2}$ or resistance equals voltage divided by current. How much resis ance to use can only be answered by the conditions of operation Where a car is used steadily during the day and very seldom at night it may be necessary to reduce the charge by two-thirds. In the cas of a 6-volt system normally charging at 12 amperes, the generate delivers current at 7 to 7½ volts in order to overcome the voltag of the battery when fully charged. Selecting 7 volts, we see that the resistance in circuit when the current is 12 amperes is  $7 \div 12$ , or . ohm approximately. Now when the charging current is 4 ampere we must have 7 ÷ 4, or 1.75 ohms in circuit; that is, to reduce th current from 12 to 4 amperes, a resistance of 1.75-.6, or 1.15 ohm must be inserted. The amount of resistance wire necessary to giv this resistance or any other resistance necessary may be found i tables of wire sizes and resistances of special wire employed for thi purpose. The wire is bare and must be wound on the tube so tha adjacent coils do not touch. An extreme instance is cited here. I may be necessary in many cases to reduce the charging rate by very much smaller fraction. Ordinarily the charging rate should not be altered.
- Q. When the battery is constantly gassing, or "boiling" as the car owner usually puts it, what is the trouble?
- A. It is being constantly overcharged. This will greatly reduce the life of the battery, and the charging rate should be reduced, a mentioned in the preceding answer. It is essential that the batter, be kept fully charged; but if it is continually overcharged, this will keep the cells at an abnormal temperature which is injurious to the plates. The battery treatment will vary with the season, for the demand on it is much heavier during cold weather than in summer

### **Hydrometer Tests**

- Q. Why should the battery be tested with the hydrometer at regular intervals of a week or so?
  - A. Because the specific gravity of the electrolyte is the most certain indication of the battery's condition.
  - Q. What should the hydrometer read when the battery is fully charged?
    - . A. 1.280 to 1.300.
  - Q. What point is it dangerous to permit the specific gravity of the electrolyte to fall below, and why?
  - A. 1.250; because below this point, the acid begins to attack the plates and the battery plates sulphate. The lower the specific gravity, the faster sulphating takes place.
  - Q. What should be done when the hydrometer reading is 1.250 or lower?
  - A. The battery should be put on charge immediately, either by running the engine or by charging from an outside source of current until the gravity reading becomes normal.
  - Q. If the hydrometer reading of one cell is lower than that of the others, what should be done?
  - A. Inspect the cell to see if the jar is leaking; note whether electrolyte is over the plates to the depth of ½ inch and whether the electrolyte is dirty. If these causes are not apparent, the cell will have to be opened and inspected for short-circuits from an accu-



- Q. Why should the voltage readings not be taken while the battery is charging?
- A. Because the voltage of the charging current (always in excess of six volts) will cause the voltage of a battery in good condition to rise to normal or above the moment it is placed on charge, such readings are not a good indication of the battery's condition.
  - O. What should the voltage of the cells be?
- A. In any battery in good condition, the voltage of each cell a the battery's normal low discharge rate (5 to 10 amperes, as in carry ing the lamp load) will remain between 2.1 and 1.9 volts until it begin to approach the discharged condition. A voltage of less than 1.9 volt per cell indicates either that the battery is nearly discharged or that it is in bad condition. The same state is also indicated when the voltage drops rapidly after the load has been on a few minutes.

### Joint Hydrometer-Voltmeter Test

- Q. What should the hydrometer and voltmeter readings be for a fully charged battery in good condition?
  - A. Hydrometer 1.275 to 1.300; voltage 2 to 2.2 volts per cell
- Q. What does a hydrometer reading of 1.200 or less with a voltage of 1.9 volts or less per cell indicate?
- A. This shows that excess acid has been added to the electrolyte. Under these conditions, the lights will burn dimly even though the hydrometer test alone would appear to show that the battery is more than half charged.
  - Q. What does a hydrometer reading in excess of 1.300 indicate:
- A. It indicates that an excessive amount of acid has been added to the electrolyte, regardless of whether the voltage reading is high, low, or normal.
- Q. Where a low voltage reading is found, how can it be determined whether the battery is in bad condition or merely discharged:
- A. Stop the discharge by switching off the load (lamps) and put the battery on charge, cranking the engine by hand. After a few minutes of charging, note whether the voltage of each cell promptly rises to 2 volts or more. Any cells that do not are probably short-circuited or otherwise in bad condition.
- Q. How can a rough test of the condition of the battery be made without the use of any instruments?

- A. On systems fitted with a battery cut-out in the generator battery circuit, remove the cover of the cut-out (the generator being stationary) and momentarily close the cut-out points with the finger. The discharge shown by the ammeter the monent the points are closed should be anywhere from 10 to 20 amperes, differing, of course, with different systems. In any case, it should be equal to or greater than the maximum normal output of the generator, provided the battery is at least three-quarters charged.
- Q. What effect will allowing the electrolyte to fall too low in the cells have, apart from the damage that it will cause to the plates?
- A. It will tend to increase the voltage if the battery is otherwise in good condition, and this may be carried to a point where it will burn out the lamps.
  - Q. What is meant by "floating the battery on the line"?
- A. This describes the relation of the battery to the generator and lighting circuits in systems where the current for lighting is taken directly from the generator when running, any excess over the requirements of the lamps being absorbed by the battery. The moment the generator speed falls below the point where it supplies sufficient current to supply all that is needed for the lamps, the battery automatically supplies the balance. When the generator is idle, the battery, of course, supplies the current for lighting as well as for starting.

#### Gassing

Why should the cell tops be wiped dry from time to time

## Q. What is the cause of gassing?

A. When a battery is charged, the water of the electroly is decomposed by the current into gases. During the early par of the charge these gases unite with the active material of the plate but as the charge proceeds, more gas is evolved than the plate can take care of and it bubbles up through the electrolyte. The is known as the gassing point, and the temperature of the cell als begins to rise at that point.

## Q. Is gassing harmful to the battery?

A. The greatest wear on the positive plates takes place durin the gassing period, and, if carried too far, they may be injured b reaching a dangerous temperature (105° F., or over) which will ten to loosen the active material.

## O. How can gassing be checked?

A. By cutting down the charge. In some systems this ca be effected by the insertion of extra resistance provided for the purpose. Where this cannot be done and it is necessary to kee the car running, turn on all the lamps or start the engine once a twice to reduce the charge of the battery. As the lamps usuall consume 80 to 95 per cent of the generator output, they should be sufficient to prevent a further overcharge.

# Q. Can the generator be disconnected from the battery 1 prevent overcharge?

A. Not unless it is short-circuited, as directed in the instructions covering different systems. Otherwise, it will blow its fiel fuse or, where one is not provided, burn out its windings, excer in cases where special provision is made to guard against this.

#### Sulphating

## Q. Why must a battery never be allowed to stand in a fully discharged state?

A. Because the acid of the electrolyte then attacks the plate and converts the lead into white lead sulphate which is deposite on them in the form of a hard coating that is impenetrable to th electrolyte, so that the plates are no longer active. The batter then is said to be *sulphated*.

Q. Can a sulphated battery be put in good condition, and whatreatment must be given it to do so?

A. If the sulphating has not gone too far, the battery may be brought back to approximately normal condition by a long heavy charge at a higher voltage than ordinary. Where the battery has become badly sulphated, it is preferable to remove it from the car and charge from an outside source of current, as it may require several days to complete the process. (Note instructions regarding the running of the generator when disconnected from the battery, as otherwise it may be damaged.) If avoidable, the car should not run with the battery removed. If the battery has not stood discharged for any length of time, the charge may be given on the car by running steadily for 8 to 10 hours with all lights off. No lamps must be turned on, as the increased voltage is liable to burn them out.

#### Voltage Tests


- Q. What is the purpose of the voltmeter in connection with the battery?
- A. It is chiefly useful for showing whether a cell is short-circuited or is otherwise in bad condition.
- Q. Can the voltmeter alone be relied upon to show the condition of the cells?
- A. No; like the hydrometer, its indications are not always conclusive, and it must be used in conjunction with the hydrometer to insure accuracy.
- Q. What type of voltmeter should be employed for making these tests?



- Q. What precautions should be taken before using the volumeter?
- A. Always see that the place on the battery connector select for the contact is bright and clean and that the contact itself is fin otherwise the reading will be misleading since the increased resistan of a poor contact will cut down the voltage.
  - Q. How is the instrument connected to the battery?
- A. The positive terminal of the voltmeter must be brought contact with the positive terminal of the battery and the negatiterminal of the voltmeter in contact with the negative terminal the battery.
- Q. In case the markings on the battery are indistinct, how cathe polarity be determined?
- A. Connect the voltmeter across any one cell. Should the pointer not give any voltage reading, butting against the stop at the left instead, the connections are wrong and should be reversed; if the instrument shows a reading for one cell, the positive terminal of the voltmeter is in contact with the positive terminal of the batter. This test can be made without any risk of short-circuiting the ce since the voltmeter is wound to a high resistance and will pass we little current. Such is not the case with the meter, which shou never be used for this purpose.
- Q. When the battery is standing idle, what is the cell volta; and why is this not a good test?
- A. Approximately two volts, regardless of whether the batter is fully charged or not. Voltage readings taken when the battery is copen circuit, i.e., neither charging nor discharging, are only of value when the cell is out of order.
- Q. If the battery is in good condition and has sufficient charg what should the voltmeter reading show?
- A. Using the lamps for a load, the voltage reading after the los has been on for five minutes or longer should be but slightly low (about .1 volt) than if the battery were on open circuit.
- Q. When one or more cells are discharged, what will the reading show?
- A. The voltage of these cells will drop rapidly when the load first put on and sometimes even show reverse readings, as when a c is out of order.

- Q. What will the voltmeter indicate when the battery is nearly discharged?
- A. The voltage of each cell will be considerably lower than if on open circuit after the load has been on for five minutes or more.
- Q. How can the difference be distinguished between cells that are merely discharged and those that are in bad condition?
- A. Put the battery on charge, cranking the engine by hand to start, and test again with the voltmeter; if the voltage does not rise to approximately 2 volts per cell within a short time, it is evidence that there is internal trouble which can be remedied only by dismantling the cell.
  - Q. What effect has the temperature on voltage readings?
- A. The voltage of a cold battery rises slightly above normal on charge and falls below normal on discharge. This last is one of the chief reasons for its decreased efficiency in cold weather.
- . Q. What is the normal temperature of the battery and to what does this refer?
- A. The normal temperature of a battery is considered at 70° F., but this refers to the temperature of the electrolyte in the battery as shown by a battery thermometer and not to the temperature of the surrounding air. If the battery has been charging at a high rate for some time, it may be normal even though the weather be close to zero at the time.

#### Sediment

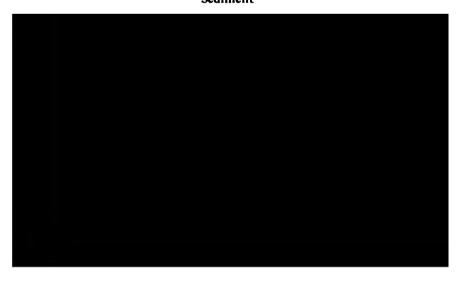

starting condition, or if it has been subjected to short-circuits by grounding or by dropping tools on its terminals, the plates will disintegrate much quicker than where proper treatment has been given it. With the old-style jar, only an inch or so is allowed to hold this accumulation of sediment below the plates, while in later types fully 3 inches or more are allowed in the depth of the cell for this purpose. A battery with jars of the latter type that has been cared for properly should not require washing out under two years. The procedure is the same as that given for removing the effects of impure water. The plates must never be allowed to dry.

#### Washing the Battery

- Q. What is meant by washing the battery, and why is it necessary?
- A. Washing a battery involves cutting the cells apart, washing the elements and the jars, and reassembling with new separators and new electrolyte. It is necessary to prevent the accumulation of sediment, consisting of active material shaken from the plates, to a point where it will touch them and thus cause a short-circuit.
  - Q. How often is it necessary to wash a battery?
- A. This will depend on the type of cell in the battery and the age of the latter. If the battery has the modern-style jar with extra deep mud space, it probably will not be necessary to wash it until it has seen two to three seasons' use. With the older form of cell in which the space allowed for sediment is much less, washing doubtless will be necessary at least once a season. As the battery ages, it will be necessary to wash it oftener.
- Q. What other causes besides the type of jar and the age of the battery influence the frequency with which it is necessary to wash the battery?
- A. The treatment the battery has received. If it has been abused by overcharging and permitting the cells to get too hot, the active material will be forced out of the grids much sooner.
  - Q. How can the necessity for washing be determined?
- A. The presence of one or more short-circuited cells in a battery that has not been washed for some time will indicate the necessity for it. Each cell should be tested separately with the low-reading voltmeter; a short-circuited cell will either give no

voltage reading or one much below that of the others. Cut such a cell out and open it; if the short-circuit has been caused by an accumulation of sediment, the others most likely are approaching the same condition.

### Q. How is a battery washed?

A. By cutting the cells apart, unsealing them, and lifting out the elements which should be immersed immediately in a wooden tub of clean pure water. The separators then are lifted out and the positive and negative groups of plates separated, but they must be marked so that the same groups may go back in the right cells. Before disposing of the old electrolyte, its specific gravity should be noted, as new electrolyte of the same density must be used. The plates should be washed in copious running water for several hours, but their surfaces must never be exposed to the air. Reassemble with new separators, fill the jars with fresh electrolyte of the same specific gravity as that discarded, and keep the elements under water until ready to place in the jars, which then should be sealed and the lead connectors burned together again.

Give a long slow charge after reassembling. The battery will not regain its normal capacity until it has been charged and discharged several times.

#### Connectors

Q. Why should lead connectors be employed, and why is it necessary to burn them together?



wire. It will either be burned up in a flash or it will cut down t amount of current from the battery, thus causing unsatisfacts operation.

### **Buckled Plates**

Q. What is the cause of badly disintegrated or buckled plate

A. Sudden discharge due to a short-circuit or to constrabuse of the starting motor on an insufficiently charged battery.

Q. Is there any remedy for such a condition?

A. If the plates are not badly buckled and have not lost me of their active material, the cells may be put in service again washing and reassembling as described, but if there is any considerable loss of active material, new plates will be necessary.

### Low Battery

Q. What are the indications of a low battery?

A. The starting motor fails to turn the engine over, or does very slowly, or only a part of a revolution. The lights burn very dim The hydrometer shows a specific-gravity reading of 1.250 or le Voltmeter test shows less than 5 volts for a 3-cell battery (for grea number of cells, in proportion), or 1.75 volts or less for each cell.

Q. What are the causes of a low battery?

A. The electrolyte not covering the plates, or being t weak or dirty. A short-circuit in the battery due to the accumulati of sediment reaching the bottom of the plates. An excessive lar load, all lights being burned constantly with but little daylig running the car. Generator not charging properly.

## Specific Gravity; Voltage

- Q. What are the specific gravity and voltage of fully discharg and fully charged cells?
- A. Total discharge: 1.140 to 1.170 on the hydrometer; and 1. to 1.85 volts on the voltmeter. Fully charged: 1.276 to 1.300 speci gravity; 2.35 to 2.55 volts.
  - Q. Are these readings always constant for the same condition
- A. No. The charging voltage readings will vary with t temperature and the age of the cell; the higher the temperature and the older the cell the lower the voltage will be. Hydromes

readings also depend on the temperature to some extent. For every ten degrees Fahrenheit rise in temperature, the specific gravity reading will drop .003 or three points, and vice versa.

- Q. Under what conditions should voltage tests be made?
- A. Only when the battery is either charging or discharging. Readings taken when the battery is idle are of no value.
  - O. Under what conditions should hydrometer tests be made?
- A. The electrolyte must be half an inch over the plates and it must have been thoroughly mixed by being subjected to a charge. Hydrometer readings taken just after adding water to the cells are not dependable.
  - Q. When should acid be added to the electrolyte?
- A. As the acid in a battery cannot evaporate, the electrolyte should need no addition of acid during the entire life of the battery under normal conditions. Therefore, if no acid has leaked or splashed out and the specific gravity is low, the acid must be in the plates in the form of sulphate and the proper specific gravity must be restored by giving the battery an overcharge at a low charging rate.
- Q. What does a specific gravity in some cells lower than in others indicate?
- A. Abnormal conditions, such as a leaky jar, loss of acid through slopping, impurities in the electrolyte, or a short-circuit.
  - O. How can it be remedied?
- A. Correct the abnormal conditions; and then overcharge the cells at a low rate for a long period, or until the specific gravity



charging, it may be necessary to continue the overcharge for 10 15 hours longer. Should the specific gravity exceed 1.300 at t end of the charge, draw off a small amount of electrolyte with t syringe from each cell and replace with distilled water. If bel 1.270, proceed as mentioned above for addition of acid.

### **Charging from Outside Source**

- Q. What is meant by charging from an outside source?
- A. A source of direct current other than the generator the car.
- Q. Why is it necessary to charge the battery from an outsi source?
- A. When the battery has become sulphated, has been standifule for any length of time, or has been run down from any otl cause so that it is out of condition, a long charge at a uniform rais necessary, and it would seldom be convenient to run the care 8 or 10 hours steadily simply to charge the battery; frequently longer charging period than this is necessary.
  - Q. How is charging from an outside source effected?
- A. This will depend upon the equipment at hand and the nation of the supply, i.e., whether alternating or direct current. If the current is alternating, a means of converting it to direct current necessary, such as a motor-generator, a mercury-are rectifier, cher callor vibrating type of rectifier. These are mentioned about in the order of the investment involved. In addition, a charging panel needed to complete the equipment, this panel being fitted with switches, voltmeter, and ammeter, and a variable resistance for regulating the charge. Where direct-current service is obtainable at 1 or 220 volts, the rectifier is unnecessary.
- Q. How can a bactery be charged from direct-current serving mains without a special charging panel?
- A. By inserting a double-pole single-throw switch and 10- or ampere fuses on taps from the mains and ordinary incandesce lamps in series with the battery to reduce the voltage, Fig. 40
  - Q. How many lamps will be needed?
- A. This will depend upon their character and size, as we as upon the amount of charging current necessary. For a 10-ampecharge for a 6-volt storage battery, seven 110-volt 100-watt (

e.p.) carbon-filament lamps, or their equivalent, will be needed; i.e., fourteen 110-volt 50-watt (16 c.p.) carbon-filament lamps; sighteen 110-volt 40-watt tungsten lamps, or twenty-eight 110-volt


For a

of lamps will have to be decreased in proportion in order not to cut the voltage of the supply current below that of the battery. For 220-volt d.c. supply mains, if a three-wire system is employed, the taps should be taken from the center wire and one outside wire; this will give 110 volts. If the service is 220-volt two-wire, more lamps will be needed to reduce the voltage, which should exceed that of the battery by only 1½ to 2 volts except where a high voltage charge to overcome sulphating is being given, in which case it may be slightly higher.

25-watt tungsten lamps.

12-volt or 24-volt battery the number

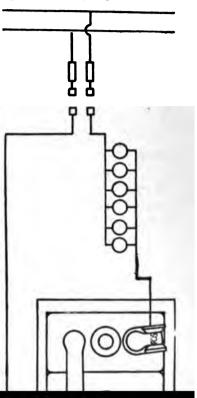Q. Where no outside source of current is available, or where no rectifier is at hand to convert alternating current, how can the battery be given the long charge necessary?



make certain that the battery will be charged in the proper direction.

### Q. How can this be done?

A. If a suitable voltmeter is at hand, i.e., one of the proper voltage for the 110-volt current, connect it to the mains. If the needle does not move over the scale but shows a tendency to butt against the stop pin at the left, reverse the connections. The needle will then give a proper reading and the positive connection to the meter must be used for the positive side of the battery. Should no voltmeter of the right voltage be available, connect two short wires with bared ends to the fused end of the switch. Dip the bared ends of the wire in a glass of water, being careful to keep them at least an inch part. When the switch is closed, fine bubbles will be given off by the wire connected to the negative side. The battery terminals are stamped *Pos.* and *Neg.*, and the connections should be made accordingly.

#### Intermittent and Winter Use

### Q. What should be done with an idle battery?

A. If it is to be idle for any length of time, as where the car is to be stored, it should be given a long overcharge as described above before being put out of service. Fill the cells right to the top with distilled water to allow for evaporation and absorption of acid by the plates. Give the battery a freshening charge at a low rate once a month. Discharge the battery and re-charge before putting it into service again. If it has stood out of service for a long period, the battery will be found at a low efficiency point and will not reach its maximum capacity again until it has had several charges and discharges.

## Q. Does cold weather have any effect on the storage battery?

A. It causes a falling off in its efficiency. If not kept charged, the electrolyte will freeze under the following conditions: battery fully discharged, sp. gr. 1.120,20° Fahrenheit; battery three-quarters discharged, sp. gr. 1.160, temperature zero; half discharged, sp. gr. 1.210, 20 degrees below zero; one quarter discharged, sp. gr. 1.260, 60 degrees below zero. When storing away for the winter, the battery must either be kept charged or put where the temperature does not go lower than 20 degrees above zero.

### **Edison Battery**

- Q. Is it ever necessary to wash out an Edison battery?
- A. No. The cells are permanently sealed, as the active material cannot escape from its containers.
- Q. Do all of the foregoing instructions apply to the Edison as well as to the lead-plate battery?
- A. No. The Edison requires very little attention, practically the only care necessary being to keep the cars replenished with distilled water at intervals.

Charging rates for Edison cells are given in the article on Electric Automobiles. S.A.E.-standard instructions for lead-plate cells are also given in the same article.





## Index of Wiring Diagrams

Diagrams with Plate Numbers Are Blueprints Placed in Numerical Order throughout the Volume; Numbers Opposite Remaining Diagrams Refer to Bottom Folios in the Volumes Noted.

A		
Abbott-Detroit 1917—Remy System Abbott-Detroit 1916-17, Model 6-44—Remy System Ahrens-Fox Fire Engine—Delco System Allen 1916, Roadster, Model 37—Westinghouse System Ammeter, Method of Connecting to Shunt. Ammeter Principle Anderson 1920, Series 20—Remy System Apperson—Bijur System Apperson 1916-17-18—Remy Ignition System Apperson 1919-20, Anniversary Model—Bijur System Apperson, Model 8-18-A—Remy System Apperson, Model 8-18-A—Remy System Apperson, Models 6-16, 8-16, 6-17, 8-17—Remy Ignition and Bijur	. Plate . Plate . Page . Page . Plate . Page . Page . Plate	636 336 18 363 529
Starting and Lighting Systems.  Atlas Three-Quarter-Ton Truck—Remy System.  Atterbury 1920, U. S. A. Class B Military Truck—Delco System.  Atwater-Kent Ignition System—Hollier Eight.  Auburn 1916, Models 4-38, 6-38, 6-40—Remy System.  Auburn 1917, Model 6-39—Remy System.  Auburn, Models 4-40, 4-41, 6-45, 6-46—Remy System.  Auburn, Model 6-40—Delco Single-Unit System.  Auburn, Model 6-44—Delco System.  Austin Twelve—Delco System.  Auto-Lite Four-Pole Generator.  Automatic Electromagnetic Pinion Shift.	Plate Plate Page Page Plate Page Page Page Page Page	581 528 527 8 324 391 392 340
B	Page Page Page	35

2 INDEX

Cadillac 1914—Delco System	Page	408
Cadillac 1915—Delco System	Page	409
Cadillae 1919, Model 57 -Deleo System	Plate	15
Cadillae 1920, Model 59 - Delco System Plat	[68] [5	4, 20
Cadillac, Model 53—Delco System. Cadillac, Model 55—Delco System.	rage Dam	410
Continuent 1014 Model 7 Delec System	rage Dista	91
Cartegory 1015 Model 0 - Dolgo System	Plate	9-)
Cara 1015 Model 20 Westinghouse System	Plata	92
Case 1917, Model T-17—Auto-Lite System	Plate	- 21
Carterear 1914, Model 7—Delco System. Carterear 1915, Model 9—Delco System. Case 1915, Model 30—Westinghouse System. Case 1917, Model T-17—Auto-Lite System. Case 1920, Model V, Serial Nos. 34860-36860 and Serial No. 36961 and		
Up Deleo System	Plate	25
Case 1920 Enclosed Cars, Model V—Delco Ignition and Westinghouse		
Starting and Lighting Systems	Plate	26
Chalmers 1915, Model 29 - Westinghouse System	Plate	27
Chalmers 1916-17 Remy Ignition and Westinghouse Starting and		
Lighting Systems Chalmers 1917-18, Model 6-30 - Westinghouse System.	Page	531
Chalmers 1917-18, Model 6-30 - Westinghouse System.	Plate	28
Chalmers 1918 -Remy Ignition and Westinghouse Starting and Light-		
ing System. Chandler 1917, Light-Weight Six, Serial Nos. 35001-60000, Gray and	l'age	532
Chandler 1917, Light-Weight Six, Serial Nos. 35001-00000, Gray and	n	400
Davis System	rage	497
System System	2000	461
Chandler 1920, New Series Model—Westinghouse System	Pluta	100
Chevrolet 1917-18-19, Model D -Auto-Lite System	Plate	30
Chevrolet 1918, Models D-4 and D-5 -Remy System.	Plate	31
Chevrolet 1918, Models D-4 and D-5 -Remy System	Plate	32
Choyedat 1920 Model FRRemy Ignition and Auto-Lite Starting		
and Lighting Systems  Chevrolet, Model F. Auto-Lite System.  Chevrolet, Model 490—Auto-Lite Single-Wire System.  Chevrolet Royal Mail and Baby Grand Models—Auto-Lite Two-Wire	Plate	33
Chevrolet, Model F. Auto-Lite System I	Page	342
Chevrolet, Model 490 Auto-Lite Single-Wire System.	Page	339
Chevrolet Royal Mail and Baby Grand Models—Auto-Lite Two-Wire		
System	age	326
Cole 1915, Models 4-40, 4-50, and 0-607-Detco System	late	34
Cole 1913, Model 4-40 - Deleo System	Plate	35 36
Colo 1014 Savios 0 Siv—Dolgo System	Plate	37
Cole 1914, Series 9, Four and Six       I         Cole 1914, Series 9, Six—Delco System       I         Cole 1915, Model 4-40—Delco System       I         Cole 1915, Model 6-50—Delco System       I         Cole 1918, Model 8-70—Delco System       I         Cole 1918, Model 8-70—Delco System       I         Cole 1919, Model 8-70—Delco System       I	Plate	38
Cole 1915 Model 6-50Delco System	late	39
Cole 1918, Model 870Deleo System	Plate	40
Cole 1919, Model 870, Serial Nos. 34000-51001 - Deleo System I	Plate	41
Cole 1920, Model 870, Serial No. 57200 and Up- Deleo System I	Plate	42
Cole, Model 860 - Delco System	age	395
Cole 1919, Model 870, Serial Nos, 34000-51001 - Delco System.       I         Cole 1920, Model 870, Serial No. 57200 and Up - Delco System.       I         Cole, Model 860 - Delco System.       I         Cole, Model 870 - Delco System.       I         Columbia 1920, Series 7R - Auto-Lite System.       I         Commerce, Model E - Remy System.       I         Compound-Wound Generator.       I	age	396
Columbia 1920, Series 7R · Auto-Lite System	Plate	43
Commerce, Model E Remy System	?late	44
Compound-Wound Generator	age	44
Crow Elkhart 1910, Model 50 - Dyneto System.	1ate	40
Crow Elkhart 1940-14, Model C 25- Dyneto System	STATE	40
Commingual 1945-14, Model M. North East System	auce	41
Compound-Wound Generator Crow Elkhart 1916, Model 30 - Dyneto System Crow Elkhart 1916-17, Model C 23- Dyneto System Cunningham 1913-14, Model M - North East System Cunningham 1913, Model M, Hearses and Ambulances System Fig. 1917-1918 System Fig. 27-10-10-10-10-10-10-10-10-10-10-10-10-10-	Plate	48
Cunningham 1918-19, Model V-3 Delco System	late	49
System I Cunningham 1918-19, Model V-3 - Delco System I Cunningham, Model V - Westinghouse System I I	Page	63 i
The second secon		
D		
	Page Plate	

## INDEX

Davis, Models 6-H, 6-I, 6-K—Delco System	Page :
Davis, Model 6-J—Delco System	Page 4
Delco Cutout Relay	Page 4
Delco Cutout Relay Delco Generator, Adjusting Third Brush	Page 4
Delco Starting-Motor Circuit	Page 4
Delco Third-Brush Regulator.	Page :
Delco Two-Unit System	416
Dixie Magneto Pages 113	114 1
Dodge—North East System.	Page
Dodge 1915—North East System.	Plate
Dodge 1917—North East System  Dodge 1917—North East Single-Wire System	
Dorris 1920, Model 6-80—Westinghouse System	
Dort 1915, Models 4 and 5—Splitdorf-Apelco System	
Dort 1916-17—Connecticut Ignition and Westinghouse Starting	1 18.06
Dort 1910-17—Connecticut Igintion and Westinghouse Starting	5 Domo 6
Systems.  Dort 1916-17—Westinghouse System.	Doge (
Dort 1917, Model M-9T—Westinghouse System.	Disks
Dort 1917, Wodel M-91 — Westinghouse System.	Plate
Dry Cells in Series Multiple for Ignition Circuit  Dual Ignition System	rage
Dual Ignition System Page	8 118,
Duplex Ignition System	
Dyneto Generator Circuit	rage '
Dyneto Two-Wire System	rage
Dyneto Regulator Cut-out	8 402,
Dyneto Starting-Motor Circuit	. Page
E	
I.	
Elcar 1917-18-19, Models D. E. G 4 and D. E. G 6 Dyneto System.	Plata
Elgin 1920, Model K—Wagner System	Plato
Eigin 1917, Model 17—Wagner System.	Plata
Flore 1000.—Doloo System	Plata
Elcar 1920—Delco System Elgin 1917 Six—Wagner System	Dogo 4
Elgin 1918—Wagner System	Dage (
Elgin, Model 6-E-16—Delco System	Dage (
Eigin, Model 0-17-10-Deleo System	. Page 4
Elkhart, 1917 Model — Deleo System. Elkhart, Models G-H-K-D, Serial No. 15000 and Up — Deleo System.	rage
Eikhart, Models U-H-N-D, Serial No. 19000 and Up -Deico System.	. Plate
Empire 1915, Model 31Remy System	riate
Empire 1916, Model 33—Remy System.	
Enger 1916-17 Twelve—Remy System.	riate
	***
Essex 1919, Model A—Delco System. Essex 1920 Model A—Delco System.	Plate

4 INDEX

Grant 1919, Model G-Wagner System		
Gray and Davis Dynamo and Regulator	Page	486
Gray and Davis Lighting Switch. Gray and Davis Single-Wire System with Grounded Motor.	Page	470
Gray and Davis Single-Wire System with Grounded Motor	Page	470
Gray and Davis System—Peerless, Model 56	rage	471
Grounds, Locating	LIG 440	455
tifounds, Locating	120, 220,	200
Н		
HAL Twelve—Remy Ignition and Westinghouse Starting and Lig	ht-	
ing Systems.  II A L Twelve, Model 21—Remy Ignition and Westinghouse Start	Page	537
11 A L Twelve, Model 21—Remy Ignition and Westinghouse Start	ing Dam	201
and Lighting Systems Hall Double Headlight	Page	217
Harroun 1918, Model A-A-1—Remy System	Plate	911
Harroun, Model A-A-1 –Remy System	Page	538
Haynes 1915-16 Models 33 34 35 36 37—Remy System	Plate	60
Haynes 1915-16, Models 33, 34, 35, 36, 37—Remy System. Haynes 1916-17—Remy Ignition System. Haynes 1917, Light Six—Leece-Neville System.	Page	534
Haynes 1917, Light Six—Leece-Neville System	Page	505
Haynes 1920. Model 46. Twelve—Leece-Neville System	Plate	70
Haynes Light Six Leece-Neville System Haynes, Models 40, 40-R, 41 Delco Ignition System	Page	502
Haynes, Models 40, 40-R, 41 -Delco Ignition System	Page	423
Headlight, Double.	Page	317
Heinze-Springfield Current Regulator and Battery Cutout	Page	492
Heinze-Springfield System - Regal	Page	491
High-Tension Ignition System	Pages 85	, 92
Headlight, Double Heinze-Springfield Current Regulator and Battery Cutout Heinze-Springfield System —Regal High-Tension Ignition System High-Tension Magneto System Hollier Eight -Atwater-Kent Ignition and Splitdorf Starting a Lighting Systems	l'age	107
Holher Eight Atwater-Nent Ignition and Spittdori Starting 8	ind Da	PO1
Lighting Systems Holmes 1918-19-20 —Dyneto System Hudson 1914, Model 6-40 —Delco System	. Page	271 71
Holmes 1918-19-20 - Dyneto System	Dlata	71
Hudson 1914, Model 0-40 - Deleo System	Plate	72
Hudson 1914, Model 6-54 - Deleo System. Hudson 1915, Model 6-40 - Deleo System.	Plate	74
Hudson 1915, Model 6-54 · Delco System.	Plate	75
Hudson 1916, Model 6-40 — Delco System.	Plate	76
Hudson 1916, Model 6-40 —Delco System Hudson 1917, Super-SixDelco System Hudson 1919-20, Super-Six, Model O — Delco System	Page	424
Hudson 1919-20, Super-Six, Model O Delco System	Plate	77
Hupmobile Buur Starting Motor Installation	Page	358
Hupmobile Bijur System	Page	362
Hupmobile Westinghouse Single-Unit System	. Page	623
Hupmobile Bijur System HupmobileWestinghouse Single-Unit System Hupmobile 1916-17, Series N., Serial No. 60000 and Up.	Page	625
I		
Ignition Distributor, Relation to Engine Crankshaft	Page	142
Ignition Systems	. 85. 92.	107
Interstate 1916-17 Remy System	Page	541
Interstate, Model TF—Remy System	Plate Plate	78
Interstate Model TR —Remy System.	Plate	79
J		
Jackson 1915, Models 48, 6-40 - Delco System Jackson 1917, Wolverine, Model 349 - Auto-Lite System Jeffery 1916, Chesterfield Six - Bijur Two-Wire System Jeffery, Chesterfield Six - Bijur Two-Wire System Jeffery Six, Model 671 - Bijur System Jordan 1920, Model F - Delco System Jordan 1920, Model F - Series 2 - Delco System Jordan 1920, Model M - Delco System Jordan Sixty Bijur System	Plate	80
Jackson 1917, Wolverine, Model 349 - Auto-Lite System	Page	343
Jeffery 1916, Chesterfield Six Bijur Two-Wire System	Page	327
Jeffery, Chesterfield Six "-Bijur Two-Wire System"	Page	360
Jeffery Six, Model 671 - Bijur System	Page	368
Jordan 1920, Model F—Delco System	Plate	81
Jordan 1920, Model F, Series 2 Delco System	Plate	82
Jordan 1920, Model M. Delco System	Plate	83
Jordan Sixty—Bijur System	Page	357

## K

K-W Magneto Circuits       Page 112         King 1915, Models C and D—Ward Leonard System       Plate 84         King 1916, Models D and E—Ward Leonard System       Plate 85         King 1917-18, Models EE and F—Bijur System       Plate 86         King 1920, Model H—Westinghouse System       Plate 87         King Eight, Model EE—Bijur System       Page 356         Kissel 1915, Model 4-36—Westinghouse System       Plate 88         Kissel 1916, Models 4-32 and 4-36—Westinghouse System       Plate 90         Kissel 1916, One Hundred Point Six—Remy Ignition and Kissel Starting and Lighting Systems       Page 542         Kissel 1917, One Hundred Point Six—Westinghouse System       Plate 91         Kissel 1917 Twelve—Delco System       Page 427         Kissel 1918, One Hundred Point Six—Remy System       Plate 92         Kline 1916, Model 6-36—Westinghouse System       Plate 92         Kline 1916, Model 6-36—Westinghouse System       Plate 93         Krit 1915—North East System       Page 513
<del>-</del>
LaFayette 1920 Eight—Delco System
Starting and Lighting Systems
Lexington, Series 6-0-17 and 6-00-17—Connecticut Ignition and Westinghouse Starting and Lighting Systems
Liberty 1919-20, Models 10-B and 10-C-Wagner System. Plate 96
Lighting CircuitPage12Locomobile 1911-12—Bosch-Rushmore SystemPlate97
Locomobile 1913, Models 38 and 48—Bosch Dual Ignition System Plate 98
Locomobile 1915, Closed Car—Westinghouse System
Starting and Lighting Systems
М
McLaughlin—Remy System Page 551 Madison 1916-17-18—Remy System Plate 101

Moline Tractor, Model D-Remy System	Plate l
Mitchell 1916-17, Model C-42—Remy System	Plate 1
Mitchell 1916-17, Model C-42—Remy System Mitchell 1920, Model F-40—Remy System Mitchell-Splitdorf System—Mitchell 1917, Model D-40.	Plate 1
Mitchell-Splitdorf System-Mitchell 1917, Model D-40	Page 5
Moon 1914, Model 42—Delco System	Plates 113, 1
Moon 1914, Model 6-50—Delco System.	Plate l
Moon 1914, Model 42—Delco System  Moon 1914, Model 6-50—Delco System  Moon 1915, Model 4-38—Delco System	Plate 1
Moon 1916, Models 6-30 and 6-10—Deico System	Plate i
Moon, Model 6-43—Delco System	Page 4
Moon, Model 6-43—Delco System Moon, Model 6-66—Delco System	Page 4
	•
. <b>X</b>	
Nash 1919, Models 681 and 682—Delco System. Nash 1920, Models 681 and 682—Wagner System.	Plate 1
Nash 1920, Models 681 and 682—Wagner System	Plate 1
Nash, Model 681—Delco System.	Page 4
Nash Truck—Delco System	Plate 1
Nash Truck—Delco System. National 1917-18, Highway Six—Delco Ignition and Westingh Starting Systems.	ouse
Starting Systems	Page 6
National 1918, Model AF3—Delco System.	Plate 1
National 1918, Model AF3—Delco System. National 1920, Series BB, Serial No. 6000 and Up—Westingh System. National, Highway Twelve—Delco Ignition and Bijur Starting Lighting Systems	ouse
System	Plate 1
National, Highway Twelve-Delco Ignition and Bijur Starting	and
Lighting Systems	Page 3
National Six—Remy Double-Deck Unit	Page 5
National Twelve, Series A-K-Delco Ignition System.	Page 4
Non-Vibrator High-Tension System.	Page
Non-Vibrator High-Tension System.  North East Dynamotor.	Page 5
North East Model "B" Starter-Generator.	Page 5
North East Model "B" Starter-Generator. North East Model "D" Starter-Generator.	Page 5
0	
•	
Oakland 1914, Model 36—Delco System.	Plate 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oukland 1914, Model 36—Delco System.	Plata 1
Oakland 1914, Model 36—Delco System. Oakland 1914, Models 48-62—Delco System. Oakland 1914, Models 48-62-B—Delco System. Oakland 1915, Model 37—Delco System. Oakland 1915, Model 49—Delco System. Oakland 1917, Model 32-B—Delco System. Oakland 1917, Model 34-B—Remy System. Oakland 1920, Model 34-C—Delco System. Oakland, Model 32—Remy System. Oakland, Model 34—Delco System. Oldsmobile 1913, Model 53—Delco System. Oldsmobile 1914, Model 54—Delco System. Oldsmobile 1915, Model 55—Delco System. Oldsmobile 1915, Model 55—Delco System. Oldsmobile 1917, Model 37—Remy System. Oldsmobile 1917, Model 37—Remy System. Oldsmobile 1917, Model 45-Delco System. Oldsmobile 1917, Model 45-A—Delco System. Oldsmobile 1919, Model 45-A—Delco System. Oldsmobile 1919, Model 45-B—Delco System. Oldsmobile 1919, Model 45-B—Delco System. Oldsmobile 1920, Model 45-B—Delco System. Olympian 1917—Auto-Lite System. Overland —Auto-Lite System. Overland Light Four Model 90-4—Auto-Lite System.	Plate 1 lates 125, 1 Plate 1 Plate 1 Page 4 Page 551, 5 Page 4 Plate 1 Plate 3 Plate 1 Plate 3
Oukland 1914, Model 36—Delco System.	Plate 1 lates 125, 1 Plate 1 Plate 1 Page 4 Page 551, 5 Page 4 Plate 1 Plate 3 Plate 1 Plate 3
Oakland 1914, Model 36—Delco System. Oakland 1914, Models 48-62—Delco System. Oakland 1914, Models 48-62—Belco System. Oakland 1915, Model 37—Delco System. Oakland 1915, Model 37—Delco System. Oakland 1917, Model 32-B—Delco System. Oakland 1917, Model 32-B—Delco System. Oakland 1920, Model 34-B—Remy System. Oakland, Model 32—Remy System. Oakland, Model 32—Remy System. Oakland, Model 34—Delco System. Oldsmobile 1913, Model 53—Delco System. Oldsmobile 1914, Model 54—Delco System. Oldsmobile 1915, Model 54—Delco System. Oldsmobile 1915, Model 55—Delco System. Oldsmobile 1917, Model 37—Remy System. Oldsmobile 1917, Model 37—Remy System. Oldsmobile 1917, Model 45-Delco System. Oldsmobile 1919, Model 45-A—Delco System. Oldsmobile 1919, Model 45-A—Delco System. Oldsmobile 1919, Model 45-B—Delco System. Oldsmobile 1920, Model 45-B—Delco System.	Plate 1 lates 125, 1 Plate 1 Plate 1 Page 4 Page 551, 5 Page 4 Plate 1 Plate 3 Plate 1 Plate 3
Oakland 1914, Model 36—Delco System. Oakland 1914, Models 48-62—Delco System. Oakland 1914, Models 48-62-B—Delco System. Oakland 1915, Model 37—Delco System. Oakland 1915, Model 49—Delco System. Oakland 1917, Model 32-B—Delco System. Oakland 1917, Model 34-B—Remy System. Oakland 1920, Model 34-C—Delco System. Oakland, Model 32—Remy System. Oakland, Model 34—Delco System. Oldsmobile 1913, Model 53—Delco System. Oldsmobile 1914, Model 54—Delco System. Oldsmobile 1915, Model 55—Delco System. Oldsmobile 1915, Model 55—Delco System. Oldsmobile 1917, Model 37—Remy System. Oldsmobile 1917, Model 37—Remy System. Oldsmobile 1917, Model 45-Delco System. Oldsmobile 1917, Model 45-A—Delco System. Oldsmobile 1919, Model 45-A—Delco System. Oldsmobile 1919, Model 45-B—Delco System. Oldsmobile 1919, Model 45-B—Delco System. Oldsmobile 1920, Model 45-B—Delco System. Olympian 1917—Auto-Lite System. Overland —Auto-Lite System. Overland Light Four Model 90-4—Auto-Lite System.	Plate 1 lates 125, 1 Plate 1 Plate 1 Page 4 Page 551, 5 Page 4 Plate 1 Plate 3 Plate 1 Plate 3

Packard 1916 Six—Bijur Two-Unit Two-Wire System.	Page 278
Packard 1916 Twin Six—Bijur System Packard 1919-20, Models 3-25 and 3-35—Delco System	Plate 141
Packard 1919-20, Models 3-25 and 3-35—Delco System	Plate 142
Packard 1920, Models 3-25 and 3-35—Bijur System	Plate 143
Packard 1920, Models 3-25 and 3-35—Bijur System.  Packard 1920, Single Six—Deleo Ignition and Atwater-Kent S	tarting
and Lighting Systems.  Packard Twelve—Bijur System	Plate 144
Packard Twelve—Bijur System	Page 378
Packard Twin Six, Models 2-25 and 2-35	Page 377
Paige 1916-17, Model 6-39—Remy Ignition System	Page 545
Paige-Detroit, Model 6-40—Remy System	
Paige 1920, Models 6-42 and 6-55-Atwater-Kent Ignition an	d Gray
and Davis Starting and Lighting Systems.	Plate 146
and Davis Starting and Lighting Systems  Paige, Model 6-55—Remy System Pan, Model 250—Remy System Parallel Control for Dimming Headlights.  Paterson 1914, Models 32 and 33—Deleo System Paterson 1915, Models 4-32 and 6-48—Deleo System.	Page 546
Pan, Model 250—Remy System	. Plate 147
Parallel Control for Dimming Headlights	Page 316
Paterson 1914, Models 32 and 33—Delco System	. Plate 148
Paterson 1915, Models 4-32 and 6-48 - Delco System.	. Plate 149
Paterson 1916, Model 6-42—Delco System.	. Plate 150
Paterson 1917, Models 6-45 and 6-45 R -Delco System	Plate 151
Paterson 1920, Model 6-47 (Using 7-R Continental Engine)	
System	Plate 152
System  Paterson 1920, Models 6-46 and 6-46 R (Using 7-W Con-	tinental
Pathfinder 1917 Twelve—Delco System	Page 453
Peerless 1917, Series 2 and 3—Auto-Lite System.	Plate 154
Peerless 1917, Series 2 and 3—Auto-Lite System. Pierce-Arrow 1919-20, Models 38 and 48—Delco System.	Plate 155
Pierce-Arrow, Series Four, Models 38, 48, and 66 -Bosch	Ignition
System	Page 617
	nghouse
System	Pages 618, 619
Pilot 1917, Model 6-45—Delco System	Page 454
Premier 1914, Model A—Remy System.	nghouse Pages 618, 619 Page 454 Plate 156 Plates 157, 158 Page 459 Plate 160
Premier 1915, Model 6-50—Remy System	Plates 157, 158
Premier 1917, Model 6-B—Delco System	Page 459
Premier 1919, Models 6-B and 6-C -Deleo System	Plate 159
Premier 1920, Model 6-D—Delco System	Plate 160


## INLEX

comprehense. Name (- long rong	<del>.</del>
Series Control of Imminito Fier on to	-
Commission of the Commission Commission Commission of the Commissi	-
Special products (Special productions) Filters and Comparisons	. :
Step 1-V and content or	'
and the second section of the second	
Specifier Tagging element club VI Field (1997).	-
Service of the Control of the Contro	÷
Strong-Approximate Important Strong	
The property of the second property and the second property of the s	
Stephen Start Cole North Section 2. The Section Sectio	
<ul> <li>Structure transfer described in the second of /li></ul>	
trops. Light for the Station States. States August Model SEL 4—Ronn States.	
CONTROLLED LIBERT AND CONTROL OF AND	<u>:</u> - <u>-</u> -
Stephens I of The Dept. Sciences. Stephens (1975) Means Thate The I have Science. Stephens of the Stephens Thate The I have Science. Stephens of the Stephens I of Means I have Server.	
o entreprise de la companya del companya del companya de la companya del la companya de la comp	
in the control of the	•
Stronge Fairtest Chargery from Lagritud to the commit- stronge Frances Methods of Institution	
The particular of the same of	•
TO HOUSE ENGINEEN, 1987 THE FAMILY OF LIBERTALIES	:_ <b>:</b>
Storing Butters, Testing Rate of Discharge Storing Buttery Tweek-stage Connections Tronge Butters Votings Testing  1	-
The stage points for Assistage Describe	
St. product 1814-17. Or om sen Batters—Remo Systom St. product 1814-15. Insulated Batters—Remo Systom	
ht potential Fig. 10 secuted Batter, — New York T.	:- '-
Steller John 17 - Reng Ignetica System	
7 (2) 1914-15   Reny 5) stem.	
at richted er 1918. Moneis all, L.H. snu Live Remain was m	
Step ted er 1920, Series 20-Remy Ignation and Wagner St. 2012	<u>-</u> :
I giving System	
Streetheer Four and Six, Models SI and ED-Ham Lights	
Wagner Starting and Lighting Systems	
St. 42 1916-17 Reply System	<u> </u>
est de Veles Series S. Deleo Ignation System est de la Model 4-8 Deleo Ignation System	
- 77 (2.2) (1.7) April 19-7 (1.2) (1.2) April 20-74-742	
Social gers So. Moder 17—Remy System	• • • •
Ţ	
Temp v 1918-19-20 Model A-4-45 Remy System	$\Gamma_{i,j}$
To ting set	i
T <sup>-</sup>	
1	
1 + L 12 6 Volt External-Regulator System	T)
1 34, 24 12-Volt External-Regulator System	Page
1 - 1, 24 12-Volt Inherently Regulated System	Page
to the the continuous in the state of changing	Page :
V	
Variable Discourse Day of the second	T)
Variable Dimining Resistance	Page 3
Veine 1916, Model 22   Remy System Veloc 1918 10 Alreldo 28, 20 7 and 20   Sport   Dama System	Page :
Vehic 1918-19, Models 38, 39-7, and 39, Sport—Remy System	_Plate 1
Vehe 1920, Model 48 - Atwater-Kent Ignition and Bijur Starting at Lighting Systems	
Vehe 1920, Model 34 Atwater-Kent Ignition and Westinghou	Plate !
Starting and Lighting Systems.	
	Plate 1
In the state of th	. Page 5
	Page 5
	Page 3
** Treeter, Method of Shunting in Circuit	Page
	Page
Park and 1915 Models in	

## $\mathbf{w}$

Westcott 1915 U-6 and O-35—Delco System	Plate 187
Westcott, Series 19—Delco System	Plate 188
Westcott 1917-18—Delco System	Page 420
Westcott 1920, Models A-38 and C-38—Delco SystemPlan	
Westcott 1920, Model C-48 (Using 9-N Continental Engine)—De	lco
SystemPla	tes 191, 192
Westinghouse External-Regulator System	Page 629
Westinghouse Generator with Self-Contained Regulator	Page 628
White—Leece-Neville System	Page 503
White, Model G-M—Leece-Neville System	Page 506
Willys-Knight, Model 88-4—Auto-Lite System	Page 352
Willys-Knight, Model 88-8—Auto-Lite System	Page 353
Winton—Bijur System	Page 359
Winton, Limousine Six, Model 22-A—Bijur System	Page 376
Winton, Touring Six, Model 22-A—Bijur System	Page 373



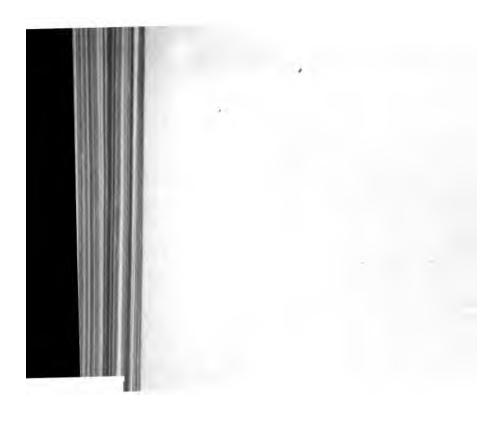

The page numbers of this volume will be found at the bottom of the pages; the numbers at the top refer only to the section.

Pa A	ıge	Automatically timed systems	age 138
<del></del>	11	Eisemann centrifugal-governor	100
	71	type	139
Advance and retard of spark	29	Herz ball-governor type	140
	30	Herz ban-governor type	140
analysis of oscillograph dia-	.00	В	
	34	Back-kick releases	303
calculation of small time allow-	.04	Batteries 53, 79, 86,	
	30	symbol for	320
	32	Battery cut-out 600, 609, 630,	
	35		761
	.00	summary of instructions	600
Allen, firing order and ignition advance	47	in Wagner system	630
	47	in Westinghouse system	000
Ammeter readings in testing elec-	200	Battery cut-out tests, Auto-Lite	354
	336	system	173
Apperson 147, 361, 3		Buttery Birtion Systems, Indiana	176
	145	Atwater-Kent	179
Brammar Branch con	146	Connecticut	
G	49	Delco	185
open- or short-circuited genera-		effect of starting and lighting	170
	150	developments on ignition	173
short circuits between motor and		generator design follows mag-	. 70
	149	neto precedent	173
Armature windings	38	Remy	182
Atwater-Kent battery ignition		Westinghouse	175
	76	Battery in starting and lighting	
Atwater-Kent interrupter	89	systems, summary of in-	
Auburn, firing order and ignition		structions	776

	Page	Page	
Bijur system (continued)	· ·	Chemical sources of ignition cur-	
instructions		rent (continued)	
Нирр	370	storage batteries 87	•
Jeffery -	367	Chevrolet, firing order and ignition	
Packard	375	advance 149	)
Scripps-Booth	374	Chevrolet-Auto-Lite electrical sys-	
Winton	<b>364</b>	tem, diagram for 325	
in-truments	358	Circuit 3, 11, 33, 66	š
regulation	354	multiple or shunt	
wiring diagrams	358	series 1.	
Apperson	361	series-multiple 13	
Нирр	361	Circuit breaker 289, 329	
Jeffery	358	summary of instructions 766	
Scripps-Booth	361	testing 437	-
Winton	358	Circuit of high-tension magneto 100	j
	8, 191	Cleaning repair parts of electrical	_
Bosch incandescent lamp	312	equipment 72	ĩ
Bosch-Rushmore automatic en		cleaning outfit 72:	
gagement	300	method of cleaning parts 725	
Bosch-Rushmore system	379	Cleaning storage battery 689, 78	6
generator	379	Clutches to disengage starter from	
instructions	383	gasoline engine 301	
<ul> <li>instruments and protective de</li> </ul>	·-	necessity for disengaging device 30	l
vices	381	roller type 300	3
regulation	379	Coil in low-tension system 90	
starting motor	379	Coils 320	0
wiring diagram	383	Cole, firing order and ignition ad-	
Briscoe, firing order and ignitio	n	vance 150	0
advance	148	Columbia, firing order and ignition	
Brushes	46	advance 150	0
Buckled battery plates, summar	v	Commutator 3	5
of instructions	788	Commutator and brushes, sum-	
Buick 14	8, 408	mary of instructions 74:	3
Buick-Delco electrical system, die	1-	Commutator maintenance in Delco	
gram for	321	system 44:	2
••		Compound distributor 113	5
$\mathbf{c}$		Compound-wound generator 4-	4
Cable in electrical equipment, ca	1-	Condenser 9	4
culating size of	165	capacity of 29	9
	8, 405	office of 100	()
Capacity of battery	667	symbol for 32	1
Capacity of condensers	29	Conductors 8, 16, 6;	3
Case, firing order and ignitio	n	Connecticut battery system 179	
advance	149	automatic switch 183	2
Cell of storage battery (see Storage		Connections, importance of good 160	b
	5, 666	Connectors of battery, summary	
Chalmers, firing order and ignitio	II.	of instructions 78	7
advance	149	Constant-current generator 28	1
Chandler, firing order and ignitio	11	Contact breaker, inspection of 19	4
advance	149	Contact makers 28	9
Charge, testing rate of	719	Contact points, summary of in-	
Charging storage battery	707	structions 76	1
equalizing charges necessary	709	Contact timers 8	_
methods of	710	Contacts, symbol for 319	
from outside source	707	Control in starting lighting systems	-
in series for economy	710	Splitdorf 573	5
Chemical sources of ignition cur		Wagner 599, 600	
rent	56	Westinghouse 62:	
primary batteries	56	Crossed wires, symbol for 32:	
Paramity Duttering	,	The state of the s	•

]	Page		Page
Crow-Elkhart, firing order and		Driving connections of starting	ng
ignition advance	150	motor	299
Cunningham, firing order and		Dry cells, defects of	86
ignition advance	150	Dual ignition system	118
	3, 31	distributor	121
chemical effect	19	Bosch type	118
heating effect	18	Remy type	120
Current direction	318	wiring diagram	122
Cut-out, testing	432	Duplex ignition system	123
D		Dynamo	34 51
	185	Dynamotor	
Delco ignition system earlier model interrupter	186	Dynamotor in starting and ligh	16
timer with resistance unit	187	ing systems North East	510
Delco starting and lighting system		Simms-Huff	565
instructions	000	Wagner	599
adjusting third brush	425	Westinghouse	623
commutator maintenance	442	Dyneto system	461
general instructions	422	six-volt; two-unit	462
seating brushes	438	generator	462
testing armatures	445	instructions	467
testing circuit-breaker	437	regulation	462
testing cut-out	432	starting motor	466
testing field coils	452	wiring diagrams	466
tests of wiring	429	twelve-volt; single-unit; singl	e-
six-volt; single-unit; single-wire	389	wire	461
control	390	dynamotor	461
dynamotor	389	instructions	462
protective devices	<b>4</b> 01		
regulation	394	E	
wiring diagrams	405		70 <b>, 793</b>
six-volt; two-unit; single-wire	415	Eisemann centrifugal - govern	or
generator	415	automatically timed sy	·8-
regulation	416	tem	139
starting motor	416	Electric circuit	3, 66
starting switch	419	chemical effect of current	19
wiring diagram	419	circuits	11
Delco third-brush	425	conductors	8

1	Page	P:
Electric starting and lighting systems (continued)		Electrode arrangement in spark
general features		Electrolyte of storage battery cell
methods of regulation	281	664,
protective devices	288	Electromagnets
standardisation	289	Elements of storage battery cell
starting motors	290	Elgin, firing order and ignition
transmission and regulation devices	296	advance Equalizing charges of storage bat-
variations of operating units		tery
and wiring plans	276	Essex, firing order and ignition
practical analysis of types	318	advance
Auto-Lite system	337	_
Bijur system	354	<b>F</b>
Bosch-Rushmore system	379	Field coils, testing
Delco system	389	grounded fields
Disco system	461 461	open-circuits in fields
Dyneto system Ford system	640	short-circuits between coils short-circuits between windings
Gray and Davis system	468	voltmeter field tests
Gray and Davis system for		Field magnets
Ford cars	646	forms of field magnets
Heinze-Springfield system	490	permanent field used in mag-
Leece-Neville system	499	neto
North East system	510	self-excited fields
Remy system	535	Filaments for incandescent lamps
Simms-Huff system	565 575	Firing order
Splitdorf system U. S. L. system	583	magneto mounting
Wagner system	599	possible combinations typical orders
Westinghouse system	623	wiring
starting and lighting storage		Firing orders and ignition advance
batteries	661	Allen
summary of instructions	731	Apperson
battery	776	Auburn
electric gear-shift	774	Briscoe
generators	731	Buick Cadillac
lighting and indicators protective devices	767 758	Case
starting motor	749	Chalmers
wiring systems	752	Chandler
Electrical equipment, cleaning	727	Chevrolet
Electrical equipment for gasoline c		Cole
electric starting and lighting sys-		Columbia
tems	275	Crow-Elkhart
elementary electrical principles	2	Cunningham Dodge
ignition	81	Dodge Dorris
practical analysis of types	318	Dort
testing, adjusting, and main-		Elgin
tenance	196	Essex
	4, 30	Ford
Electrical principles, elementary 2		Franklin
electric circuit	3	Grant
induction principles in genera- tors and motors	27	Haynes Holmes
magnetism	20	Holmes Hudson
***	321	Hupmobile
Electrically operated switches	307	Jordan
Note.—For page numbers see foot of page	۵.	

	_		_
	Page		Page
Firing orders and ignition advance			34, 70
(continued)		armature windings	38
King	153	brushes	46
Kissel-kar	153	classification	34
Lexington	154	commutators	35
Liberty	154	elementary dynamo	34
Locomobile	154	field magnets	40
Marmon	154	Generator in starting and lighting	ng
Maxwell	154	systems	400
McFarlan	155	Leece-Neville	499
Mercer	155	removing generator in Fo	ra 644
Metz	155	system	
Mitchell	155	Remy	535 731
Moline-Knight	156	summary of instructions	743
Nash	156	commutator and brushes	733
National Oakland	156	loss of capacity	735
Oldsmobile	157	methods of regulation	738
Overland	157 157	regulators	731
	158	types and requirements windings	741
Paige Peerless	158	testing generator with ammet	
Pierce-Arrow	159	in Gray and Davis syste	m T
Premier	159	for Ford cars	659
Reo	159	Wagner	609
Saxon	160	Westinghouse	627
Scripps-Booth	160	Generator output, control of	281
Stearns-Knight	160	Generator-starting motor	
Stephens	160	Gray and Davis system	647
Studebaker	160	U. S. L. system	583
Stutz	161	Generator tests	
Templar	161	Auto-Lite system	351
Velie	161	Gray and Davis system	485
Westcott	161	Gray and Davis special system f	or
Willys-Knight	162	Ford cars	646
Winton	162	installation	646
Fixed-spark ignition systems	138		ნ, 657
Ford, firing order and ignition advance	n	testing generator with ammete	
<b>a</b> dvance	151	Gray and Davis system	468
	0-10		446

	Page	]	Page
Heinze-Springfield system	Ü	Ignition principles, fundamental	
(continued)		(continued)	
generator	490	distinctions between low tension	
instructions	494	and high tension	81
regulation	492 490	faulty ignition cause of much	81
starting motor wiring diagram	490 494	early trouble high-tension system	84
Herz ball-governor automatically		low-tension system	83
timed system	140	Ignition setting point	141
High-tension cables in electrical		Ignition switch in Remy system	182
equipment	162	Ignition systems	
	, 205	modern battery systems	173
High-tension magneto	105	standard types	118
circuit	106	Illuminating gas lead-burning out-	
description	105	fit	701
safety gap	107	Incandescent lamps	312
type with coil	107	Bosch type	312
wiring connections	108	Mazda type	312 312
Holmes, firing order and ignition	152	tungsten and other filaments Indicators 500, 543,	
advance Hudson, firing order and ignition		Indicators 500, 543, Induction	27
advance	153	Induction coil, symbol for	321
Hupmobile	153	Induction principles in generators	
Hydraulic analogy in ignition sys-			7, 61
tem	99	capacity of condensers	29
current	99	circuits	33
office of condenser	100	comparison of generator current	
transformer	101	to water flow	29
Hydrogen gas lead-burning outfit	703	current and volume	31
	, 725	electric motor principles	47
frozen cells	675	friction and resistance	31
hydrometer tests 673, 678,		generator principles	34
low cells	676	induction	27
variations in readings	676	power comparison	32 30
Hydrometer tests of battery, summary of instructions		pressure and voltage self-induction	28
summary or instructions	113	Induction sources of ignition cur-	20
1		rent	102
1		Inductor-type magneto	109
Ignition	81	timing	114
chemical sources of current	86	typical construction details and	
fundamental ignition principles	81	current production	109
ignition systems	173	Installation of starting motor	296
induction sources of current	102	Installing new storage battery	705
sources of current	86	Instructions on individual starting	
spark timing	$\frac{129}{205}$	and lighting systems	640
summary of Instructions		Ford Cray and Davis system for Ford	040
voltage and spark control device Ignition advance (see Firing orders		Gray and Davis system for Ford cars 646,	657
and ignition advance)	147	Leece-Neville	501
Ignition batteries, summary	254	to adjust third brush	508
Ignition current, sources of	86	brush replacements	509
chemical	86	generator or motor failure	<b>50</b> 9
magnetos	102	regulating brush	507
<ul> <li>voltage and spark control device</li> </ul>		testing field winding	504
Ignition failure, general causes of	265	North East	514
Ignition in Ford system	644	battery cut-out and regulator	
Ignition methods, changes in	~~	(relays)	516
Ignition principles, fundamental	81	five-terminal type unit	519
NoteFor page numbers see foot of pages			

_	INI	)EX	7
	Page		Page
Instructions on individual starting	;	Instructions on starting and light	-
and lighting (continued)		ing, summary (continued)	
North East	***	battery	=00
starting switch	522	voltage tests	783
Remy	548	washing battery	786
ammeter	565	electric gear-shift	774
battery discharge	548	generators	731
dim lights	<b>56</b> 0	commutator and brushes	743
failure of lighting, ignition,		loss of capacity	733
starting	560	methods of regulation	735
Simms-Huff	570	regulators	738
failure of cut-out or of regu-		types and requirements	731
lator -	573	windings	741
generator tests	573	lighting and indicators	767
Splitdorf	580	instruments	770
failure of engine to start	580 580	lamps	767
oiling of starting motor	586	protective and operative device	
U.S.L	• • •	battery cut-out	761
ammeter .	593 593	circuit-breaker	760
battery cut-out	590	contact points fuses	764 759
brush pressures	591	switches	766
external regulator radial and angular brushes	591	starting motor	749
starting switch	590	wiring systems	752
testing carbon pile	593	different plans	752
touring switch	586	faults in circuit	753
Wagner six-volt	613	proper conduction	756
cautions	616	Instruments used in starting and	
ground in starting or in light-		lighting systems	•
ing circuits	613	Lecce-Neville	500
localizing any ground	614	Remy	543
localizing short-circuit	616	Simms-Huff	565
short-circuit tests	615	summary of instructions	770
Wagner twelve-volt	603	U. S. L	585
failure due to battery cut-out	608	Internal damage	686
lack of capacity through		Interrupters 182, 186	
faulty gear box	607	•	,
method of tooling commutator	r 603	J	
switch or generator parts to be	5	Jeffery	367
1	400	1 2 15:11	

S INDEX

	Page		Page
Lead burning (continued)	•	Magneto (continued)	·
illuminating gas outfit	701	inductor-type	109
methods of burning	700	low-tension	103
type of outfit	699	magnetos for 8-cylinder and 12-	
Leakage at distributor	199	cylinder motors	115
Leece-Neville system	499	permanent field used in	40
generator	499	summary	208
instructions	501	timing	111
instruments	500	typical construction details and	
regulation	499	current production	109
starting motor	500	working principle	102
wiring diagram	501	Magneto mounting	170
Lexington, firing order and ignition		Magneto mountaing Magneto speeds	137
advance	154		132
		Magneto timing	
Liberty, firing order and ignition	154	Magnetos for 8- and 12-cylinder	115
advance		motors	
Lighting	312	Maintenance of electrical equip-	100
dunning devices	316	ment	196
headlight glare	315	Marmon, firing order and ignition	
meandescent lamps	312	advance	154
lamp voltages	313	Master vibrator	91
lighting batteries	313	Maxwell, firing order and ignition	
reflectors	314	advance	154
summary of instructions	767	Mazda incandescent lamp	311
Lighting batteries	313	McFarlan, firing order and ignition	
Lighting in Ford system	644	advance	155
Lines of magnetic force	25	Mea method of advancing spark	135
Locomobile, firing order and igni-		Mercer, firing order and ignition	
tion advance	154	advance	155
Loose connections in Gray and		Metz, firing order and ignition	
Davis system	480	advance	156
Low battery	788	Misfiring	128
Low cells	676	Mitchell, firing order and ignition	
Low-tension ignition system 83	, 205	advance	155
Low-tension magneto	103	Moline-Knight, firing order and	
		ignition advance	156
M		Motor	
Magnet, weak	197	summary	76
Magnet recharger	202	theory of operation	47
Magnetic attraction and repulsion,		types of	50
laws of	21	Motor-generator as rectifier	711
Magnetic field	$\tilde{23}$	Motor windings and poles	294
Magnetic force, lines of	$\tilde{25}$	commercial forms	295
Magnetic plugs	$\tilde{97}$	standard designs	294
Magnetic substances	22	Multi-vibrator, complications of	91
	0, 58	Multiple circuit	13
	22	Muniple circuit	10
electromagnets		N	
laws of magnetic attraction and	21		
repulsion	$\frac{21}{25}$	Nash, firing order and ignition	1-0
lines of magnetic force	23	advance	156
magnetic field		National, firing order and ignition	1 = 0
magnetic substances	22	advance Non-conductors	156
natural and artificial magnets	20	Non-conductors	10
poles of magnet	21	Non-vibrator coil	92
solenoids	25	North East system	510
Magneto	200	dynamotor	510
breakdown of	200	instructions	514
Dixie	112	protective devices	510
high-tension	105	regulation	510

Note.—For page numbers see feet of pages

INDEV

	11/1	)EA	9
	D		
N-st Est sester (sestimed)	Page	D	Page
North East system (continued) switch tests	523	R Reflectors	214
wiring diagrams	512		314
withing diagrams	012	Regulation, methods of	281
0		constant-current generator necessity for control of generator	
Oakland, firing order and ignition	m	output	281
advance	157		, 296
Ohm's law	5, 57	Regulation in starting and lighting	
Oldsmobile, firing order and ign		systems	,
tion advance	157	Leece-Neville	499
Oscillograph diagrams, analysis of	of 134	North East	510
Overhauling storage battery	693	Remy	535
checking connections	696	constant-voltage method	535
dismounting cells	694	thermostatic switch	536
reassembling battery	695	third-brush method	536
reconnecting cells	698	Simms-Huff	<b>565</b>
renewals	698	Splitdorf	576
treating plates	695	U. S. L.	584
Overland, firing order and ignitio			, 609
advance	157		, 627
n		Regulators, summary of instruc-	
P	075	tions	738
Packard	375	Remagnetizing	201
Paige, firing order and ignitio	158		, 182 183
Parabolic reflector	314	detecting grounds ignition switch	184
Peerless, firing order and ignitio		interrupter and distributor	184
advance	158	Remy system	535
Pierce-Arrow, firing order and ign		single-unit	544
tion advance	159	instructions	548
Planetary gear on Wagner starte	r 602	mechanical combination	544
Plug threads	98	wiring diagrams	544
Poles of magnet	21	two-unit	535
Power unit	6	generator	<b>5</b> 35
Premier, firing order and ignitio		instruments and protective	
advance	159	devices	<b>54</b> 3
Pressure	4, 30	regulation	535
Primary batteries	86	starting motor	<b>54</b> 3
defects of dry cells	86	Reo, firing order and ignition ad-	150
hand heltenes		Manag	1211

Short-circuits         15         Spark timing (continued)           Shunt circuit         13         ignition-system fixed timing point           Shunt-wound generator         44         point         138           Simms-Huff system change of voltage         565         magneto speeds         137           Spark timing (continued)         138         138           Sparking, effect of irregular         129		Page		Page
Shunts-Wound generator Simms-Huff system change of voltage dynamotor connections instructions ingle-unit instructions ingle-u	Short-circuits	15	Spark timing (continued)	
Shunt-wound generator Simms-Huff system dynamotor connections instructions instruct	Shunt circuit	13	ignition-system fixed tim	ing
change of voltage dynamotor connections of dynamotor connections instructions instructions 566 instructions 576 instruments 566 regulation 565 regulation 565 regulation 566 starting switch 566 wiring diagram 570 single unit electrical systems 570 beloo 389 too high 575 beloo 389 byneto 461 North East 510 Remy 544 Simms-Huff 565 Spittdorf 575 Six-volt systems 499 535 Simple-wire electrical system compared with two-wire diagrams for 576 Six-volt systems 499 535 Simple-wire systems 499 535 Simple-wire systems 499 535 Six-volt systems 499 535 Spark called a system 575 Spark, effect of compression on Spark control devices 58 Spark plugs electrode arrangement 576 magnetic plugs 97 hydrometer fundamental requisite magnetic plugs 98 park tuning advance and retard automatically timed systems effect of irregular 576 Spark tuning advance and retard automatically timed systems effect of irregular 576 spark cannot centrifugal-governor type 140 cychaling battery 693 replacing jar replacing jar prostring suphated battery 696 firing order 140 cychaling battery 696 firing order 140 cycha	Shunt-wound generator	44		
dynamotor dynamotor connections dynamotor connections dynamotor connections dynamotor connections dynamotor connections dynamotor connections instructions 566 instructions 570 instruments 565 regulation 565 starting switch 565 starting switch 565 starting switch 565 starting switch 566 starting switch 569 wiring diagram 5770 Single unit electrical systems 276 dynamotor 575 dynamotor 575 beloo 389 Dyneto 461 North East 510 Remy 544 swagner 575 Splitdorf 575 U. S. L. 583 Wagner 565 Single-wire electrical system compared with two-wire diagrams for 321, 348, 383, 419, 475, 494 Single-wire systems 579 Single-wire systems 570 Remy 570 Single-wire	Simms-Huff system		magneto speeds	137
dynamotor dynamotor connections instructions instructions 566 instructions 570 instruments 565 starting switch 565 starting switch 565 starting switch 565 starting switch 566 starting switch 566 starting switch 567 starting switch 568 starting switch 569 swiring diagram 5770 single unit electrical systems Bijur 570 single unit electrical systems 570 single-unit 575 single-unit 575 single-unit 575 single-unit 576 splitdorf 575 two-unit 576 control 576 instructions 580 systems 576 starting motor 576 instructions 580 systems 576 starting motor 576 starting motor 576 standard ignition systems 118 starting motor 578 starting motor 578 starting motor 578 starting motor 578 starting motor 579 standard ignition systems 112 starting and lighting developments, effect on ignition 578 starting and lighting storage batteries 565 systems 499 535 and lighting storage batteries 566 systems 499 535 and lighting storage batteries 567 system-volt systems 499 535 and lighting storage batteries 661 starting and lighting storage batteries 670 spark systems 499 535 adjustible water 670 starting and lighting storage batteries 661 starting and lighting storage batteries 661 starting and lighting storage batteries 670 spark systems 672 starting and lighting storage batteries 673 starting and lighting storage batteries 661 starting and lighting storage batteries 661 starting and lighting storage batteries 661 starting and lighting storage batteries 670 spark curing and lighting storage batteries 670 spark turning always specific gravity 670 spark turning plugs 98 spark turning 190 spark	change of voltage		Sparking, effect of irregular	129
dynamotor connections instructions instructions instructions 570 instruments 565 starting switch 565 starting switch 565 starting switch 565 starting switch 569 starting diagram 570 single unit electrical systems 276 instructions 570 single unit electrical systems 276 dynamotor 575 ingle unit 575 dynamotor 575 dynamotor 576 dynamotor 576 instructions 580 dynamotor 576 starting motor 577 standard ignition systems 118 double-spark 124 dual ignition 124 dual ignition 125 dual ignition 124 dual ignition 125 dual ignition 125	dynamotor	565	Sparking at safety gap	200
instructions instructions 570 single unit electrical systems 575 summary of instructions 788 summary of instructions 589 summary of instructions 580 single-unit 575 single-unit 575 single-unit 575 single-unit 575 single-unit 575 single-unit 576 singl			Specific gravity 665, 676, 6	85, 788
regulation starting switch 569 swiring diagram 570 Single unit electrical systems Bijur 570 Deleo 389 Dyneto 461 North East 510 Remy 544 Singhest 683 Splitdorf 575 Starting motor 579 Standard ignition 576 Standardization of electrical equipment 575 Movestinghouse 623, 627 Six-volt systems 499, 535 Six-ten-volt system, North East 510 Sketen-volt system, North East 510 Spark, effect of compression on 199 Spark centrol devices 88 Spark plings electrode arrangement 576 Spark, effect of compression on 199 Spark centrol devices 88 prinning plugs 58 series plugs 577 summary 237 hydrometer 579 summary 237 summary 237 symmary 237 hydrometer 681 sympary 242 symmary 2437				
regulation 565 wiring diagram 570 Single unit electrical systems 276 dynamotor 575 Spitledorf system 575 dynamotor 575 dynamotor 575 dynamotor 575 dynamotor 576 dynamotor 578 dynamotor 578 dynamotor 578 dynamotor 578 dynamotor 578 dynamotor 579 dynamotor 578 dynamotor 576 dynamotor 576 dynamotor 576 dynamotor 576 dynamotor 578 dynamotor 578 dynamotor	instruments			788
wiring diagram Single unit electrical systems Bijur 354 Deleo 389 Deleo 399 Deleo 389				685
single unit electrical systems 276 Bijur 354 Deleo 389 Deleo 389 Deleo 389 Deleo 389 Deleo 389 Deleo 389 L S L 46 Simms-Huff 565 Splitdorf 575 Standard ignition systems 118 double-spark dual ignition 1123 Standardization of electrical equipment 576 Standard ignition systems 118 Starting and lighting developments, effect on ignition 173 Starting and lighting development 173 Starting			Splitdorf system	575
Bijur 354 Deleo 389 Deleo 389 Deleo 389 Dyneto 461 North East 510 Remy 544 Simms-Huff 565 Splitdorf 575 U. S. L. 583 Wagner 599 Westinghouse 623 Single-wire electrical system compared with two-wire diagrams for 321, 348, 383, 419, 475, 494 Single-wire systems 510 Remy 535 Simns-Huff 565 Swolt systems 499, 555 Lecce-Neville 499 Sixvolt systems 499, 555 Lecce-Neville 499 Sixteen-volt system, North East 510 Sixvent systems 499, 555 Lecce-Neville 499 Sixteen-volt system, North East 510 Sixpen systems 499, 555 Lecce-Neville 499 Sixteen-volt system, North East 510 Sixpen systems 499, 555 Lecce-Neville 499 Sixteen-volt system, North East 510 Sixpen systems 499, 555 Lecce-Neville 499 Spark, effect of compression on 199 Spark control devices 88 Spark plugs electrode arrangement fundamental requisite magnetic plugs plug threads prinning plugs 98 Spark plugs 97 waterproof plugs 98 Spark timing 129 advance and retard automatically timed systems effect of irregular sparking 129 advance and retard automatically timed systems effect of irregular sparking 129 automatically timed systems 18 double-spark until two-unit control 576 starting diagram 557 two-unit control 576 standard ignition systems 118 double-spark 124 dual ignition 113 starting and lighting developments, effect on ignition 173 starting and lighting storage batteries care of battery 128 ear of battery 661, 670 A. C. rectifiers 711 adding acid 671 adding acid 67 ear of battery 681, 681 eare of battery 681, 681 eare of battery	wiring diagram		single-unit	
Bigur   Deleo   389				
Deteo Joyneto 461 North East 510 Remy 544 Simms-Huff 565 Splitdorf 575 L. S. L. 583 Wagner 599 Westinghouse 623 Single-wire electrical system compared with two-wire diagrams for 321, 348, 383, 419, 475, 494 Single-wire systems North East 510 Remy 535 Simms-Huff 565 Swestinghouse 623, 627 Six-volt systems 499, 535 Lecce-Neville 499 Remy 535 Lecce-Neville 499 Sixteen-volt system, North East 510 Remy 535 Sixteen-volt system, North East 510 Spark, effect of compression on 199 Spark, effect of compression on 199 Spark control devices 88 Spark pluss electrode arrangement 602 and and split general plus prinning plugs 97 systems plugs 97 summary 237 waterproof plugs 98 Spark timing 129 advance and retard advance and retard advance and retard automatically timed systems effect of irregular sparking 129 automatically timed systems 128 automatically timed systems 128 automatically timed systems 129 automatically timed systems 120 automa				
North East 510 control 556 North East 510 instructions 580 Remy 544 regulation 576 Smims-Huff 565 Splitdorf 575 U. S. L. 553 Wagner 599 Westinghouse 623 Single-wire electrical system compared with two-wire diagrams for 321, 348, 383, 419, 475, 494 Single-wire systems 535 North East 510 Remy 535 Westinghouse 623, 627 Remy 535 Westinghouse 623, 627 Six-volt systems 499, 535 Westinghouse 623, 627 Remy 535 Six-volt systems 499, 535 Skieten-volt system, North East 510 Remy 535 Skieten-volt system, North East 510 Spipping-clutch, regulation of general and signification of general and lighting storage batteries and lighting storage batteries care of battery 661, 670 A. C. rectifiers 711 adding acid 671 adding distilled water 670 adding series for economy 710 clear of battery in winter 71 charging in series for economy 710 clear of battery in winter 71 charging in series for economy 710 clear of battery in winter 71 charging in series for economy 710 clearing battery 689 higher charge needed in cold weather 681 priming plugs 98 port tuning 129 priming plugs 98 spark tuning 129 waterproof plugs 98 Spark tuning 129 advance and retard 130 advance 130 advance 140 advance 157 bx starting motor 12		389		
North East Remy 544 Simms-Huff 565 Simms-Huff 565 Splitdorf 575 L. S. L. 583 Wagner 599 Westinghouse 623 Single-wire electrical system compared with two-wire diagrams for 321, 348, 383, 419, 475, 494 Single-wire systems 510 Remy 535 Six-volt systems 499, 535 Six-volt systems 499, 535 Six-volt system, North East 510 Remy 535 Six-volt system, North East 510 Lecce-Neville 499 Ilemy 635 Sixitene-volt system, North East 510 Spark, effect of compression on 199 Spark, effect of compression on 199 Spark control devices 88 Spark plugs electrode arrangement 96 plug threads 98 priming plugs 98 series plugs 97 series plugs 98 spark timing 129 advance and retard automatically timed systems 138 effect of irregular sparking 129 Ilez ball-governor type 140 Ilez ball-governor type 140 Interval automatically timed systems 138 lead burning battery 693 fring order 143 replacing in instructions regulation 576 starting motor 579 Standard ignition systems 118 double-spark double-spark double-spark 124 do		461		
Remy Simms-Huff Simms-Huff Siplitdorf Splitdorf Standard ignition systems I18 double-spark dual ignition Stanting moto clectrical equipments, effect on ignition Splitdorf Standard ignition Standard ignition I23 Starting and lighting developments, effect on ignition Splitdorf Standard ignition Standardization of electrical equipments, effect on ignition Stanting and lighting developments, effect on ignition Stanting and lighting development, erac of battery 661, 670 A. C. rectifiers Adding acid 677 adding acid 677 adding acid 671 adding distilled water care of battery in winter rear of b	North East	510		
Simms-Huff Splitdorf Standard ignition systems Spartd magneto Stanting motor Standard ignition systems Splitdon Starting and lighting developments, effect on ignition Starting and lighting developments, effect on ignition Starting and lighting developments, effect of battery Starting and lighting developments, effect on ignition Starting and lighting developments, effect on ignition Starting and lighting developments, effect on ignition 173 Starting and lighting developments, effect on ignition 174 Standardization of electrical equipment Starting and lighting storage batteries Care of battery 661, 670 A. C. rectifiers 711 adding acid developments, effect on ignition 173 Adding distilled water 671 adding distilled water 672 care of battery in winter 71 charging in series for economy 710 cleaning battery 689 celectrode arrangement 690 electrical equipment 691 eare of battery in the dual ignition 123 Starting and lighting storage batteries 681 eare of bat	Remy	544		
Spintdort U. S. L. 558 Wagner Westinghouse 599 Westinghouse 623 single-wire electrical system compared with two-wire diagrams for 277 Single-wire systems 707 Remy 535 Simms-Huff 565 Westinghouse 623, 627 Six-volt systems 499, 535 Leece-Neville 499 Remy 535 Sixtensylle 709 Remy 535 Sixtensylle 709 Remy 535 Sixtensylle 709 Remy 535 Sixtensylle 700 Starting and lighting developments, effect on ignition 173 Starting and lighting storage batter; 661 Remy 661, 670 A. C. rectifiers 711 Adding acid 671 Adding distilled water 670 adjusting specific gravity 676 Spark, effect of compression on 199 Spark control devices 88 Spark plugs electrode arrangement 696 For magnetic plugs 98 Spark plugs electrode arrangement 696 For magnetic plugs 98 Spark plugs electrode arrangement 696 For magnetic plugs 98 For magnetic plugs 98 Spark timing 129 Spark plugs 98 Spark timing 129 Active 700 Spark plugs 98 Spark timing 129 Active 700 Spark plugs 98 Spark timing 129 For dual ignition 118 double-spark dual ignition 118 Starting and lighting developments, effect on ignition 173 Starting and lighting storage batter; 661 Care of battery 661, 670 A. C. rectifiers 711 A. C. rectifiers 711 Adding acid 671	Simms-Huff	565		
Wagner Westinghouse Single-wire electrical system compared with two-wire diagrams for 321, 348, 383, 419, 475, 494 Single-wire systems North East 510 Remy 535 Westinghouse 623, 627 Six-volt systems 499, 535 Lecce-Neville 499 Remy 535 Westinghouse 623, 627 Six-volt systems 499, 535 Lecce-Neville 499 Remy 535 Six-volt systems 499, 535 Six-colt system, North East 510 Slipping-clutch, regulation of generator by 50park, effect of compression on 199 Spark control devices 88 Spark plugs electrode arrangement 696 Spark control devices 88 Spark plugs electrode arrangement 696 plug threads 98 priming plugs 98 series plugs 97 summary 237 summary	Splitdorf	575		
Wagner Westinghouse Single-wire electrical system compared with two-wire diagrams for 321, 348, 383, 419, 475, 494 Single-wire systems North East 510 Remy 535 Six-volt systems 499, 535 Six-volt systems 499, 535 Sixer-out systems 499, 535 Sixer-out system, North East 510 Remy 535 Sixer-out system, North East 510 Spark, effect of compression on 199 Spark, control devices 88 Spark control devices 88 Spark control devices 88 Spark control devices 89 Spark control devices 89 Spark plugs electrode arrangement 96 Electrode arrangement 96 Electrode arrangement 97 Indiamental requisite 95 Ingle wire electrical system compared with two-wire diapetic in the stating and lighting developments, effect on ignition 123 Starting and lighting developments, effect on ignition 513 Starting and lighting storage batteries 661 Care of battery 661, 670 Starting and lighting developments, effect on ignition 123 Starting and lighting developments, effect on ignition 513 Starting and lighting developments, effect on ignition 713 Starting and lighting developments, effect on ignition 513 Starting and lighting developments, effect on ignition 123 A. C. rectifiers 661 A. C. rectifiers 671 adding acid 671 adding developments, effect on ignition 123 adding distilled water 670 care of battery 670 adding distilled water 670 galaxing specific gravity 670 care of battery 670 adding distilled water 670 adding distilled water 670 sandardization of electrical equipments, effect on igniti	U. S. L.	583		
Single-wire electrical system compared with two-wire diagrams for 321, 348, 383, 419, 475, 494  Single-wire systems North East 510 Remy 535 Simms-Huff 565 Westinghouse 623, 627 Six-volt systems 499, 535 A. C. rectifiers 711 Adding acid 671 A. C. rectifiers 711 Adding distilled water 670 adding distilled water 670 adjusting specific gravity 676 care of battery in winter 71 care of battery in winter 71 care of battery in winter 71 care of battery 689 charging in series for economy 710 cleaning repair parts 727 detecting deranged cells 687 care of battery 689 charging in series for economy 710 cleaning battery 689 charging in series for economy 710 gassing magnetic plugs 97 magnetic plugs 98 park timing 129 advance and retard automatically timed systems effect of irregular sparking 129 methods of charging order 143 replacing jar restoring sulphated battery 691 morthods of charging in rectart of the damage 688 feed burning 699 methods of charging in replacing jar restoring sulphated battery 691 morthod core farging in replacing jar restoring sulphated battery 692 coverhauling battery 693 methods of charging in replacing jar restoring sulphated battery 693 coverhauling battery 693 coverhauling battery 694 coverhauling battery 695 c	Wagner	599		
Ford magneto   124   289   289   289   289   289   31, 348, 383, 419, 475, 494   340   3	Westinghouse	623		
pared with two-wire diagrams for 321, 348, 383, 419, 475, 494  Single-wire systems North East 510 Remy 535 Westinghouse 623, 627 Six-volt systems 499, 535 Lecce-Neville 499 Alexander and lighting storage batteries 661, 670 A. C. rectifiers 711 adding acid 671 adding aci	Single-wire electrical system co	m-		
Single-wire systems North East Sinma-Huff Sinws-Huff Six-volt systems Six-volt systems Accessively learned by Six-volt systems Six-volt systems Leece-Neville Remy Six-volt systems Leece-Neville Remy Six-volt systems Leece-Neville Remy Six-volt system, North East Slipping-clutch, regulation of generator by Solenoids Spark, effect of compression on 199 Spark control devices Spark plugs cleetrode arrangement plugs cleetrode arrangement plugs priming plugs series plugs priming plugs series plugs summary Spark timing Leece-Neville Sixtens Starting and lighting development, effect on ignition Starting and lighting storage batteries Care of battery A. C. rectifiers 711 adding acid 671 adding distilled water 670 adjusting specific gravity 676 care of battery in winter care of battery early form outside source charging from outside source charging in series for economy 710 cleaning battery 689 cleaning repair parts detecting deranged cells 687 equalizing charges necessary 709 gassing 679 higher charge needed in cold weather 681 weather 681 weather 682 683 how to take readings 684 how to take readings 685 how to take readings 686 686 688 priming lips 129 meter tests 688 liphing developments, effect on ignition 173 Starting and lighting storage batteries care of battery 681 671 adding acid 672 care of battery 676 care of battery 670 adding acid 671 adding acid 671 adding distilled water 670 adjusting specific gravity 676 care of battery 670 adjusting specific gravity 676 care of battery 670 adding distilled water 670 adjusting specific gravity 676 care of battery 671 adding distilled water 670 adjusting specific gravity 689 clean				
Single-wire systems North East Simms-Huff Six-volt systems Six-volt s	diagrams for			
North East 510 Remy 535 Starting and lighting storage batteries 661 Westinghouse 623, 627 care of battery 661, 670 Six-volt systems 499, 535 A. C. rectifiers 711 Leece-Neville 499 adding acid 671 Remy 535 adding distilled water 670 Sixteon-volt system, North East 510 adjusting specific gravity 676 Slipping-clutch, regulation of generator by 281 charging from outside source reator by 281 charging in series for economy 710 Spark, effect of compression on 199 cleaning battery 689 Spark plugs 285 cleaning repair parts 727 Spark plugs 286 cleating dearnged cells 687 equalizing charges necessary 709 fundamental requisite 95 gassing 679 higher charge needed in cold plug threads 98 weather 681 priming plugs 98 how to take readings 687 series plugs 97 hydrometer 671 summary 237 installing new battery 705 waterproof plugs 98 internal damage 688 park timing 129 joint hydrometer and voltady advance and retard 129 methods of charging 710 effect of irregular sparking 129 methods of charging 710 overhauling battery 693 firing order 143 replacing sulphated battery 684		175, 494		
Remy Simms-Huff 565 Westinghouse 623, 627 Six-volt systems 499, 535 Leece-Neville 499 Remy 535 Remy 535 Leece-Neville 499 Remy 535 Remy 535 Remy 535 A. C. rectifiers 711 A. C. rectifiers 711 A. C. rectifiers 711 A. C. rectifiers 711 Adding acid 671 adding distilled water 670 adjusting specific gravity 676 care of battery in winter 71 care of battery in winter 670 adjusting specific gravity 676 care of battery in winter 71 care of battery in winter 71 care of battery in winter 71 care of battery in winter 670 adjusting specific gravity 676 care of battery in winter 71 care of battery in winter 71 care of battery in winter 71 care of battery in winter 670 adjusting specific gravity 676 care of battery in winter 71 care of battery in winter 71 care of battery in winter 670 adjusting specific gravity 676 care of battery in winter 670 adjusting specific gravity 676 care of battery in winter 71 care of battery in winter 670 adjusting specific gravity 676 care of battery in winter 71 care of battery in winter 670 adjusting specific gravity 676 care of battery in winter 670 adjusting specific gravity 676 care of battery in winter 71 care of battery in winter 670 adjusting specific gravity 676 care of battery in winter 670 adjusting specific gravity 676 care of battery in winter 670 adjusting specific gravity 676 care of battery in winter 670 adjusting specific gravity 676 care of battery in winter 71 care of battery in winter 670 adjusting specific gravity 676 care of battery in winter 670 care of battery in winter 670 care of battery in winter 670 adjusting specific gravity 676 care of battery in winter 670 care of	Single-wire systems		Starting and lighting develop	p-
Simms-Huff Westinghouse 623, 627 Six-volt systems 499, 535 Leece-Neville 499 A. C. rectifiers 711 Leece-Neville 499 adding acid 671 Remy 535 Sixteen-volt system, North East Site adding distilled water 670 Sixteen-volt system, North East Site adding distilled water 671 adding distilled water 672 adjusting specific gravity 673 Sixteen-volt system, North East Site adding distilled water 674 adding distilled water 675 adding distilled water 676 A. C. rectifiers 711 adding acid 671 adding distilled water 670 adjusting specific gravity 676 care of battery in winter 71 care of battery in winter 71 care of battery in winter 72 charging from outside source 747 charging in series for economy 740 cleaning battery 689 cleating deranged cells 687 equalizing charges necessary 749 gassing 679 higher charge needed in cold weather 681 priming plugs 98 how to take readings 687 summary 98 park timing 129 advance and retard 129 firing order 143 replacing jar 140 restoring sulphated battery 684  186 681 reries 681 reries 681 reries 682 682 682 683 684 685 686 686 686 686 687 688 688 688 688 688	North East	510	ments, effect on igniti	on 173
Simms-Huff Westinghouse 623, 627 Care of battery 661, 670 Six-volt systems 1499, 535 Leece-Neville 1499 Sixteen-volt system, North East Slipping-clutch, regulation of generator by 281 Spark, effect of compression on Spark, effect of compression on Spark plugs cleetrode arrangement spark plugs cleetrode arrangement spark plugs specific gravity 670 Spark plugs cleetrode arrangement spark plugs specific gravity 670 Spark plugs spark control devices Spark plugs cleetrode arrangement spark plugs specific gravity 670 Spark plugs spark control devices Spark plugs specific gravity 670 care of battery in winter 707 care of battery in winter 707 charging from outside source 708 charging in series for economy 710 cleaning battery 689 cleaning repair parts 727 detecting deranged cells 687 equalizing charges necessary 709 gassing 679 higher charge needed in cold weather 681 weather 681 summary 98 weather 681 weather 681 summary 98 priming plugs 98 how to take readings 687 syndrometer 671 summary 98 spark timing 129 joint hydrometer 688 automatically timed systems 138 lead burning 129 sperious deal damage 129 methods of charging 710 motor-generator 711 motor-generator 711 motor-generator 711 motor-generator 711 replacing jar 690 restoring sulphated battery 684	Remy	535	Starting and lighting storage be	at-
Six-volt systems 499, 535 Leece-Neville 499 Remy 535 Sixteen-volt system, North East 510 Slipping-clutch, regulation of generator by 281 Spark, effect of compression on 199 Spark control devices 88 Spark plugs 495 Clectrode arrangement 96 Indiamental requisite 95 Ingular threads 98 Ingular thread		565	teries	661
Six-volt systems 499, 535 Leece-Neville 499 adding acid 671 Remy 535 adding distilled water 670 Sixteen-volt system, North East 510 adjusting specific gravity 676 Slipping-clutch, regulation of generator by 281 charging in series for economy 710 Spark, effect of compression on 199 cleaning battery 689 Spark control devices 88 Spark plugs detecting deranged cells 687 electrode arrangement 96 electrode arrangement 95 magnetic plugs 97 higher charge needed in cold plug threads 98 weather 681 priming plugs 98 how to take readings 687 series plugs 97 hydrometer 671 summary 237 installing new battery 705 waterproof plugs 98 Spark timing 129 advance and retard 129 meter tests 688 automatically timed systems 138 effect of irregular sparking 129 firing order 143 replacing sulphated battery 684 firing order 143 replacing sulphated battery 684 firing order 1440 restoring sulphated battery 684	Westinghouse	523, 627	care of battery 6	61, 670
Lecce-Neville Remy Sixteen-volt system, North East Slipping-clutch, regulation of generator by Solenoids Spark, effect of compression on Spark control devices Spark plugs cleetrode arrangement fundamental requisite priming plugs Series plugs Series plugs Series plugs Series plugs Spark timing Spark timi				
Remy Sixteen-volt system, North East Slipping-clutch, regulation of generator by Solenoids Spark, effect of compression on Spark control devices Spark plugs cleetrode arrangement fundamental requisite priming plugs spring plugs series plugs series plugs series plugs series plugs Spark timing summary series plugs Spark timing advance and retard advance and retard summarically timed systems effect of irregular sparking Eisemann centrifugal-governor type firing order Herz ball-governor type  130  adding distilled water adjusting specific gravity care of battery in winter charging from outside source charging from outside source charging from outside source charging from outside source charging in series for economy 710 cleaning battery 689 detecting deranged cells equalizing charges necessary 709 gassing 689 weather 681 weather 681 weather 681 summary installing new battery 705 installing new battery 705 meter tests 688 lead burning 699 methods of charging 710 motor-generator 711 motor-generator 711 motor-generator 711 motor-generator 711 replacing jar 690 replacing jar 690 replacing jar 690 replacing jar 690 restoring sulphated battery 684			adding acid	671
Sixteen-volt system, North East Slipping-clutch, regulation of generator by Solenoids Spark, effect of compression on Spark control devices Spark plugs cleetrode arrangement spring plugs priming plugs series plugs Spark timing advance and retard advance and retard advance and retard sizemann centrifugal-governor type firing order Solenoids Spark, effect of compression on Spark control devices Series plugs Spark plugs Spark control devices Series plugs Spark control devices Sea detecting deranged cells Sequalizing charges necessary Top gassing Spassing Spassi		535		670
Slipping-clutch, regulation of generator by 281 charging from outside source 707 Solenoids 25 charging in series for economy 710 Spark, effect of compression on 199 cleaning battery 689 Spark control devices 88 cleaning repair parts 727 detecting deranged cells 687 electrode arrangement 96 equalizing charges necessary 709 magnetic plugs 97 magnetic plugs 98 higher charge needed in cold plug threads 98 weather 681 priming plugs 98 how to take readings 687 series plugs 97 hydrometer 671 summary 237 installing new battery 705 waterproof plugs 98 internal damage 686 summary 237 installing new battery 705 internal damage 686 summary 237 installing new battery 705 internal damage 686 automatically timed systems 138 lead burning 699 methods of charging 710 verhauling battery 693 firing order 143 replacing jar 690 Herz ball-governor type 140 restoring sulphated battery 684		st 510		676
crator by   281   charging from outside source   707				71
Solenoids 25 charging in series for economy 710 Spark, effect of compression on 199 cleaning battery 689 Spark control devices 88 cleaning repair parts 727 detecting deranged cells 687 electrode arrangement 96 equalizing charges necessary 709 fundamental requisite 95 gassing 679 higher charge needed in cold plug threads 98 weather 681 priming plugs 98 how to take readings 687 series plugs 97 hydrometer 671 summary 237 installing new battery 705 waterproof plugs 98 internal damage 686 Spark timing 129 joint hydrometer and voltadvance and retard 129 internal damage 686 automatically timed systems 138 lead burning 699 effect of irregular sparking 129 methods of charging 710 type 139 overhauling battery 693 firing order 143 replacing jar 690 Firing order 1440 restoring sulphated battery 684				e 707
Spark, effect of compression on 199 cleaning battery 58park control devices 88 cleaning repair parts 727 Spark plugs detecting deranged cells 687 fundamental requisite 95 gassing 7679 magnetic plugs 97 higher charge needed in cold plug threads 98 weather 681 priming plugs 98 how to take readings 687 series plugs 97 hydrometer 671 summary 237 installing new battery 705 waterproof plugs 98 internal damage 686 Spark timing 129 joint hydrometer and voltadvance and retard 129 meter tests 688 automatically timed systems 138 lead burning 699 effect of irregular sparking 129 methods of charging 710 Eisemann centrifugal-governor type 139 overhauling battery 693 firing order 143 replacing jar 690 Herz ball-governor type 140 restoring sulphated battery 684		$^{-25}$		
Spark control devices         88         cleaning repair parts         727           Spark plugs         detecting deranged cells         687           electrode arrangement         96         equalizing charges necessary         709           fundamental requisite         95         gassing         679           magnetic plugs         97         higher charge neceded in cold         681           priming plugs         98         how to take readings         687           series plugs         97         hydrometer         671           summary         237         installing new battery         705           waterproof plugs         98         internal damage         686           Spark timing         129         joint hydrometer and voltand voltand voltand tically timed systems         688           advance and retard         129         meter tests         688           automatically timed systems         138         lead burning         699           effect of irregular sparking         129         methods of charging         710           Eisemann centrifugal-governor         type         139         overhauling battery         693           firing order         143         replacing jar         690		199		
Spark plugs electrode arrangement 96 equalizing charges necessary 709 fundamental requisite 95 gassing 679 magnetic plugs 97 higher charge needed in cold plug threads 98 weather 681 priming plugs 98 how to take readings 687 series plugs 97 hydrometer 671 summary 237 installing new battery 705 waterproof plugs 98 internal damage 686 spark timing 129 methods of charging 699 effect of irregular sparking 129 methods of charging 710 Eisemann centrifugal-governor type 139 Herz ball-governor type 140 restoring sulphated battery 684				727
electrode arrangement   96   equalizing charges necessary   709   fundamental requisite   95   gassing   679   magnetic plugs   97   higher charge needed in cold   plug threads   98   weather   681   priming plugs   98   how to take readings   687   series plugs   97   hydrometer   671   summary   237   installing new battery   705   waterproof plugs   98   internal damage   686   Spark timing   129   joint hydrometer and voltadvance and retard   129   meter tests   688   automatically timed systems   138   lead burning   699   effect of irregular sparking   129   methods of charging   710   Eisemann centrifugal-governor   type   130   overhauling battery   693   firing order   143   replacing jar   690   restoring sulphated battery   684				
fundamental requisite 95 gassing 679 magnetic plugs 97 higher charge needed in cold plug threads 98 weather 681 priming plugs 98 how to take readings 687 series plugs 97 hydrometer 671 summary 237 installing new battery 705 waterproof plugs 98 internal damage 688 Spark timing 129 joint hydrometer and voltady automatically timed systems 138 lead burning 699 effect of irregular sparking 129 methods of charging 710 Eisemann centrifugal-governor type 139 overhauling battery 693 firing order 143 replacing jar 690 Herz ball-governor type 140 restoring sulphated battery 684		96		
magnetic plugs 97 higher charge needed in cold weather 681 weather 681 priming plugs 98 how to take readings 687 series plugs 97 hydrometer 671 summary 237 installing new battery 705 waterproof plugs 98 internal damage 686 Spark timing 129 joint hydrometer and voltadvance and retard 129 meter tests 688 automatically timed systems 138 lead burning 699 effect of irregular sparking 129 methods of charging 710 Eisemann centrifugal-governor type 139 overhauling battery 693 firing order 143 replacing jar 690 Herz ball-governor type 140 restoring sulphated battery 684				
plug threads   98   weather   681				
priming plugs 98 how to take readings 687 series plugs 97 hydrometer 671 summary 237 installing new battery 705 internal damage 686 spark timing 129 internal damage 686 automatically timed systems 138 lead burning 699 effect of irregular sparking 129 methods of charging 710 Eisemann centrifugal-governor type 139 overhauling battery 693 firing order 143 replacing jar 690 Herz ball-governor type 140 restoring sulphated battery 684				
series plugs 97 hydrometer 671 summary 237 installing new battery 705 waterproof plugs 98 internal damage 686 Spark timing 129 internal damage 686 automatically timed systems 138 lead burning 699 effect of irregular sparking 129 methods of charging 710 Eisemann centrifugal-governor type 139 overhauling battery 693 firing order 143 replacing jar 690 Herz ball-governor type 140 restoring sulphated battery 684				
summary         237         installing new battery         705           waterproof plugs         98         internal damage         686           Spark timing         129         joint hydrometer and voltand voltand treated         688           advance and retard         129         meter tests         688           automatically timed systems         138         lead burning         699           effect of irregular sparking         129         methods of charging         710           Eisemann centrifugal-governor type         139         overhauling battery         693           firing order         143         replacing jar         690           Herz ball-governor type         140         restoring sulphated battery         684				
waterproof plugs         98         internal damage         686           Spark timing         129         joint hydrometer and voltage in the voltage of the point hydrometer and voltage in the voltage of the point hydrometer and voltage in the voltage of the voltage in t				
Spark timing 129 joint hydrometer and voltadvance and retard 129 meter tests 688 automatically timed systems 138 lead burning 609 effect of irregular sparking 129 methods of charging 710 Eisemann centrifugal-governor type 139 overhauling battery 693 firing order 143 replacing jar 690 Herz ball-governor type 140 restoring sulphated battery 684				
advance and retard         129         meter tests         688           automatically timed systems         138         lead burning         699           effect of irregular sparking         129         methods of charging         710           Eisemann centrifugal-governor type         139         overhauling battery         693           firing order         143         replacing jar         690           Herz ball-governor type         140         restoring sulphated battery         684				
automatically timed systems effect of irregular sparking 129 methods of charging 710 Eisemann centrifugal-governor type 139 overhauling battery 693 firing order 143 replacing jar 690 Herz ball-governor type 140 restoring sulphated battery 684			•	
effect of irregular sparking 129 methods of charging 710 Eisemann centrifugal-governor type 139 overhauling battery 693 firing order 143 replacing jar 690 Herz ball-governor type 140 restoring sulphated battery 684				
Eisemann centrifugal-governor type 139 overhauling battery 693 firing order 143 replacing jar 690 Herz ball-governor type 140 restoring sulphated battery 684				
type 139 overhauling battery 693 firing order 143 replacing jar 690 Herz ball-governor type 140 restoring sulphated battery 684			0, 0	
firing order 143 replacing jar 690 Herz ball-governor type 140 restoring sulphated battery 684				
Herz ball-governor type 140 restoring sulphated battery 684				
The state of the s				
ignition setting point 111 special gravity too night 000		7.7		
	ignition secting point		Alexande Maritin too mgn	300

Note: -- For page numbers see foot of pages.

ľ

	Page		age
Starting and lighting (continued)		Storage battery in Gray and Davis	~=~
care of battery		system for Ford cars	652
starting harder in cold	713	Storage battery jar, replacing	690
weather	713 705	Storage cells	87
storing battery	682	Storing battery	705
sulphating temperature variations in	002	Studebaker, firing order and ignition advance	160
voltage	688	Stutz, firing order and ignition ad-	100
to test rate of charge	719	vance	161
to test rate of discharge	716	Sulphating of storage battery 682,	
voltage tests	723	extra time necessary for charging	
importance of battery	661	restoring sulphated battery	684
principles and construction	662	summary of instructions	782
action of cell on charge	665	Switch tests for North East system	
action of cell on discharge	666	ground tests	523
capacity of battery	667	mechanical and electrical char-	
construction details	669	acteristics	526
Edison cell not available	670	operation test	523
function of storage battery	662	replacing Dodge chain	526
parts of cell	663	Switches, summary of instructions	
specific gravity	665	247,	766
Starting motor		Switches in starting and lighting	
clutches	300	systems	304
design requirements	291	electrically operated	307
driving connections	298	miscellaneous starting	306
Ford system 640,		Westinghouse starting	305
installation	295	Symbols, significance of	318
Leece-Neville system	500	general and special usage	321
motor windings and poles	294	<b>m</b>	
Remy system	543	T	
Splitdorf system	579	Tables	
summary of instructions	749 294	American wire gage (B.&S.)	17
voltage	294 609	carrying capacity of wires	20
Wagner system	634	characteristics of North East	
Westinghouse system electromagnetic switch	639	starting and lighting ap-	524
magnetic engaging type	634	paratus test chart for Gray and Davis	J24
variations	634	generators	485
var arcions	1709	generators	200

	Page	
Testing instruments, special	334	U
Testing rate of charge	719	U. S. L. System
Testing rate of discharge	715	generator-starting motor
Thermostatic switch in Remy		instructions
regulation	536	instruments and protective de
Third brush, adjusting	425	vices
Time factor of induction coil, ad-	100	Nelson system
justing for	130	regulation
·····	258	twelve-volt system
Timer with resistance unit with		fuse blocks
Delco system	187	starting switch
Transformer	101	variations
Transformer principle	27	wiring diagrams "Unisparker," operation of
Transmission and regulation de-		Unisparker, operation of
vices	296	v
automatic engagement	300	Velie, firing order and ignition ad
back-kick releases	303	,
elutches	301	Vance Vibrator soils summers
driving connections	299	Vibrator coils, summary Vibrators
electric horns	310	
fuses	308	complication of multi-vibrator
installation	296	master vibrator
switches	304	necessity for
Tungsten filaments for incandes-		non-vibrator coil
cent lamps	312	Voltage Voltage drop
	575	effect on lights
Splitdorf	583	Voltage readings, how to take
U. S. L.		Voltage and spark control devices
Twelve-volt systems 510, 565, 599,		changes in ignition methods
North East	510	coils and vibrators
Simms-Huff	565	condenser
Wagner	599	contact makers or timers
Westinghouse	623	distributor
Twenty-four stwelve-volt system.		hydraulic analogy in ignition
U. S. L.	583	system
Twenty-four volt system, North		spark plugs
Fast 535.	510	Voltage standards
	275	Voltage of starting systems
Two-unit electrical systems Auto-Lite	337	Voltage tests
Bijur	354	335, 686, 688, 723, 725, 780
Bosch-Rushmore	379	summary of instructions temperature variations in
Deleo	115	Voltmeter tests
diagrams for	325	686, 688, 723, 725, 780
Disco	161	000, 000, 120, 120, 150
I'	461	W.
Dyneto Grav and Davis	168	
	490	Wagner system single-unit
Heinze-Springfield	499	
Leece-Neville	535	control; transmission
Remy	609	dynamotor instructions
Wagner Two who systems	1877	regulation
Two-wire systems 499, 510, 575, 583,	500	
	199	wiring diagram two-unit
Loece-Neville	510	control
North Elast	575	
Splitdorf	583	general characteristics
U. S. L.	599	generator instructions
Wagner		instructions
Note of repair cambers see foot of pones.		


•	Page	Page
Wagner system (continued)	_	Wiring connections of ignition
two-unit		systems 108
starting motor	609	Wiring diagrams of electrical
wiring diagram	610	equipment 122, 321
Waterproof plugs	98	Auto-Lite 347
Weak magnets	197	Bijur 357
Westcott, firing order and ignitio	n	Bosch-Rushmore 382
advance	161	Delco 405, 419
Westinghouse ignition unit	175	Dyneto 466
Westinghouse starting switch	305	Gray and Davis 475
Westinghouse system	623	Heinze-Springfield 494
double-unit	627	Leece-Neville 501
battery cut-out	630	North East 512
generators	627	Remy 544
instructions	639	National 548
regulation	627	Oakland 548
starting motors	634	Reo 548
wiring diagram	630	Velie 544
single-unit	623	significance of symbols 318
control	623	Simms-Huff 570
dynamotor	623	single-wire system 321
instructions	623	Splitdorf 575
regulation	623	two-wire system 325
wiring diagram	623	U. S. L. 586
Willys-Knight, firing order and	d	Wagner 599, 610
ignition advance	162	Westinghouse 623, 630
Winter care of storage battery 68	1, 713	Wiring in electrical equipment 162
higher charge needed	681	calculating size of cable 165
starting harder	714	effect on lights 165
Winton	162	importance of good connections 166
Wiring, testing	429	importance of voltage drop 164
locating breaks in wires	432	necessity for high-tension cables 162
locating grounds	429	summary of instructions 752

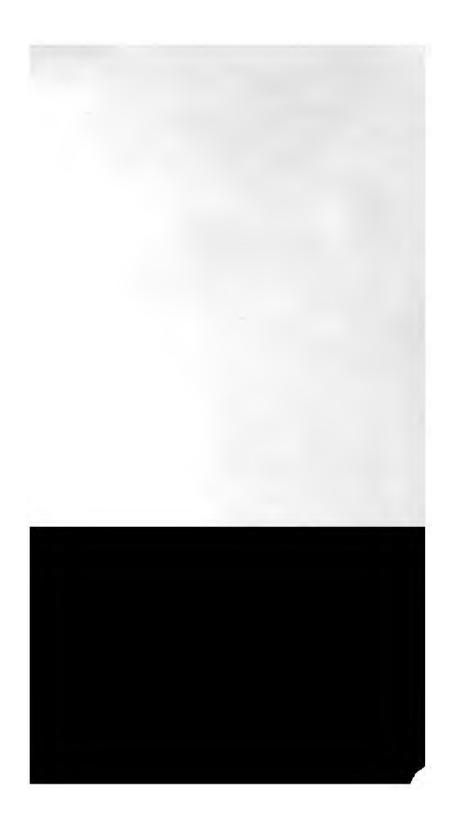Note.—For page numbers see foot of pages.









## To renew the charge, book must be brought to the desk.

. IE Ju

3 9015 00295 1633

